

5/11/13

Lec 39

LTV Model

$$\varphi(t) = \frac{1}{R_{max}} \left[\frac{C_0}{2} \int_{-\infty}^t i(\tau) d\tau + \sum_{n=1}^{\infty} C_n \int_{-\infty}^t i(\tau) \cos(n\omega_0 \tau) d\tau \right]$$

$$i(t) = I_m \cos((m\omega_0 + \Delta\omega)t) \quad \text{noise current @ } (m\omega_0 + \Delta\omega)$$

$$\varphi(t) \approx \frac{I_m C_m \sin \Delta\omega t}{2V_{max} \Delta\omega}$$

$v_o(t) = A \cos(\omega_0 t + \varphi(t))$ phase & voltage conversion

disturbance $\varphi(t) = v_n \cos \omega_m t$

$$v_o(t) = A \cos \omega_0 t + \frac{A v_n K_{v\phi}}{2\omega_m} \left[\cos((\omega_0 + \omega_m)t) \right]$$

$$P_{SB}(\Delta\omega) \approx 10 \log \left[\frac{(\overline{i_n^2}/\Delta f) \cdot \sum_{m=0}^{\infty} C_m^2}{4q^2 \Delta\omega^2} \right]$$

when noise is white

$$\sum C_m^2 = 2 \Gamma_{rms}^2$$

$$L(\Delta\omega) = 10 \log \left[\frac{(\overline{i_n^2}/\Delta f) \cdot \Gamma_{rms}^2}{2q_{max}^2 \cdot \Delta\omega^2} \right]$$

Flicker Noise

$$\overline{i_n^2}_{1/f} = \overline{i_n^2} \cdot \frac{\omega_{1/f}}{\Delta\omega} \text{ is } 1/f \text{ noise region}$$

$$L(\Delta\omega) = 10 \log \left[\frac{(\overline{i_n^2}/\Delta f) \cdot C_0^2}{8q_{max}^2 \Delta\omega^2} \cdot \frac{\omega_{1/f}}{\Delta\omega} \right]$$

$$\Delta\omega_{1/f}^3 = \omega_{1/f} \cdot \frac{C_0^2}{4\Gamma_{rms}^2} = \omega_{1/f} \left(\frac{\Gamma_{dc}}{\Gamma_{rms}} \right)^2$$

1/f noise can be reduced by reducing Γ_{dc}

* Flat noise region due to noise of buffers & measurement NF

VCO Design

1) ~~$f_0 = \frac{1}{2\pi\sqrt{LC}}$~~

2) R_p of tank - decides amplitude

R_p : assume due to L alone

$$R_p = Q \cdot \omega_0 L$$

* To a first order $R_p \ll L$


* to get max amplitude (given I_T), we need to maximise R_p

⇒ maximise L

⇒ C is minimum (low tuning range)



* Design CC pair, say startup gain = 3

* Replace C with varactors

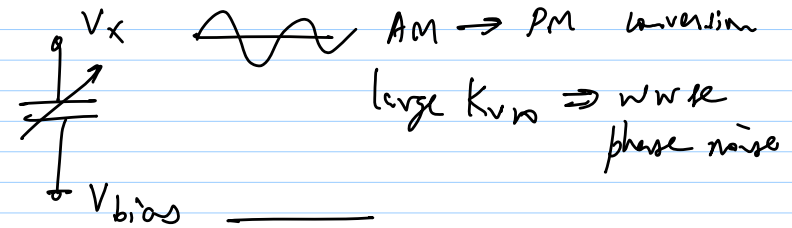

$$C = C_{var} + C_{sw}$$

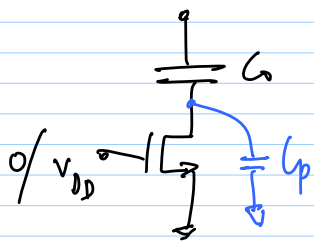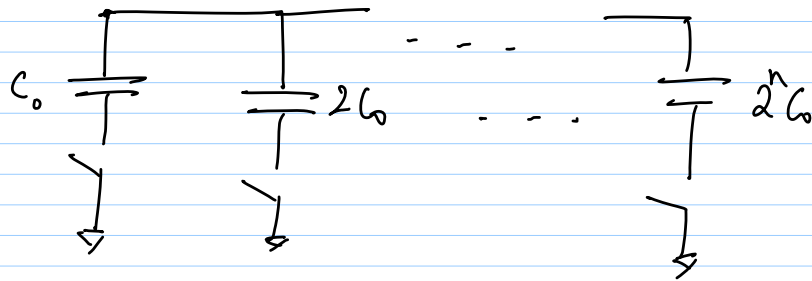\swarrow \leftarrow "0" - C_{max}
 $K_{vm} \approx 50 - 500 \text{ Hz/V}$



$$C_{min} = \frac{C_0 C_p}{C_0 + C_p}$$

$$C_{max} = C_0$$

trade-off between Q & $\frac{C_{max}}{C_{min}}$

