
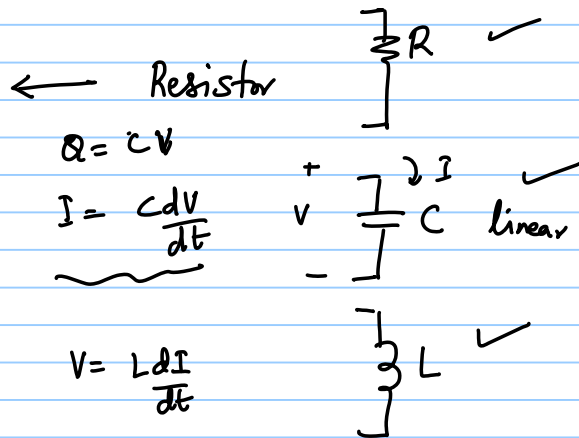
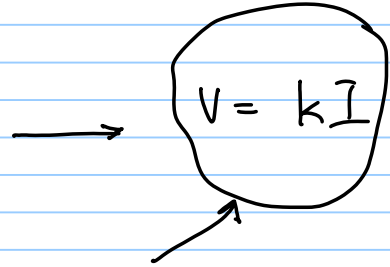
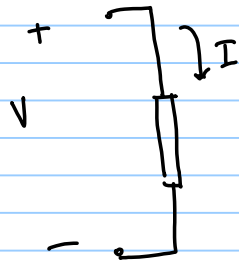


8/8/17

ANALOG ELECTRONIC CIRCUITS

"Microelectronic Circuits"
Sedra & Smith

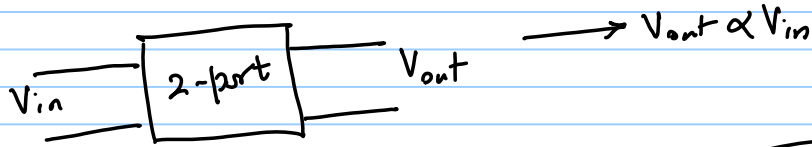

$$Y = f(X)$$

$$\left. \begin{matrix} X_1 \rightarrow Y_1 \\ X_2 \rightarrow Y_2 \end{matrix} \right\}$$

$$X_1 + X_2 \rightarrow Y_1 + Y_2$$

$$aX_1 + bX_2 \rightarrow aY_1 + bY_2$$

"Superposition"

$$Y = X + 2$$


"Not linear"

$$\left. \begin{array}{l} X_1 = 0 \rightarrow Y_1 = 2 \\ X_2 = 1 \rightarrow Y_2 = 3 \end{array} \right\} \begin{array}{l} X_1 + X_2 \\ 1 \end{array} \rightarrow 3$$

For linearity: $X = 0 \Rightarrow Y = 0$

Non-linear 2-T element

pn junction diode

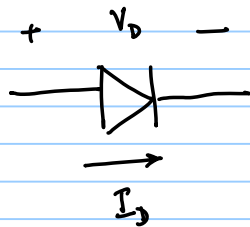

$$I_D = I_s \left[\exp\left(\frac{V_D}{V_t}\right) - 1 \right]$$

reverse saturation current


thermal voltage $V_t = \frac{kT}{q}$
 $\approx 25.9 \text{ mV @ RT}$

$$\approx I_s \exp\left(\frac{V_D}{V_t}\right) \text{ if } \exp\left(\frac{V_D}{V_t}\right) \gg 1$$





V across each element
 I through " "

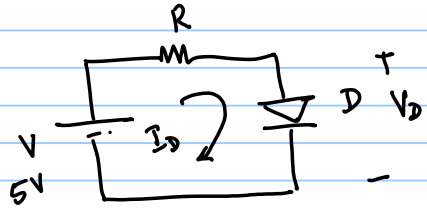KVL, KCL + element relationships } - solve



$$V = I_D R + V_D$$


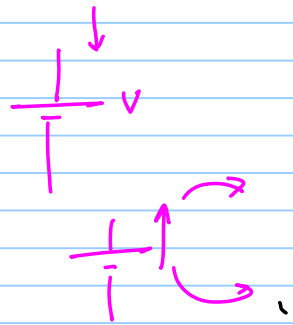
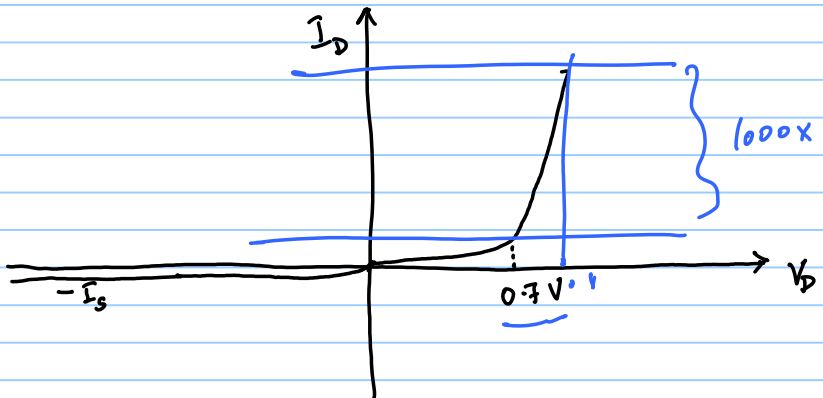
$$I_D = I_s \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right]$$




$$\frac{V - V_D}{R} = I_D = I_s \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right]$$

1) Iteration

2) Graphically

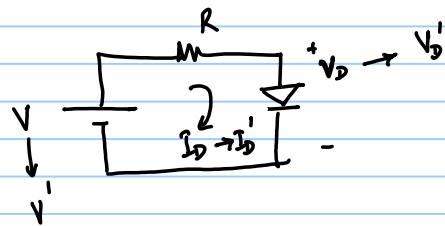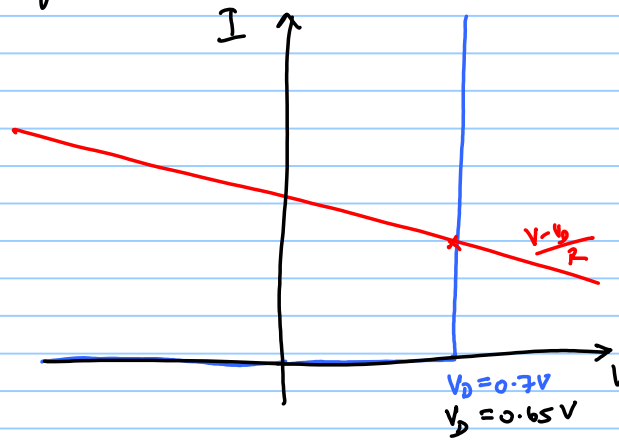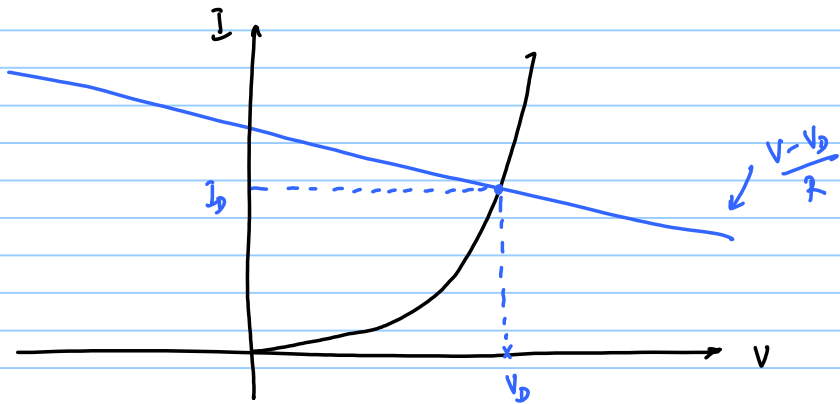

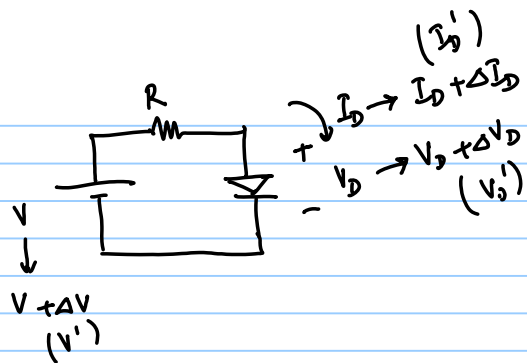

$$\frac{V - V_D}{R} = I_D = I_s \left[\exp\left(\frac{V_D}{V_t}\right) - 1 \right]$$

$$\frac{V' - V_D'}{R} = I_D' = I_s \left[\exp\left(\frac{V_D'}{V_t}\right) - 1 \right]$$

Taylor Series

$$y = f(x)$$

$$y_0 = f(x_0) \leftarrow \text{operating point}$$

$$y(x) = \sum_{n=0}^{\infty} \frac{f^{(n)}(x_0)}{n!} \cdot (x - x_0)^n \leftarrow$$

$$= f(x_0) + f'(x_0) \cdot (x - x_0) + \frac{f''(x_0)}{2} \cdot (x - x_0)^2 + \dots$$

$$x = x_0 + \Delta x$$

$$I_D' = I_D + \Delta I_D = I_s \left[\exp\left(\frac{V_D + \Delta V_D}{V_t}\right) - 1 \right]$$

$$= \underbrace{I_s \left[\exp\left(\frac{V_D}{V_t}\right) - 1 \right]}_{f(x_0)} + \frac{I_s}{V_t} \exp\left(\frac{V_D}{V_t}\right) \cdot \Delta V_D + \dots \left(\Delta V_D^2, \Delta V_D^3 \dots \right)$$

$\leftarrow f'(x_0) \cdot (x - x_0)$

$$\frac{(V + \Delta V) - (V_D + \Delta V_D)}{R} = I_D + \Delta I_D = I_s \left[\exp\left(\frac{V_D}{V_t}\right) - 1 \right] + \frac{I_s}{V_t} \exp\left(\frac{V_D}{V_t}\right) \cdot \Delta V_D$$


$$\frac{V - V_D}{R} + \frac{\Delta V - \Delta V_D}{R} = I_D + \Delta I_D = I_s \left[\exp\left(\frac{V_D}{V_t}\right) - 1 \right] + \frac{I_s}{V_t} \exp\left(\frac{V_D}{V_t}\right) \cdot \Delta V_D$$

$$\frac{\Delta V - \Delta V_D}{R} = \Delta I_D = \frac{I_D}{V_t} \cdot \Delta V_D$$



$$\approx \frac{I_D}{V_t}$$

$\Delta V, \Delta V_D, \Delta I_D \rightarrow$ increments
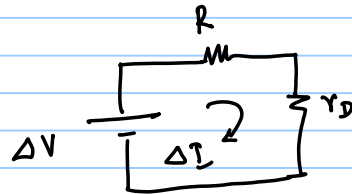
$$\frac{\Delta V_D}{\Delta I_D} = r_D = \frac{V_t}{I_D}$$



Incremental equivalent
circuit

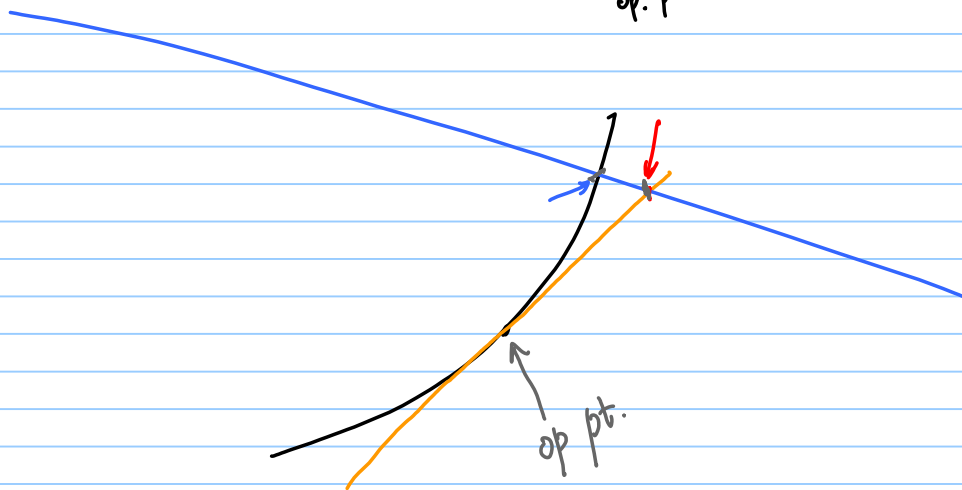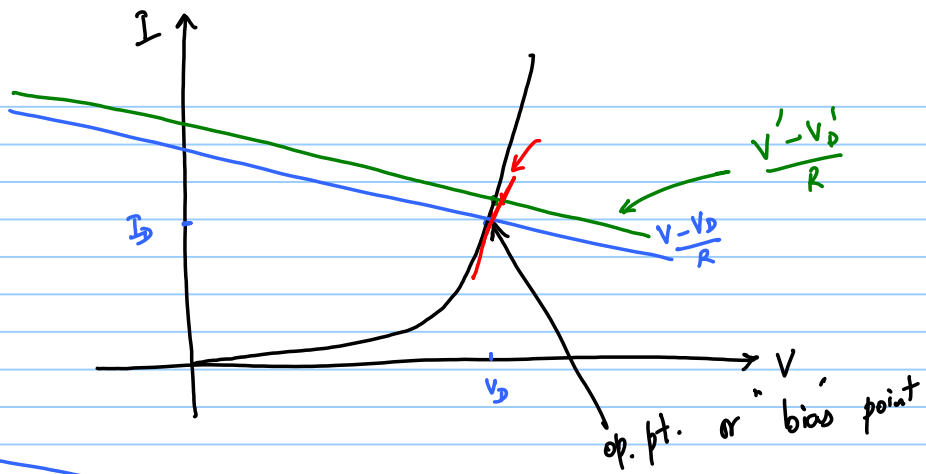


www.ee.iitm.ac.in/~vlsi/teaching/start.html



[/~negendra/Videolectures.doku](http://www.ee.iitm.ac.in/~negendra/Videolectures.doku)



10/8/17

lec 2

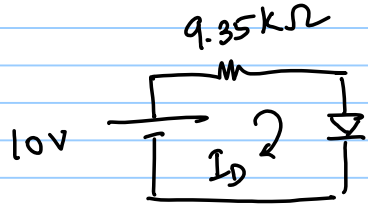

$$V_D = 0.65V$$

$$I_D = 1mA = \text{op pt. } I_D$$

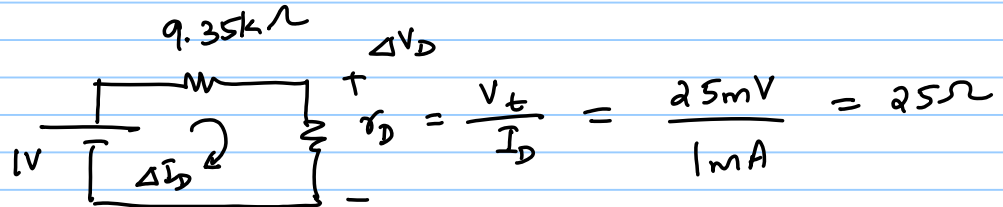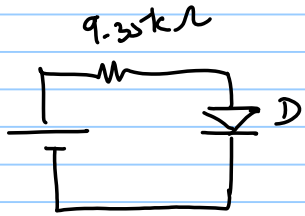

$$r_D = \frac{V_T}{I_D} = \frac{25mV}{1mA} = 25\Omega$$

$$\Delta I_D = \frac{1V}{9.35k + 25} = 107\mu A$$

$$\Delta V_D = \Delta I_D \cdot r_D = 2.7mV$$

$$V_D' = V_D + \Delta V_D = 0.65V + 2.7mV$$

$$I_D' = I_D + \Delta I_D = 1.107mA$$

op pt. \nearrow
 \nearrow incr.
 \rightarrow 9V

$$V_D'' = 0.65V - 2.7mV$$

$$I_D'' = 0.893mA$$

$$I_D' = I_s \left[\exp\left(\frac{V_D}{V_t}\right) - 1 \right]$$

$f(v)$

$f'(v)$

$f''(v)$

$$+ \frac{I_D}{V_t} \cdot \Delta V_D$$


$$+ \frac{1}{2} \cdot \frac{I_D}{V_t^2} \cdot \Delta V_D^2$$

$$\frac{\frac{I_D}{2 V_t^2} \cdot \Delta V_D^2}{\frac{I_D}{V_t} \Delta V_D} \ll 1$$

$\Delta V_D \ll 2 V_t$


$$2.7 \text{ mV} \ll 50 \text{ mV}$$



incremental (linear) approx. is valid.

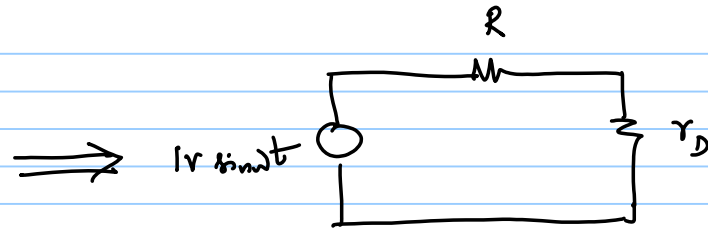


Small-signal
eq.ckt

Element	SS eq.
R	R
C	C
L	L
F.B.	$r = \frac{V_T}{I_D}$
R.B.	O.C.
$I = f(V)$	$\frac{1}{f'(V)}$
V	S.C.
I	O.C.

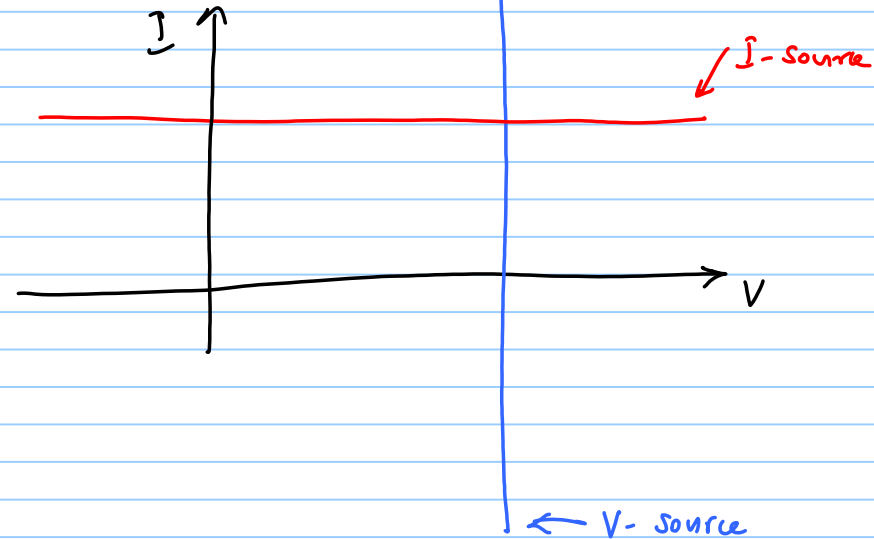

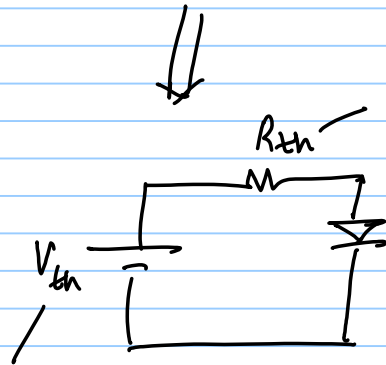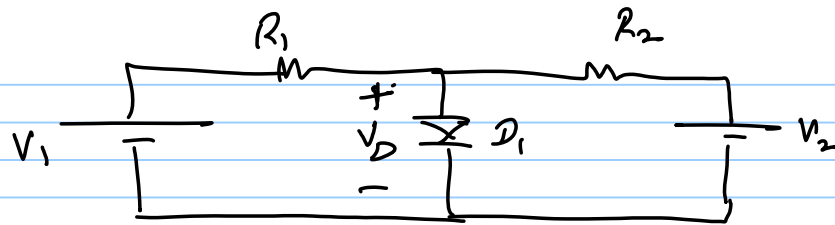

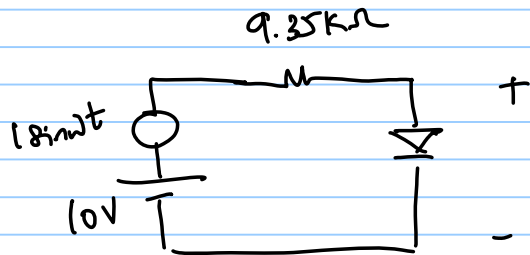
$$\frac{V_{th} - V_D}{R_{th}} = I_D = (\quad)$$



$$V_D = 0.65V, I_D = 1mA \Rightarrow r_D = 25\Omega$$

$$i_{in} \cdot R = v_d \Rightarrow v_d = \frac{r}{R+r} \cdot i_{in}$$

Operating
Quiescent
Bias point

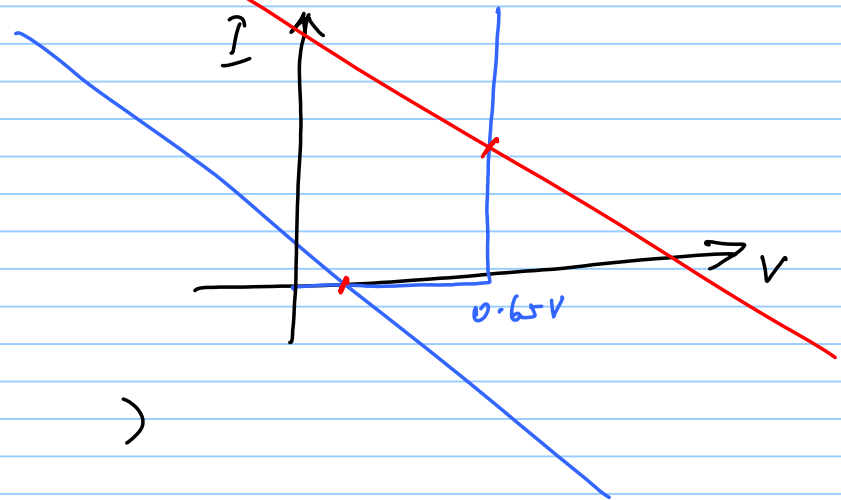


Transformer — Voltage gain ✓

Power gain ✗

Diode — Voltage gain possible if r is negative
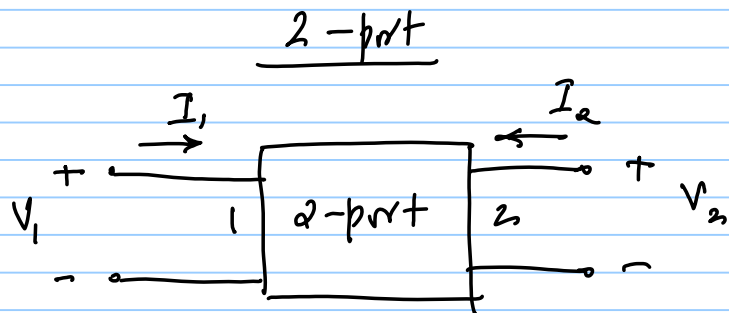
$$r = \frac{1}{f'(v)} \leftarrow \text{negative slope}$$



$[Z]$, $[Y]$, $[G]$, $[H]$, $[ABCD]$, $[A^T B^T \dots]$


$[S]$

$$\begin{aligned} I_1 &= Y_{11}V_1 + Y_{12}V_2 \\ I_2 &= Y_{21}V_1 + Y_{22}V_2 \end{aligned} \Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$[I] = [Y] \cdot [V]$$

17/8/17

Lec 3

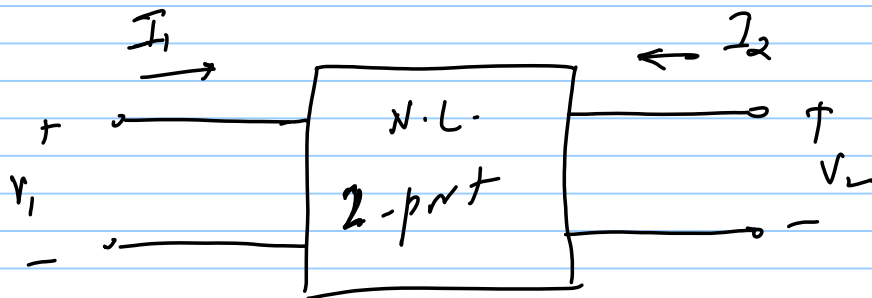

$$I_1 = f(v_1, v_2)$$

$$I_2 = g(v_1, v_2)$$

2-D Taylor Series

$$I_1 + \Delta i_1 = I_1' = f(v_1, v_2) \Big|_{op. pt.} + \frac{\partial f}{\partial v_1} \cdot \Delta v_1 + \frac{\partial f}{\partial v_2} \cdot \Delta v_2 + \dots$$

$$I_2 + \Delta i_2 = I_2' = g(v_1, v_2) \Big|_{op. pt.} + \frac{\partial g}{\partial v_1} \cdot \Delta v_1 + \frac{\partial g}{\partial v_2} \cdot \Delta v_2 + \dots$$

$$\Delta i_1 = \partial f / \partial v_1 \cdot \Delta v_1 + \frac{\partial f}{\partial v_2} \cdot \Delta v_2$$



$$\Delta i_2 = \partial g / \partial v_1 \cdot \Delta v_1 + \partial g / \partial v_2 \cdot \Delta v_2$$

$$i_1 = \partial f / \partial v_1 \cdot v_1 + \partial f / \partial v_2 \cdot v_2$$

$$i_2 = \partial g / \partial v_1 \cdot v_1 + \partial g / \partial v_2 \cdot v_2$$




$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} \partial f / \partial v_1 & \partial f / \partial v_2 \\ \partial g / \partial v_1 & \partial g / \partial v_2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$
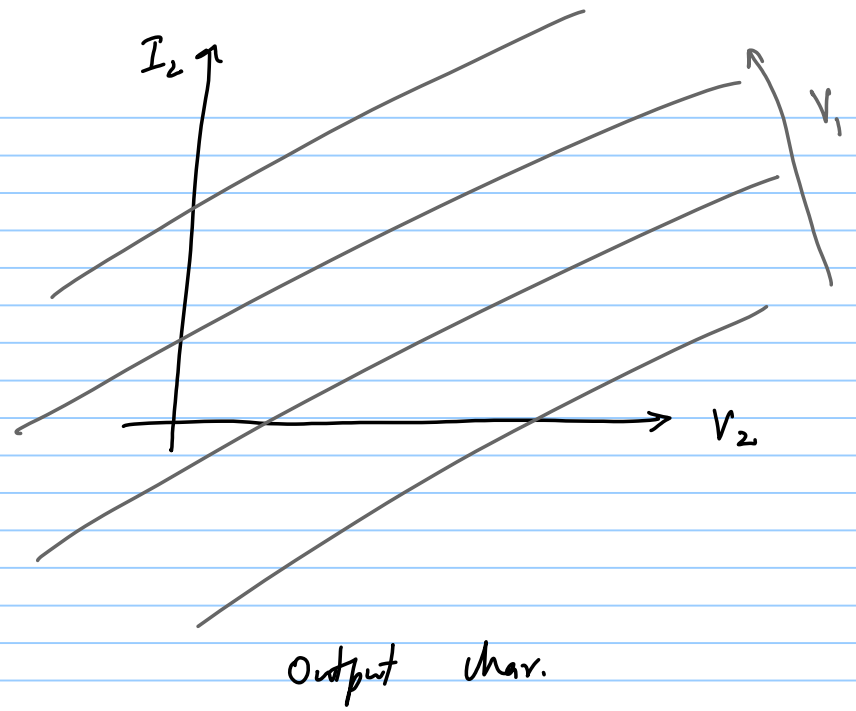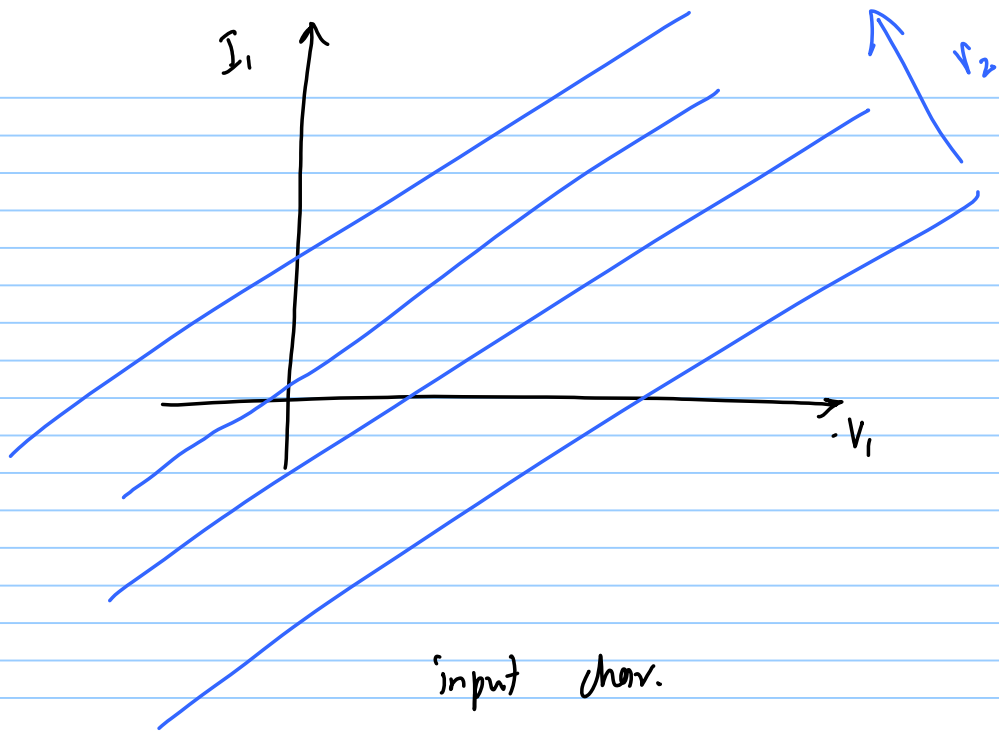
$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \underbrace{\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$




Amplifier

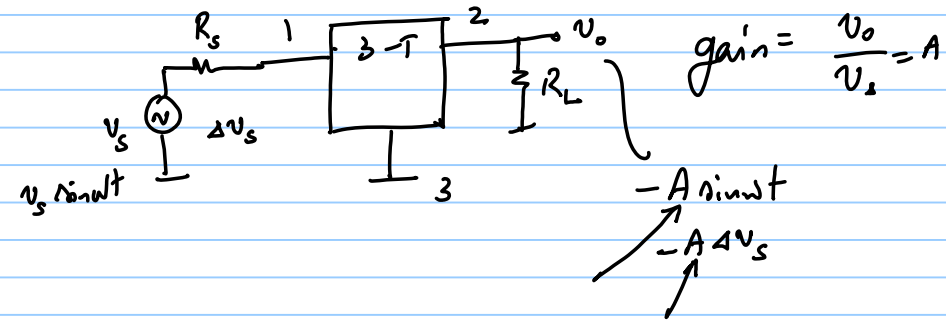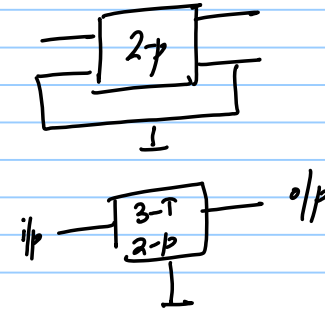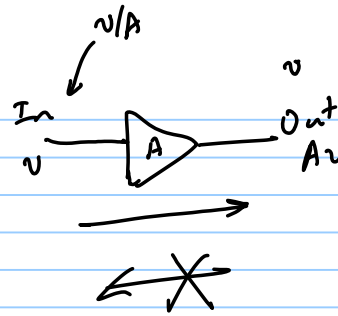
- 1) High gain
- 2) gain independent of R_s
- 3) " " of R_L
- 4) " Unilateral " 2-port




$$i_1 = y_{11} v_1 + y_{12} v_2$$

$$i_2 = y_{21} v_1 + y_{22} v_2$$

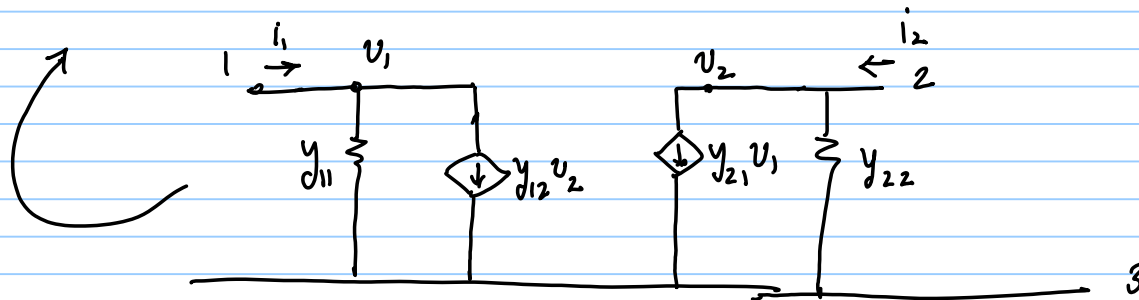

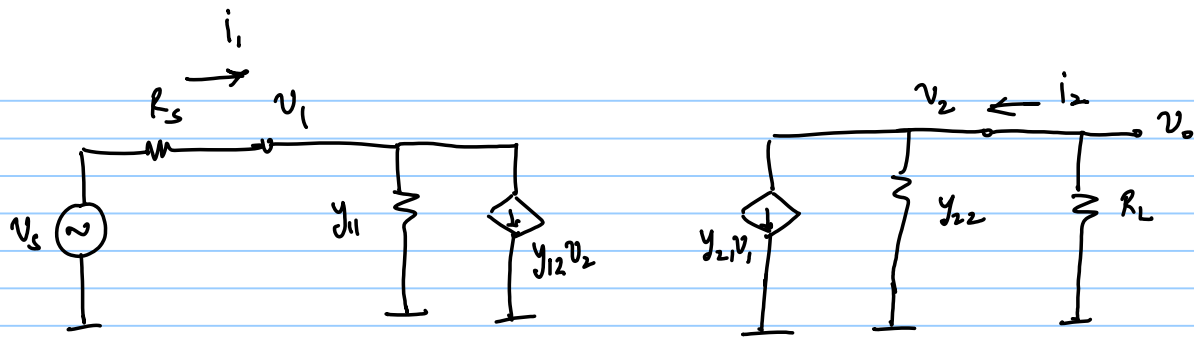
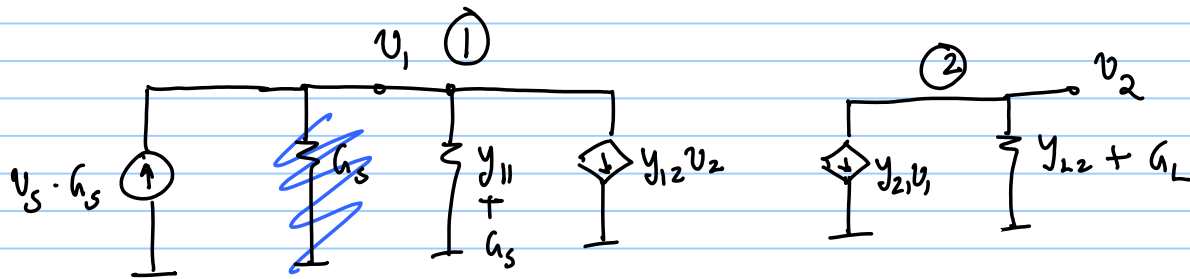
$$\frac{v_o}{v_s} = ? \left\{ = \frac{v_2}{v_s} \right\}$$



$$\text{KCL @ } \textcircled{1} \Rightarrow v_s \cdot g_s = v_1 (y_{11} + g_s) + y_{12} v_2$$

$$\text{KCL @ } \textcircled{2} \Rightarrow y_{21} v_1 + (y_{22} + g_L) \cdot v_2 = 0$$

$$v_1 = (v_s \cdot g_s - v_2 \cdot y_{12}) \cdot \frac{1}{y_{11} + g_s}$$

← plug back into

$$\left(\frac{y_{21}}{y_{11} + G_s} \right) (v_s G_s - v_2 \cdot y_{12}) + v_2 (y_{22} + G_L) = 0$$

$$v_s \cdot (y_{21} \cdot G_s) = v_2 \cdot [y_{12} y_{21} - (y_{11} + G_s)(y_{22} + G_L)]$$

$$\boxed{\frac{v_2}{v_s} = \frac{y_{21} G_s}{y_{12} y_{21} - (y_{11} + G_s)(y_{22} + G_L)}}$$

1) High gain $\rightarrow \infty$ gain if $y_{12} y_{21} = (y_{11} + G_s)(y_{22} + G_L)$ \times Happens due to instability

4) Unilateral: $\boxed{y_{12} = 0}$

$$\frac{v_2}{v_s} = \frac{-y_{21} G_s}{(y_{11} + G_s)(y_{22} + G_L)}$$

2) Gain indep. of R_S : $y_{11} = 0$

$$\frac{v_2}{v_s} = \frac{-y_{21}}{y_{22} + G_L}$$

$$y_{22} = 0$$

$$\frac{v_2}{v_s} = \frac{-y_{21}}{G_L}$$

$$y_{21} = \text{as large as possible}$$

3) Indep of R_L ? \leftarrow gain will be a fn. of R_L

$$y_{11} = 0$$

$$y_{12} = 0$$


$$[y] = \begin{bmatrix} 0 & 0 \\ \text{large} & 0 \end{bmatrix}$$

$$y_{21} = \text{as large as possible}$$

$$y_{22} = 0$$

$$y_{11} = \frac{\partial f}{\partial v_1} = 0 \quad \text{and} \quad y_{12} = \frac{\partial f}{\partial v_2} = 0 \quad \Rightarrow \quad \boxed{I_1 = \text{constant}}$$

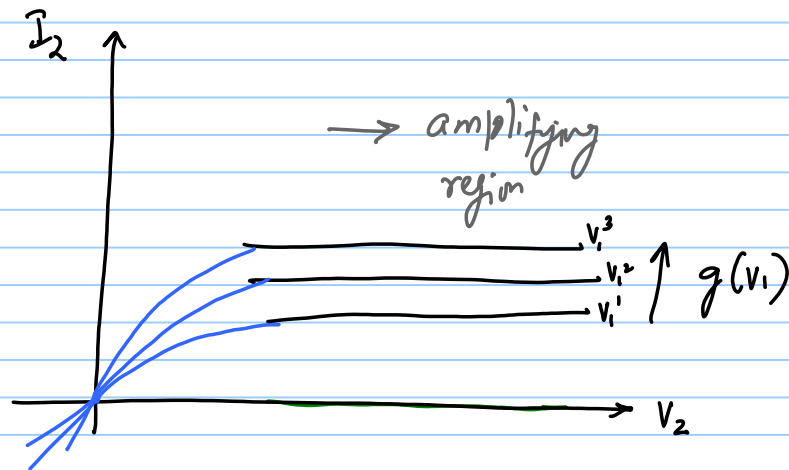
$$y_{22} = \frac{\partial g}{\partial v_2} = 0 \quad \Rightarrow \quad \boxed{I_2 = g(v_1)}$$




→ * MOSFET : $I_1 = 0$; $I_2 = g_1(v_1)$

* BJT, JFET : $I_1 = \text{small, constant}$
 $I_2 = g_2(v_1)$

MOSFET

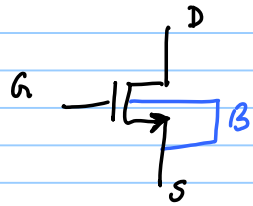

n MOSFET n nMOS
 e^- : charge carriers

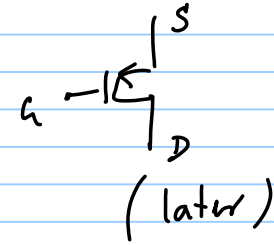


pMOS
 holes : charge carriers

G : port 1

D : port 2

S : ref. terminal

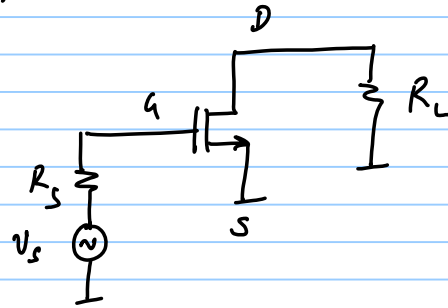

$$I_a = 0 = I_i$$

$$I_2 = I_D = 0 \quad \text{if } V_{GS} < V_T$$

$$\left. \begin{aligned}
 &= \mu_n \epsilon_{ox} \left(\frac{W}{L} \right) \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right] \quad \text{for } V_{DS} < V_{GS} - V_T \\
 &= \frac{1}{2} \mu_n \epsilon_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2 \quad \text{for } V_{DS} \geq V_{GS} - V_T
 \end{aligned} \right\} V_{GS} > V_T$$

V_T : Threshold Voltage


μ_n : mobility of e^- s



C_{ox} : Oxide capacitance (per unit area cap.)

W, L : Width & length of MOSFET (channel) — geometric parameters

"enhancement" mode nMOSFET : $V_T > 0$ $V_{T_e} = 0.3V$

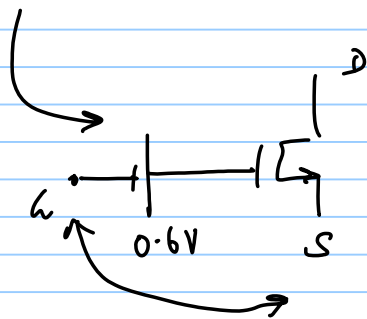"depletion" mode nMOSFET : $V_T < 0$ $V_{T_d} = -0.3V$



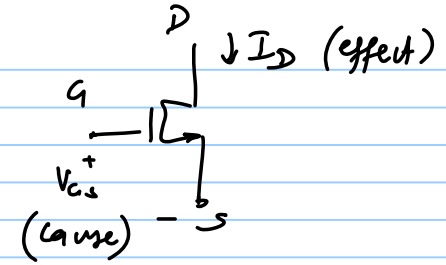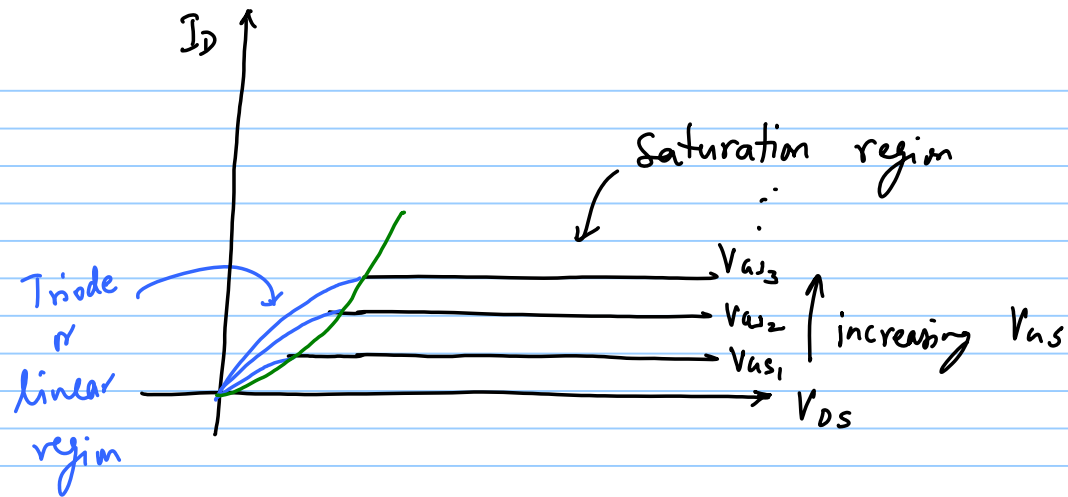

In saturation:

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2$$

$$y_{11} = y_{12} = 0 \quad \text{bec. } I_G = 0$$

$$y_{22} = 0 \quad \text{bec. } I_D = g(V_{GS}) \text{ only}$$

$$y_{21} = \frac{\partial g}{\partial V_1} = \frac{\partial I_D}{\partial V_{GS}} = \text{"transconductance"} \quad g_m$$


$$(V_{GS} - V_T) = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}}$$

$$g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T) \quad \text{at op pt. value } V_{GS}$$

$$g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} \quad (1)$$

$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D} \quad (2)$$

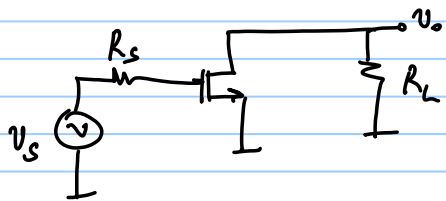
$$g_m = \frac{2I_D}{(V_{GS} - V_T)} \quad (3)$$



$$\frac{v_o}{v_s} = \frac{-y_{21}}{y_L} = -g_m R_L$$

22/8/17

Lec 4

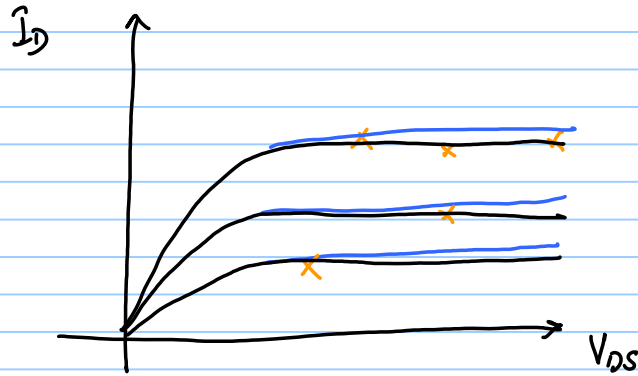

$y_{22} \neq 0$, but a small number

"channel length modulation" $L \rightarrow L + \Delta L$
 \downarrow
 $f(V_{GS})$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

$\lambda = \text{units of } V^{-1}$



$\lambda = \text{v. small}$

$$y_{22} = \frac{\partial I_D}{\partial V_2} = \frac{\partial I_D}{\partial V_{DS}} = \underbrace{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2}_{I_D} \cdot \lambda$$

$$y_{22} \approx \lambda \cdot I_D$$



$$\rightarrow r_{ds} = \frac{1}{\lambda I_D} \quad \text{v. large}$$



Small-signal model of MOSFET

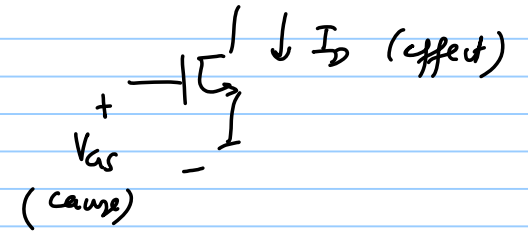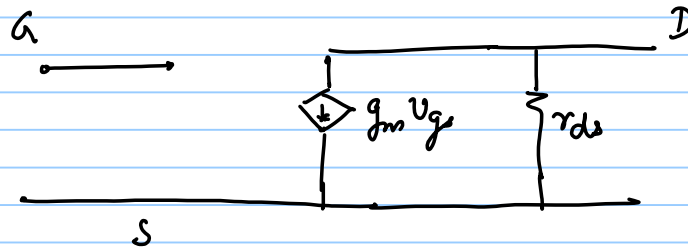


Op pt. $\rightarrow (V_{GS}, V_{DS})$

Small Signal

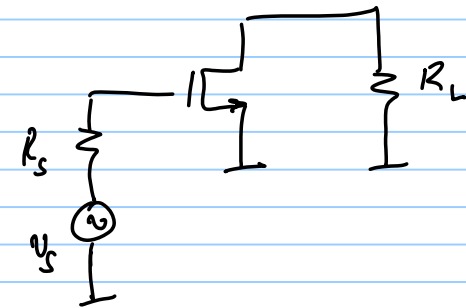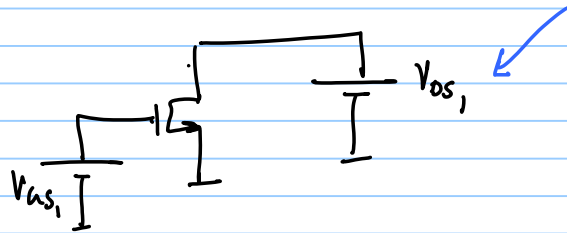


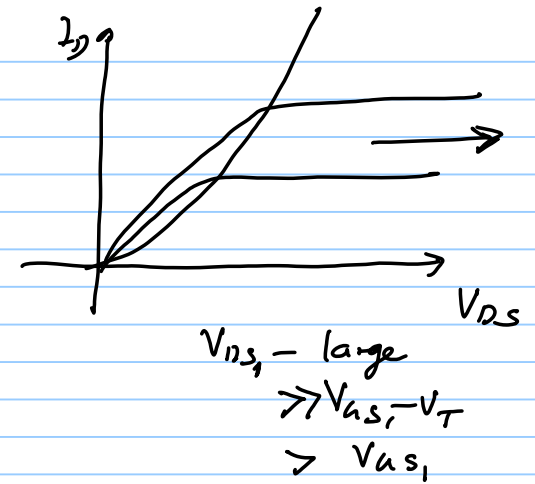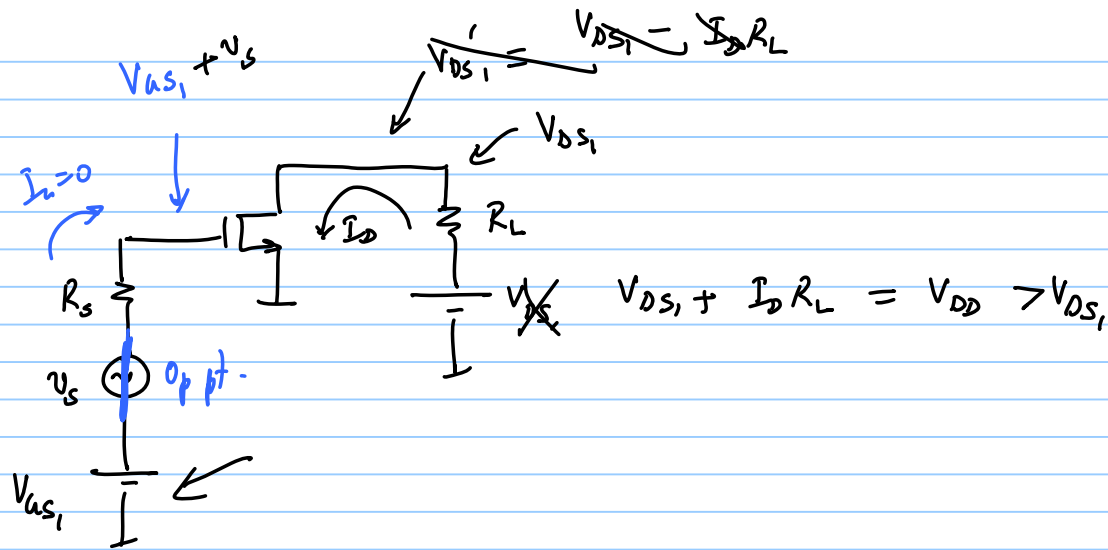



generate V_{gs1} from V_{DD}



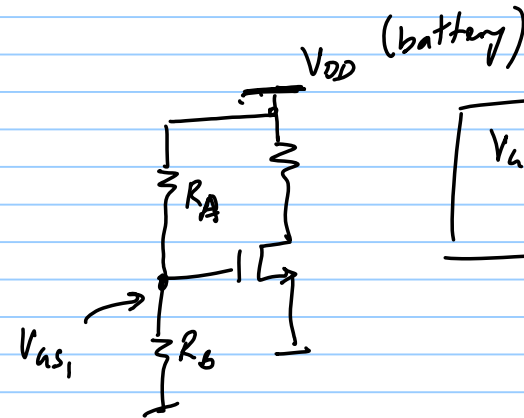

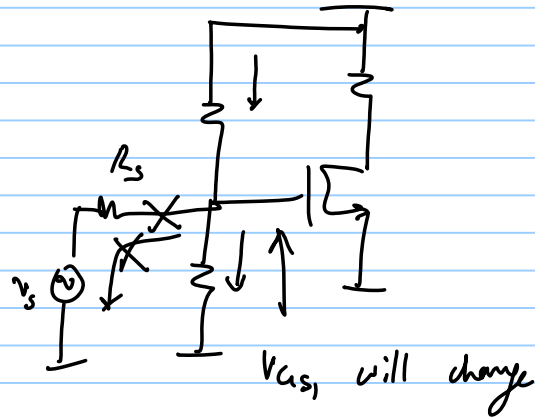
$$V_{gs1} = \frac{R_B}{R_A + R_B} \cdot V_{DD}$$




Op pt. = $f(R_s)$ X

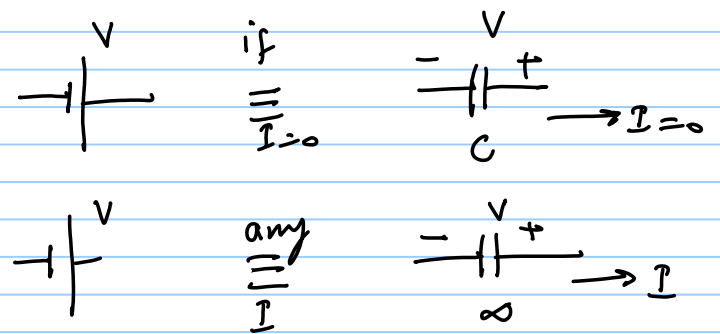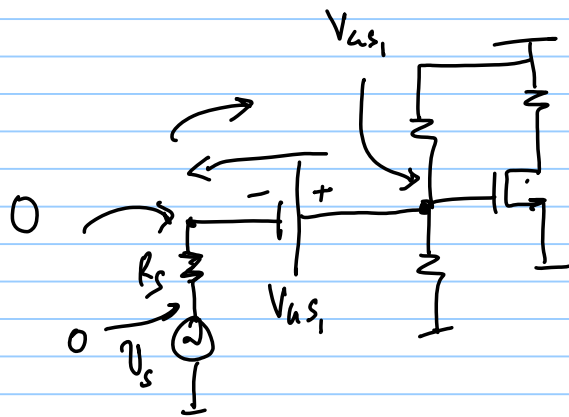

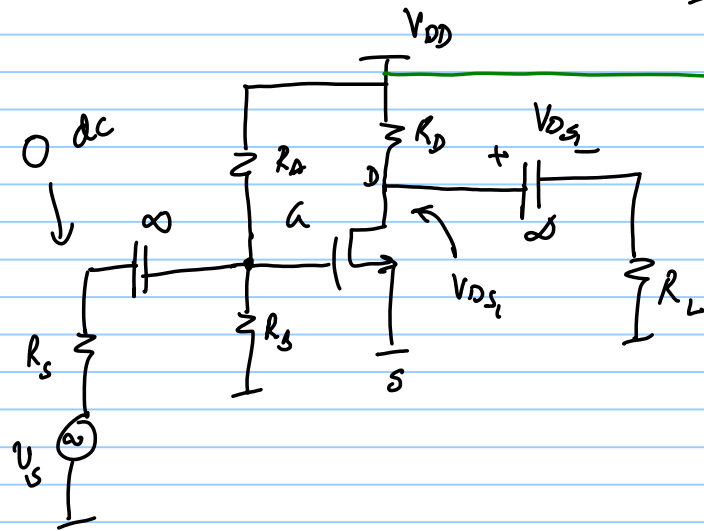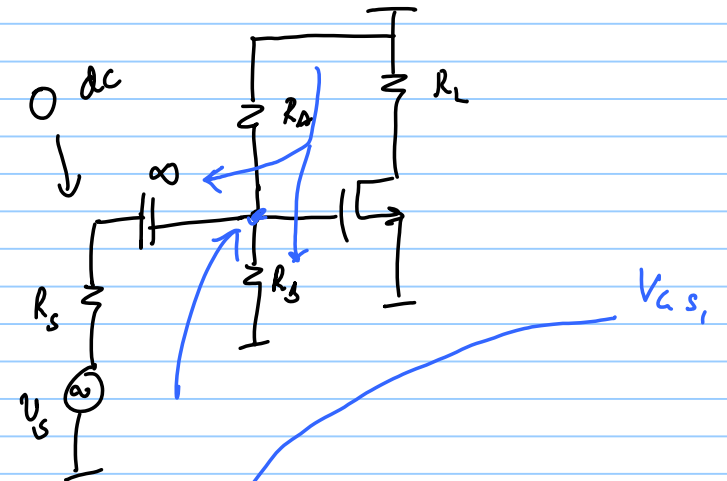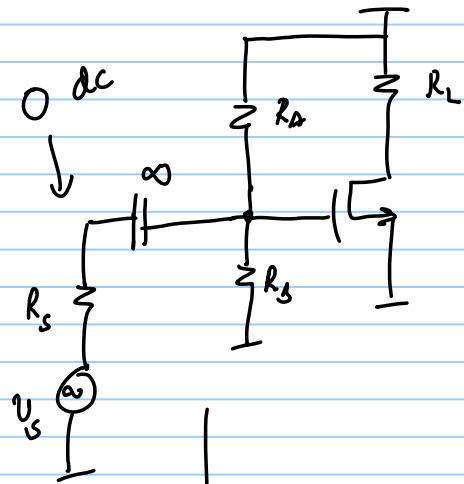


$$V_{DD} = V_{ds_1} + I_D R_D$$

"Common Source Amplifier"

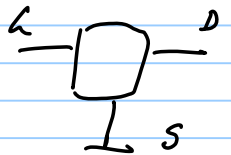

Small signal equivalent circuit

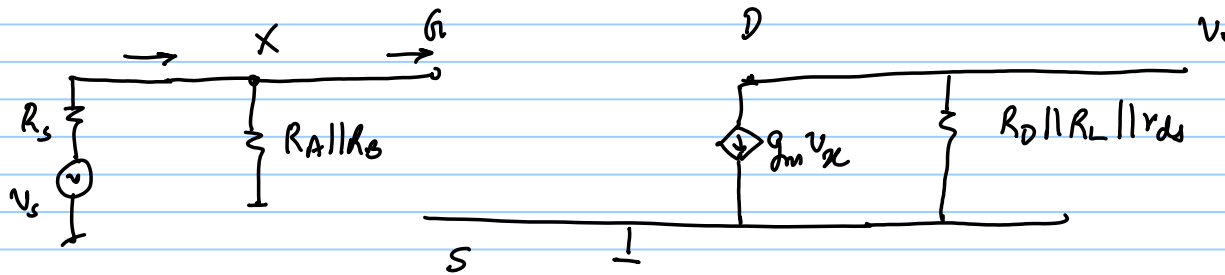

$$v_x = v_s \cdot \frac{R_A \parallel R_B}{R_s + R_A \parallel R_B} \quad ; \quad \text{we want } v_x = v_s$$

$$v_x \approx v_s \quad \text{if} \quad R_A \parallel R_B \gg R_s \quad \leftarrow \quad R_A \& R_B \gg R_s$$


$$v_{gs} = \frac{R_B}{R_A + R_B} \cdot V_{DD}$$

$$v_o = -g_m (R_D \parallel R_L \parallel r_{ds}) \cdot v_x$$


$$\text{we want } v_o = -g_m R_L v_s$$

+ $r_{ds} \gg R_D \& R_L \Rightarrow \lambda$ should be v. small


* $R_D \gg R_L$

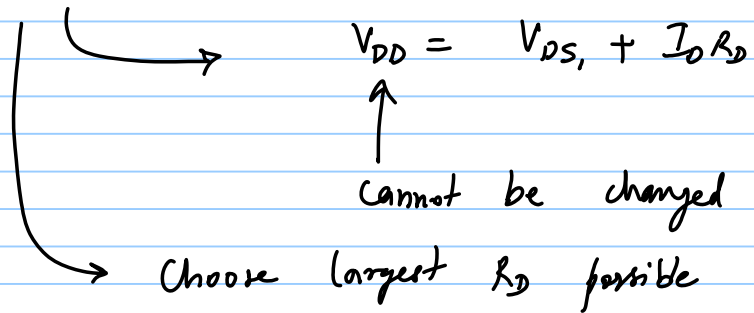


cannot be changed by a large amount

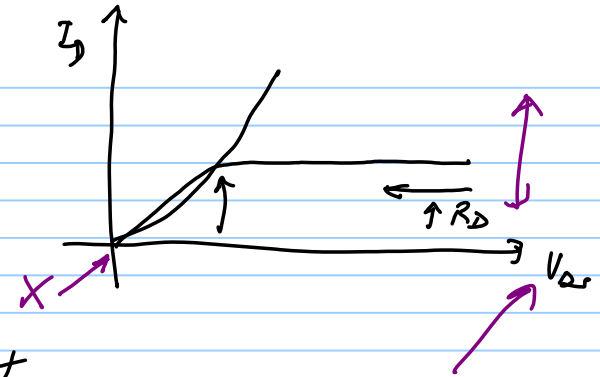

gain $\frac{v_o}{v_s} = -g_m (R_D || R_L)$

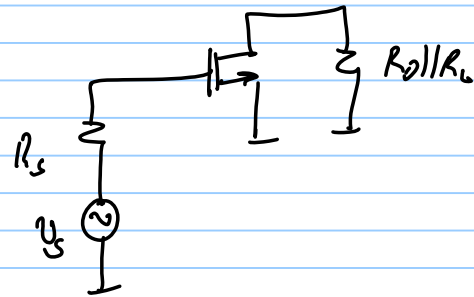


S.S. picture

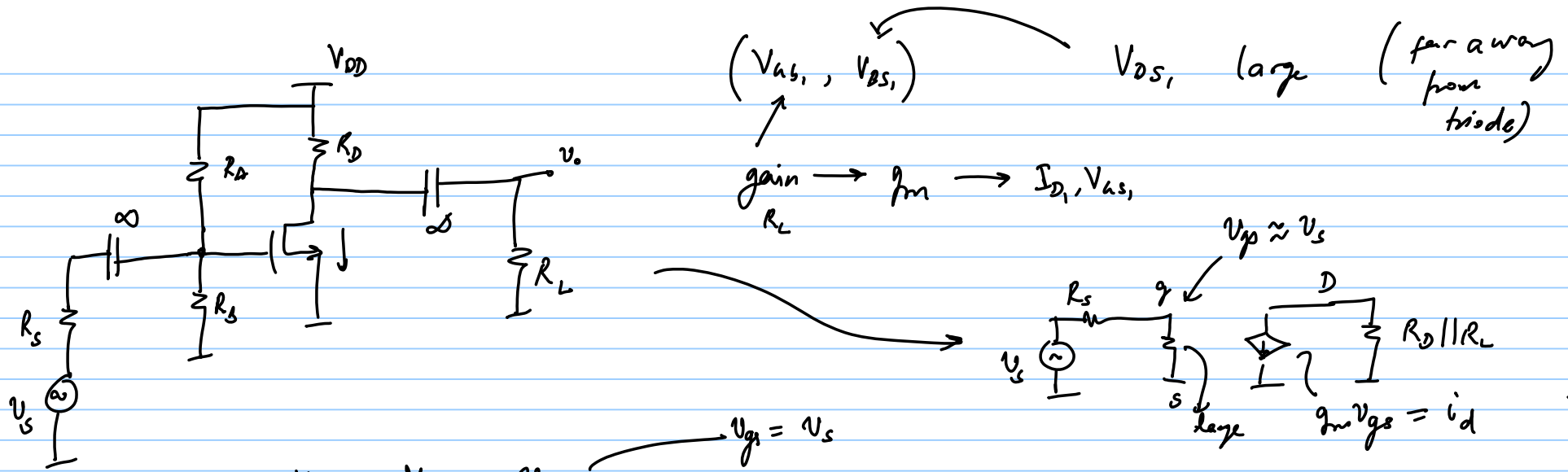


$$\begin{aligned}
 & \rightarrow V_{as} = V_{as1} + v_{gs} \quad \xrightarrow{v_{gs} = v_s} \\
 & \rightarrow V_{ds} = V_{ds1} + v_{ds} \quad \xrightarrow{v_{ds} = -g_m (R_D || R_L) \cdot v_s = -A v_s} \\
 & \rightarrow I_D = I_{D1} + i_d \quad \xrightarrow{i_d = g_m v_{gs} = g_m v_s}
 \end{aligned}$$

Op pt. : $V_{ds1} > V_{as1} - V_T$ ✓
 $V_{ds1} > V_{as1}$
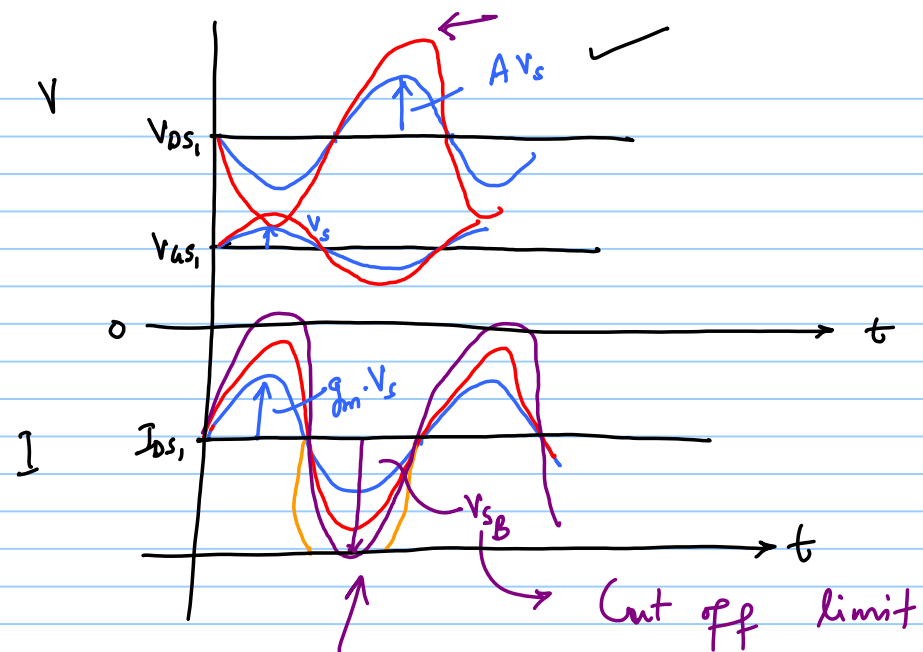
$$\begin{aligned}
 v_s &= V_s \sin \omega t \\
 i_d &= g_m V_s \sin \omega t \\
 v_d &= -A V_s \sin \omega t
 \end{aligned}$$



$V_s \uparrow$

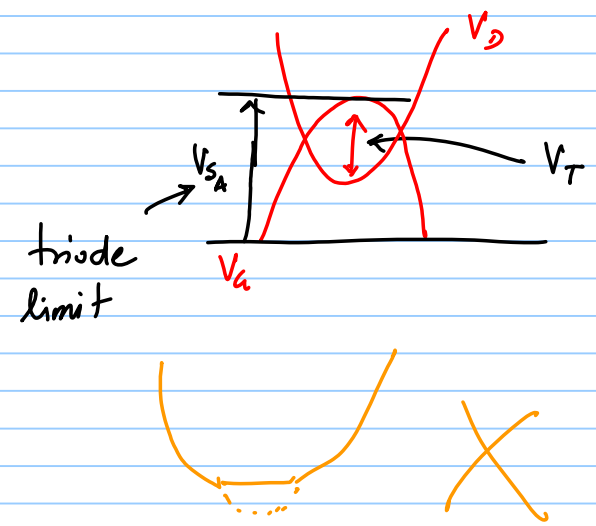

$$i_d = g_m V_s \sin \omega t$$

$$I_{D_1} + i_d = 0 \Rightarrow I_{D_1} - g_m V_{S_B} = 0 \Rightarrow$$

$$V_{S_B} = \frac{I_{D_1}}{g_m}$$

triode limit: $V_{DS} \gg V_{GS} - V_T$

$$V_D - V_S \gg V_G - V_S - V_T$$


$$V_D \gg V_G - V_T$$

$$V_{DS_i} - AV_{SA} = V_{GS_i} + V_{SA} - V_T$$

$$V_{SA} = \frac{V_{DS_i} - (V_{GS_i} - V_T)}{1+A}$$

Swing limit of C.S.A = minimum $\{V_{SA}, V_{SB}\}$ V_{SB}'

$$I_D = 0 \Rightarrow V_{GS} < V_T$$

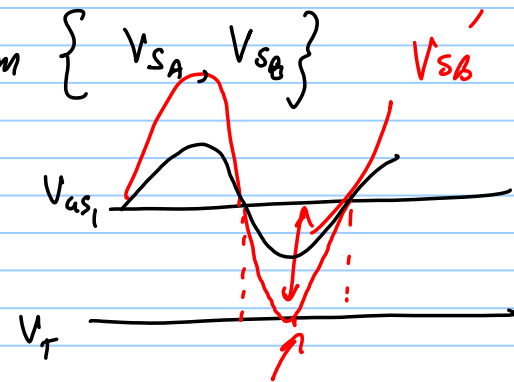

24/8/17

Lec 5

Quiz 1 - September 19th (Tuesday)


Quiz 2 - October 24th (Tue)

Quiz 3 - November 19th (Sun) -

End Semester - December 14th (Thu)

10:30 am - noon

Triode

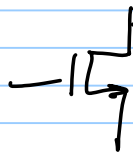

$$I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) \left[(V_{GS} - V_T) \cdot V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$y_{11} = y_{12} = 0$$

$$y_{21} = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \left(\frac{W}{L} \right) \cdot V_{DS}$$

↳ smaller than y_{21} (sat.)


$$y_{22} = \frac{\partial I_D}{\partial V_{DS}} = \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T - V_{DS})$$

↳ larger than y_{22} (sat.)

$$\text{gain} = \frac{-y_{21}}{y_{22} + G_L}$$

⇒ gain drops due to larger y_{22}

gain drops due to smaller y_{21}

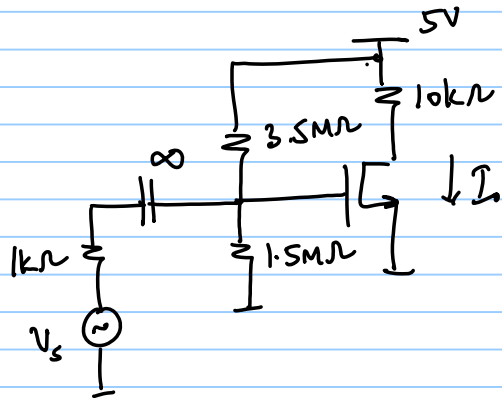

$$\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$$

$$V_T = 1\text{V}$$

$$\left(\frac{W}{L}\right) = 10$$

$$V_{GS1} = 1.5\text{V} \quad ; \quad (V_{GS1} - V_T) = 0.5\text{V} \quad \checkmark$$

$$I_{D1} = \frac{1}{2} \times 100 \mu\text{A} \times 10 \times (0.5)^2 = 125 \mu\text{A}$$

$$V_{DS1} = 5 - 1.25 = 3.75\text{V} \quad \checkmark$$


$$g_m = \frac{2 I_{D1}}{V_{GS1} - V_T} = \frac{2 \times 125 \mu\text{A}}{0.5\text{V}} = 0.5 \text{ mS}$$

$$\text{gain} = -g_m R_L = -5$$

$$V_{sB} = \frac{I_{D1}}{g_m} = \frac{125 \mu\text{A}}{0.5 \text{ mS}} = 250 \text{ mV}$$

$$V_{sA} = \frac{V_{DS1} - (V_{GS1} - V_T)}{1 + g_m R_L} = \frac{3.75 - 0.5}{6} = 545 \text{ mV}$$

Swing limit
= 250 mV

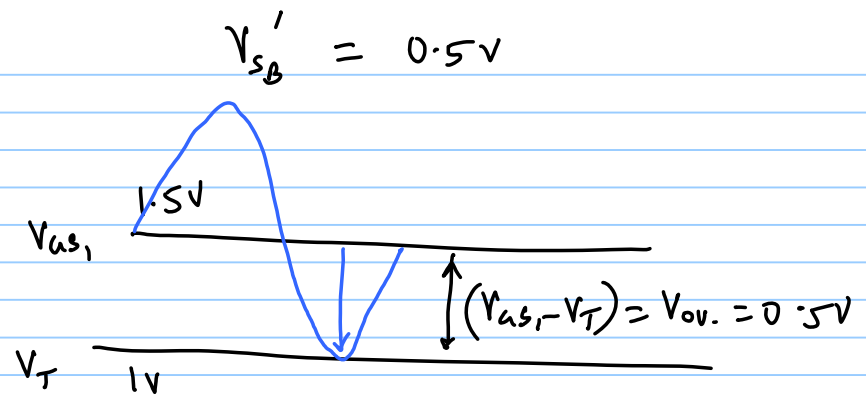


$I_D = 0 \Rightarrow V_{gs} \leq V_T$

$V_{gs} > 0$

250mV (V_{SB})

500mV (V_{SB}')

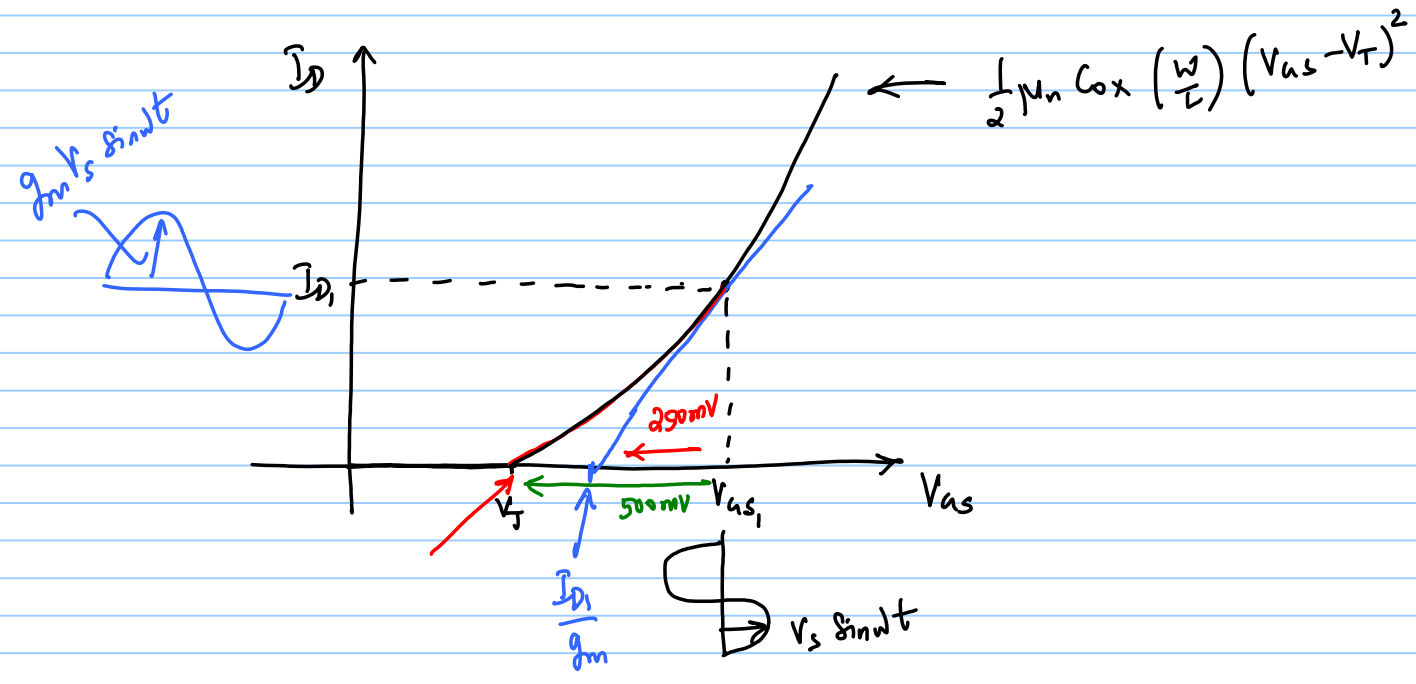

When is SS approx. Valid??

$$I_D = f(V_{gs}, V_{ds})$$

$$I_{D1} + i_d = f(V_{gs1}, V_{ds1}) + \frac{\partial f}{\partial V_{gs}} \cdot v_{gs} + \frac{\partial f}{\partial V_{ds}} \cdot v_{ds} + \frac{1}{2} \frac{\partial^2 f}{\partial V_{gs}^2} \cdot v_{gs}^2 + \frac{1}{2} \frac{\partial^2 f}{\partial V_{ds}^2} \cdot v_{ds}^2 + \frac{\partial^2 f}{\partial V_{gs} \cdot \partial V_{ds}} \cdot v_{gs} \cdot v_{ds} + \dots$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{gs} - V_T)^2$$

$$\frac{\partial I_D}{\partial V_{gs}} = g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{gs} - V_T)$$



$$\frac{\partial^2 I_D}{\partial V_{gs}^2} = \mu_n C_{ox} \left(\frac{W}{L}\right)$$

$$\frac{1}{2} \frac{\partial^2 I_D}{\partial V_{as}^2} \cdot v_{gs}^2 \ll \frac{\partial I_D}{\partial V_{as}} \cdot v_{gs}$$

$$\frac{1}{2} \cdot \mu_n C_{ox} \left(\frac{W}{L}\right) \cdot v_{gs}^2 \ll \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{as} - V_T) v_{gs}$$

$$\Rightarrow \boxed{v_{gs} \ll 2(V_{as} - V_T)}$$


Not valid
when calculating V_{SB}

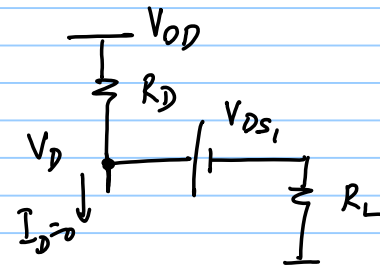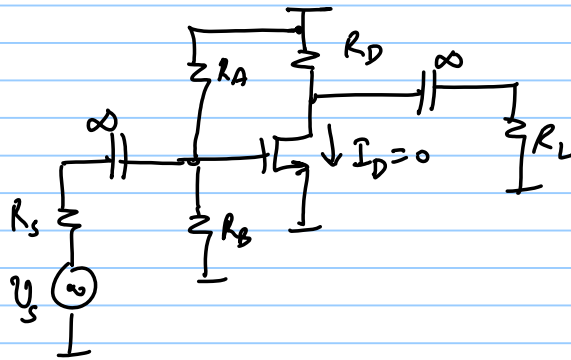

$$\frac{V_{DD} - V_D}{R_D} = \frac{V_D - V_{DS1}}{R_L}$$

$$V_D \cdot \left(\frac{1}{R_D} + \frac{1}{R_L}\right) = \frac{V_{DD}}{R_D} + \frac{V_{DS1}}{R_L}$$
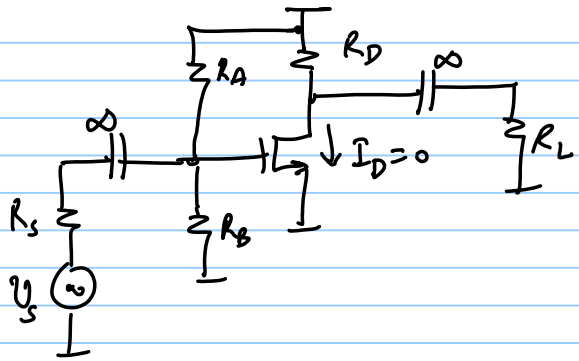
$$\boxed{V_D = \frac{V_{DD} \cdot R_L + V_{DS1} \cdot R_D}{R_D + R_L}}$$




$$A = -g_m (R_D \parallel R_L \parallel r_{ds})$$


$\uparrow R_D \Rightarrow V_{DD} \uparrow$ or $V_{DS1} \downarrow$

$$V_{DD} = V_{DS1} + I_D R_D$$

$\frac{V_o}{V_s} \rightarrow$ depends on incremental resistance



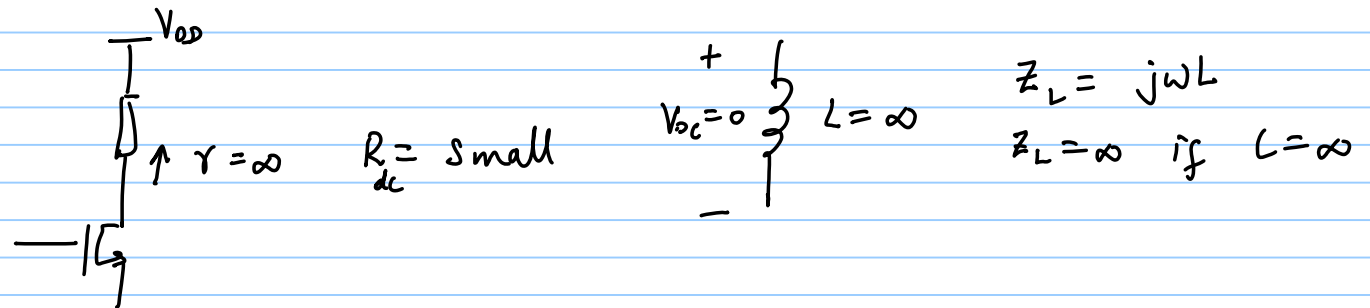
$V_{DS1} \rightarrow$ depends on total resistance



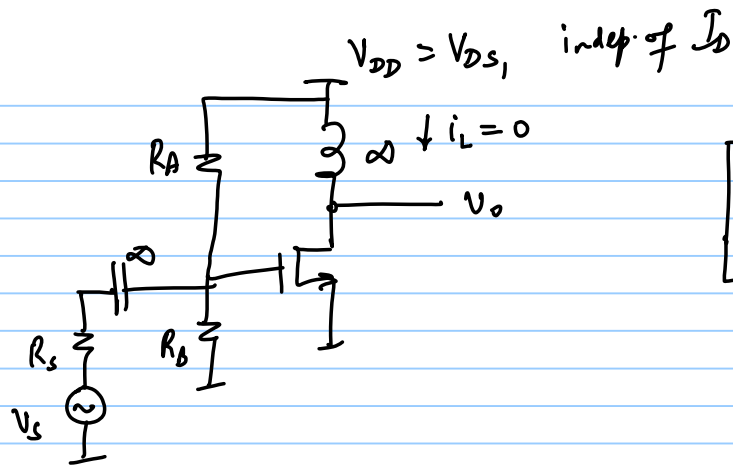




$$\frac{v_o}{v_s} = -g_m r_{ds}$$


Intrinsic gain of MOSFET (Maximum)

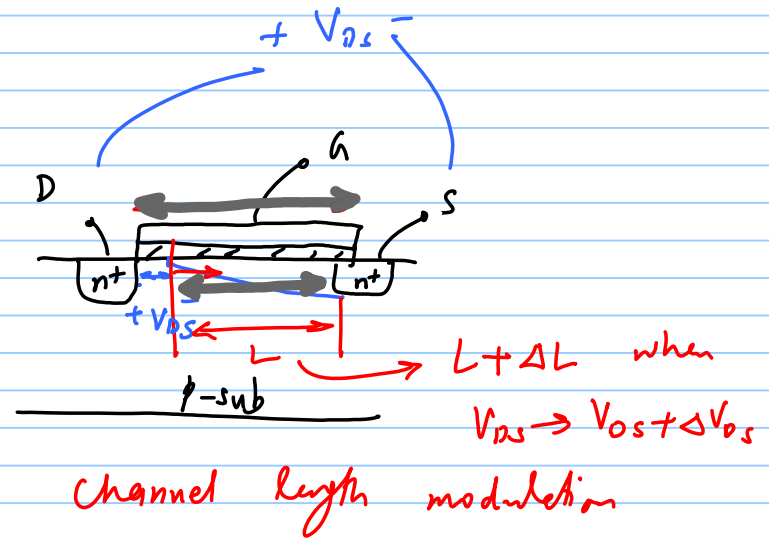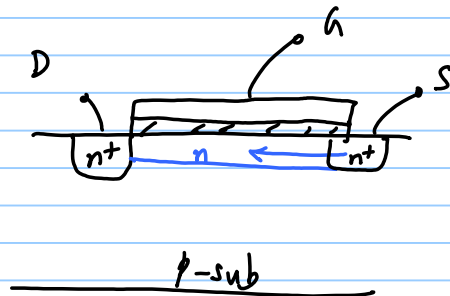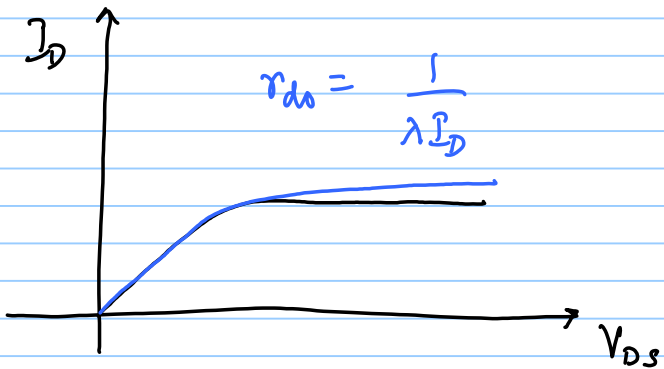

29/8/17


Lec 6

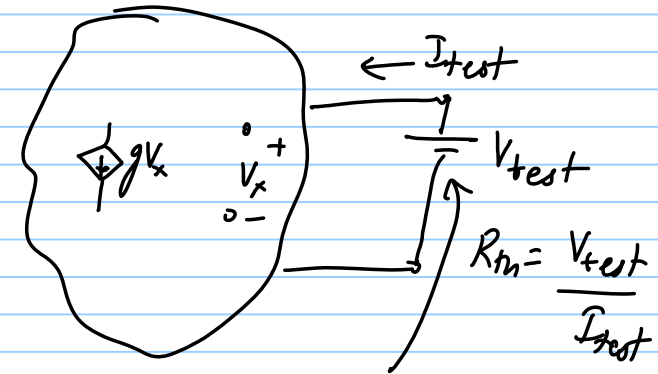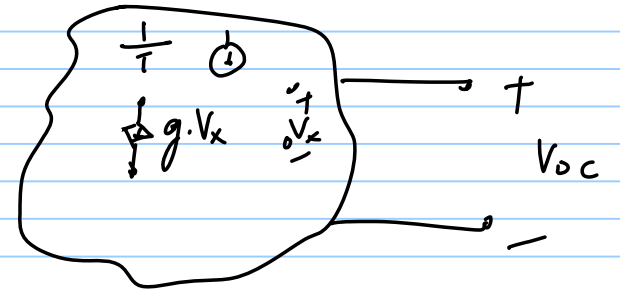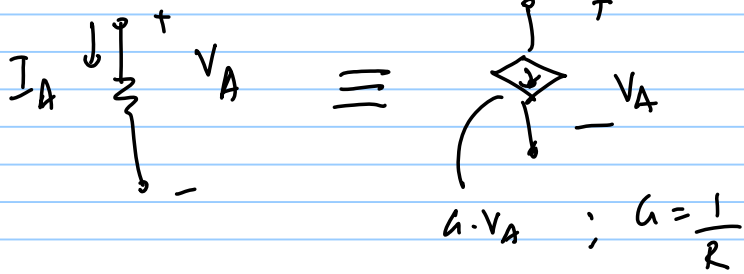

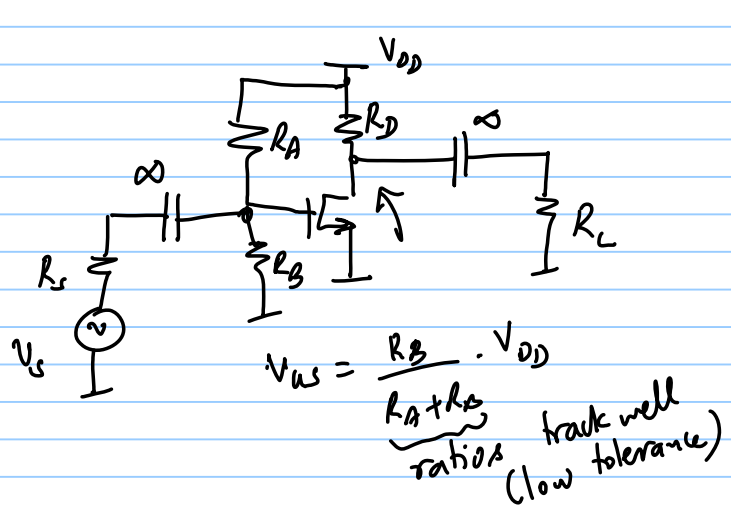

$\mu_n, C_{ox}, \left(\frac{W}{L}\right), V_T$
 Vary with T, process

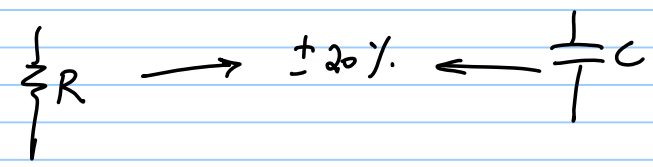g_m
 devices are nominally identical on an IC



Bias Stabilization

g_m indep. of V_T
 $g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)$

V_{GS} should track V_T

$V_{GS} - V_T = \text{constant} \Rightarrow I_D = \text{constant}$

$V_{GS} \gg V_T \Rightarrow g_m \text{ large } X$

$V_{GS} \gg V_{GS} - V_T$

Negative Feedback






Desired quantity D



Actual quantity A

- * Sense D & A
- * Compare A with D
- * Drive A towards D

desired drain current = I_0 ✓
 actual " " = I_D


$A - D$
 or
 $D - A$) - sign & magnitude

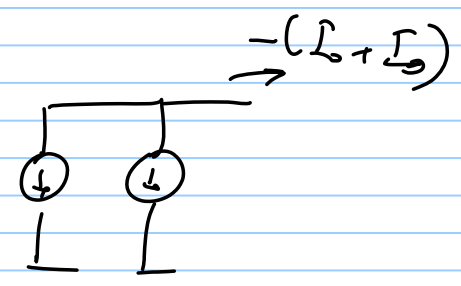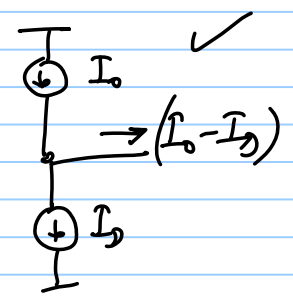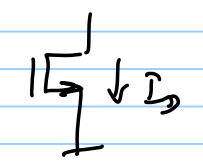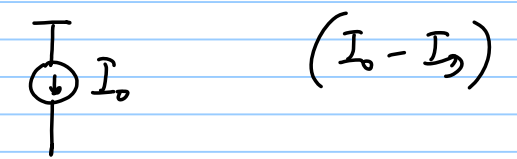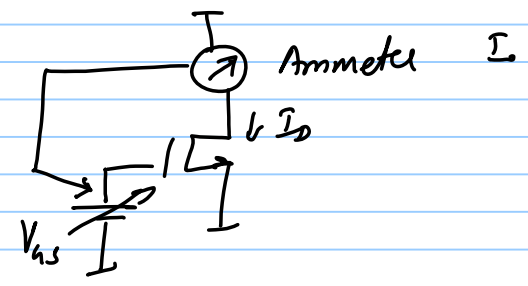


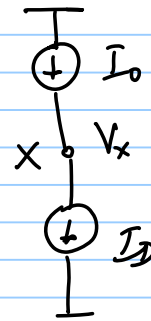
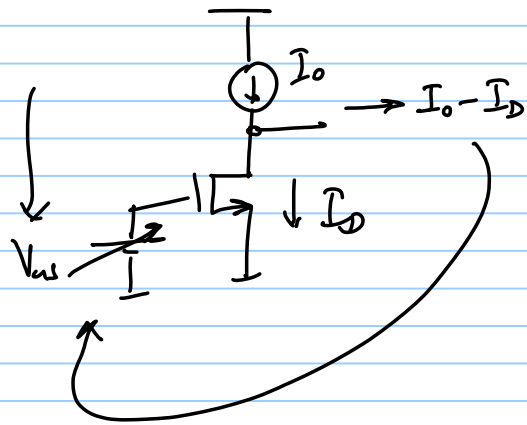


If $I_0 > I_D$, $V_x \uparrow$ (we want to $\uparrow V_{gs}$)

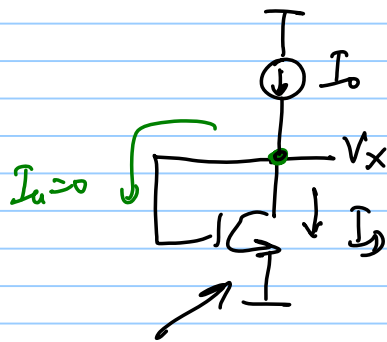If $I_0 < I_D$, $V_x \downarrow$ (we want to $\downarrow V_{gs}$)




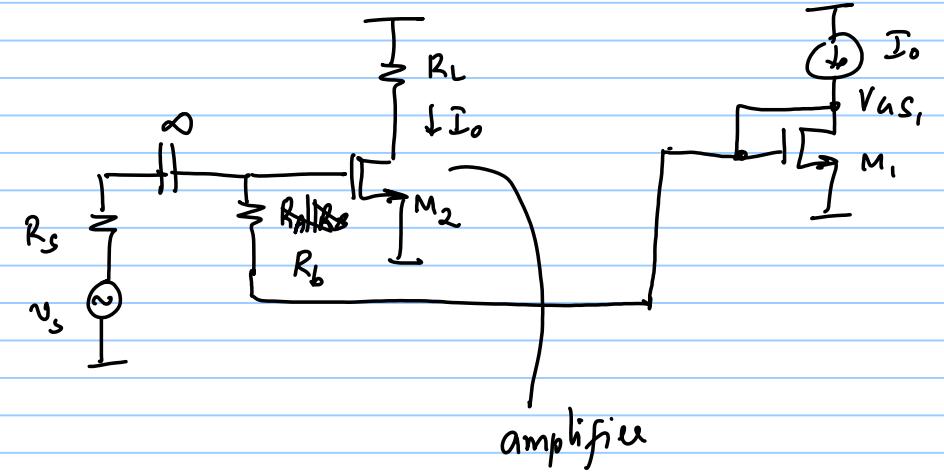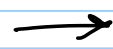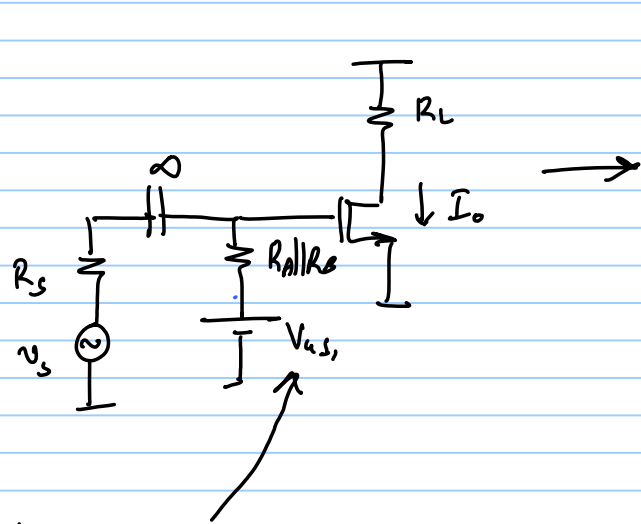$V_x = V_{gs}$ for a drain current $I_D = I_0$



amplifier


"Current Mirror"

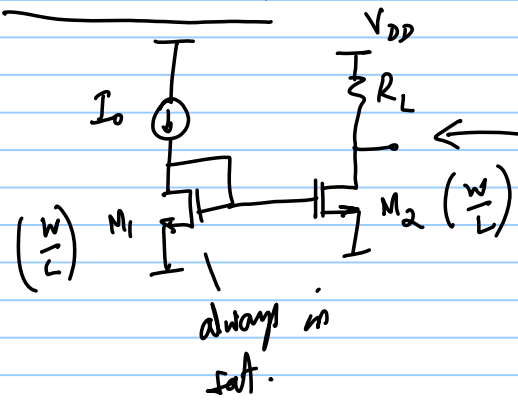




always in sat.



M_1 & $M_2 \rightarrow$ both in saturation

$$V_{DS2} = V_{DD} - I_o R_L$$

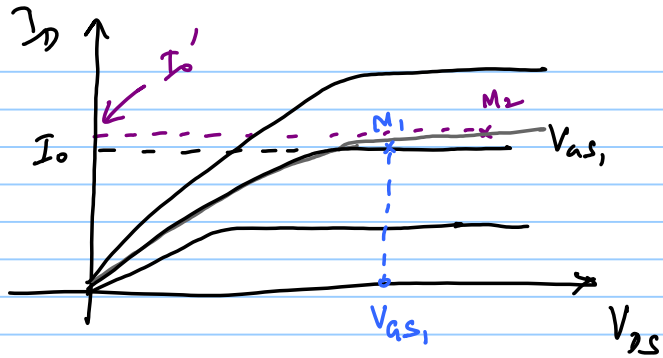


Ensure r_{ds} is large

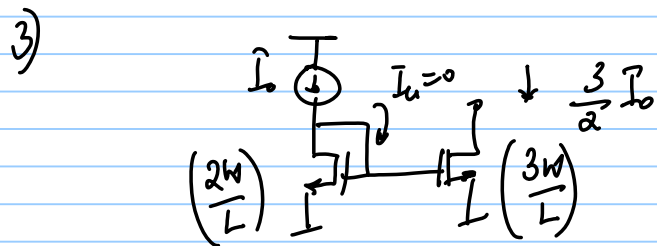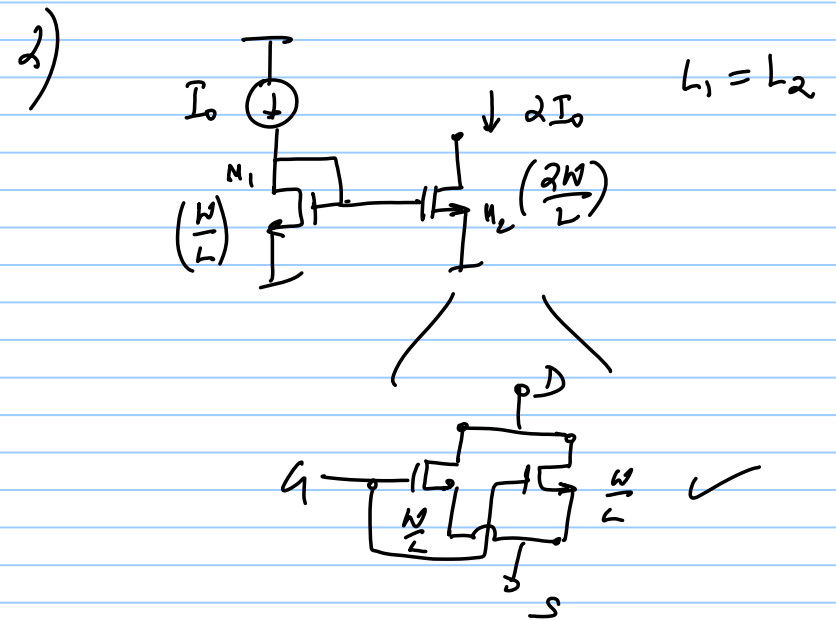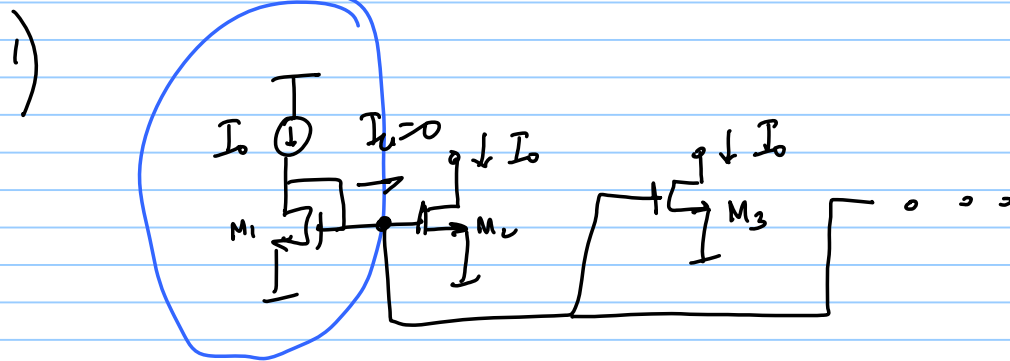

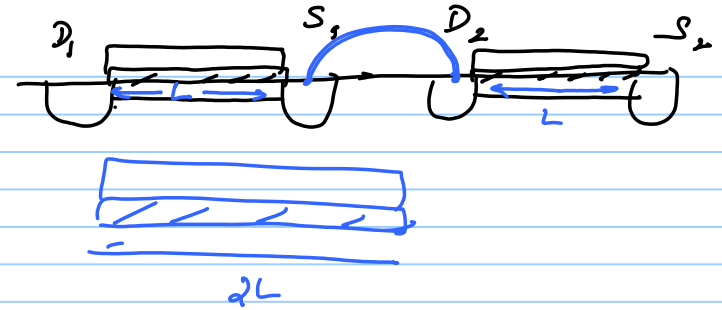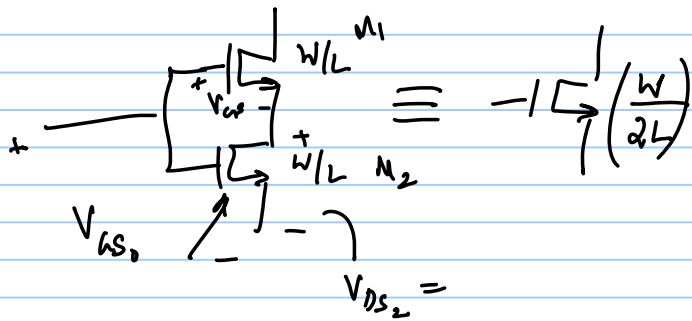


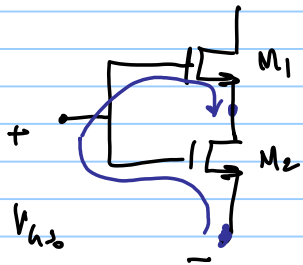$M_2 :$
 $V_{gs_2} = V_{gs_0}$
 $V_{ds_2} = V_{gs_0} - V_{gs_1}$






$$V_{ds_2} > V_{gs_2} - V_T$$
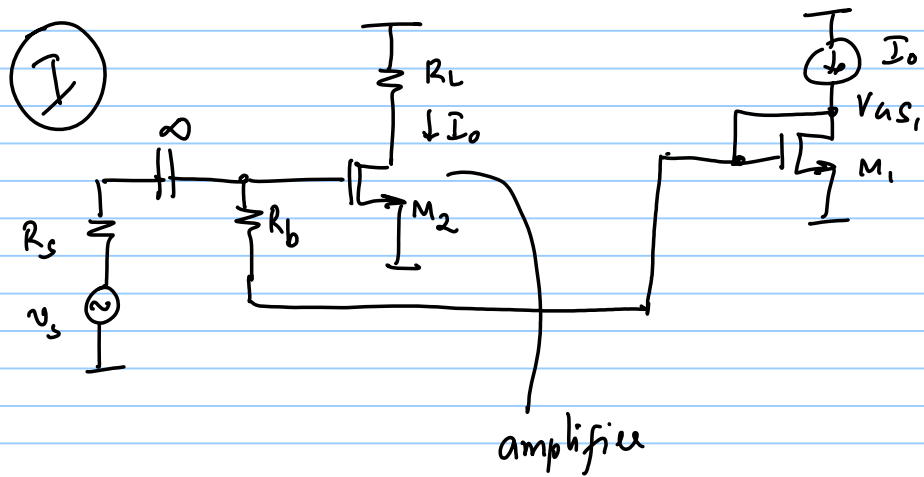
$$V_{gs_0} - V_{gs_1} > V_{gs_0} - V_T \Rightarrow V_{gs_1} < V_T \quad ??$$



SS
 eq.
 ckt.

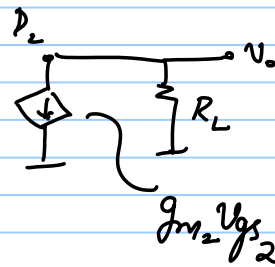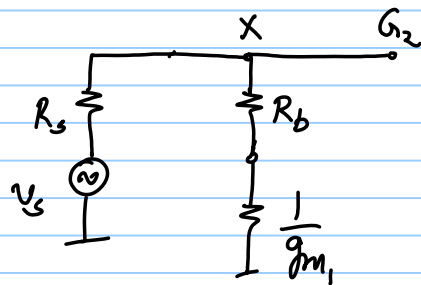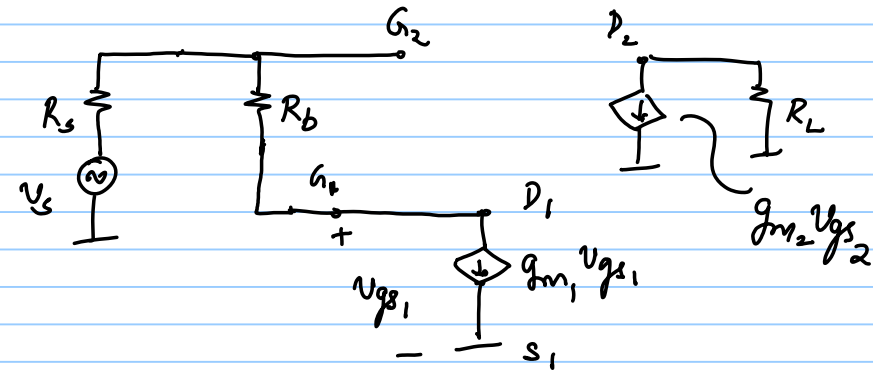

$$v_x = \frac{R_b + 1/g_{m1}}{R_s + R_b + 1/g_{m1}} \cdot v_s$$


we want $v_x \approx v_s$

$$\Rightarrow R_b + 1/g_{m1} \gg R_s$$

i.e. $R_b \gg R_s$


$$v_o = -g_{m2} R_L \cdot v_s$$

$$A-D \Rightarrow (I_D - I_o)$$

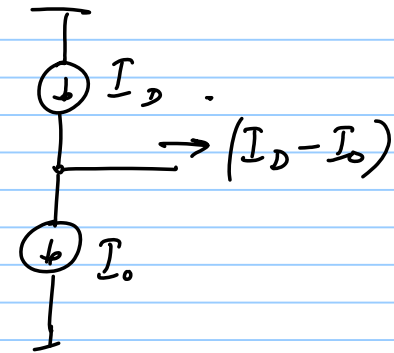

31/8/17


Lec 7

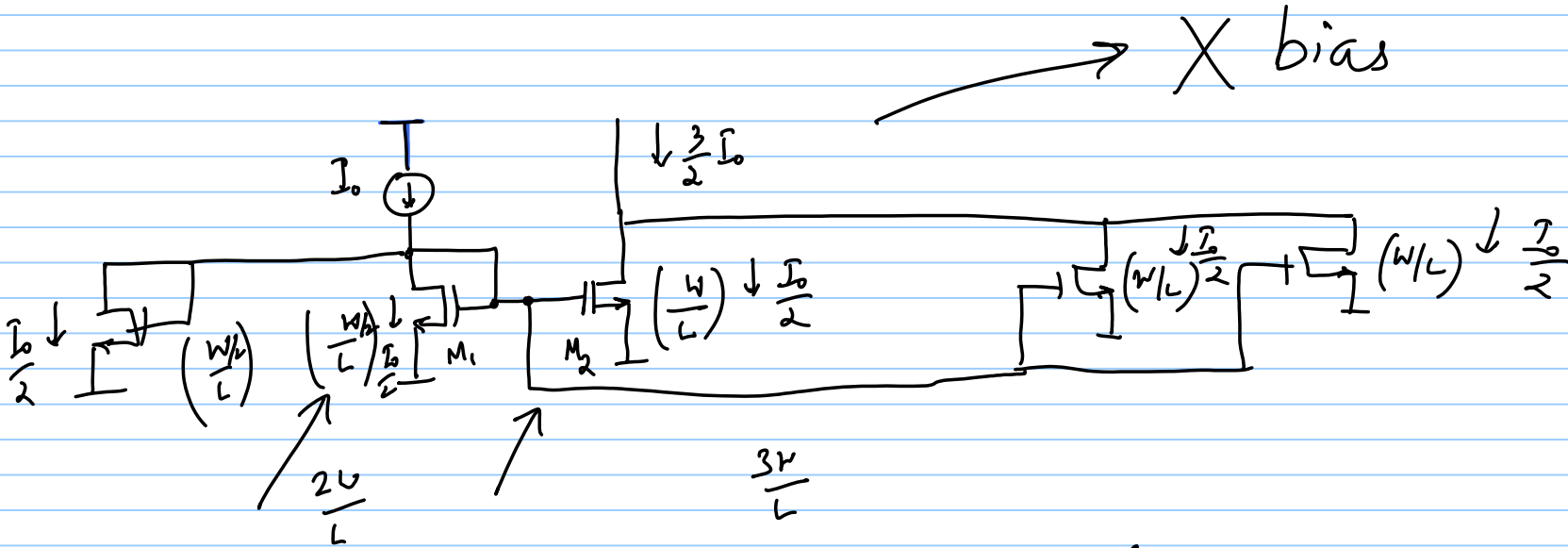

X bias


$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2$$

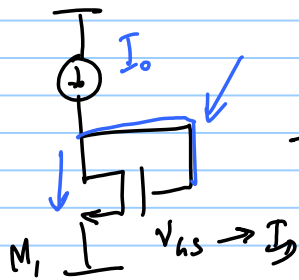$\frac{1}{2} \times$ $\frac{1}{2} \times \left(\frac{W}{L}\right)$




always in sat.

$$V_{GS} = V_{DS}$$


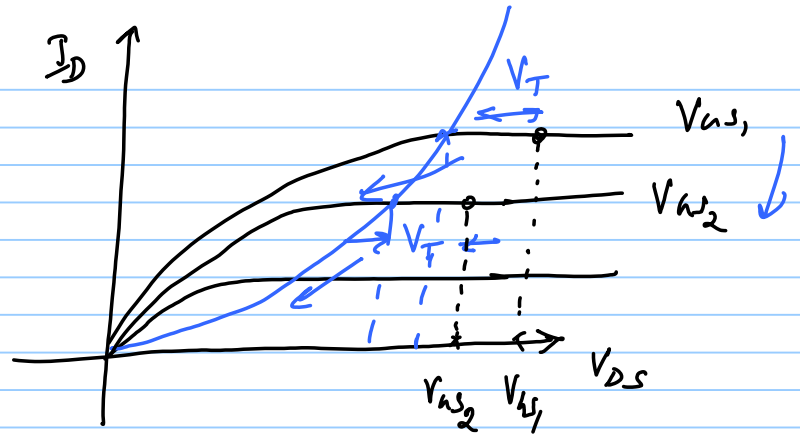


$$(I_D - I_0)$$

$$I_G = 0 \Rightarrow I_D = I_S$$

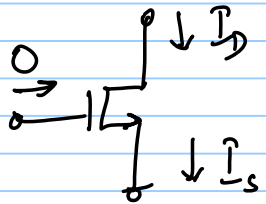

$$(I_S - I_0)$$

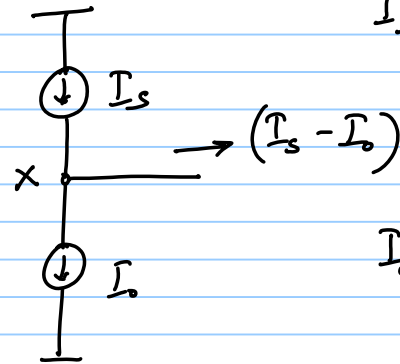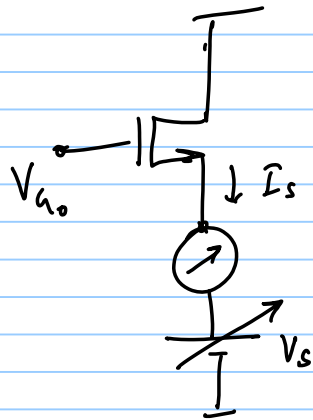


$$I_s > I_0 \Rightarrow V_x \uparrow \left\{ \begin{array}{l} \text{we want} \\ V_{as} \downarrow \Rightarrow V_s \uparrow \end{array} \right\}$$


//

$$(V_{a_0} - V_s)$$

$$I_s < I_0 \Rightarrow V_x \downarrow \left\{ \begin{array}{l} \text{we want} \\ V_{as} \uparrow \Rightarrow V_s \downarrow \end{array} \right\}$$



$$\Rightarrow V_x = V_s$$

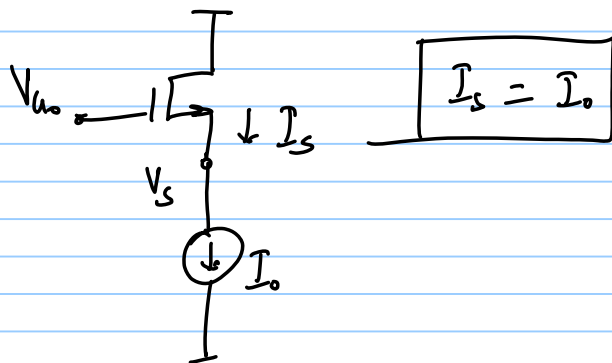



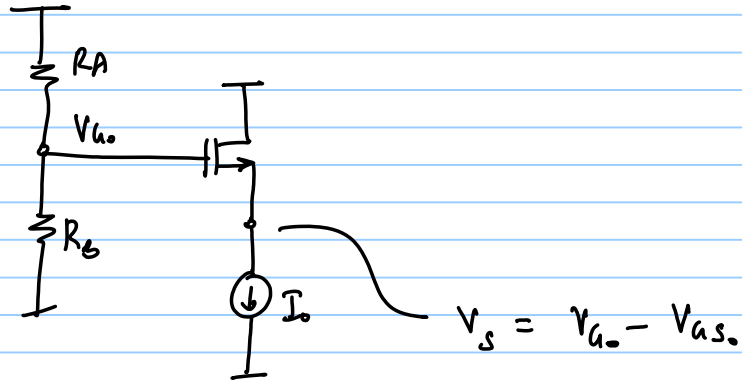


$$I_o = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{gs} - V_T)^2$$

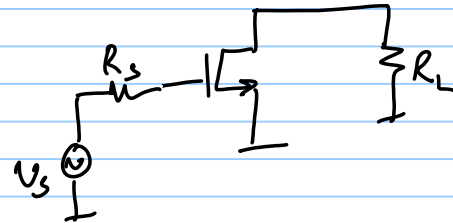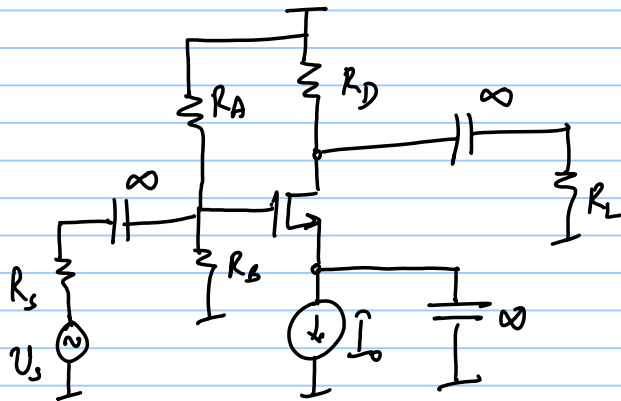
$$= \frac{V_{DD} \cdot R_B}{R_A + R_B} - \left(V_T + \sqrt{\frac{2 I_o}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} \right)$$




I_{D1}

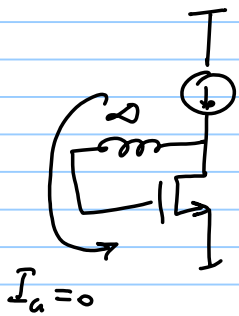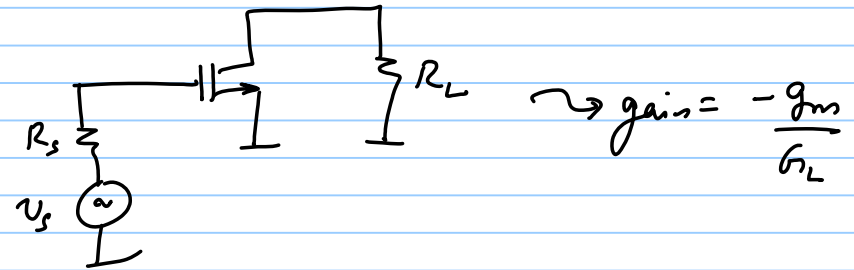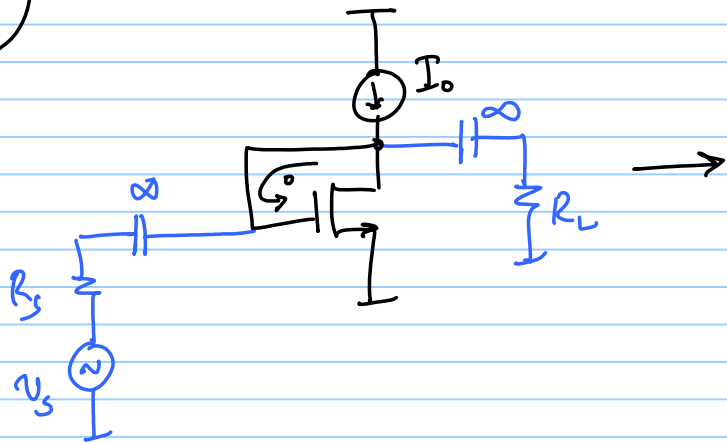

✓ L - large X

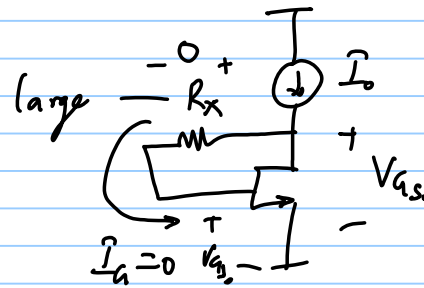

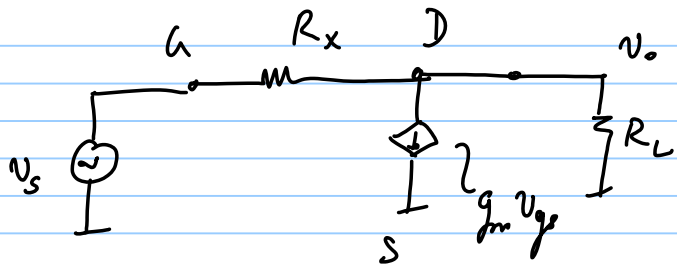

KCL @ D

$$(v_s - v_o) \cdot g_x = g_m v_s + v_o \cdot g_L$$

$$v_s (g_x - g_m) = v_o (g_x + g_L)$$

$$\frac{v_o}{v_s} = \frac{g_x - g_m}{g_x + g_L} \approx \left(-\frac{g_m}{g_L} \right) \underbrace{\left(\frac{1 - \frac{g_x}{g_m}}{1 + \frac{g_x}{g_L}} \right)}_{\approx 1}$$

$$\Rightarrow g_x \ll g_m \quad \& \quad g_x \ll g_L$$


$$R_x \gg 1/g_m \quad \& \quad R_x \gg R_L$$

$$|\text{gain}| = g_m R_L \gg 1$$

$$\Rightarrow R_L \gg 1/g_m$$

$R_x \gg R_L$

1.5

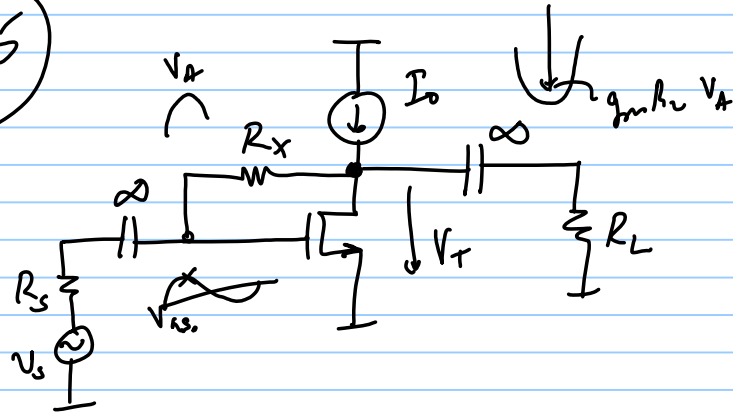

Swing limits?

(V_{as0}, V_{as})

Cut off limit = $\frac{I_0}{g_m}$


Triode limit: $\frac{V_T}{(1+g_m R_L)}$

1


Swing limits will be the same as original amplifier
 (V_{as0}, V_{as}) has not changed.

Cut off limit = $\frac{I_0}{g_m}$

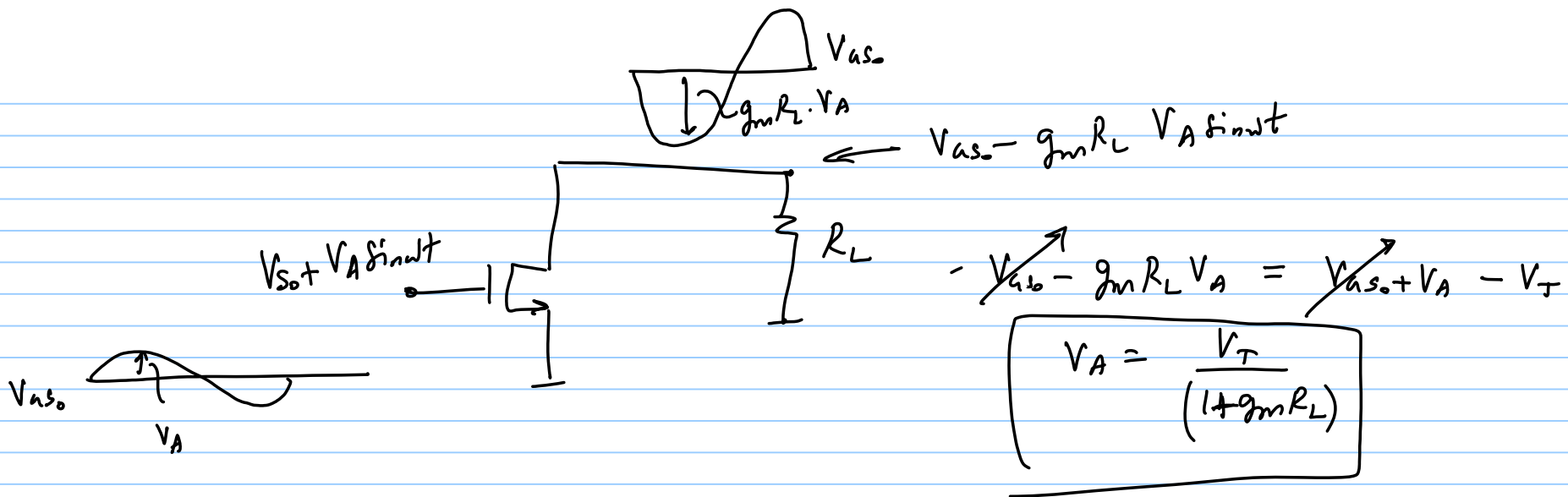Triode limit = $\frac{V_{DS0} - (V_{as0} - V_T)}{1 + g_m R_L}$ }



II

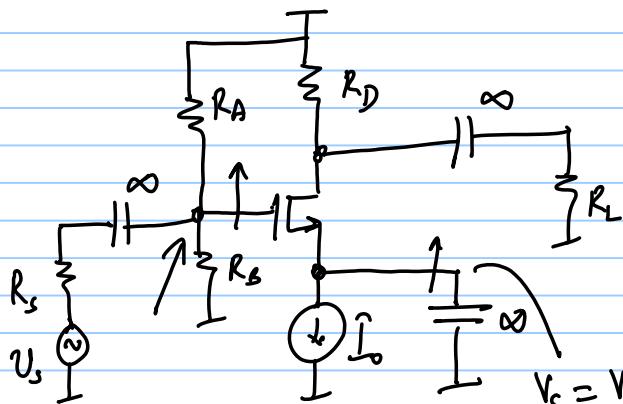

Swing limits

Cut off limit $= \frac{I_0}{g_m}$

Triode limit: $V_D = V_a - V_T$


$$\left. \begin{aligned} V_D - V_s &= V_a - V_s - V_T \\ V_{DS} &= V_{as} - V_T \end{aligned} \right\}$$

$$\underbrace{\frac{V_{DD} \cdot R_B}{R_A + R_B}}_{V_{u0}} + \underbrace{V_A \sin \omega t}_{v_s} - V_T = (V_{DD} - I_D R_D) - g_m (R_D || R_L) \cdot V_A \sin \omega t$$

$$V_A (1 + g_m (R_D || R_L)) = \frac{V_{DD} \cdot R_A}{R_A + R_B} - I_D R_D + V_T$$

$$V_A = \frac{V_T + \left(\frac{V_{DD} \cdot R_A}{R_A + R_B} - I_D R_D \right)}{1 + g_m (R_D || R_L)} \quad \text{lower than case I}$$


$$\text{Case I: } V_A = \frac{(V_{DD} - I_D R_D) - \left(\sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L} \right)}} \right)}{1 + g_m (R_D || R_L)}$$

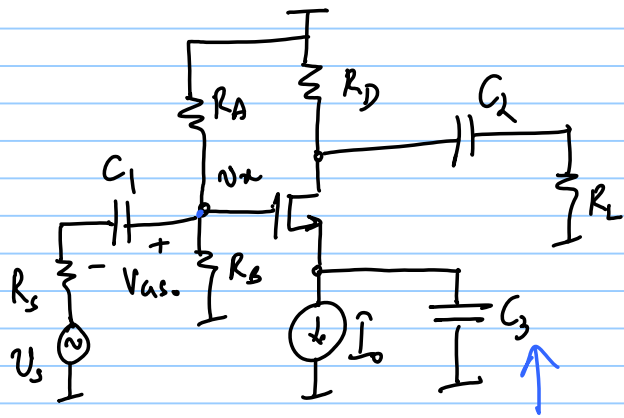

\$C_1\$: How large?


freq. \$\omega\$

$$Z_{C_1} = \frac{1}{j\omega C_1}$$

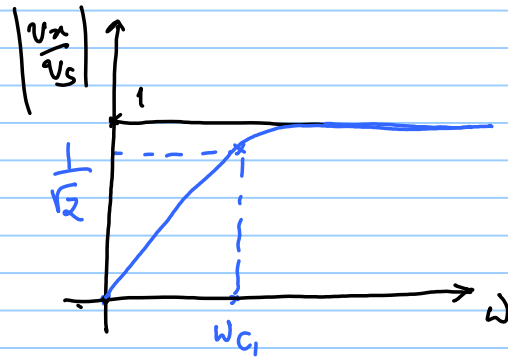

$$\omega_{C_1} = \frac{1}{C_1 (R_s + R_A || R_B)}$$

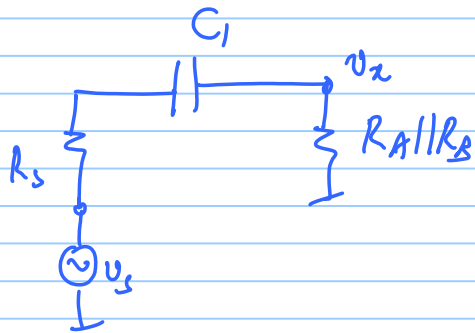$\omega_{C_1} \ll$ lowest frequency content of v_s



$$\frac{v_x}{v_s} = \frac{R_A || R_B}{R_s + R_A || R_B + \frac{1}{j\omega C_1}}$$

$C_{1 \text{ min}}$

5/9/17

Lec 8

* Quiz 3 - Nov. 19th 10:30am - noon

* Tutorial 2 - Due on 15th Sep. 2017

* Tutorial 1 discussion session with TAs - Friday 8th Sep. 4-5pm.

* Tutorial 2 " " " " - Friday 15th Sep. 5-6pm


Feedback Bias Stabilisation

Sensed: I_D , I_S } 4 ways of bias stab.
Controlled: V_u , V_S }

Sense $I_D \rightarrow$ Drive $V_u \rightarrow$ Case I


Sense $I_S \rightarrow$ Drive $V_s \rightarrow$ Case II

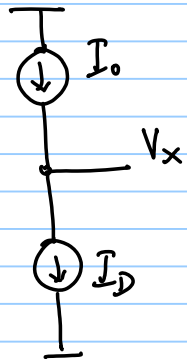Case II Sense $I_D \rightarrow$ Drive V_s



If $I_D > I_0$; $V_x \downarrow$ (we want $V_s \uparrow$)

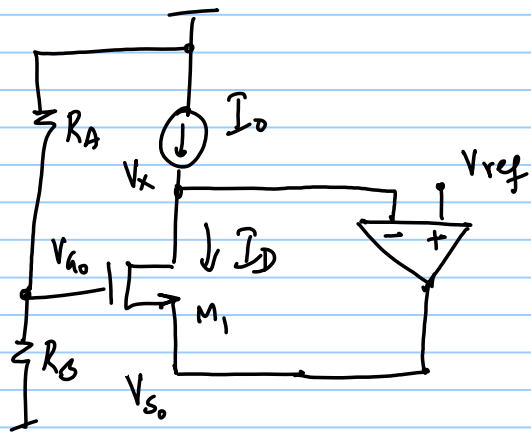
If $I_D < I_0$; $V_x \uparrow$ (we want $V_s \downarrow$)



V_{ref} chosen such that M_1 is well into the saturation region


$$V_{gs} = \frac{V_{DD} \cdot R_B}{R_A + R_B} ; I_D = I_0$$
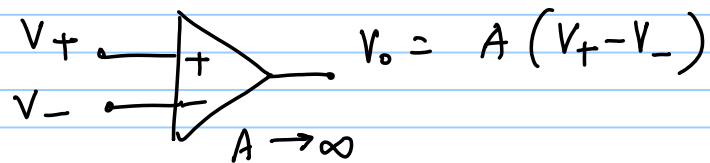
$$V_{s0} = V_T + \sqrt{\frac{2I_0}{\mu_n C_{ox} \left(\frac{W}{L}\right)}}$$



$$Z_{in} = \infty$$

$$Z_{out} = 0$$

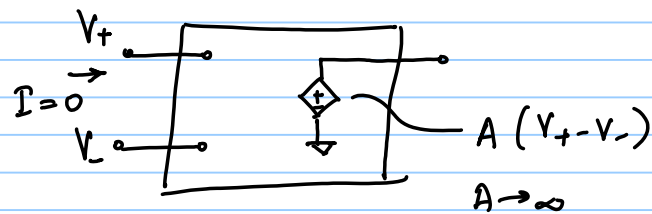

"Virtual Short" between + & - terminals


$$\left. \begin{array}{l} I_{in} = 0 \\ \text{but } V_+ = V_- \end{array} \right\} \text{Virtual Short}$$

only when opamp is placed in negative feedback


$$V_{Dsat} = \sqrt{\frac{2 I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} = V_{as} - V_T = V_{ov}$$


$$V_{S_0} = V_{G_0} - V_{as_0} = V_{G_0} - V_T - V_{Dsat}$$

$$V_{D_0} = V_x = V_{ref}$$

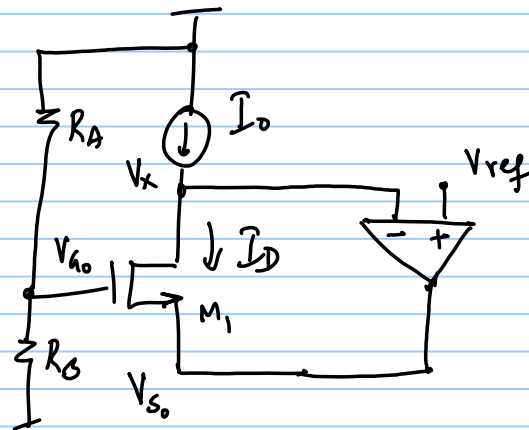


Small Signal picture

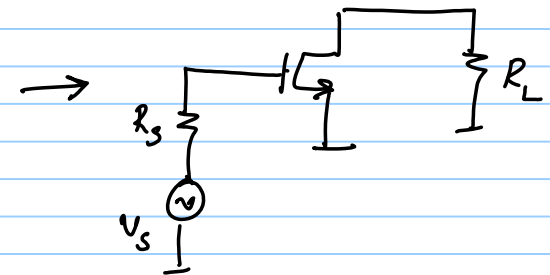

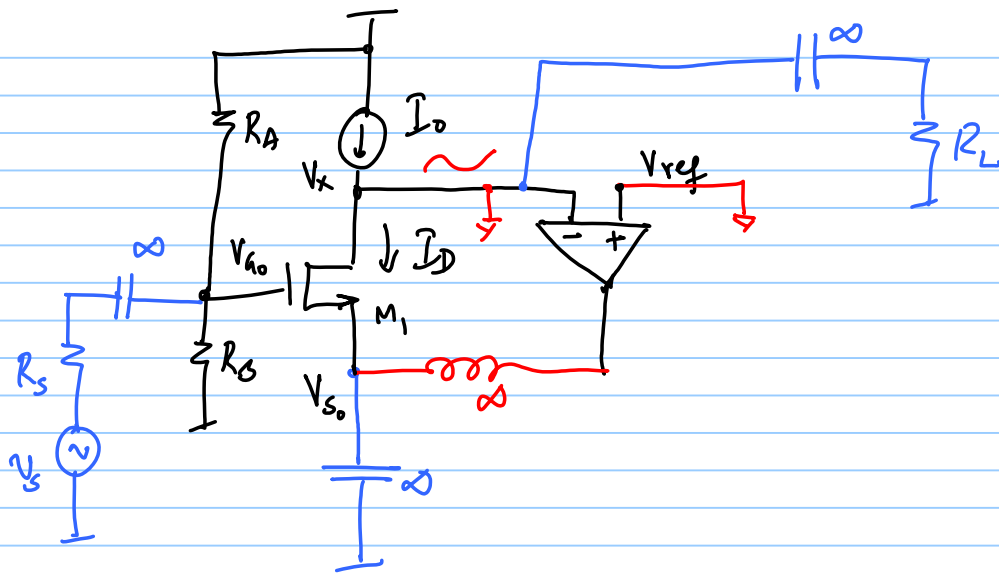

1) $L = \infty$ between opamp output & V_{s0} .

2) Use large R_x

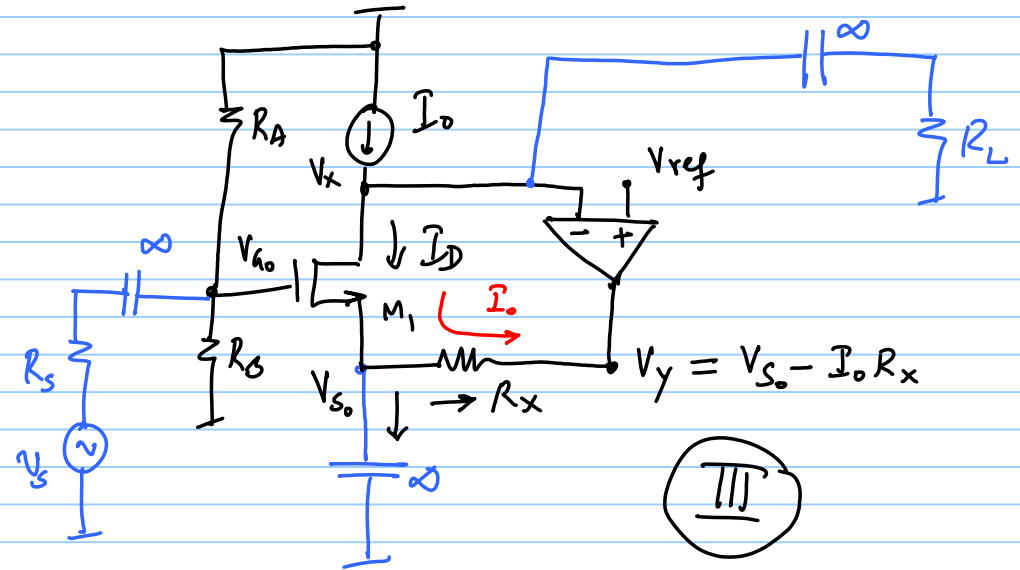


Case IV - HW

Swing limits for Cases III & IV - HW

Case IV - Sense I_s , Drive V_a



Negative feedback for AC

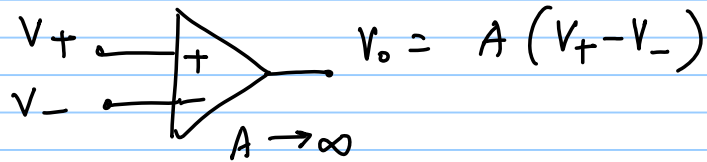

$Z_{in} = \infty$

$Z_{out} = 0$


Ideal VCVS with $A \rightarrow \infty$

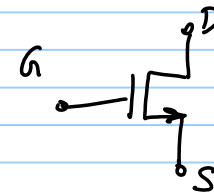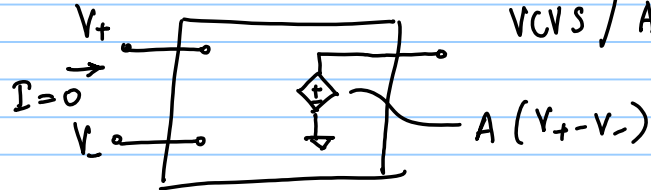


Ideal VCVS

$Z_{in} = \infty$

$Z_{out} = \infty$

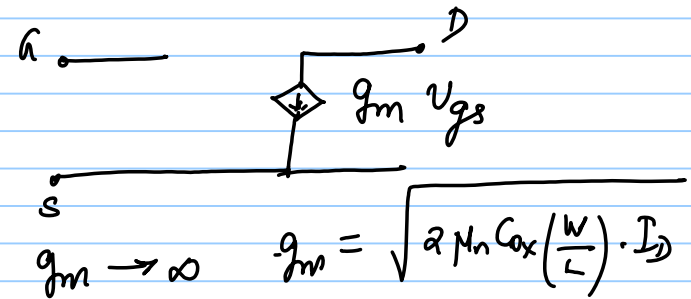

VCVS of gain = 1

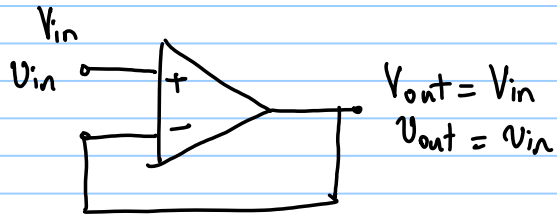

$$I_{in} = \infty$$

$$I_{out} = 0$$

$$V_{out} = V_{in}$$


$$v_{out} = v_{in}$$

MOSFET-based VCVS of gain = 1

Negative Feedback

- * Sense D & A values
- * Compare A with D
- * Drive $A \rightarrow D$


$$D = V_{in} ; A = V_{out}$$

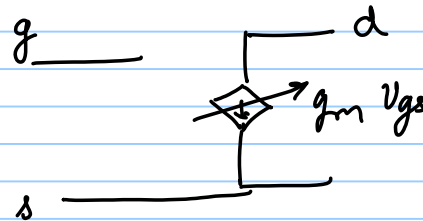

$\rightarrow i_d$ can be controlled through v_{gs}

v_{in} \uparrow
 \downarrow


v_x \uparrow
 \downarrow

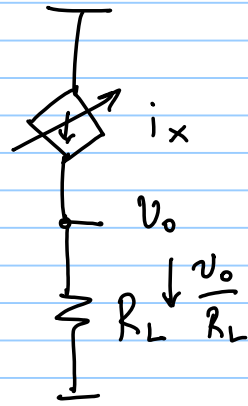


~~$v_o = i_x \cdot R_L$~~

$D = \frac{v_{in}}{R_L}$

$A = \frac{v_o}{R_L}$

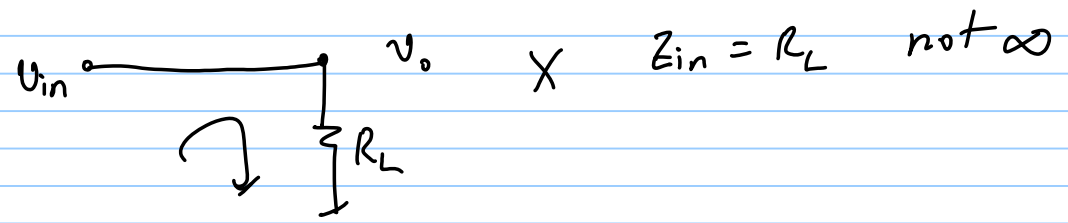

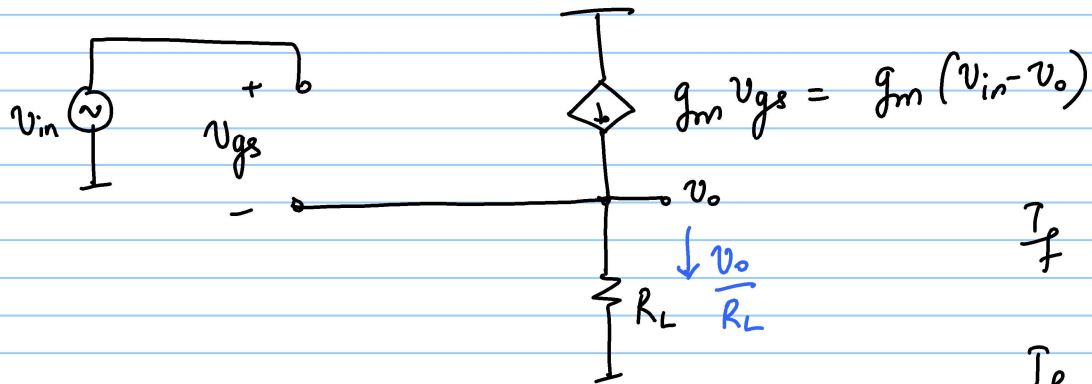

$$g_m (v_{in} - v_o) = \frac{v_o}{R_L}$$

$$v_{in} = v_o + \frac{v_o}{g_m R_L}$$

$$\uparrow \frac{v_o}{R_L} > g_m v_{gs} \Rightarrow v_o \downarrow \Rightarrow g_m v_{gs} \uparrow$$

$$\downarrow \frac{v_o}{R_L} < g_m v_{gs} \Rightarrow v_o \uparrow \Rightarrow g_m v_{gs} \downarrow$$

for $v_o = v_{in} \Rightarrow g_m \rightarrow \infty$

$$v_{in} = v_o \left(\frac{1 + g_m R_L}{g_m R_L} \right)$$

We actually want

$$g_m R_L \gg 1$$


i.e.

$$g_m \gg \frac{1}{R_L}$$

7/9/17


Lec 9

Case IV

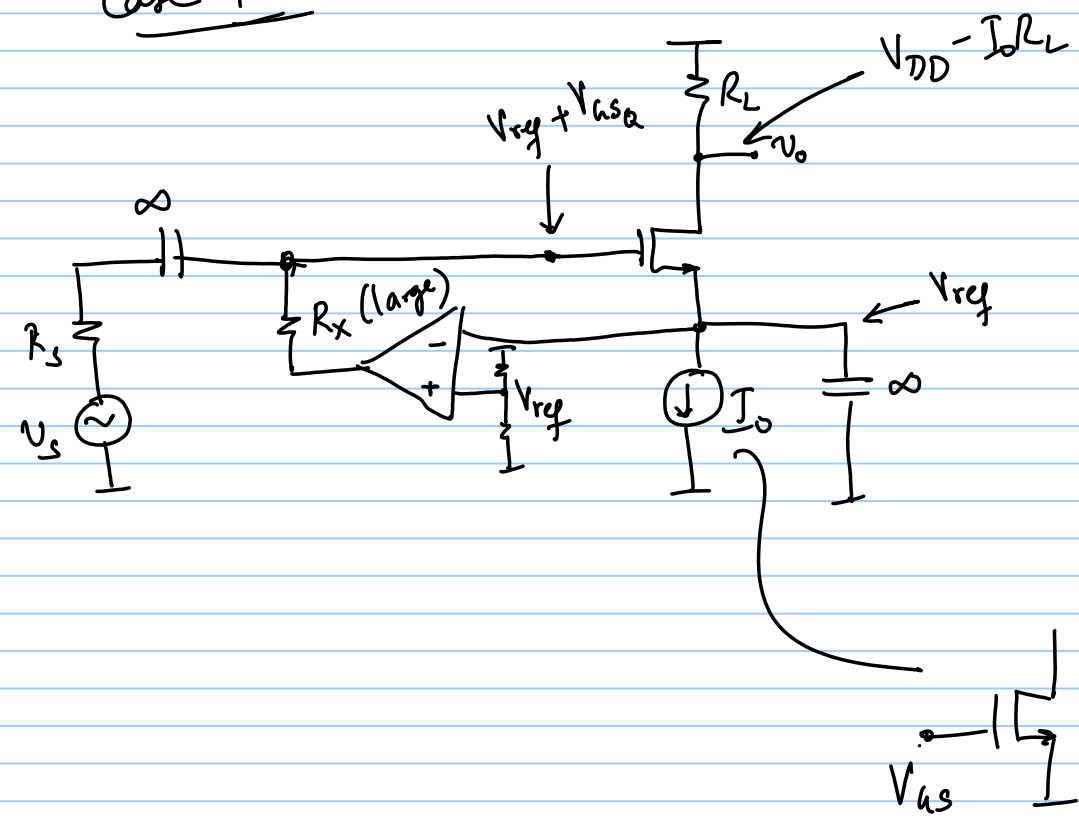


$$V_{gsQ} = V_T + \underbrace{\sqrt{\frac{2I_0}{\mu_n C_{ox} \left(\frac{W}{L}\right)}}}_{V_{Dsat,Q}}$$

$$\text{gain} = -g_m R_L$$

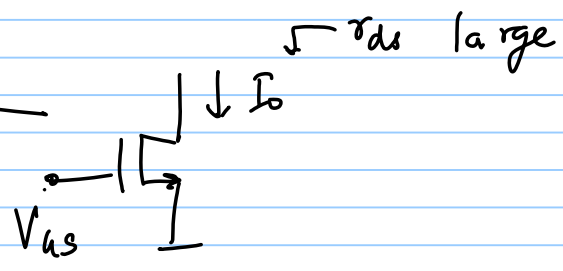

Replica
Biasing

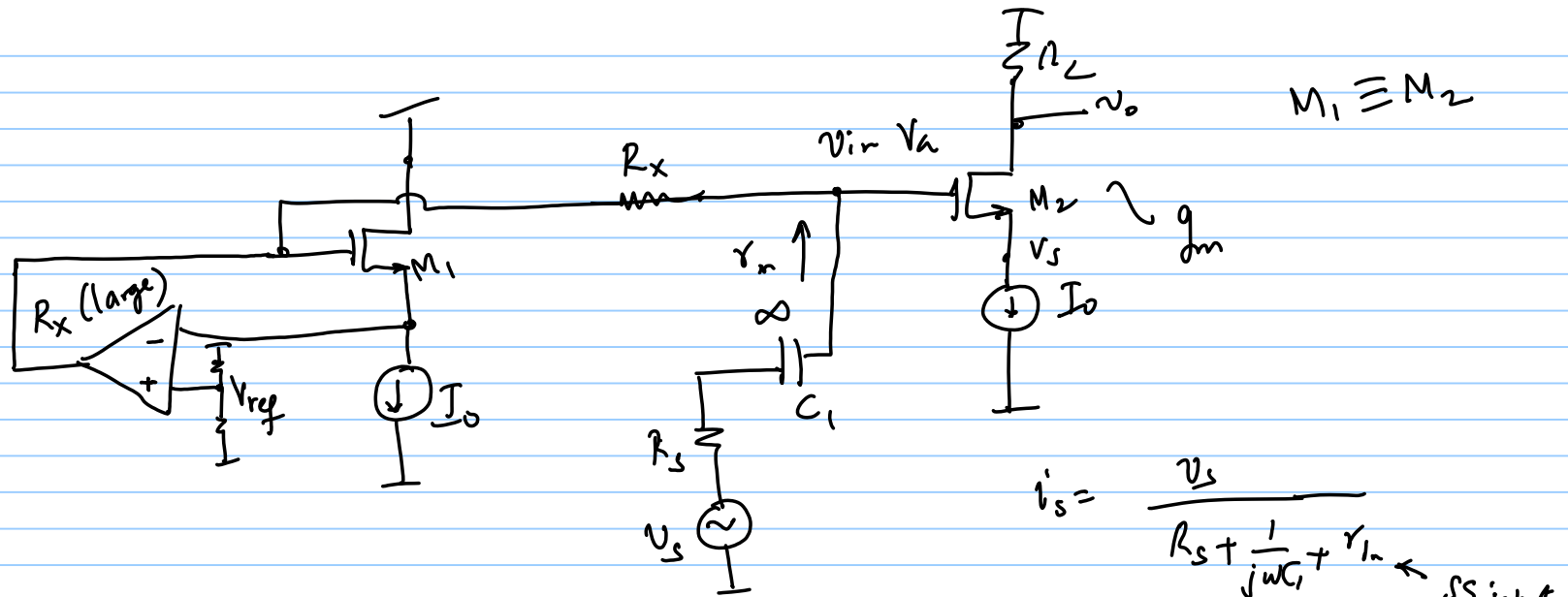

$$V_D = V_a - V_T$$


$$V_{D_0} + v_d = (V_{DD} - I_0 R_L) + (-g_m R_L) (v_a \sin \omega t)$$

$$i_s = \frac{v_s}{R_s + \frac{1}{j\omega C_1} + r_{in}}$$

SS input res.



$$i_s \times r_{in} = v_{in}$$

$$v_{in} \approx 0.99 v_s$$

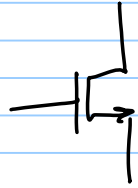


VCCs of gain = 1


$$v_o = v_{in}$$

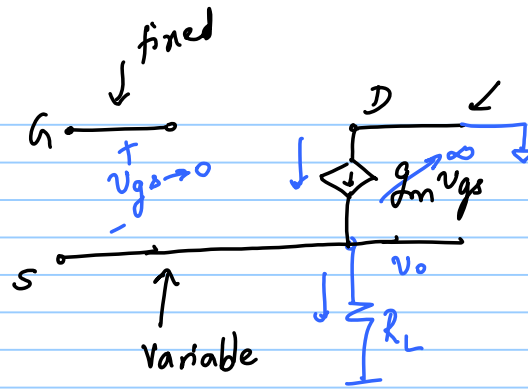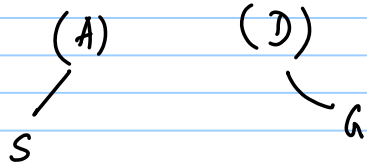

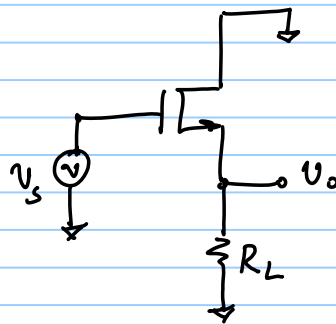If $g_m \rightarrow \infty \Rightarrow v_{gs} \rightarrow 0$
 with finite i_d
 when in -ve f.b.





signal picture only!

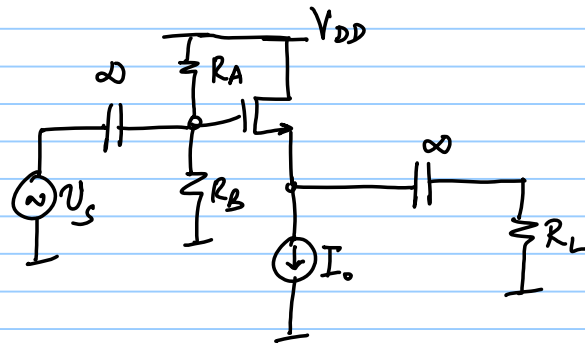

DC + AC

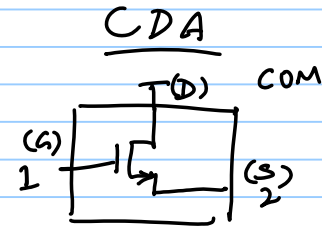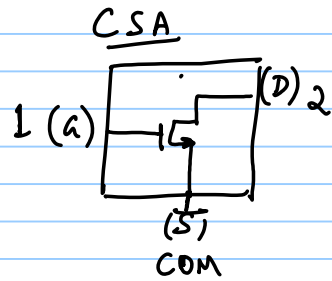"Common
Drain
Amplifier"
"Source
follower"



$$V_{GQ} = \frac{V_{DD} \cdot R_B}{R_A + R_B} ; \quad V_{DQ} = V_{DD} ;$$



$$V_{S,Q} = V_{GQ} - V_{GSQ} = V_{GQ} - V_T - V_{DSAT} \Big|_{I_o} ; \quad I_D = I_o$$


$$V_a = V_s + V_{as}$$

$Z_{in} = R_A || R_B$ should be much larger than R_s

$Z_{out} = \frac{1}{g_m} || r_{ds} \rightarrow 0$ if $g_m \rightarrow \infty$

$$\frac{V_o}{V_s} =$$

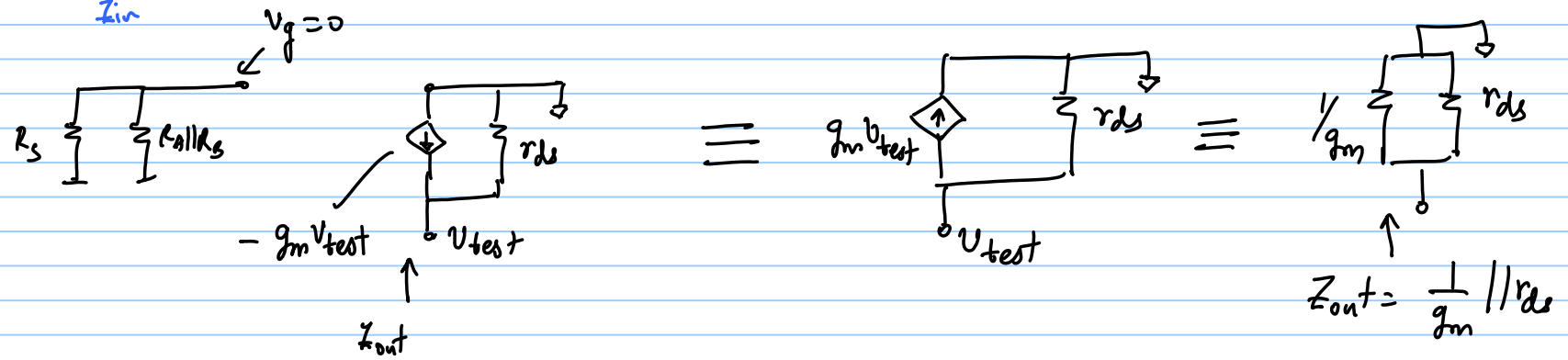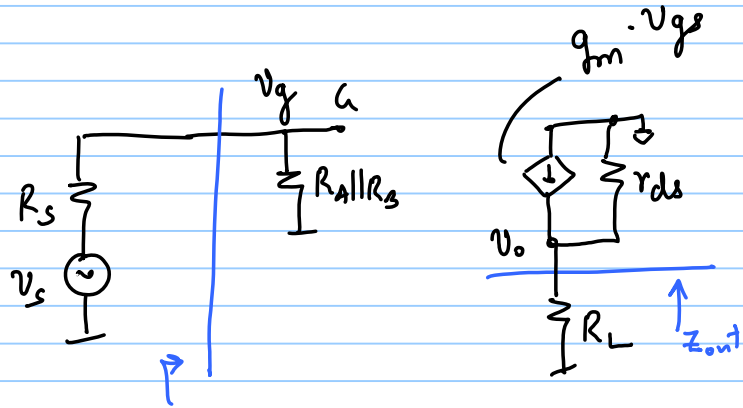

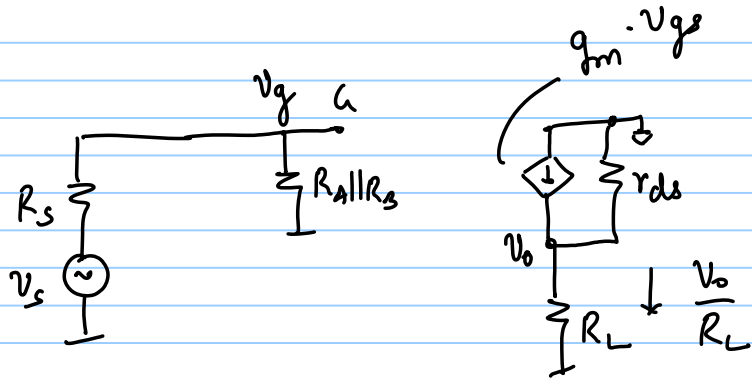

$$v_g \approx v_s$$

KCL @ Source :

$$g_m \cdot v_{gs} = (g_L + g_{ds}) \cdot v_o$$

$$g_m (v_s - v_o) = (g_L + g_{ds}) \cdot v_o$$

$$g_m v_s = (g_m + g_L + g_{ds}) \cdot v_o$$

$$\frac{v_o}{v_s} \rightarrow 1 \text{ if } g_m \rightarrow \infty$$

$\frac{v_o}{v_s}$ slightly less than 1 in practice

$$\Rightarrow \boxed{\frac{v_o}{v_s} = \frac{g_m}{g_m + g_L + g_{ds}}}$$

$$\frac{v_o}{v_s} = \frac{g_m}{g_m + g_L} = \frac{g_m R_L}{1 + g_m R_L} \rightarrow 1 \text{ if } g_m R_L \gg 1$$

Swing limits

$$v_s = V_A \sin \omega t$$

Cut off

$$I_D = \underbrace{I_a}_{I_0} + id \quad \rightarrow \quad \frac{v_o}{R_L} = \frac{1}{R_L} \cdot \frac{g_m R_L}{1 + g_m R_L} \cdot v_s$$

$$I_D = 0 \Rightarrow I_0 = \frac{1}{R_L} \cdot \frac{g_m R_L}{1 + g_m R_L} \cdot V_{A1}$$

$$\Rightarrow \boxed{V_{A1} = I_0 R_L \left(1 + \frac{1}{g_m R_L} \right)}$$

Triode

$$V_D = v_a - V_T$$

$$V_{DD} = \frac{V_{DD} \cdot R_B}{R_A + R_B} + V_{A2} \sin \omega t - V_T$$

$$V_{A2} = \frac{V_{DD} \cdot R_A}{R_A + R_B} + V_T$$


$$V_a = V_{a,Q} + v_g$$


↑
total, instantaneous

$$V_{A,max} = \min. \{ V_{A1}, V_{A2} \}$$

$V_{as,\alpha}$ →

* VCCS?

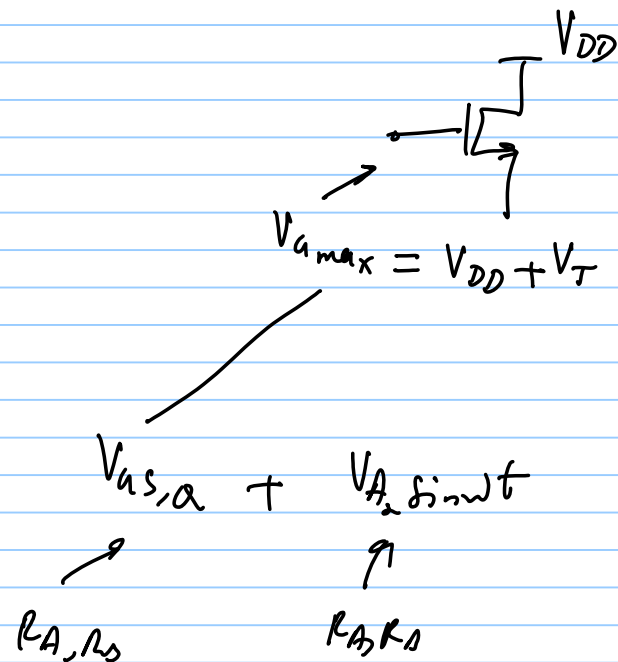

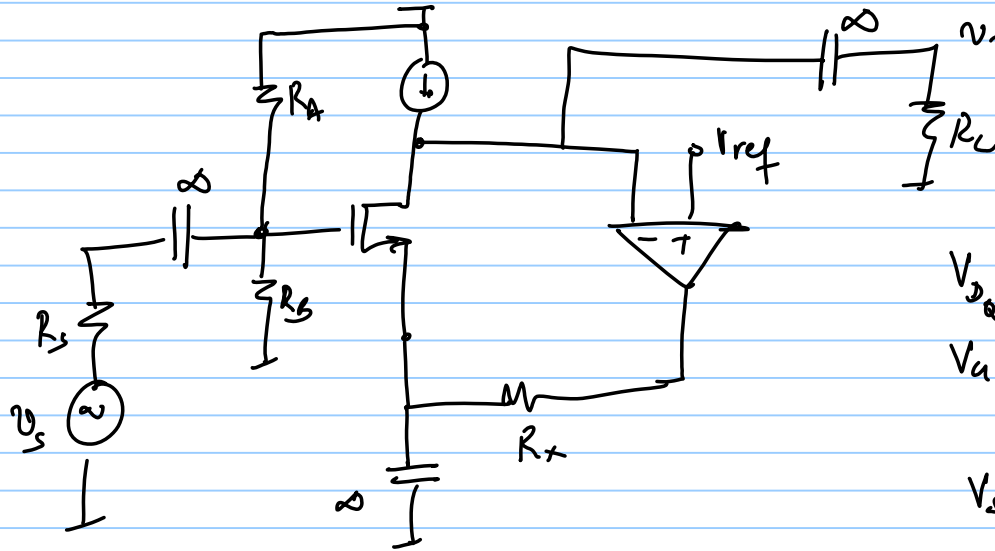

$$V_{DQ} = V_{ref}$$

$$V_{A_Q} = \frac{R_B}{R_A + R_B} \cdot V_{DD}$$

$$V_{S_Q} = V_{A_Q} - V_{GS_Q}$$

Triode : $V_D = V_A - V_T$


$$V_{ref} - g_m R_L V_{A_1} = V_{A_2} + V_{A_1} - V_T$$

$$V_{A_1} = \frac{V_{ref} - V_{A_2} + V_T}{1 + g_m R_L}$$

Cutoff

$$I_D = I_{D_2} + i_d = 0$$

$$V_{A_2} = \frac{I_D}{g_m}$$

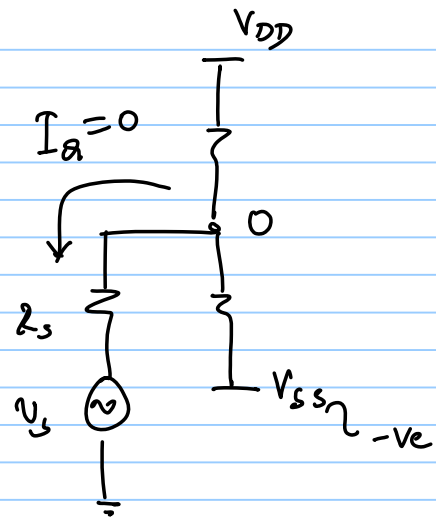

12/9/17

Lec 10

large I_D
 $(V_{GS} - V_T)$ small \leftarrow large $\left(\frac{W}{L}\right)$


$$g_m = \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right) I_D}$$

VCCS of gain $\frac{1}{R}$

$$i_{out} = \frac{V_{in}}{R}$$




$$Z_{in} = \infty$$

$$Z_{out} = \infty$$

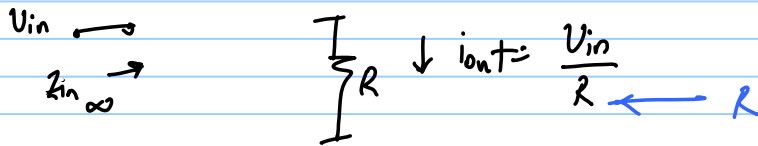



$$r_{ds} \neq \frac{V_{DSQ}}{I_{DQ}}$$


$$r_{ds} = \frac{1}{\lambda I_D}$$

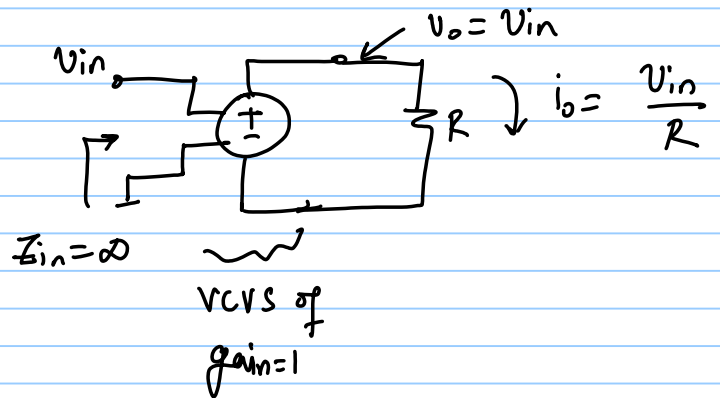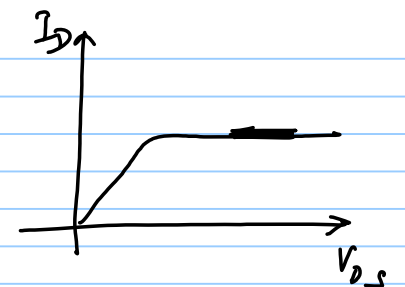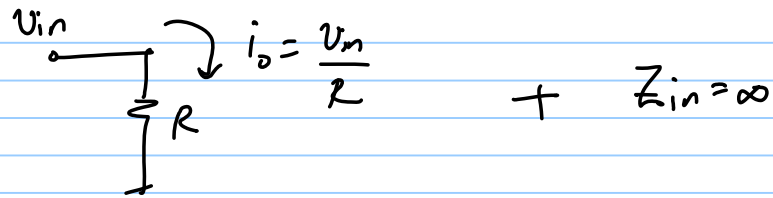


$Z_{out} = \infty$

$\frac{v_d}{i_d}$ large

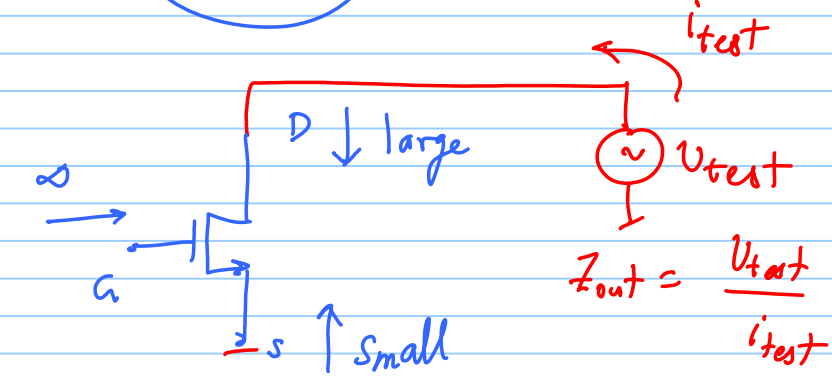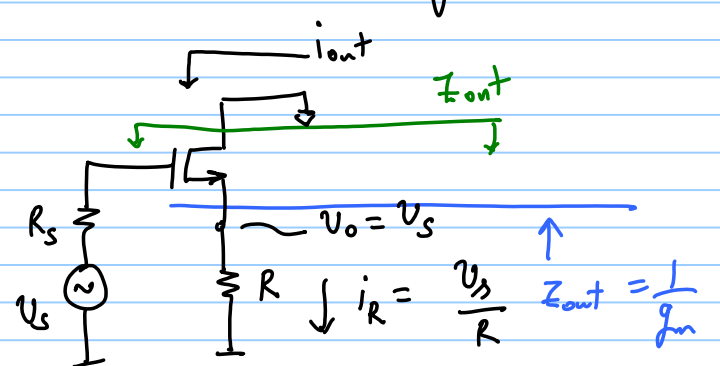

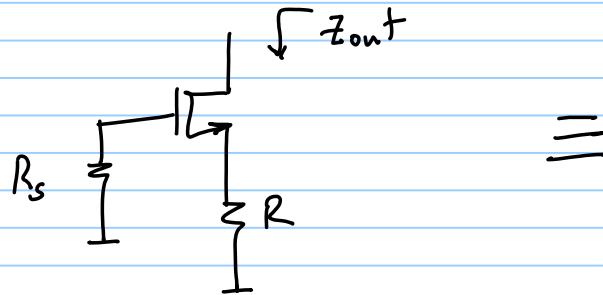

≡

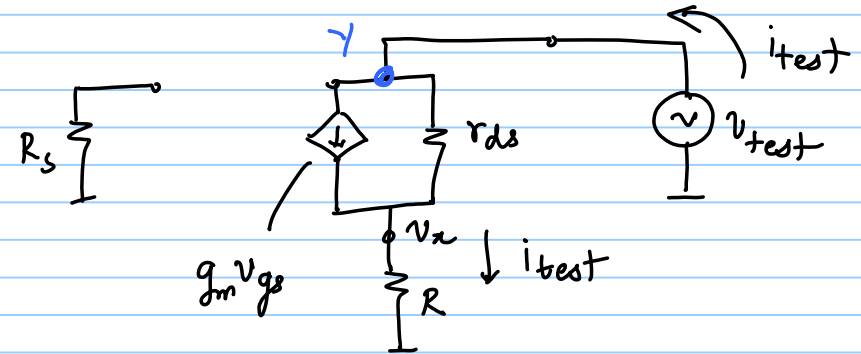


$$v_x = R \cdot i_{test} \quad ; \quad v_{gs} = -v_x$$

$$g_m v_{gs} + \frac{(v_{test} - v_x)}{r_{ds}} = i_{test} \quad \text{KCL @ node Y}$$

$$-g_m R i_{test} + g_{ds} v_{test} - g_{ds} R i_{test} = i_{test}$$

$$g_{ds} \cdot v_{test} = i_{test} (1 + g_m R + g_{ds} R)$$

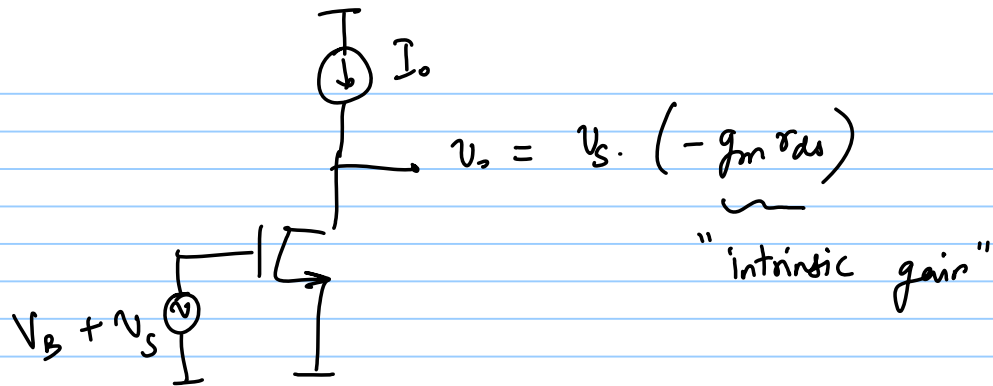
$$\frac{v_{test}}{i_{test}} = \underline{\underline{r_{ds} + g_m R \cdot r_{ds} + R}} = Z_{out}$$



$$z_{out} = r_{ds}$$



w/ -ve f.b: $z_{out} = (g_m R) r_{ds}$
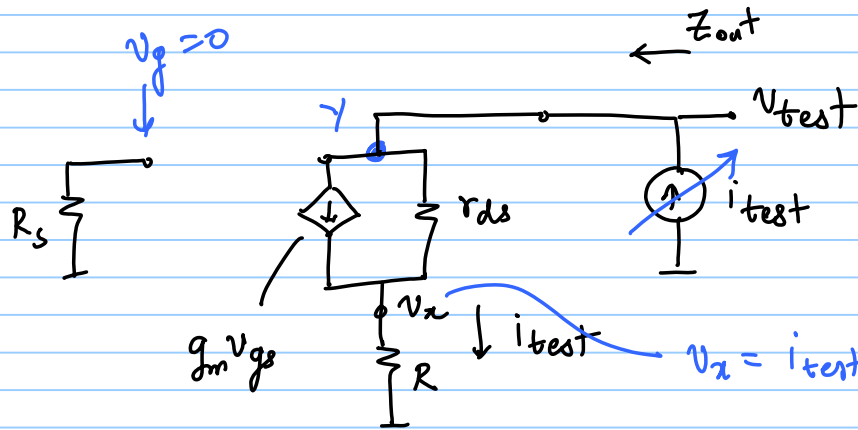
$$y_{22} = \lambda I_D \quad ; \quad r_{ds} = \frac{1}{y_{22}} = \frac{1}{\lambda I_D}$$



$v_x = i_{test} \cdot R \Rightarrow v_{gs} \downarrow \Rightarrow i_d \downarrow$ (negative f.b.)

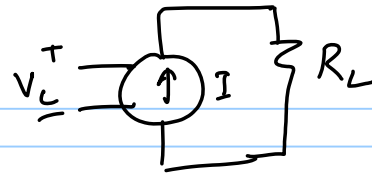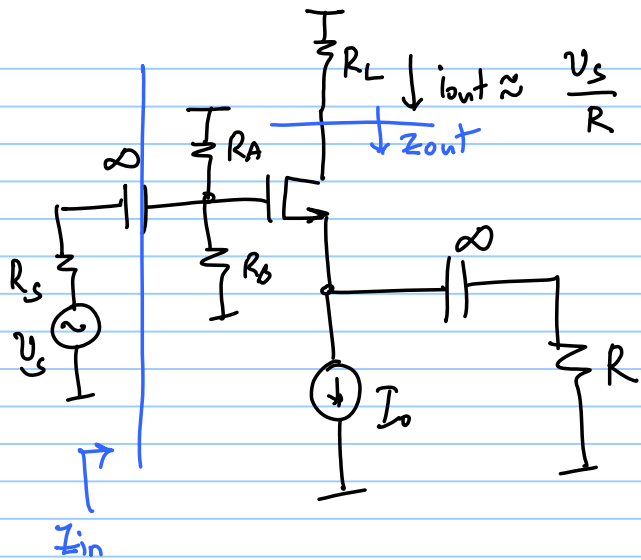
$$z_{out} = (g_m R) r_{ds} \quad (\text{very large}) \quad ; \quad z_{in} = R_A \parallel R_B \quad (\text{large})$$



$$i_{out} = \frac{g_m}{1 + g_m R} \cdot v_s$$

$$\approx \frac{1}{R} \cdot v_s \text{ if } g_m R \gg 1$$

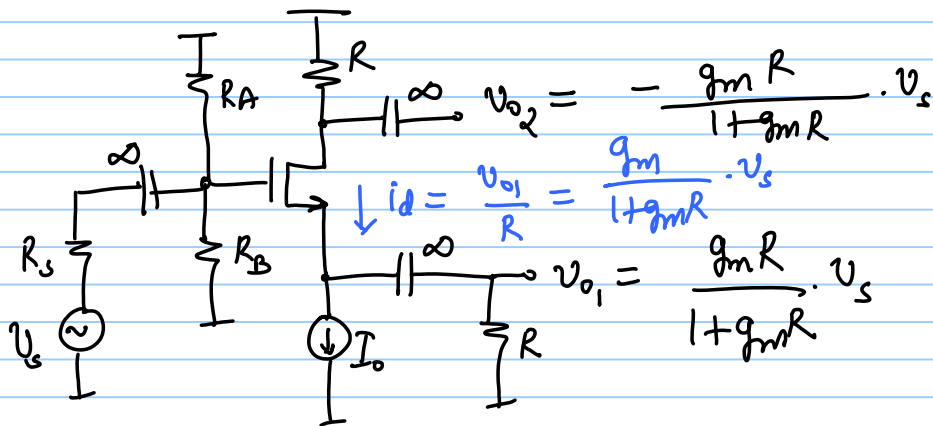"Trans admittance Amplifier"
 Swing limits - H.W.



"phase splitter"

$$v_{o1} = -v_{o2}$$

$$|v_{o1}| = |v_{o2}| \approx v_s$$

$$v_{o2} = -\frac{g_m R}{1 + g_m R} \cdot v_s$$

$$i_d = \frac{v_{o1}}{R} = \frac{g_m}{1 + g_m R} \cdot v_s$$


$$v_{o1} = \frac{g_m R}{1 + g_m R} \cdot v_s$$

CCCS of gain 1



$$i_{out} = i_{in}$$

$$Z_{in} = 0$$

$$Z_{out} = \infty$$

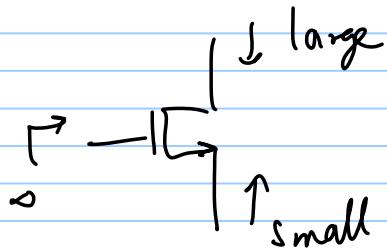
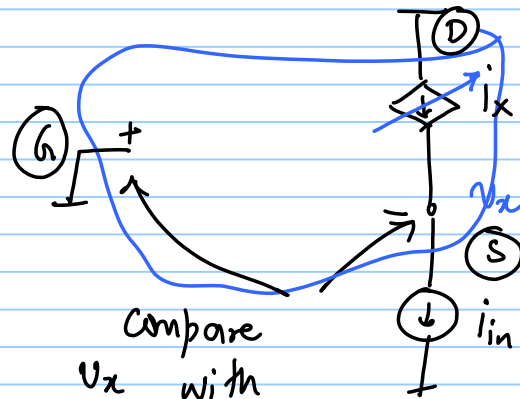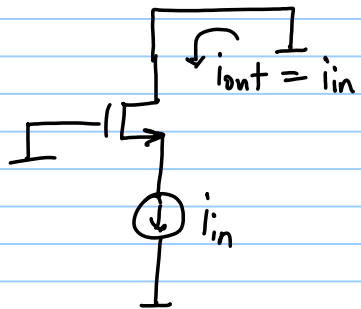
$$\text{If } g_m \rightarrow \infty \Rightarrow v_x \rightarrow 0$$



Compare v_x with signal ground

"Common gate amplifier"

$$i_{out} = i_{in}$$

Small signal quantities

If $i_x > i_{in} \Rightarrow v_x \uparrow$


If $i_x < i_{in} \Rightarrow v_x \downarrow$

If $i_x = i_{in} \Rightarrow v_x = 0$



$i_x = i_{out}$

14/9/17


Lec 11

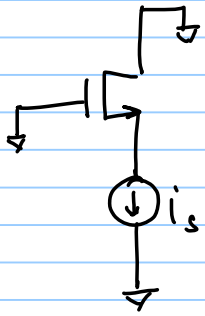


+ DC \Rightarrow

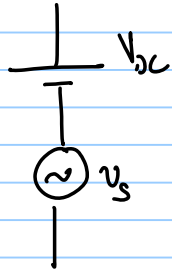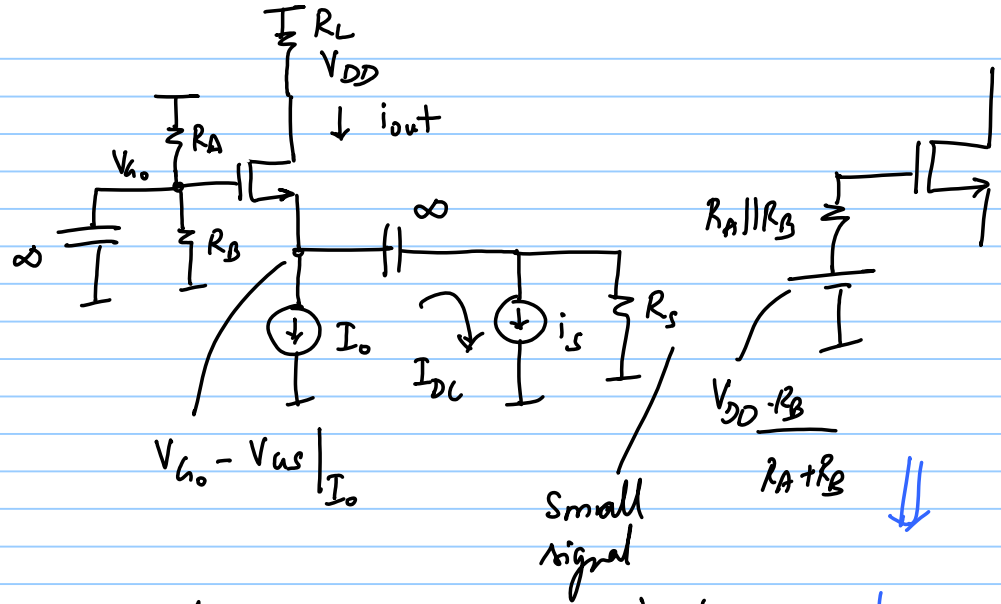


\equiv

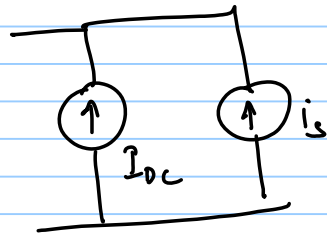

Small signal

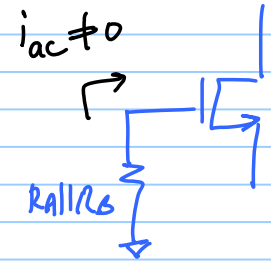


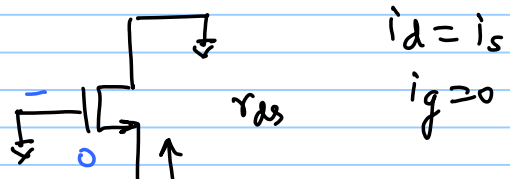


$$Z_{in} = \frac{1}{g_m} \parallel r_{ds}$$

↓
0 if $g_m \rightarrow \infty$

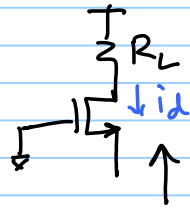* $Z_{in} = \frac{1}{g_m} \rightarrow 0$ if $g_m \rightarrow \infty$





$\frac{1}{g_m}$ if r_{ds} is ∞

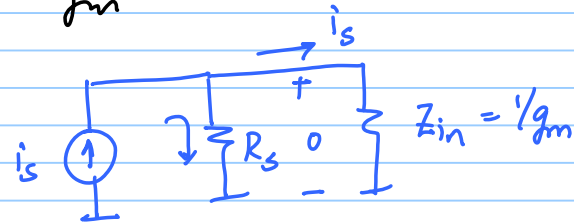

H.W.
analyse and determine
 Z_{in} if 1) $r_{ds} = \infty$
2) r_{ds} is finite

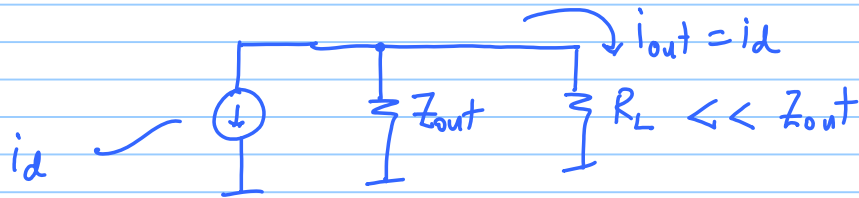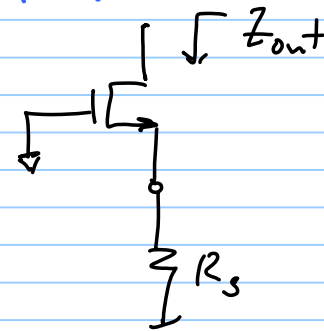* $Z_{out} = R_s + r_{ds} + g_m r_{ds} R_s \rightarrow \infty$ if $g_m \rightarrow \infty$




If $g_m \rightarrow \infty$, $i_{out} = i_{in}$


CCVS

$v_{out} = i_s \cdot R ; z_{in} = 0 ; z_{out} = 0$


$(v_o - i_s R) = 0$

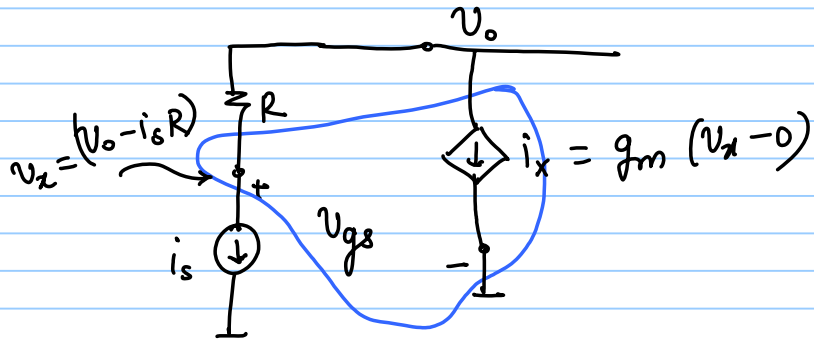


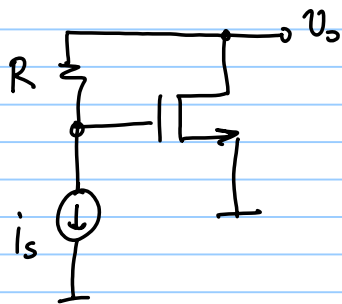If $g_m \rightarrow \infty \Rightarrow v_{gs} \rightarrow 0$ (-ve f.b.)
 $\Rightarrow v_x - 0 = 0 \Rightarrow v_o - i_s R = 0 \Rightarrow \boxed{v_o = i_s R}$




+ DC \Rightarrow

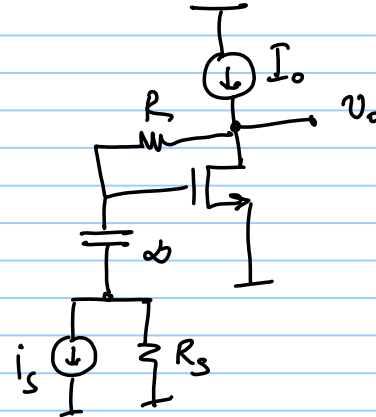


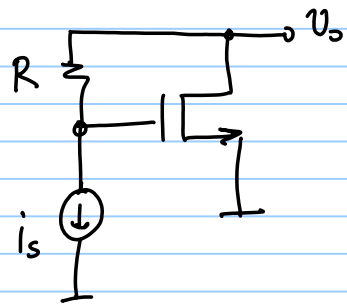



$$Z_{in} = \frac{1}{g_m}$$

$$Z_{out} = \frac{1}{g_m}$$

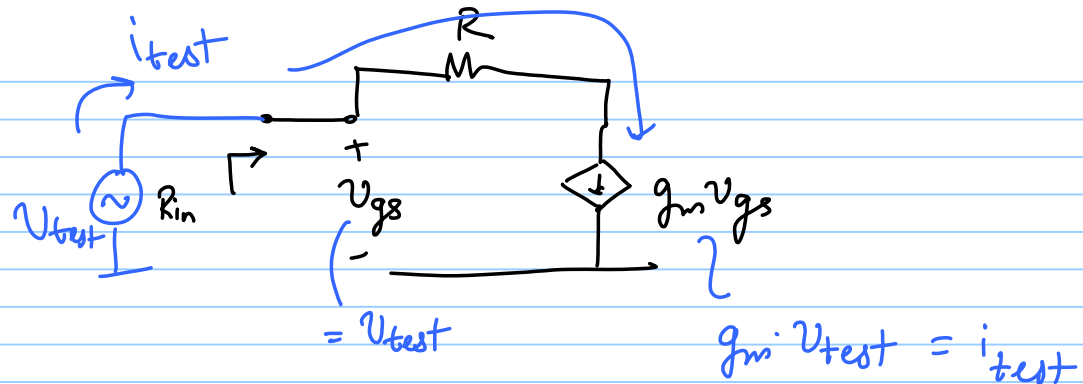
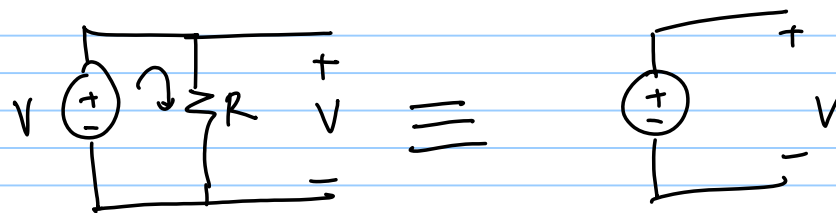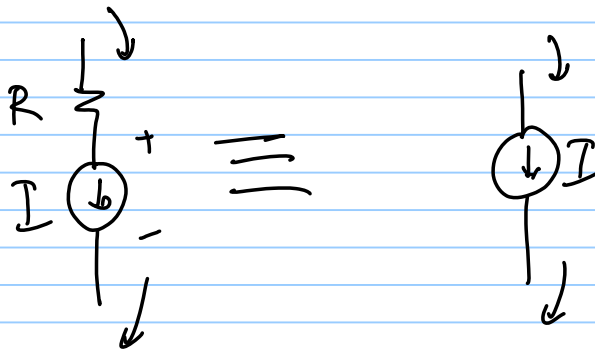
$$\Rightarrow \frac{v_{test}}{i_{test}} = \frac{1}{g_m}$$



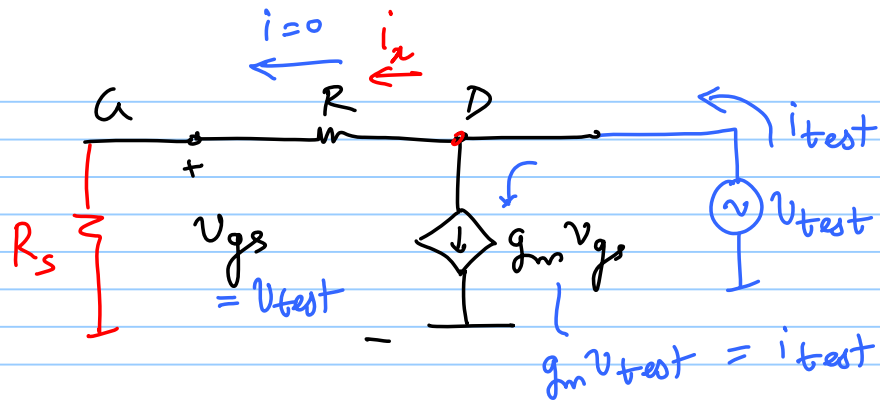

$$Z_{out} = \frac{1}{g_m}$$

$$V_{gs} = i_x \cdot R_s$$


$$i_{test} = i_x + g_m V_{gs} = i_x (1 + g_m R_s)$$


$$i_x = \frac{1}{1 + g_m R_s} \cdot i_{test}$$

$$V_{test} = i_x (R + R_s)$$

$$= \frac{R + R_s}{1 + g_m R_s} \cdot i_{test}$$
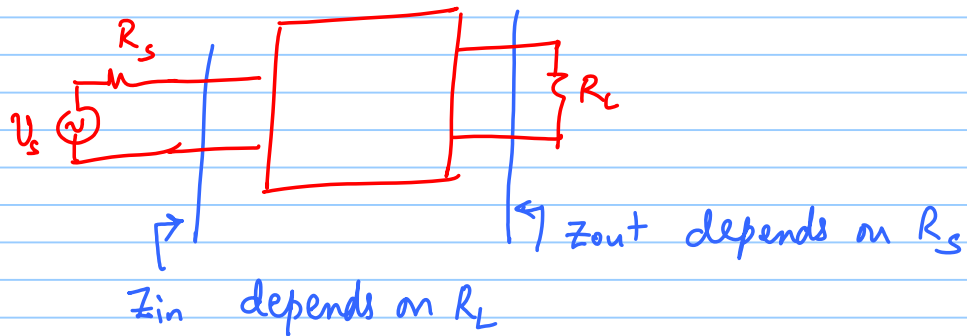
$$Z_{out} = \frac{V_{test}}{i_{test}} = \frac{R + R_s}{1 + g_m R_s}$$




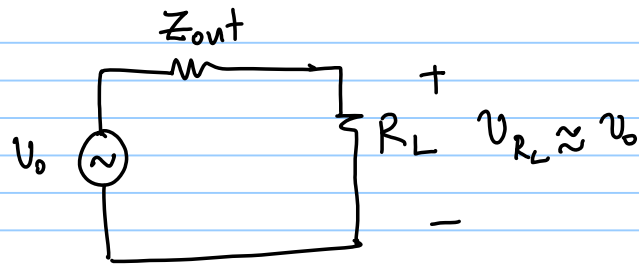


Choose g_m to be large enough such that



$$\frac{R + R_s}{1 + g_m R_s} \ll R_L$$

Z_{in} with R_L present - H.W. exercise


Swing limits

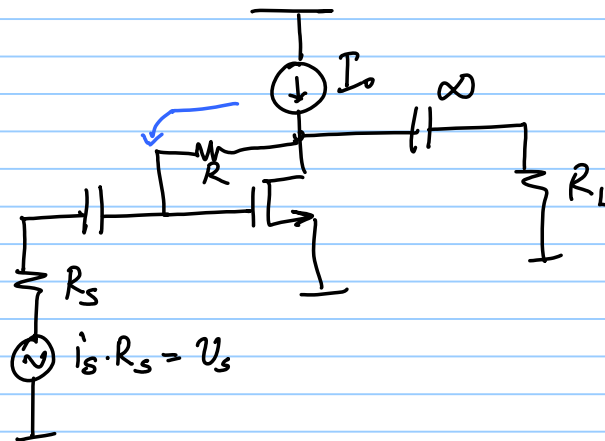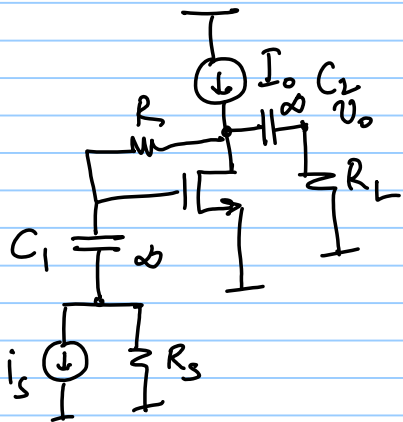




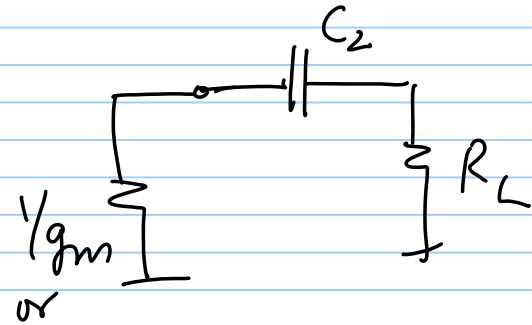
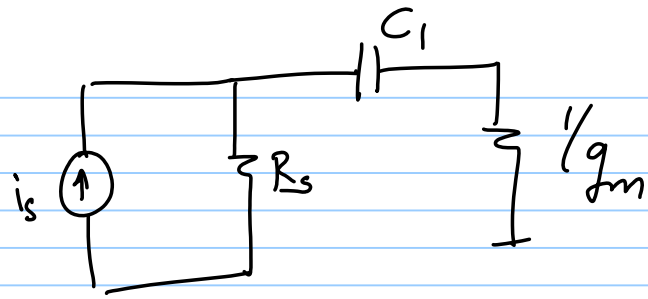
Case 1.5
 (V_{as_0}, V_{as_0}) is op. pt.




$$\frac{R + R_s}{1 + g_m R_s}$$

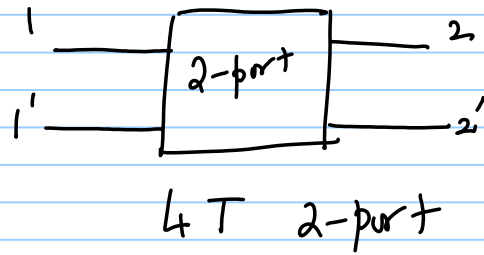

→

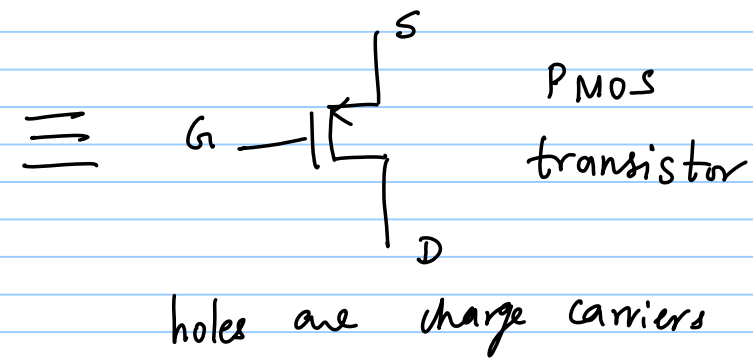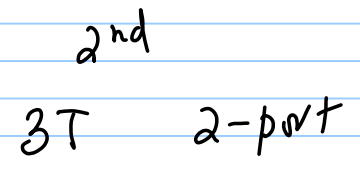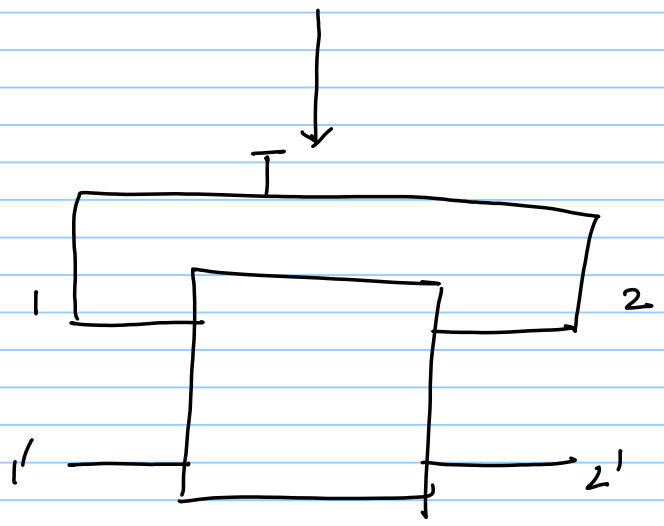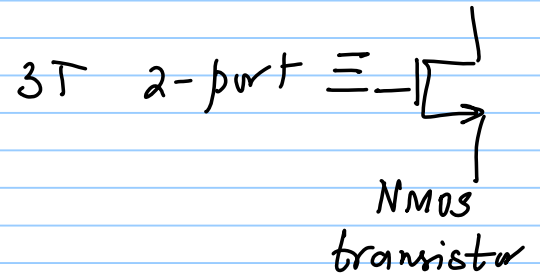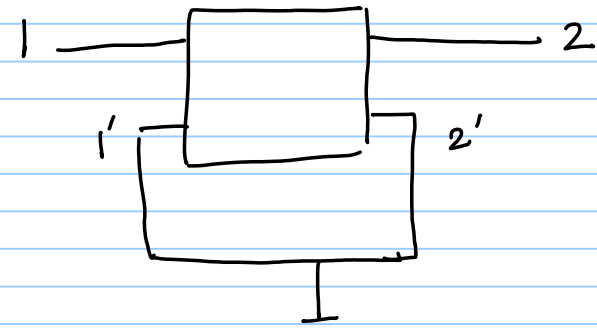


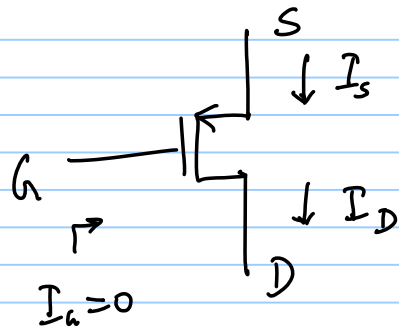


* current inside PMOS flows from $S \rightarrow D$

* $V_{SG}, V_{SD}, V_{TP} > 0$

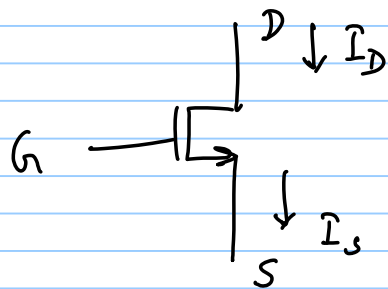* $V_{SG} > V_{TP}$ for device to conduct



$$I_D = \begin{cases} 0 & \text{if } V_{SG} < V_{TP} \\ \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_p (V_{SG} - V_{TP})^2 \cdot (1 + \lambda_p V_{SD}) & \text{if } V_{SG} \geq V_{TP} \\ & \text{and } V_{SD} \leq V_{SG} - V_{TP} \\ \mu_p C_{ox} \left(\frac{W}{L}\right)_p \left[(V_{SG} - V_{TP}) V_{SD} - \frac{V_{SD}^2}{2} \right] & \text{if } V_{SG} \geq V_{TP} \\ & \text{and } V_{SD} > V_{SG} - V_{TP} \end{cases}$$

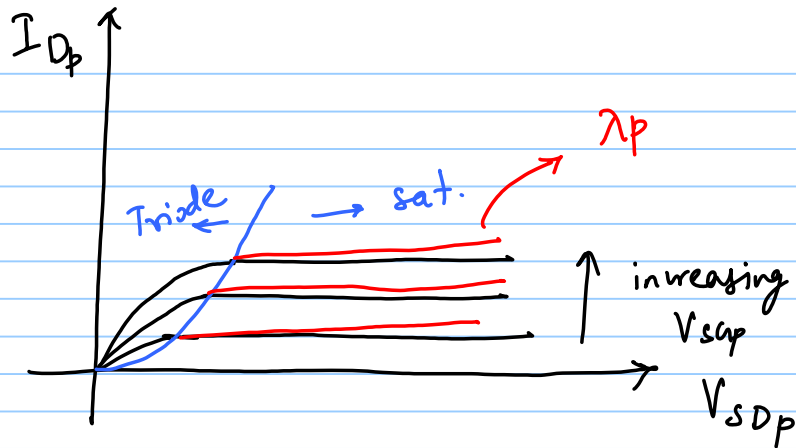

$$g_m = \mu_p C_{ox} \left(\frac{W}{L}\right)_p (V_{GS} - V_{Tp})$$

$$= \sqrt{2 \mu_p C_{ox} \left(\frac{W}{L}\right)_p \cdot I_{Dp}}$$



$$= \frac{2 I_{Dp}}{(V_{GS} - V_{Tp})}$$

Small-signal eq. ckt.

$$y_{11} = y_{12} = 0$$

$$y_{22} = \lambda_p \cdot I_{Dp} = \frac{1}{r_{dsp}}$$

$$y_{21} = \left. \frac{\partial I_{Dp}}{\partial V_{GS}} \right|_{op\ pt.} = g_m$$

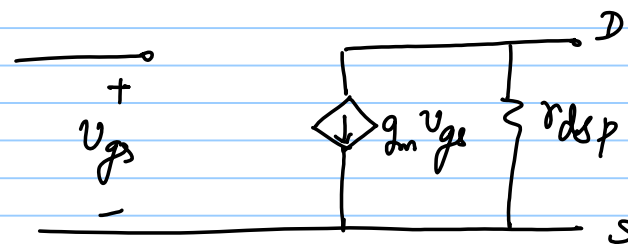
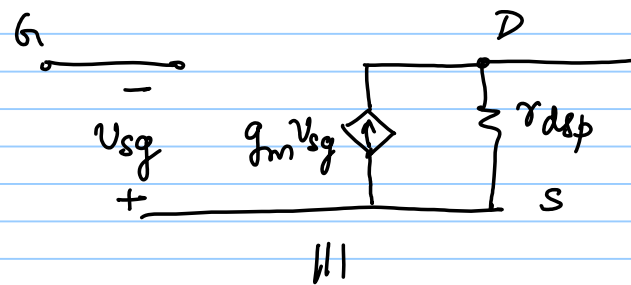


Same as that
for NMOS
transistor!



21/9/17

Lec 12

'D' C' feedback

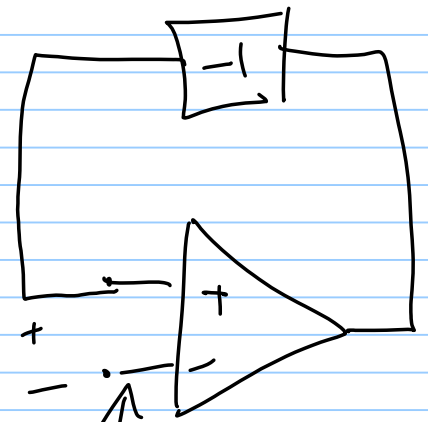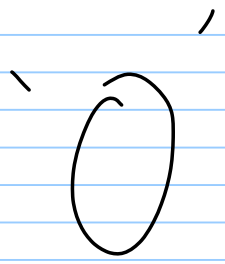


$$A (V_+ - V_-) = V_o$$

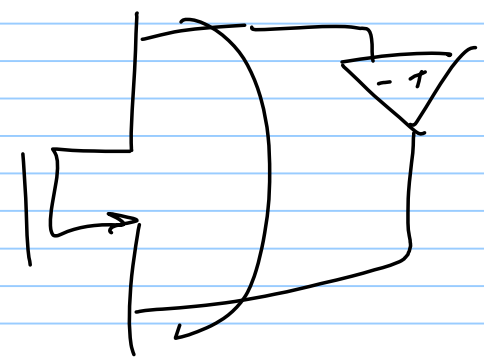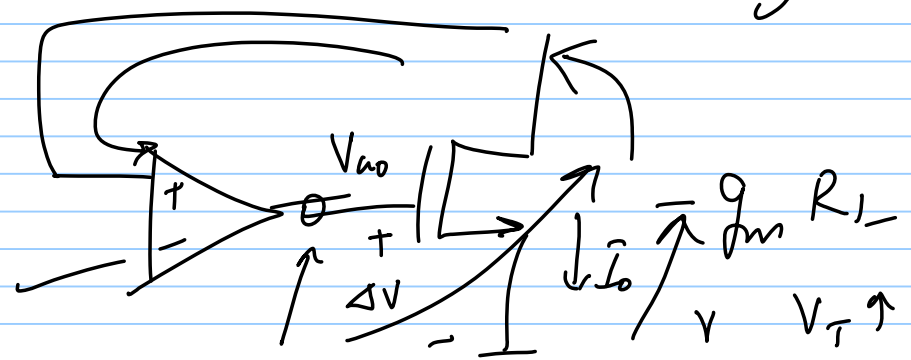

$$I_D = \frac{\beta_n}{2} (V_{as_0} - V_{T_0})^2$$


$$V_{T_0} \rightarrow V_{T_1}$$
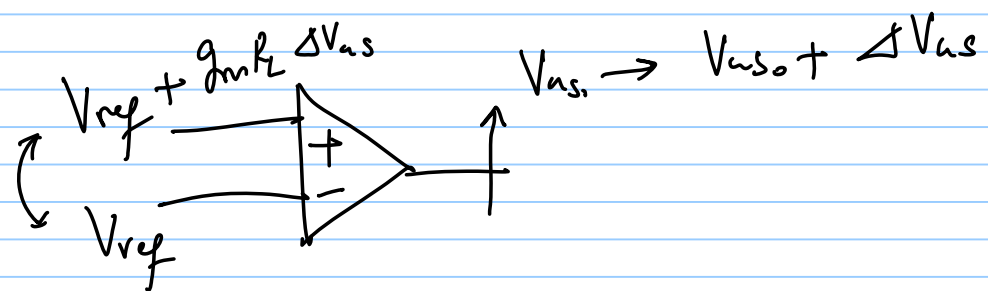
$$-\Delta V_{as} \xrightarrow{(V_{as})} -g_m \Delta V_{as} \xrightarrow{(I_D)} +g_m R_L \Delta V_{as} \xrightarrow{(V_o)}$$





Quiz 1 }
 Quiz 2 } scaled
 Quiz 3 } to
 } 50%.

Tutorials — 10%.
 Finals — 40%.

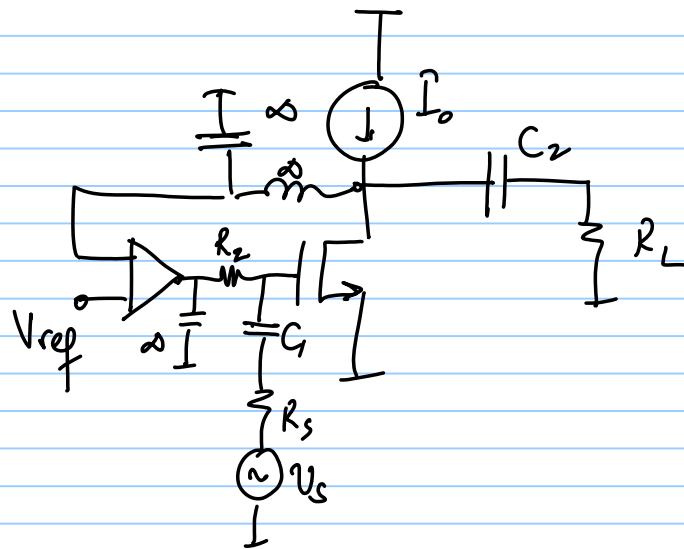

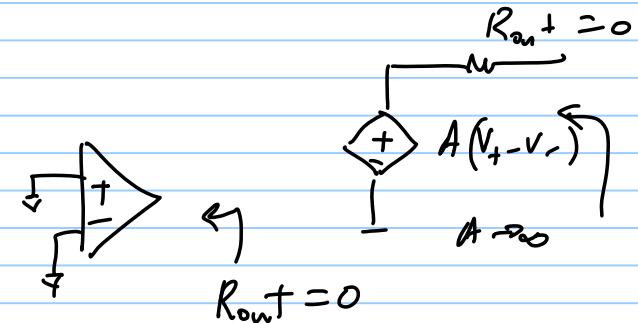Short all ind. ac sources
 open all caps, ac I sources




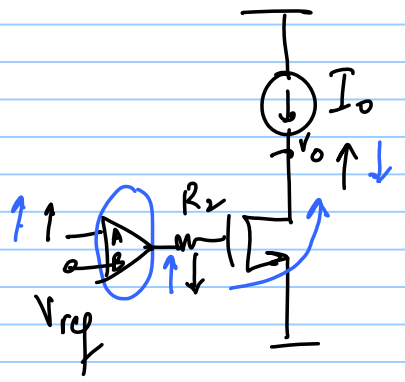





$A = -ve$
 $B = +ve$

$\left. \begin{array}{l} A = -ve \\ B = +ve \end{array} \right\} \text{+ve fb.}$

$A = +ve$
 $B = -ve$

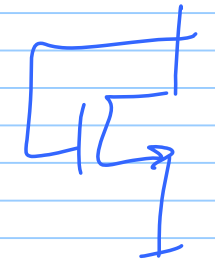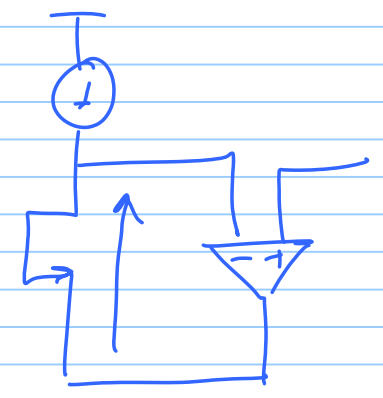$\left. \begin{array}{l} A = +ve \\ B = -ve \end{array} \right\}$ ✓



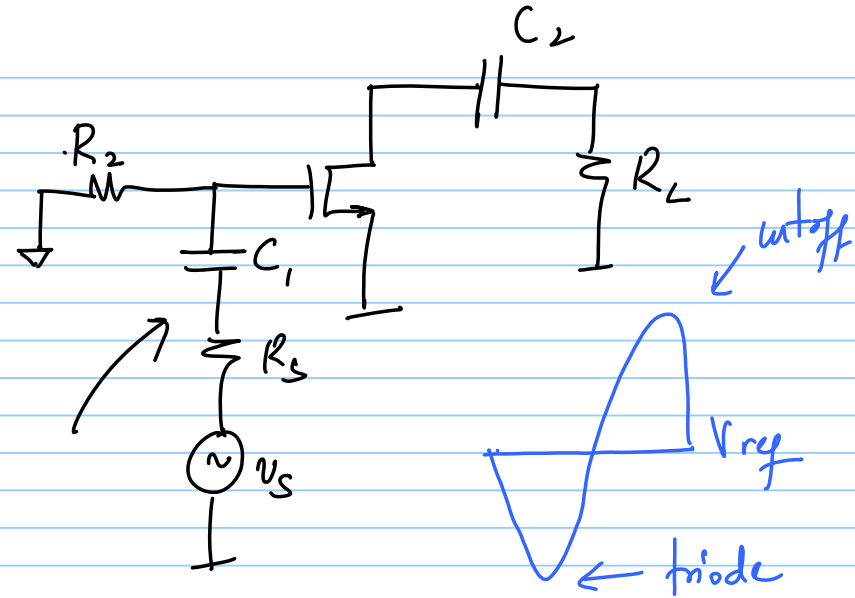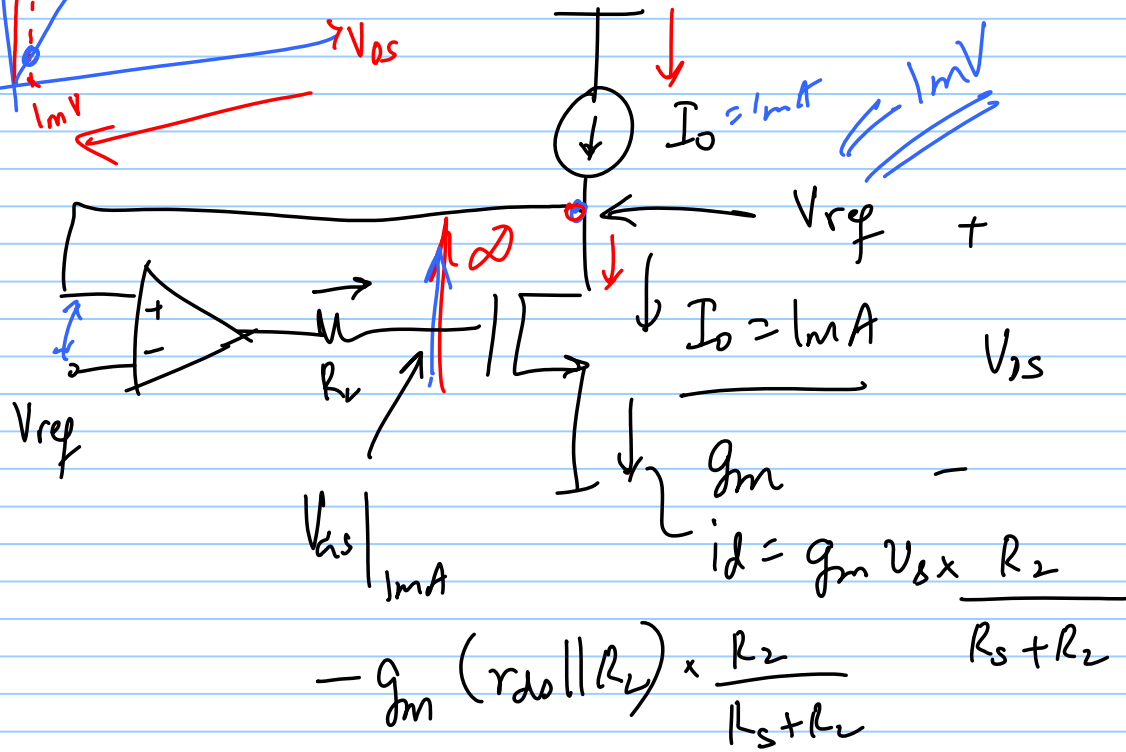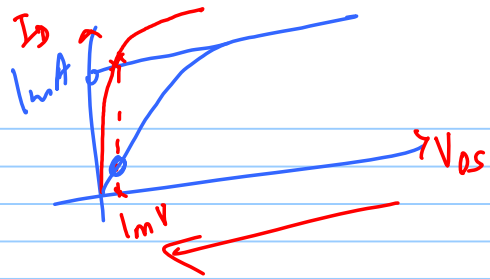

$$|i_d| = I_0$$

$$V_{A1} = \frac{I_D}{g_m \left(\frac{R_L}{R_S + R_L} \right)}$$

cut off limit = Triode limit

$$V_{rep} - g_m (r_{ds} \parallel R_L) \frac{R_2}{R_1 + R_2} V_{A_2} \sin \omega t = V_{as} + V_{A_2} \sin \omega t \cdot \frac{R_2}{R_1 + R_2} - V_T$$

$$r_{ds} = \frac{1}{\lambda I_D}$$


$$V_{as} = V_{as0} + V_{gs}$$


$$= V_{as0} + V_s \cdot \frac{R_2}{R_1 + R_2}$$

$V_A \sin \omega t$

Channel length modulation

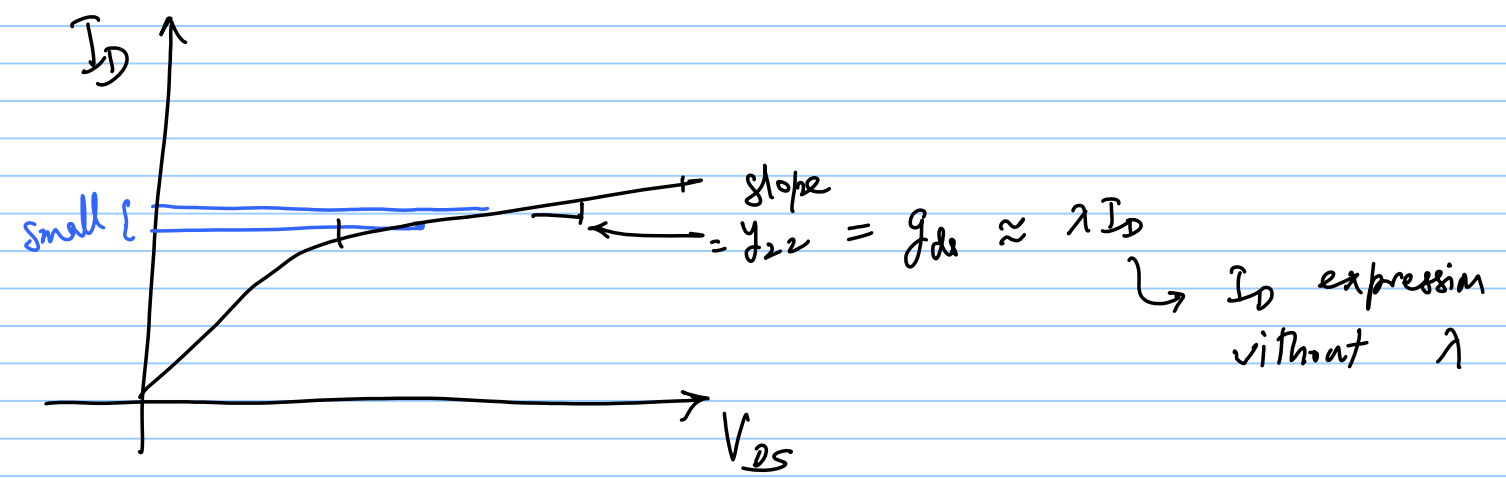- $\lambda \rightarrow$ do not use for op pt. calculations
- $\lambda \rightarrow$ use only to determine r_{ds}




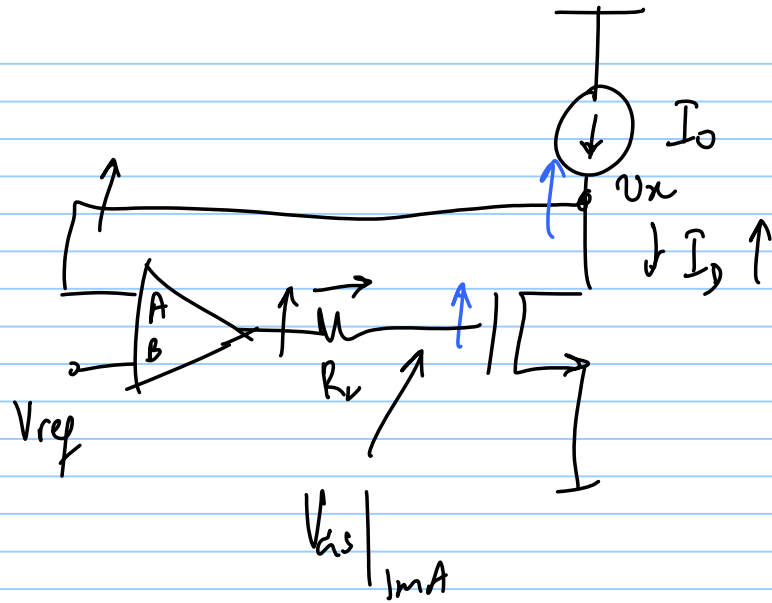


Let $I_0 < I_0 \Rightarrow v_x \uparrow$

we want $v_{gs} \uparrow \Rightarrow A = +ve$

PMOS Common Source Amplifier

op pt.

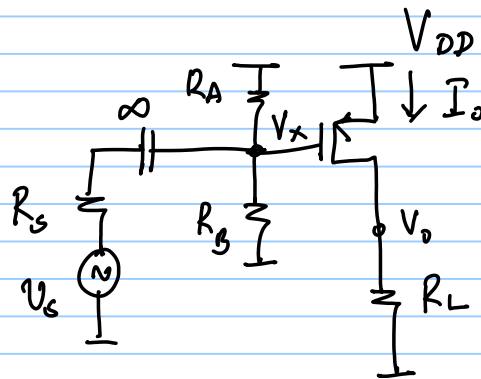
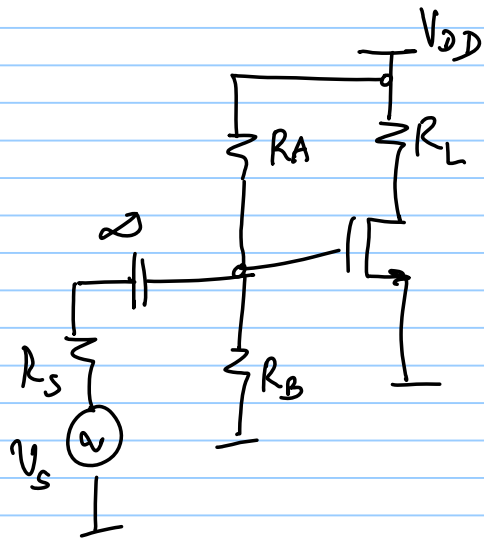


$$V_x = \frac{R_B}{R_A + R_B} \cdot V_{DD}$$

$$V_{gs0} = V_{DD} - V_x = \frac{R_A}{R_A + R_B} V_{DD}$$

$$I_o = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_p (V_{gs0} - V_{tp})^2$$

$$V_o = I_o \cdot R_L$$

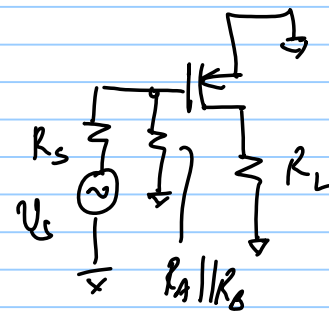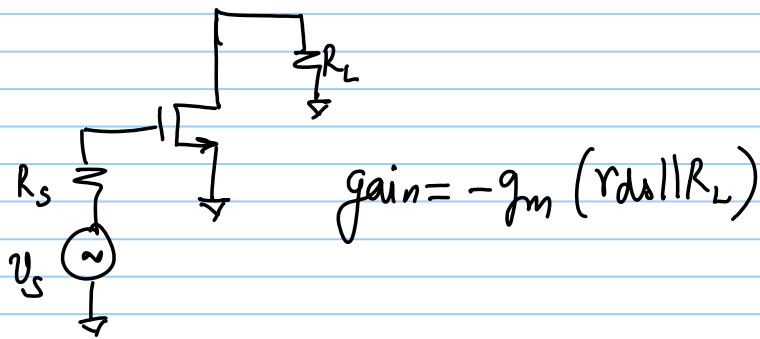


$$R_A || R_B \gg R_s$$

$$V_g = V_s$$


$$\text{gain} = -g_{m_p} (r_{ds_p} || R_L)$$

Bias Stabilization



Current Mirror

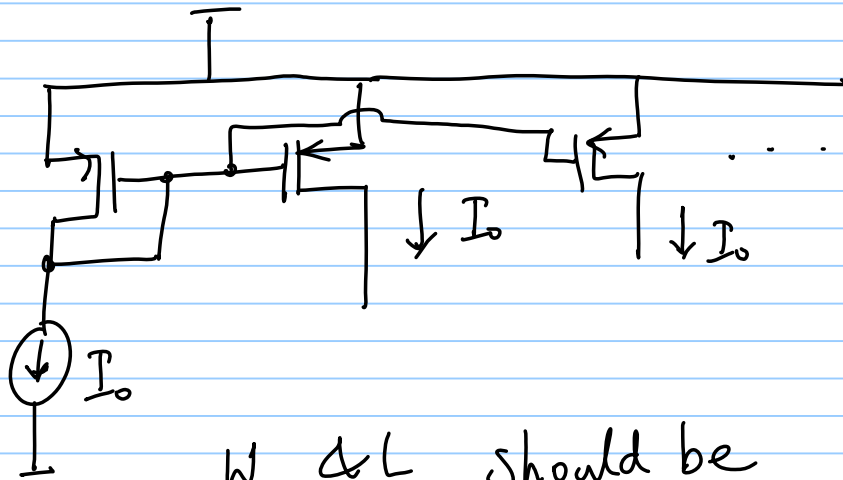



W & L should be equal


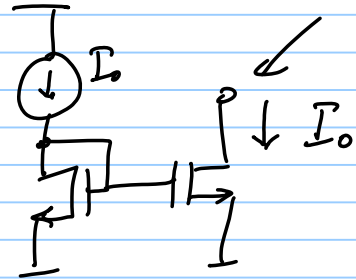


1)

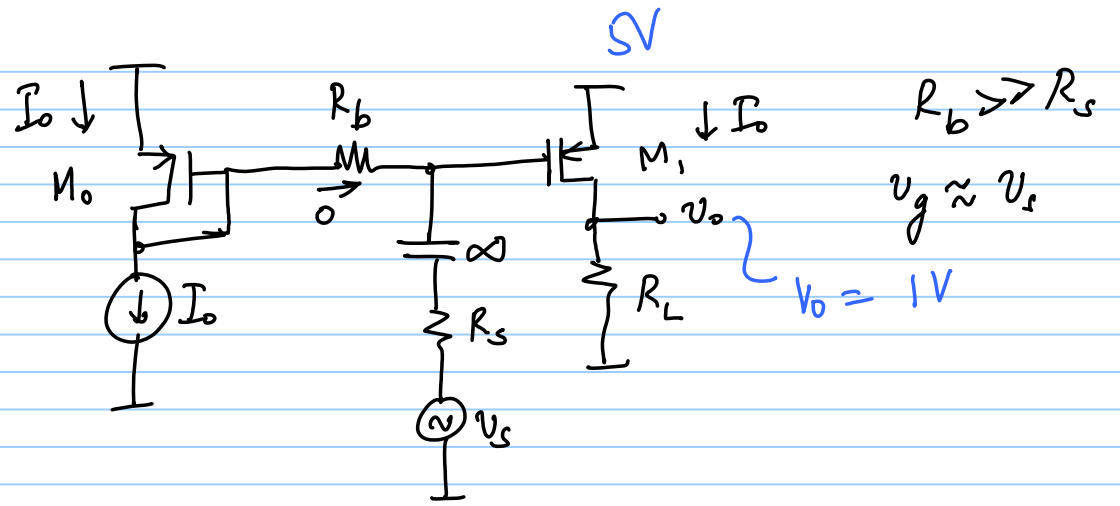
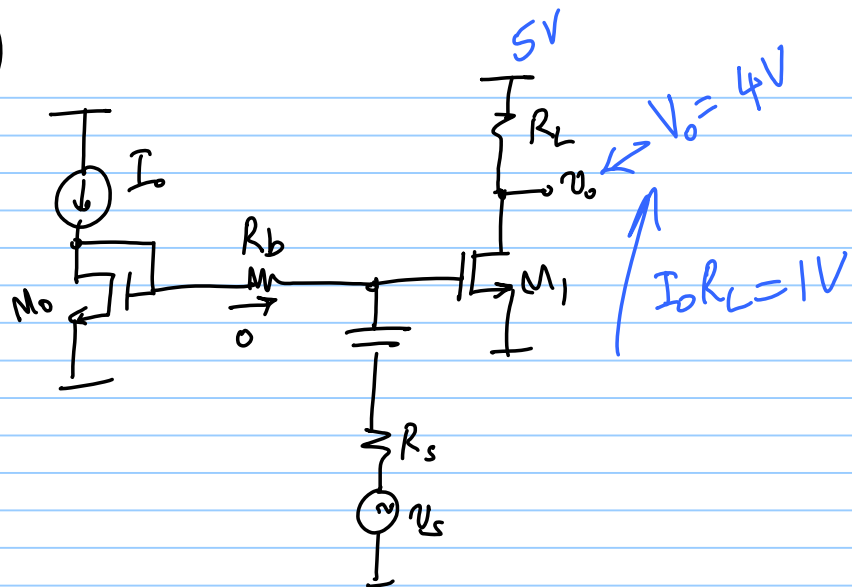


1.5)

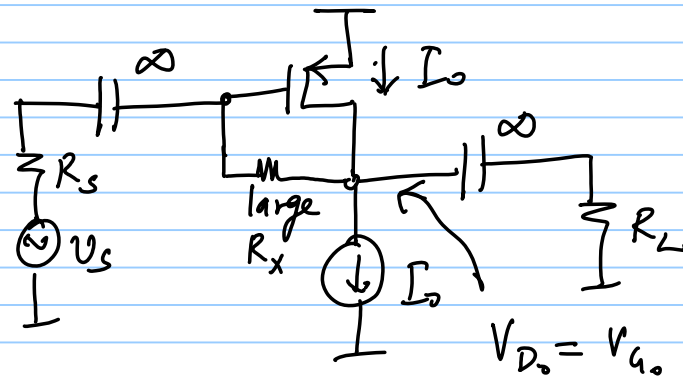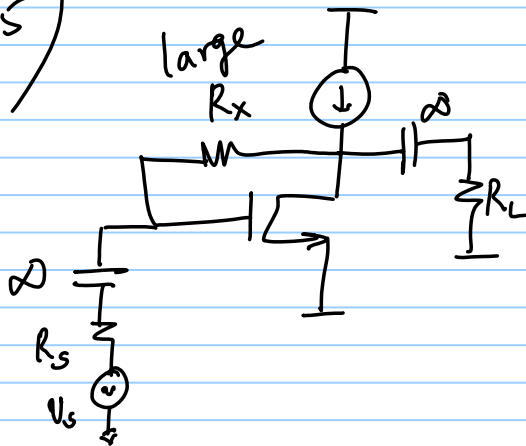


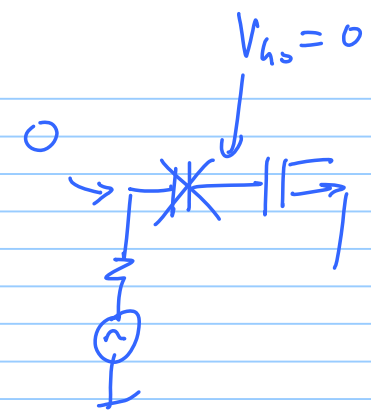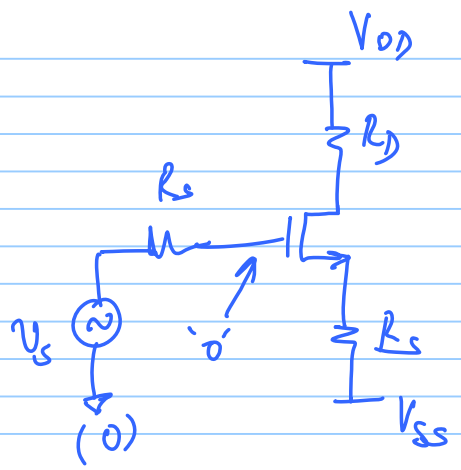


2)

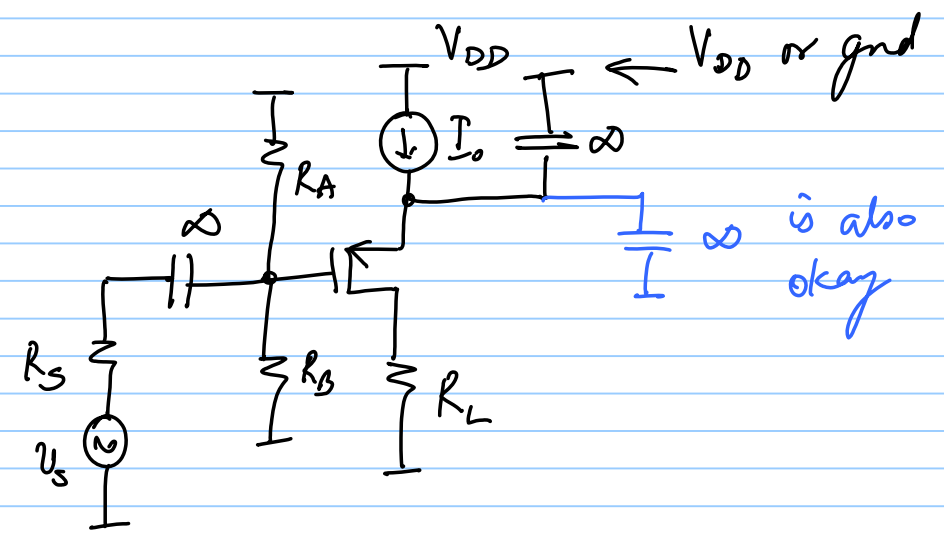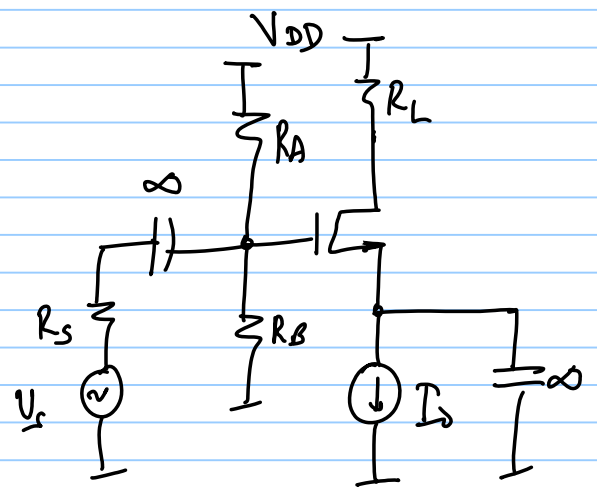

Case 3 & 4 - HW exercises

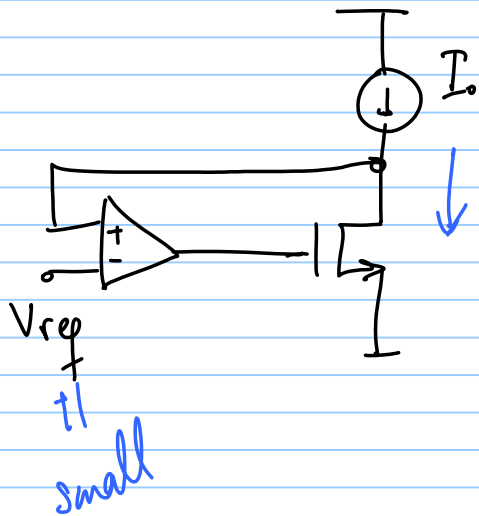




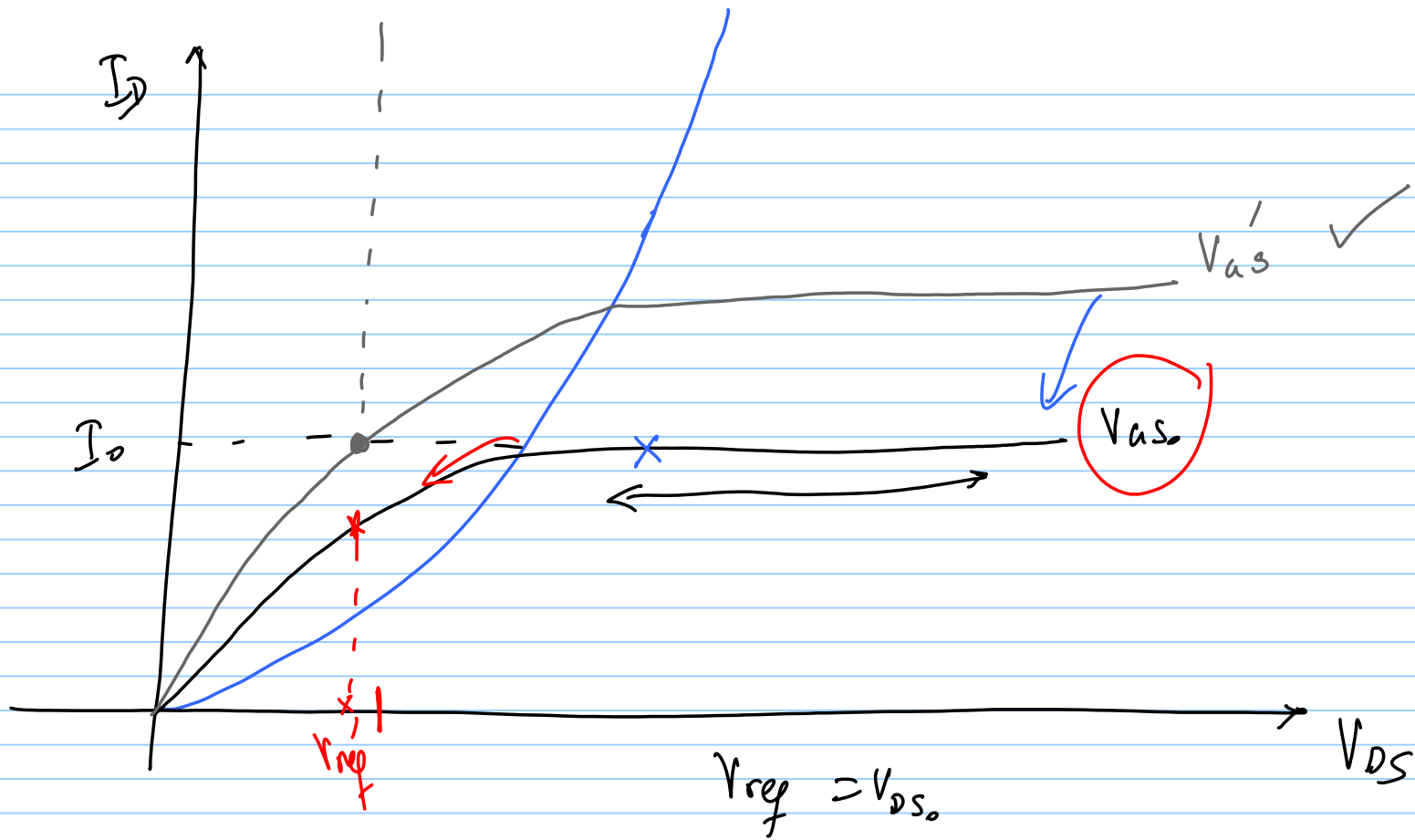
V_{ref} - design parameter
 I_0 - "
 $\frac{W}{L}$ - "
 V_{DD} -




26/9/17

Lec 13

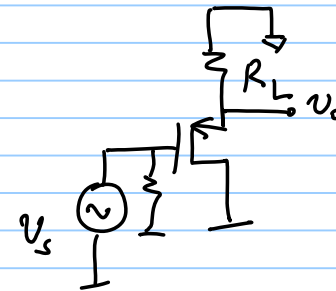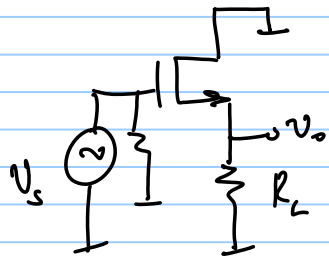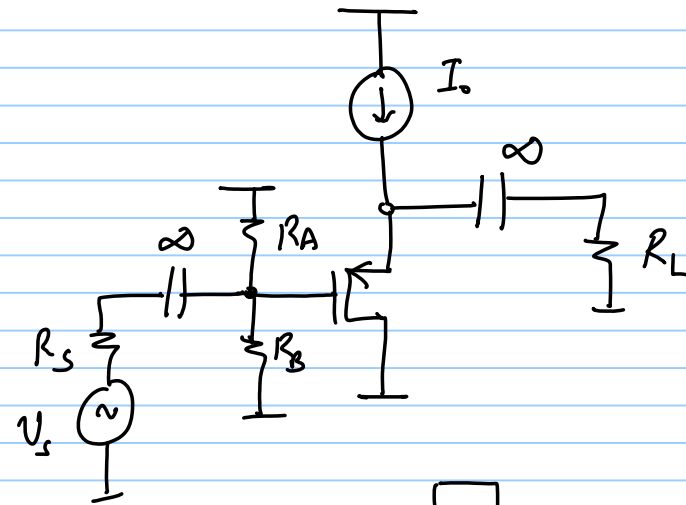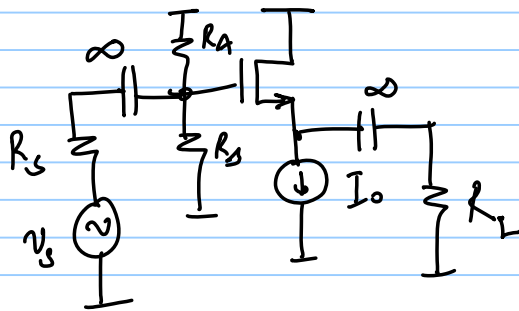1) VCVS gain = 1 $Z_{in} = \infty$ $Z_{out} = 0$




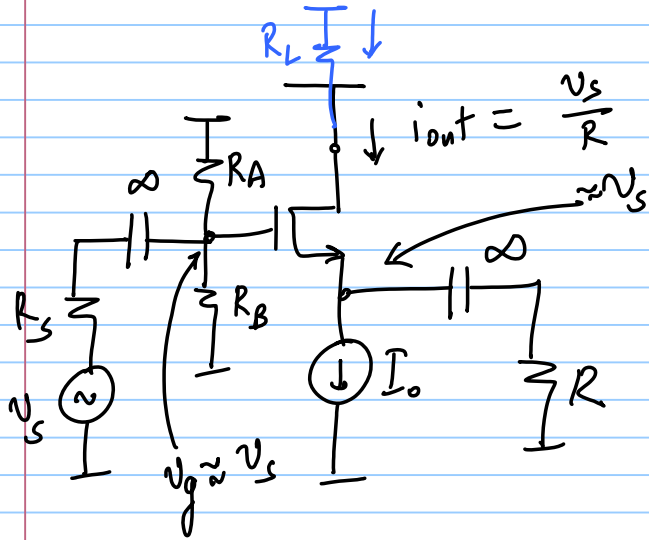2) VCCS gain $\frac{1}{R}$ $Z_{in} = \infty$, $Z_{out} = \infty$





$$R_{out} = R + r_{ds} + g_m R r_{ds}$$

" PMOS
Phase Splitter " → H.W.

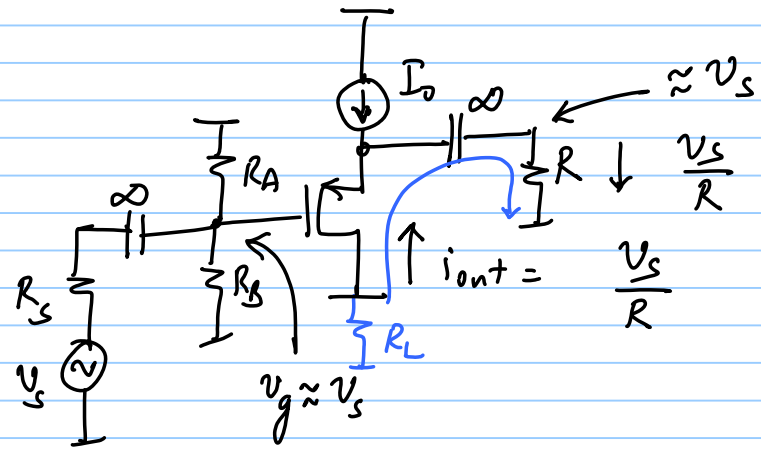

$$R_{out} = R + r_{dsp} + g_{mp} r_{dsp} R$$

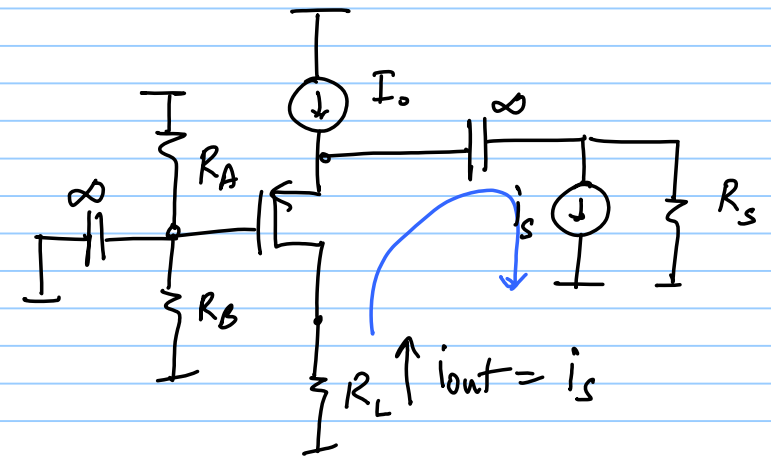
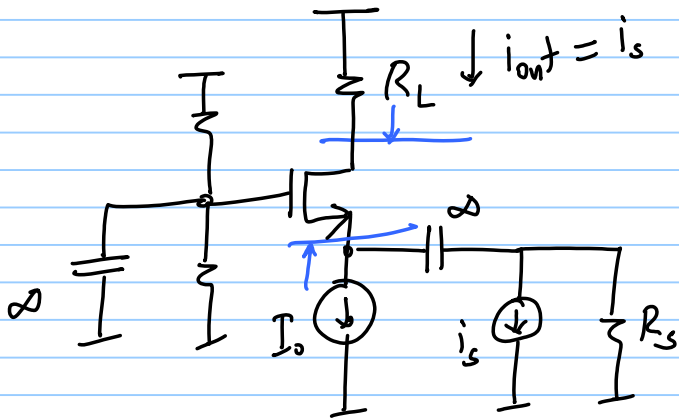
3) CCCS $gain = 1$ $Z_{in} = 0$, $Z_{out} = \infty$



$$Z_{in} \approx \frac{1}{g_{m_p}} \quad \text{small if } g_{m_p} \rightarrow \infty$$

$$Z_{out} = g_{m_p} r_{ds_p} \cdot R_s \quad \text{large if } g_{m_p} r_{ds_p} \rightarrow \infty$$

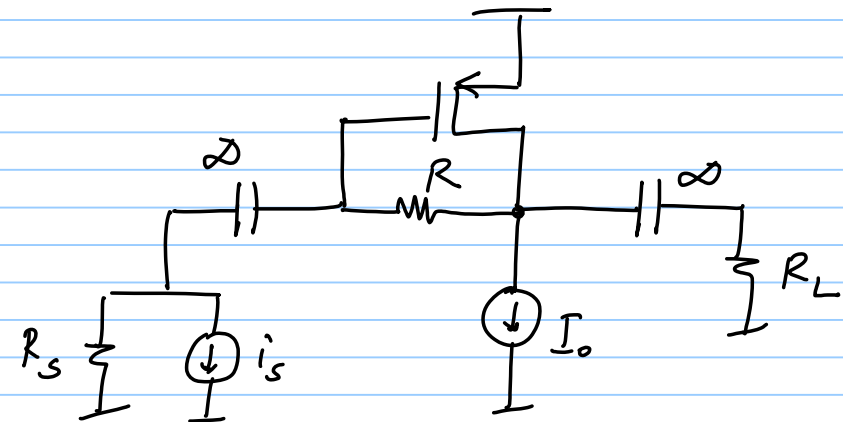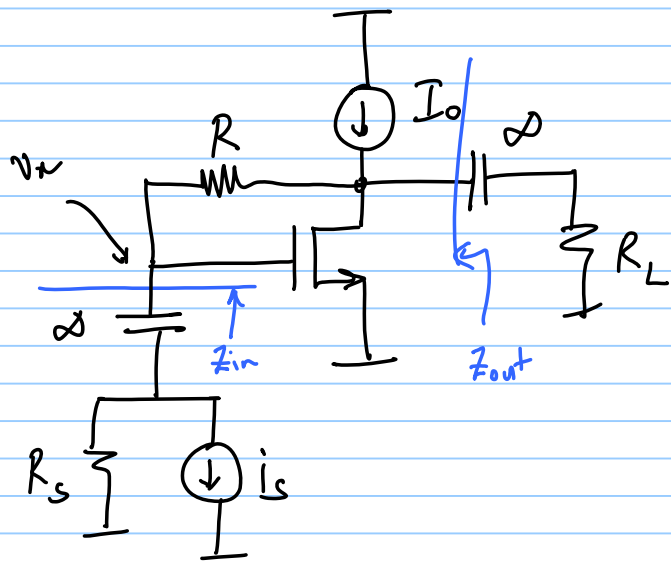
4) CCVS gain R $Z_{in} = 0$; $Z_{out} = 0$




$$v_o = R \cdot i_s$$



$$(v_o - R i_s) = 0$$

$$\underbrace{\hspace{2cm}}_{v_u}$$

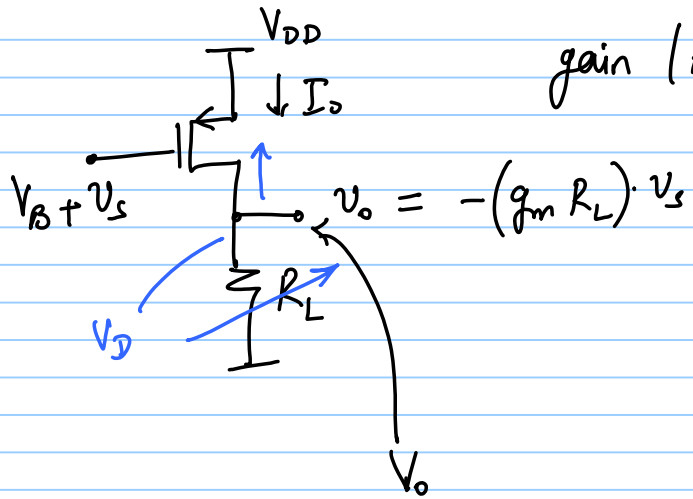

gain $|A| = g_m R_L$ * I want large A

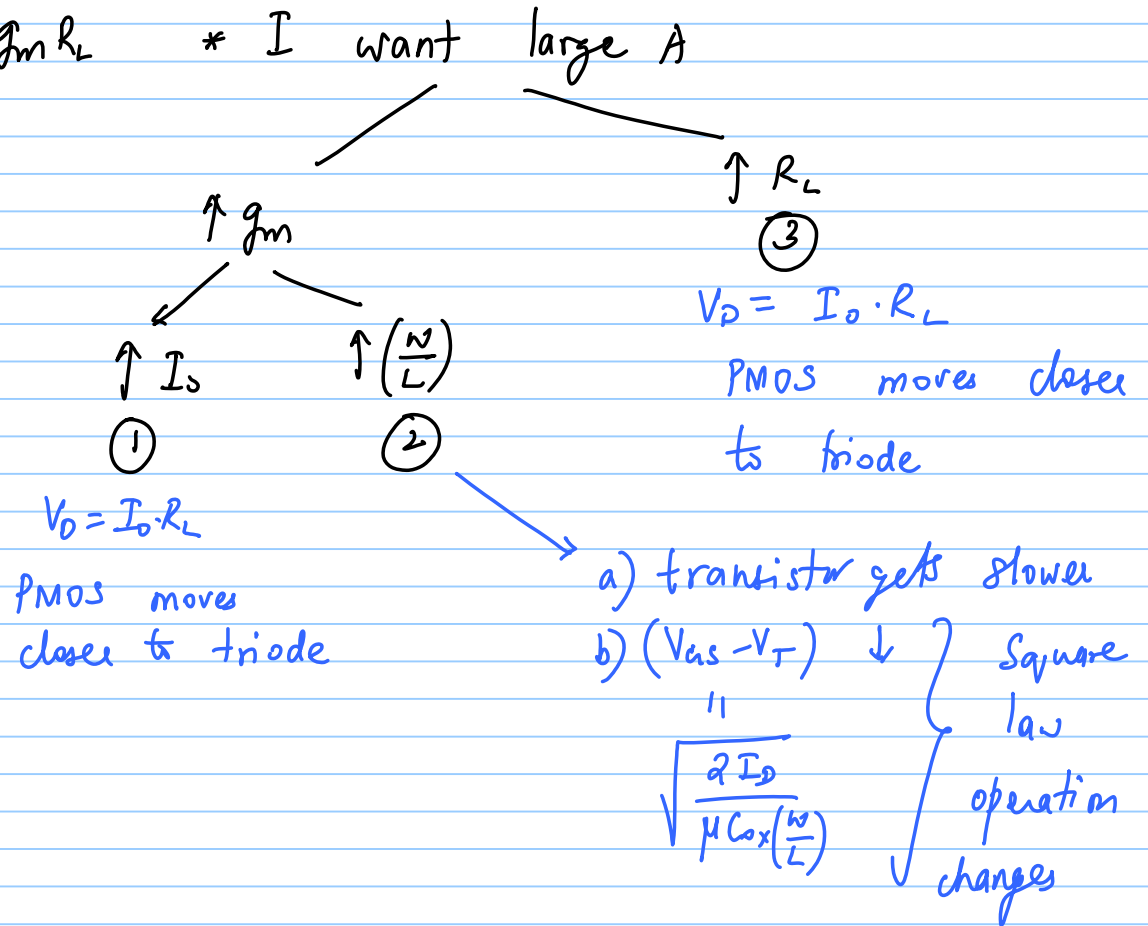


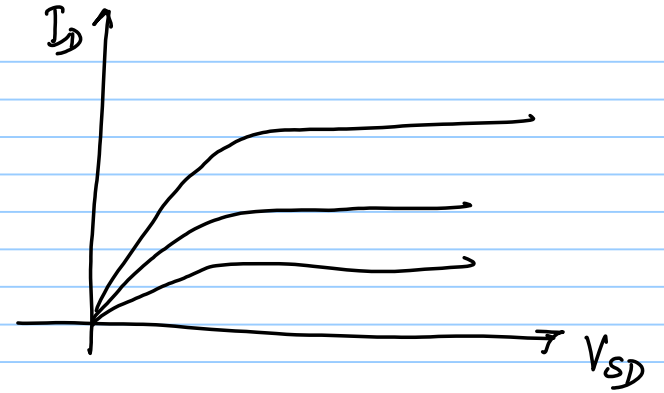
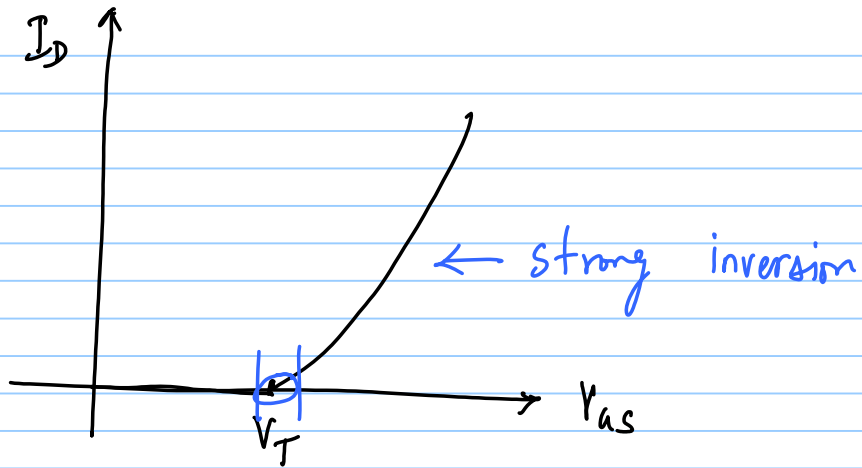


$$V_o = I_D \cdot R_L$$


$$V_{SD} = V_{DD} - V_o$$

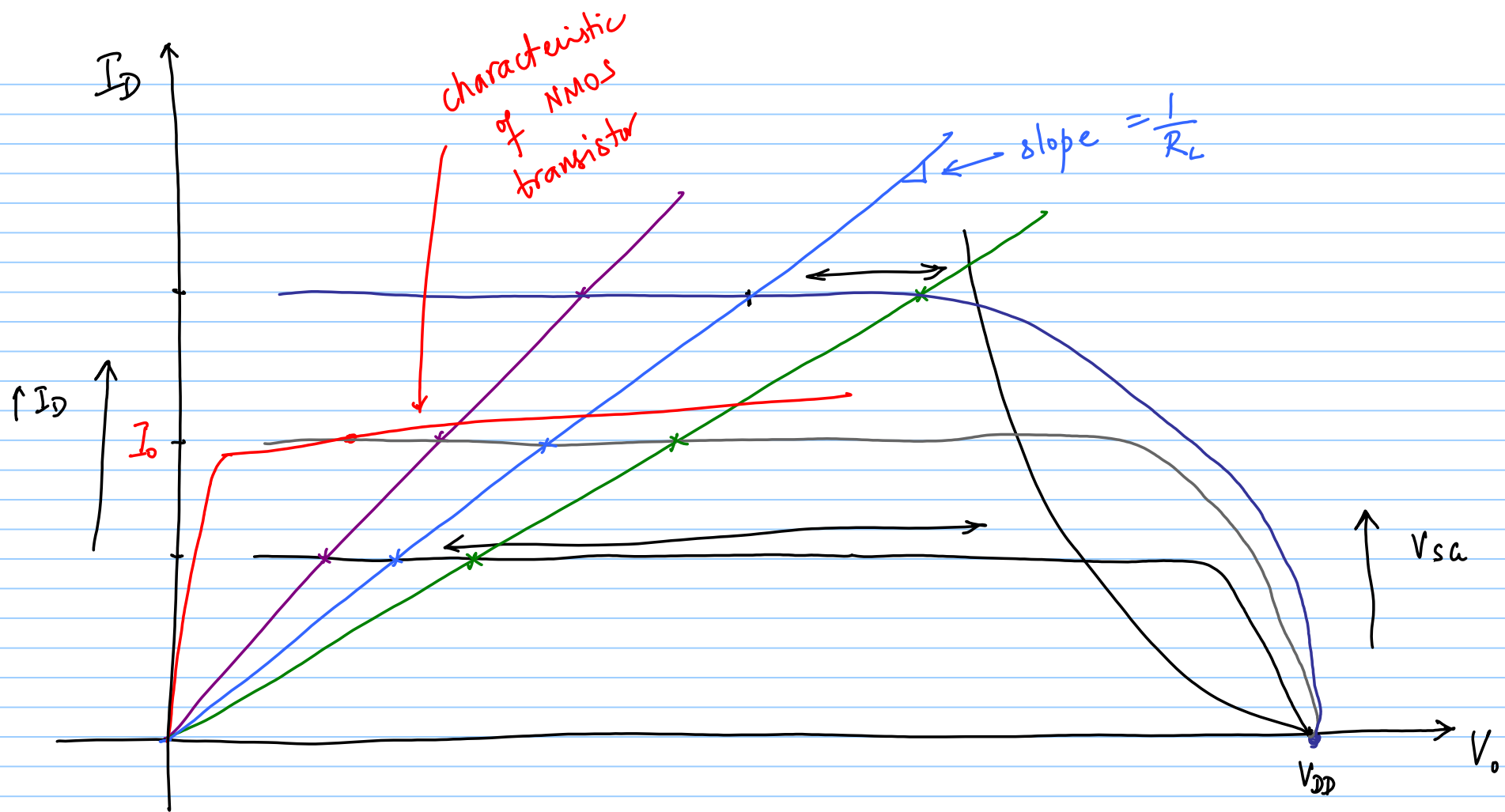A blue arrow points from the text "Curve for R_L " to the equation $V_o = I_D \cdot R_L$.
 A black arrow points from the text "Curve for PMOS" to the equation $V_{SD} = V_{DD} - V_o$.



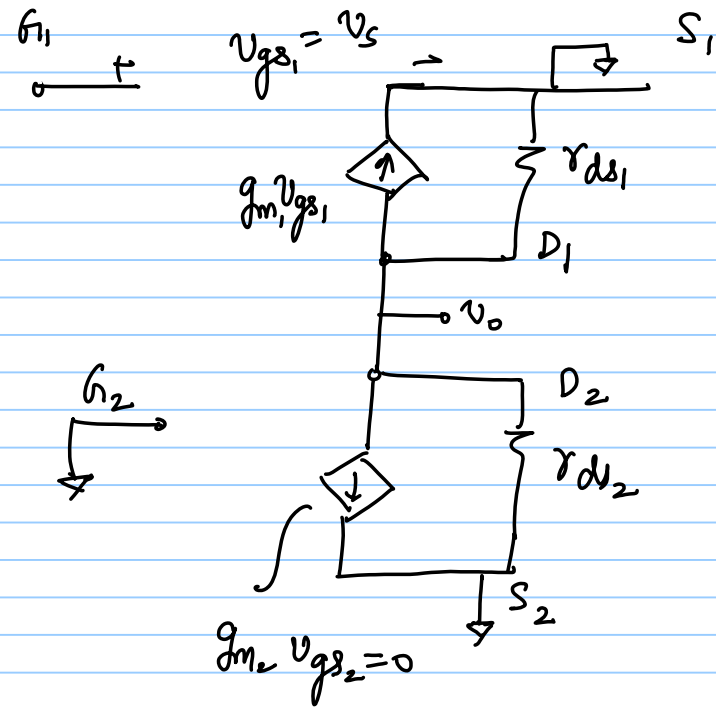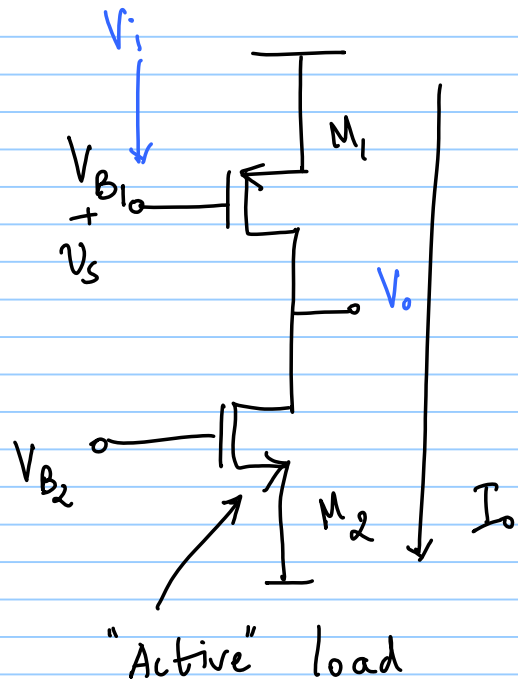

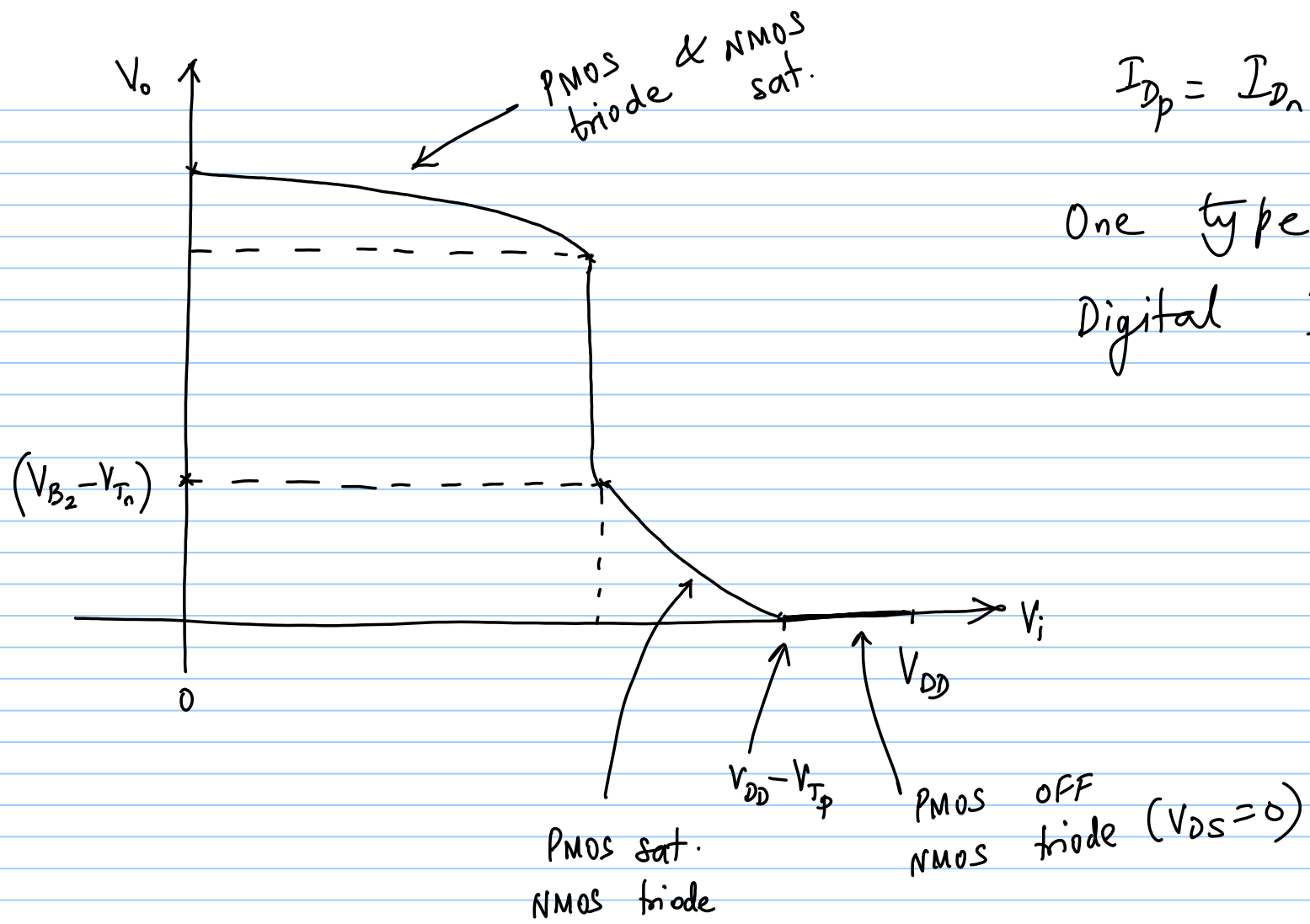
$$\frac{V_o}{v_s} = -g_{m1} (r_{ds1} \parallel r_{ds2}) = -g_{mp} (r_{ds_p} \parallel r_{ds_n})$$



$$I_{Dp} = I_{Dn}$$

One type of Digital Inverter

$$\frac{dV_o}{dV_i} = \text{gain}$$

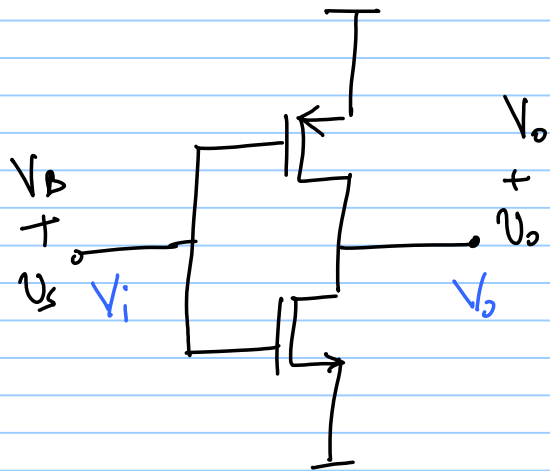

$$\frac{v_o}{v_s} = - (g_{m_n} + g_{m_p}) (r_{ds_n} \parallel r_{ds_p})$$



HW: Draw V_o vs. V_i

(DC characteristics)

Classical CMOS Inverter

3/10/2017

Lec 14

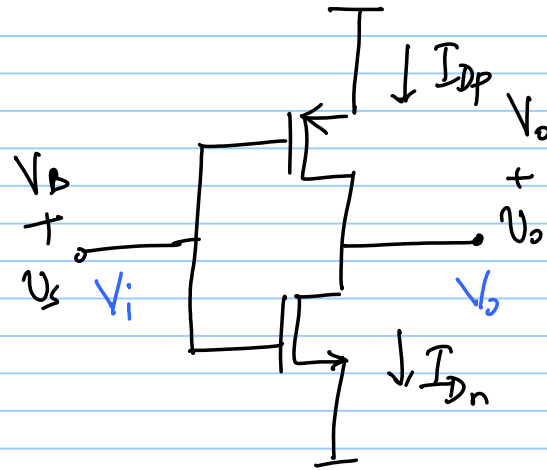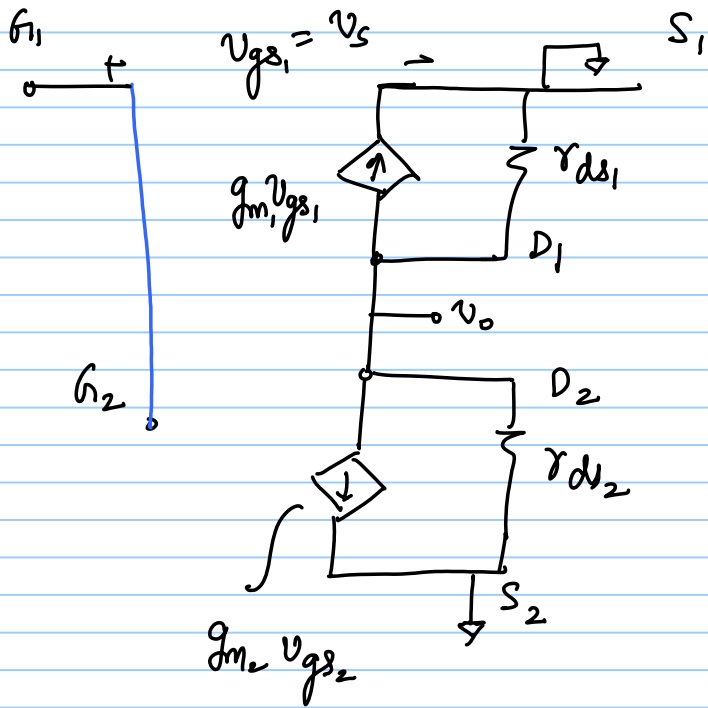


$$\frac{v_o}{v_i} = -(g_{m_n} + g_{m_p}) (r_{ds_p} || r_{ds_n})$$

$$= - \frac{g_{m_n} + g_{m_p}}{g_{ds_n} + g_{ds_p}}$$

$$g_{ds_n} = \frac{1}{r_{ds_n}}$$


$$g_{ds_p} = \frac{1}{r_{ds_p}}$$

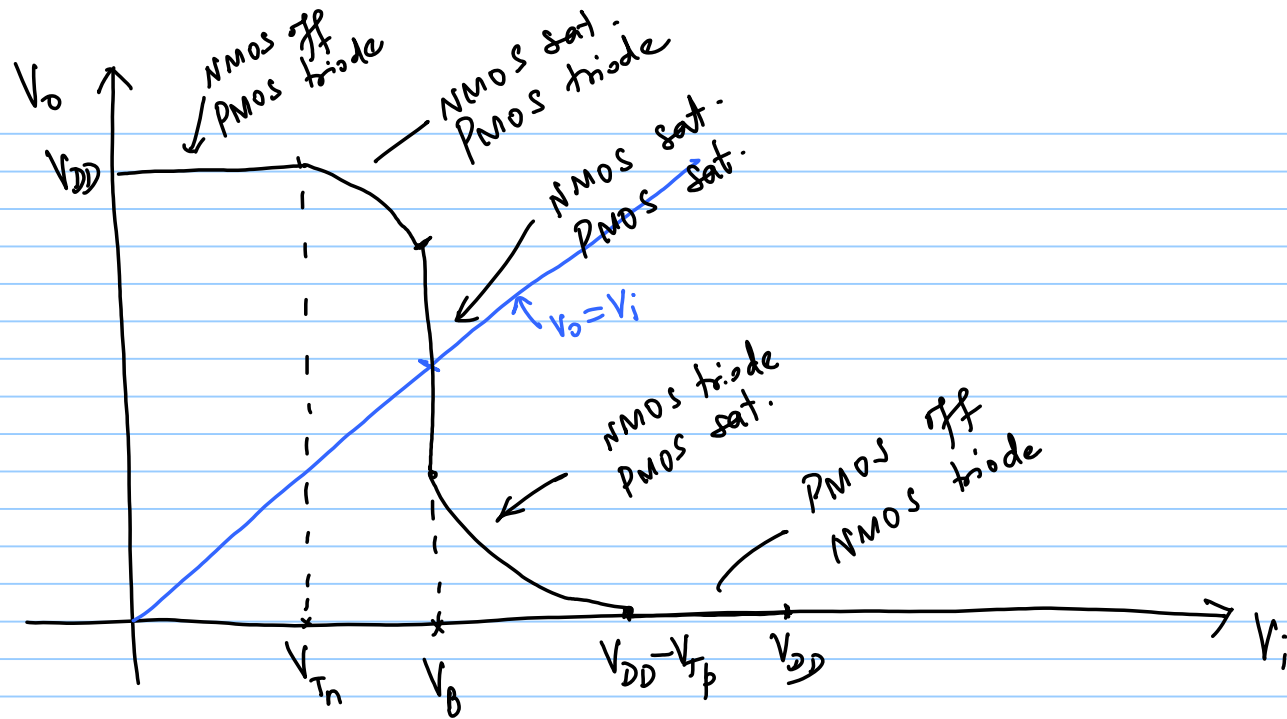

$$I_{Dp} = I_{Dn}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_p [V_{DD} - V_B - V_{Tp}]^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_n [V_B - V_{Tn}]^2$$
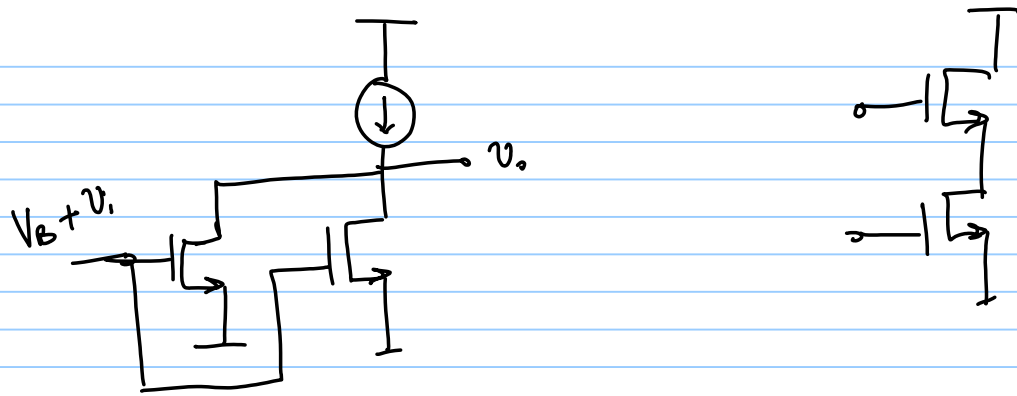
$$k = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_n}{\mu_p C_{ox} \left(\frac{W}{L}\right)_p}$$



$$\left[V_{DD} - V_B - V_{TP} \right]^2 = k \left[V_B - V_{TN} \right]^2$$

$$V_{DD} - V_B - V_{TP} = \sqrt{k} \cdot V_B - \sqrt{k} \cdot V_{TN}$$

$$V_B (1 + \sqrt{k}) = V_{DD} - V_{TP} + \sqrt{k} V_{TN}$$



$$V_B = \frac{V_{DD} - V_{TP} + \sqrt{k} V_{TN}}{1 + \sqrt{k}}$$



$$1) V_B = \frac{V_{DD}}{2} \text{ if } k=1, V_{Tn} = V_{Tp}$$

$$2) k \gg 1 : V_B \approx V_{Tn}$$



$$3) k \ll 1 : V_B \approx V_{DD} - V_{Tp}$$

(I)

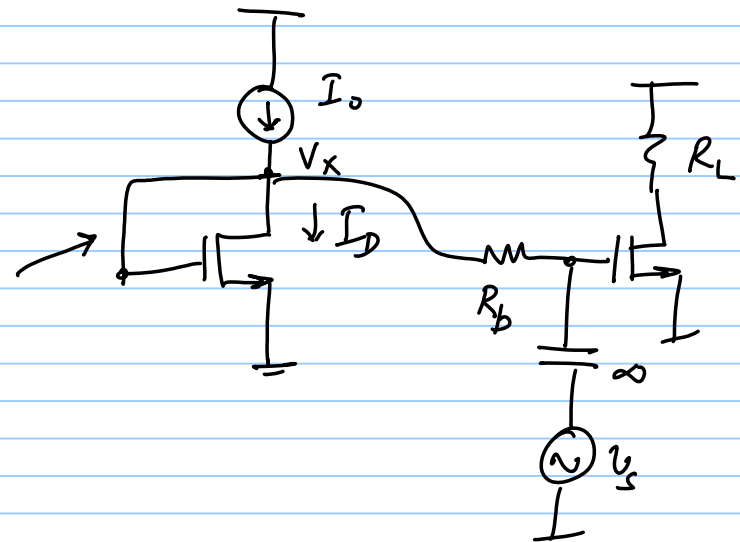
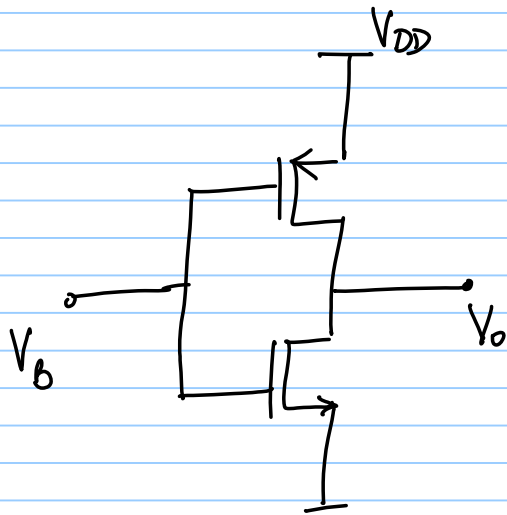


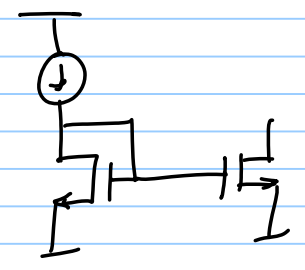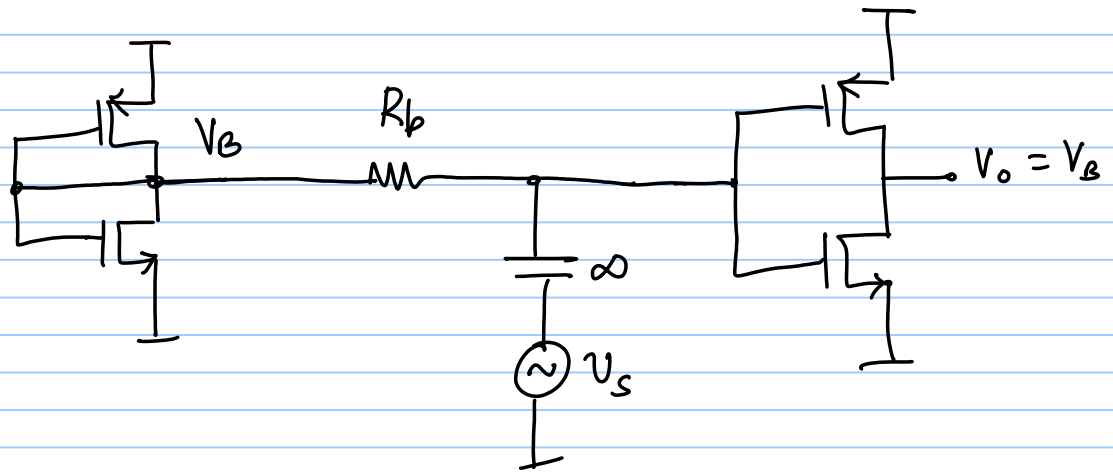


II

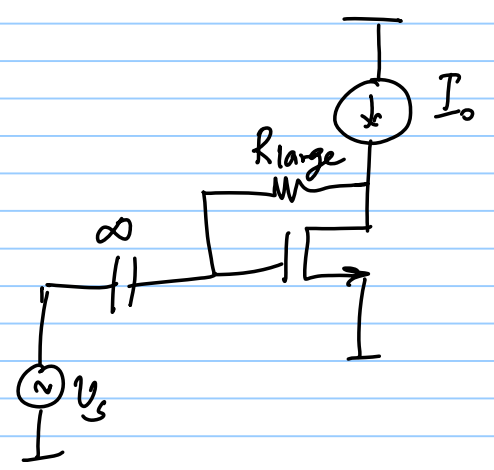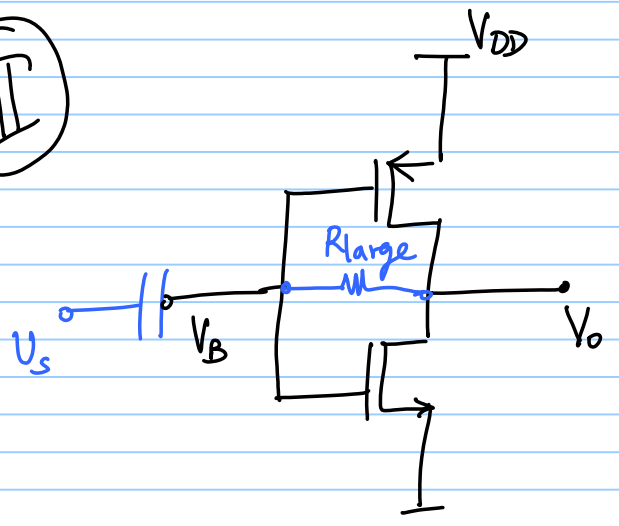

III

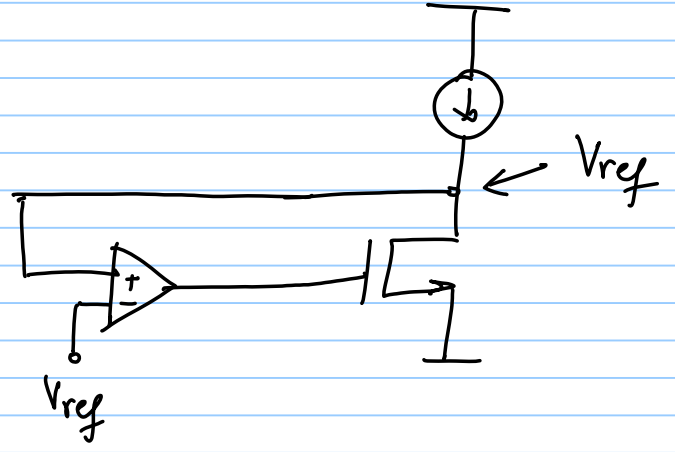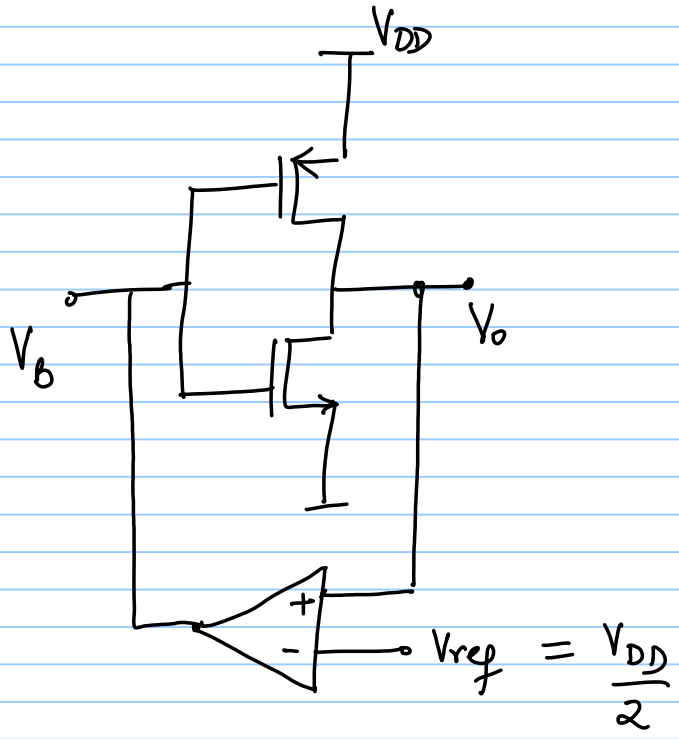

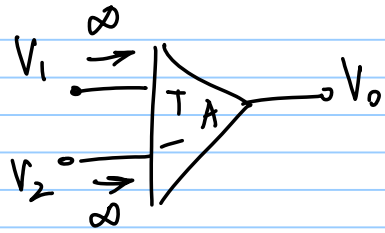



CMOS opamp



- 1) large gain
- 2) Differential input
- 3) Single output
- 4) $Z_{in} = \infty$

$$V_o = A (V_1 - V_2)$$

V_1	V_2	V_o
1	2	$-A(1)$
5	6	$-A(1)$

$$g_m r_{ds} \approx 50$$

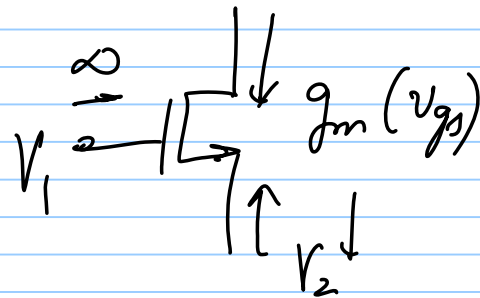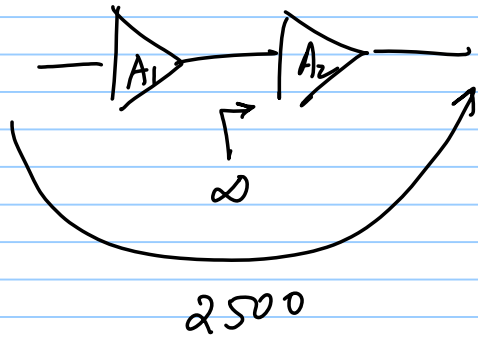


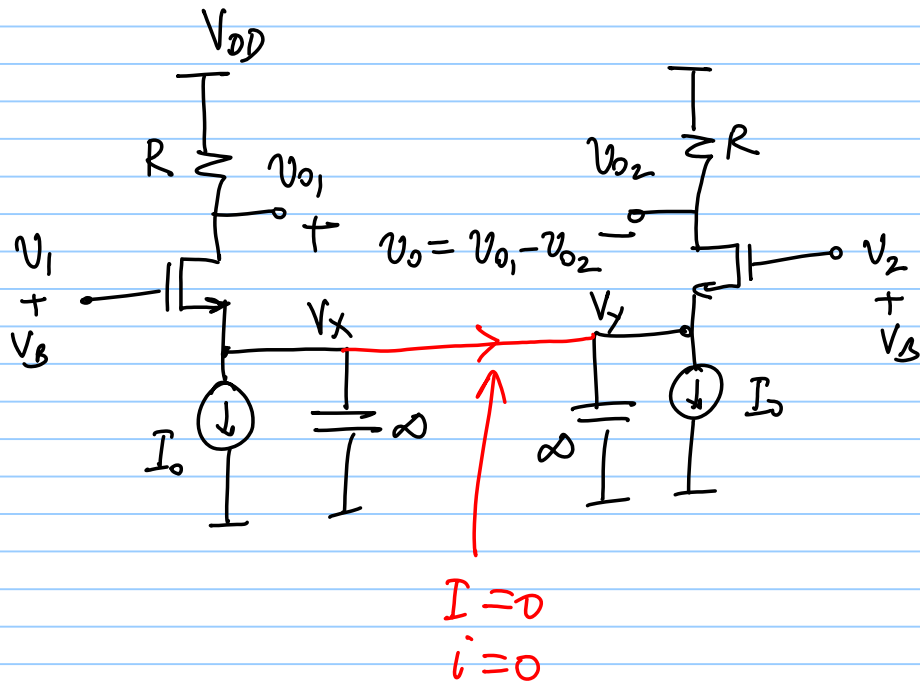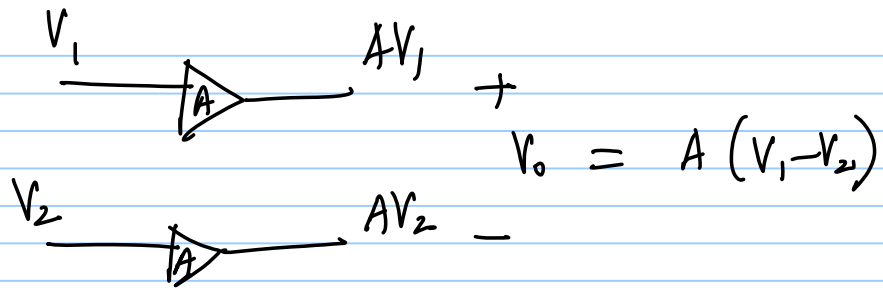

$$V_x = V_B - V_{as1}$$

$$V_y = V_B - V_{as2} = V_x$$

$$v_x = v_y = 0$$

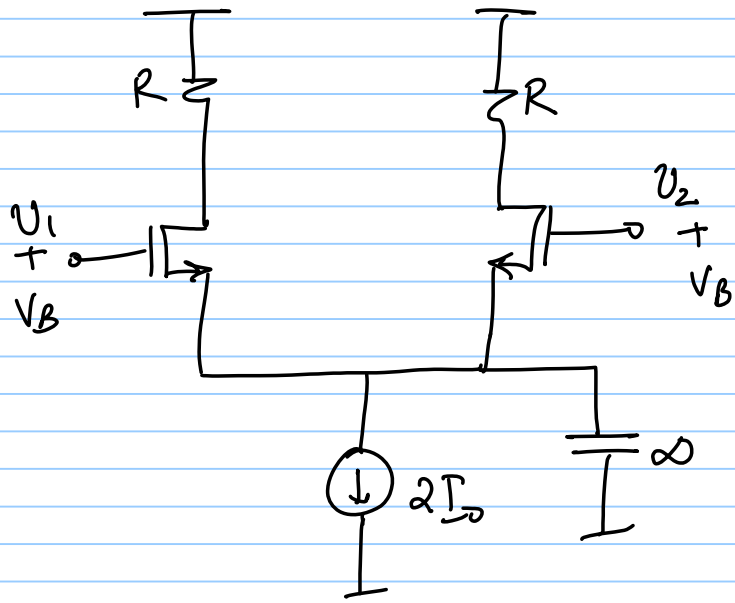

$$V_1 = V_{CM} + \frac{\Delta V}{2} \leftarrow V_{DM}$$

$$V_2 = V_{CM} - \frac{\Delta V}{2}$$

$$\frac{V_1 \ \& \ V_2}{\downarrow}$$

$$V_1 = \frac{V_1 + V_2}{2} + \frac{V_1 - V_2}{2}$$


$$V_2 = \frac{V_1 + V_2}{2} - \frac{V_1 - V_2}{2}$$

↑
average
or
common
mode
voltage

↑
differential
mode
voltage

17/10/17


Lec 15

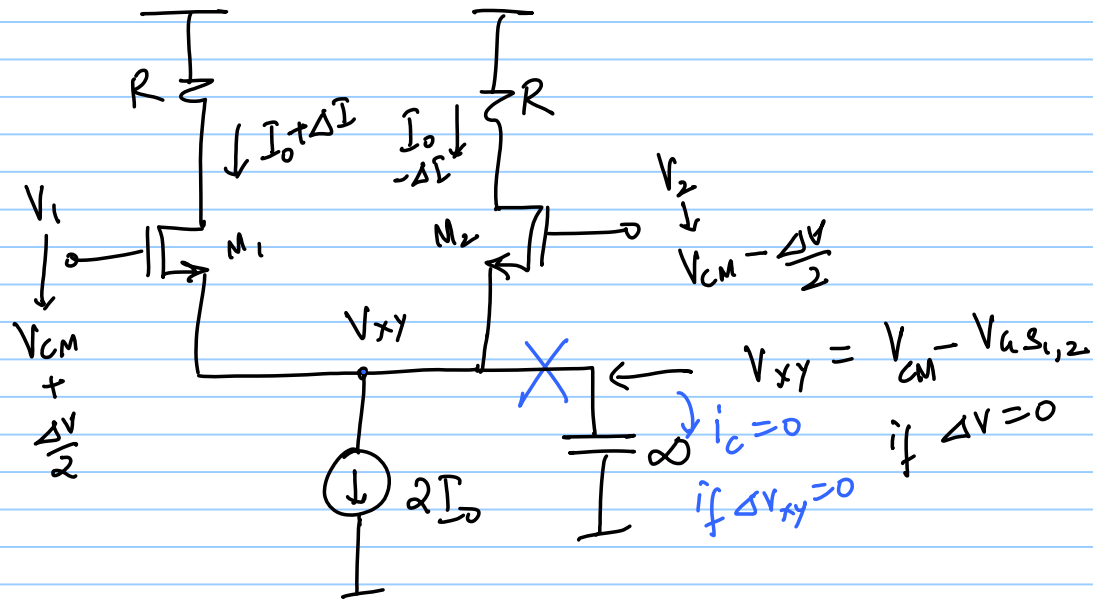

$$\Delta I = g_m \left(\frac{\Delta V}{2} - \Delta V_{XY} \right)$$


$$-\Delta I = g_m \left(-\frac{\Delta V}{2} - \Delta V_{XY} \right)$$

$$\Delta V_{XY} = 0$$

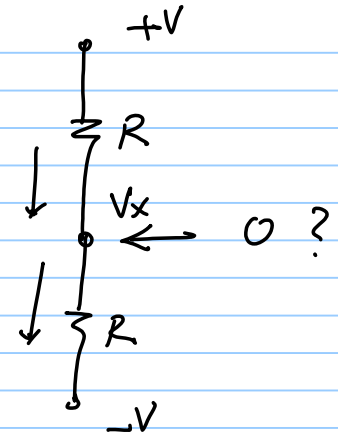

$$\frac{V - V_X}{R} = \frac{V_X - (-V)}{R}$$

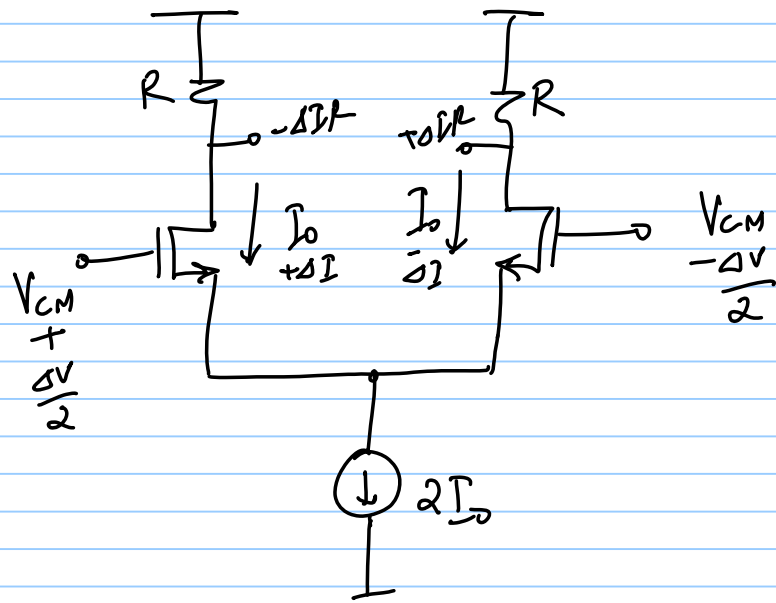
$$\frac{2V_X}{R} = 0 \Rightarrow V_X = 0$$



Half circuit analysis

CM analysis \leftarrow same voltages and currents on both sides

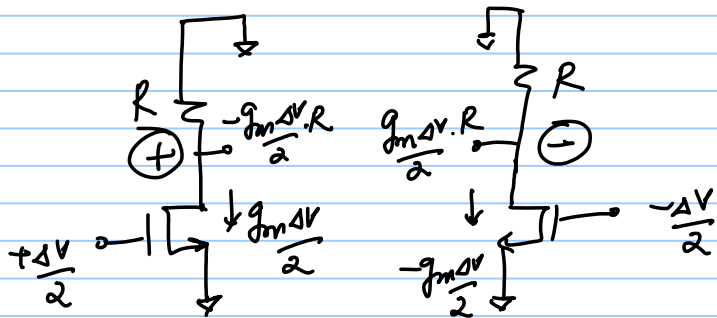DM analysis \leftarrow V_o & I_o on either side are equal in magnitude & opposite in direction





$$\Delta V_o = -g_m R \Delta V$$




$$A_{dm} = \frac{\Delta V_o}{\Delta V} = -g_m R$$


$$g_m R \gg 1$$

$$g_m \gg \frac{1}{R}$$

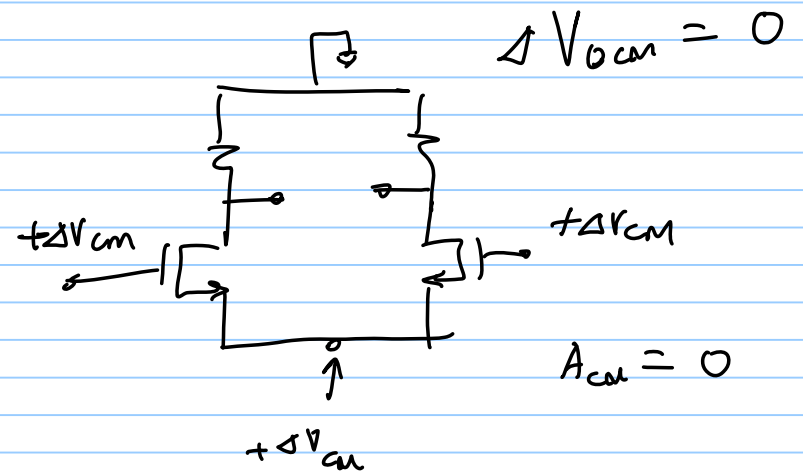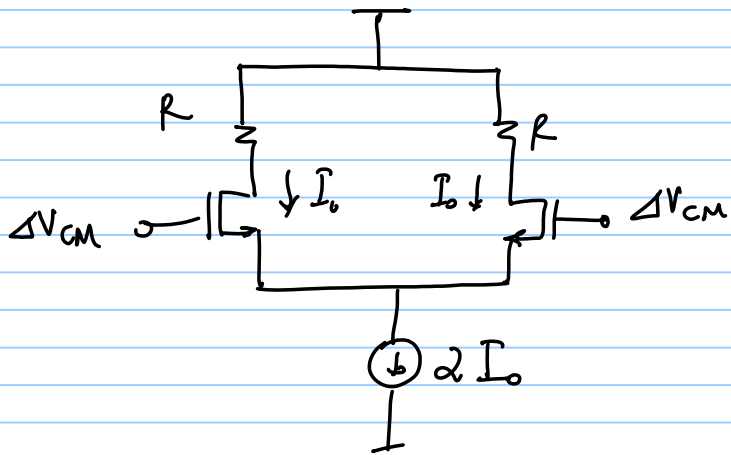

Common-mode rejection ratio = $\left| \frac{A_{dm}}{A_{cm}} \right| = \infty$ (ideally) for this circuit

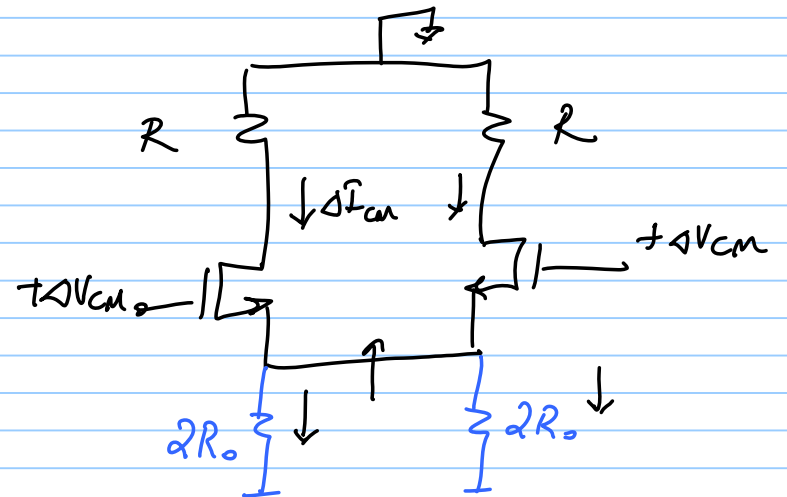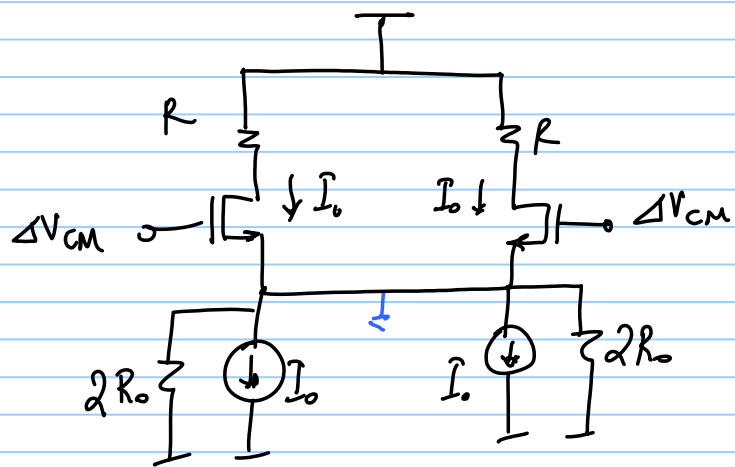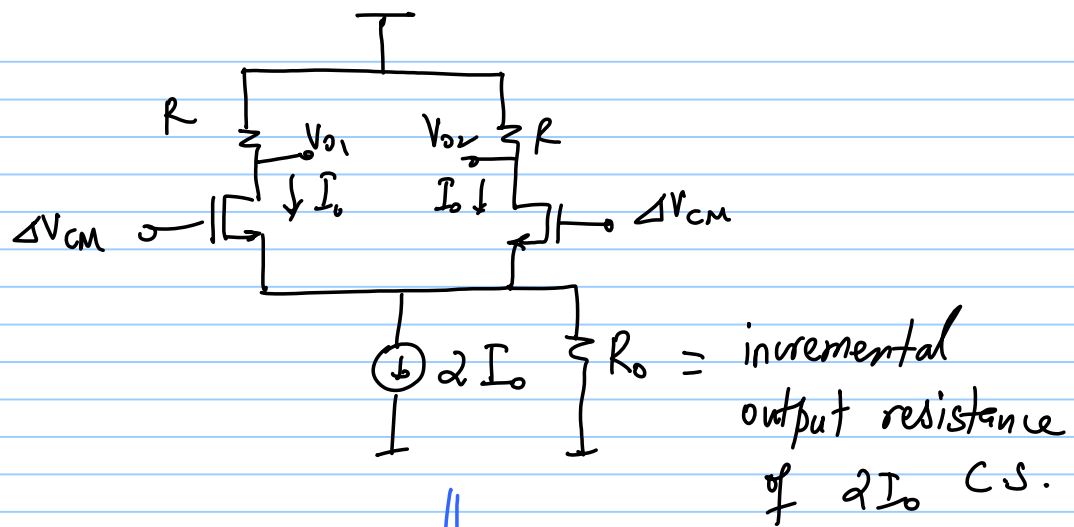

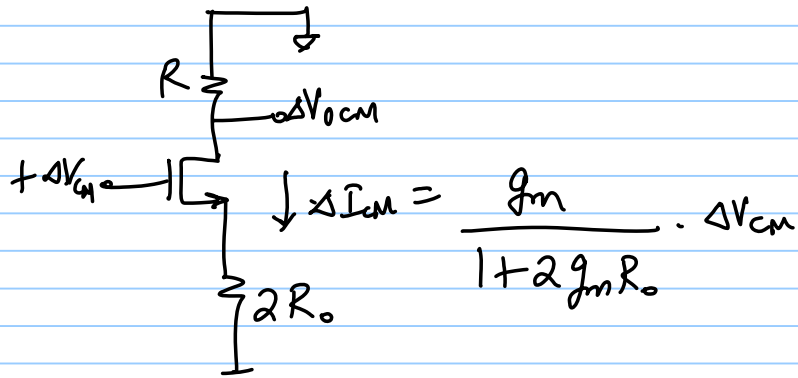

$$\Delta V_{ocm} = -\Delta I \cdot R$$

$$= \underbrace{\frac{-g_m R}{1 + 2g_m R_0}}_{A_{cm}} \cdot \Delta V_{cm}$$

$$CMRR = (1 + 2g_m R_0)$$

$$V_1 = V_{cm} + \frac{\Delta V}{2} + \Delta V_{cm}$$

$$V_2 = V_{cm} - \frac{\Delta V}{2} + \Delta V_{cm}$$

$$V_{ocm} = \frac{V_{o1} + V_{o2}}{2}$$


$$\frac{\Delta V_o}{2} = \frac{V_{o1} - V_{o2}}{2}$$

$$V_1 = 5V + 1 \sin \omega t$$

$$V_2 = 6V + 2 \sin \omega t$$

$$V_{CM} = 5.5V + 1.5 \sin \omega t$$


$$V_{DM} = -0.5V - 0.5 \sin \omega t$$

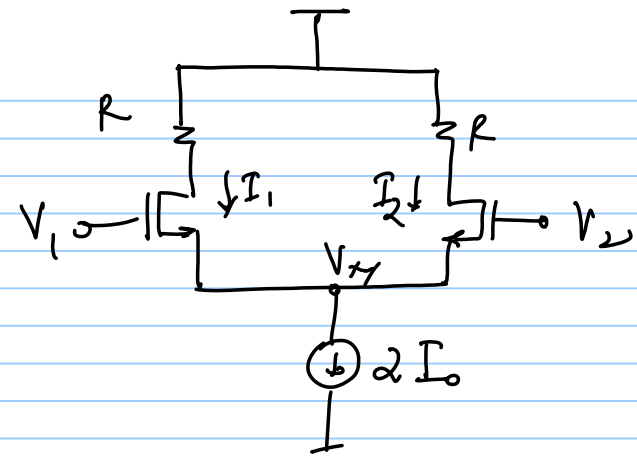

$$I_1 + I_2 = 2I_0$$


$$I_1 = \frac{1}{2} k' (V_1 - V_{th})^2$$
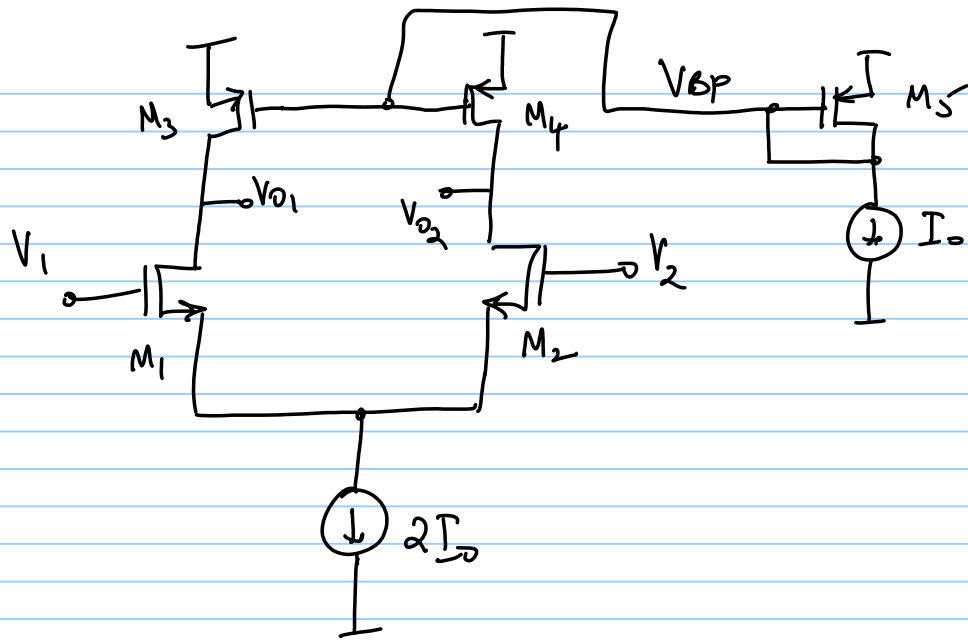
$$I_2 = \frac{1}{2} k' (V_2 - V_{th})^2$$





$$A_{DM} = -g_m (r_{ds1} \parallel r_{ds3})$$


large gain

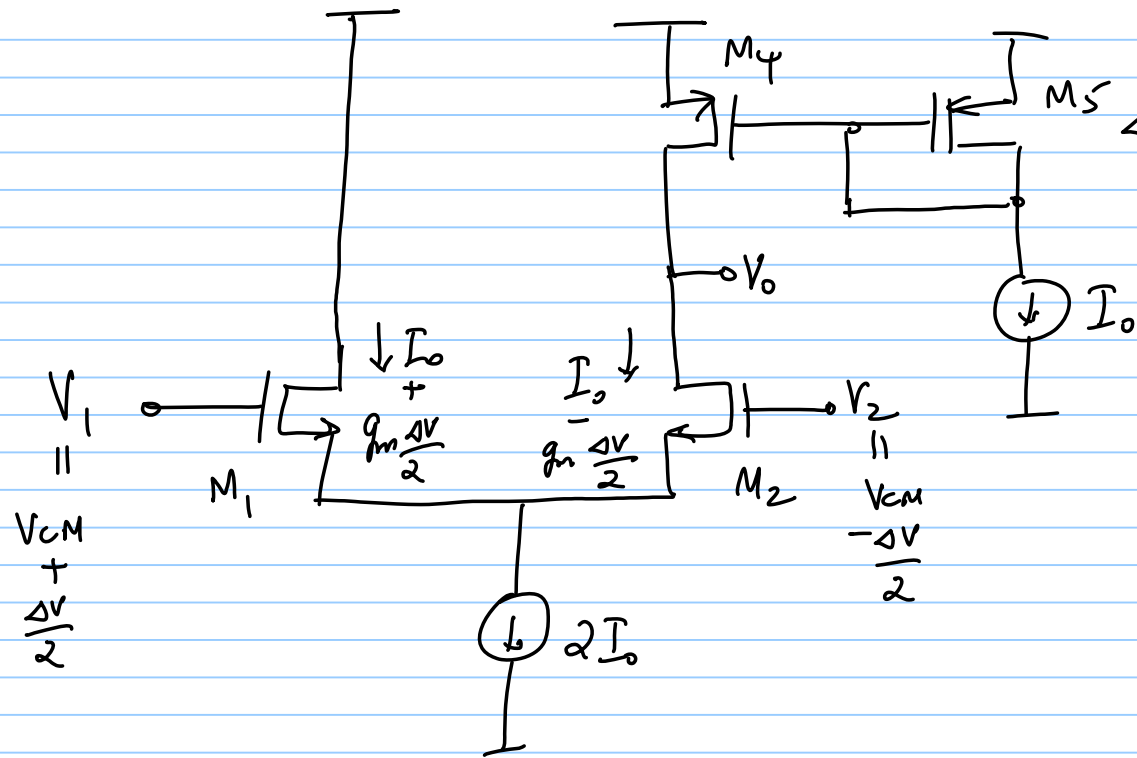

$$\Delta V_0 = g_m (r_{ds2} || r_{ds4}) \frac{\Delta V}{2}$$

$$A_{DM} = \frac{g_m (r_{ds2} || r_{ds4})}{2}$$

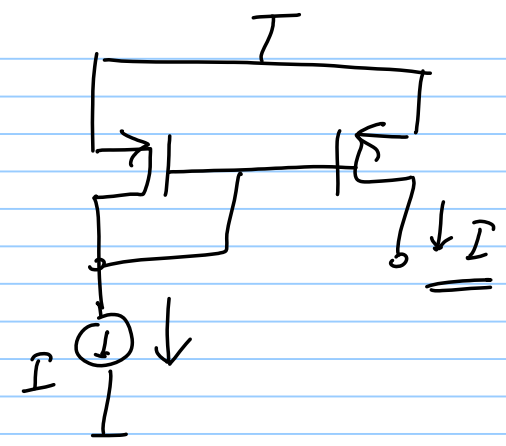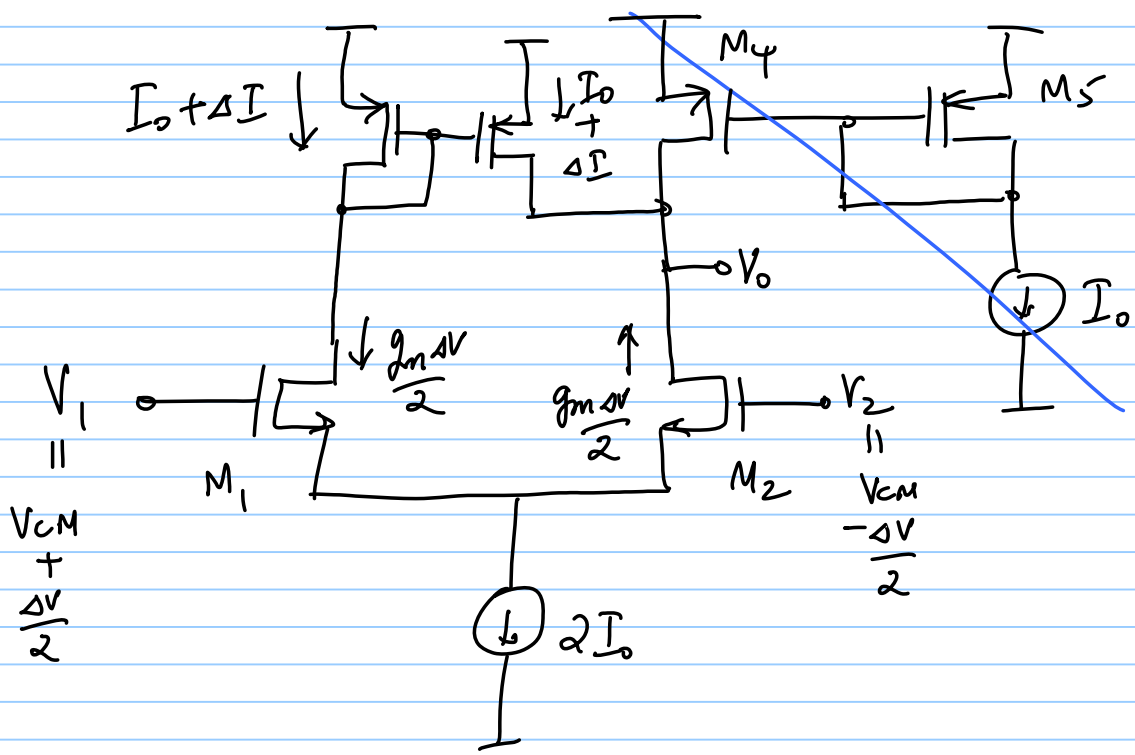

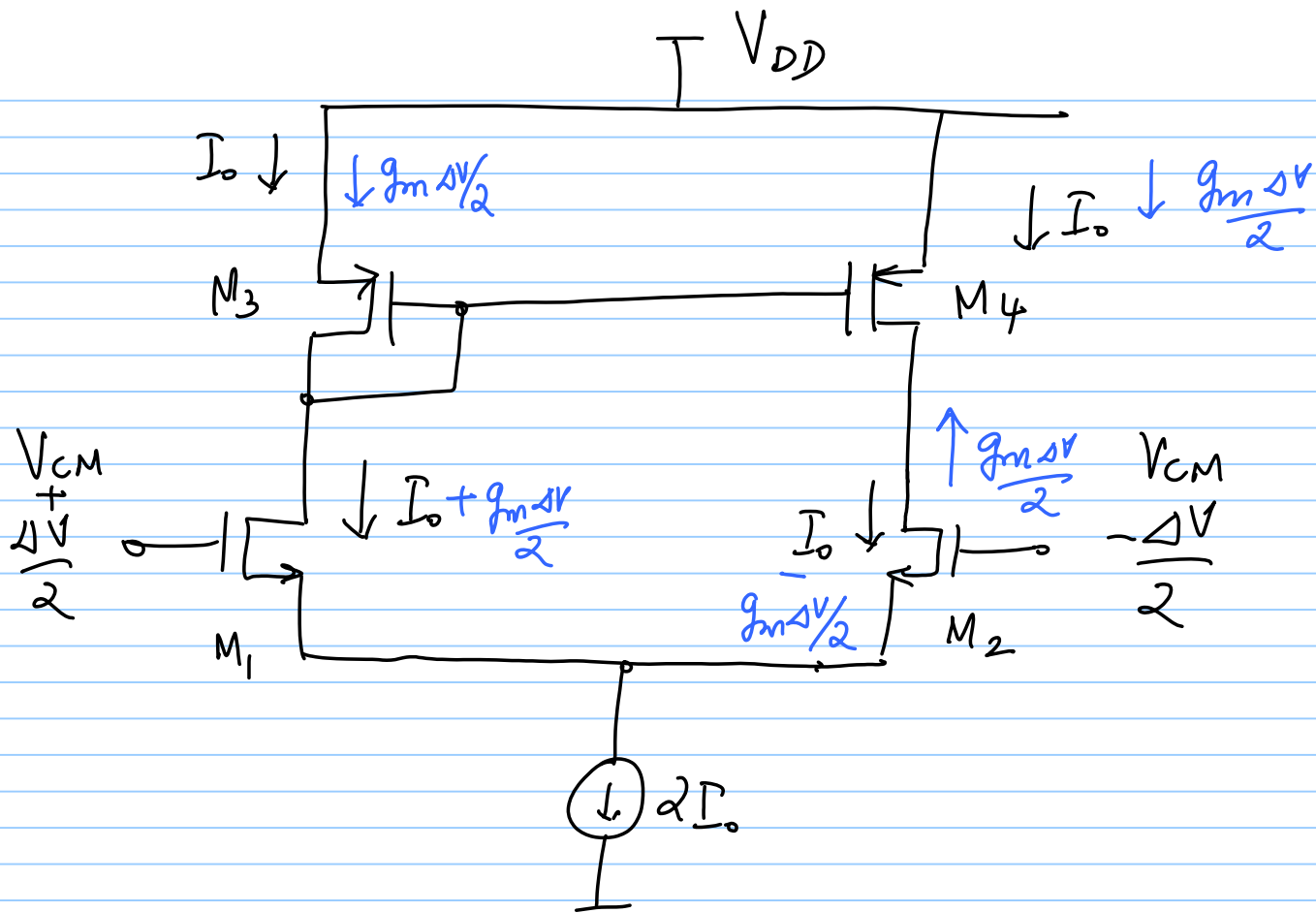


Incremental analysis
- H.W.

$$A_{DM} = g_m (r_{ds2} || r_{ds4})$$

Single Stage
Opamp

25/10/17

Quiz 2 Discussion

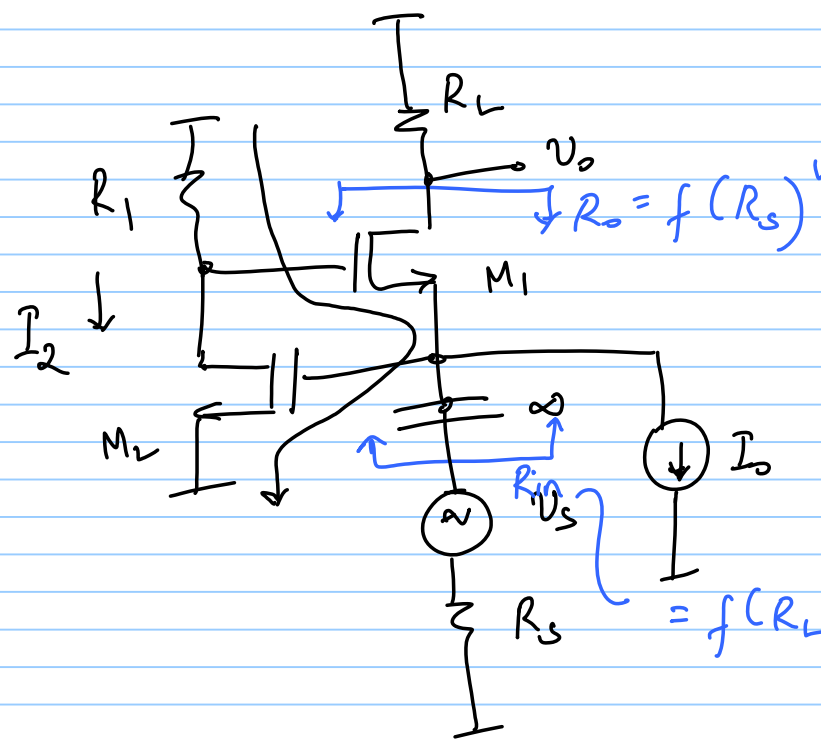

1) V_{as1} & V_{as2}


$$V_{DD} = I_2 R_1 + V_{as1} + V_{as2}$$

$$I_2 = \frac{1}{2} \mu C_{ox} \left(\frac{W}{L}\right) (V_{as2} - V_T)^2$$


2) R_{in} & R_{out}

$$R_{in} = f(R_L)$$

$$R_{out} = f(R_S)$$

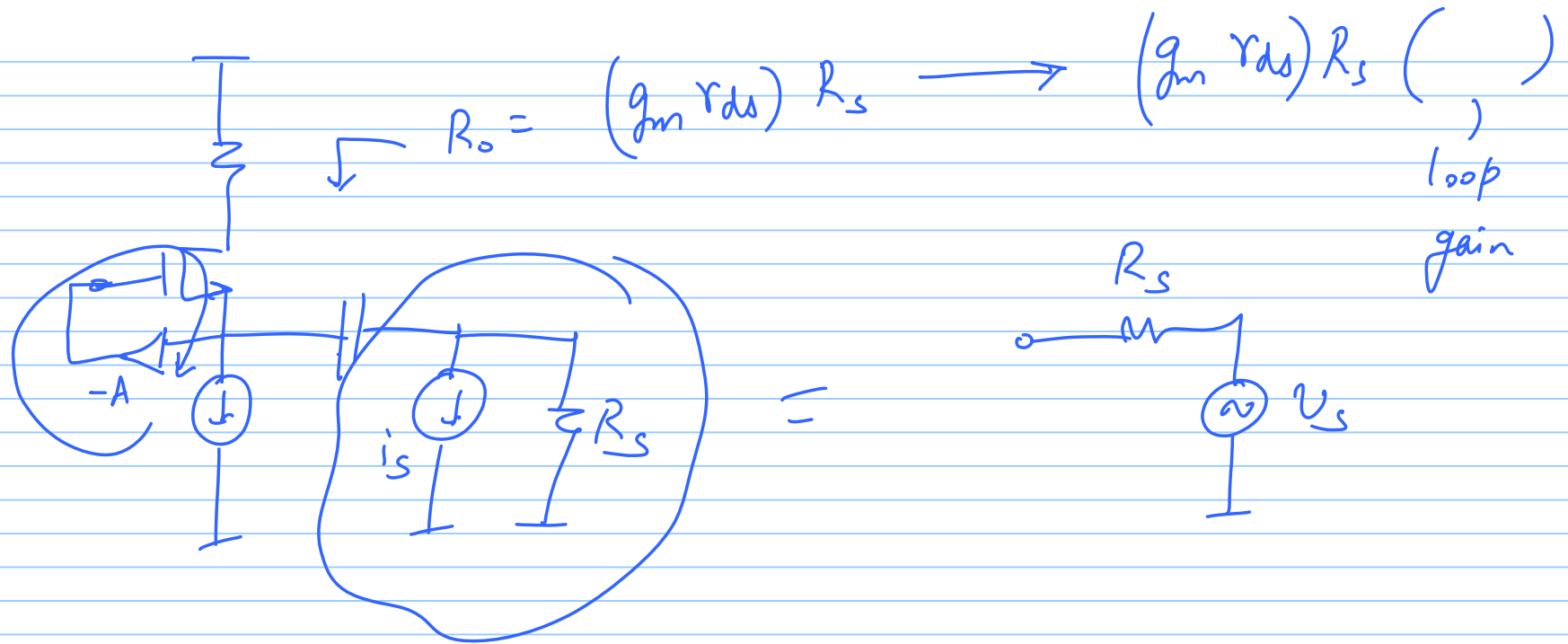

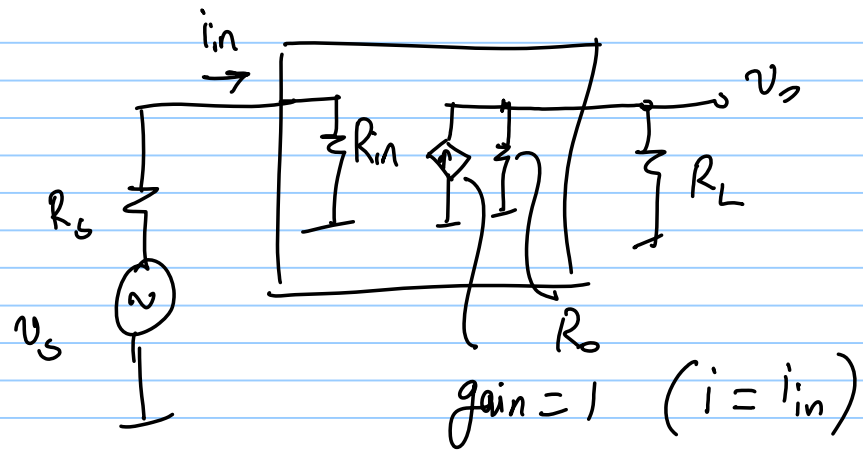$\frac{1}{g_m} \rightarrow \frac{1}{g_m} \cdot \left(\text{loop gain} \right)$




g_m


r_{ds}

25/10/17

Lec 16

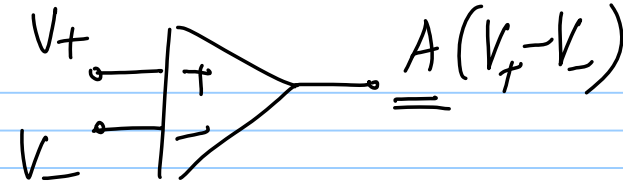


One
Stage
Opamp

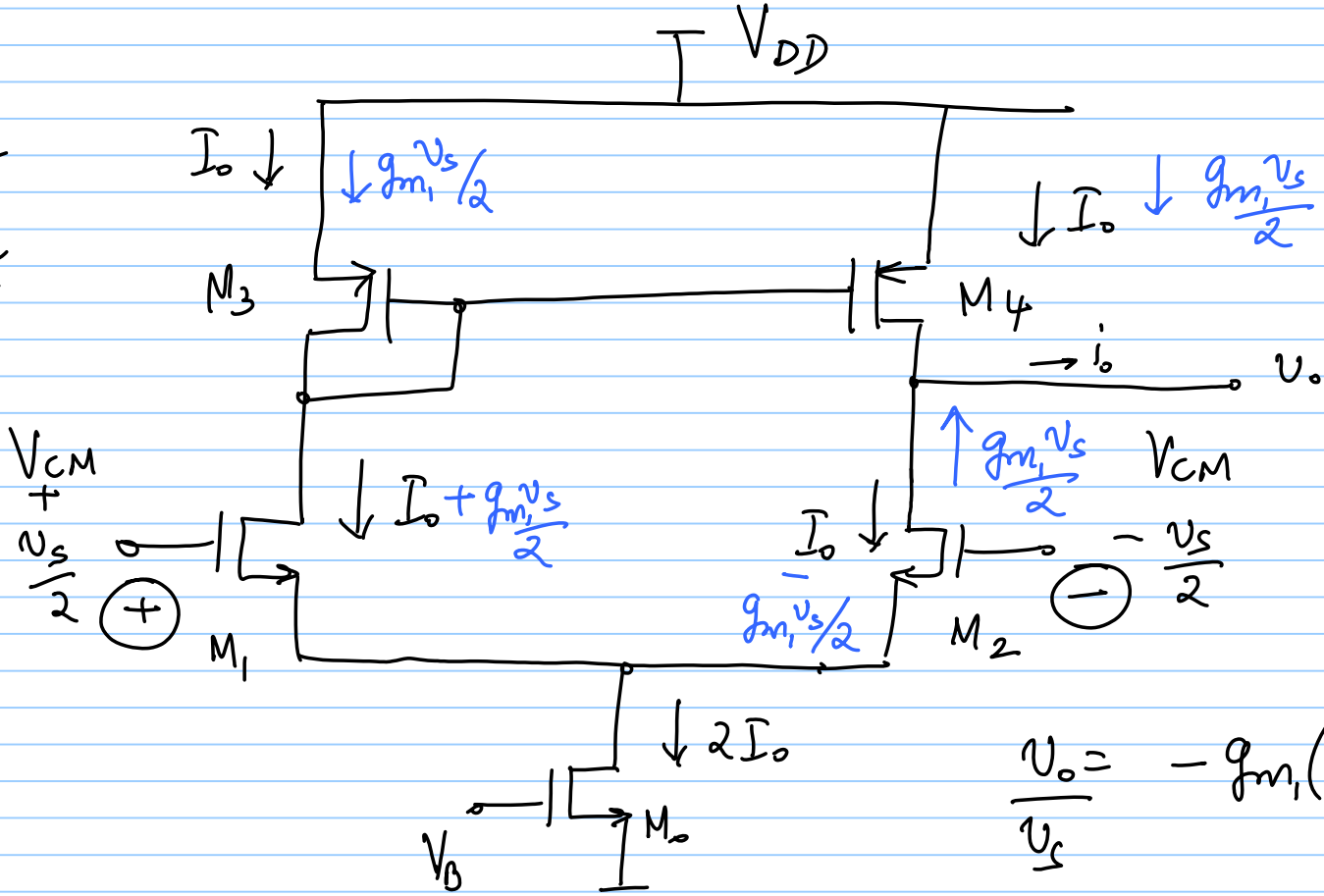

$i_o = g_{m1} v_s$
flows through
 r_{ds2} & r_{ds4}
(parallel combo)

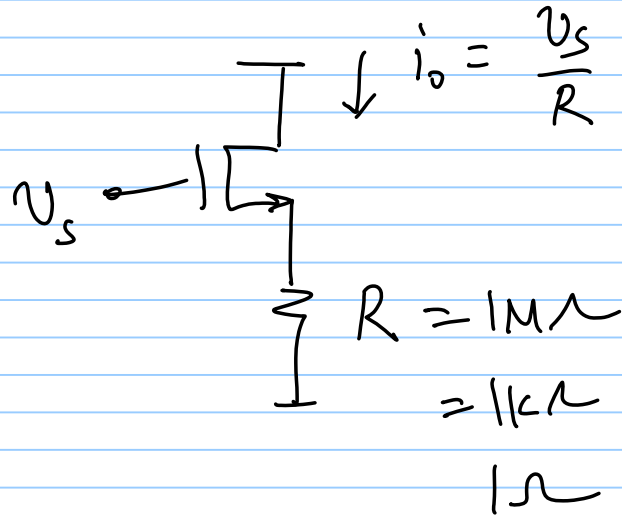
$$\frac{v_o}{v_s} = -g_{m1} (r_{ds2} \parallel r_{ds4}) \quad \text{DC or low-freq. gain of opamp}$$




$$i_o = \frac{g_m}{1 + g_m R} \cdot v_s$$


$$g_m \rightarrow \infty$$




 $g_m R \rightarrow \infty$
 g_m

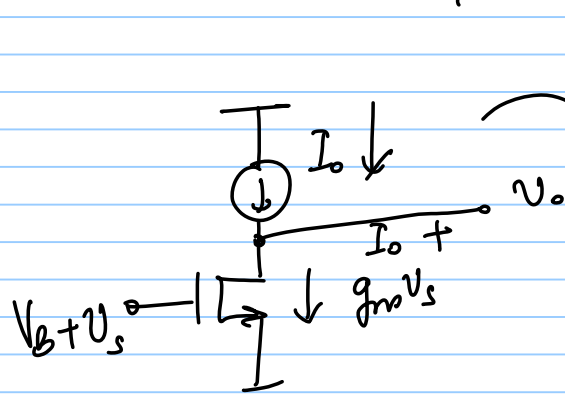

$$-g_m r_{ds}$$

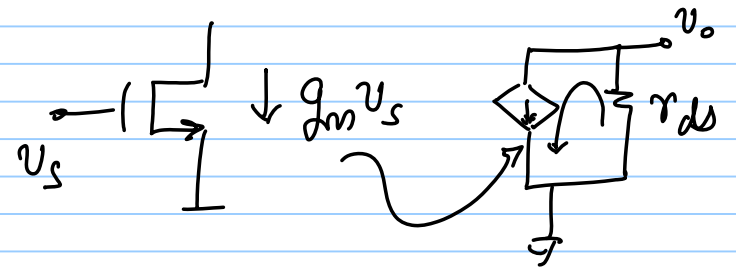

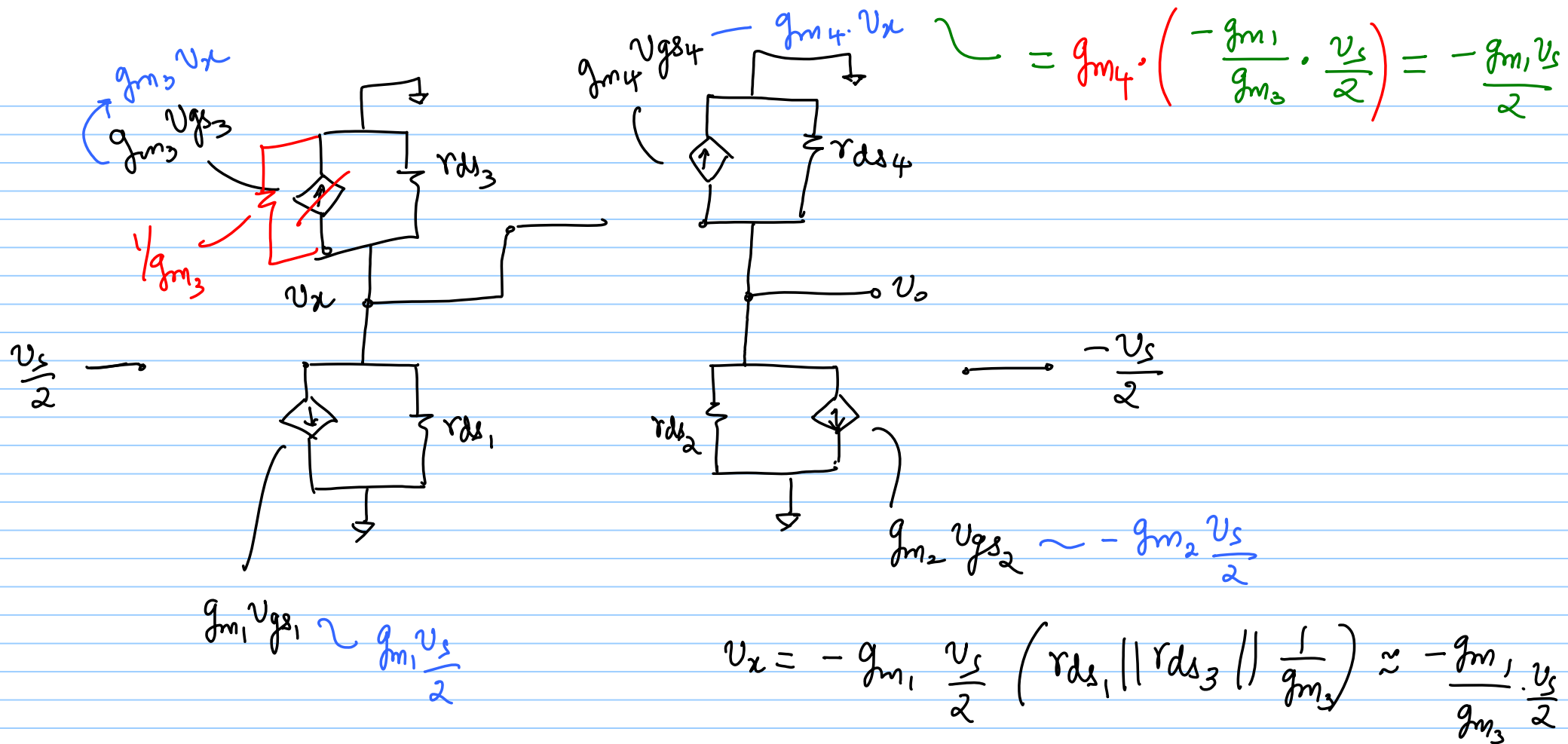

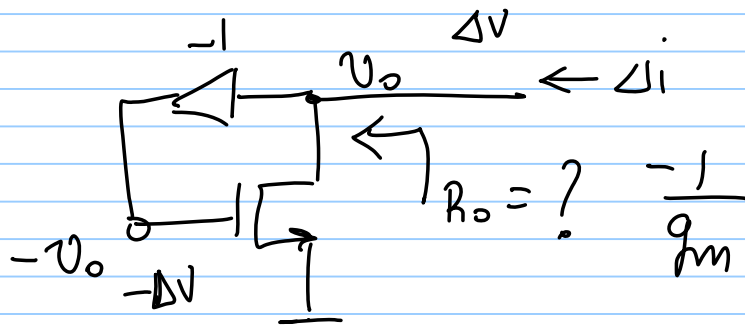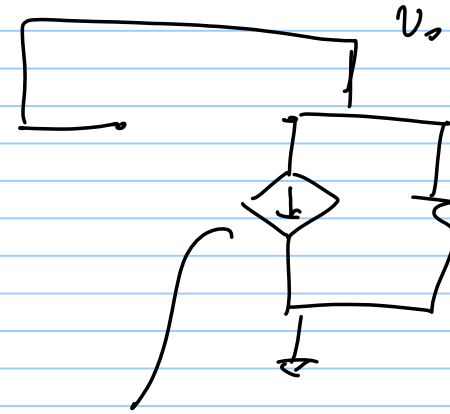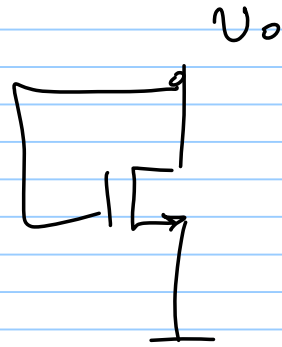

$$i = g_m \cdot v_o \Rightarrow R_o = \frac{1}{g_m}$$


$$\frac{\Delta v}{\Delta i} = R_o$$

$$v_o = g_{m1} v_s (r_{ds2} \parallel r_{ds4})$$


$$\frac{v_o}{v_s} = g_{m1} (r_{ds2} \parallel r_{ds4})$$

$$M_1 = M_2$$

$$M_3 = M_4$$

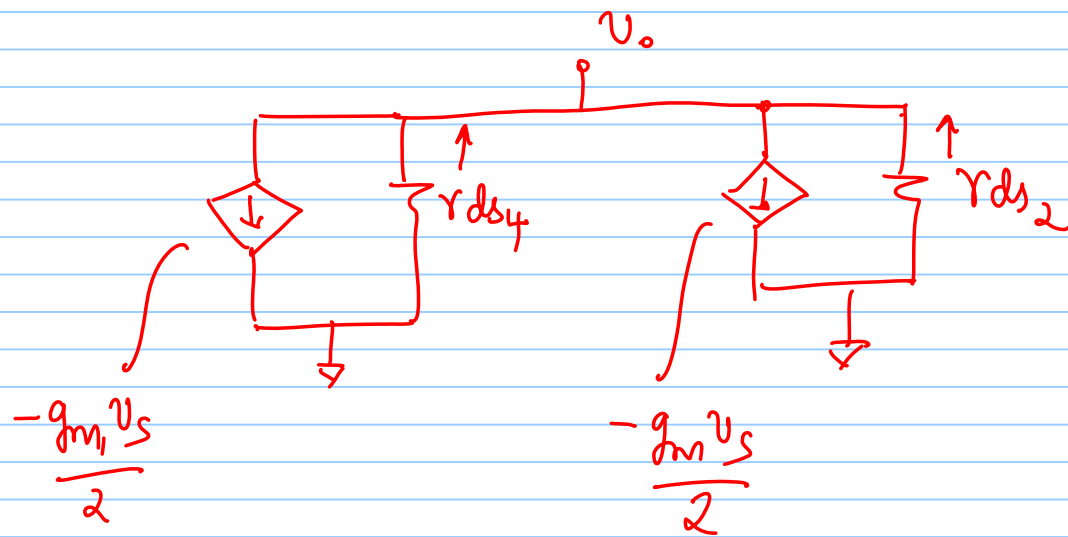

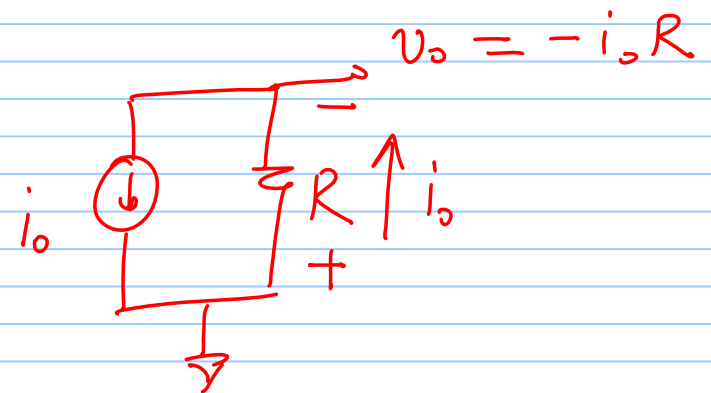
$$v_o = -(\pm g_m v_s) (r_{ds2} \parallel r_{ds4})$$






26/10/17

Lec 17

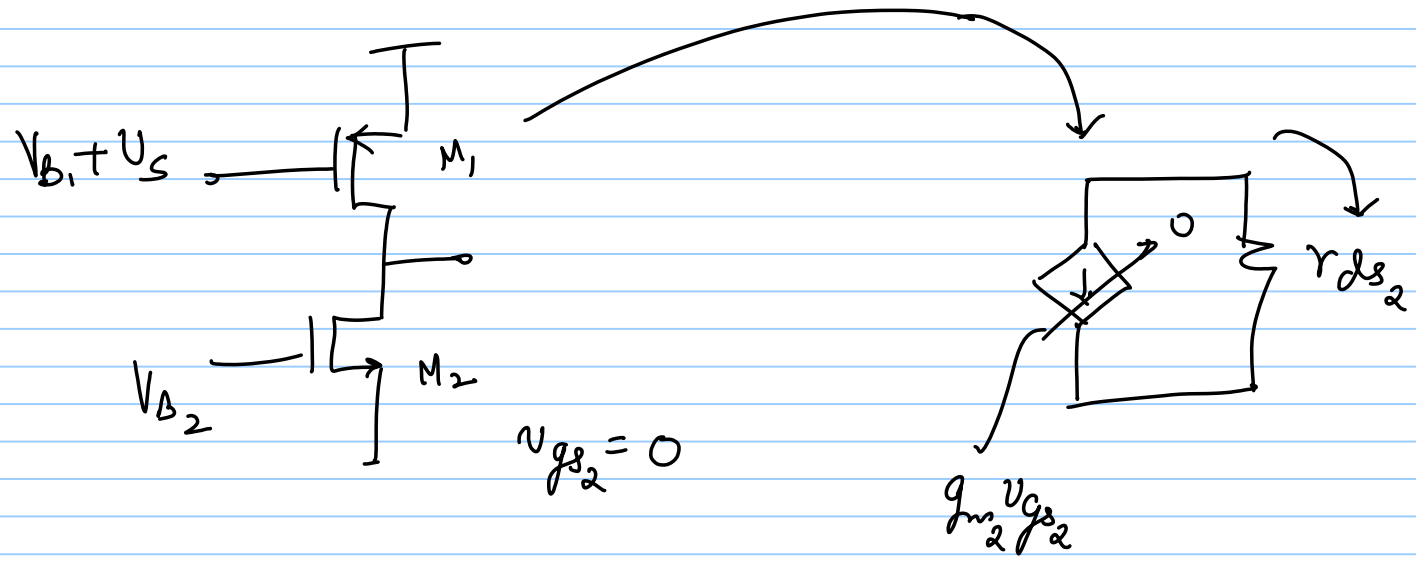CM analysis of 1-stage opamp - H.W. exercise



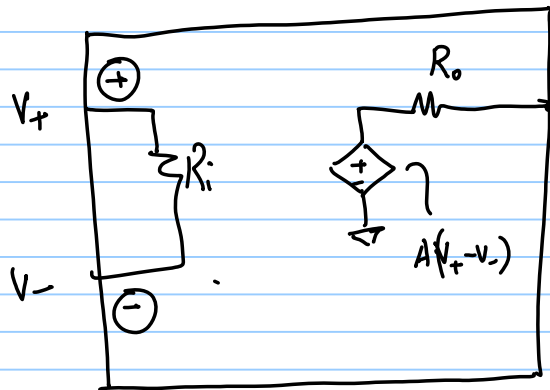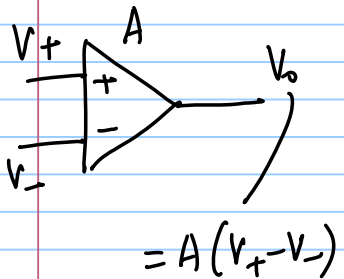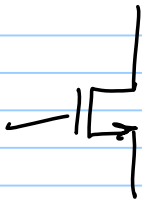1) Frequency behaviour of opamp \rightarrow affects freq. response of closed loop amplifier





$$R_i = \infty$$


$$A = g_{m1} (r_{ds2} \parallel r_{ds4})$$

$$R_o = r_{ds2} \parallel r_{ds4} \quad (\text{large})$$

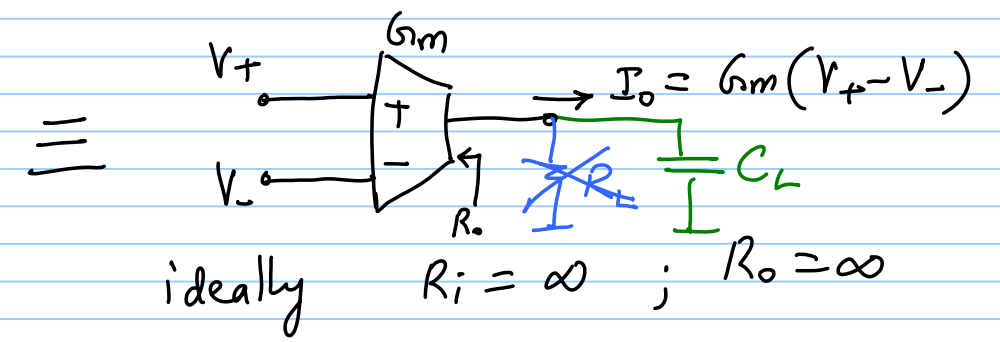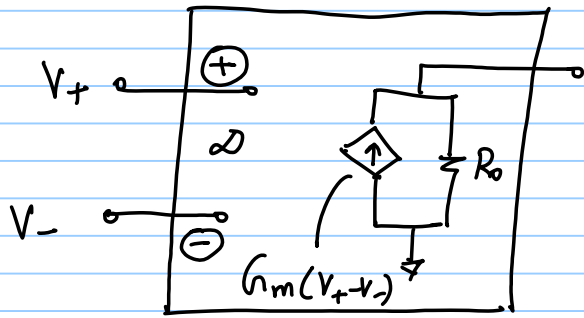CMOS opamps - Operational Transconductance Amplifiers (OTA)



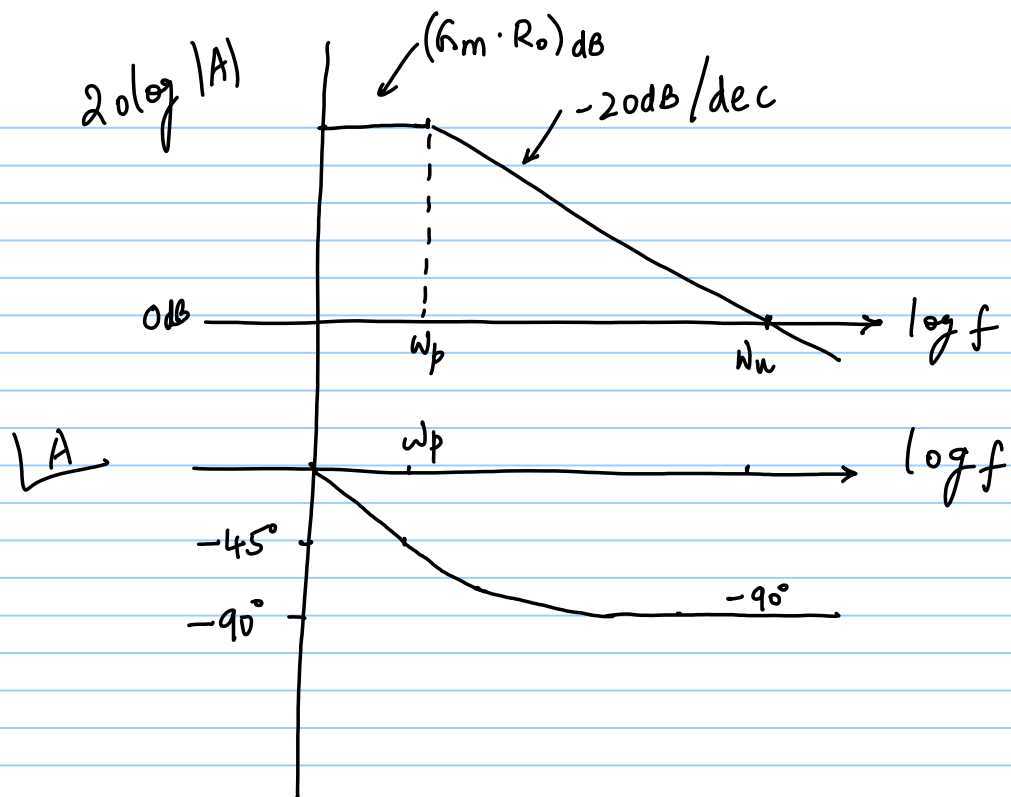- * for 1-stage opamp, $G_m = g_{m_{1-2}}$
- * Do not drive resistive loads
- * Can drive capacitive loads



$$w_u = \text{unity gain frequency} = g_m R_o \cdot w_p$$

$$w_p = \frac{1}{R_o C_L}$$

$$A(s) = \frac{A_o}{1 + s/w_p} = \frac{g_m R_o}{1 + s/w_p}$$

$$20 \log |A(s)| = 0 \text{ dB @ } w_u$$

$$\text{or } |A(s)| = 1 \text{ @ } w_u$$

$$w_u \gg w_p \Rightarrow w_u = g_m R_o \cdot w_p$$

$$\frac{g_m R_o}{\sqrt{1 + \frac{w_u^2}{w_p^2}}} = 1$$


$$\cos \theta \approx 1$$

$$\sin \theta \approx \theta$$



$$\angle A(s) = -\tan^{-1} \left(\frac{w}{w_p} \right)$$

$$\tan \theta = \frac{\sin \theta}{\cos \theta}$$

; if θ is very small \Rightarrow

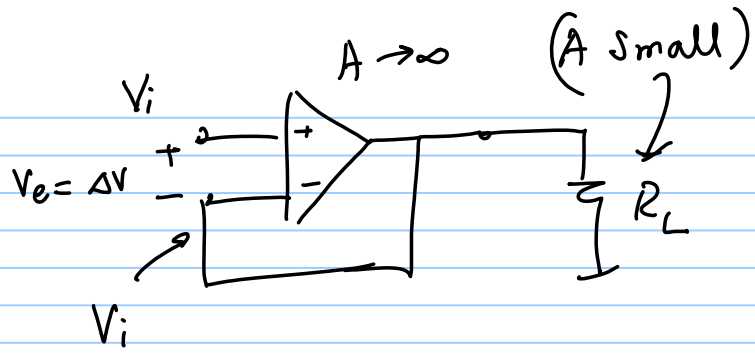

X ✓

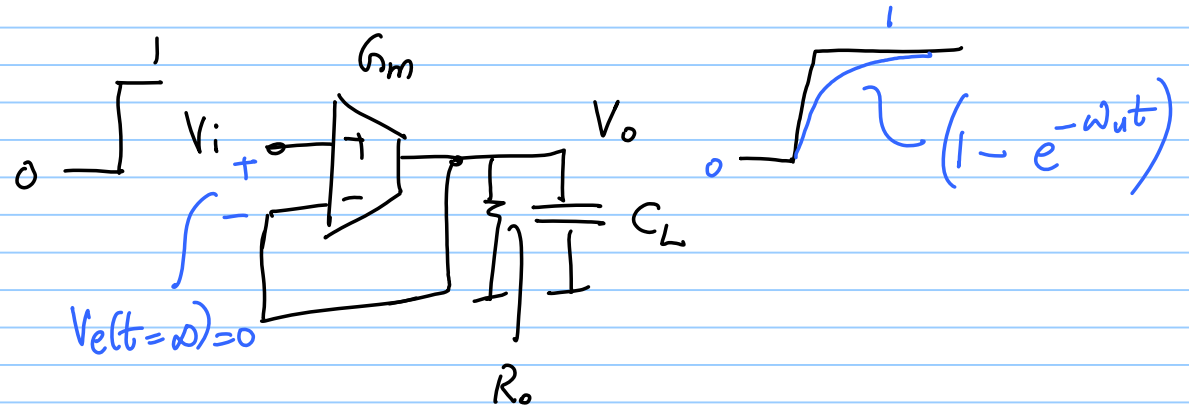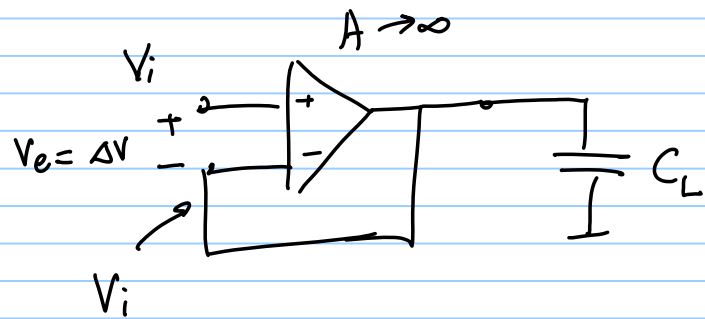

$$A(s) = \frac{f}{1 + A(s) \cdot f \cdot C \cdot L \cdot G}$$



$$A(s) = \frac{G_m R_o}{1 + s/\omega_p}$$

$$f = 1$$



$$\begin{aligned}
 CLG &= \frac{G_m R_o / (1 + s/\omega_p)}{1 + G_m R_o / (1 + s/\omega_p)} = \frac{G_m R_o}{G_m R_o + 1 + \frac{s}{\omega_p}} \\
 &= \frac{G_m R_o / (1 + G_m R_o)}{1 + \frac{s}{\omega_p (1 + G_m R_o)}} \approx \frac{1}{1 + \frac{s}{\omega_u}} \quad \text{if } G_m R_o \gg 1
 \end{aligned}$$



Steady state error = 0

MOSFET capacitances

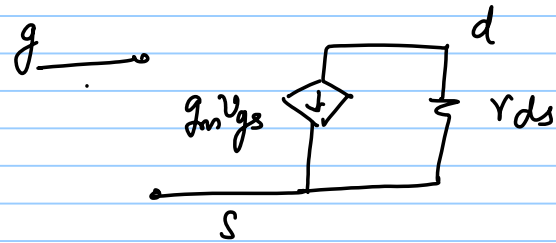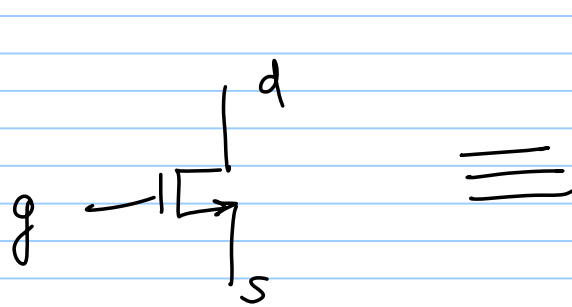


low frequency model

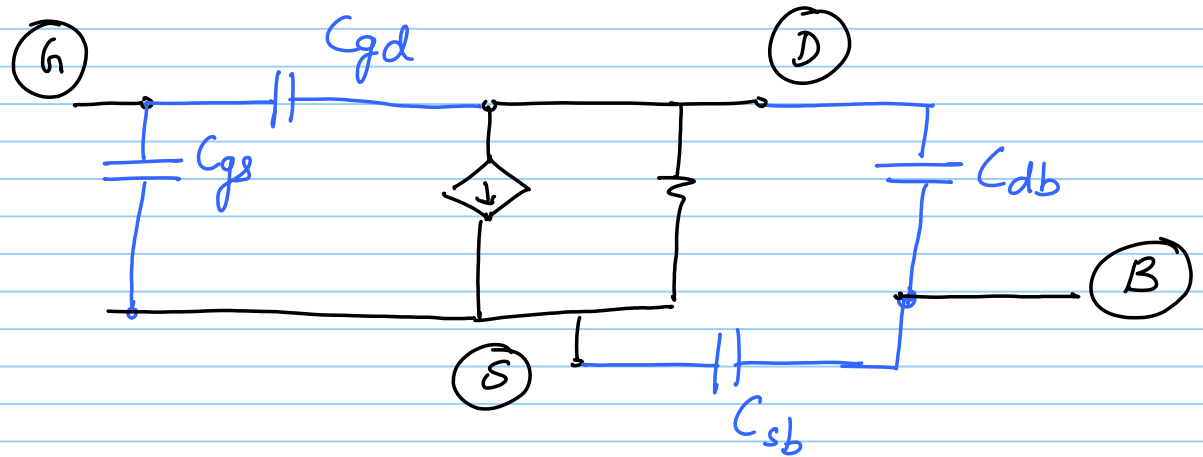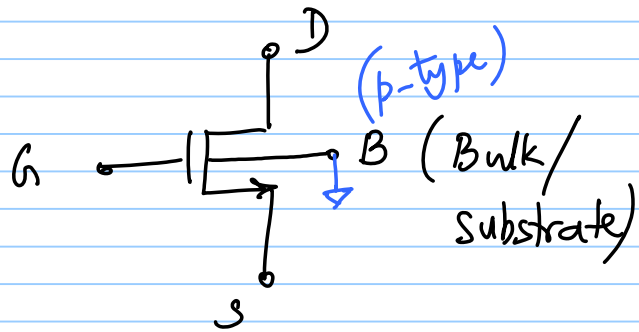

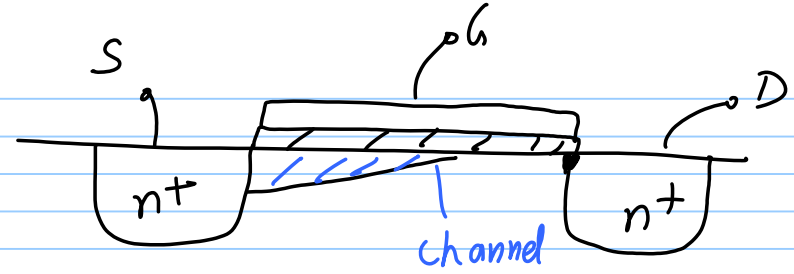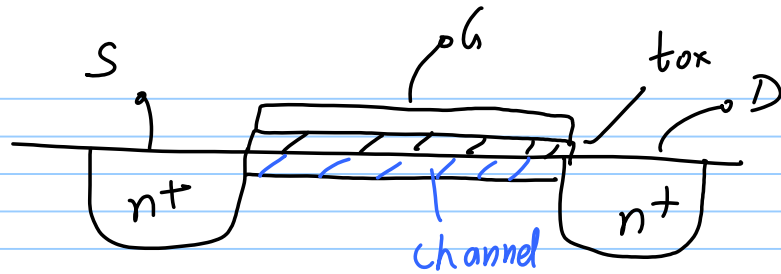


p-sub


p-sub

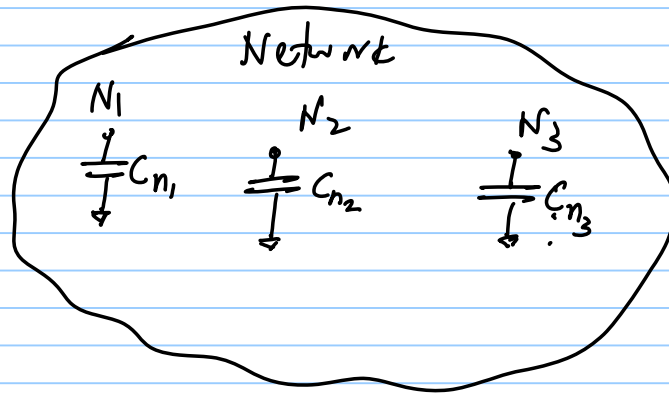


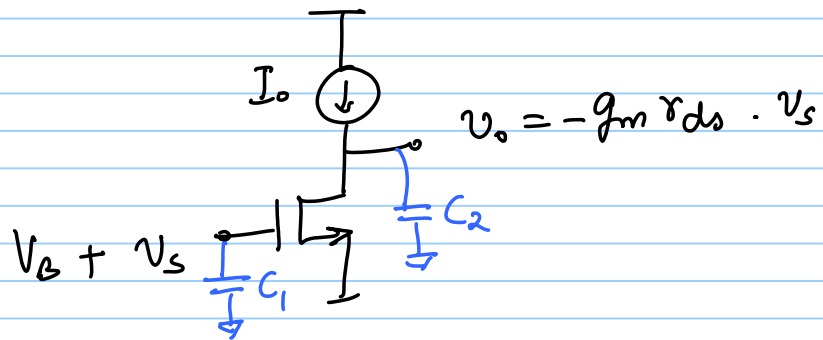C_{gs} , C_{db} etc. are functions of W , L & C_{ox} and drain area (or source)


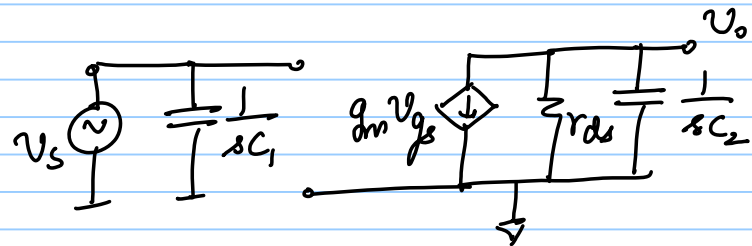
$$\frac{v_o}{v_s} = \frac{-g_m r_{ds}}{1 + s C_2 r_{ds}}$$



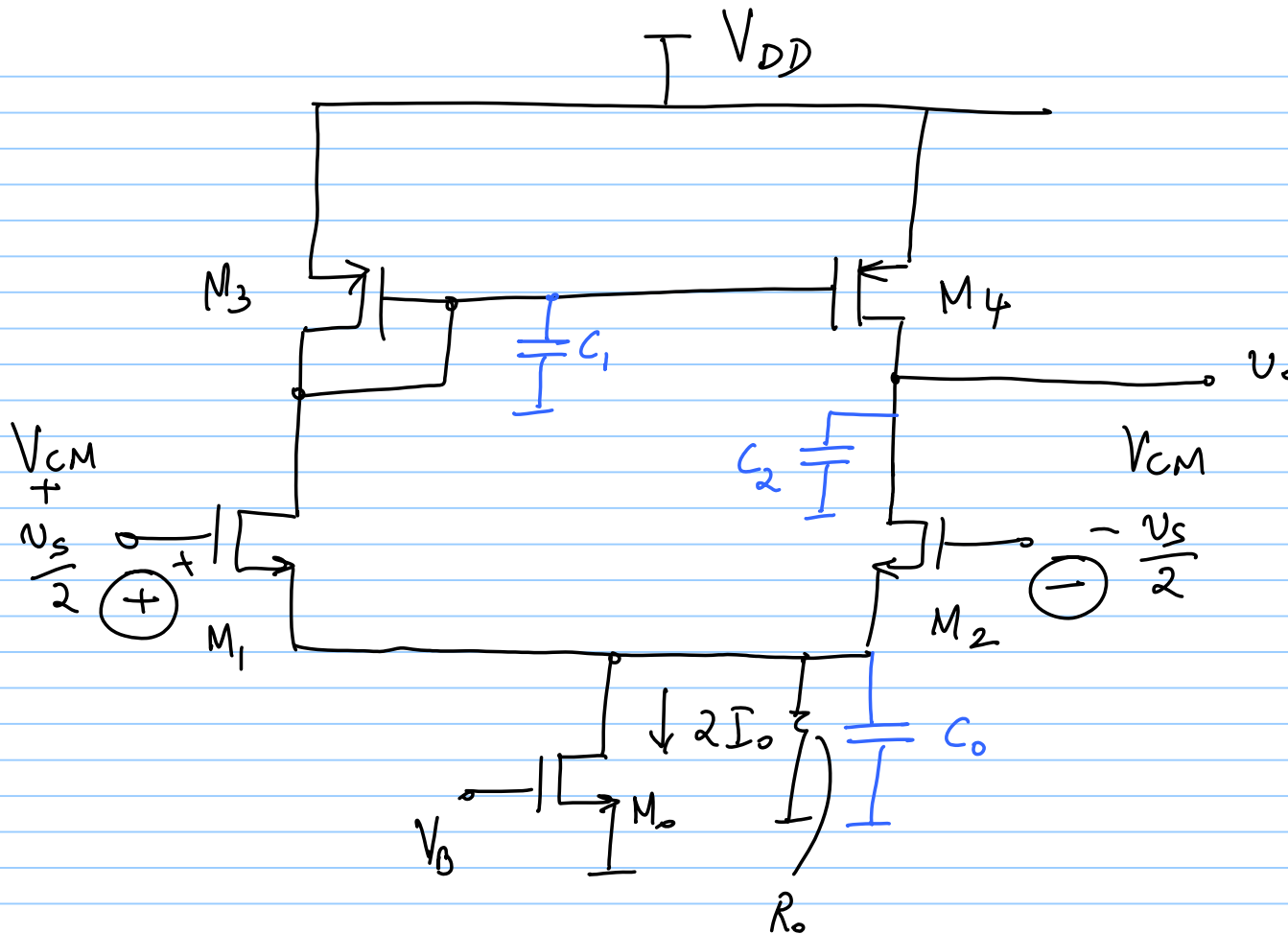

* C_o will not affect A_{dm}

* C_o will affect A_{cm} (degrades A_{cm} at high frequencies)

* at low freq:


$$A_{cm} = 0; CMRR = \infty$$

at high freq.

$$A_{cm} \rightarrow A_{dm}; CMRR \rightarrow 1$$


HW exercise

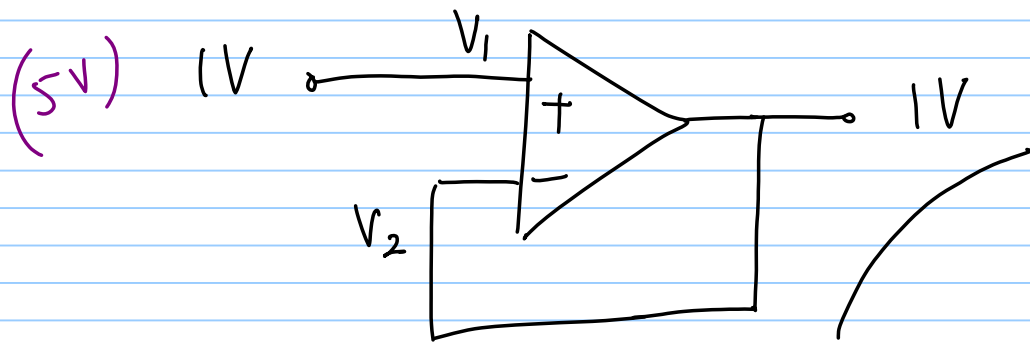Differential gain $A(\omega)$
frequency response



$$V_{CM} = 1V$$


$$V_{dm} = 0V$$

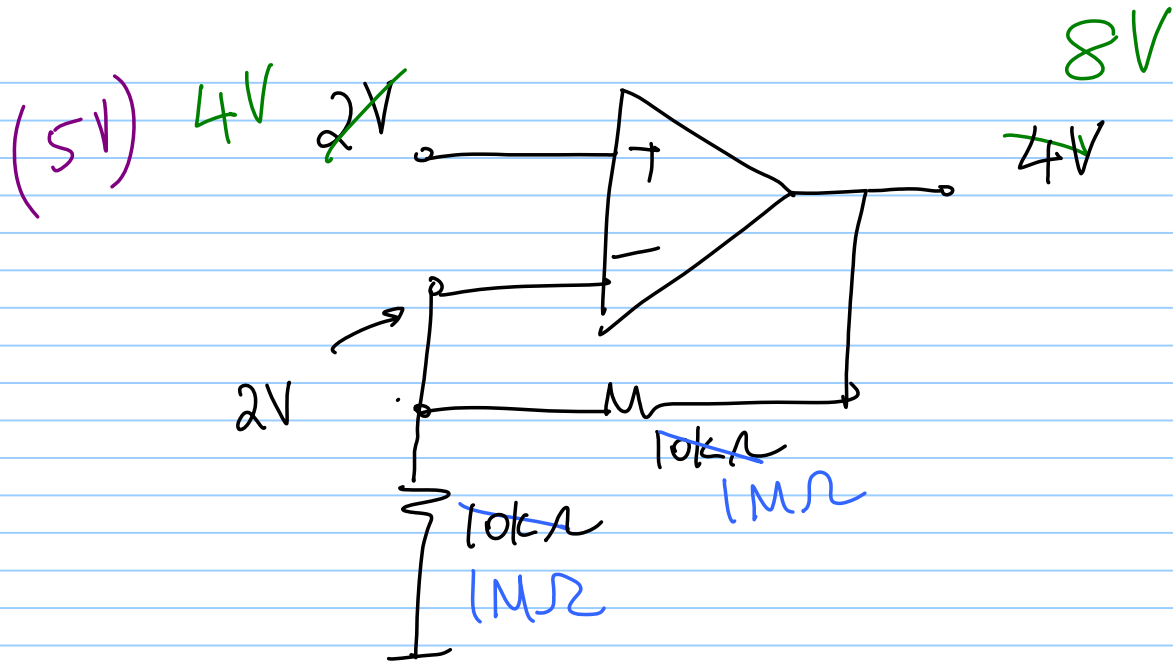

$$V_{cm} = 2V$$

$$V_{dm} = 0$$

4V

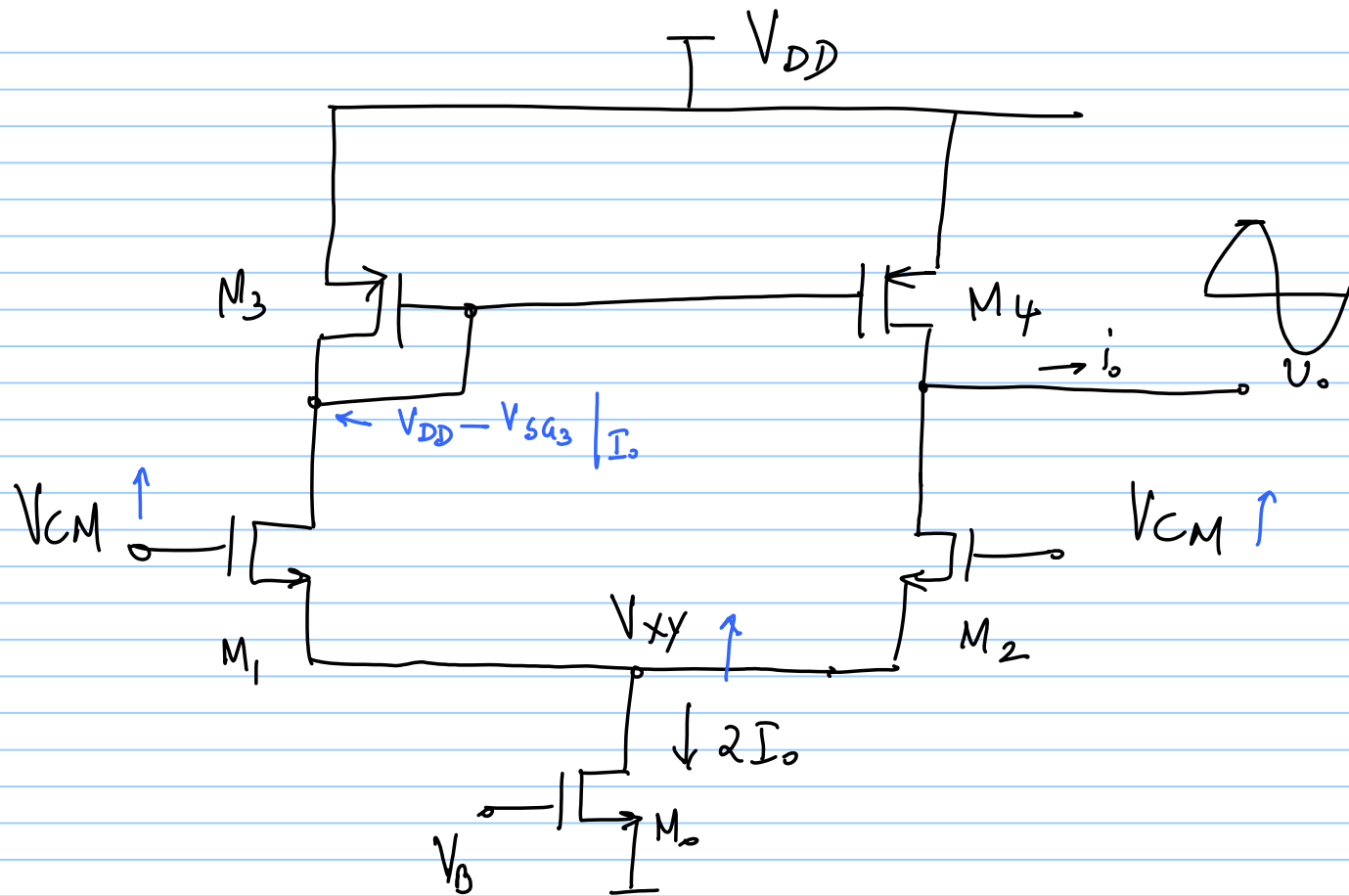

$\neq \downarrow V_{CM}$
 $V_{xy} = (V_{CM} - V_{as1}) \downarrow$
 at same rate
 till M_0 goes
 into triode.

$$\begin{aligned}
 V_{CM_{min}} &= V_B - V_{T_0} + V_{as1} \\
 &= V_{Dsat_0} |_{2I_0} \\
 &\quad + \\
 &\quad V_{as1} |_{I_0}
 \end{aligned}$$

* $\uparrow V_{CM} \Rightarrow V_{C1}$ increases

$$V_{D1} = V_{DD} - V_{S43} | I_0 = \text{constant}$$

M_1 moves towards triode region

$$V_{CM \max} = V_{DD} - V_{S43} | I_0 + V_{T1}$$

Input common-mode range of opamp

$$ICMR = \{ V_{CM \min}, V_{CM \max} \}$$


* Output swing limits: $V_{O \max} = V_{DD} - V_{S44} + V_T = V_{DD} - V_{SD \text{sat}4}$




$$V_{O \min} = V_{CM} - V_T$$

(assuming large gain)



31/10/17





Lec 18

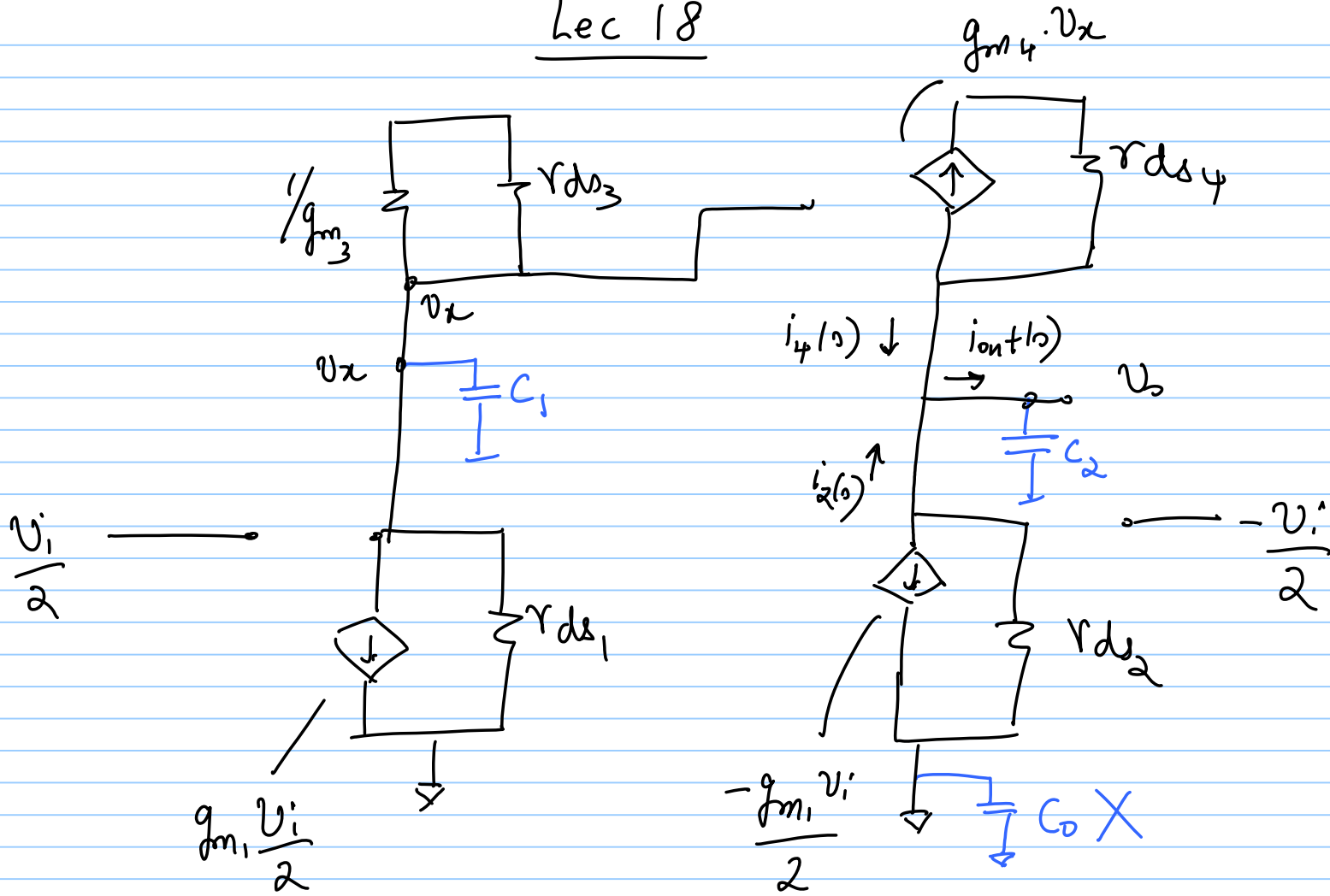

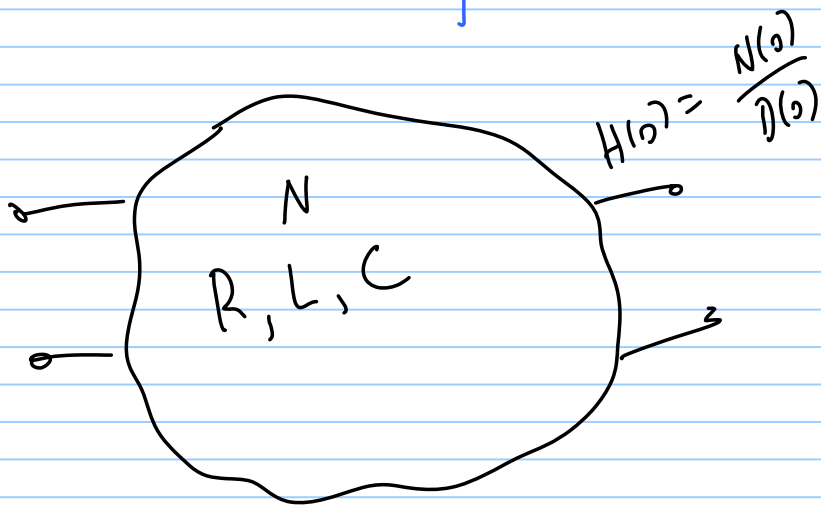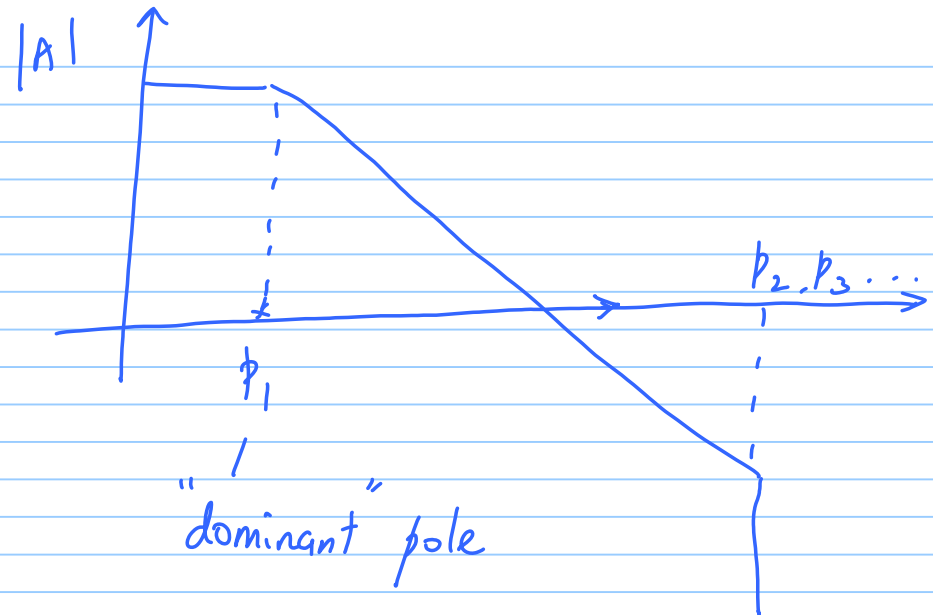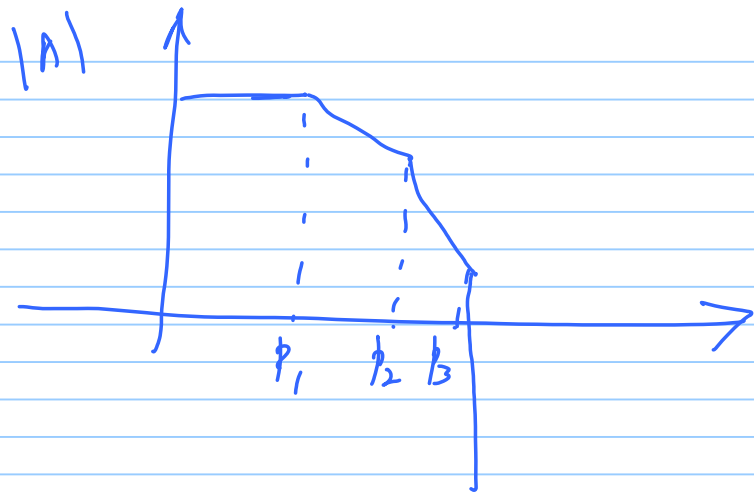

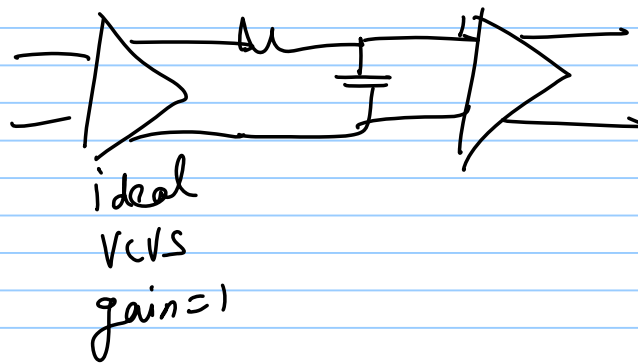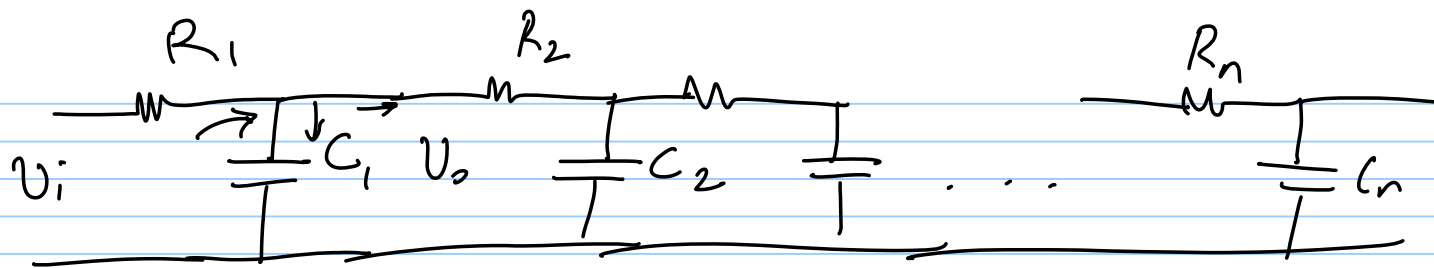of poles =
 "order" of a system
 = order of $D(s)$



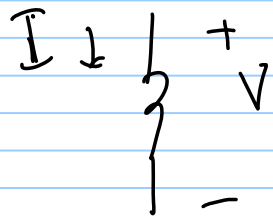
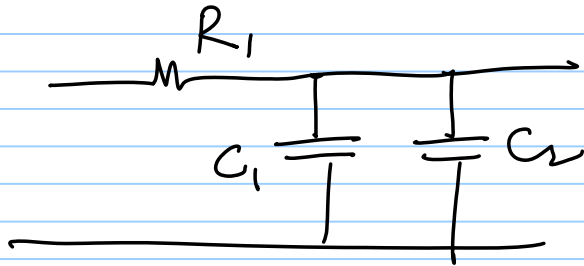
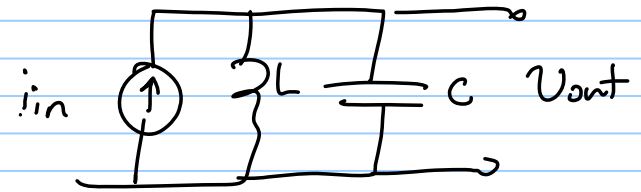
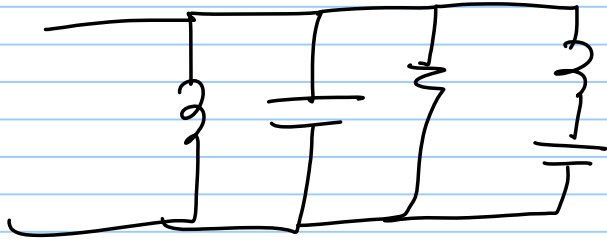


$$V = L \cdot \frac{dI}{dt}$$



$$V(s) = sL \cdot I(s)$$

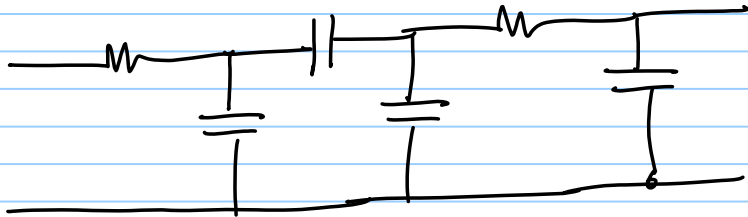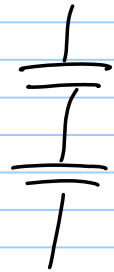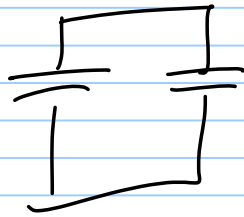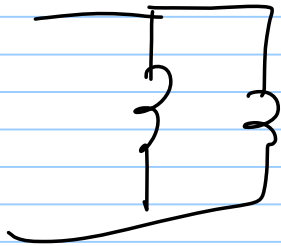Order of system = # of v reactive elements
(independent)





$$H(s) = A_0 \cdot \frac{(1 + \frac{s}{z_1}) (1 + \frac{s}{z_2}) \dots (1 + \frac{s}{z_m})}{(1 + \frac{s}{p_1}) (1 + \frac{s}{p_2}) \dots (1 + \frac{s}{p_n})} \quad \begin{array}{l} m \text{ zeroes} \\ n \text{ poles} \end{array}$$

(a) $\omega = -z_1, -z_2, \dots, -z_m \Rightarrow H(s) = 0$

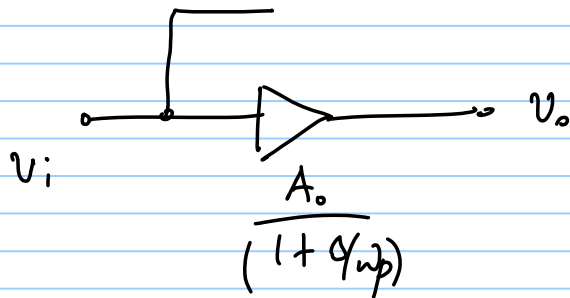(a) $\omega = -p_1, -p_2, \dots, -p_n \Rightarrow H(s) = \infty$


$\frac{v_o}{v_i}(s) = 0$ @ any particular frequencies



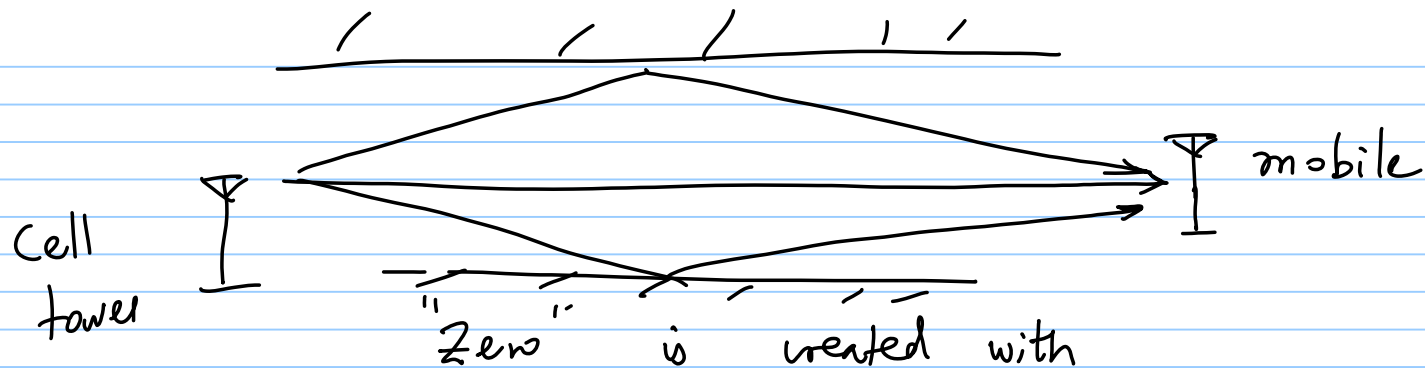


"destructive"
multipath
freq. dependent
phase is freq. dep.

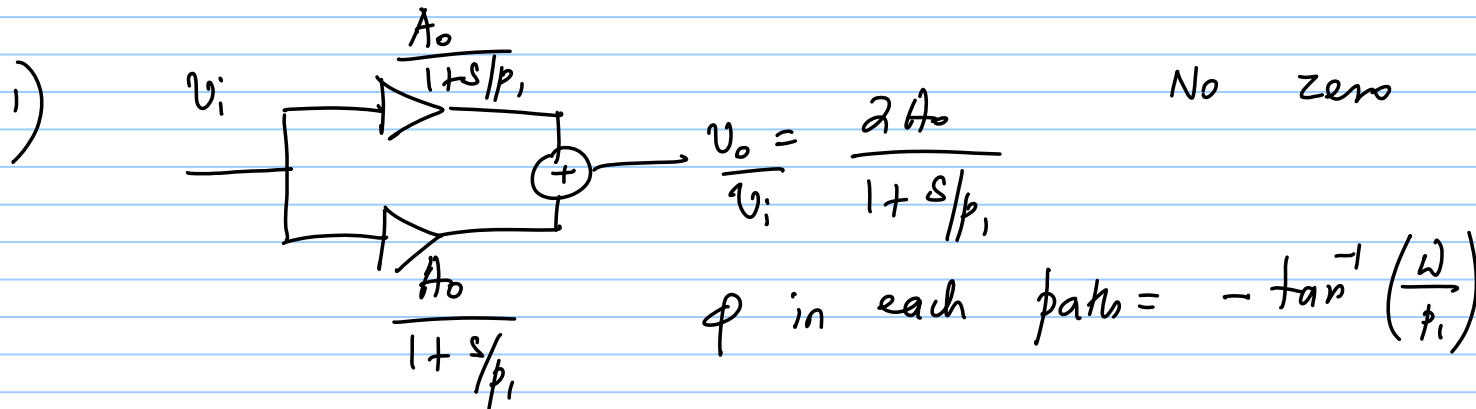"Zero" is created with
2 or more paths with
different phase shifts.




2)

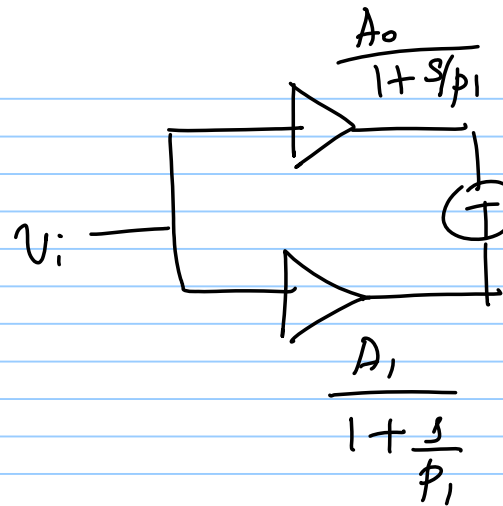

$$\frac{v_o}{v_i} = \frac{A_0 + A_1}{1 + s/p_1}$$


No zero

3)

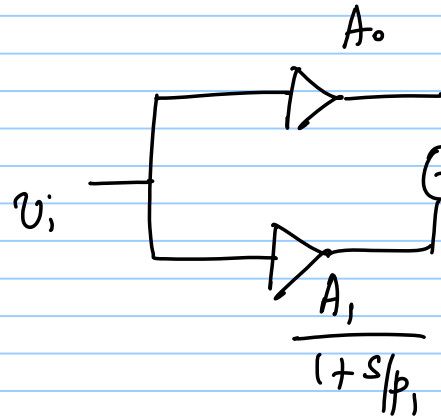

$$\begin{aligned} \frac{v_o}{v_i} &= A_0 + \frac{A_1}{1+s/p_1} = \frac{A_0 + A_1 + \frac{A_0 s}{p_1}}{1+s/p_1} \\ &= (A_0 + A_1) \cdot \frac{1 + s \cdot \frac{A_0}{A_0 + A_1} \cdot \frac{1}{p_1}}{1 + s/p_1} \end{aligned}$$

4)

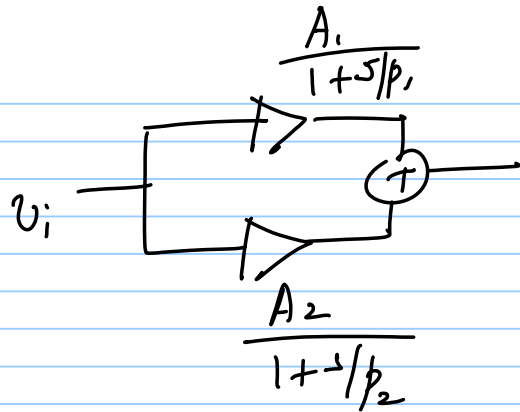


$$\frac{v_o}{v_i} = \frac{A_1}{1+s/p_1} + \frac{A_2}{1+s/p_2}$$

$$= \frac{A_1 + A_2 + \frac{A_1 s}{p_2} + \frac{A_2 s}{p_1}}{(1+s/p_1)(1+s/p_2)}$$

1 zero
2 poles

5)

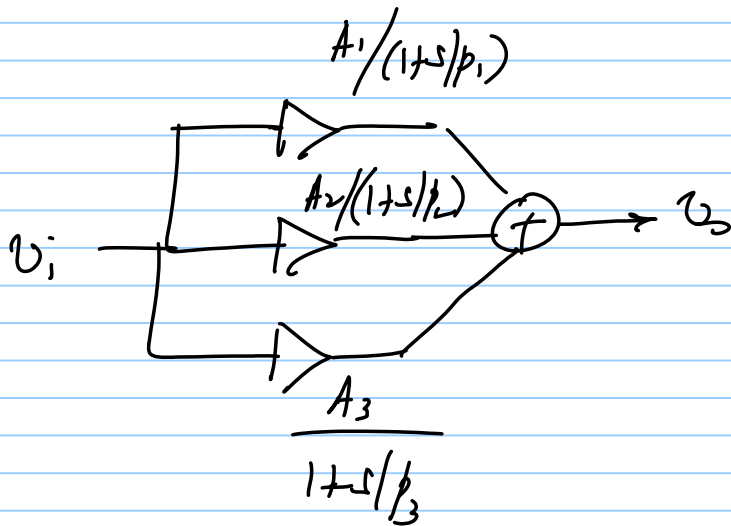

3 poles
2 zeroes

For 1-stage opamp

$$\frac{v_o}{v_i}(s) = ?$$

$$v_x(s) = -g_{m1} \frac{v_i}{2} \left[\frac{1}{g_{m3}} \parallel \frac{1}{sC_1} \right] = -\frac{g_{m1} v_i}{g_{m3}} \cdot \frac{1}{2} \cdot \left[\frac{1}{1 + \frac{sC_1}{g_{m3}}} \right]$$

$$i_4(s) = -g_{m4} v_x(s) = g_{m1} \frac{v_i}{2} \left[\frac{1}{1 + \frac{sC_1}{g_{m3}}} \right]$$

$$i_2(s) = g_{m2} \frac{v_i}{2}$$

$$i_{out}(s) = i_2(s) + i_4(s) = g_{m1} \frac{v_i}{2} \left[1 + \frac{1}{1 + \frac{sC_1}{g_{m3}}} \right]$$

$$i_{out}(s) = g_{m1} \frac{v_i}{2} \left[\frac{2 + \frac{sC_1}{g_{m3}}}{1 + \frac{sC_1}{g_{m3}}} \right]$$

$$= g_{m1} v_i \cdot \frac{1 + \frac{sC_1}{2g_{m3}}}{1 + \frac{sC_1}{g_{m3}}}$$

Zero @ $-\frac{2g_{m3}}{C_1}$

Pole @ $-\frac{g_{m3}}{C_1}$


$$v_o(s) = i_{out}(s) \cdot \left(r_{ds2} \parallel r_{ds4} \parallel \frac{1}{sC_2} \right)$$

$r_{ds2} \parallel r_{ds4} = r_o$

$$= i_{out}(s) \cdot \frac{r_{ds2} \parallel r_{ds4}}{1 + sC_2(r_{ds2} \parallel r_{ds4})} = i_{out}(s) \cdot \frac{r_o}{1 + sC_2 r_o}$$

$$v_o(s) = \underbrace{g_{m1} r_o}_{\text{DC gain (low-freq. gain)}} \cdot \underbrace{\frac{1 + \frac{sC_1}{2g_{m3}}}{\left(1 + \frac{sC_1}{g_{m3}}\right) \left(1 + \frac{sC_2}{g_o}\right)}}_{\text{gain freq. response}} \cdot v_i(s)$$
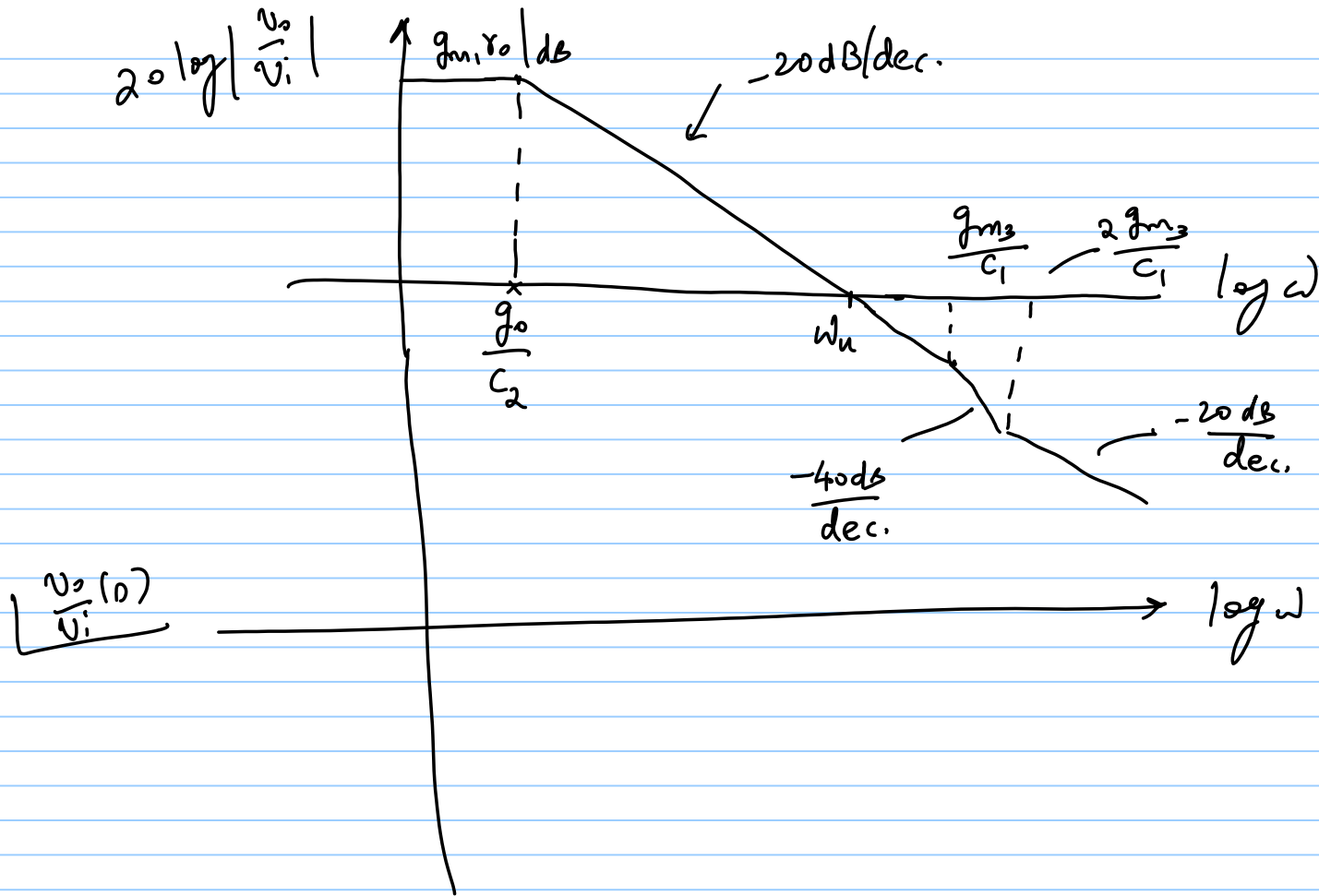
$$\left. \begin{array}{l} g_{m3} \gg g_o \\ C_2 \gg C_1 \end{array} \right) \text{Assumption}$$



HW: What happens at pole & zero freq. in bode plot?

$$A(s) = \frac{A_0}{1 + s/\omega_p} \quad ; \quad A(j\omega) = \frac{A_0}{1 + \frac{j\omega}{\omega_p}}$$

$$\textcircled{a} \quad \omega = \omega_p \quad : \quad |A(j\omega)| = \frac{1}{\sqrt{2}} A_0$$


$$A(s) = A_0 (1 + s/\omega_z)$$

$$\textcircled{a} \quad \omega = \omega_z \quad : \quad |A(j\omega)| = \sqrt{2} A_0$$

7/11/17


Lec 19

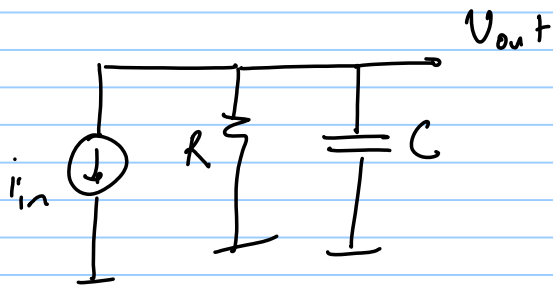- * Every node has some capacitance to ground
- * Every node in signal path will contribute a pole



$$\frac{v_{out}}{i_{in}}(s) = (R) \cdot \frac{1}{1 + sRC}$$

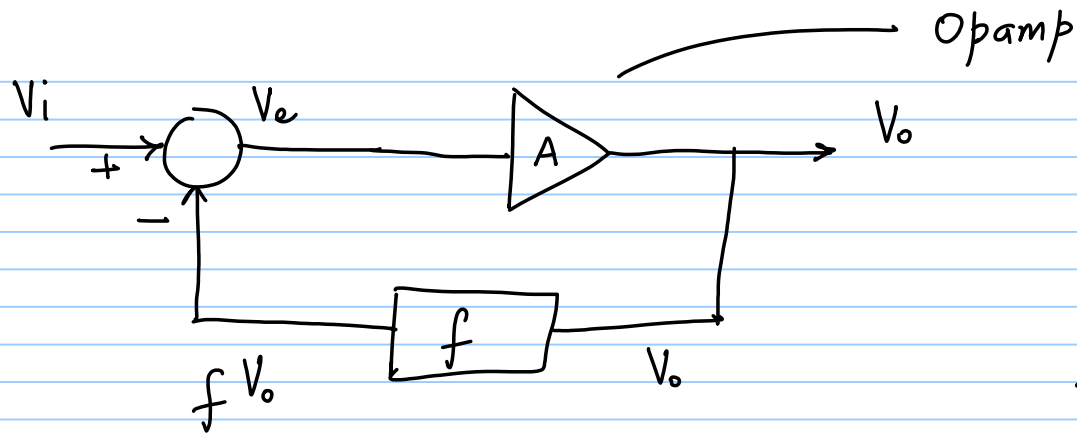- * # of poles affects negative feedback behaviour



$$\frac{V_o}{V_i} = \frac{1}{f} \cdot \frac{A f}{1 + A f}$$

$$\text{If } A f \rightarrow \infty \quad \{ \text{normally } A \rightarrow \infty \}$$

(loop gain)

$$\frac{V_o}{V_i} = \frac{1}{f} \quad \text{or} \quad V_o = \frac{V_i}{f}$$

normally $f < 1$, so $\frac{V_o}{V_i} \geq 1$

* $A = A(s)$

* $\frac{V_o(s)}{V_i} = \frac{1}{f} \cdot \frac{A(s) \cdot f}{1 + A(s) \cdot f} = \text{closed loop gain}$
 $CLG(s)$

Negative feedback is operational when $A(s) \cdot f \gg 1$

If $A(s)$ has poles, what happens?

$CLG(s)$ should be linear $\omega \ll \omega_p (1 + A_o f)$

e.g. $A(s) = \frac{A_0}{1 + s/\omega_p}$ $LG = f \cdot A(s) = \frac{f A_0}{1 + s/\omega_p}$

$$CLG(s) = \frac{1}{f} \cdot \frac{f \cdot A_0 / (1 + s/\omega_p)}{1 + f \cdot A_0 / (1 + s/\omega_p)} = \frac{1}{f} \cdot \frac{A_0 f}{1 + A_0 f} \cdot \frac{1}{1 + \frac{s}{\omega_p (1 + A_0 f)}}$$

$$f A_0 = 1000$$

$$\omega_p = (2\pi \cdot 10k) \text{ rad/s}$$



$$\text{pole of } LG = \omega_p = 2\pi \cdot 10k \text{ rad/s}$$

$$\text{poles of } CLG = 2\pi \cdot 10k \cdot 1001 \text{ rad/s.}$$



Stability : bounded input
 bounded output

We want "unconditionally
 stable" system

Extreme case: output without input

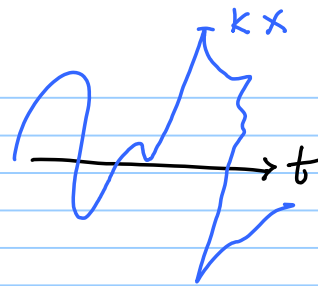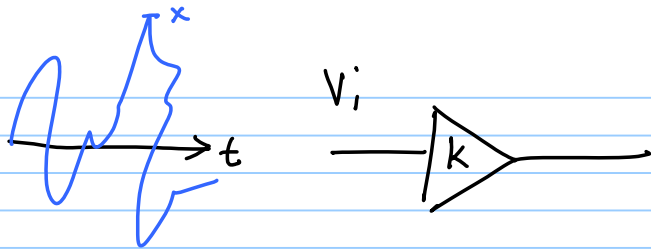

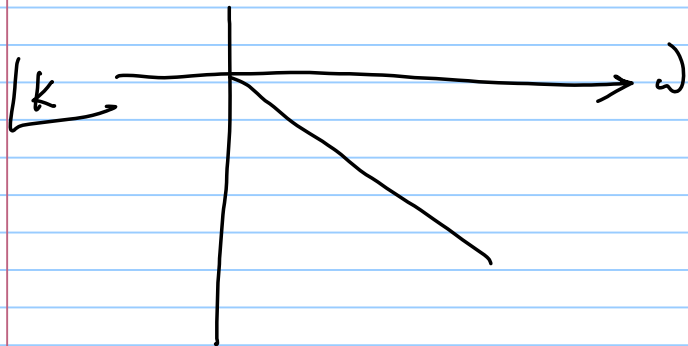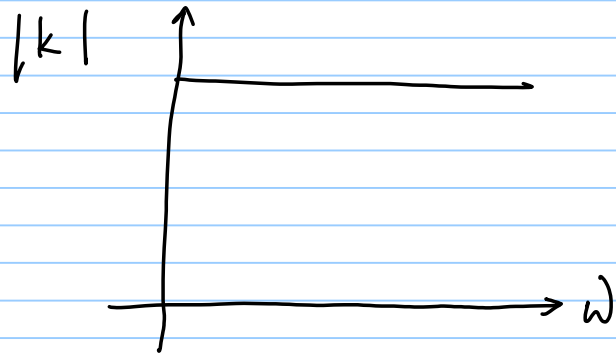phase should be linearly related to frequency




group delay should be constant

↳ delay of each freq. component of signal

k, τ

$$V_i = A e^{j\omega t}$$

$$V_o = kA e^{j\omega(t+\tau)} = \underbrace{kA}_{|k|} e^{j\omega t} \cdot \underbrace{e^{j\omega\tau}}_{\angle k}$$

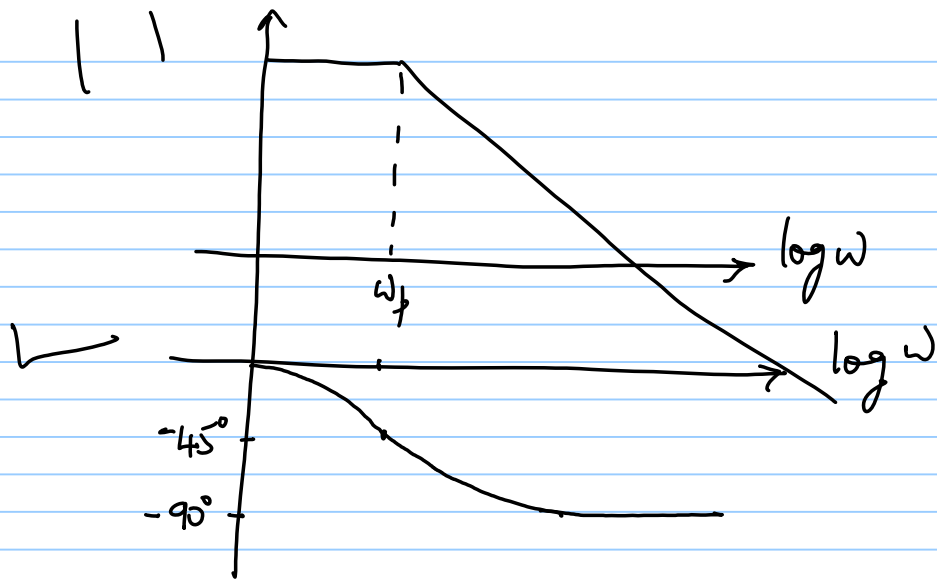

$$\frac{V_o(s)}{V_i} = \frac{1}{f} \cdot \frac{A(s) \cdot f}{1 + A(s) \cdot f}$$

$$V_i = 0$$

$V_o \neq 0$ is possible if

$$1 + A(s) \cdot f = 0$$

$$1 + LG(s) = 0$$

$$f \cdot A(s) = -1$$

$$\left\{ \begin{array}{l} |LG| = 1 \\ \angle LG = -180^\circ \end{array} \right.$$


Barkhausen

Criteria for stability

→ If true, system can become unstable

For most systems, we use

at $\angle L(s) = -180^\circ$, if $|L(s)| \geq 1$ potential for instability

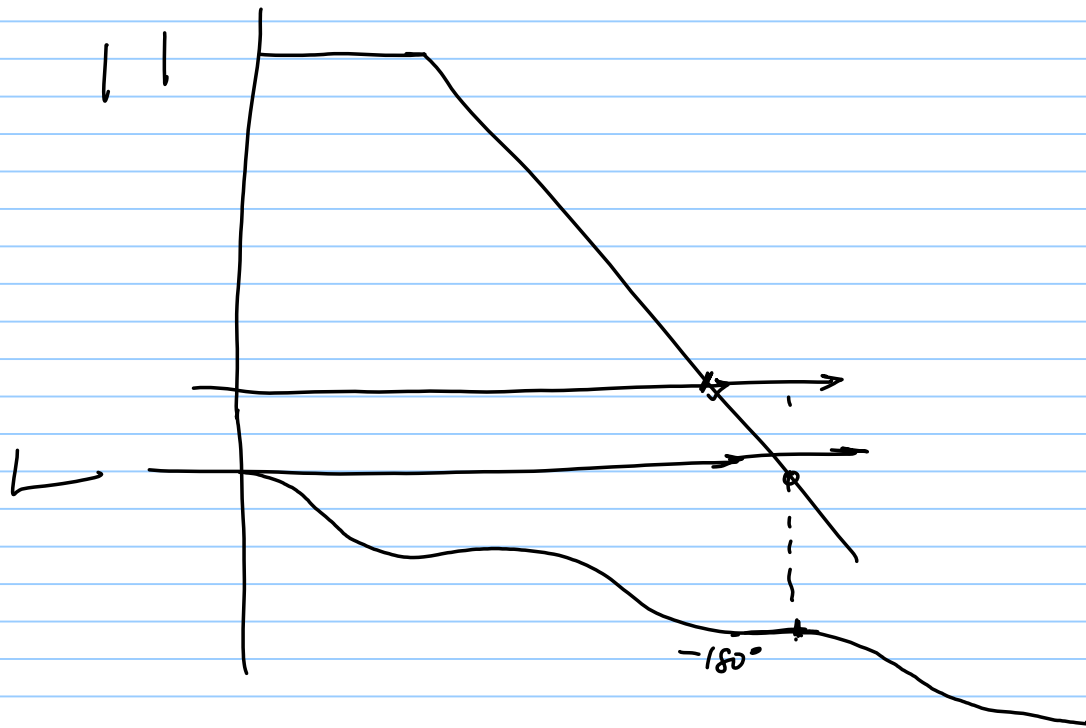

1) 1-pole system

$$A(s) = \frac{A_0}{1 + s/\omega_p}$$

We want large A_0

Easiest way to get large A_0
is to cascade amplifiers

stability = a) poles in LHP

b) $\angle A(s)$ can never go
to -180°

(a) $s \rightarrow \infty$ $\angle A(s) = -90^\circ$

Unconditionally stable

2) 2-pole system

$$A(s) = \frac{A_0}{(1 + s/\omega_p)^2}$$

$$CLA(s) = \frac{1}{f} \cdot \frac{A_{of}}{1 + A_{of}} \cdot \frac{1}{1 + \frac{2s}{A_{of}\omega_p} + \frac{s^2}{\omega_p^2 \cdot A_{of}}} \rightarrow D(s)$$

Stability:

a) LHP poles

b) $\angle G(s) = -180^\circ$ only at $\omega = \infty$

\Rightarrow unconditionally stable

General 2nd order system

Denominator $D(s) = 1 + \frac{s}{\omega_0 \cdot Q} + \frac{s^2}{\omega_0^2}$

$$\frac{s}{\omega_0} = \frac{-1}{2Q} \pm j \sqrt{1 - \frac{1}{4Q^2}}$$


small Q : 2 real poles in LHP

$Q = \frac{1}{2}$: 2 co-incident poles


$Q > \frac{1}{2}$: complex conjugate poles

$Q = \infty$: poles on $j\omega$ axis

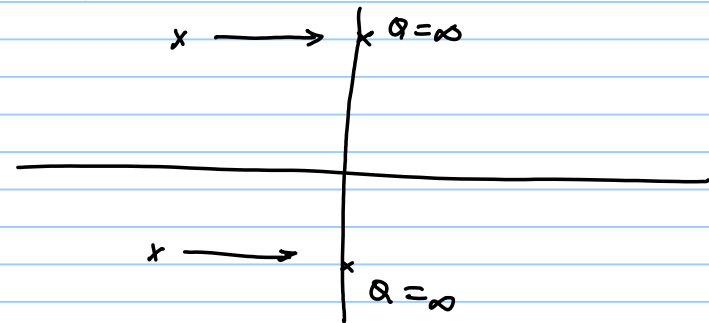eq. $\bar{\omega} \quad s^2 + 2\zeta\omega_n s + \omega_n^2$



Transient response to input step

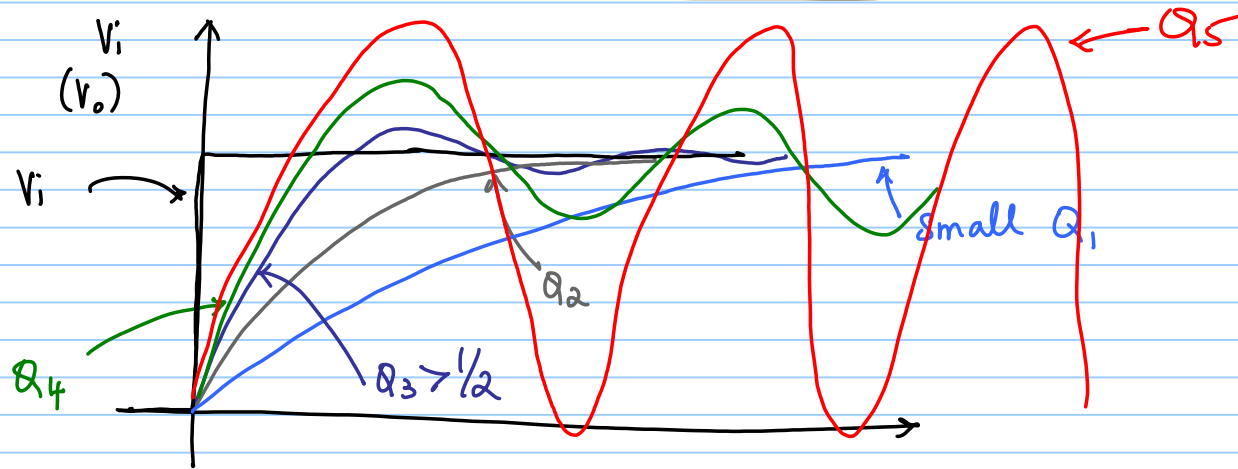

$$Q_1 < Q_2 < Q_3 < Q_4 < Q_5$$

$$Q_1 < 1/2, \quad Q_2 = 1/2$$

$$Q_5 = \infty$$

$$1 + \frac{s}{\omega_0 \cdot Q} + \frac{s^2}{\omega_0^2} \longleftrightarrow 1 + \frac{2s}{A_{of} \omega_p} + \frac{s^2}{\omega_p^2 A_{of}}$$

$$\omega_0 = \omega_p \sqrt{A_{of}} \quad ; \quad Q = \frac{\sqrt{A_{of}}}{2}$$

large gain \Rightarrow A_{of} is large \Rightarrow Q is large \Rightarrow ringing takes a long time to settle

3) 3-pole system

$$A(s) = \frac{A_0}{(1 + s/\omega_p)^3}$$

$$= \frac{A_0}{1 + \frac{3s}{\omega_p} + \frac{3s^2}{\omega_p^2} + \frac{s^3}{\omega_p^3}}$$

$$CLT(s) = \frac{1}{f} \cdot \frac{A_0 f}{1 + A_0 f} \cdot \frac{1}{1 + \left[\frac{3s}{\omega_p} + \frac{3s^2}{\omega_p^2} + \frac{s^3}{\omega_p^3} \right] \frac{1}{1 + A_0 f}}$$

$D(s)$

8/11/17

Lec 20

$$D(s) = 1 + \frac{3s}{\omega_p(1+A_0f)} + \frac{3s^2}{\omega_p^2(1+A_0f)} + \frac{s^3}{\omega_p^3(1+A_0f)}$$

$$x = \frac{s}{\omega_p}$$

$$D\left(\frac{s}{\omega_p}\right) = 1 + \frac{3x}{1+A_0f} + \frac{3x^2}{1+A_0f} + \frac{x^3}{1+A_0f}$$

Roots of $D(x)$: $(1+A_0f) + 3x + 3x^2 + x^3 = 0$

$$(1+x)^3 = -A_0f$$

$$x = -1 + (-A_{of})^{1/3} \rightarrow 3 \text{ solutions}$$


Example 1) $A_{of} = 8$

$$\left. \begin{aligned} x_1 &= -1 - 2 \\ x_2 &= -1 - 2e^{j2\pi/3} \\ x_3 &= -1 - 2e^{-j2\pi/3} \end{aligned} \right\} x = -3, \pm j\sqrt{3}$$

poles are @ $\omega_p \cdot \{x_1, x_2, x_3\}$

2) $A_{of} = 0$: $x_1 = x_2 = x_3 = -1$

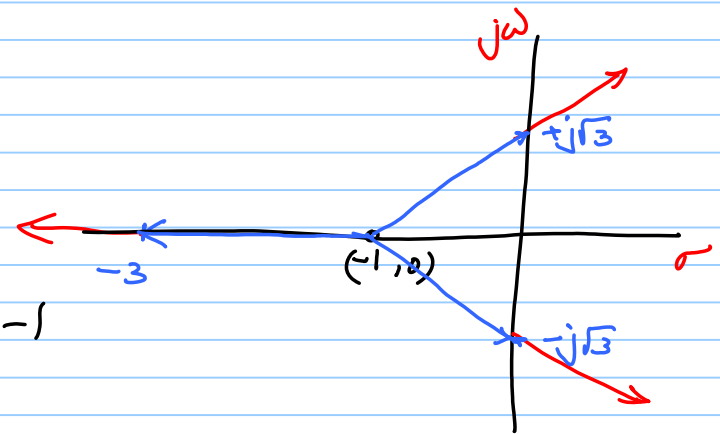3) If $A_{of} > 8$: complex conjugate poles
in RHP \Rightarrow sinusoidal component with
increasing envelope (BAD!)



4) 4-pole system will be worse

Possible solutions

1) $A(s) = \frac{A_0}{(1 + s/\omega_p)^3} \rightarrow \text{Add zeroes}$

\downarrow

$$\frac{A_0}{(1 + s/\omega_p)^2}$$

$$\frac{(1 + s/\omega_p)^2}{(1 + s/\omega_{p2})^2}$$

← Still a 3rd order system

2) 1st order system $\begin{cases} \rightarrow \text{low gain} \\ \rightarrow \text{unconditionally stable} \end{cases}$

2nd order system $\begin{cases} \rightarrow \text{moderate gain} \\ \rightarrow \text{technically stable (but possible ringing)} \end{cases}$

3rd order system $\begin{cases} \rightarrow \text{large gain} \\ \rightarrow \text{unstable if gain} \geq 8 \end{cases}$

"Make higher order system look like 1st order system"

$$\frac{A_0}{(1 + s/\omega_p)^3} \longrightarrow \frac{A_0}{(1 + s/\omega_p)^3 \left(1 + \frac{s}{\omega_d}\right)}$$



Stability matters (a)

$$L_A(s) = -1$$

$$\omega_d \ll \omega_p \quad -20\text{dB/dec.}$$

$\omega_d =$ "dominant" pole

"Dominant pole compensation"

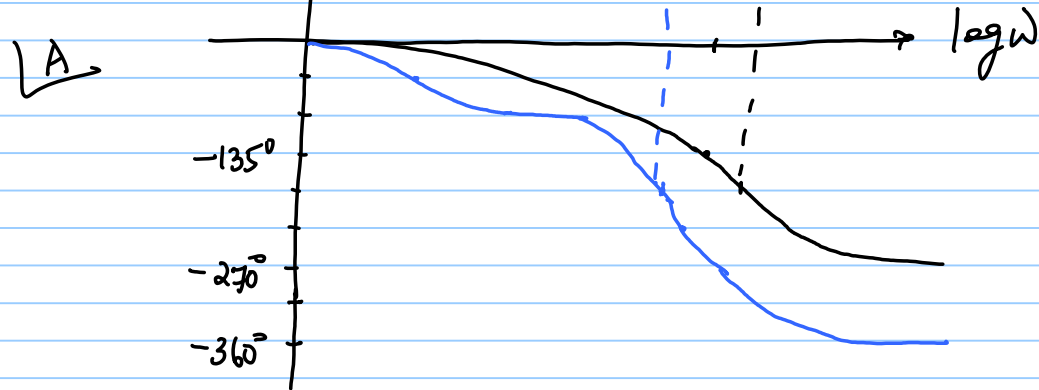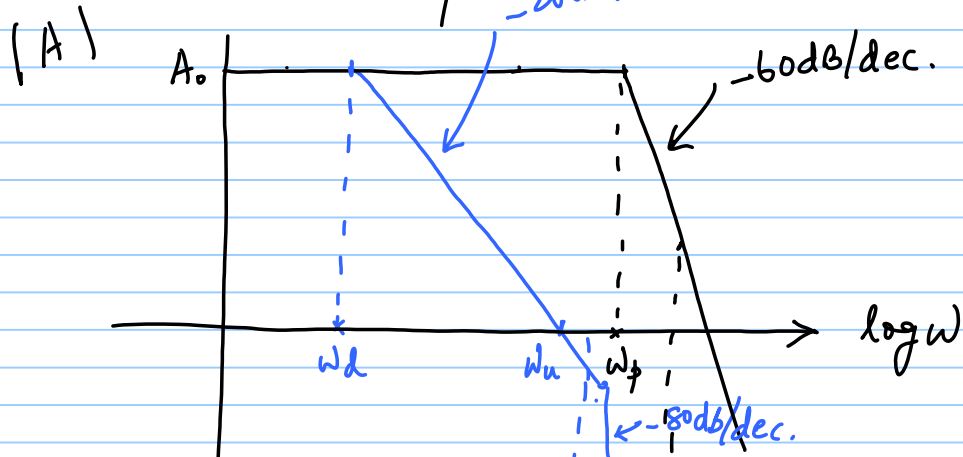

Example :

$$LG(s) = \frac{A_0 f}{(1 + s/\omega_p)^3} \rightarrow \max(A_0 f) = 8$$

add a dominant pole $\omega_d = \frac{\omega_p}{1000}$

$$\text{new } LG(s) = \frac{A_0 f}{\left(1 + \frac{s}{\omega_p}\right)^3 \left(1 + \frac{1000s}{\omega_p}\right)}$$

roots of $LG(s) = -1$

$$\frac{A_0 f}{\left(1 + s/\omega_p\right)^3 \left(1 + \frac{1000s}{\omega_p}\right)} = -1$$

$$\angle L_a = -180^\circ$$

$$0 - 3 \tan^{-1} \left(\frac{\omega_u}{\omega_p} \right) - \tan^{-1} \left(\frac{1000 \omega_u}{\omega_p} \right) = -180^\circ$$

$$\textcircled{a} \quad \omega_d : -45^\circ \text{ from } \omega_d + 0 = -45^\circ$$

$$\textcircled{a} \quad \omega_p : -90^\circ \text{ from } \omega_d + (-135^\circ) = -225^\circ$$

$\omega_d < \omega_u < \omega_p$; $\omega_u \gg \omega_d$ because $A_{of} \gg 1$

$$-3 \tan^{-1} \left(\frac{\omega_u}{\omega_p} \right) = -180^\circ + 90^\circ = -90^\circ$$

$$\tan^{-1} \left(\frac{\omega_u}{\omega_p} \right) = 30^\circ \Rightarrow \text{contribution from each } \omega_p \\ \text{pde} = -30^\circ$$

$$\frac{\omega_u}{\omega_p} = \frac{1}{\sqrt{3}}$$

Now, apply $|L_u(s)| = 1$

$$\left| \frac{A_0 f}{(1 + j/\sqrt{3})^3 (1 + j \cdot \frac{1000}{\sqrt{3}})} \right| = 1$$

$$\frac{A_0 f}{\left(\sqrt{1 + \frac{1}{3}} \right)^3 \left(\frac{1000}{\sqrt{3}} \right)} = 1 \Rightarrow A_0 f = \frac{8000}{9} \approx 890$$

maximum
value
permissible



$$\frac{A_0}{(1 + s/\omega_p)^3} \times \frac{(1 + s/\omega_p)^2}{(1 + s/\omega_{p2})^2} = \frac{A_0}{(1 + s/\omega_p)(1 + s/\omega_{p2})^2}$$

\bar{f} $\omega_{p2} \gg \omega_p \Rightarrow \omega_p$ becomes ^{new} dominant pole

"pole-zero compensation"

$$LG = A_0 \cdot f$$

opamp

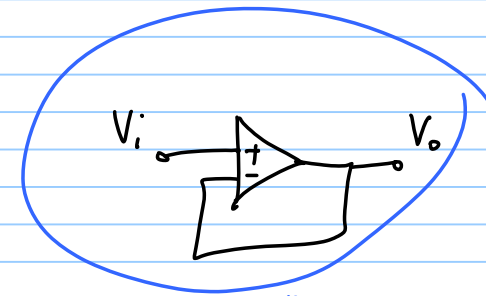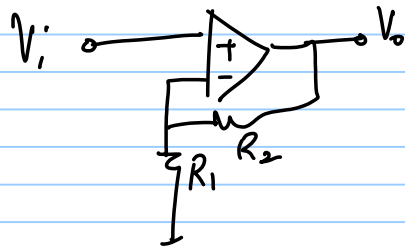

worst-case: $LG = \text{maximum} \Rightarrow f = 1$ (unity gain)

most general purpose opamps are unity-gain compensated.

Measures of Stability

1) Phase Margin: $180^\circ + \angle L_G(j\omega)$ at unity gain frequency
 $L_G = 0 \text{ dB}$
(mag. of 1)

e.g. $\angle L_G(j\omega) @ \omega_u = -135^\circ$

$\Rightarrow \text{PM} = 45^\circ$

{ $\angle L_G(j\omega) @ \omega_u = (-180^\circ)$ is calculated }

2) Gain margin: $0 \text{ dB} - |L_G(j\omega)|$ @ freq. where $\angle L_G(j\omega) = -180^\circ$

e.g. @ $\angle L_G = -180^\circ$, $|L_G| = -20 \text{ dB}$

$\Rightarrow \text{GM} = 20 \text{ dB}$


Effect of Zero

magnitude response : slope increases by $\frac{20\text{dB}}{\text{dec}} \times (\# \text{ of zeroes})$

phase response : depends on LHP or RHP zero

14/11/17

Lec 21

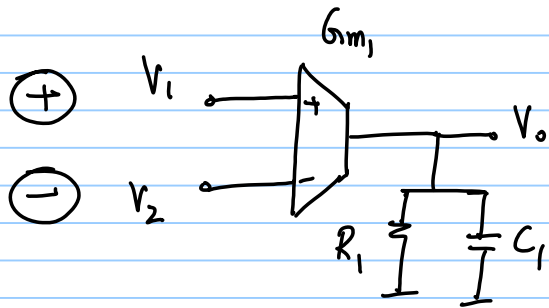

$$A(s) = \frac{A_0}{1 + sR_1C_1}$$

Single stage CMOS opamp = OTA


$R_1 = R_{out}$ of opamp (large)

$$A_0 = G_{m1} R_1$$

$C_1 =$ load cap + sum of all parasitic caps @ output node

$$\omega_{-3dB} = \frac{1}{R_1 C_1}$$

$$\omega_u = \frac{G_{m1}}{C_1}$$

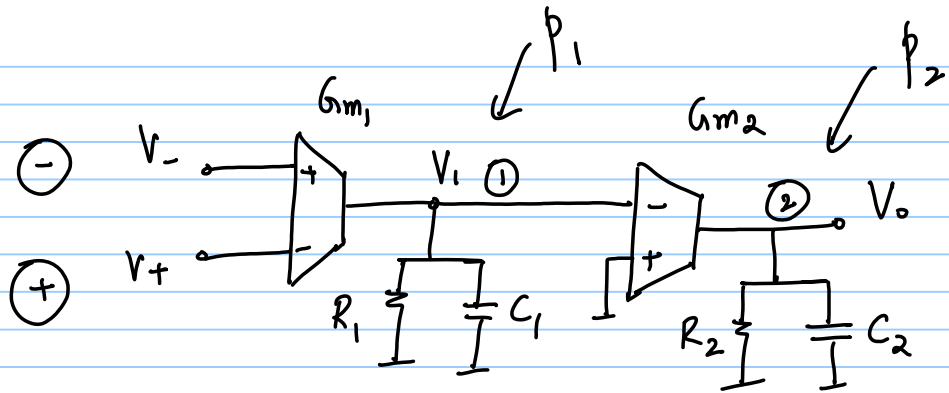


G_{m2} : large gain $= G_{m2} R_2$
 Single ended input & output

\Rightarrow Common source amplifier


$$A_o = A_1 \cdot A_2 = (G_{m1} R_1) (G_{m2} R_2)$$

$$A(s) = \frac{A_1}{1 + \frac{s}{p_1}} \cdot \frac{A_2}{1 + \frac{s}{p_2}}$$
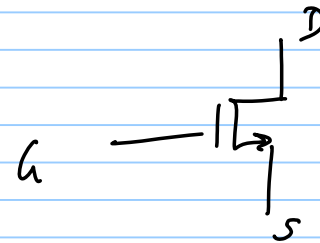
$$p_1 = \frac{1}{R_1 C_1} ; \quad p_2 = \frac{1}{R_2 C_2}$$






C_{gs}
 C_{db}, C_{sb}
 C_{gd}

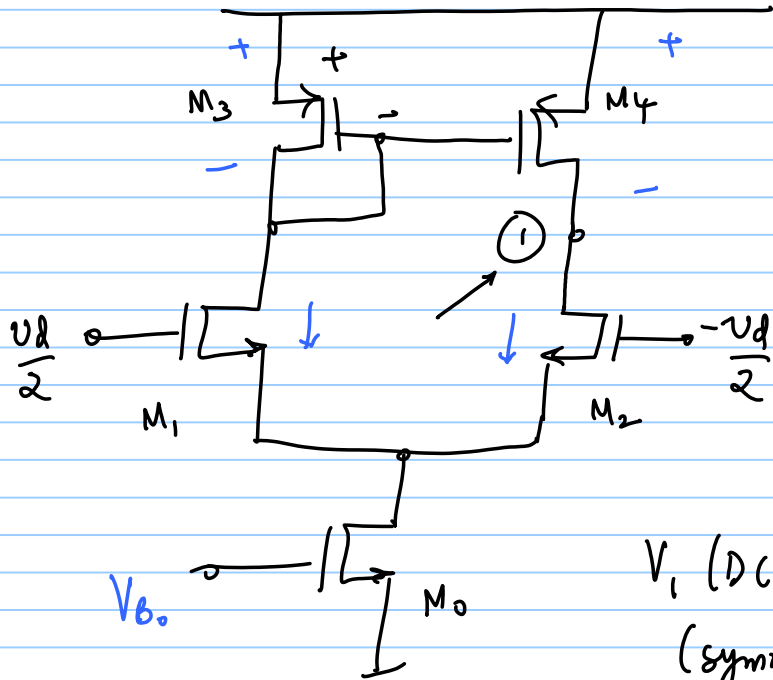


$V_i (DC) = V_{DD} - V_{SG3}$
 (symmetry)

$R_i = r_{ds4} || r_{ds2} ; C_i =$

$G_{m1} = g_{m1}$

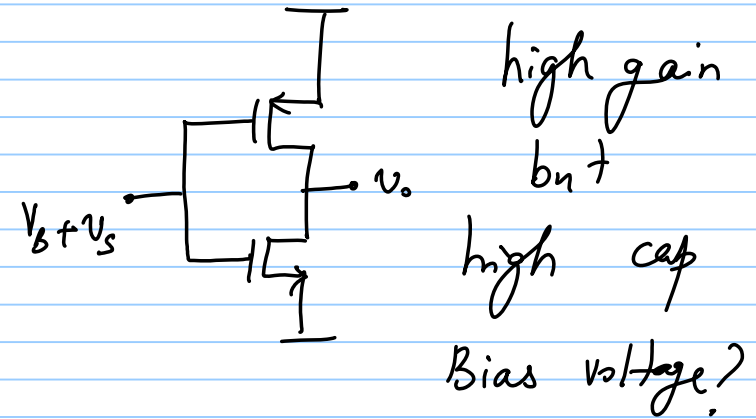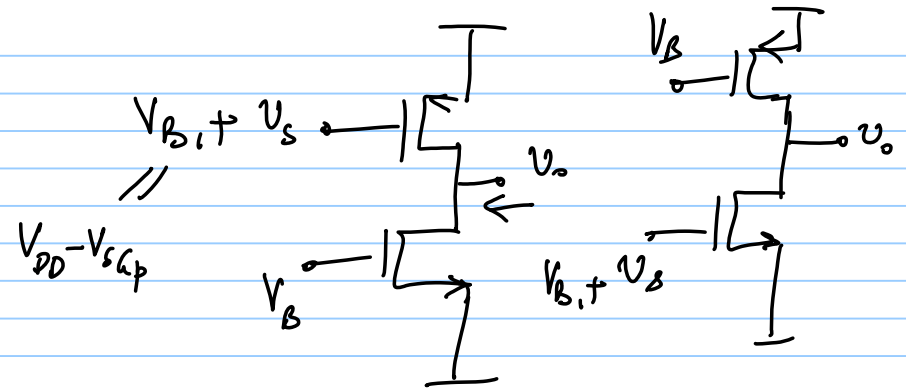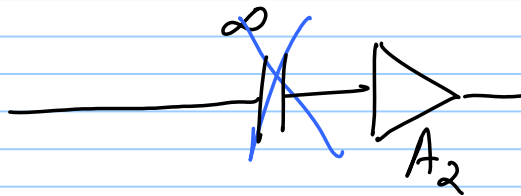

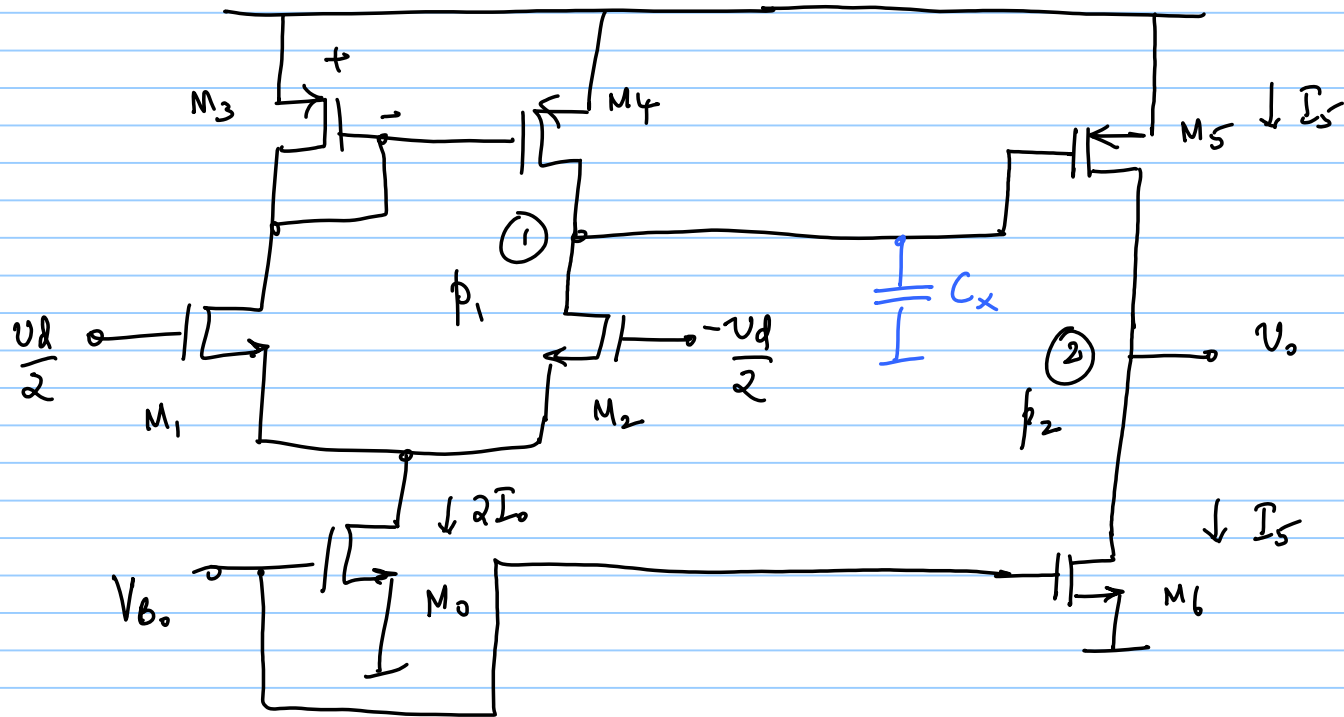

$$V_{DD} - V_{SG3} \Big|_{I_0} = V_{DD} - V_{SG5} \Big|_{I_S}$$

$$V_{SG3} \Big|_{I_0} = V_{SG5} \Big|_{I_S}$$

$$V_{T3} + \sqrt{\frac{2I_0}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}} = V_{T5} + \sqrt{\frac{2I_S}{\mu_p C_{ox} \left(\frac{W}{L}\right)_5}}$$

$$\Rightarrow \boxed{\frac{I_0}{(W/L)_3} = \frac{I_S}{(W/L)_5}}$$


M_3, M_5 should have same "Current Density"

$$V_{GS_0} = V_{GS_6} \Rightarrow \boxed{\frac{2I_0}{(W/L)_0} = \frac{I_S}{(W/L)_6}}$$

$$L_3 = L_4 = L_5 ; L_0 = L_6$$

$$A_0 = g_{m1}(r_{ds2} \parallel r_{ds4}) \cdot g_{m5}(r_{ds5} \parallel r_{ds6}) \rightarrow \text{very large}$$

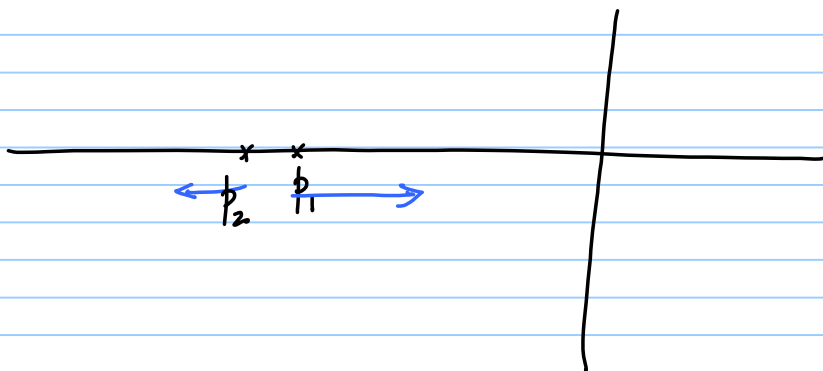
$$2 \text{ pole system: } Q = \frac{\sqrt{A_0 f}}{2} = \text{large} \Rightarrow \text{Ringing}$$



$$p_1 = \frac{1}{R_1 C_1}$$

f_f $R_1 \uparrow \Rightarrow$ already as large as possible for A_0

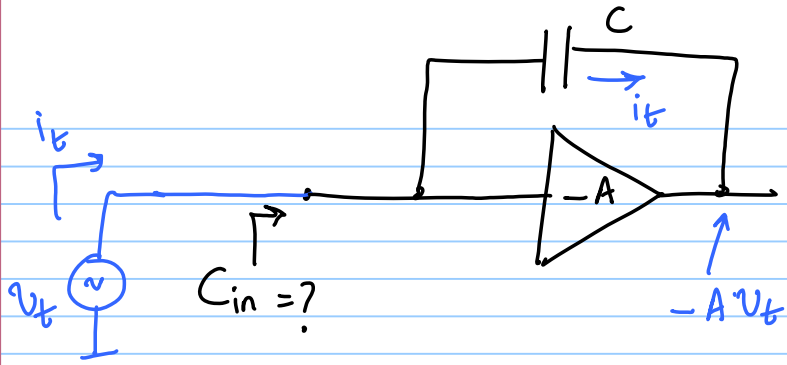$C_1 \uparrow \Rightarrow$ add C_x , but C_x is very large



$$\frac{v_t}{i_t} = \frac{1}{sC_{in}} \quad \text{or} \quad i_t = sC_{in} \cdot v_t$$


$$i_t = \left\{ v_t - (-A v_t) \right\} \cdot sC$$

$$\frac{i_t}{v_t} = sC_{in} = sC [1+A] \Rightarrow \boxed{C_{in} = (1+A)C}$$


"Miller" Effect

"Miller" Compensation


"pole-splitting"

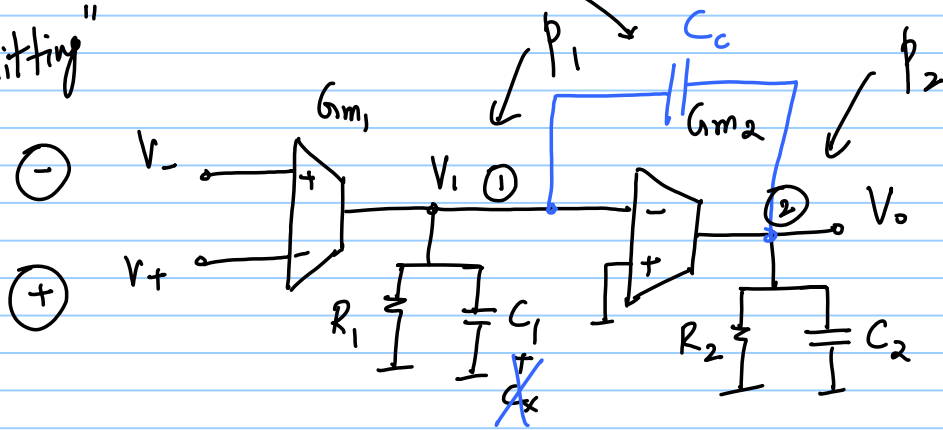

"MOSCAP"

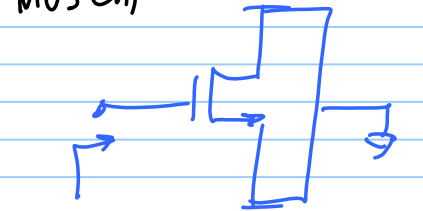

C_g high density non-linear

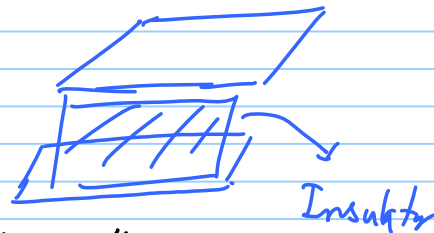

"MIM" Cap high-k dielectric



"MOM" Cap


$$\text{effective } C_x = (1+A) \cdot C_c$$

$\underbrace{\hspace{10em}}_{Gm_2 R_2 \gg 1}$

$$C_x \approx Gm_2 R_2 C_c \Rightarrow C_{1, \text{orig}}$$




Two paths from (1) to (2) \Rightarrow through C_c & Gm_2

Expect a zero!!

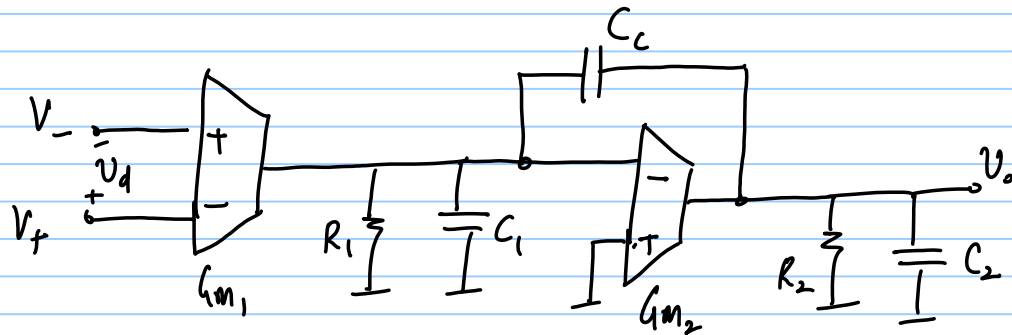

$$\frac{v_o}{v_d}(s) = ?$$

HW exercise

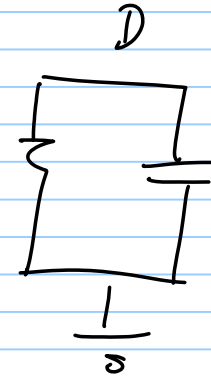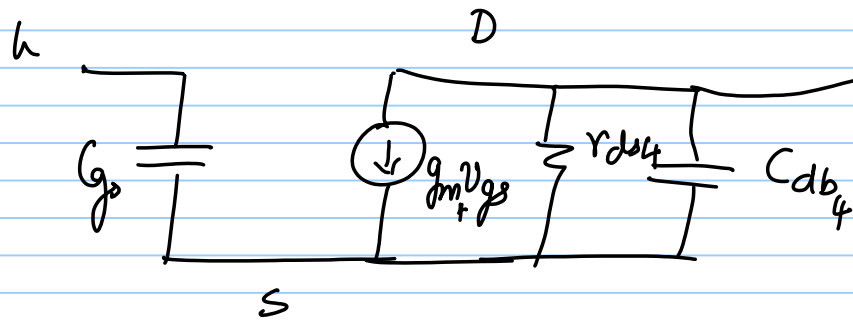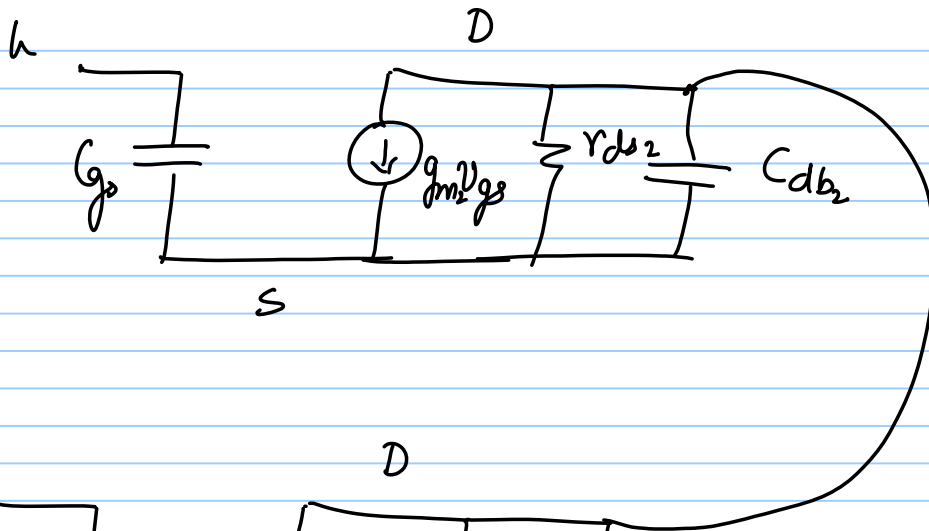


OTA - VCCS
because R_{out} is large

- 1 class : BJTs
- 2 classes : Other opamps

3 classes : B.G ref + LDO

15/11/17

Lec 22

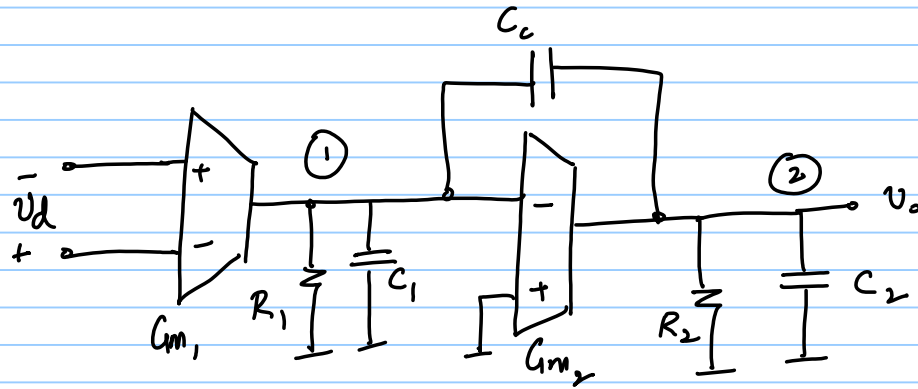

$$A_0 = G_{m1} R_1 \cdot G_{m2} R_2$$

$$= \frac{G_{m1}}{G_1} \cdot \frac{G_{m2}}{G_2}$$

$$Z = + \frac{G_{m2}}{C_c} \quad (\text{RHP zero})$$

$$\text{pole} = - \frac{\text{conductance}}{\text{capacitance}}$$

$$\frac{v_o}{v_d}(s) = A_0 \frac{(1 - s/z)}{as^2 + bs + c}$$

p_1 & p_2 : roots of $ax^2 + bx + c = 0$



We know $p_1 \ll p_2$

$$p_1 \approx -\frac{c}{b} \quad ; \quad p_2 \approx -\frac{b}{a}$$


$$p_1 = - \frac{G_1}{C_1 + (1 + G_{m2} R_2) C_c} + \dots$$

$$\approx - \frac{G_1 G_2}{G_{m2} C_c} \quad (\text{LHP})$$

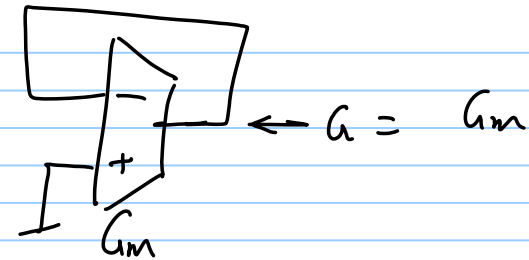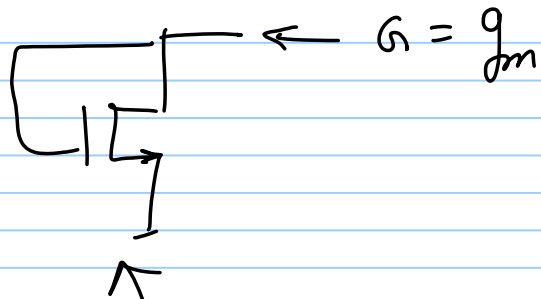
$$p_2 \approx - \frac{G}{C} = - \frac{G_2 + \frac{C_c}{C_1 + C_c} \cdot G_{m2}}{C_2 + \frac{C_c C_1}{C_c + C_1}} \quad (\text{LHP})$$


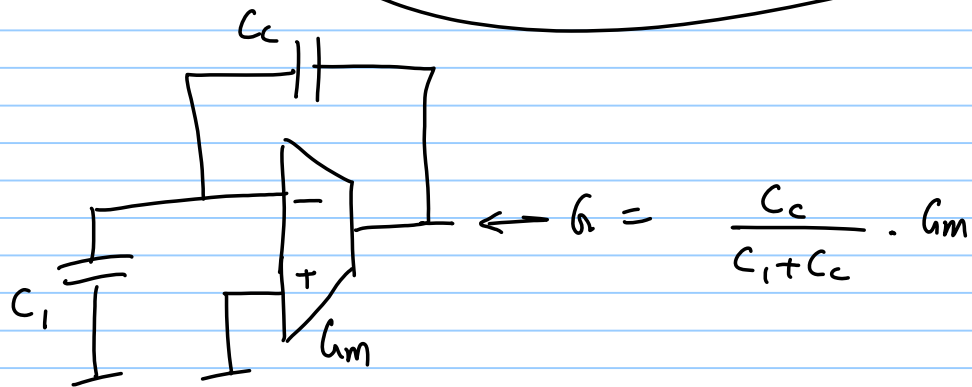
$$A(s) = A_0 \frac{(1 - s/z)}{(1 + \frac{s}{p_1})(1 + \frac{s}{p_2})}$$



$$\underline{|A(\omega)|} = -\tan^{-1}\left(\frac{\omega}{z}\right) - \tan^{-1}\left(\frac{\omega}{p_1}\right) - \tan^{-1}\left(\frac{\omega}{p_2}\right)$$

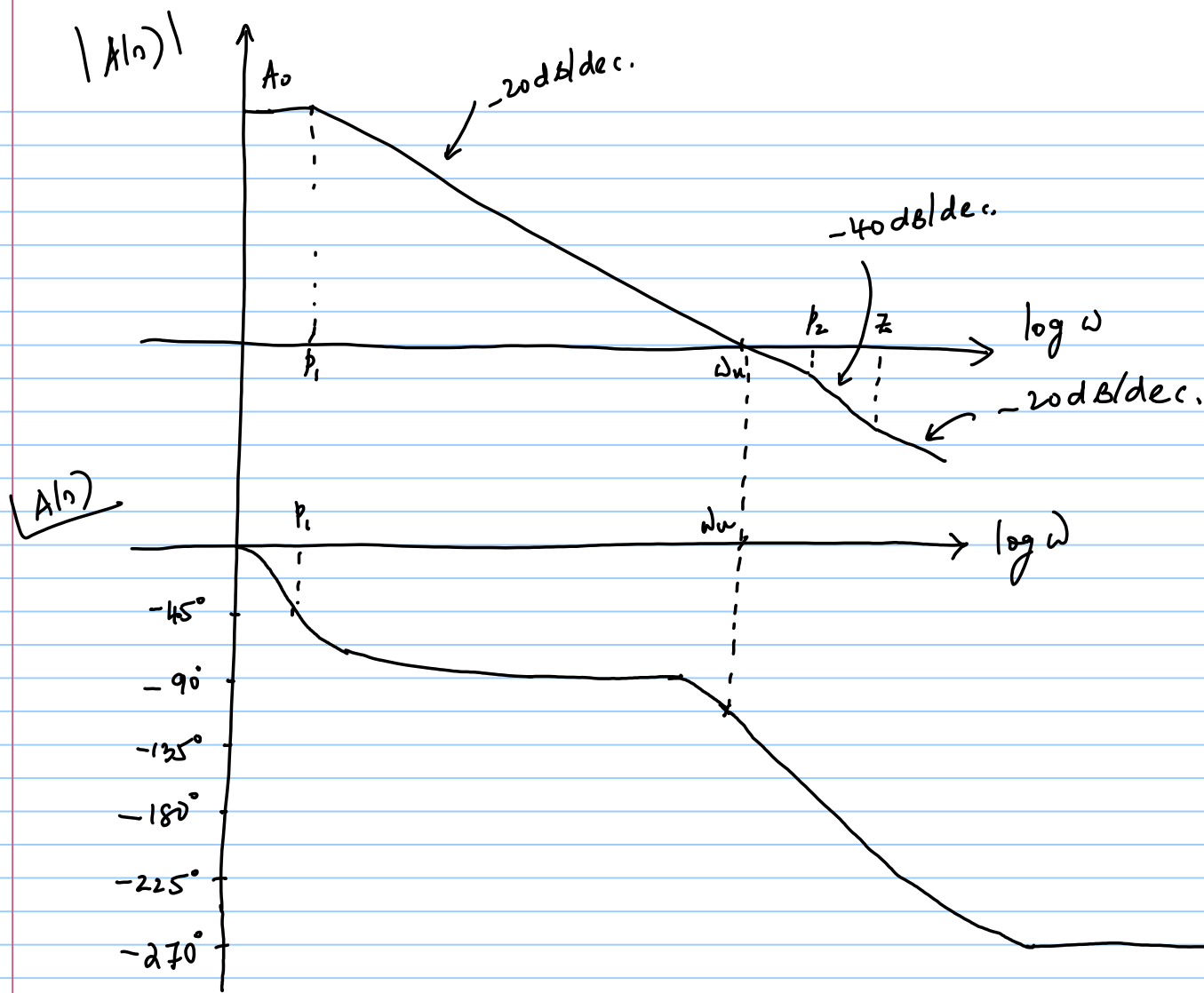


$$\left. \begin{aligned} \omega_u &= \frac{G_{m1}}{C_E} \\ z &= \frac{G_{m2}}{C_C} \end{aligned} \right\}$$

$$\begin{aligned} \text{phase @ } \omega_u &= -90^\circ - \tan^{-1}\left(\frac{\omega_u}{p_2}\right) \\ &\quad - \tan^{-1}\left(\frac{\omega_u}{z}\right) \end{aligned}$$

Phase margin = $180^\circ + \text{phase @ } \omega_u$
 choose positions of p_2 & z so
 that phase margin is adequate

e.g. no phase impact from zero: $\frac{\omega_u}{z} \ll 1 \Rightarrow \omega_u \ll z$

$\Rightarrow G_{m2} \gg G_{m1}$

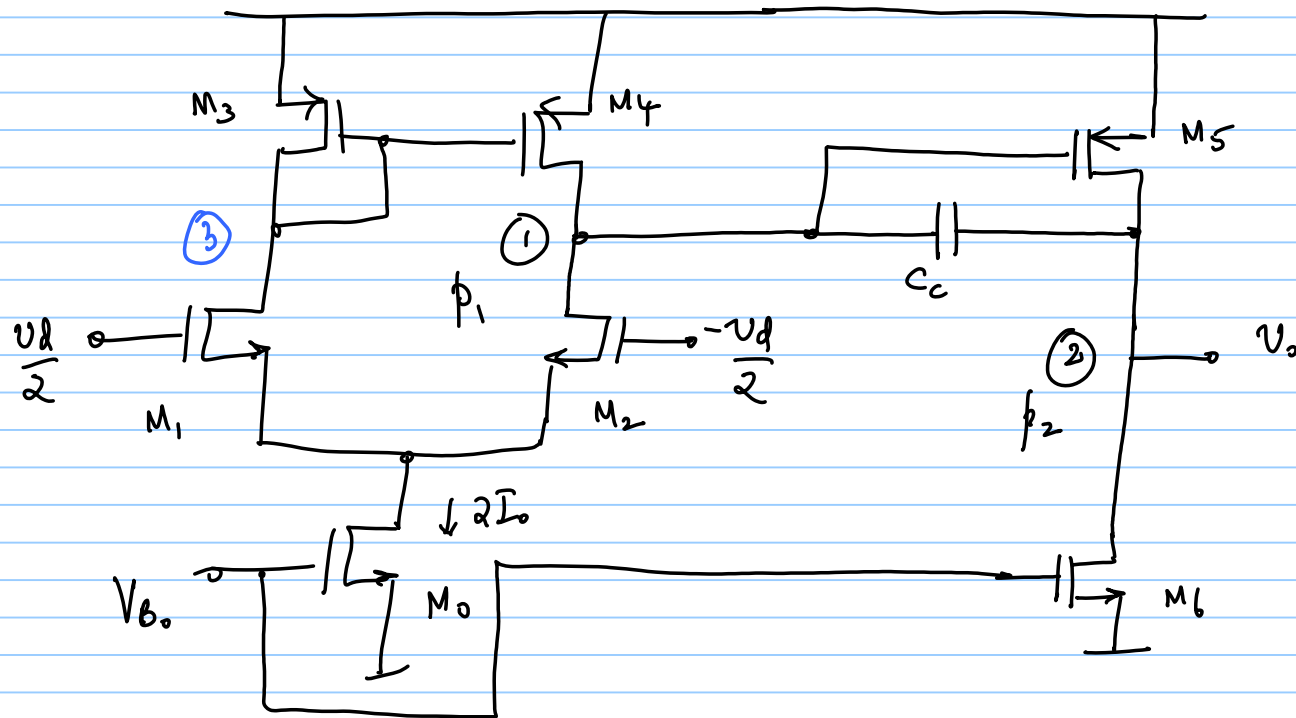

$G_{m1} = g_{m1} ; G_{m2} = g_{m5}$

$C_1 = \text{tot cap @ (1)}$



$C_2 = \dots \dots \dots \text{(2)}$

$R_1 = r_{ds2} \parallel r_{ds4}$

$R_2 = r_{ds5} \parallel r_{ds6}$

$p_3 = \frac{g_{m3}}{C_3} \quad p_3 \& z_2 \gg \omega_u$

$z_2 = \dots$

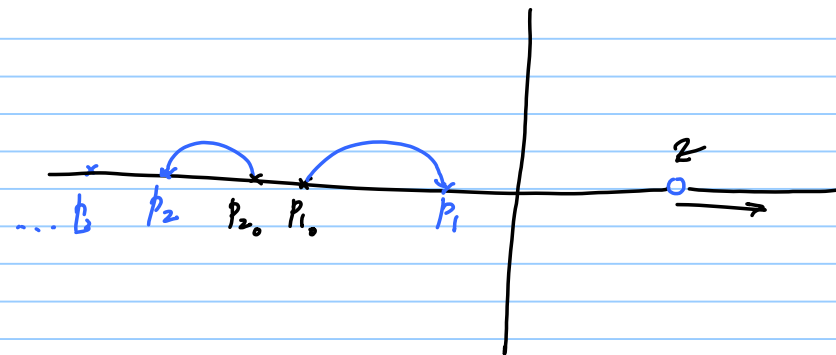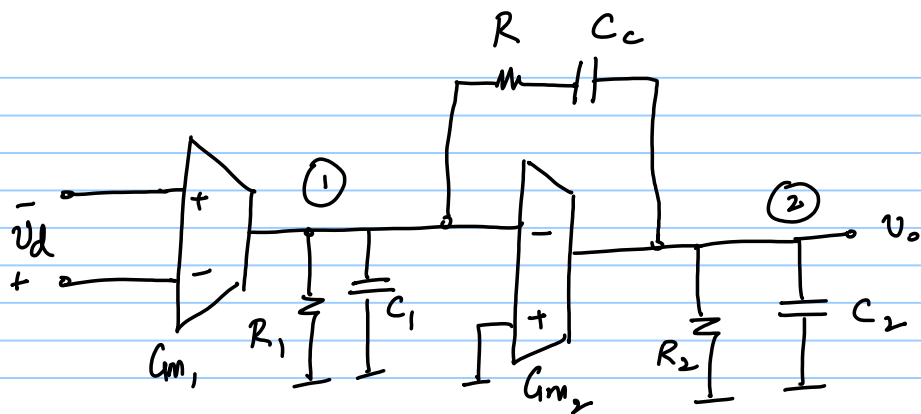

p_1 & p_2 are almost same as before

pole-zero cancellation


$$p_3 > p_2$$

RC miller compensation

$$z = \frac{G_{m2}}{C_c (1 - G_{m2} R)}$$


1) move $z \rightarrow \infty$: set $G_{m2} R = 1 \Rightarrow R = \frac{1}{G_{m2}}$

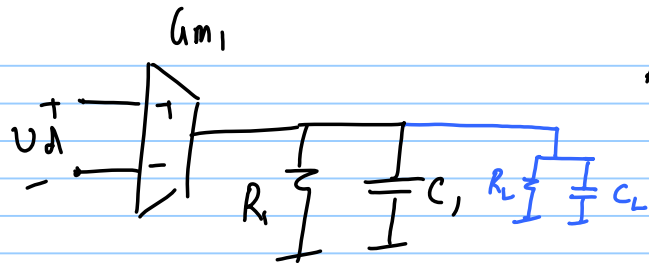2) $G_{m2} R > 1 \Rightarrow$ LHP zero \Rightarrow Use this to cancel $p_2 \Rightarrow p_3$ becomes first non-dominant pole





$$A_o = G_{m1} R_1 \rightarrow G_{m1} R_L$$

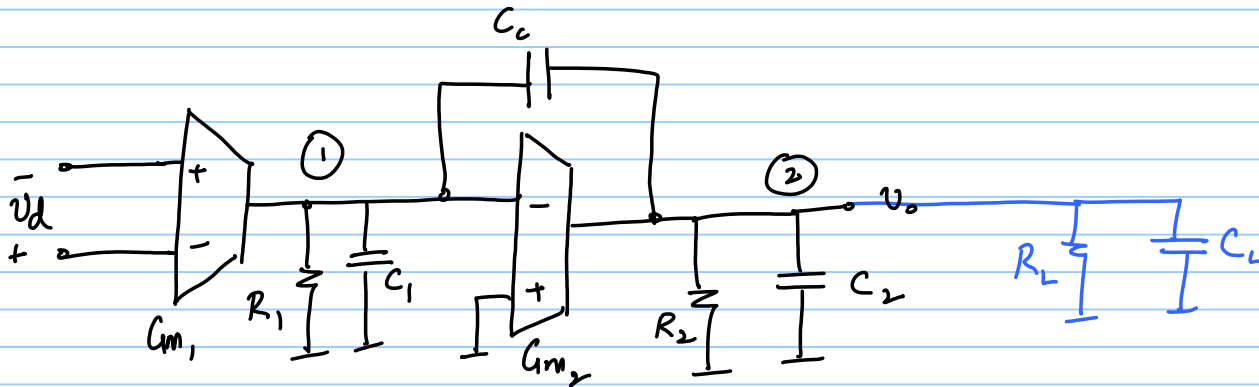* Cannot drive resistive loads
(reduced DC gain A_o)




$$A_o = G_{m1} R_1 G_{m2} R_2$$

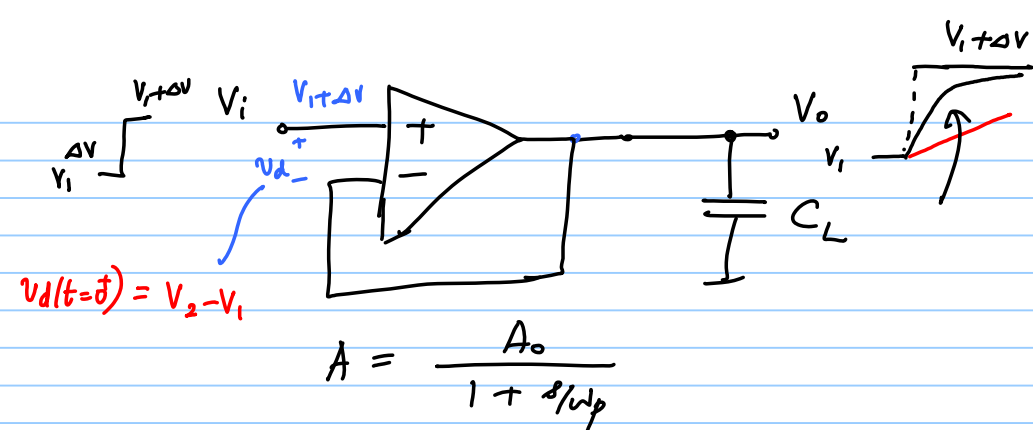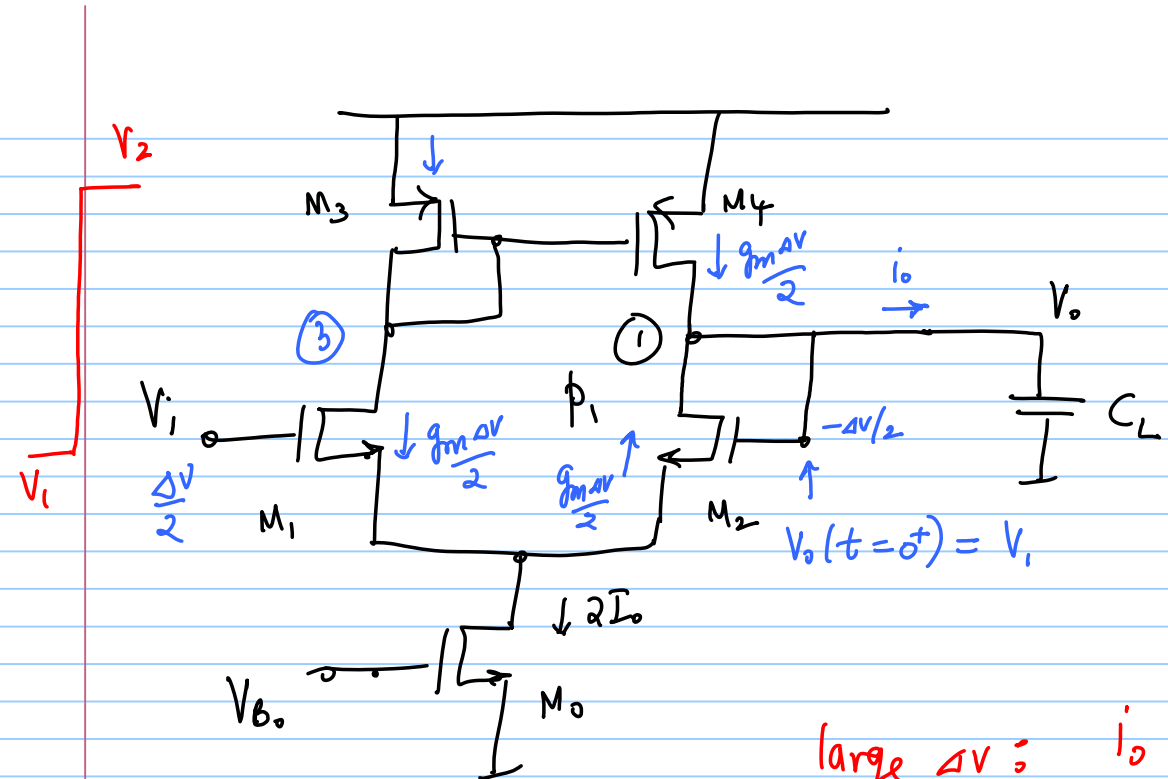↓
 $G_{m1} R_1$ $G_{m2} R_L$
 DC gain from 1st stage



large ΔV : $i_o = 2I_0$


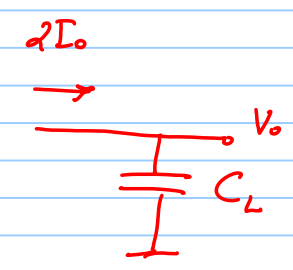


Small ΔV } $i_o = g_m \Delta V$

$\Rightarrow V_o = \frac{2I_0}{C_L} \cdot t + V_i$

output increases linearly

"slew" rate = $\frac{2I_0}{C_L}$ V/s

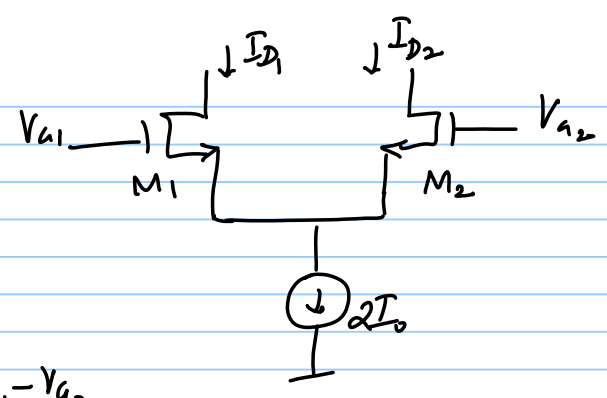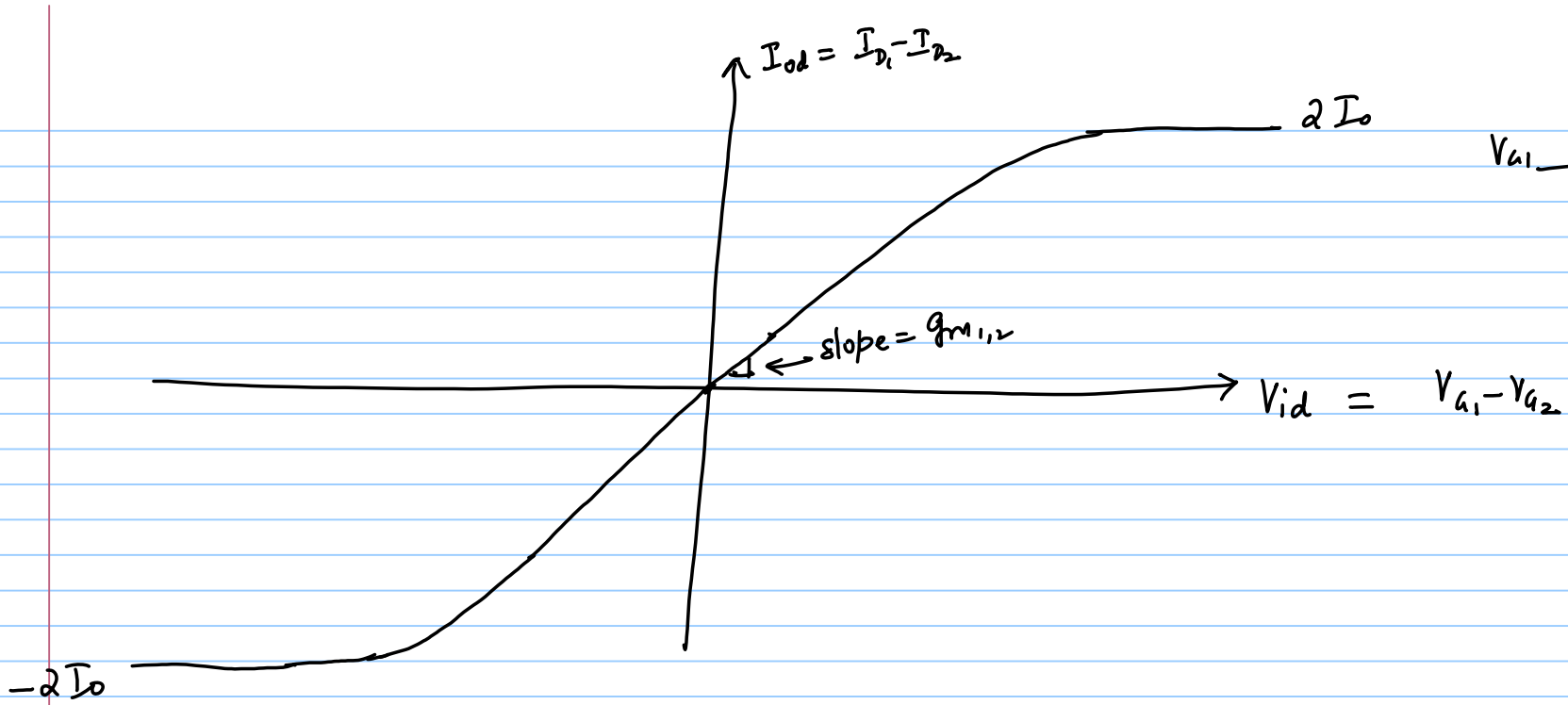


2/11/17

Lec 23

BJT

"Bipolar Junction Transistor"

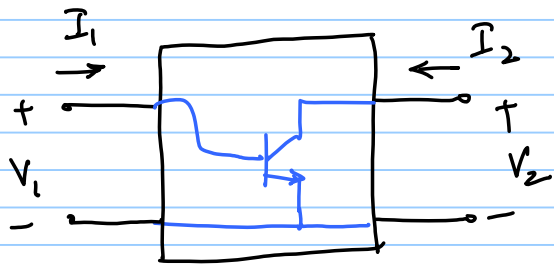

$$I_1 = f(V_1, V_2)$$

$$I_2 = g(V_1, V_2)$$



$$I_1 = \text{constant}$$




$$I_2 = g(V_1)$$

$$y_{11} = \frac{\partial I_1}{\partial V_1} \text{ etc.}$$


$$y_{11} = 0 = y_{12} = y_{22}$$

$$y_{21} = \text{large}$$

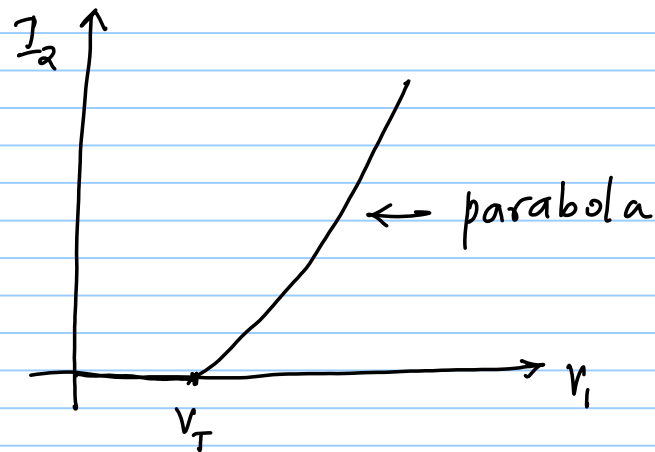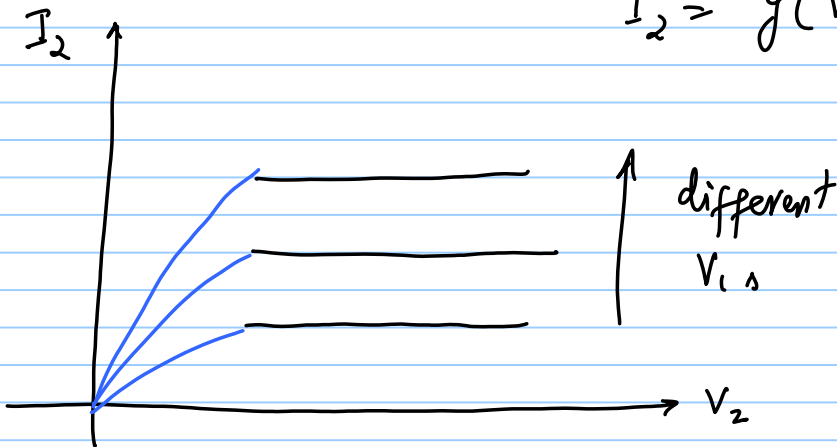

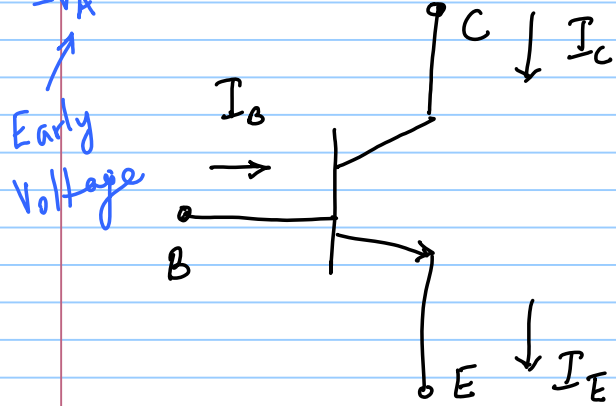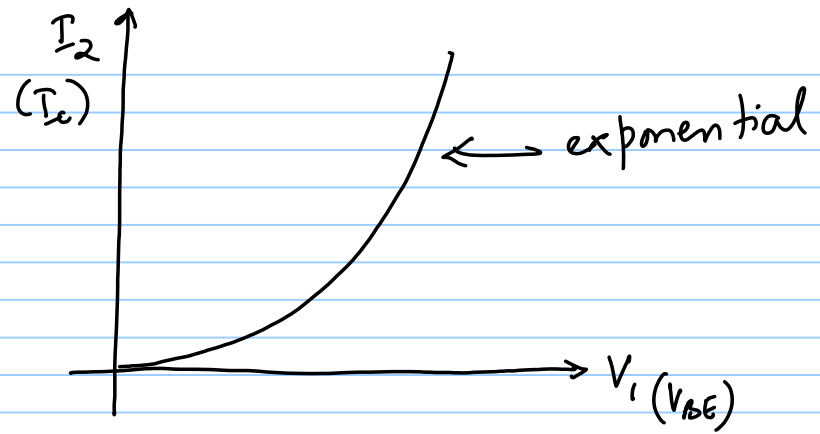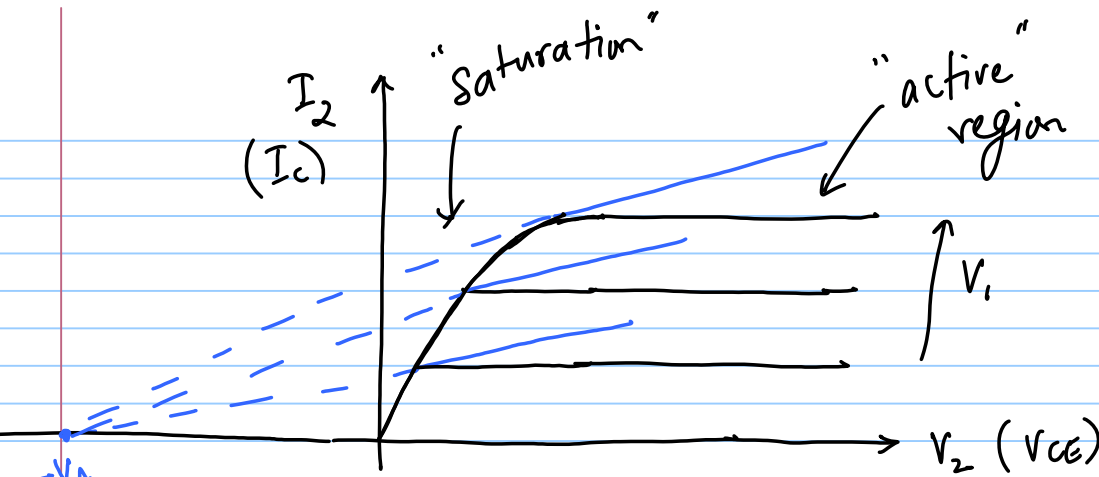

npn BJT

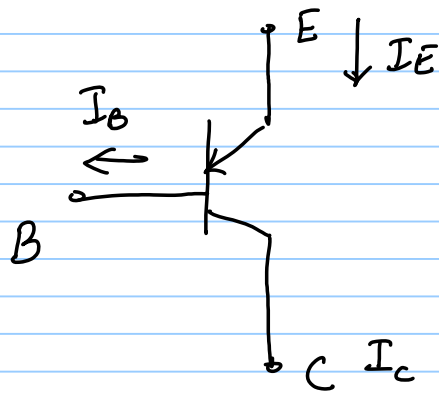

pnp BJT

$$I_B + I_C = I_E$$

$$\beta = \frac{I_C}{I_B} \text{ should be as large as possible}$$

~ say 100-200

$$I_C = \frac{\beta}{\beta + 1} I_E = \alpha I_E \rightarrow \sim 1$$

$$I_c = I_s \left\{ \exp\left(\frac{V_{BE}}{V_t}\right) - 1 \right\} \left\{ 1 + \frac{V_{CE}}{V_A} \right\}$$

$\frac{kT}{q}$ thermal voltage $\approx 25.9 \text{ mV}$ @ 300 K

$$V_{BE_{on}} \approx 0.7 \text{ V}$$




Small-signal parameters


$$y_{11} = \frac{\partial I_B}{\partial V_{BE}} = \frac{1}{\beta} \frac{\partial I_c}{\partial V_{BE}} = \frac{1}{\beta} \cdot I_s \cdot \frac{1}{V_t} \cdot \left\{ \exp\left(\frac{V_{BE}}{V_t}\right) \right\}$$

$$\approx \frac{I_c}{\beta V_t} \quad \text{because} \quad \exp\left(\frac{V_{BE}}{V_t}\right) \gg 1 \quad \text{for} \quad V_{BE} \sim 0.7 \text{ V}$$

$$y_{12} = 0 \quad ; \quad y_{21} = \frac{\partial I_c}{\partial V_{BE}} \approx \frac{I_c}{V_t} \quad ; \quad y_{22} = \frac{\partial I_c}{\partial V_{CE}} \approx \frac{I_c}{V_A}$$
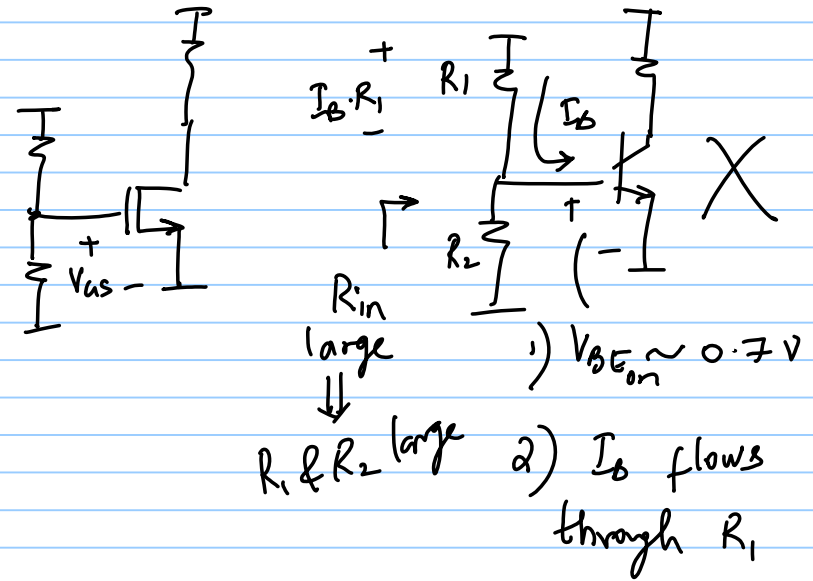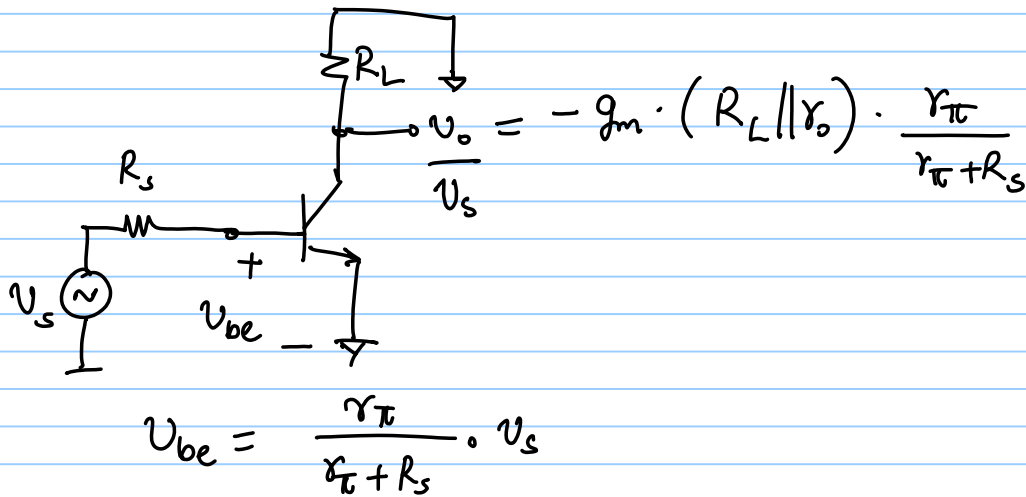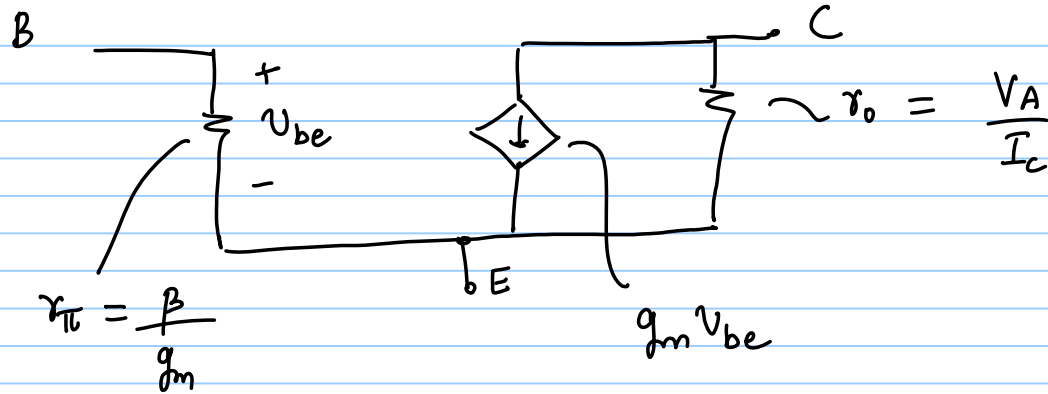
$$g_m \parallel \Rightarrow y_{11} = \frac{g_m}{\beta}$$



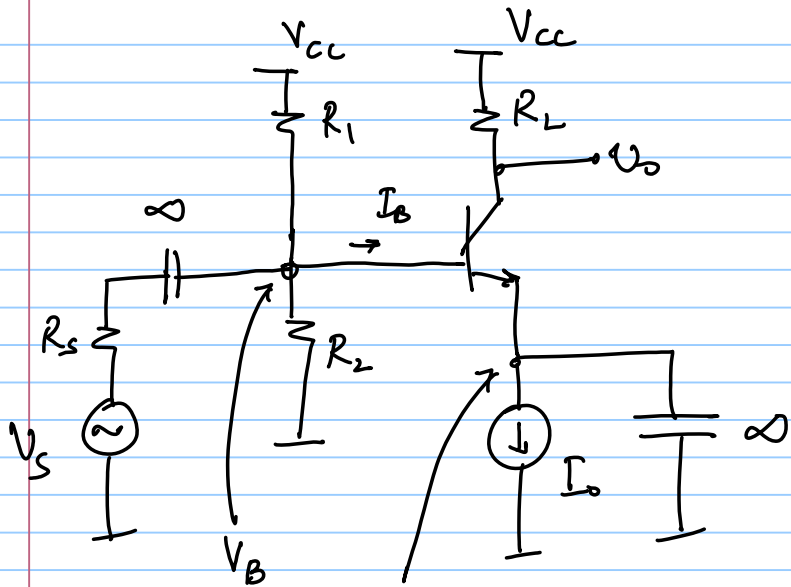

R_1 & R_2 should not be too large because of $I_B \cdot R_1$ drop

$$r_{\pi} = \frac{\beta}{g_m} \quad \text{e.g.} \quad g_m = 1 \text{ mS} ; \beta = 200$$

$$r_{\pi} = 200 \text{ k}\Omega$$

$$V_B - V_{BE(on)} = V_B - 0.7 \text{ V} > V_{\min} \text{ for Current source}$$


$$r_{\pi} = \frac{\beta}{g_m} \quad \text{large because of large } \beta$$

$$g_{m_{BJT}} = \frac{I_C}{V_t}$$

$\underbrace{\hspace{2cm}}_{25.9 \text{ mV}}$


$$g_{m_{MOS}} = \frac{2 I_D}{(V_{GS} - V_T)} = \frac{I_D}{\underbrace{(V_{GS} - V_T)/2}_{100 - 200 \text{ mV}}}$$

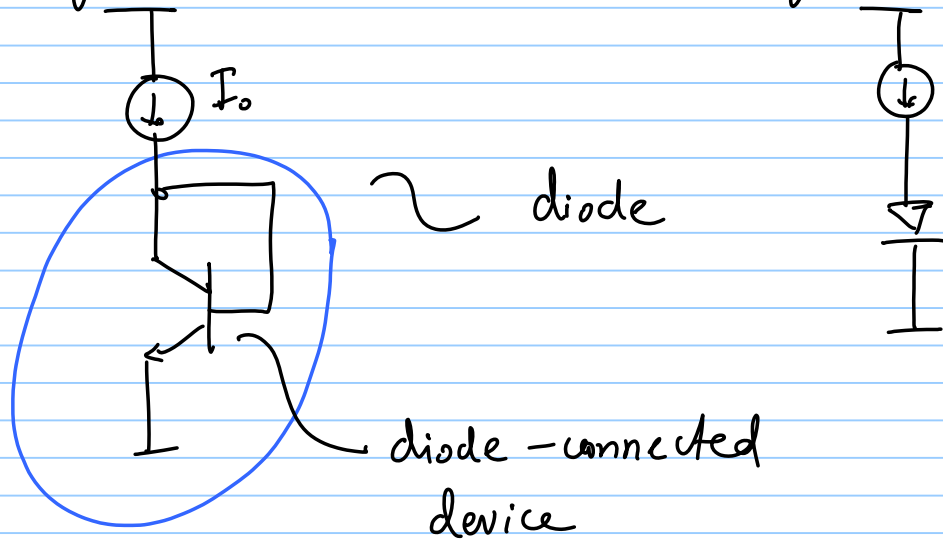for a given bias current, BJT gives more g_m i.e. more gain



Current Mirror

$$Q_1 = Q_2$$

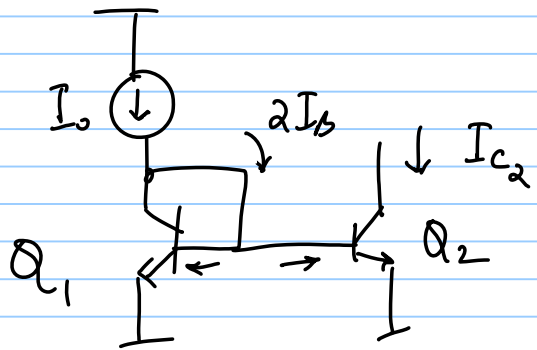


relate I_C to V_{BE}

$$V_{BE_1} = V_{BE_2} \Rightarrow I_{C_1} = I_{C_2} \Rightarrow I_{B_1} = I_{B_2}$$

$$I_{C_1} = I_0 - 2I_B = I_0 - \frac{2I_{C_1}}{\beta}$$
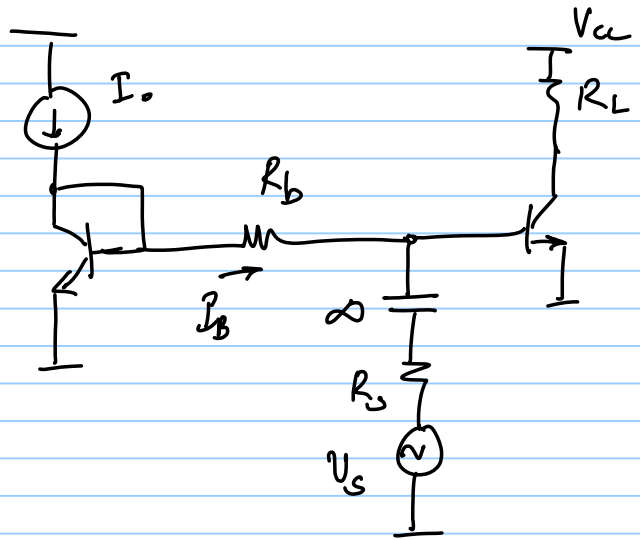
$$I_{C_1} = I_{C_2} = \frac{\beta}{\beta + 2} I_0$$





Swing limits


$I_c = 0$ cut off limit

$V_{CE} \geq V_{CEsat}$; $V_{CEsat} \approx V_{BEon} = 0.7V$
saturation limit

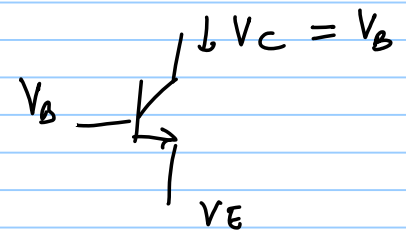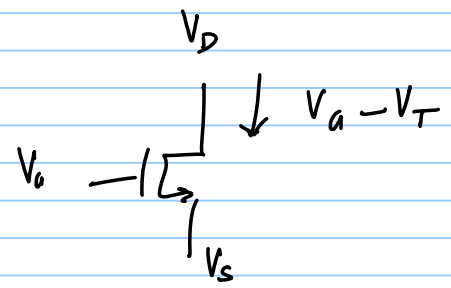MOS: $V_{DS} \geq V_{DSat}$ for saturation region
operation
 $V_{GS} - V_T$



VCVS (CCA)

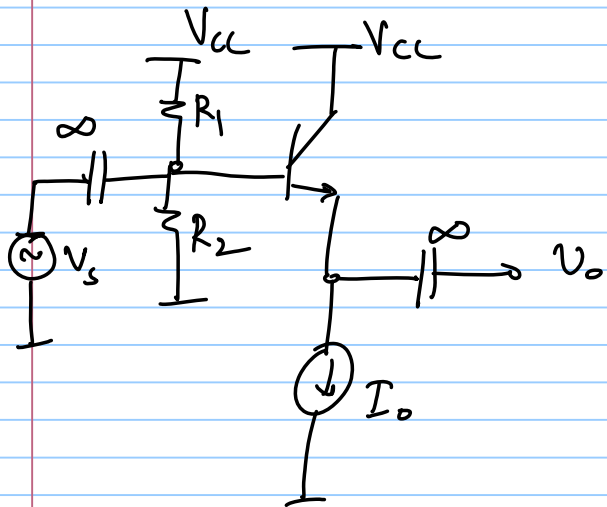


$$\frac{V_o}{V_s} \approx 1$$

$$r_{out} = \frac{1}{g_m}$$

$$r_{in} = \text{high}$$


CCCS (CGA)

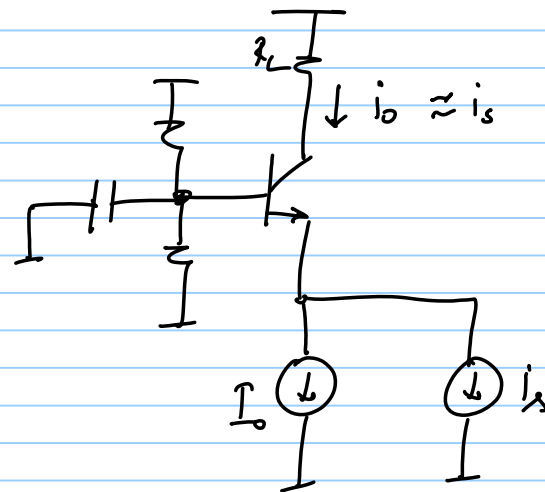


CCVS

HW


VCLS

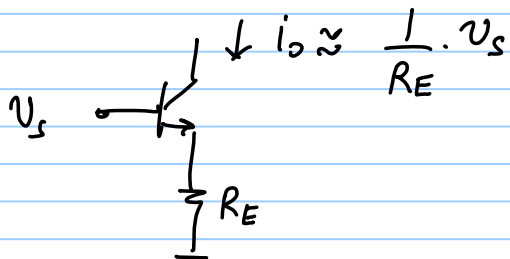

Differential Amplifier

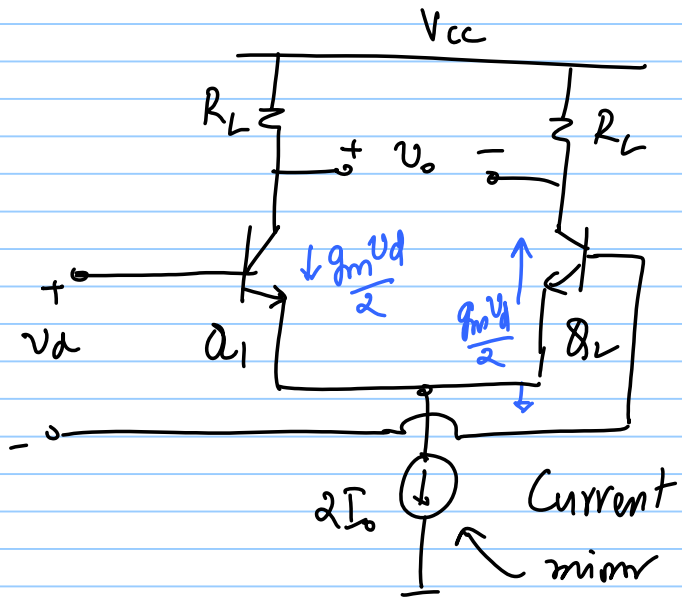

" 741 opamp

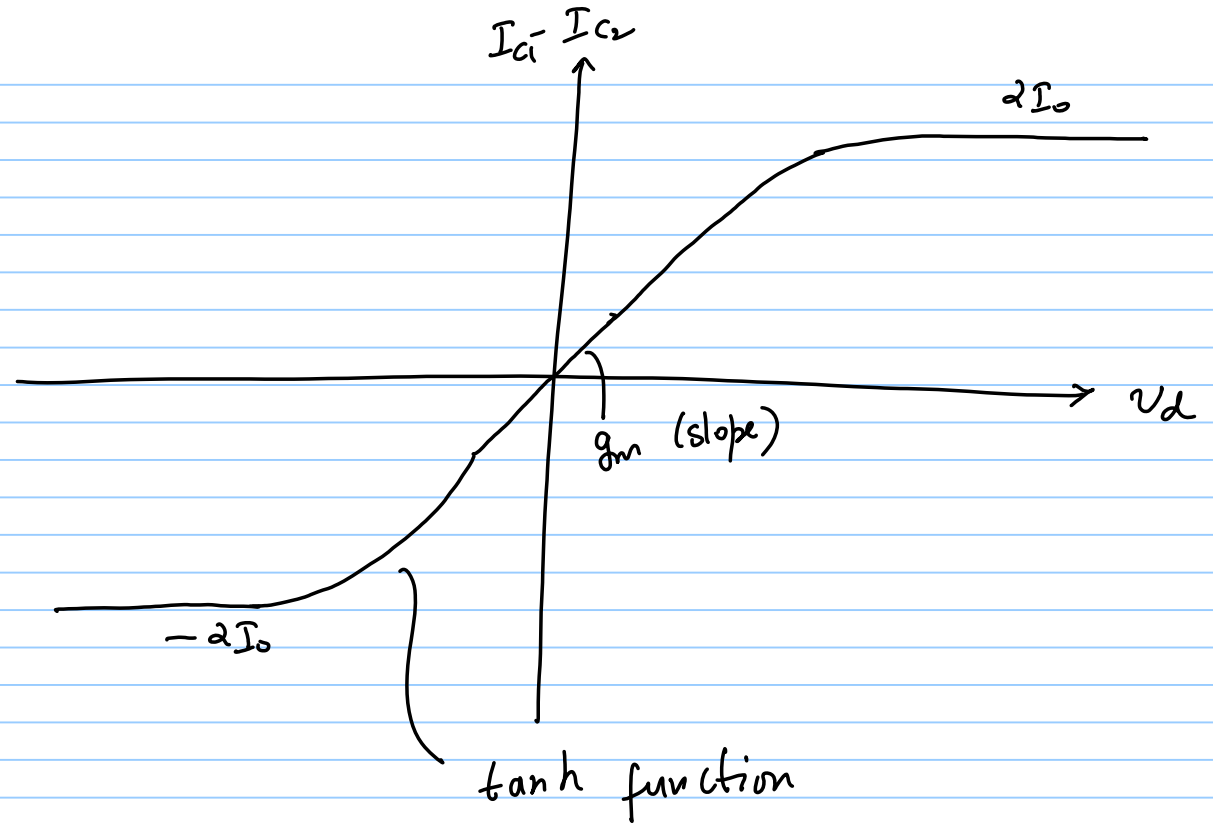

23/11/17

Lec 24

Bandgap Reference

V_{ref} independent of V_{DD} , T , Process etc.
→ Silicon bandgap

$$V_{ref} = \alpha_1 V_1 + \alpha_2 V_2$$

tempco tempco

$$\frac{\partial V_{ref}}{\partial T} = 0 \Rightarrow \alpha_1 \frac{\partial V_1}{\partial T} + \alpha_2 \frac{\partial V_2}{\partial T} = 0 \quad \leftarrow \text{ @ } 300K$$

α_1 & α_2 have to be chosen such that this is true

V_{BE} or V_{Diode}

$$I_D = I_s \left[\exp\left(\frac{V_{BE}}{V_t}\right) - 1 \right]$$

$$I_s = b \cdot T^{4+m} \exp\left(\frac{-E_g}{kT}\right)$$

$E_g =$ BG of Silicon $\approx 1.1\text{eV}$

$$V_{BE} = V_t \ln\left(\frac{I_D}{I_s}\right)$$

$$V_t = \frac{kT}{q}$$

$$\frac{\partial V_{BE}}{\partial T} = \frac{\partial V_t}{\partial T} \cdot \ln\left(\frac{I_D}{I_s}\right) - \frac{V_t}{I_s} \cdot \frac{\partial I_s}{\partial T} \rightarrow V_t \frac{\partial}{\partial T} \left\{ \cancel{\ln I_D} - \ln I_s \right\}$$

$$\frac{\partial I_s}{\partial T} = b(4+m) T^{3+m} \exp\left(\frac{-E_g}{kT}\right) + b T^{(4+m)} \exp\left(\frac{-E_g}{kT}\right) \cdot \left(\frac{E_g}{kT^2}\right)$$

$$= \frac{4+m}{T} \cdot I_s + \frac{E_g}{kT^2} I_s$$

$$\frac{V_t}{I_s} \cdot \frac{\partial I_s}{\partial T} = (4+m) \cdot \frac{V_t}{T} + \frac{E_g}{kT^2} \cdot V_t$$


$$\frac{\partial V_{BE}}{\partial T} = \frac{V_t}{T} \ln\left(\frac{I_D}{I_S}\right) - (4+m) \cdot \frac{V_t}{T} - \frac{E_g}{kT^2} \cdot V_t$$

$$= \frac{V_{BE} - (4+m)V_t - E_g/q}{T}$$

$$\left. \frac{\partial V_{BE}}{\partial T} \right|_{300K} \approx -1.5 \text{ mV/K} \quad \text{negative tempco}$$

$$V_t = \frac{kT}{q} \quad \leftarrow \text{positive tempco}$$
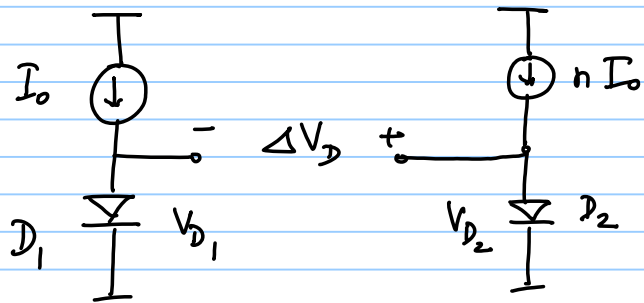
$$B_{ref} = \alpha_1 V_{BE} + \alpha_2 V_t$$



$$D_1 = D_2 \Rightarrow I_{S1} = I_{S2} = I_S$$

$$\Delta V_D = V_{D2} - V_{D1}$$

$$= V_t \ln\left(\frac{nI_0}{I_S}\right) - V_t \ln\left(\frac{I_0}{I_S}\right)$$

$$= V_t \ln(n) = \frac{kT}{q} \ln(n) \quad \text{positive temp } \omega$$


$$\frac{\partial \Delta V_D}{\partial T} = \frac{k}{q} \ln(n) \approx 0.086 \ln(n) \text{ mV/K}$$

$$V_{ref} = \alpha_1 V_1 + \alpha_2 V_2$$

$$= V_{D1} + \Delta V_D$$

for 0 temp ω @ 300k \Rightarrow set $\frac{\partial V_{ref}}{\partial T} \Big|_{300k} = 0$
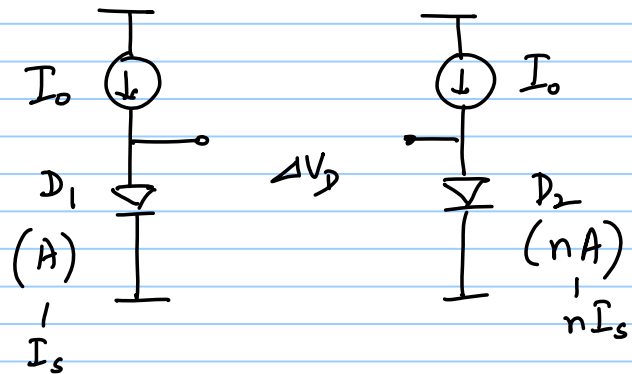
$$\Rightarrow \ln(n) = \frac{1.5}{0.086} \approx 17.4$$



alternative implementation


1) Add V_D & ΔV_D

↳ generate a current $\propto \Delta V_D$

↳ pass current through resistor

↳ connect resistor in series with diode

2) Don't need current sources

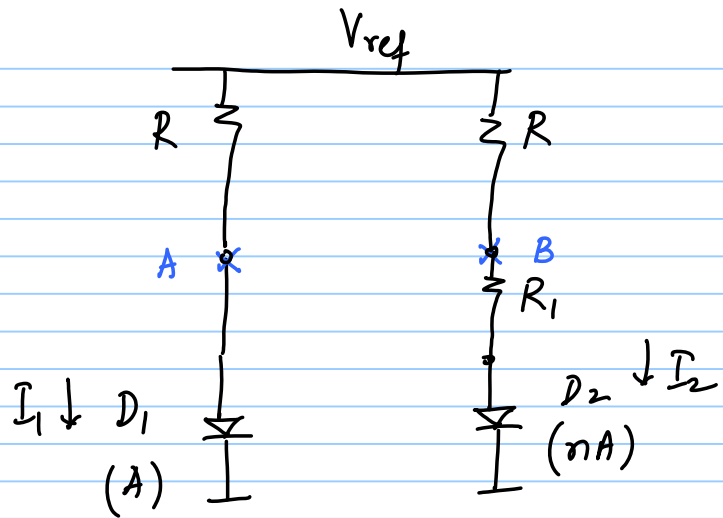

$$I_f \quad I_1 = I_2 \Rightarrow V_{D_1} > V_{D_2}$$

$$V_{D_1} = V_t \ln \left(\frac{I_D}{I_s} \right)$$


$$V_{D_2} = V_t \ln \left(\frac{I_D}{n I_s} \right)$$

$$I_f \quad V_A = V_B \Rightarrow V_{R_1} = V_{D_1} - V_{D_2} = \Delta V_D$$

$$V_B = V_{D_2} + \Delta V_D$$

$V_A = V_B$ through opamp placed in -ve f.b. $\Rightarrow I_1 = I_2$
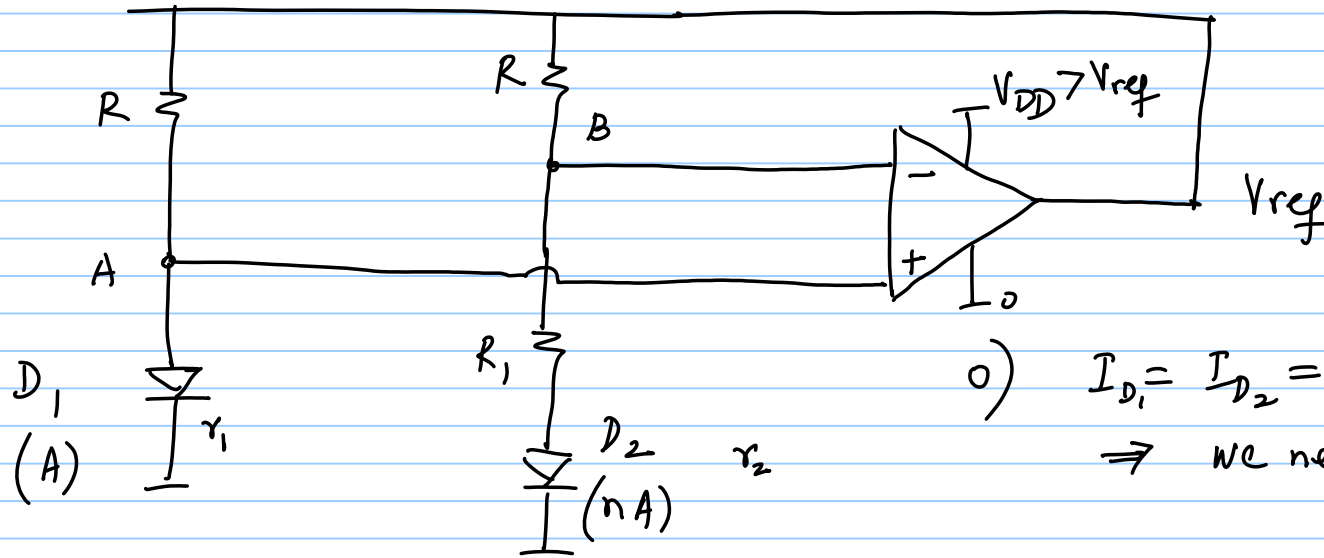
$$V_{ref} = V_{D_2} + I_2 (R + R_1) = V_{D_2} + \frac{\Delta V_D}{R_1} (R + R_1) = V_{D_2} + \Delta V_D \left(1 + \frac{R}{R_1} \right)$$



0) $I_{D1} = I_{D2} = 0$ is a valid state
 \Rightarrow we need a startup circuit

- 1) This ckt has +ve & -ve f.b.
- 2) Ensure that -ve f.b. is stronger than +ve f.b.

$$V_A = \frac{r_1}{r_1 + R} \cdot V_{ref} \quad ; \quad V_B = \frac{r_2 + R_1}{r_2 + R_1 + R} \cdot V_{ref}$$

normally $r_1, r_2 \ll R, R_1 \Rightarrow V_B > V_A$

$$V_{ref} = V_{D2} + I_2 (R_1 + R) = V_{D2} + \frac{\Delta V_D}{R_1} (R_1 + R)$$

$$= V_{D2} + \frac{kT}{q} [\ln(n)] \left[1 + \frac{R}{R_1} \right]$$

tempco }
$$\begin{array}{l} \swarrow -1.5 \text{ mV/K} \\ \searrow 0.086 [\ln(n)] \left[1 + \frac{R}{R_1} \right] \end{array}$$

$$\left. \frac{\partial V_{ref}}{\partial T} \right|_{300K} = 0 \Rightarrow \left(1 + \frac{R}{R_1} \right) \ln(n) = 17.4$$


$$V_{ref} = V_{D2} + \frac{kT}{q} \times 17.4 \sim 1.25V$$


1) Tempco of resistors : choose R & R_1 to be same type of res.

$$\frac{R}{R_1} = \text{constant}$$

$$2) \quad I_1 = I_2 = \frac{\Delta V_D}{R} = \frac{kT}{qR_1} \cdot \ln(n) \propto T$$

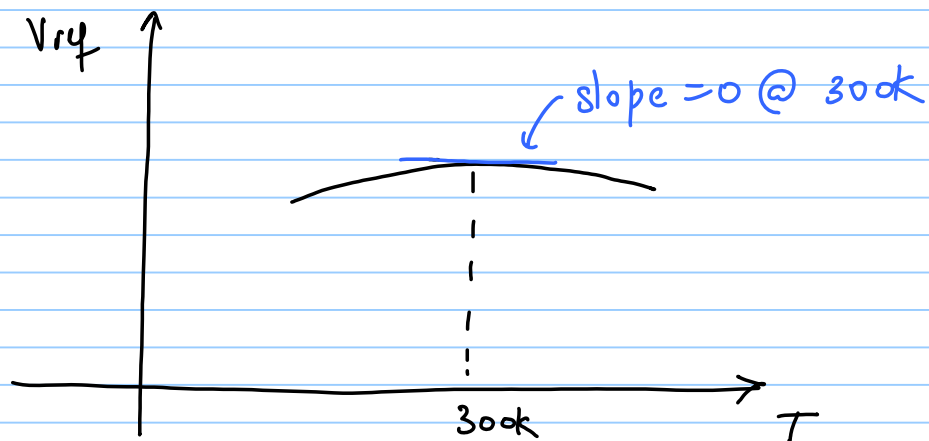"PTAT" current
"proportional to absolute temperature") Useful to bias circuits




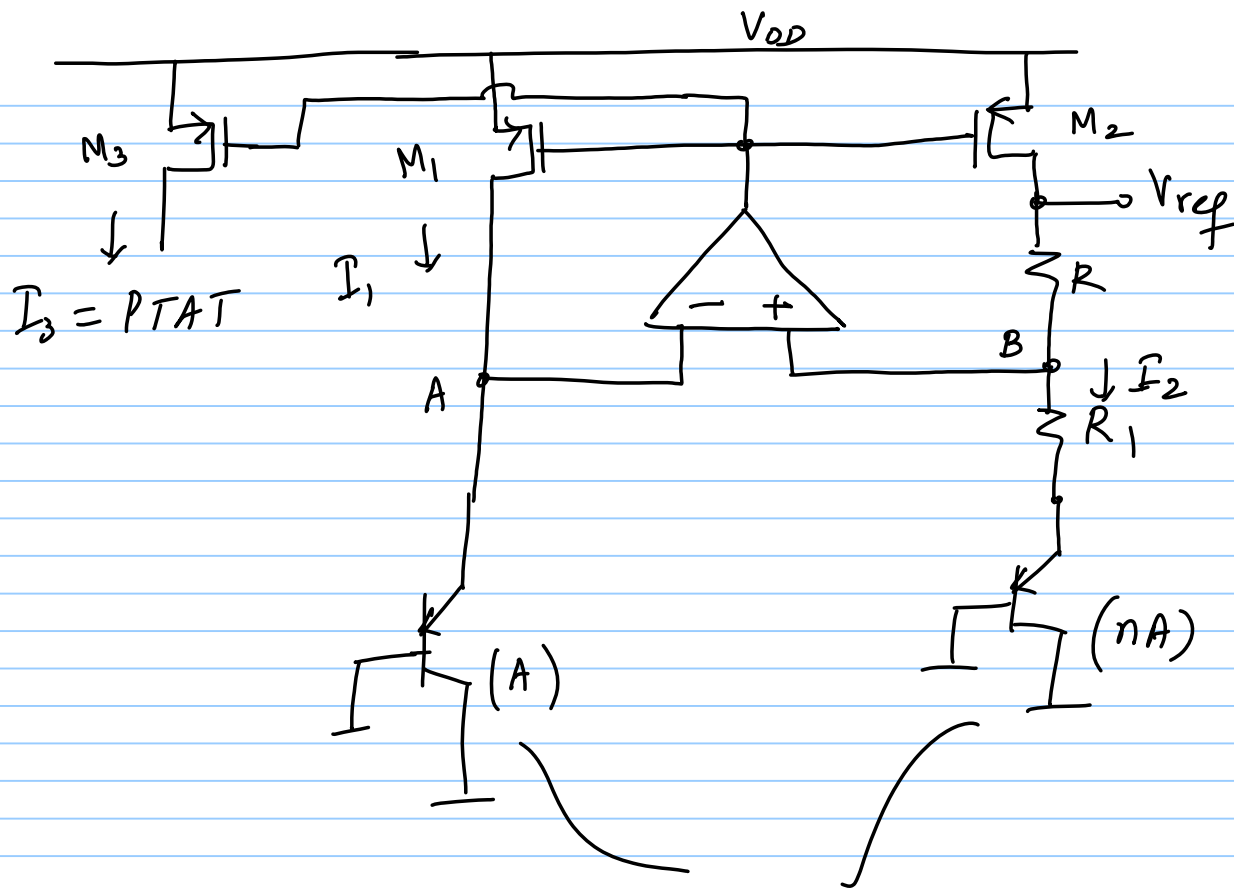

$$M_1 = M_2$$

$$V_A = V_B$$

$$I_1 = I_2 = PTAT \text{ current}$$

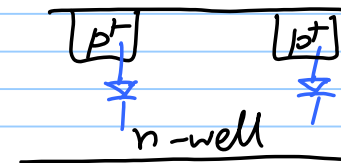

→ make it behave as pnp

parasitic pnp transistors

1) What happens if $V_{DD} < 1.25V$? "Fractal" BG

28/11/17


Lec 25

Fractional B_G

$$V_{ref} = V_D + \alpha \Delta V_D \approx 1.25V$$


What if $V_{DD} < 1.25V$
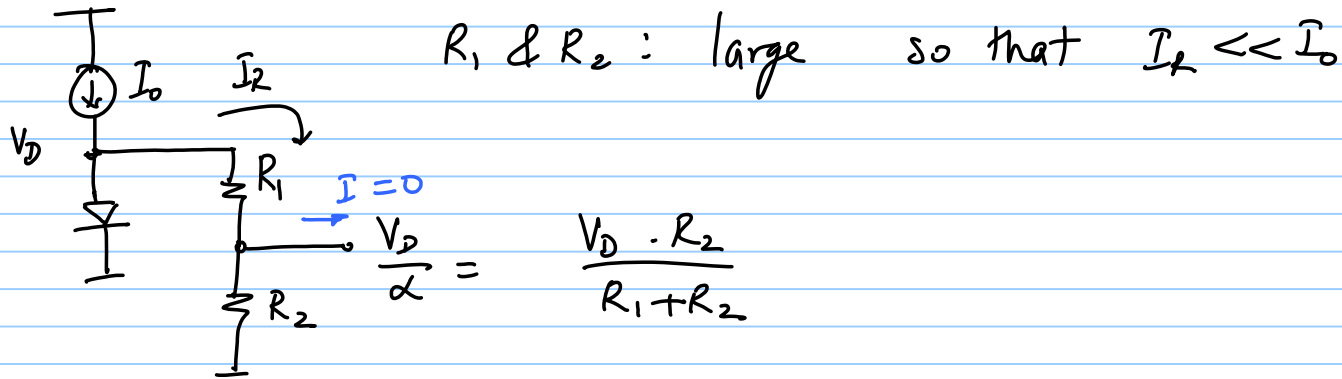
$$\frac{V_{ref}}{\alpha} = \frac{V_D}{\alpha} + \Delta V_D$$




Fractional Bandgap Reference

Conceptual
Circuit

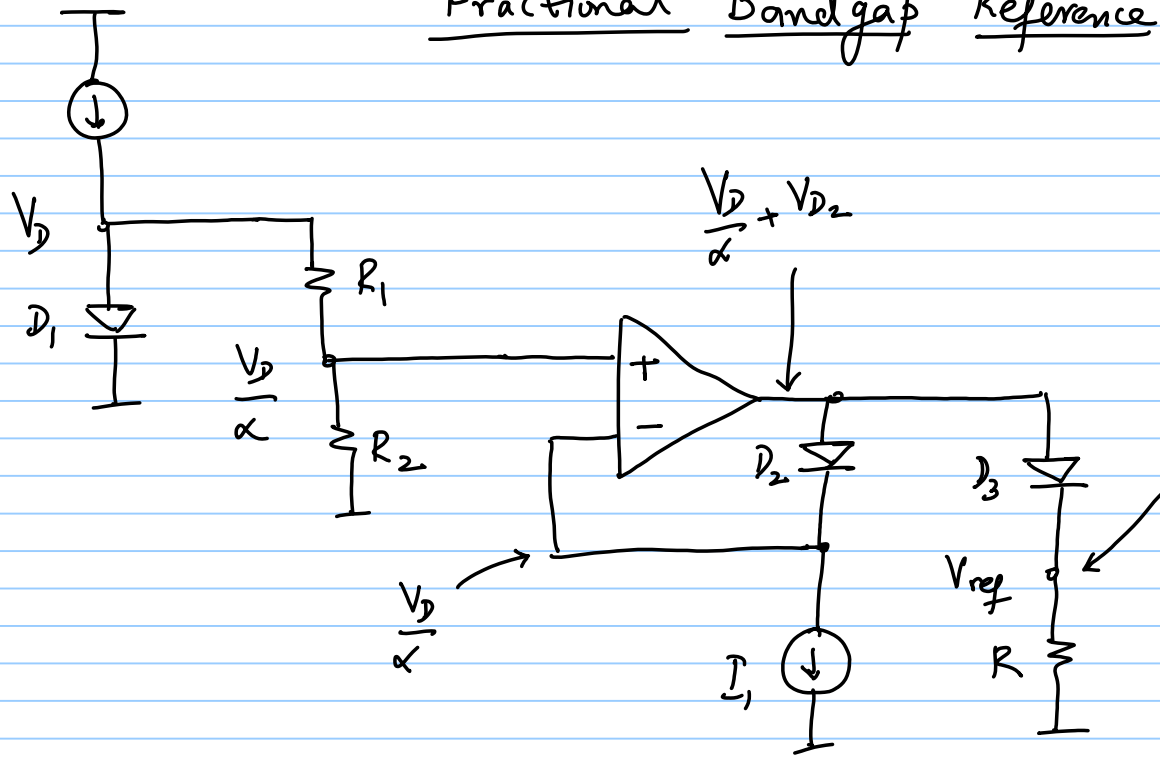

$$V_{ref} = \frac{V_D}{\alpha} + (V_{D2} - V_{D3})$$
$$= \frac{V_D}{\alpha} + \Delta V_D$$

Voltage Regulators

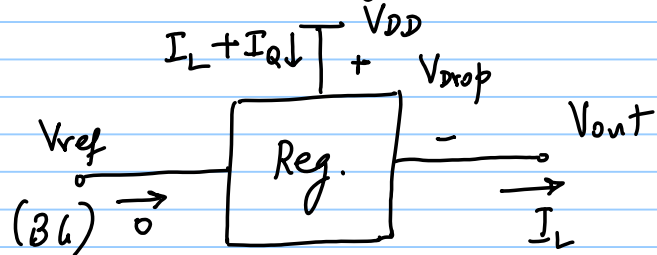


- * $V_{out} = V_{DD} - V_{drop}$ — dropout voltage
- * $V_{out} = \text{constant}$
- * $R_{out} = \text{low}$
- * $\eta = \text{efficiency}$ should be high

$$P_{out} = V_{out} \cdot I_L ; P_{in} = V_{DD} (I_L + I_Q)$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V_{out} \cdot I_L}{V_{DD} (I_L + I_Q)} = \frac{V_{out}}{V_{out} + V_{drop}} \cdot \frac{I_L}{I_L + I_Q}$$

“LDO”: Low Dropout Regulator

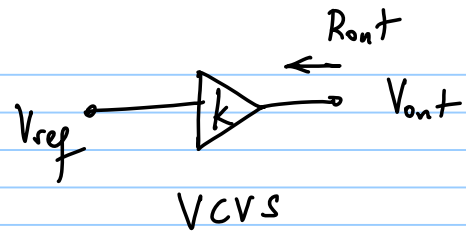We want minimum V_{drop} & I_Q for best efficiency





negative
use feedback

- * Load regulation: $\frac{\Delta V_{out}}{\Delta I_L} = \text{small signal } R_{out}$
 - * Line regulation: $\frac{\Delta V_{out}}{\Delta V_{DD}}$
- } We want both to be small


* step changes in I_L : change in V_{out} to be small

* Frequency response of feedback circuit

* $\left| \frac{V_{out}(f)}{V_{DD}(f)} \right| \ll 1$ (small-signal)
 "Power Supply Rejection Ratio" or PSRR

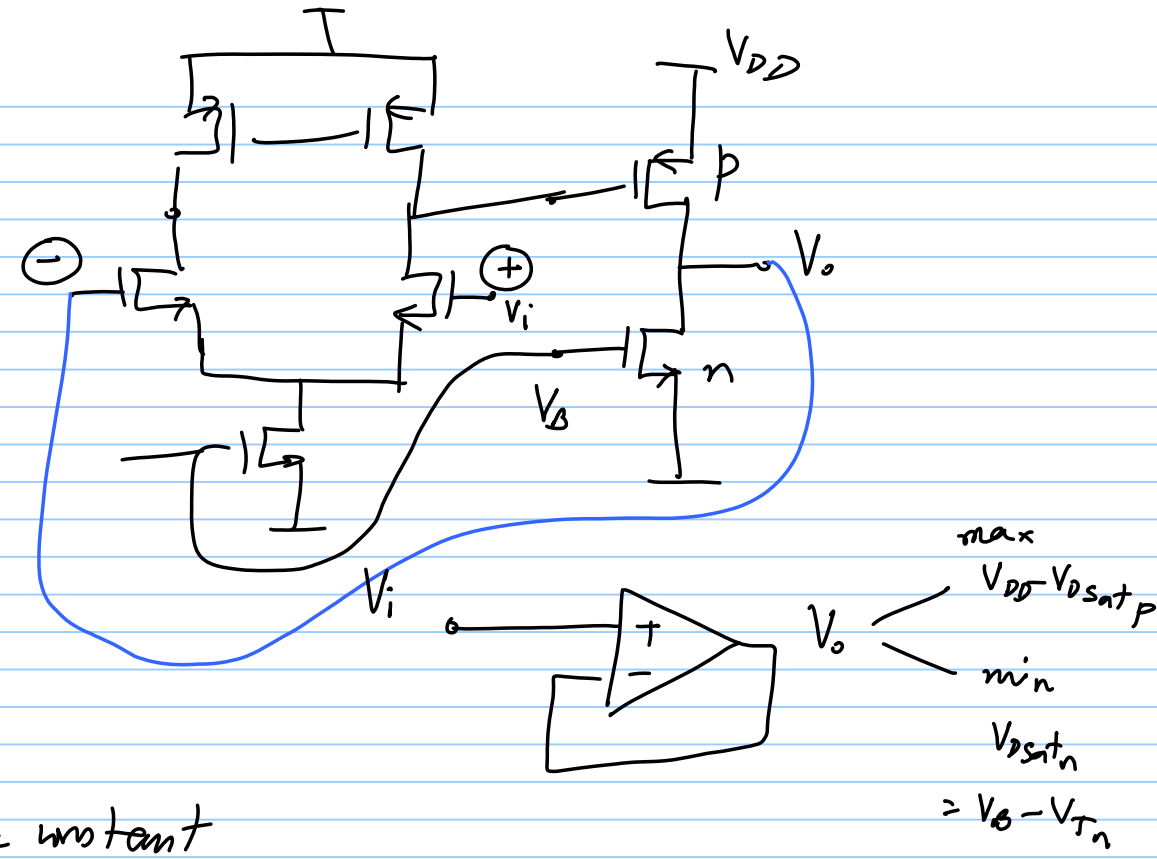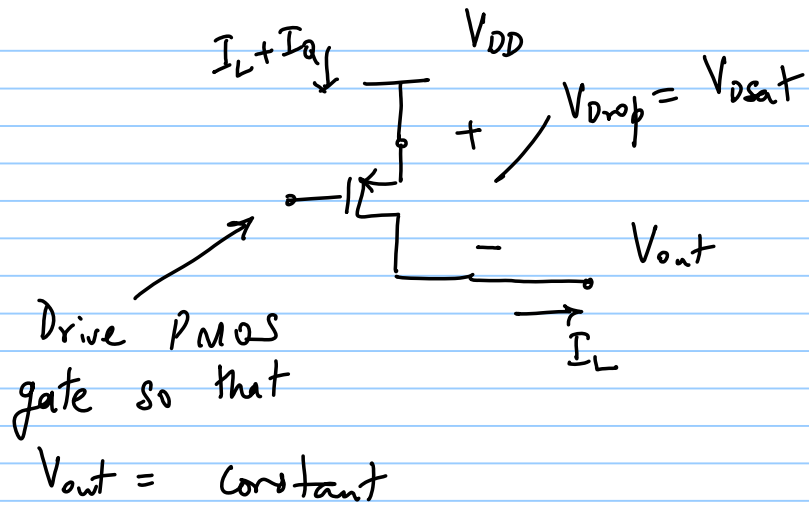

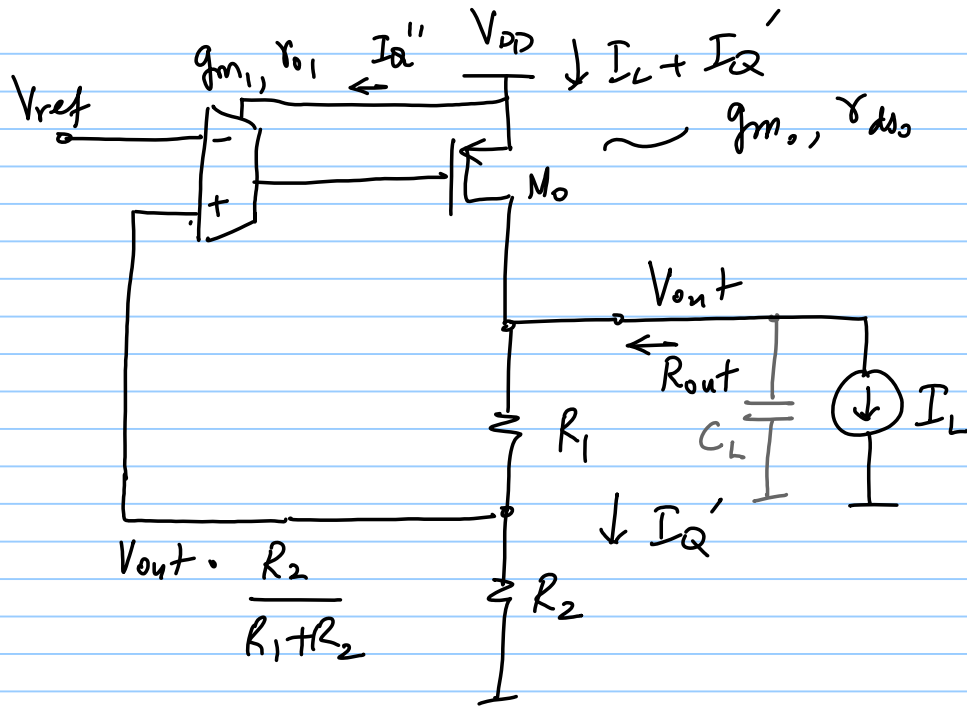- * Sense V_{out} (or a portion)
- * Compare to V_{ref}
- * Drive PMOS gate so that $V_{out} = \text{constant}$



R_1, R_2 : large (small I_Q)


$$I_{Q}'' + I_{Q}' = I_Q$$


$$r_{ds0} \ll R_1, R_2$$

$$R_{out} = \frac{r_{ds0}}{1 + A_0}$$

$$A_0 = g_{m1} r_{o1} \cdot g_{m0} r_{ds0} \cdot \frac{R_2}{R_1 + R_2}$$

(dc gain of loop)

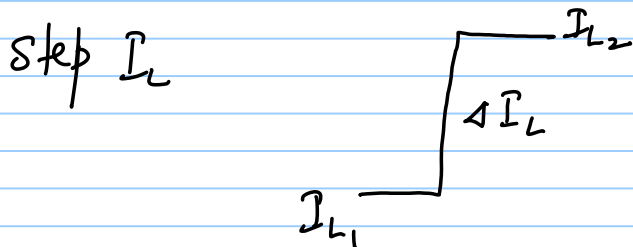

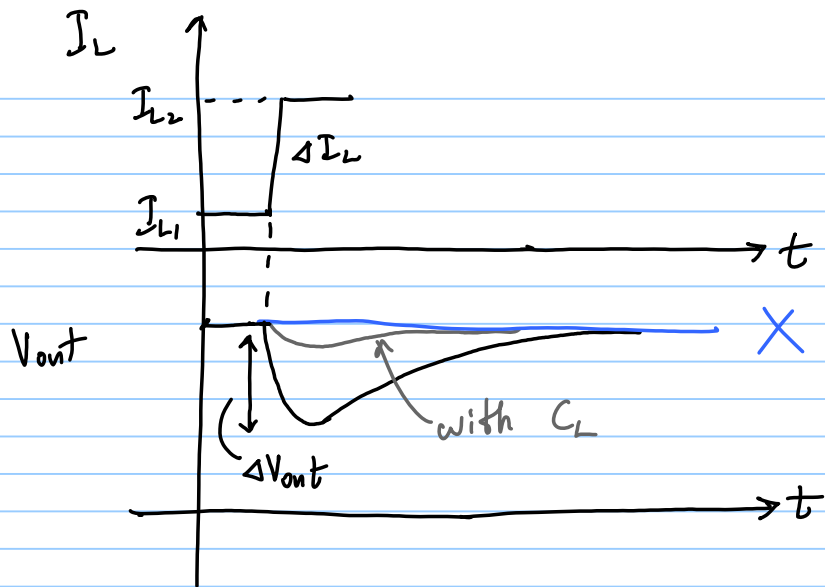


$$\Delta V_{out} = \Delta I_L \cdot r_{ds0}$$

$$\text{exact: } \Delta I_L \cdot \left(r_{ds0} \parallel (R_1 + R_2) \right)$$

{ can be large }


Add large cap. C_L at output node to deliver ΔI_L

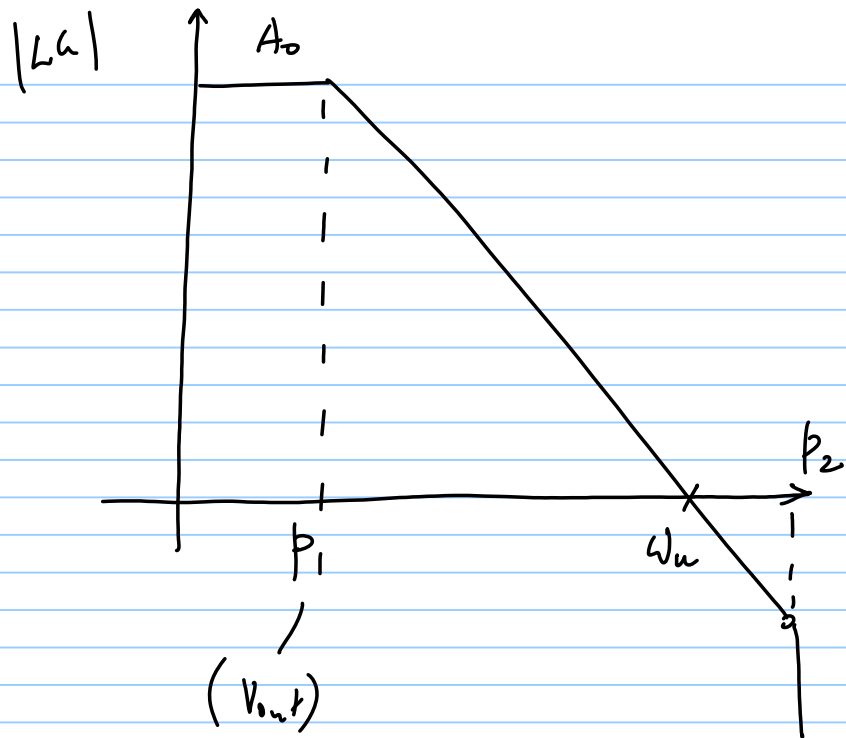V_{out} becomes the dominant pole node for freq. response



$$p_1 = \frac{1}{C_L \cdot r_{ds0}} ; p_2 = \frac{1}{C_{gs0} \cdot r_{o1}}$$

$$\omega_u = p_1 \times A_0$$

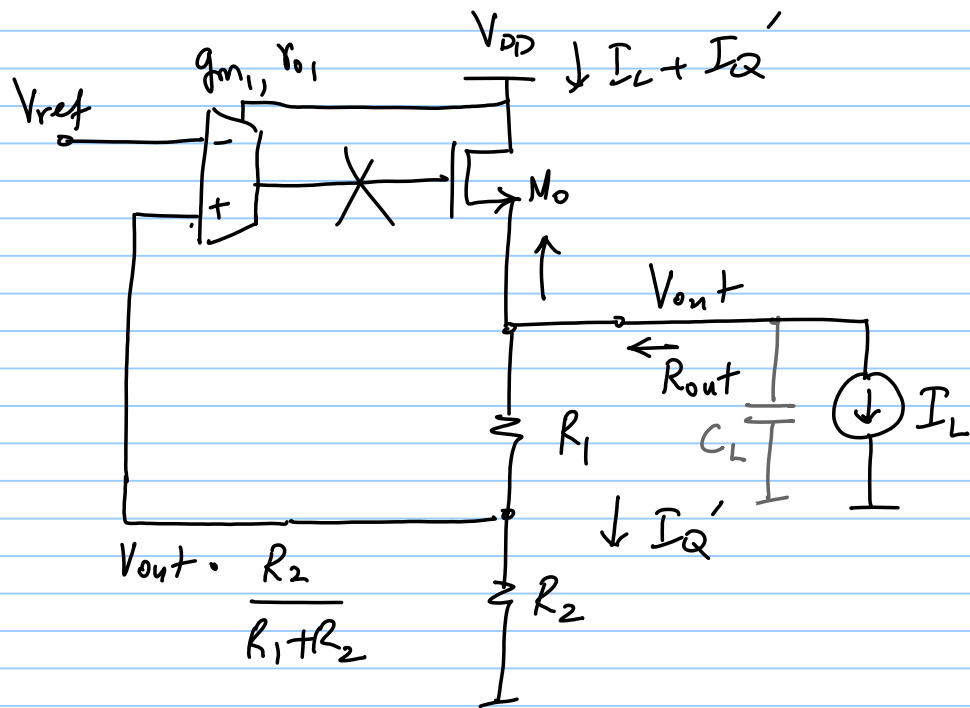

NMOS reg:

High BW

high Dropout