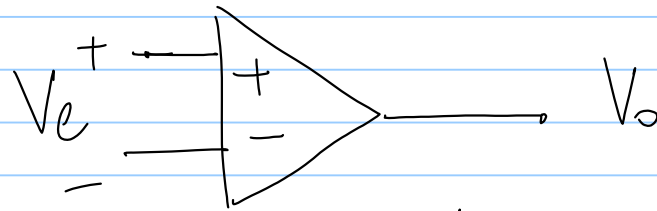


12/02/2019




Offset

Lec 14



$$V_o = A V_e$$

$$V_o = A (V_e + \Delta V)$$

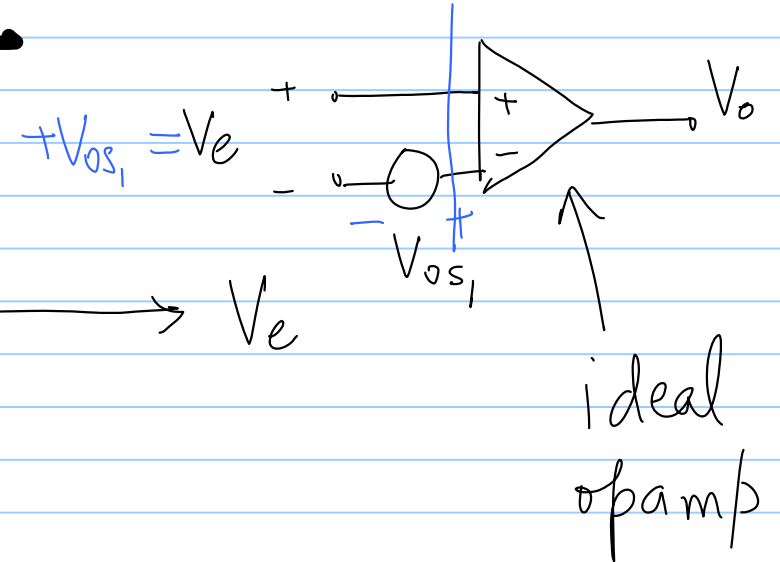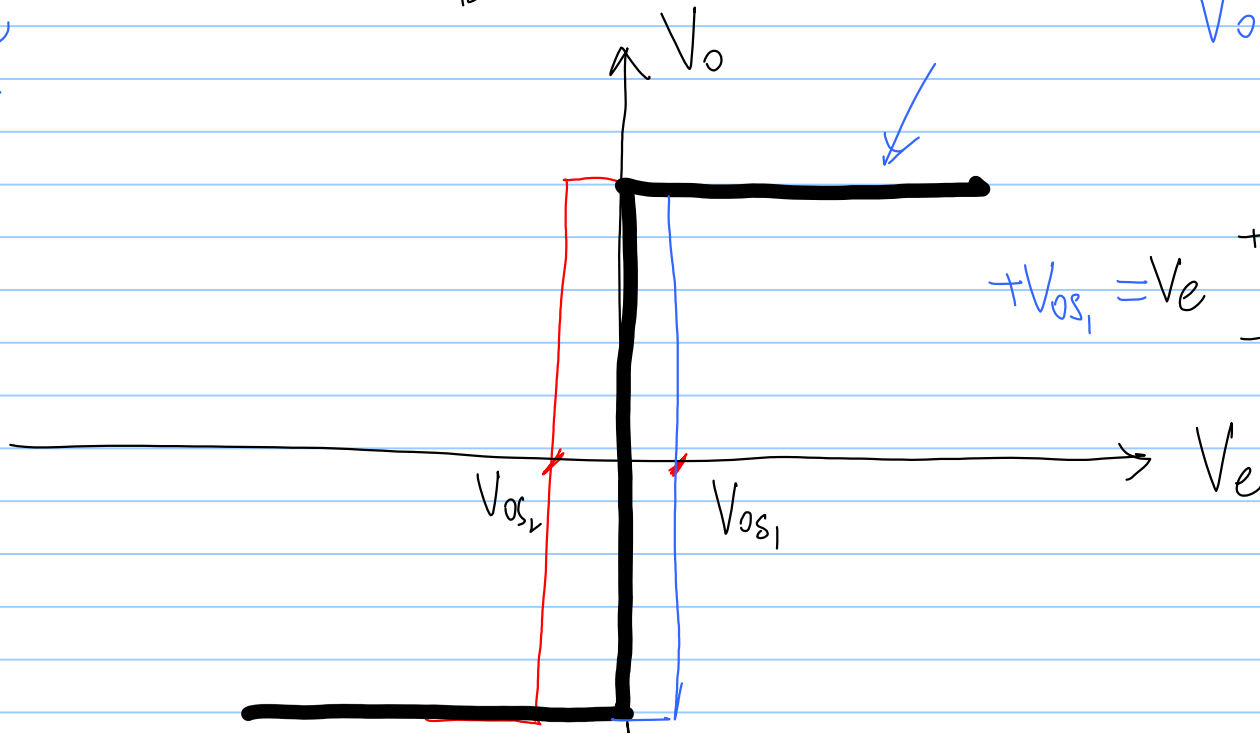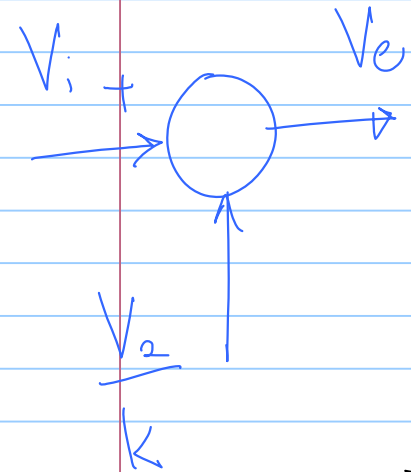

Signs of opamp

