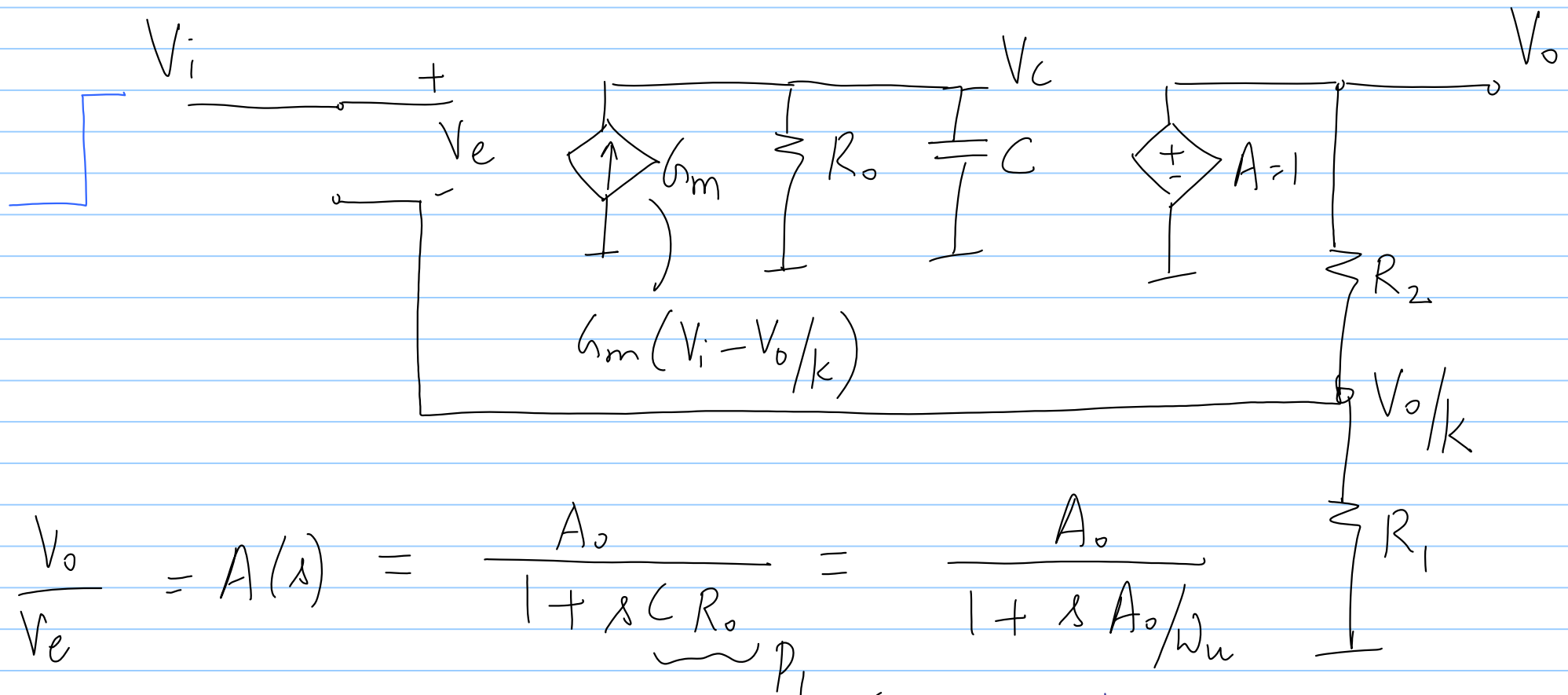



13/2/19

Lec 15



$$\frac{V_o}{V_e} = A(s) = \frac{A_o}{1 + s \underbrace{C R_o}_{p_1}} = \frac{A_o}{1 + s \underbrace{A_o / \omega_u}_{\omega_u}}$$
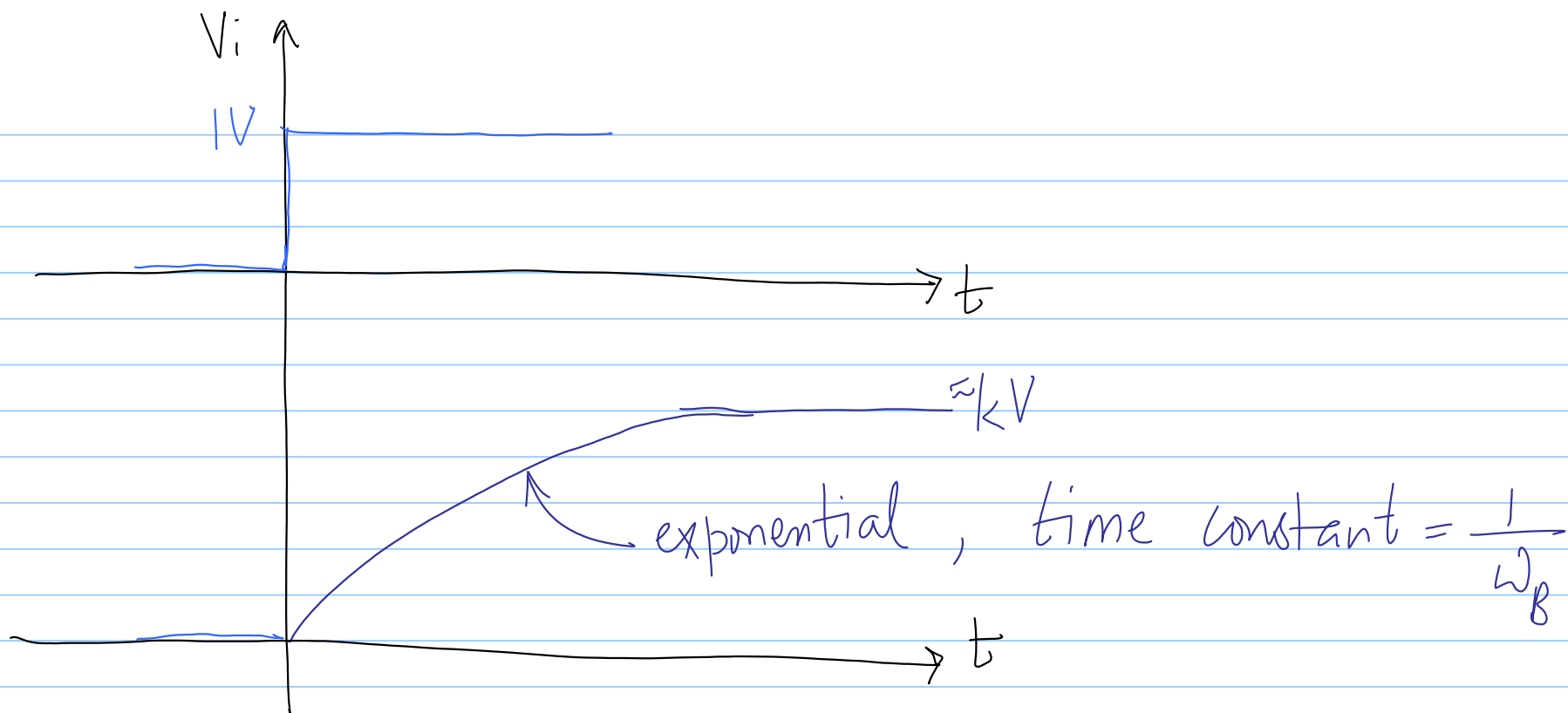
$$A_o = G_m R_o ; \quad \omega_u = \frac{G_m}{C}$$



$$\frac{V_o}{V_i}(\omega) = ?$$


$$V_e(s) = V_i(s) - \frac{V_o(s)}{k}$$

$$V_o(s) = A(s) \cdot V_e(s)$$

$$= V_i(s) \cdot A(s) - V_o(s) \cdot \frac{A(s)}{k}$$

$$V_o(s) \left\{ 1 + \frac{A(s)}{k} \right\} = V_i(s) \cdot A(s)$$
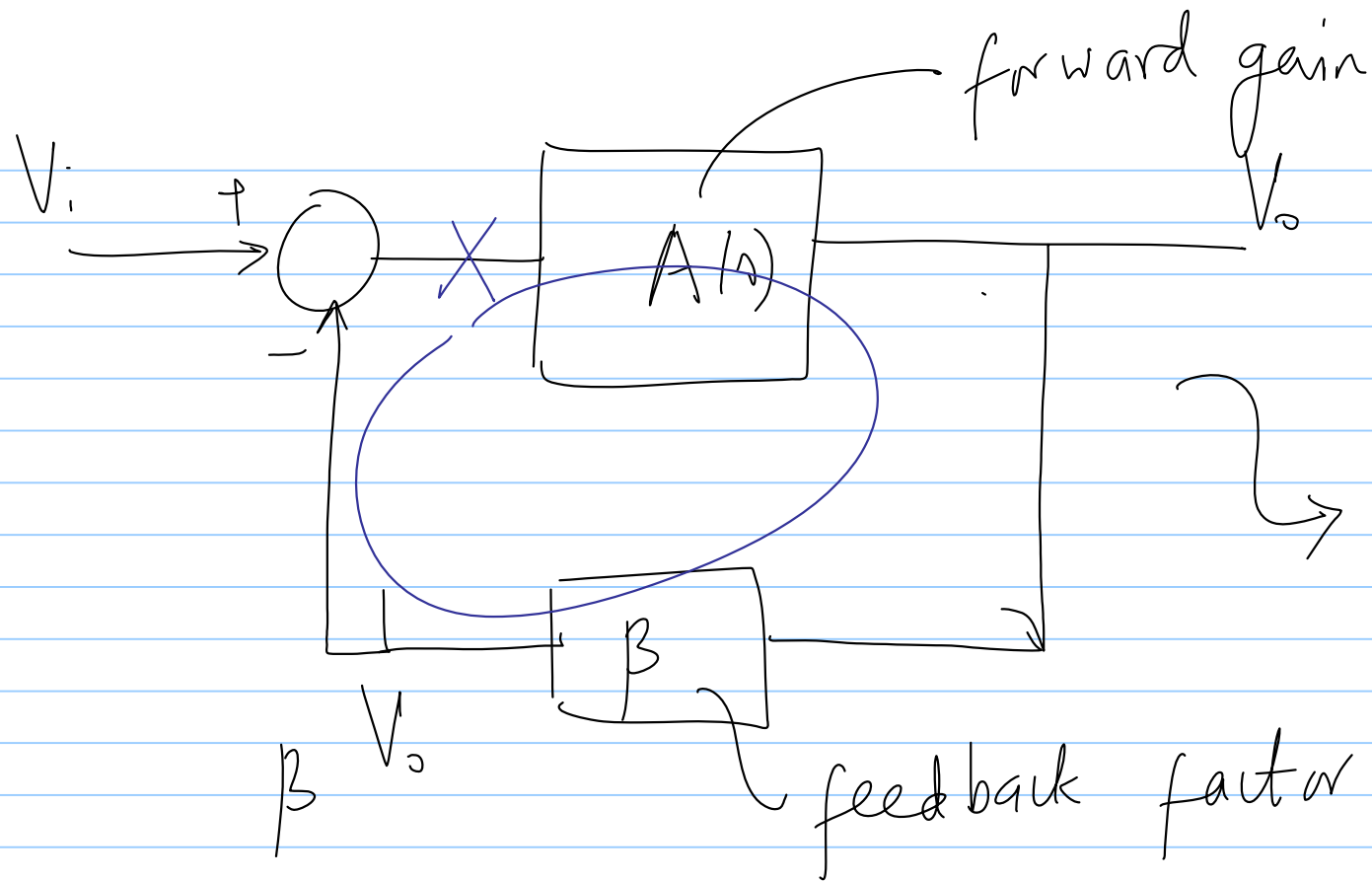
$$\frac{V_o(s)}{V_i(s)} = \frac{A(s)}{1 + \frac{A(s)}{k}}$$



$$\frac{V_o}{V_i} = \frac{A(s)}{1 + \beta A(s)}$$

"closed loop gain"

$$\beta A(s) = \text{"Loop gain"}$$

$$\frac{V_o}{V_i}(s) = \frac{A(s)}{1 + \frac{A(s)}{k}} = \frac{A_o / (1 + sCR_o)}{1 + \frac{A_o / (1 + sCR_o)}{k}}$$

$$= \frac{k A_o}{k(1 + sCR_o) + A_o} = \frac{k A_o}{k + A_o + sCR_o}$$

$$= k \cdot \left(\frac{1}{1 + \frac{k}{A_o}} \right) \cdot \frac{1}{1 + \frac{s}{\omega_B}}$$



$$\omega_B = \frac{A_o + k}{CR_o k}$$


$$\omega_B = p_1 \left(1 + \frac{A_0}{K} \right)$$

1 pole @ $p_1 \left(1 + \frac{A_0}{K} \right)$
(LHP)

" -3dB Bandwidth "

$$\left| \frac{A}{(1 + s/p)^2} \right| = \frac{A}{\sqrt{2}}$$


$$|| @ p = \frac{A}{\sqrt{2}}$$

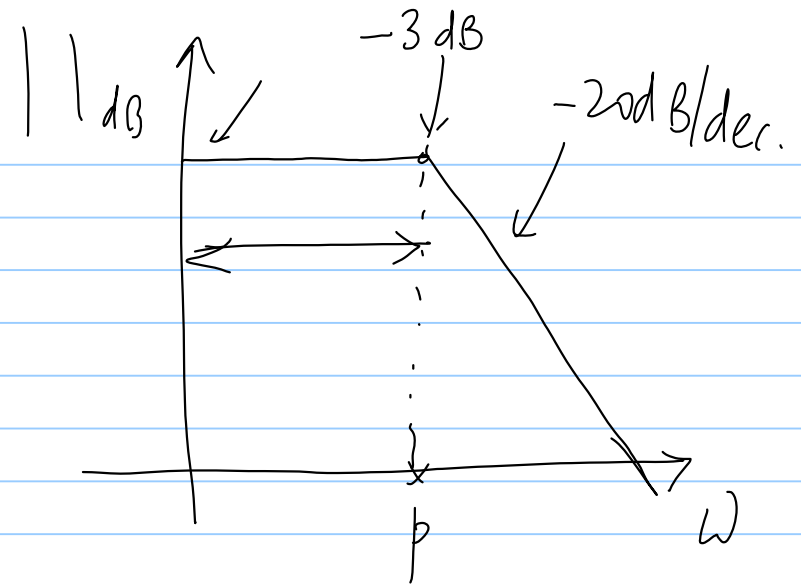

1-pole system.

fast response $\rightarrow$ large $\frac{A_0}{k}$; large ω_n
 $\downarrow$
large G_m
small C

$G_m R_o$ — finite
few 10^5 to 100-200

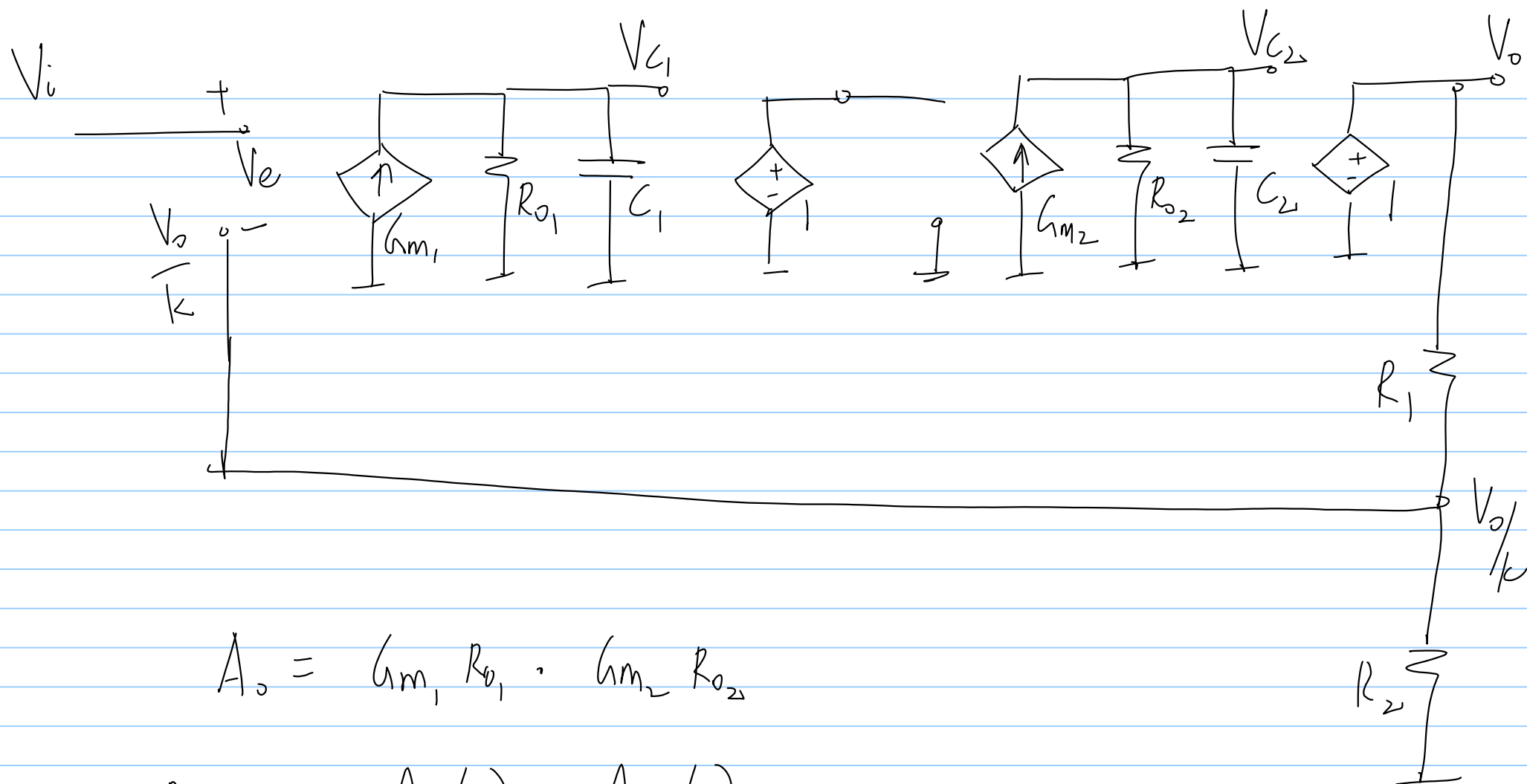

$$A_o = G_{m1} R_{o1} \cdot G_{m2} R_{o2}$$

$$A(s) = A_1(s) \cdot A_2(s)$$

$$A_1(s) = \frac{A_{01}}{1 + \underbrace{sC_1 R_{01}}_{1/p_1}}; \quad A_2(s) = \frac{A_{02}}{1 + \underbrace{sC_2 R_{02}}_{1/p_2}}$$

$$\frac{V_o(s)}{V_e(s)} = A(s)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{A(s)}{1 + \frac{A(s)}{K}}$$

$$p_1 = \frac{1}{C_1 R_{01}}; \quad p_2 = \frac{1}{C_2 R_{02}}$$