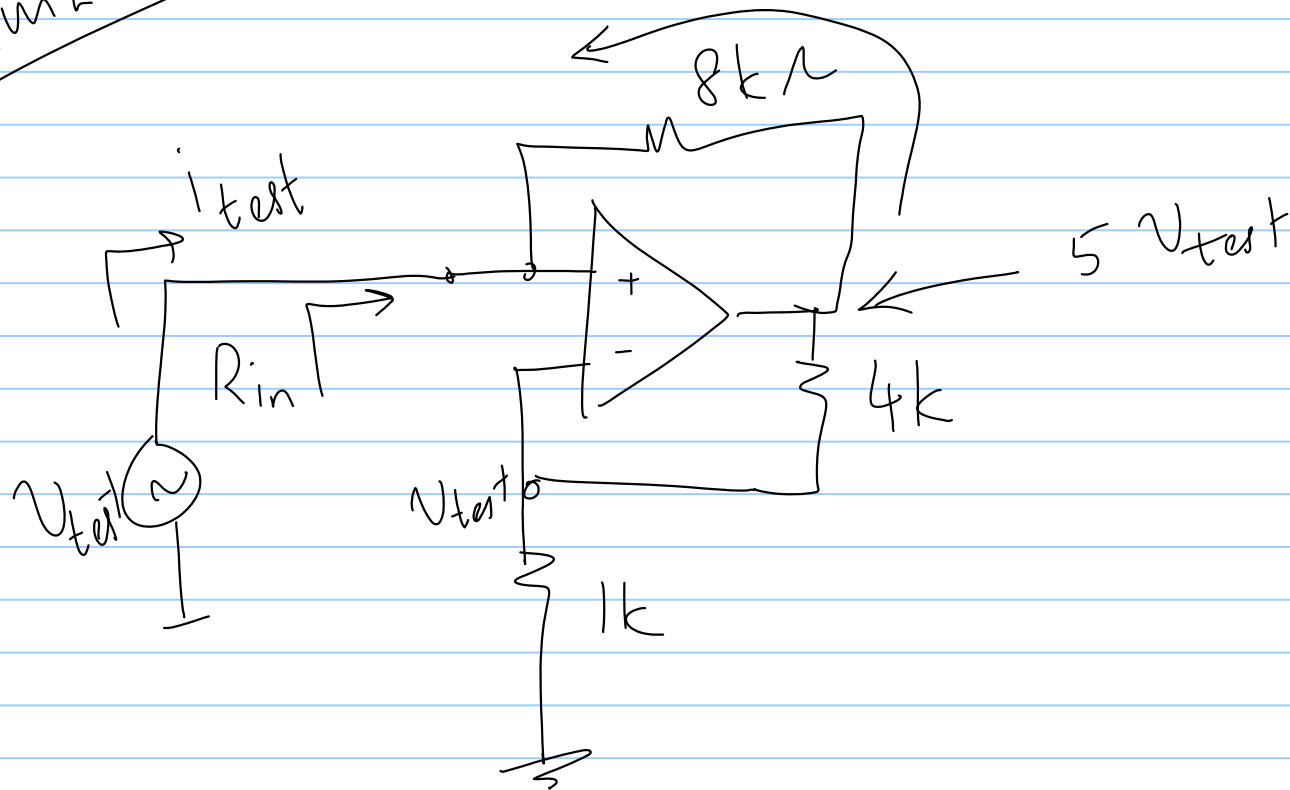



15/2/19

Quiz 1

Lec 16



2-stage opamp

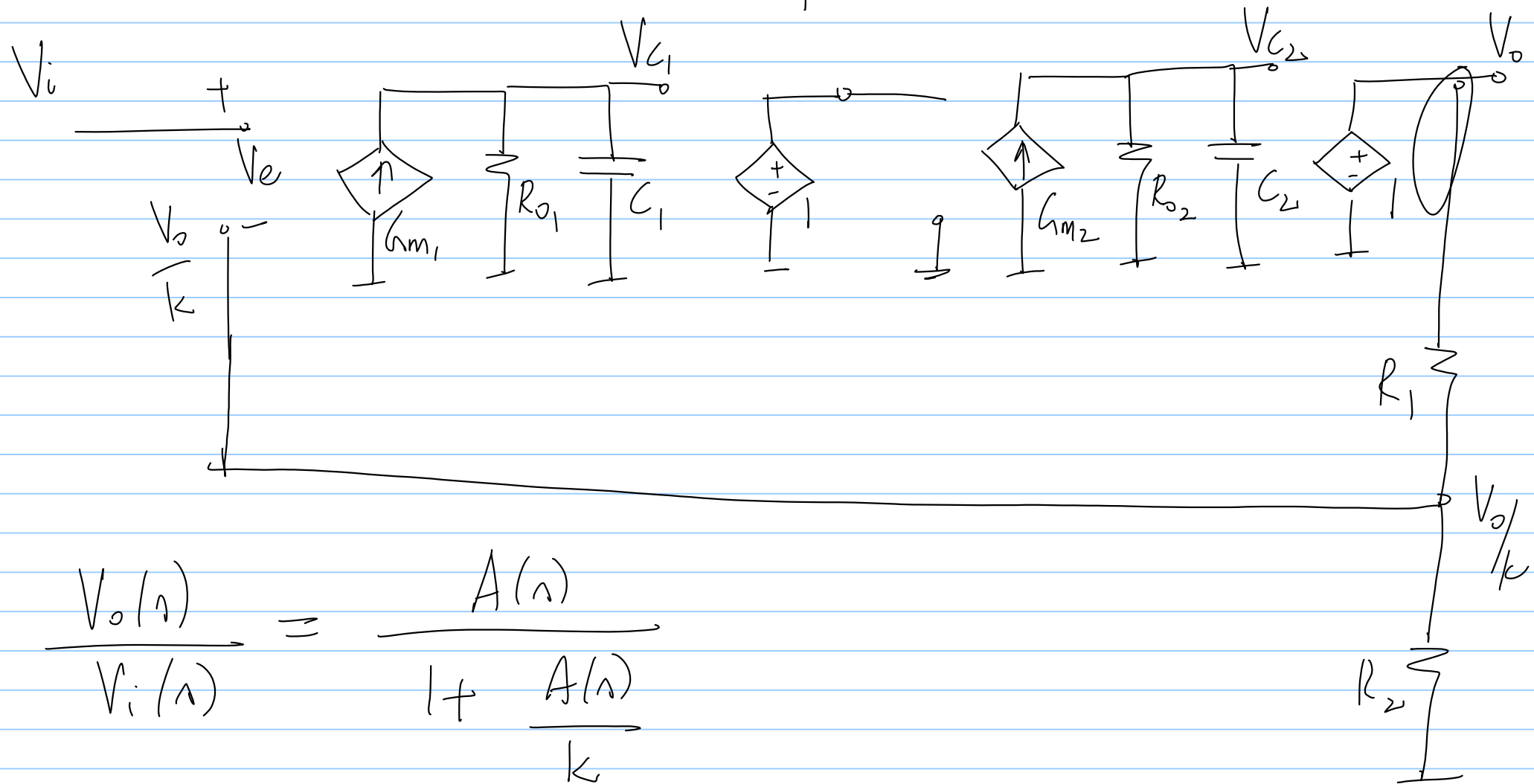

$$A(s) = A_1(s) \cdot A_2(s) \quad ; \quad A_0 = A_{01} \cdot A_{02}$$


$$= \frac{A_{01}}{\left(1 + s/p_1\right)} \cdot \frac{A_{02}}{\left(1 + s/p_2\right)}$$


$$\frac{V_o(s)}{V_i(s)} = \frac{k}{1 + \frac{k}{A(s)}} = \frac{k}{1 + \frac{k}{A_0} \cdot \left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)}$$

$$= \frac{k}{\left(1 + \frac{k}{A_0}\right) + \frac{s k}{A_0} \left(\frac{1}{p_1} + \frac{1}{p_2}\right) + s^2 \frac{1}{p_1} \cdot \frac{1}{p_2} \cdot \frac{k}{A_0}}$$

all coefficients +ve $\Rightarrow$ Roots in LHP
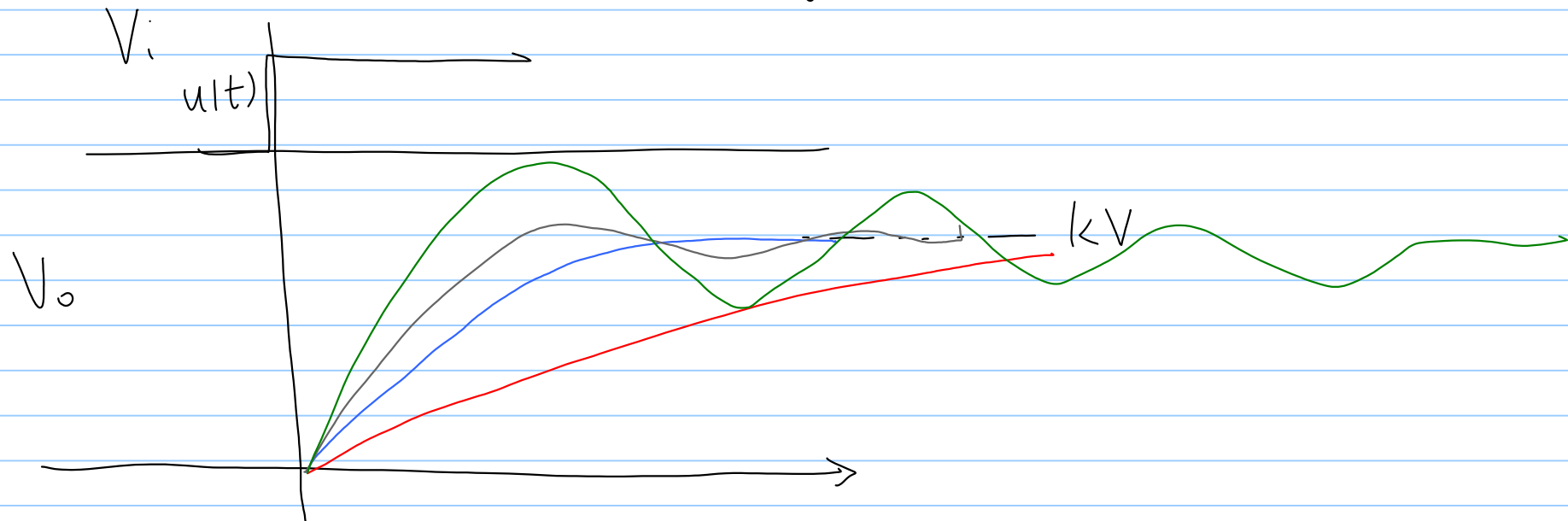
$$\left. \begin{aligned} s^2 + 2\zeta\omega_n s + \omega_n^2 \\ s^2 + \frac{\omega_n s}{Q} + \omega_n^2 \end{aligned} \right\} \begin{array}{l} \text{Std. forms of} \\ \text{2nd order system} \end{array}$$




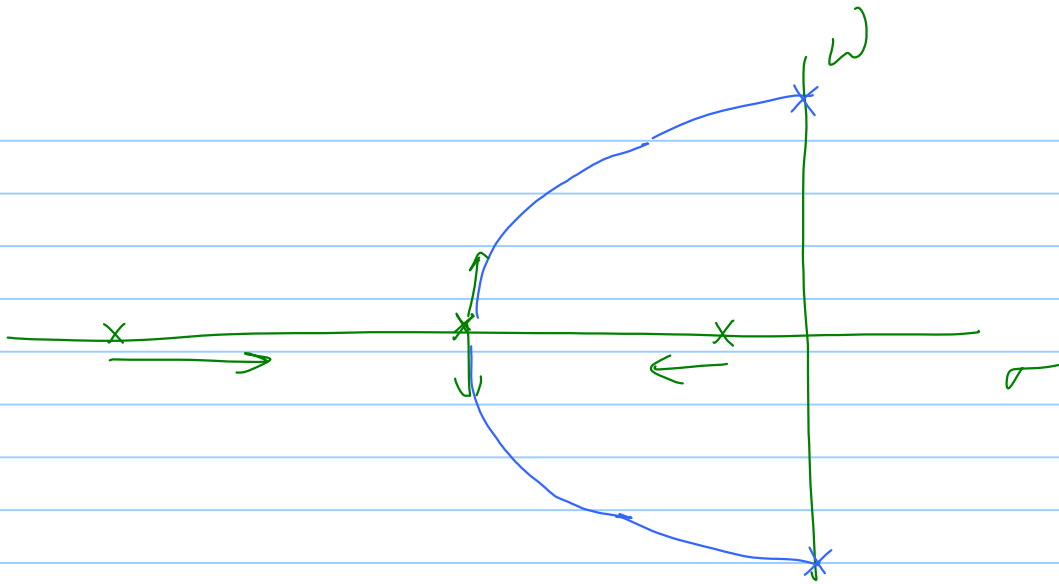

$$\omega_n = \sqrt{\left(\frac{A_0}{k} + 1\right) (p_1 p_2)}$$

$$\zeta = \frac{1}{2} \left[\sqrt{\frac{p_1}{p_2}} + \sqrt{\frac{p_2}{p_1}} \right] \sqrt{\frac{k}{A_0 + k}}$$
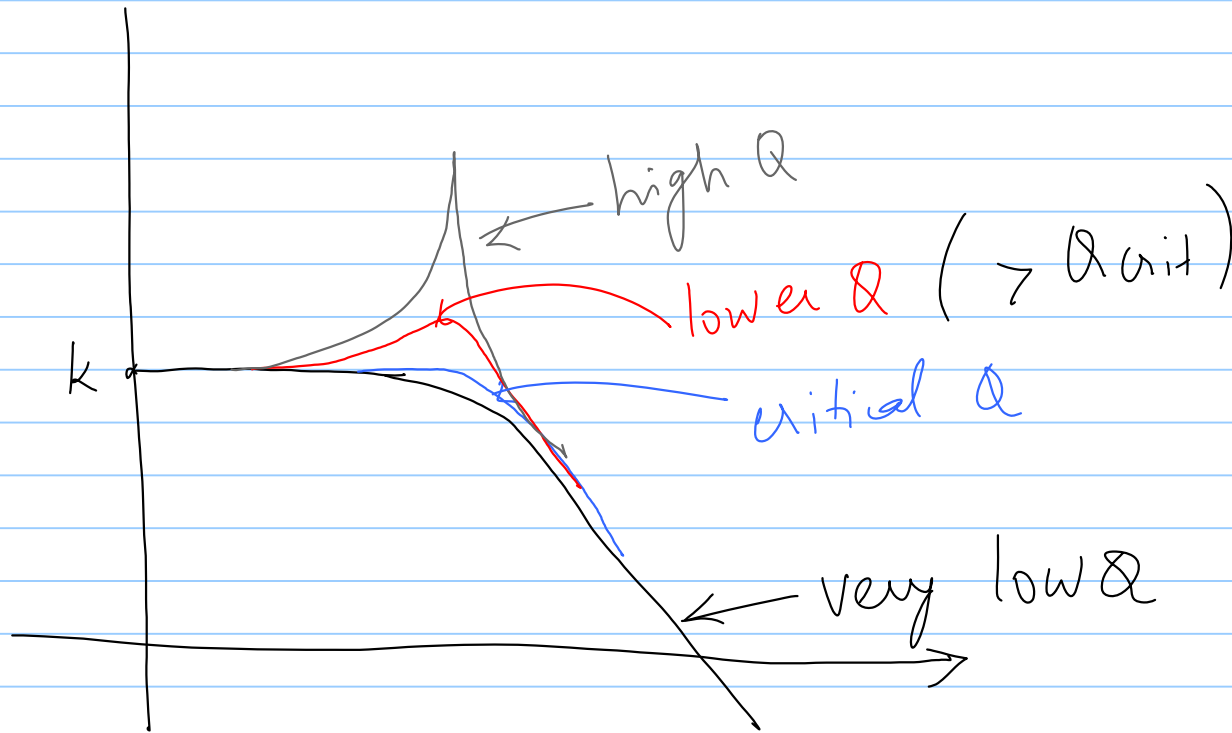
$$Q = \frac{1}{2\zeta} = \frac{1}{\sqrt{\frac{A_0 + k}{k} \left(\sqrt{\frac{p_1}{p_2}} + \sqrt{\frac{p_2}{p_1}} \right)}}$$



* unconditionally stable

* ringing possible

* well-spaced apart poles. avoids ringing

Next step - 3 stage opamp

$$A(s) = \frac{A_0}{(1 + s/p)^3}$$

} even more
tending towards
ringing