

21/2/19

Lec 19

$$L(h/s) = \frac{A_0/k}{\left(1 + s/p_1\right)\left(1 + \frac{s}{p_2}\right)}$$

$$\beta = 1/k$$

$$p_2 \gg p_1$$

$$A_0/k \gg 1$$

roots
of


$$1 + L(h/s) = 0$$

$$z = \frac{1}{2} \left[\sqrt{\frac{p_1}{p_2}} + \sqrt{\frac{p_2}{p_1}} \right] \sqrt{\frac{k}{A_0 + k}}$$

$$\omega_n = \sqrt{\frac{A_0}{k} + 1} \sqrt{p_1 p_2}$$

3	$p_2/\omega_{u,loop}$	Phase lag @ $\omega_{u,loop}$	PM = $180^\circ + \text{phase lag}$
1	4	$-90 - \tan^{-1}(1/4)$	76°
$\frac{1}{\sqrt{2}}$	2	$-90 - \tan^{-1}(1/2)$	63°
$\frac{1}{2}$	1	$-90 - \tan^{-1}(1)$	45°
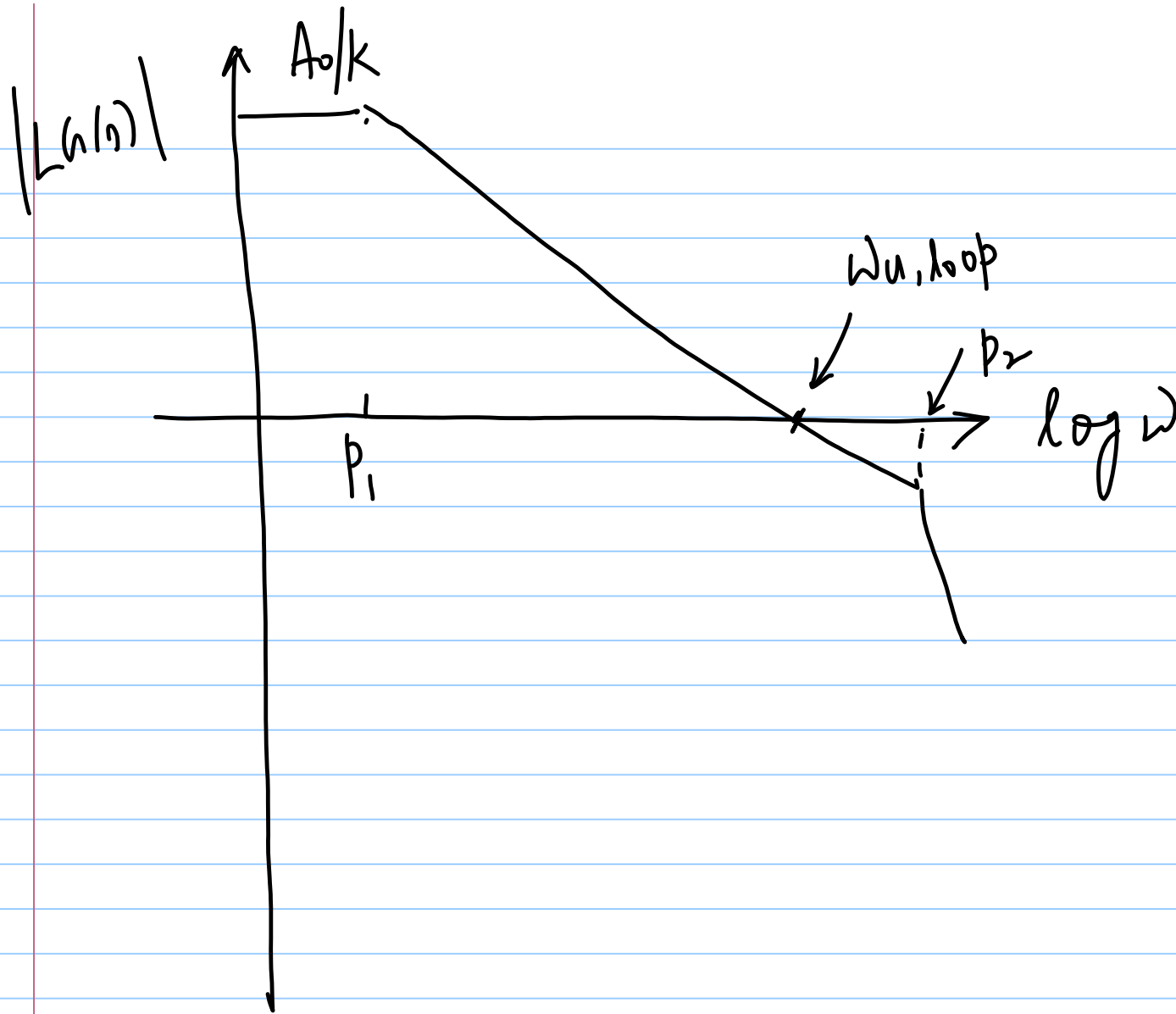
$$\text{Phase lag} = \underbrace{-\tan^{-1}\left(\frac{\omega_{u,loop}}{p_1}\right)}_{-90^\circ} - \tan^{-1}\left(\frac{\omega_{u,loop}}{p_2}\right) \quad \checkmark$$




$$\omega_{u,loop} = \frac{1}{p_1} \frac{A_0}{k}$$


$$\zeta = \frac{1}{2} \left[\sqrt{\frac{p_1}{p_2}} + \sqrt{\frac{p_2}{p_1}} \right] \cdot \sqrt{\frac{k}{A_0 + k}}$$

$$= \frac{1}{2} \sqrt{\frac{p_2}{p_1}} \cdot \sqrt{\frac{k}{A_0}}$$

$$= \frac{1}{2} \sqrt{\frac{p_2}{\omega_{u,loop}}}$$

$V_o(t)$

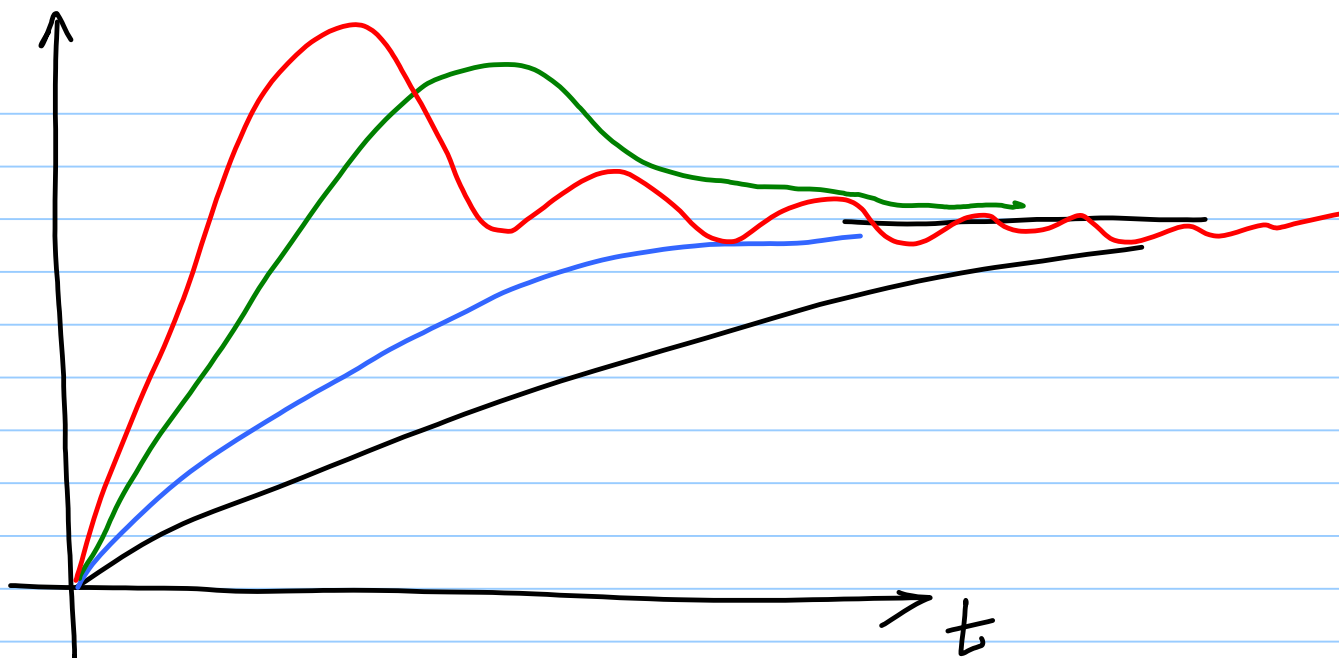

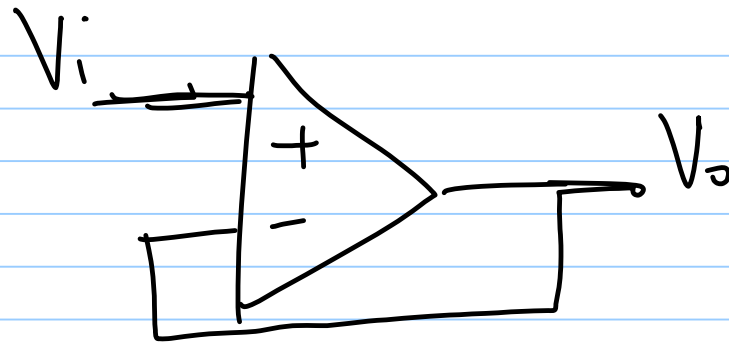

"Unity gain compensated" of amp

↳ assured of stability even for
other gains (k)