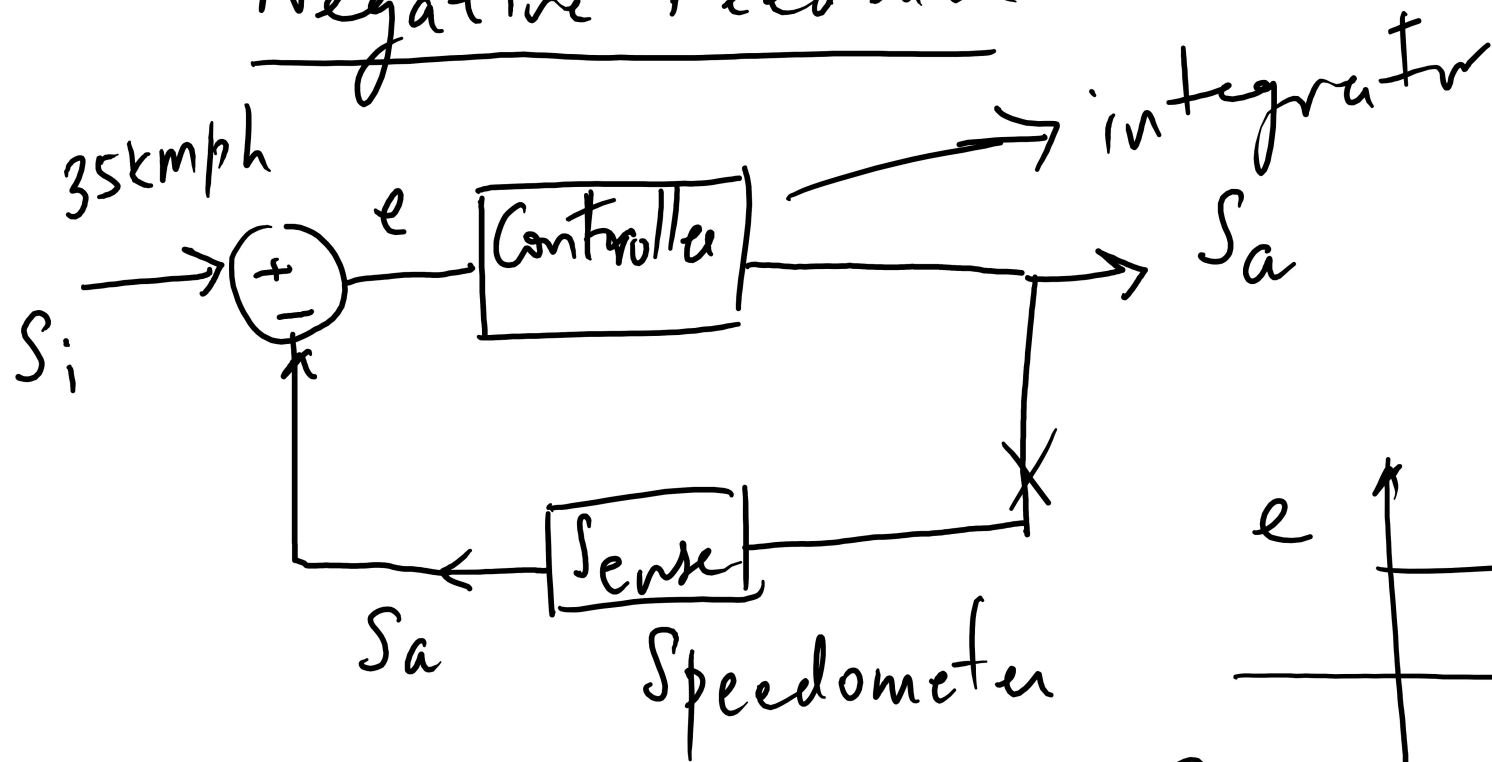


18/1/19


Lec 2



Negative Feedback



$$S_a = k \int e dt$$

$\underbrace{\hspace{10em}}_{\omega_u}$

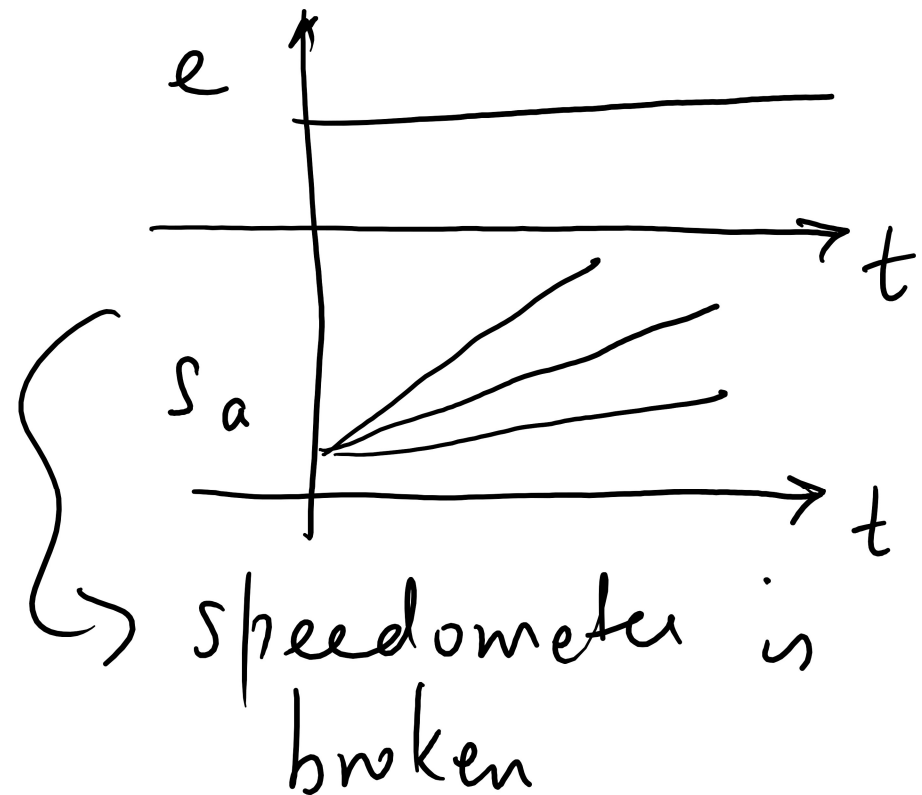

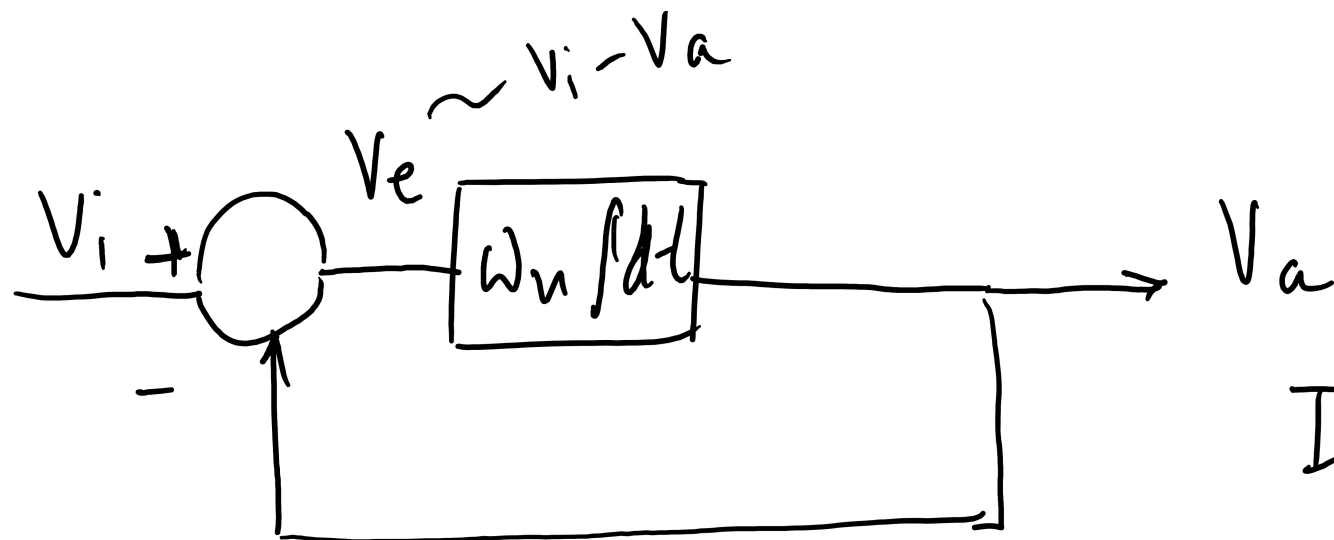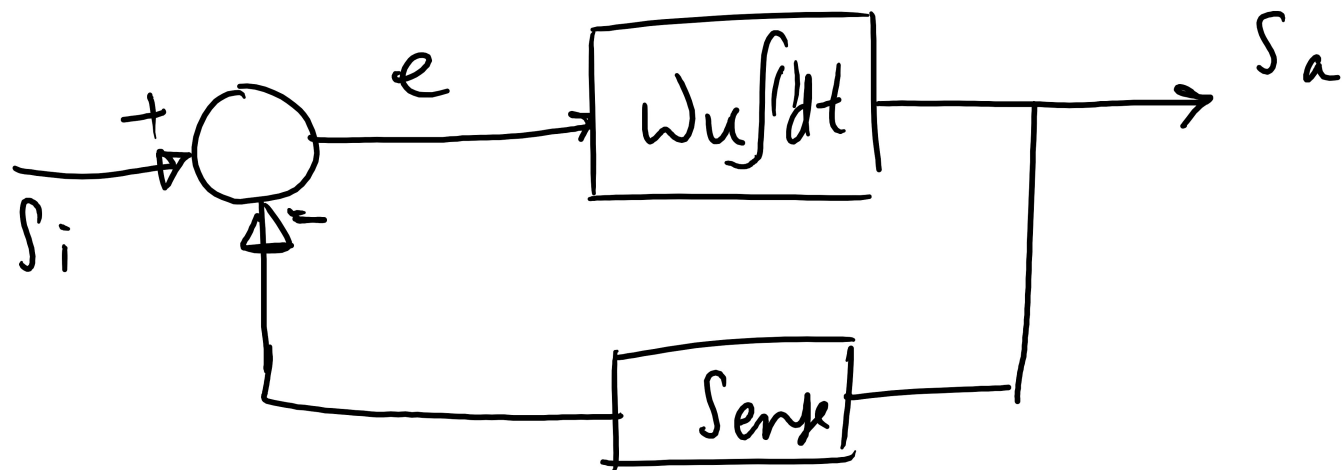

In steady state

$$V_a = V_i$$


$$\{V_e = 0\}$$

Amplifier




$$V_a = k V_i$$



$$V_i = \frac{V_a}{k}$$

Compare

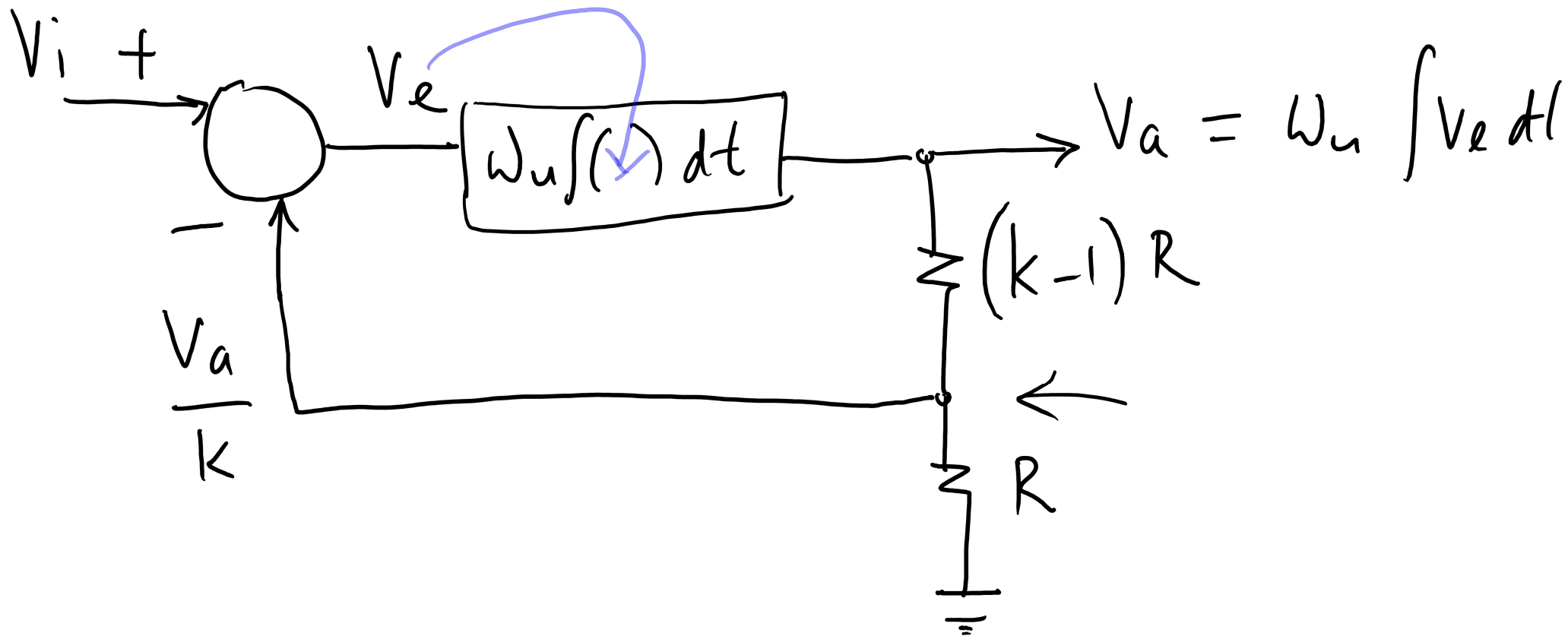
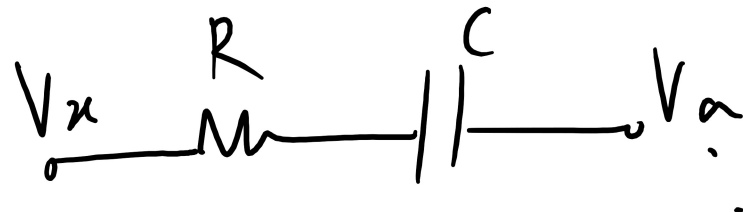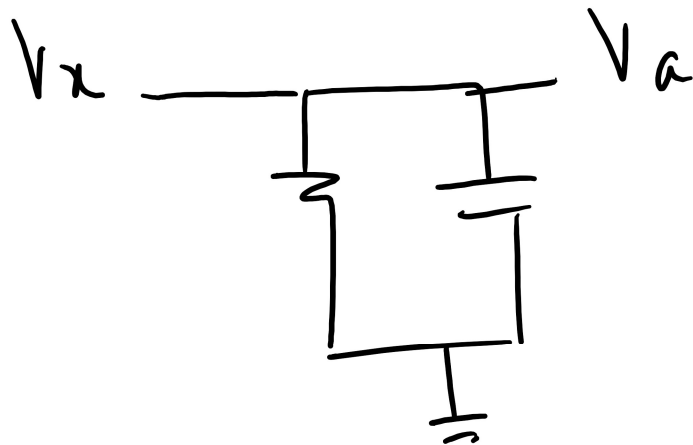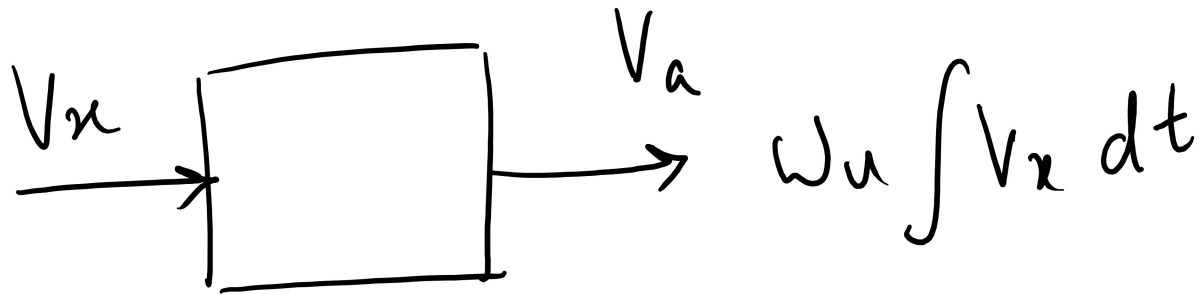
$$\frac{1}{Wu} \frac{dV_a}{dt} + \frac{V_a}{K} = V_i \quad \leftarrow \text{Solution} \\ \text{— HW} \\ \text{(exponential)}$$



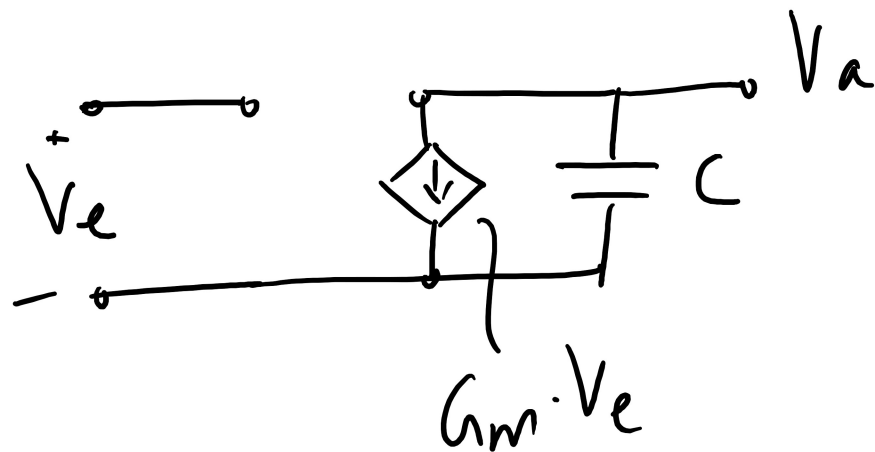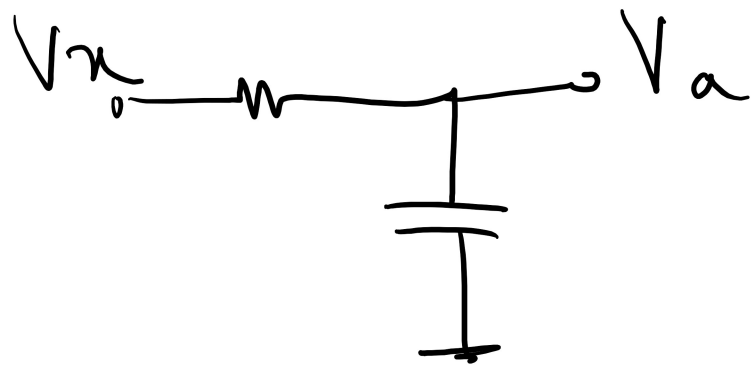

$$i_c = C \frac{dV_c}{dt}$$

$$G_m \cdot V_e = C \frac{dV_a}{dt}$$

$$V_a = \frac{G_m}{C} \int V_e dt$$

Wu

