



22/2/19

Lec 20

$$p_1 \ll p_2 \Rightarrow \text{large PM}$$



$$\underbrace{\quad}_{LH} \quad A(\lambda) \cdot \frac{1}{K}$$

$$\rightarrow \rightarrow CLH$$

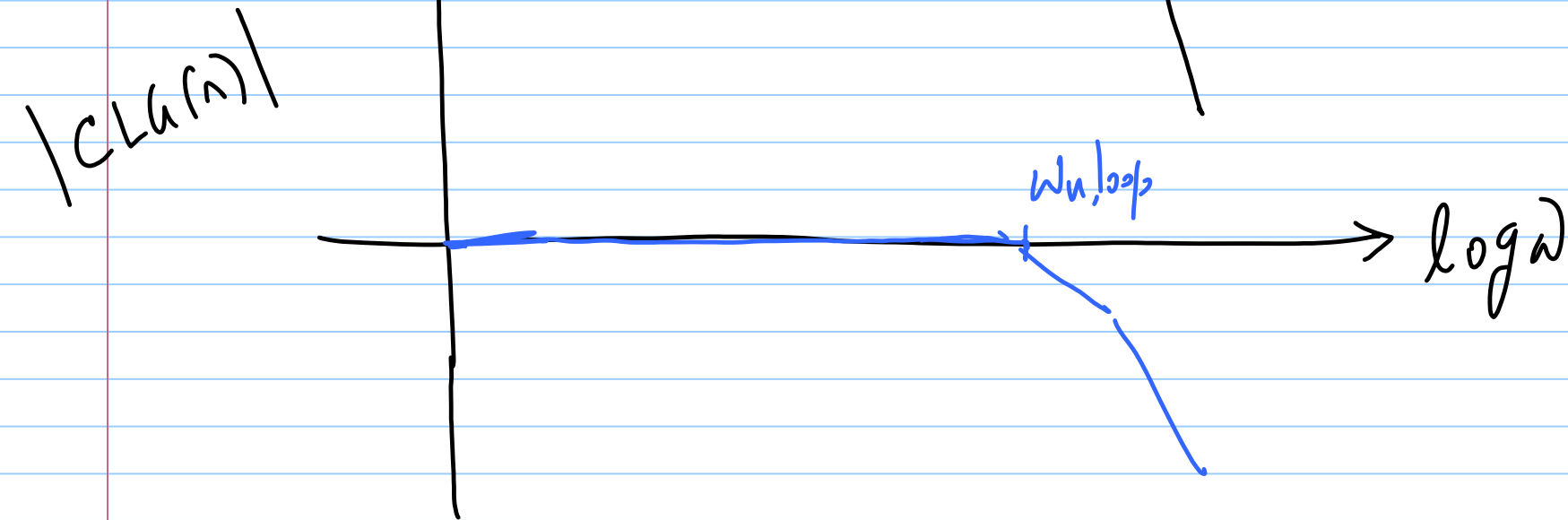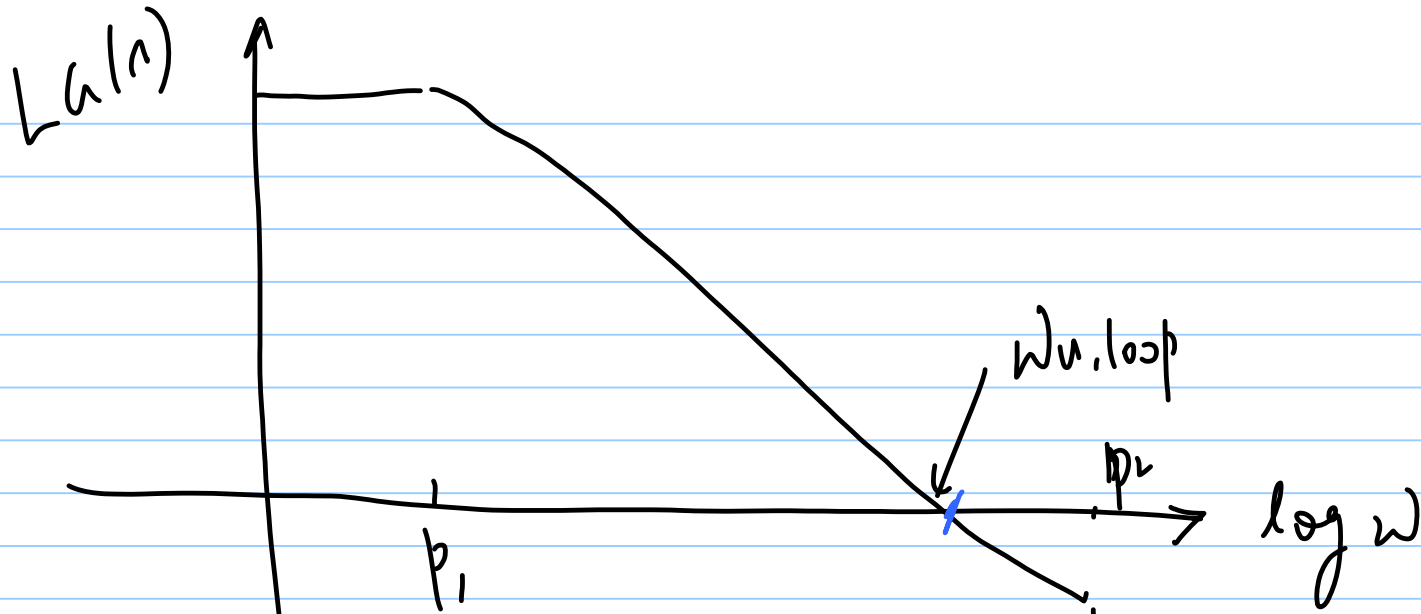

e.g. buffer
 $\frac{V_o}{V_i} = 1$

"Nyquist Plot"

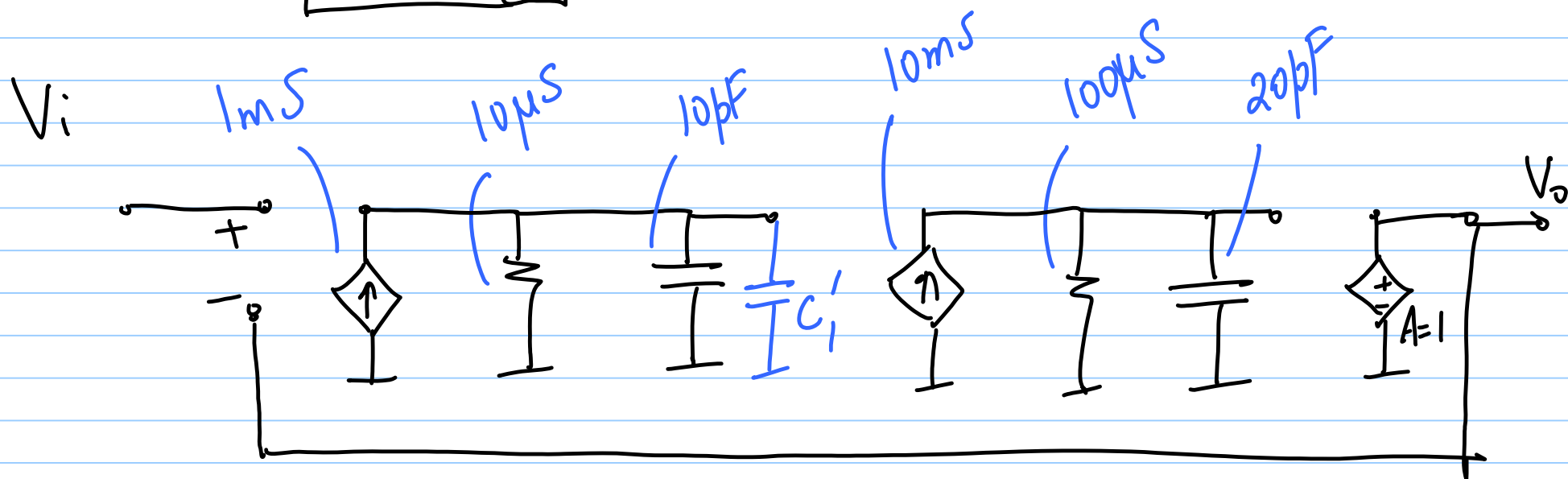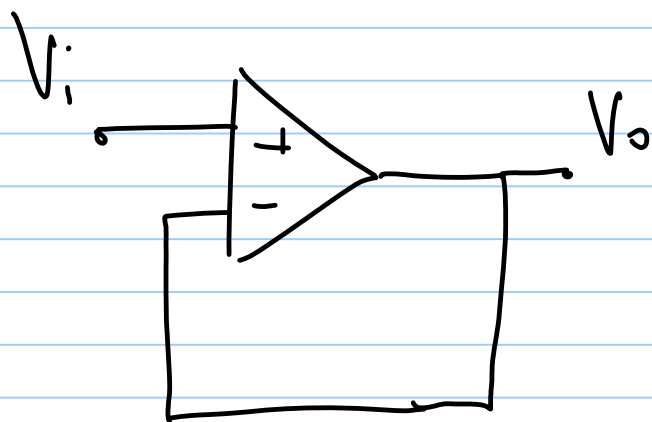


$$A_0 = 100 \times 100 = 10^4$$

$$k = 1 \quad \{ \beta = 1 \}$$

$$p_1 = \frac{G_{01}}{C_1} = \frac{10 \mu S}{10 pF} = 10^6 \text{ rad/s} \leftrightarrow 160 \text{ kHz}$$

$$p_2 = \frac{G_{02}}{C_2} = \frac{100 \mu S}{20 pF} = 5 \times 10^6 \text{ rad/s} \leftrightarrow 800 \text{ kHz}$$
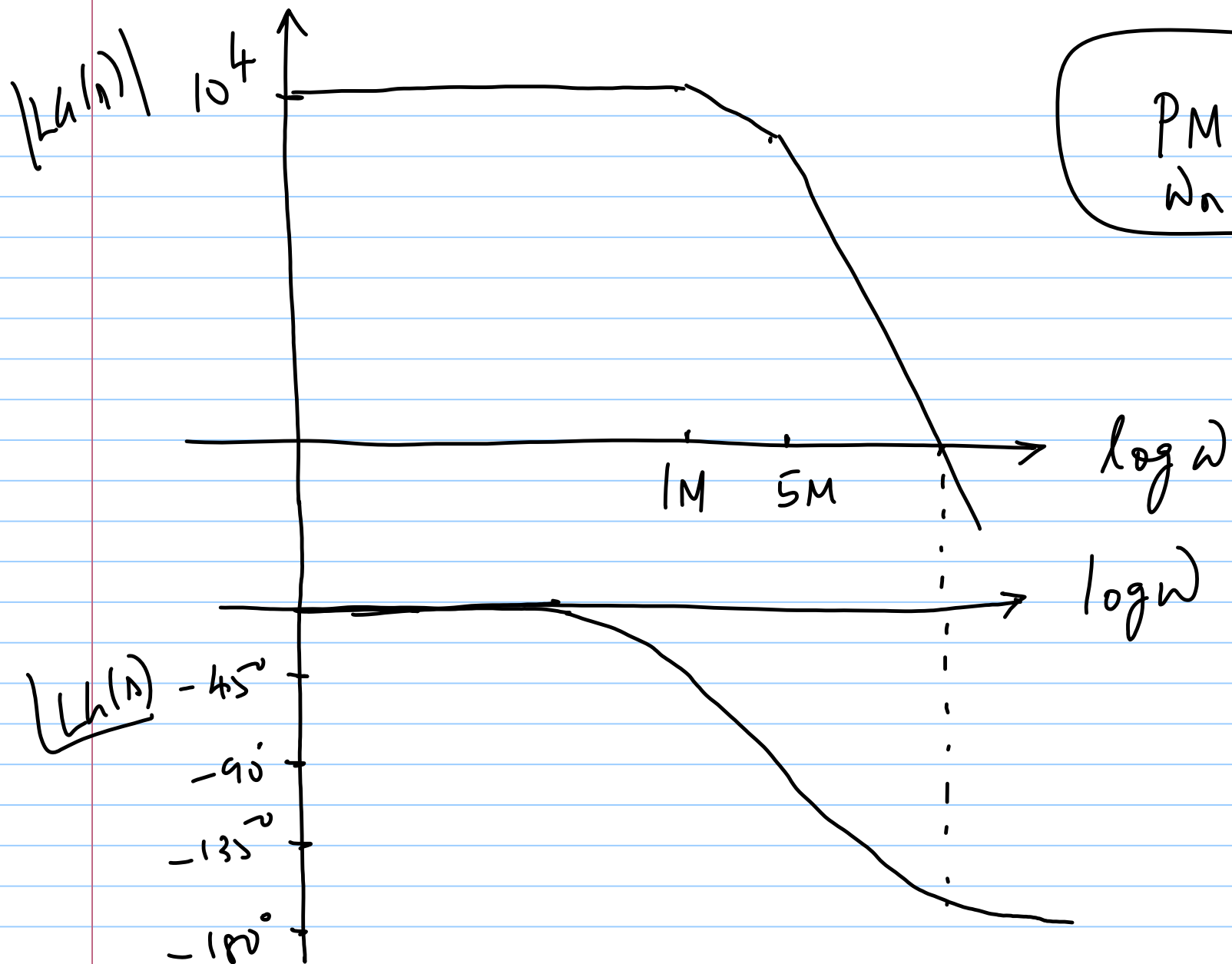
$$\begin{aligned} \zeta &= \frac{1}{2} \left(\sqrt{\frac{p_1}{p_2}} + \sqrt{\frac{p_2}{p_1}} \right) \cdot \sqrt{\frac{k}{A_0 + k}} = \frac{1}{2} \left(\sqrt{\frac{1}{5}} + \sqrt{5} \right) \cdot \sqrt{\frac{1}{10^4}} \\ &= 0.013 \end{aligned}$$



$$\omega_n = \sqrt{\frac{A_0}{k} + 1} \sqrt{p_1 p_2}$$

$$= 100 \sqrt{p_1 p_2}$$

e.g. 1) $p_1 = \frac{1}{100} \cdot p_2 \Rightarrow \omega_n = 10 \cdot p_2 = 50 \text{ M rad/s}$
 poles @ $500 \text{ k rad/s}, 50 \text{ M rad/s}; \omega_{u, \text{loop}} = 10^4 \cdot 500 \text{ k}$

2) $p_2 = \frac{1}{100} p_1 \Rightarrow \omega_n = 10 p_1 = 10 \text{ M rad/s}$

poles @ $100 \text{ k rad/s}, 10 \text{ M rad/s}; \omega_{u, \text{loop}} = 10^4 \cdot 100 \text{ k}$

* clearly p_1 should be decreased.

* by how much?

e.g. $\zeta = 1$, $PM = 76^\circ$

$$\frac{p_2}{\omega_{u,loop}} = 4 \Rightarrow \omega_{u,loop} = 1.25 \text{ Mrad/s}$$

$$\omega_{u,loop} = p_1' \cdot \frac{A_0}{K}$$

$$p_1' = \frac{1.25 \text{ Mrad/s}}{10^4} = 125 \text{ rad/s}$$

$C_{tot.}$ for p_1' :

$$\frac{G_{01}}{C_{tot.}} = p_1'$$

$$C_{tot.} = \frac{10 \mu s}{125} = 80 nF$$

$$C_1' = C_{tot.} - C_1$$