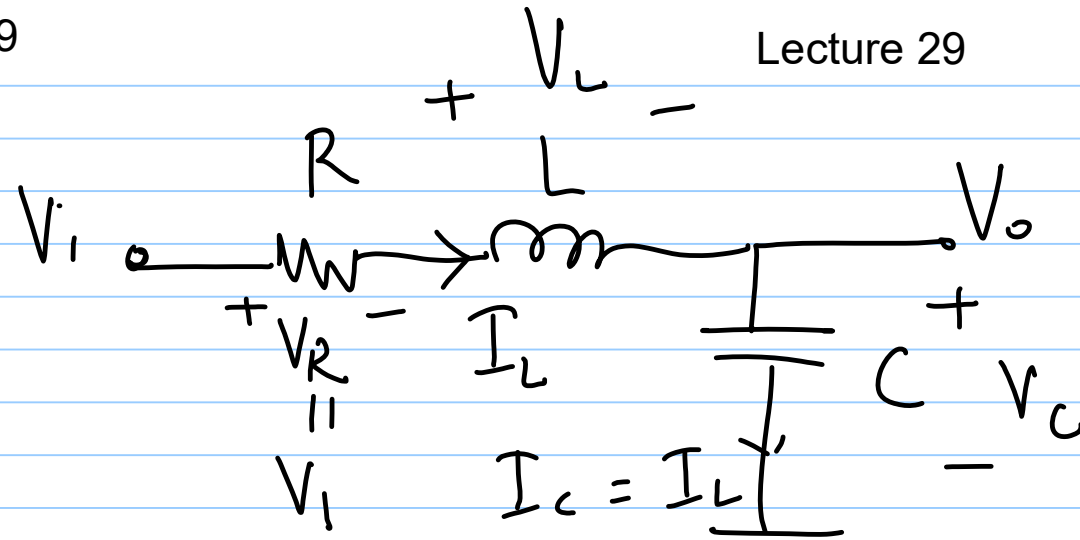


19/03/2019

Lecture 29




L-match network
"State Variable"
Filter

* Integrator is the basic building block

$$\frac{V_o(s)}{V_i(s)} = \frac{1/sC}{R + sL + 1/sC} = \frac{1}{1 + sCR + s^2LC}$$
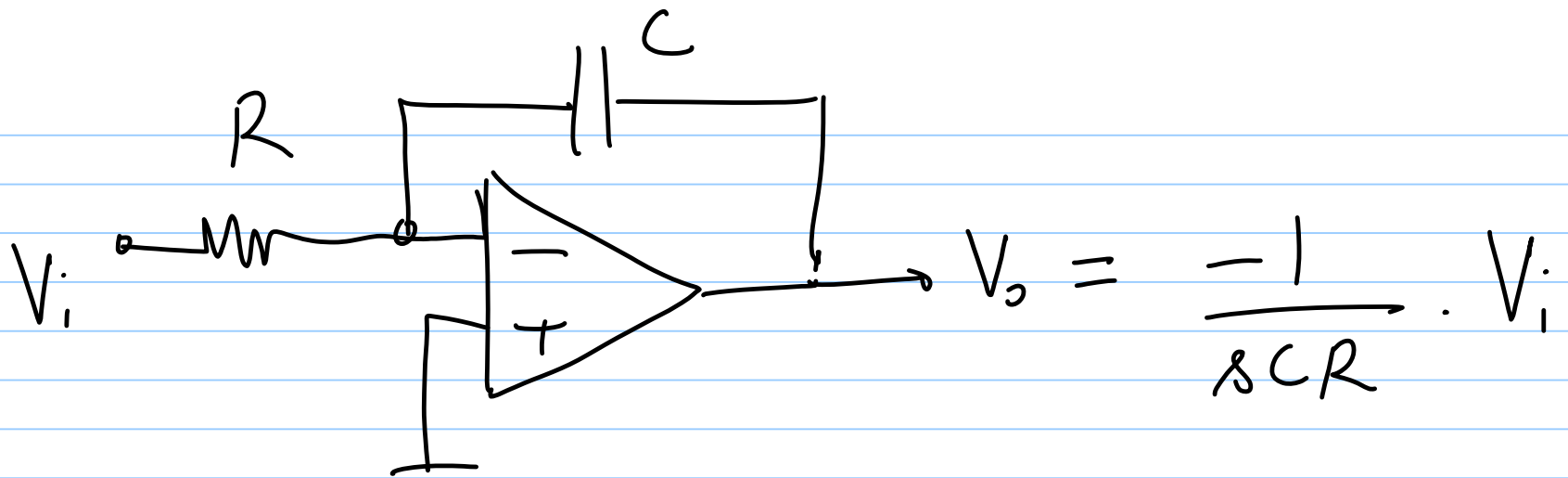
$$\text{Integrator} = \frac{(\quad)}{s(\quad)}$$



$$I_c = C \frac{dV_c}{dt}$$

$$I_c(s) = sC V_c(s)$$

$$R \cdot I_L(s) = sCR V_c(s)$$

$$V_i(s) = sCR V_c(s)$$

$$V_c(s) = \frac{V_i(s)}{sCR}$$

— (1)

$$V_L = L \frac{dI_L}{dt}$$

$$V_L(s) = sL I_L(s)$$



$$I_L(s) = \frac{V_L(s)}{sL}$$


$$V_i = V_R + V_L + V_C$$

$$V_i(s) = I_L(s)R + V_L(s) + V_C(s)$$

$$V_1(s) = R \cdot I_L(s) = \frac{V_i(s) - R I_L(s) - V_C(s)}{sL/R}$$

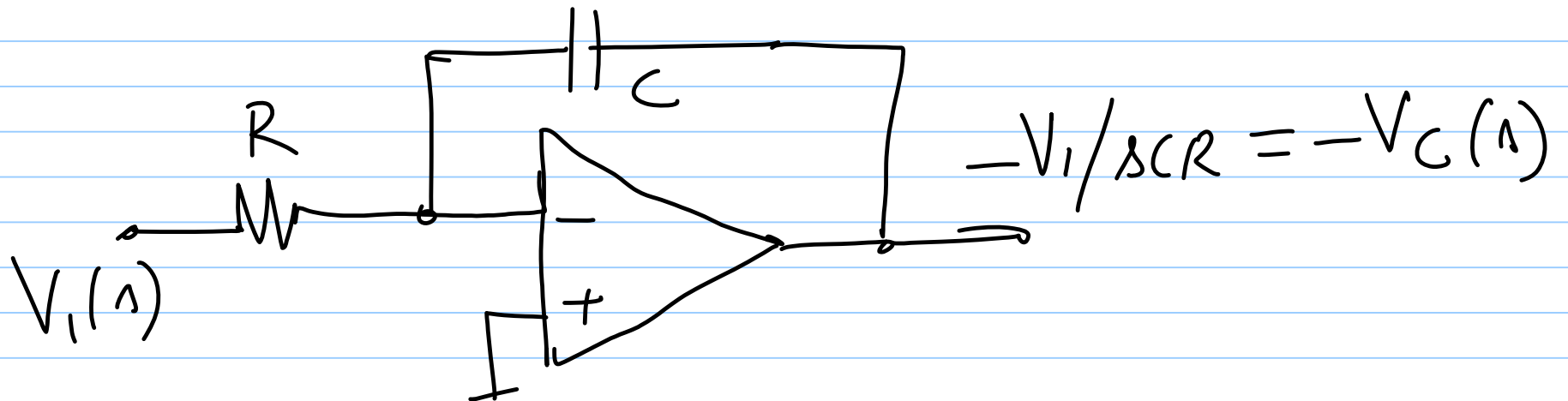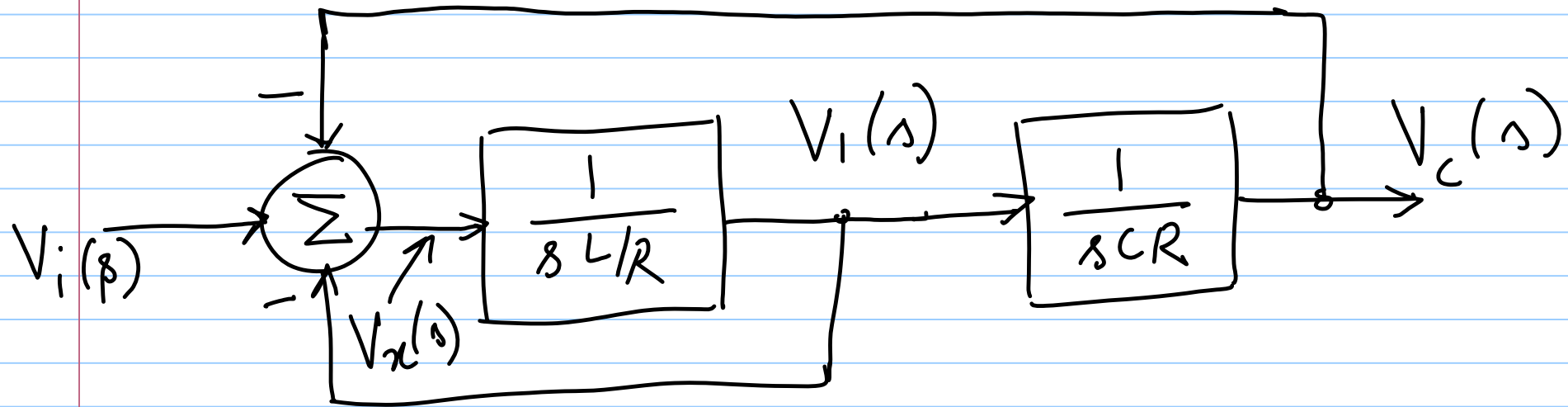
$$V_1(s) = \frac{V_i(s) - V_1(s) - V_C(s)}{sL/R} \quad \text{--- (2)}$$



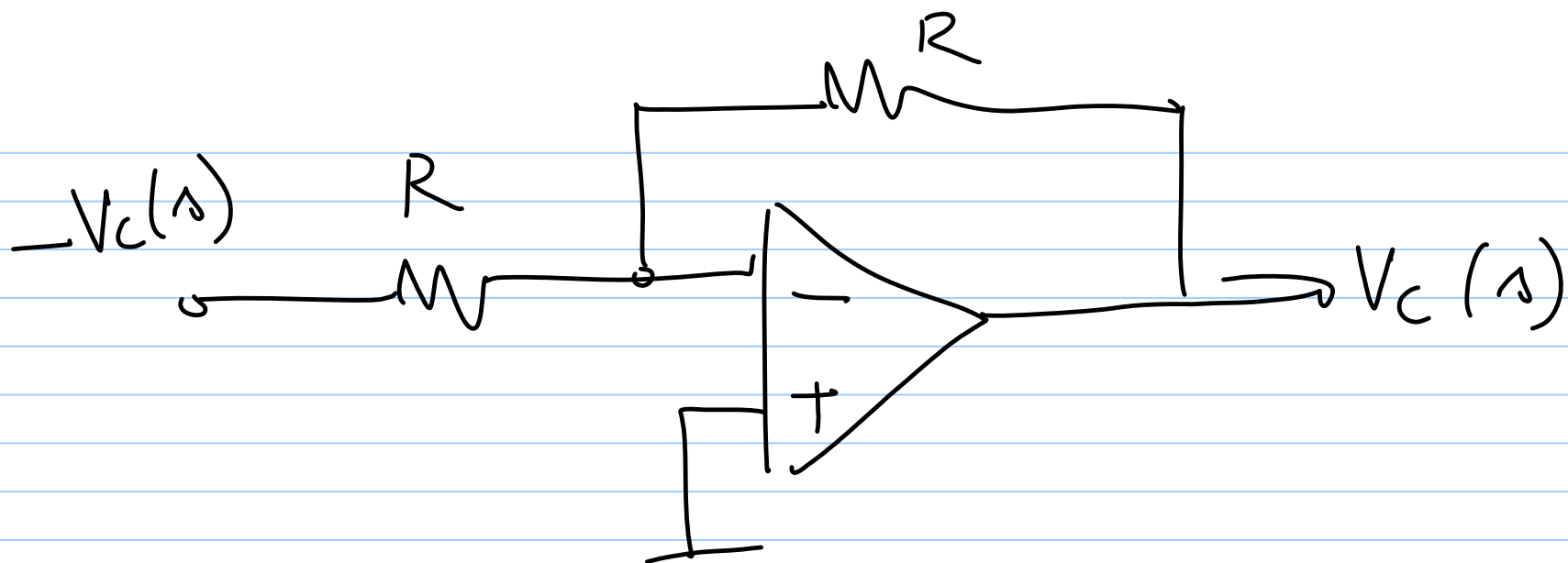


|||




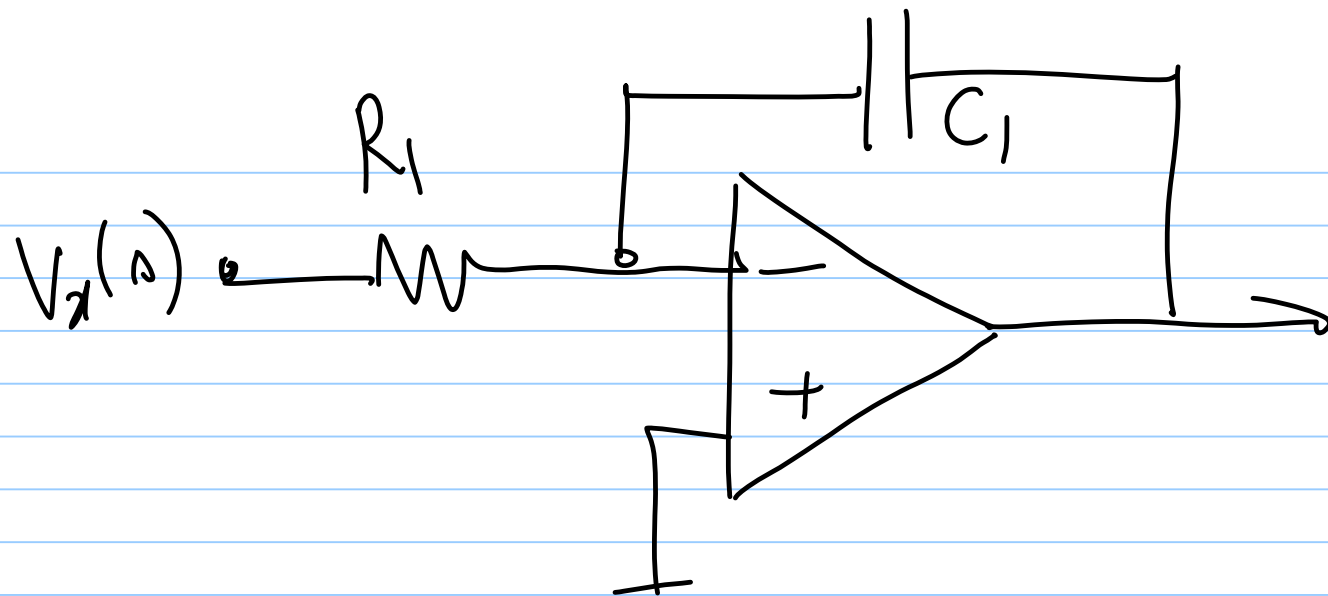


$$\frac{-V_x(s)}{sC_1R_1} = -V_1(s)$$

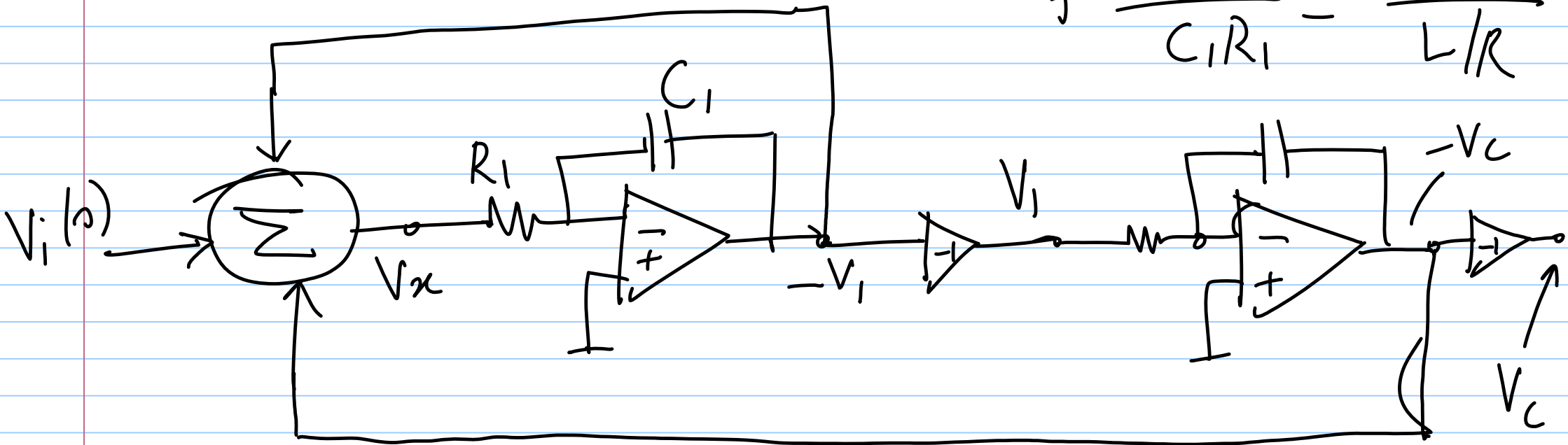
$$\text{if } \frac{1}{C_1R_1} = \frac{1}{L/R}$$



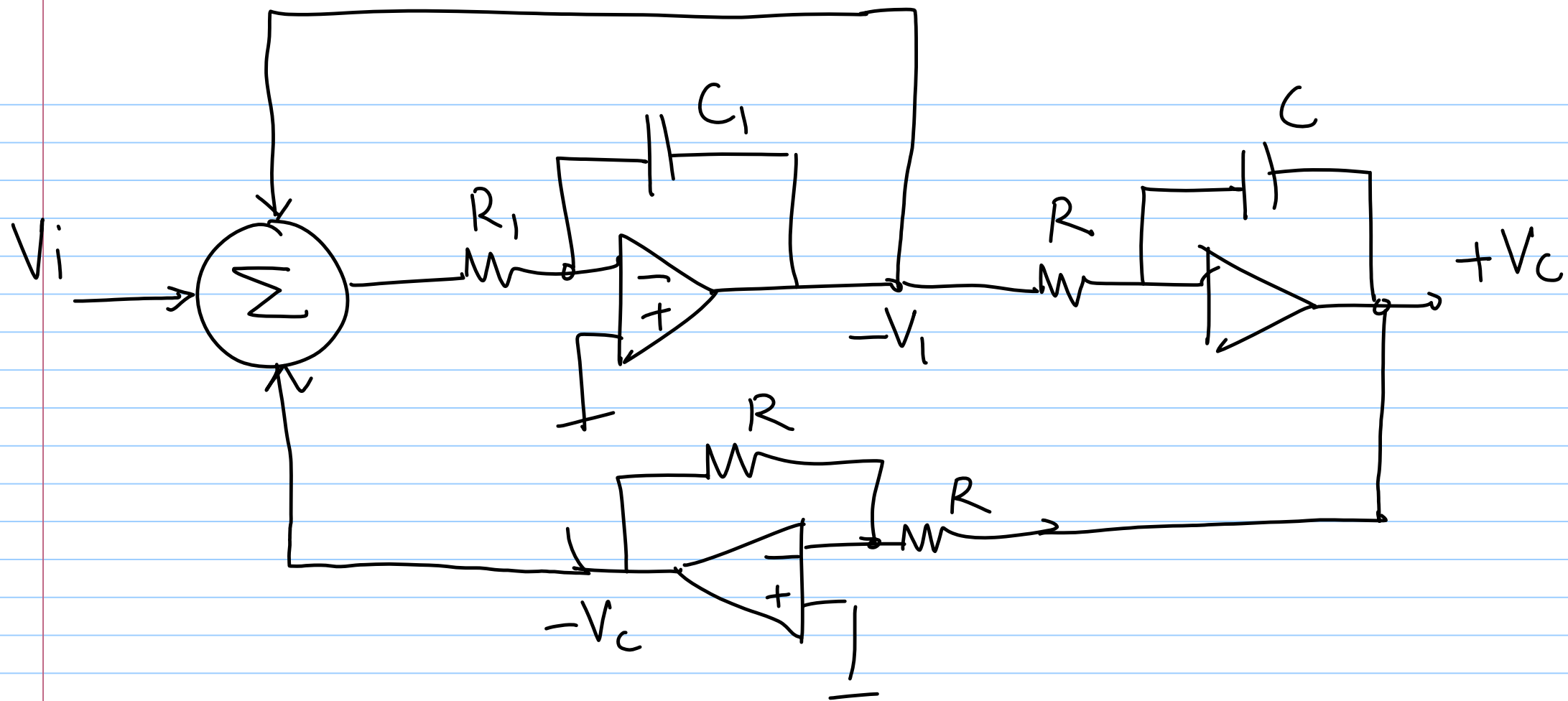

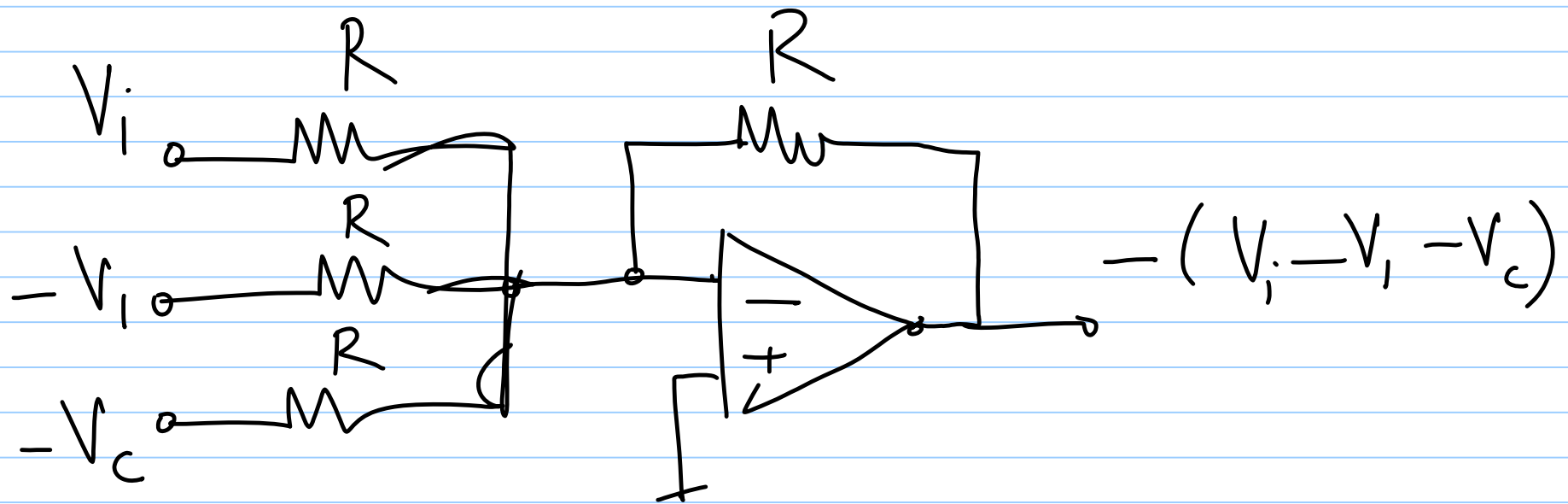

"Tow-Thomas" Biquadratic Filter

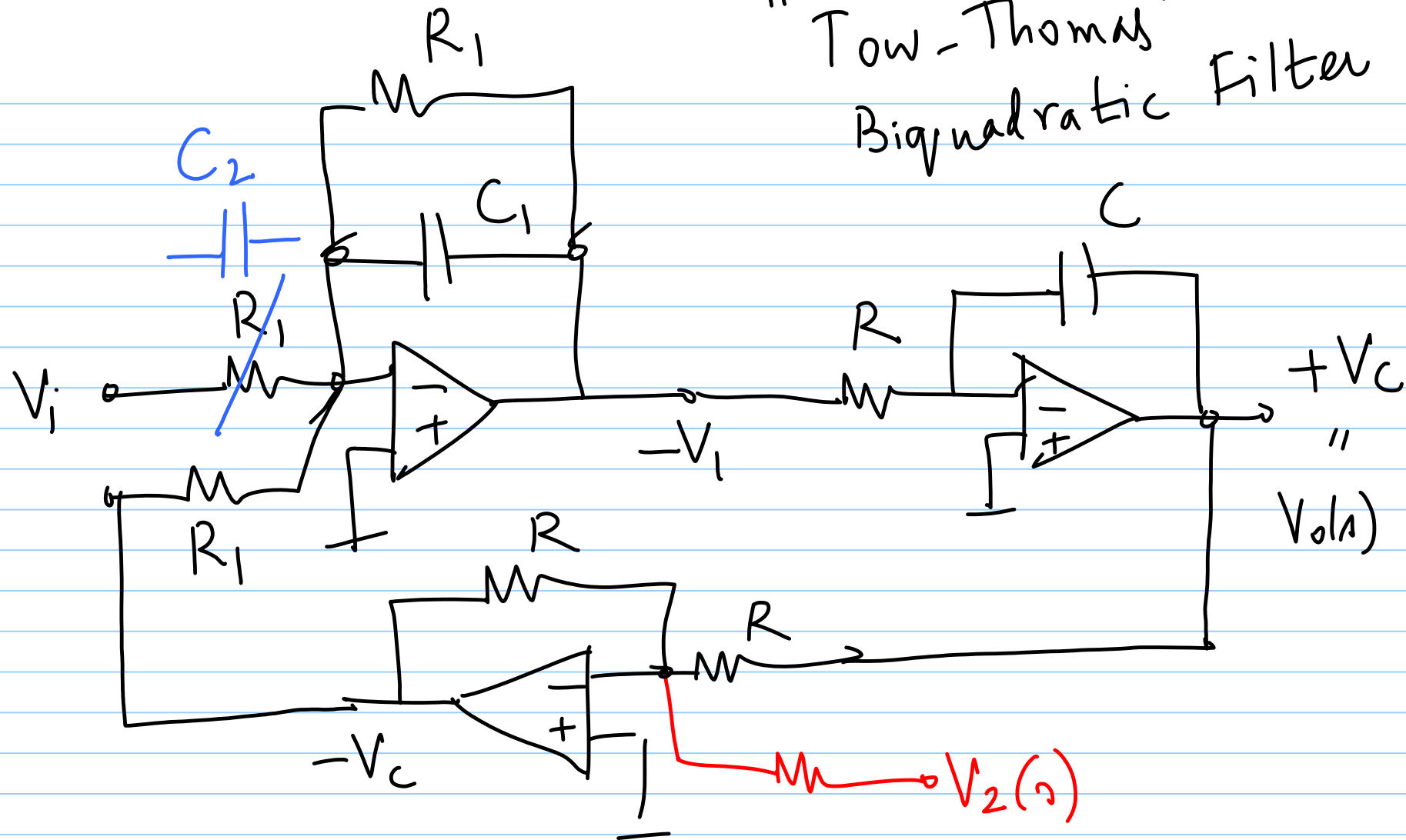

$$-V_1 = \frac{-V_i(s) + V_1(s) + V_c(s)}{sC_1R_1}$$

$$-V_1 = \frac{-1}{sC_1R_1} [V_i(s) - V_1(s) - V_c(s)]$$

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + sCR + s^2LCRC_1R_1}$$

$$V_c(s) = \frac{V_i(s)}{sCR}$$

$$\frac{V_i(s)}{V_i(s)} = sCR \cdot \frac{V_c(s)}{V_i(s)}$$

$$= \frac{sCR}{1 + sCR + sC_1R_1CR}$$

1 1

