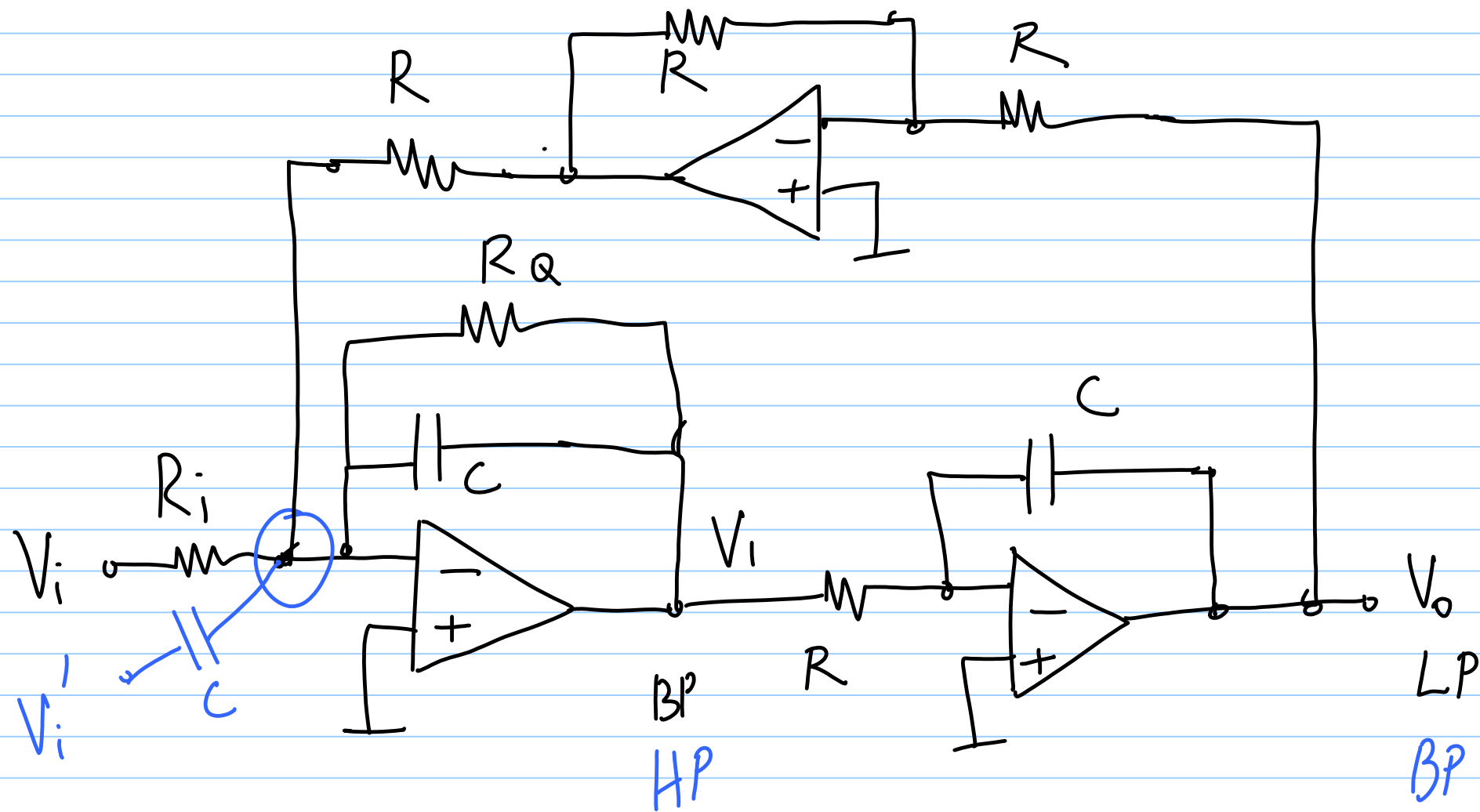


20/03/2019

Lecture 30



$$\frac{V_o(s)}{V_i(s)} = \frac{\left(R/R_i \right)}{1 + sCR \left(\frac{R}{R_Q} \right) + s^2 C^2 R^2}$$

DC gain
 R_i changes
 DC gain


$$1 + \frac{s}{\omega_n \cdot Q} + \frac{s^2}{\omega_n^2}$$

$\frac{R_Q}{R}$ changes

$$s^2 + 2\zeta \omega_n s + \omega_n^2$$


$$\omega_n = \frac{1}{RC}$$

$$2\zeta = \frac{1}{Q}$$

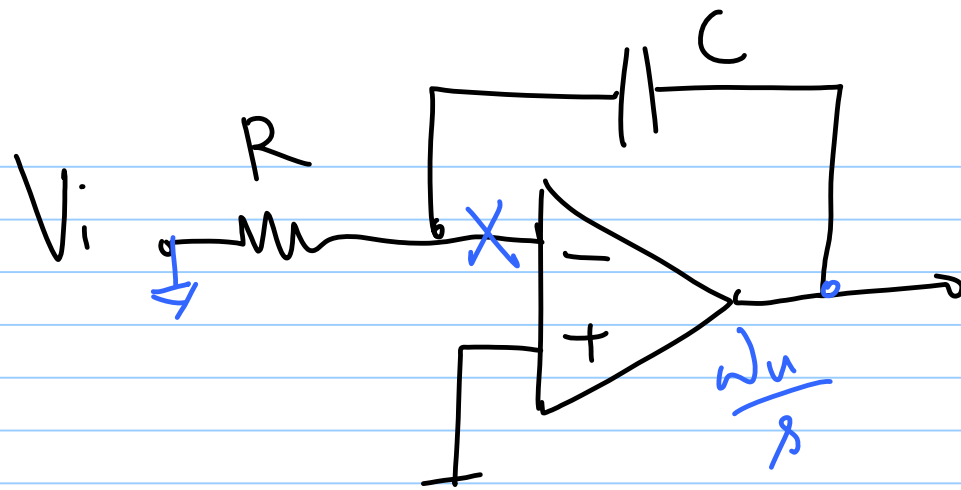

$$V_o = - \frac{V_i}{sCR} \quad \text{Integrator}$$

$$\beta = \frac{sCR}{1 + sCR}$$


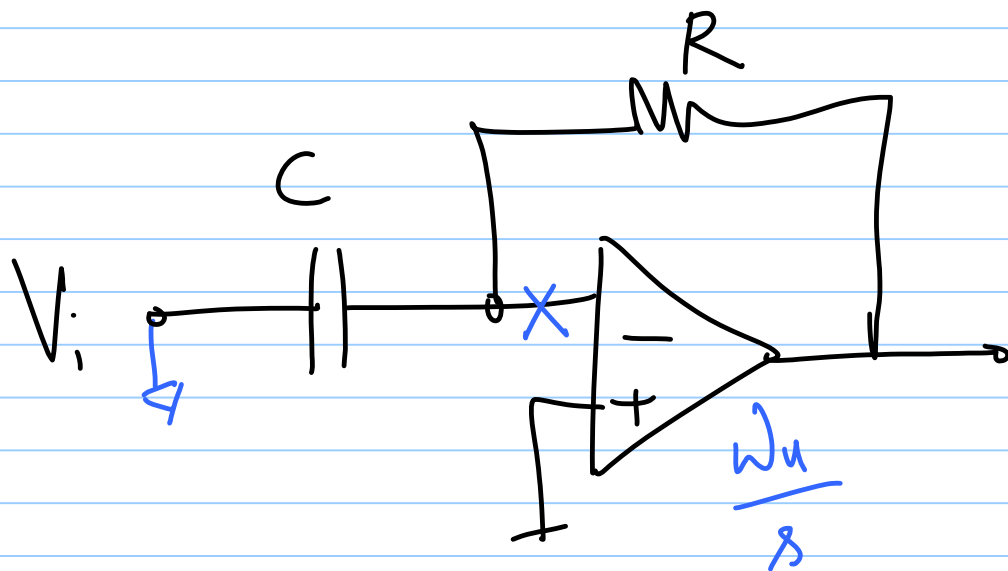


$$V_o = -sCR \cdot V_i$$

Differentiator

$$w_u \gg 1/RC$$

$$\beta = \frac{1}{1 + sCR}$$

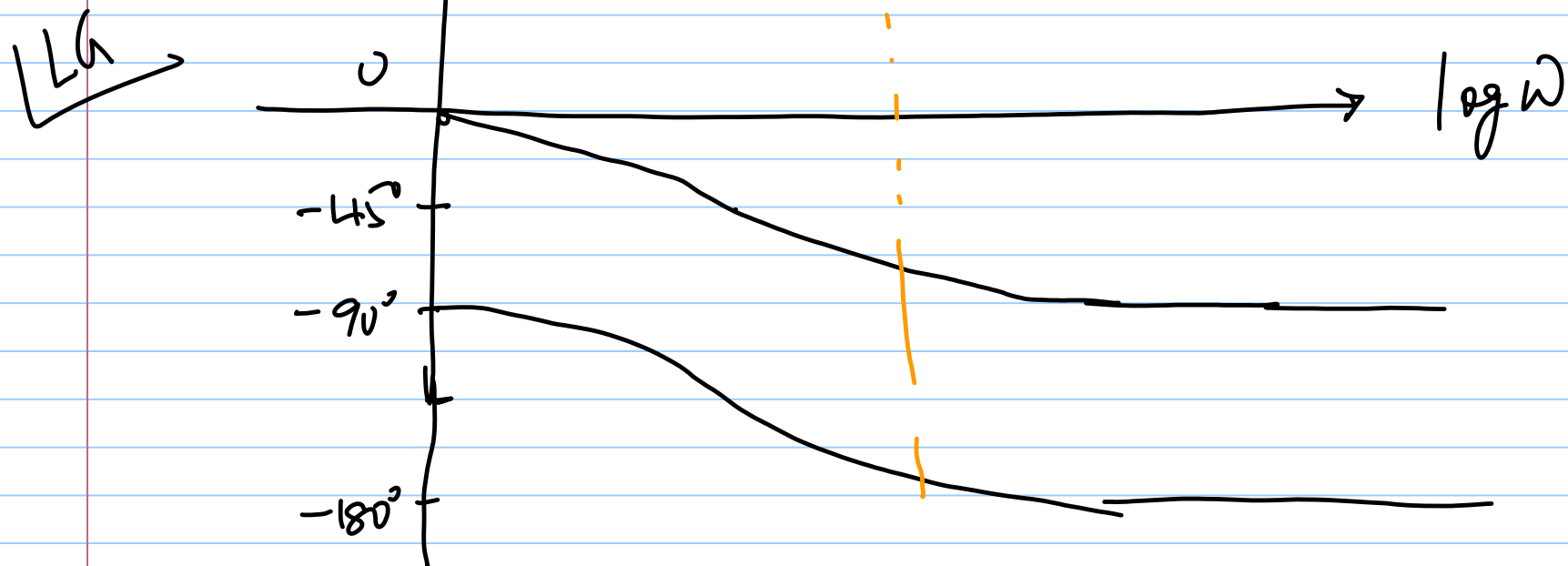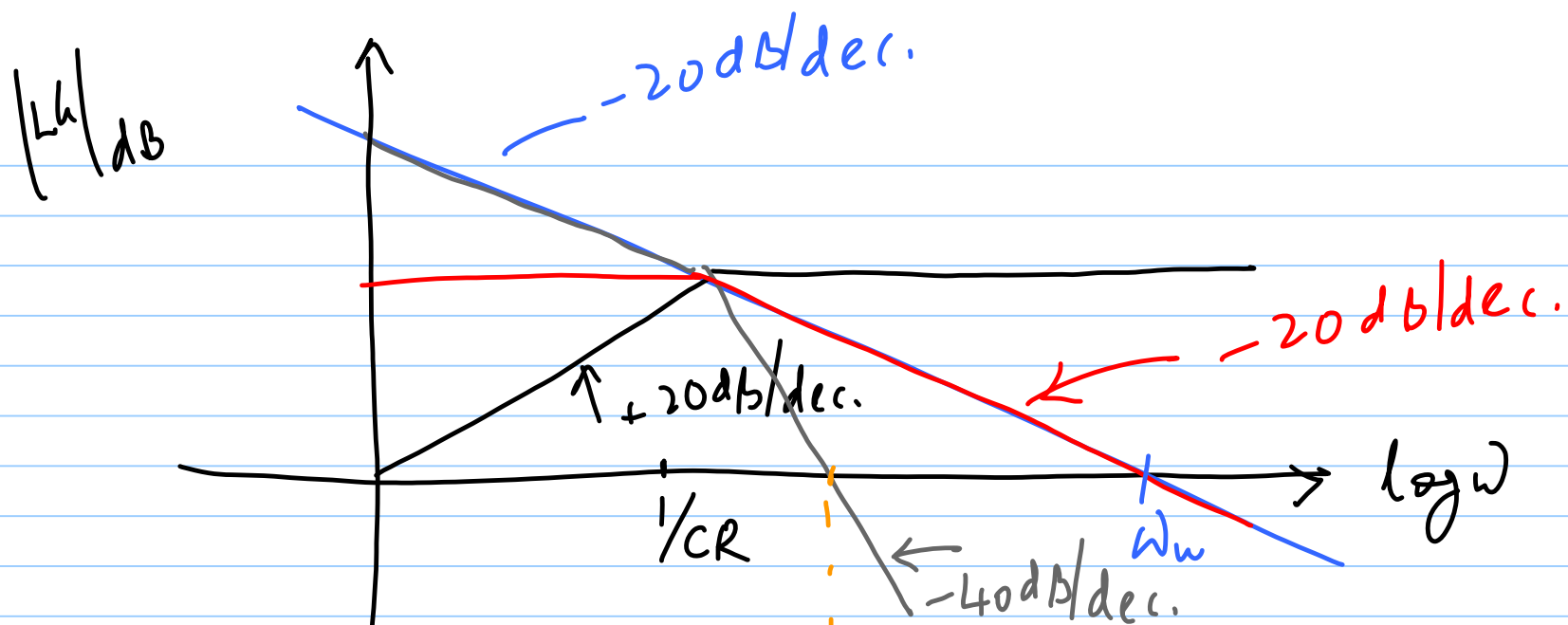

Integrative


$$L_G(s) = - \frac{sCR}{1+sCR} \cdot \frac{W_u}{s}$$

$$= - \frac{W_u CR}{1+sCR}$$

$$|L_G(j\omega)| = \frac{W_u CR}{\sqrt{1+\omega^2 C^2 R^2}}$$

Differentiator
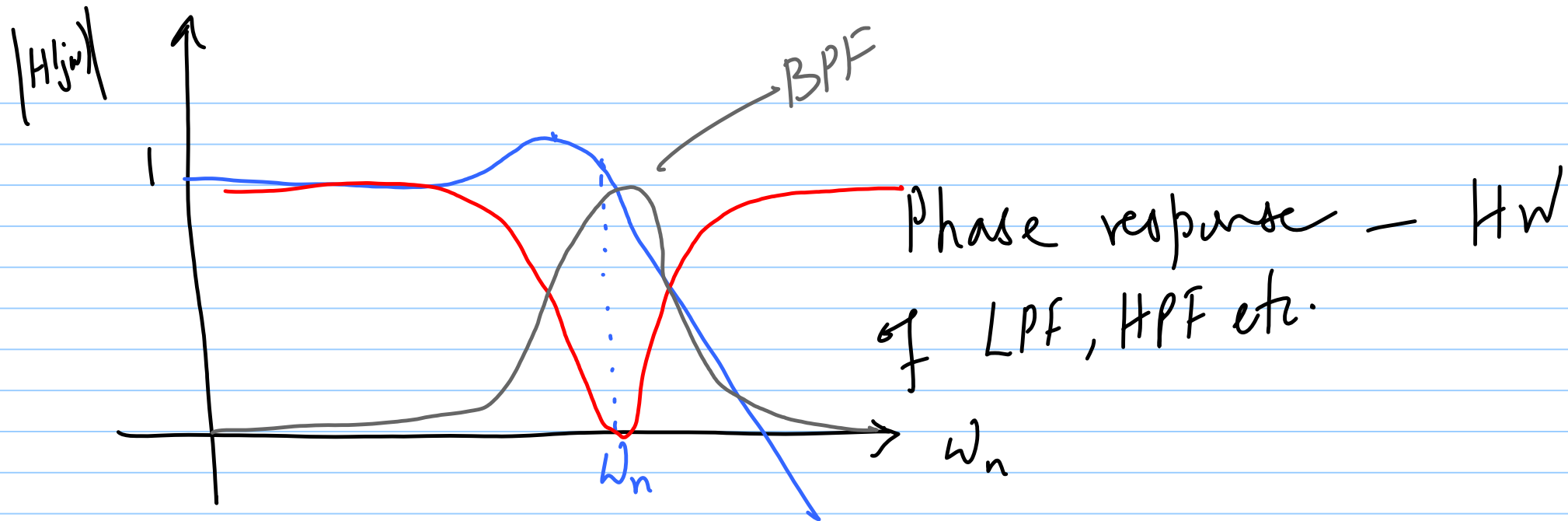
$$L_G(s) = -\frac{w_u}{s} \cdot \frac{1}{1 + sCR}$$



$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{1 + sCR + s^2 LCR C_1 R_1} \quad \text{LPF}$$

$$\text{HPF : } H_2(s) = \frac{s^2/\omega_n^2}{1 + \frac{s}{\omega_n Q} + \frac{s^2}{\omega_n^2}}$$

$$\text{BPF : } H_3(s) = \frac{s/\omega_n}{1 + \frac{s}{\omega_n Q} + \frac{s^2}{\omega_n^2}}$$

Notch Filter
or Band stop filter

$$H_4(s) = \frac{(?)}{(?)} \quad \text{Hw}$$