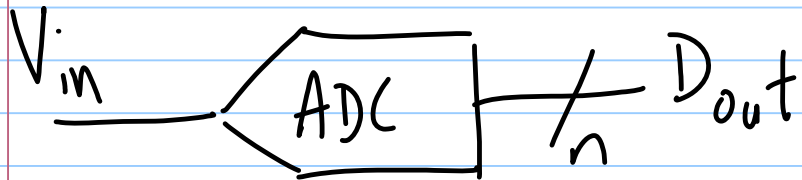


12/04/2019

Lecture 39

ADCs



$$D_{out} = k \quad \text{if}$$

$$\frac{V_{ref}}{2^n} \cdot k < V_{in} \leq \frac{V_{ref}}{2^n} (k+1)$$

n : # of bits


DACs




$$V_{out} = D_{in} \cdot \underbrace{\frac{V_{ref}}{2^n}}_{LSB}$$

DACs



Resistor String

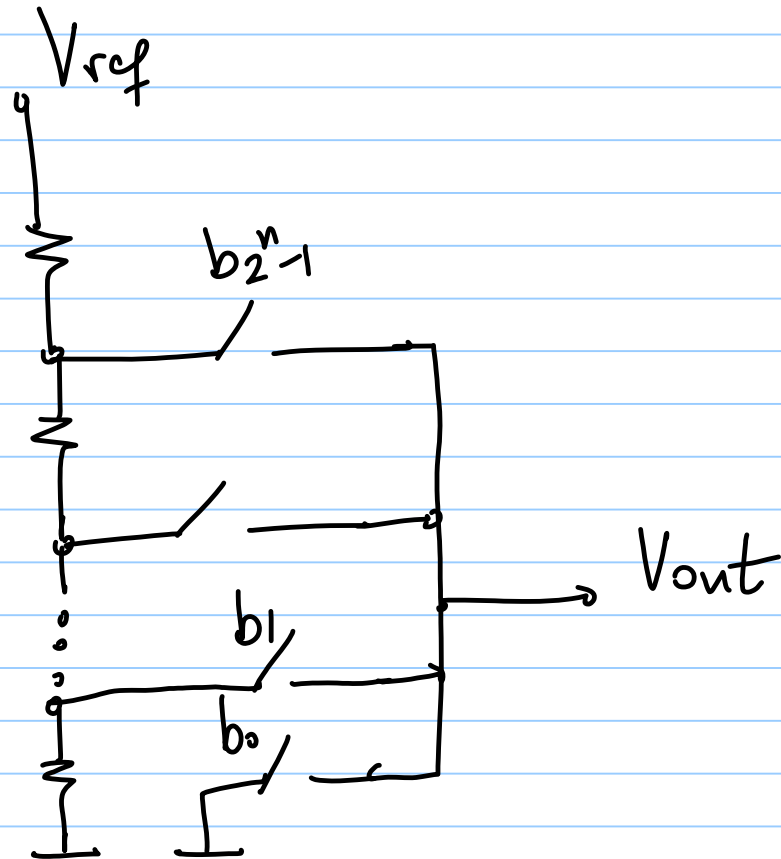


Binary weighted DAC

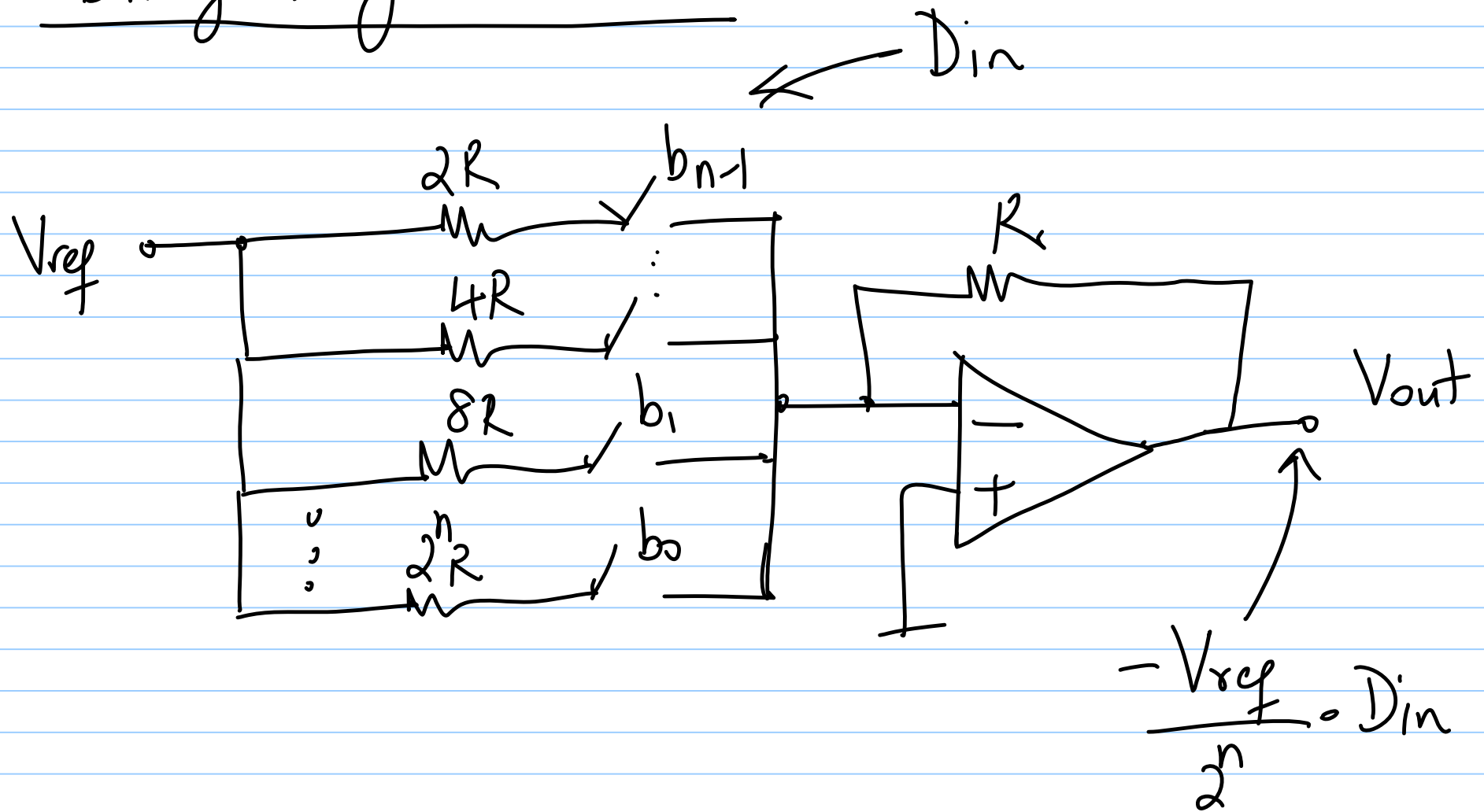

R-2R Ladder DAC

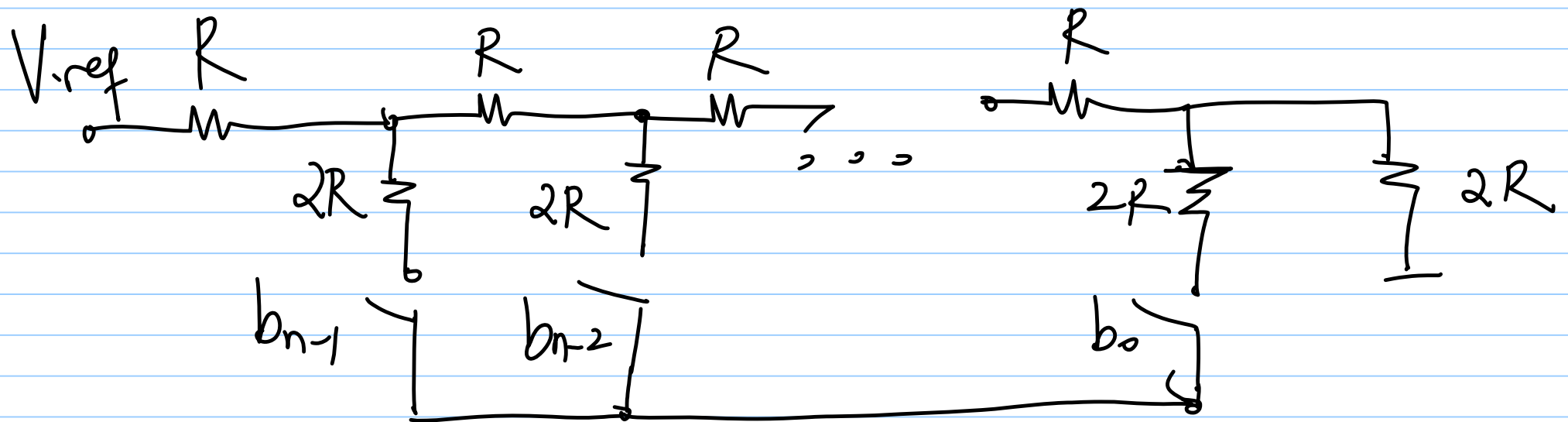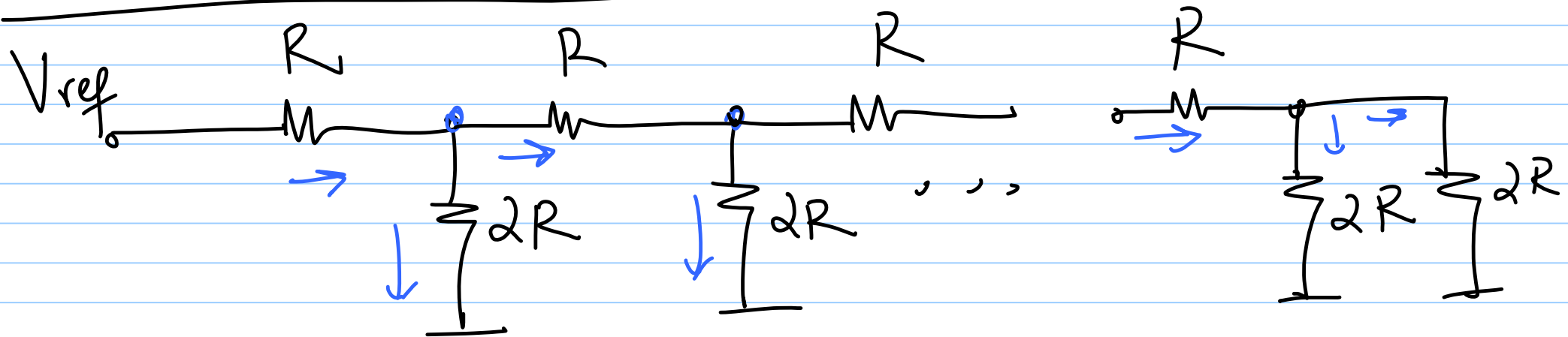

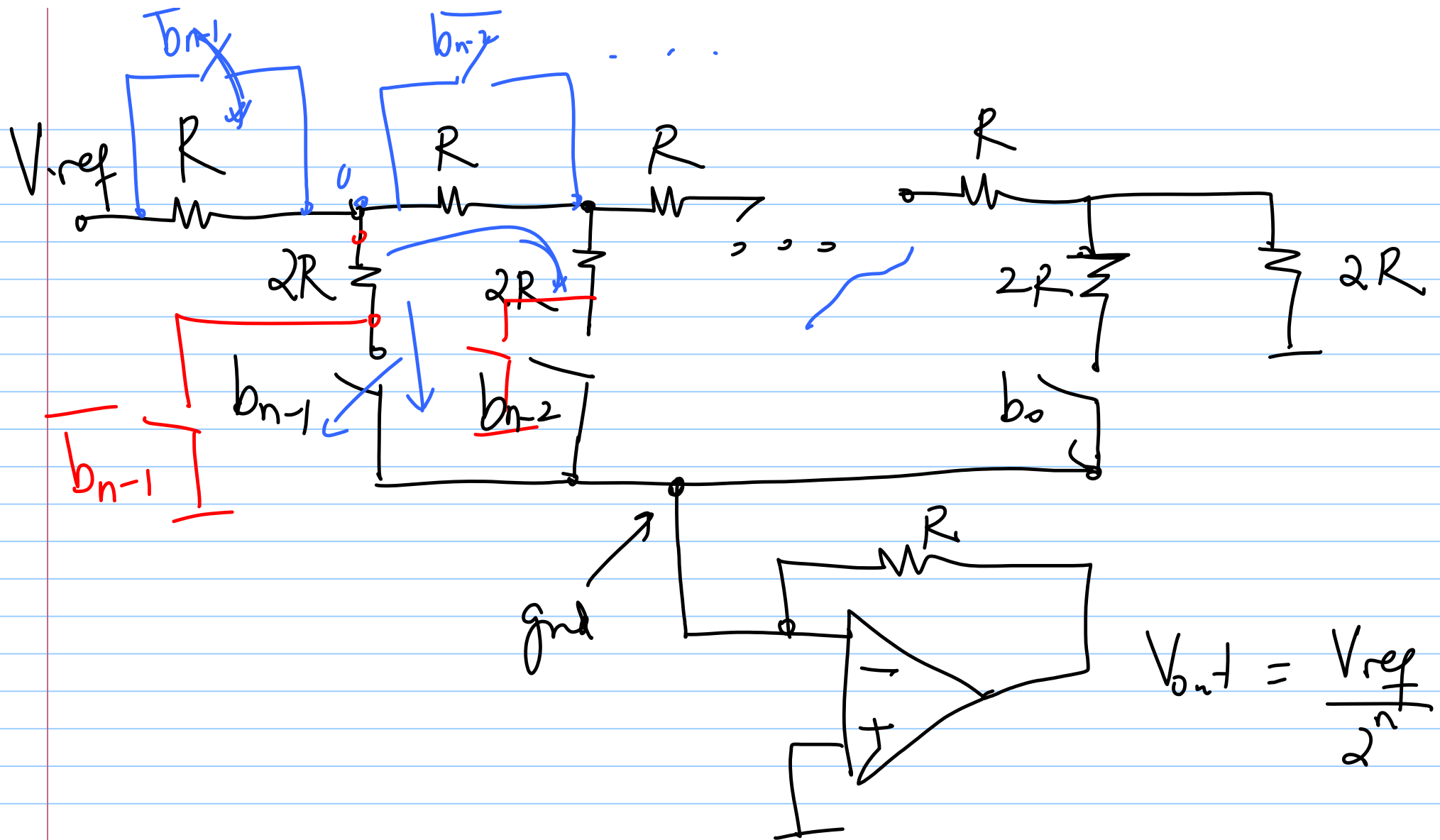

$$V_{out} = \frac{V_{ref}}{2^n} \cdot D_{in}$$