
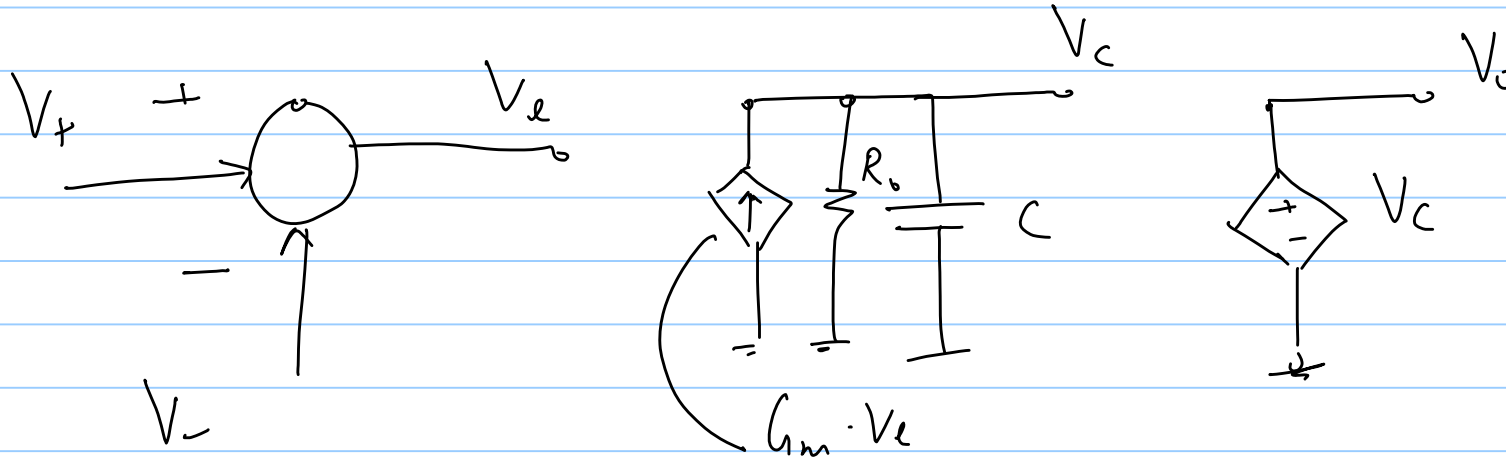


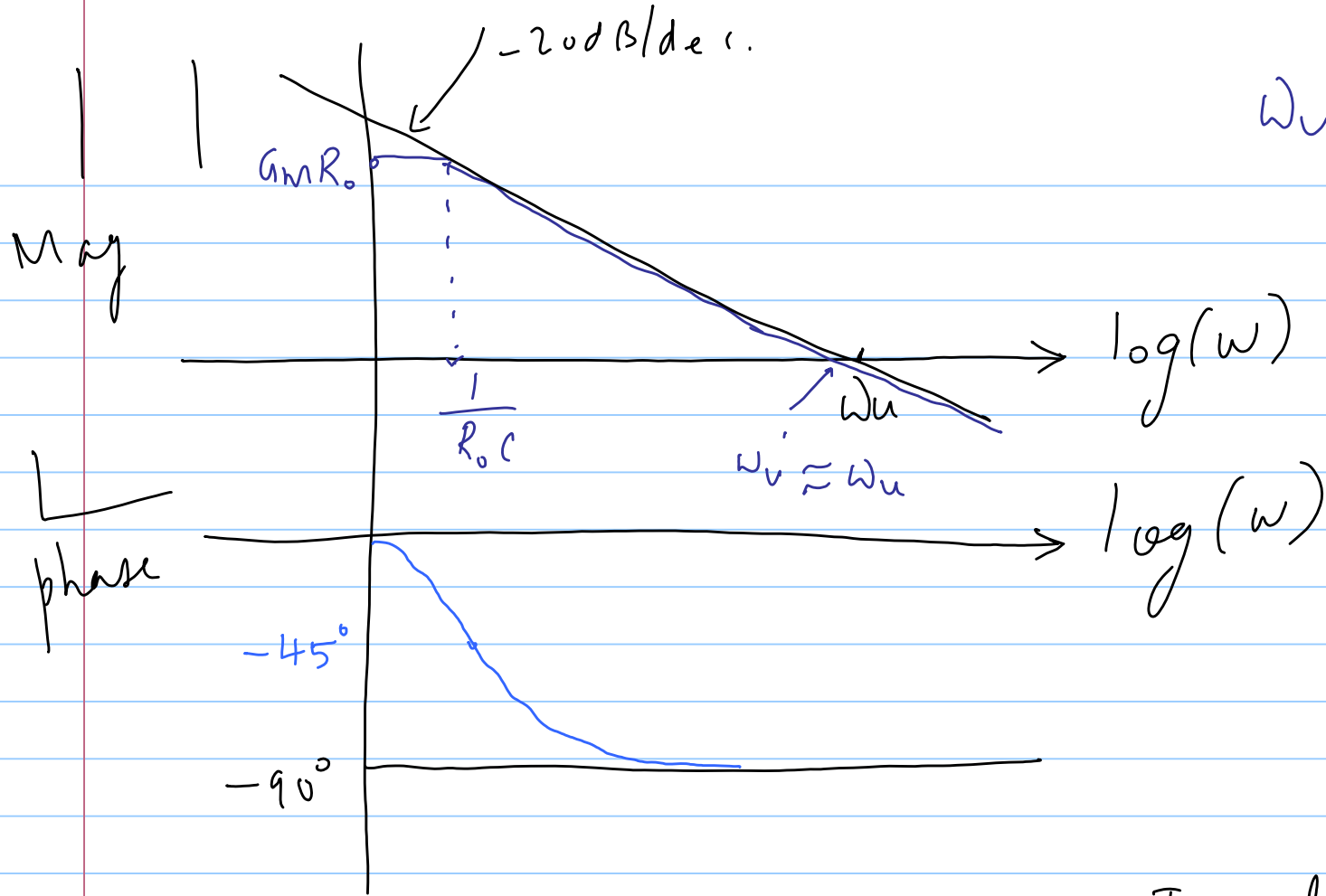


$$\frac{V_o}{V_+ - V_-}(s) = \frac{G_m R_o}{1 + s C R_o}$$

pole @ $-\frac{1}{R_o C}$



$\omega_u = \text{unity gain frequency}$

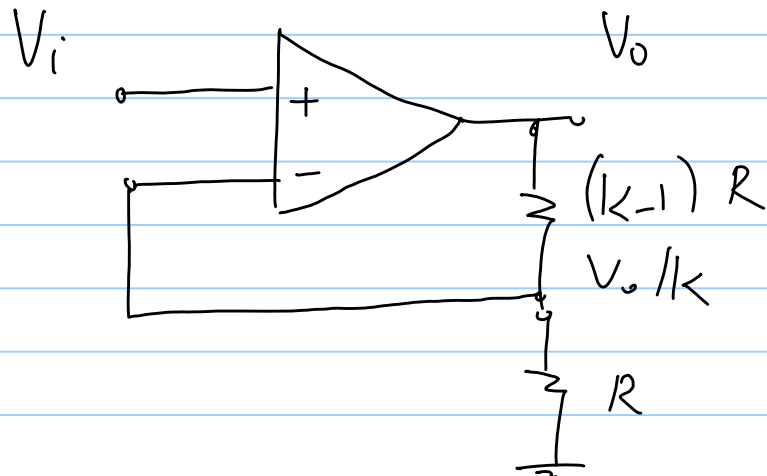

Ideal: $V_o = k V_i$

Non-ideal opamp

$$\text{Opamp } H(s) = \frac{G_m R_o}{1 + s C R_o}$$

$$\frac{V_o}{V_i}(s) = \frac{G_m R_o k}{k + G_m R_o + s C R_o k}$$

$$\frac{V_o}{V_i}(s) = \frac{G_m R_o k}{k + G_m R_o + s C R_o k} = k \cdot \left(\right)$$

$$= k \cdot \frac{G_m R_o}{k + G_m R_o + s C R_o k}$$

$$= k \cdot \frac{1}{1 + \frac{k}{G_m R_o} (1 + s C R_o)}$$


closed
loop
UGF

$$\omega_{ucl} =$$




$$H W \left(\begin{array}{l} s = j\omega \\ |H(j\omega)| = 1 \end{array} \right)$$
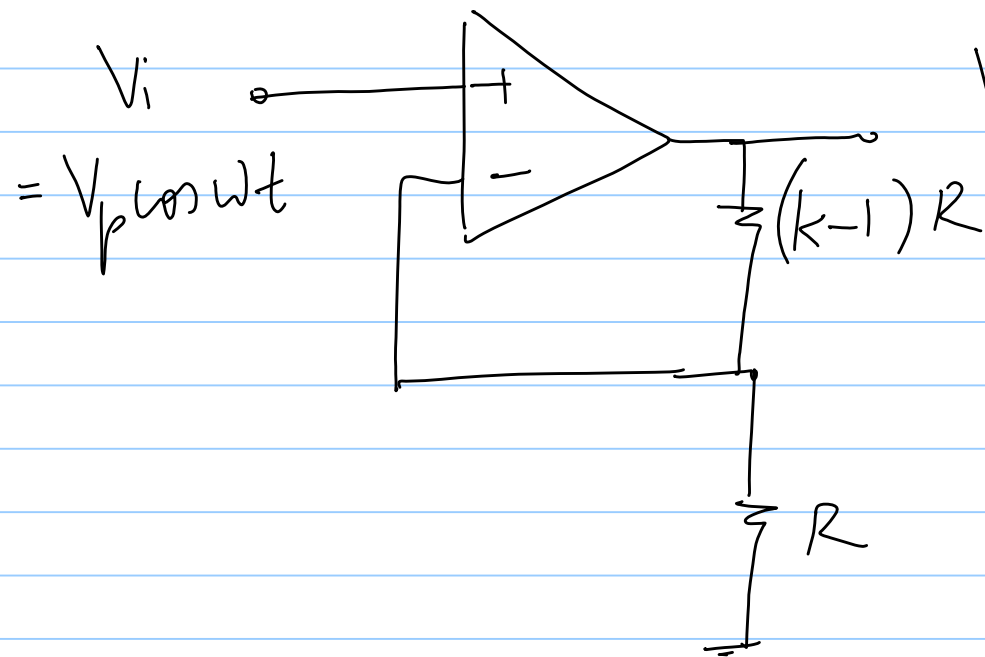
$$\frac{V_o(s)}{V_i(s)} = \frac{k(1 + s C R_o)}{k + G_m R_o + k s C R_o} \quad ?$$


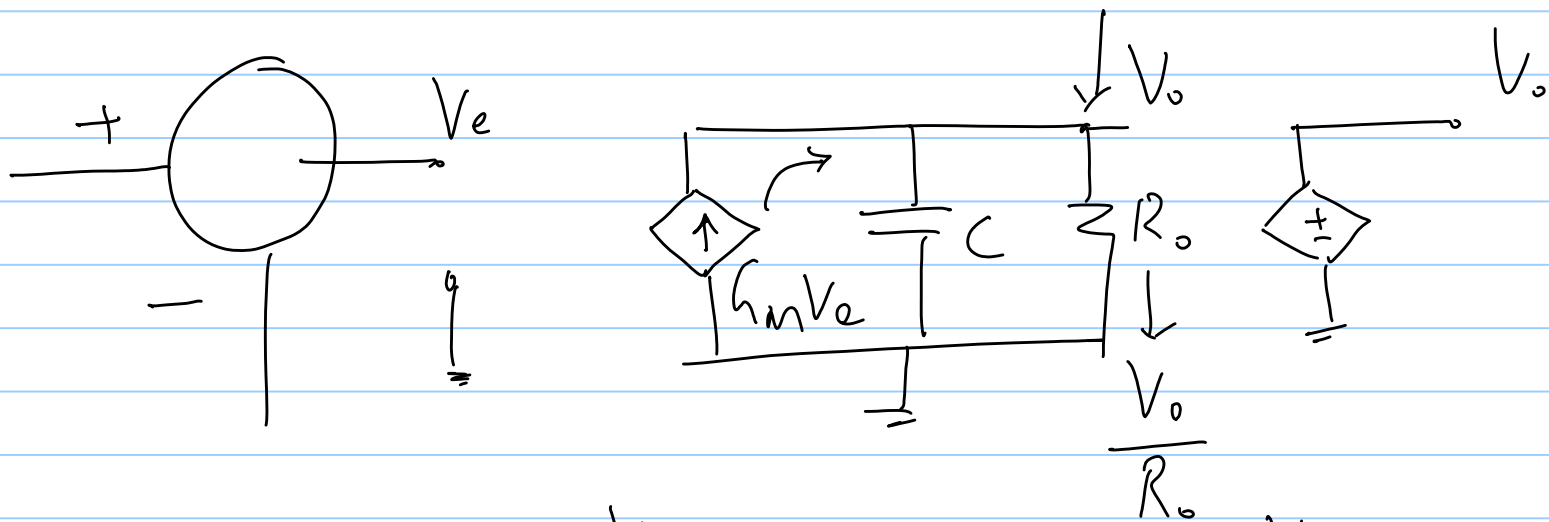
$$V_o = k V_p \cos \omega t \quad (\text{ideally})$$



$$G_m V_e = \frac{V_o}{R_o} \Rightarrow V_e = \frac{V_o}{G_m R_o}$$

Small $\omega \rightarrow$ env is almost same as DC case