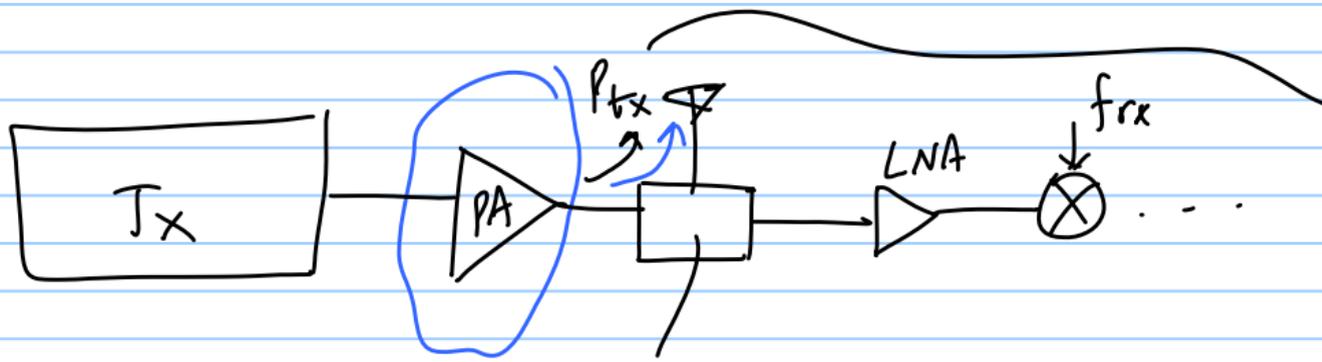





23/4/2019



CMOS Power Amplifiers (RF PA)




Cellular mW
WiFi ~ 100s of mW
Bluetooth ~ few mW

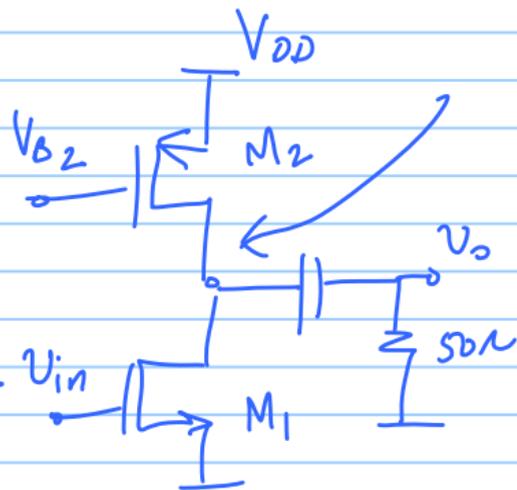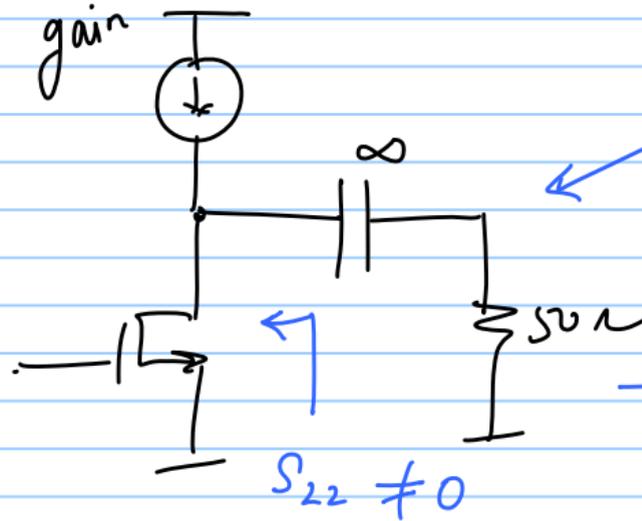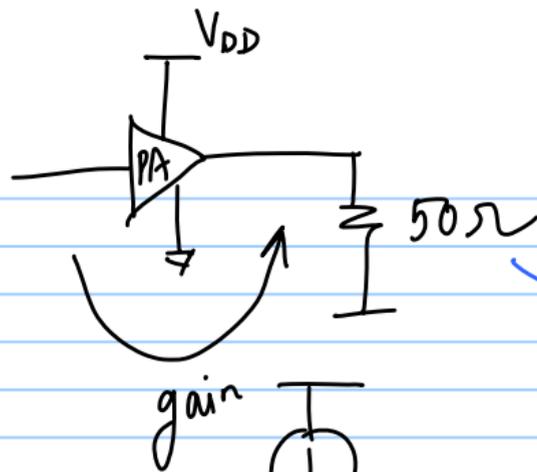duplexer or switch or duplexer
(FDD) (TDD) (FD)



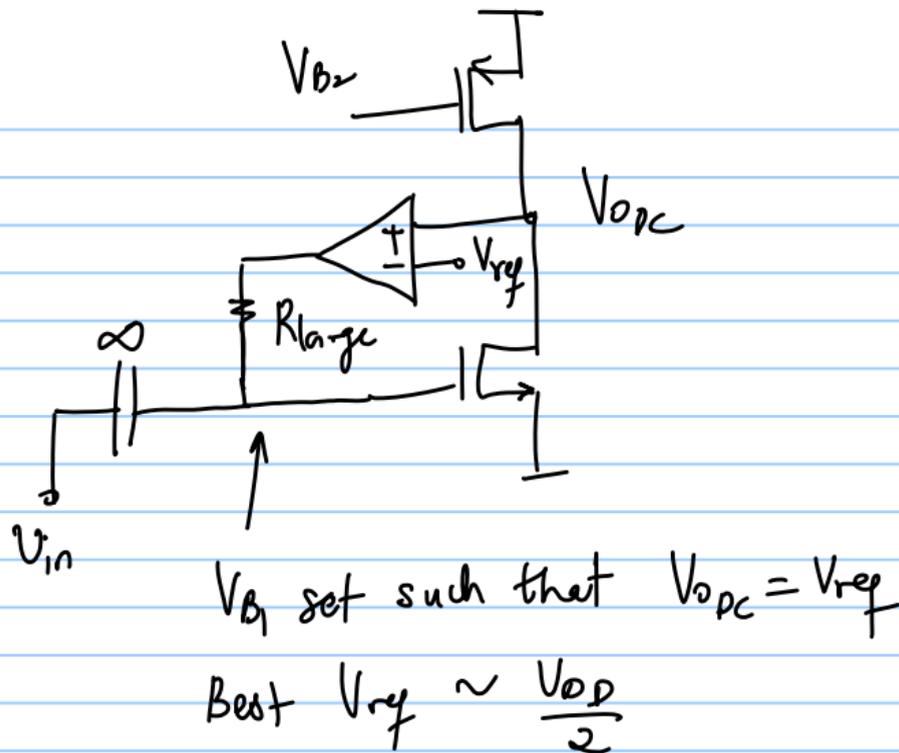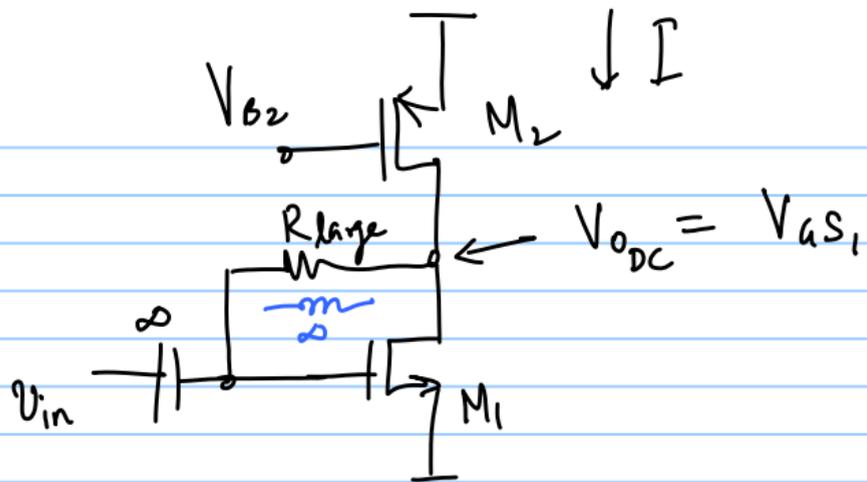


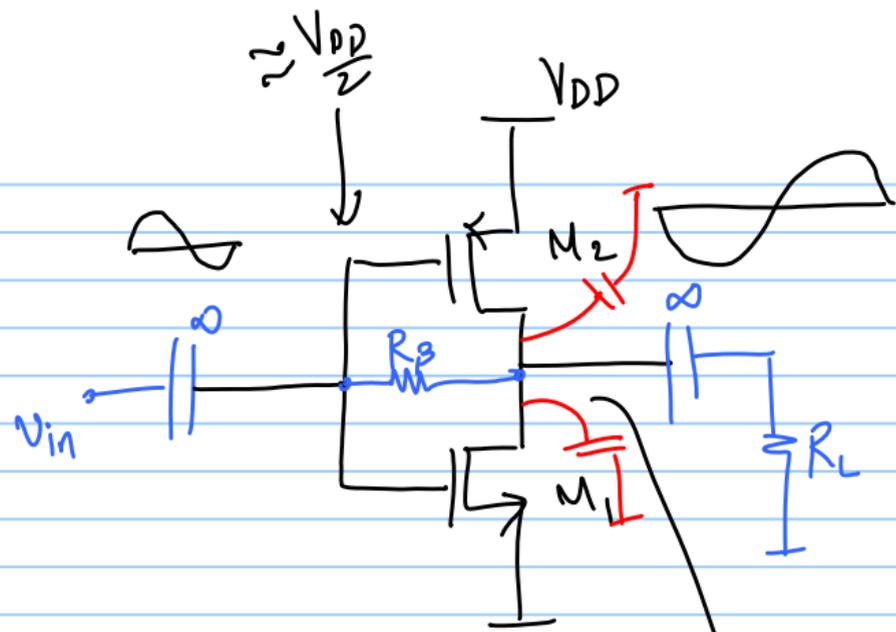

$g_{mp} \approx g_{mn}$ if $\frac{W_p}{L_n} \approx \frac{\mu_p}{\mu_n}$

low-freq.: max gain = $-\frac{g_{m_n} + g_{m_p}}{g_{ds_n} + g_{ds_p}}$

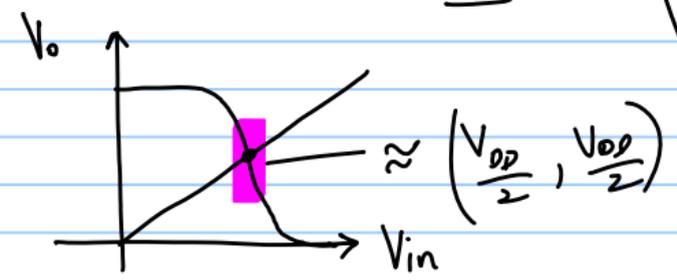RF: gain $\approx -(g_{m_n} + g_{m_p}) \cdot R_L$




max amplitude $\approx V_T$ (linear operation)

p-p swing = $2V_T$

Limitations :

- 1) # of degrees of freedom in design $\{W_n\}$
- 2) BW : Parasitic capacitances @ output node $\{C_{db}\}$
limited to a few GHz

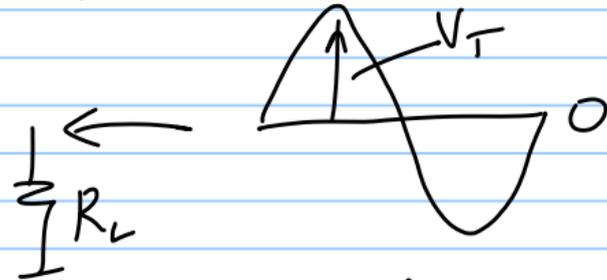
3) $\max \underline{P_{out}} : \frac{V_T^2}{2R_L} = \frac{V_T^2}{100}$




e.g. $V_T = 0.5V \Rightarrow P_{out}(\max) = 2.5 \text{ mW}$

$$P_{\text{sat}} = \frac{V_{\text{omax}}^2}{2R_L}$$

$$= \frac{(V_{\text{DD}}/2)^2}{2R_L}$$


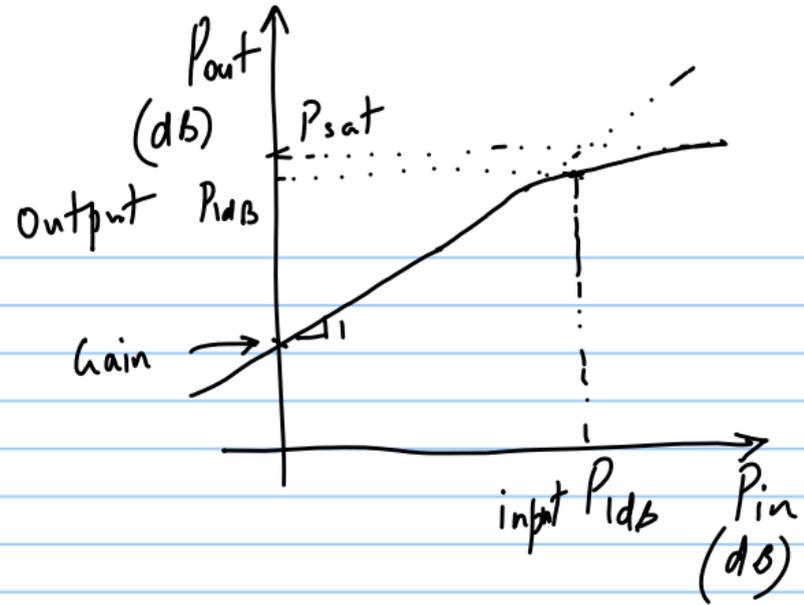


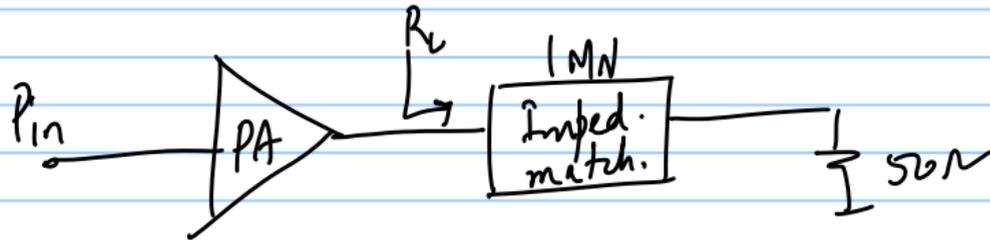e.g. $V_{\text{DD}} = 1.8\text{V} \Rightarrow P_{\text{sat}} = 8.1\text{mW}$



R_L can not be arbitrarily reduced
 * Q of IMN
 * layout parasitics

+ larger swing, P_{out}
 + wider BW

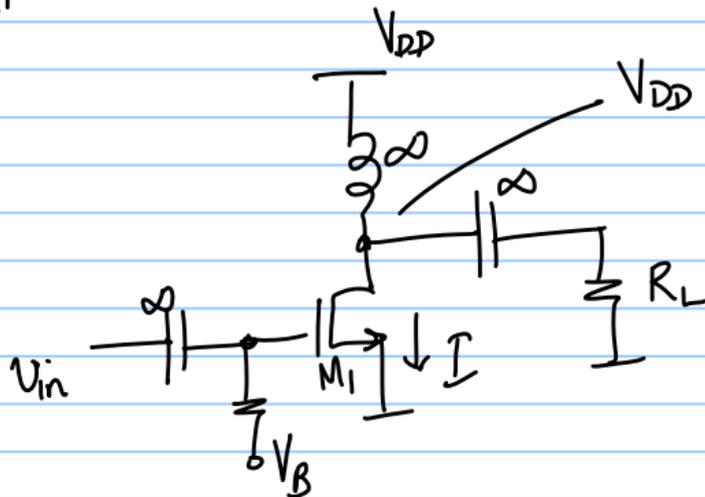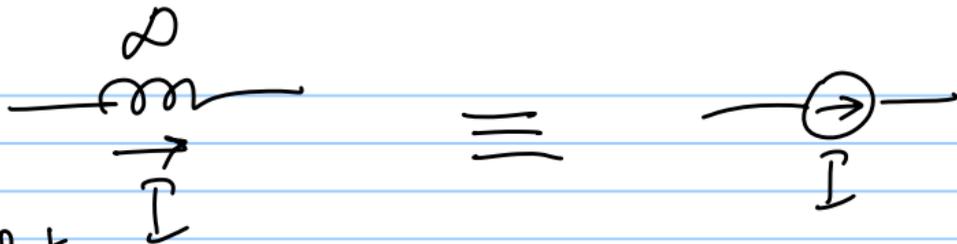


$$V_{O_{DC}} = V_{DD}$$


$$v_{o_{max}} = V_{DD} - V_{D_{sat}}$$


e.g. $v_{o_{max}} = 1.8V - 0.2V = 1.6V$

$$P_{out_{max}} = 40mW$$

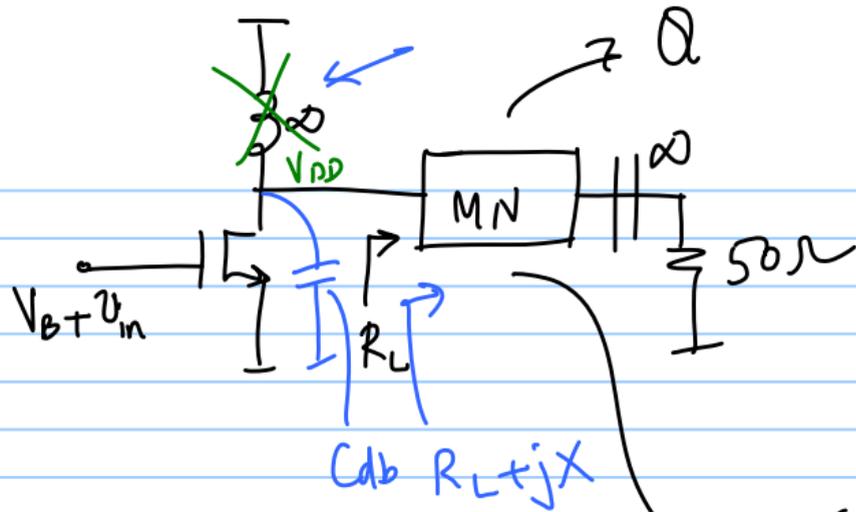

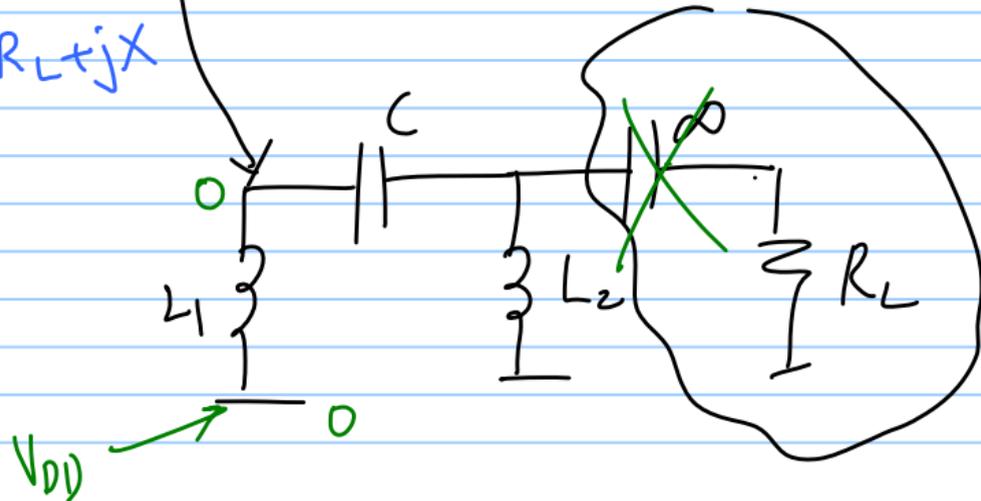e.g. $R_L = 12.5 \Omega$, $P_{out_{max}} = 160 \text{ mW}$



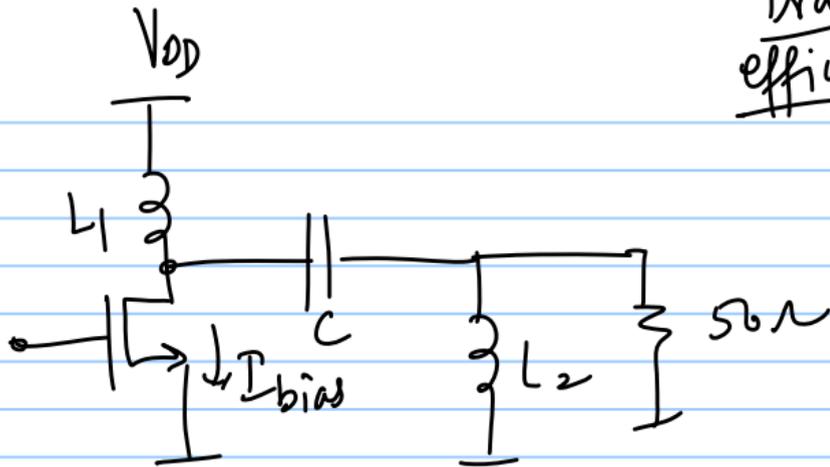

Drain efficiency $\eta =$

$$\approx \frac{V_{out}^2}{2R_L} \times 100$$

$P_{\text{delivered to load}} \times 100$


$P_{\text{taken from } V_{DD}}$

$$V_{DD} I_{\text{bias}}$$



η_{max} : = ?

$I_{\text{bias}} = ?$

+ o
 $V_{gs} = V_{in}$
- p

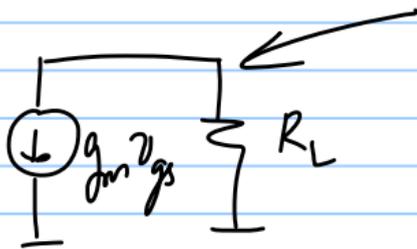

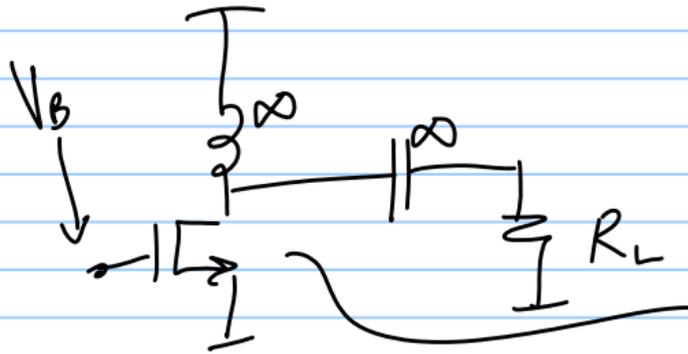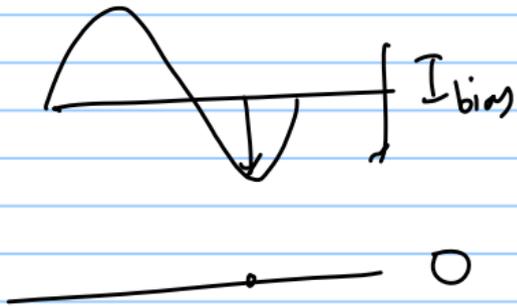Cutoff condition for M_1 $\rightarrow = I_{bias} + g_m V_{in}$
 $= I_{bias} + g_m V_{in} \sin \omega t$
 total $I_D > 0$ for no cutoff



$$\text{gain} = g_m R_L$$

$$P_{out} = i_{d,rms}^2 R_L$$


\rightarrow sets I_{bias}

W, I_{bia}

Cut off when: $I_{bias} = g_m V_{in}$ ← input signal amplitude
 $= i_d$

✓ ≠ Set

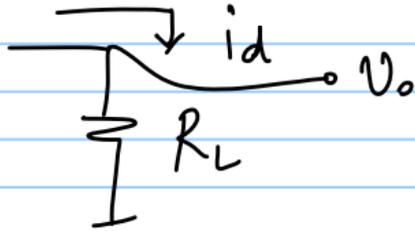Cut off & Triode swing limits to be equal.



$i_d = \frac{V_o}{R_L}$ → set to triode limit

$I_{bias} = \frac{V_{o_{max}}}{R_L} = \frac{V_{DD} - V_{DS_{sat}}}{R_L}$

$P_{out_{max}}$ sets $V_{DS_{sat}} \rightarrow I_{bias} \rightarrow W$

$$* P_{out_{max}} = P$$

$$* \eta_{max.} = \eta$$

$$P_{out} = i_{d_{rms}}^2 \cdot R_L$$

$$1) \quad P = \frac{(V_{DD} - V_{Dsat})^2}{2R_L} \Rightarrow V_{Dsat} \text{ is set} \left. \vphantom{\frac{(V_{DD} - V_{Dsat})^2}{2R_L}} \right\} \Rightarrow W \text{ is set}$$

$$2) \quad I_{bias} = \frac{V_{DD} - V_{Dsat}}{R_L} \Rightarrow I_{bias} \text{ is set}$$

neglect V_{sat} :

$$P_{\text{omax}} = \frac{V_{\text{DD}}^2}{2R_L}$$


$$I_{\text{bias}} = \frac{V_{\text{DD}}}{R_L}$$

$$\eta_{\text{max}} = \frac{P_{\text{omax}}}{V_{\text{DD}} \cdot I_{\text{bias}} \Big|_{P_{\text{omax}}}} = \frac{V_{\text{DD}}^2 / 2R_L}{V_{\text{DD}} \cdot V_{\text{DD}} / R_L} = \frac{1}{2} = 50\%$$


Other 50% dissipated in M_1
 $V_{\text{D rms}} \cdot I_{\text{D rms}}$

24/4/2019

CMOS RF PAS - 2

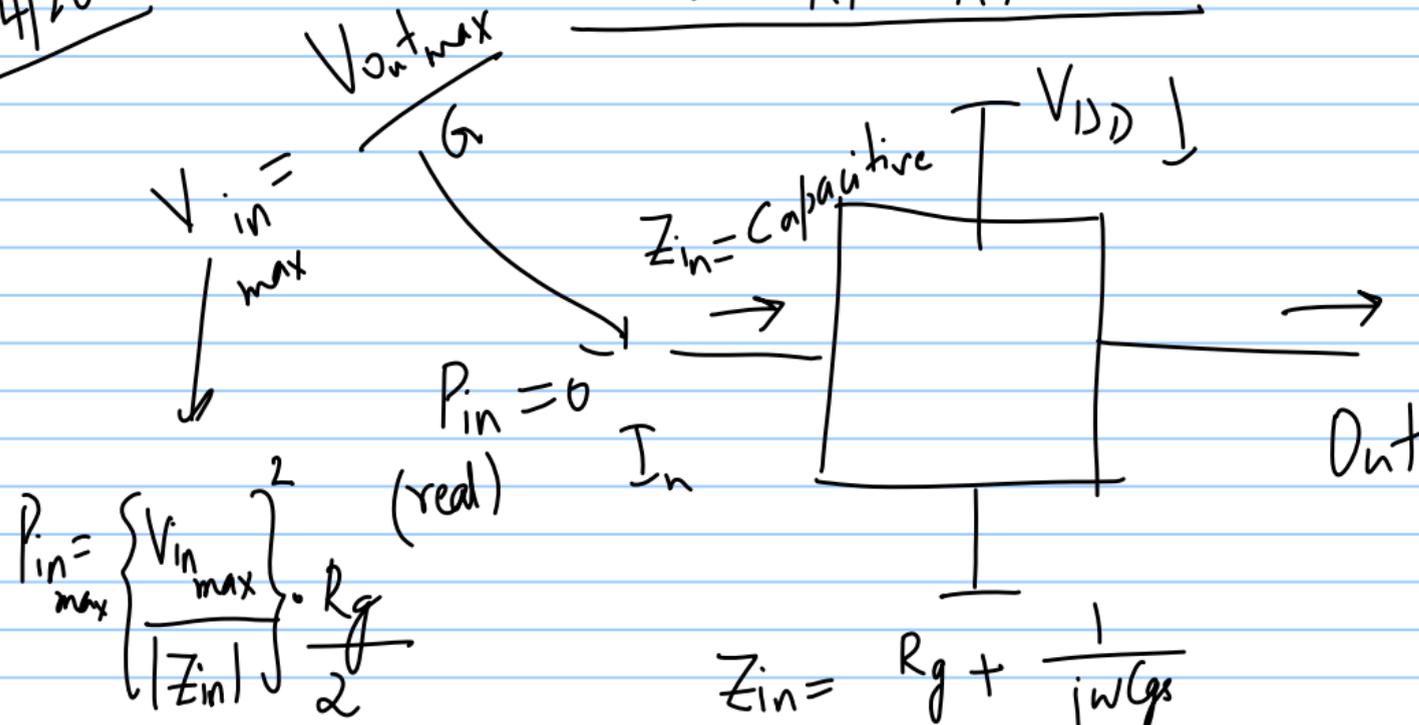


$$P_{in_max} = \frac{\left\{ \frac{V_{in_max}}{|Z_{in}|} \right\}^2 \cdot R_g}{2}$$

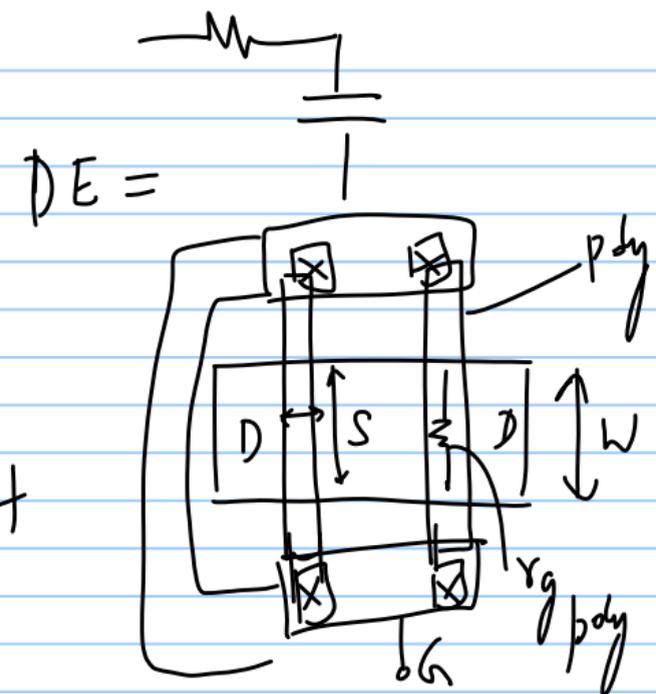


$$\text{PAE} = \frac{P_{\text{out}}}{P_{\text{in}} + P_{\text{dc}}} \times 100\%$$

power added efficiency

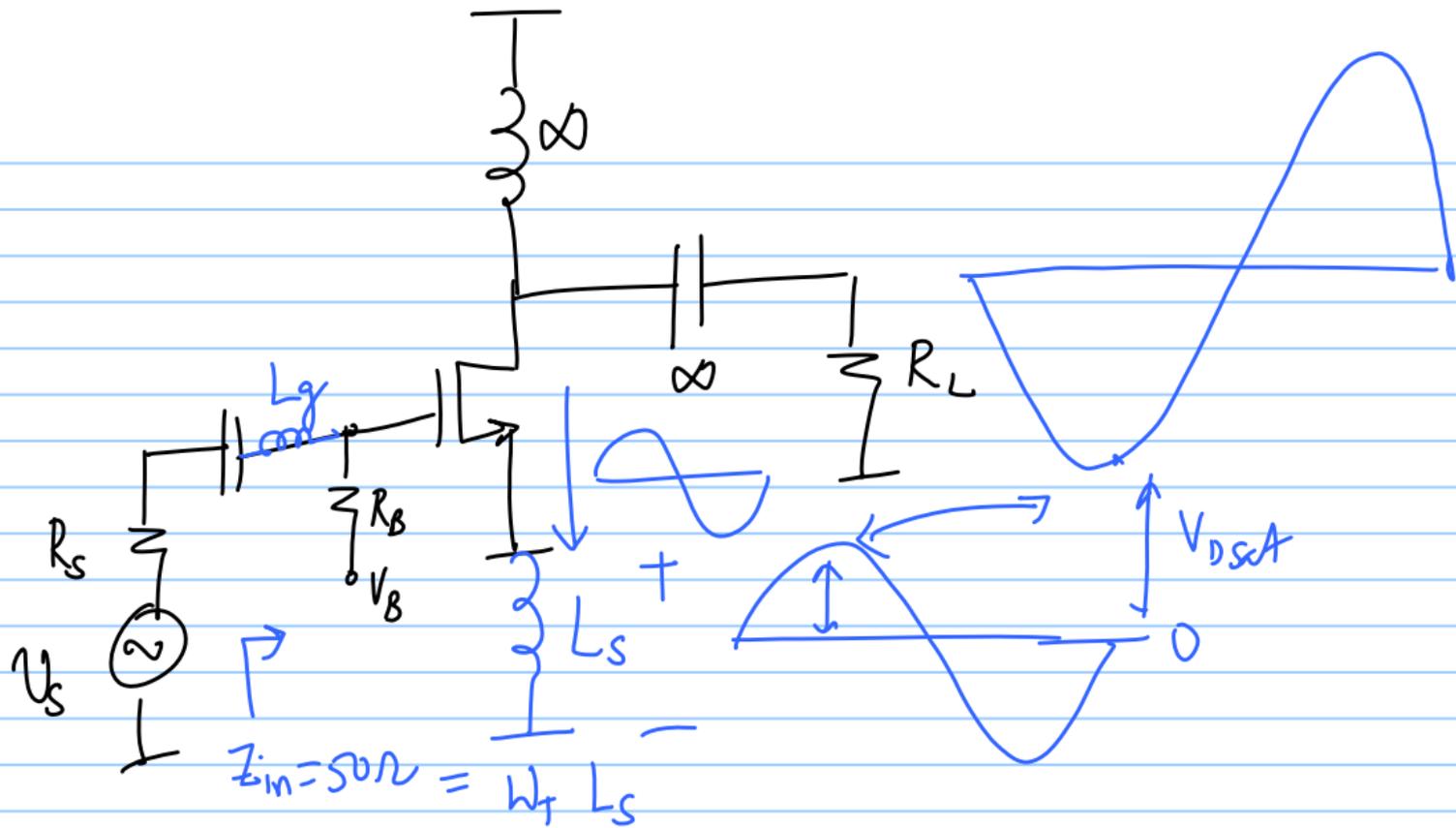PA module: matched @ input & output to 50Ω



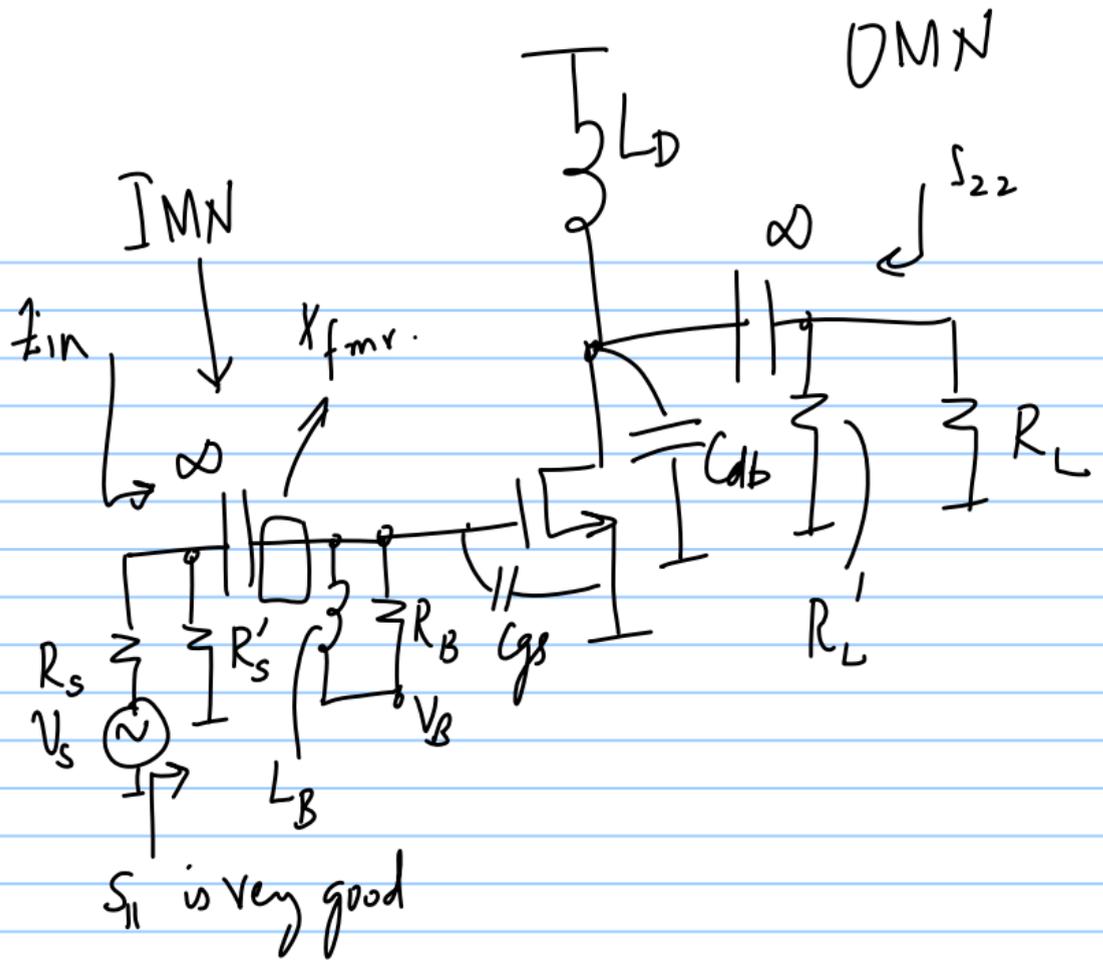


R'_s is chosen so that


$$\text{Re}\{Z_{in}\} = 50\Omega = R_s$$

L_B : so that it resonates with C_{gs}

R'_L : so that S_{22} is low


L_D : so that it resonates with C_{db}

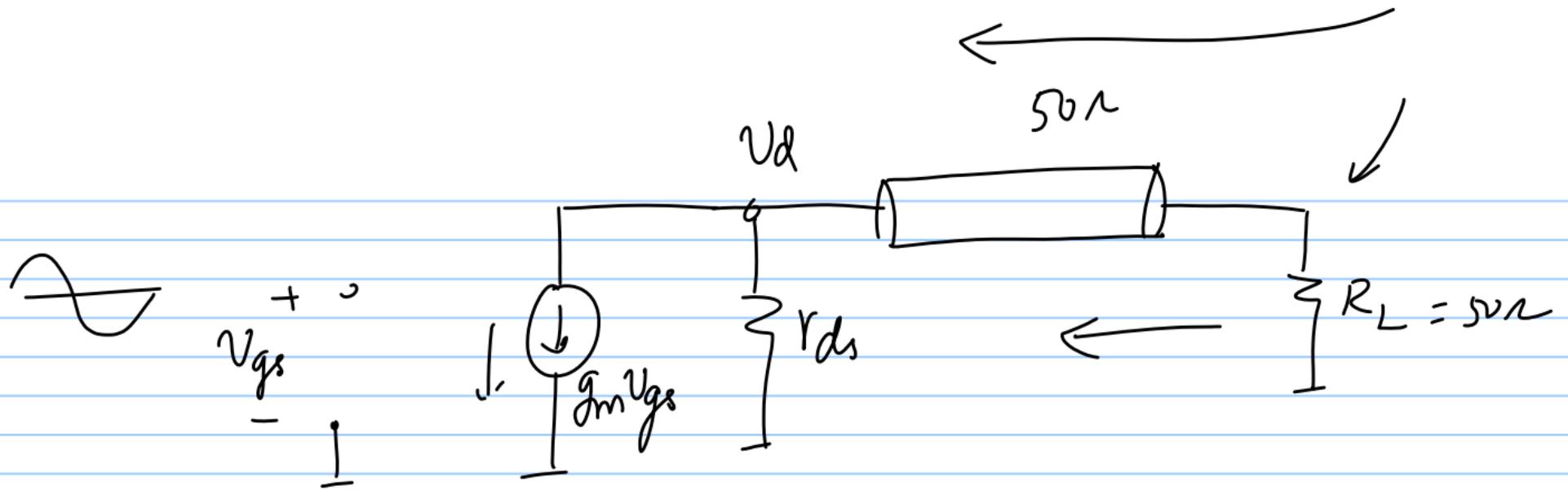

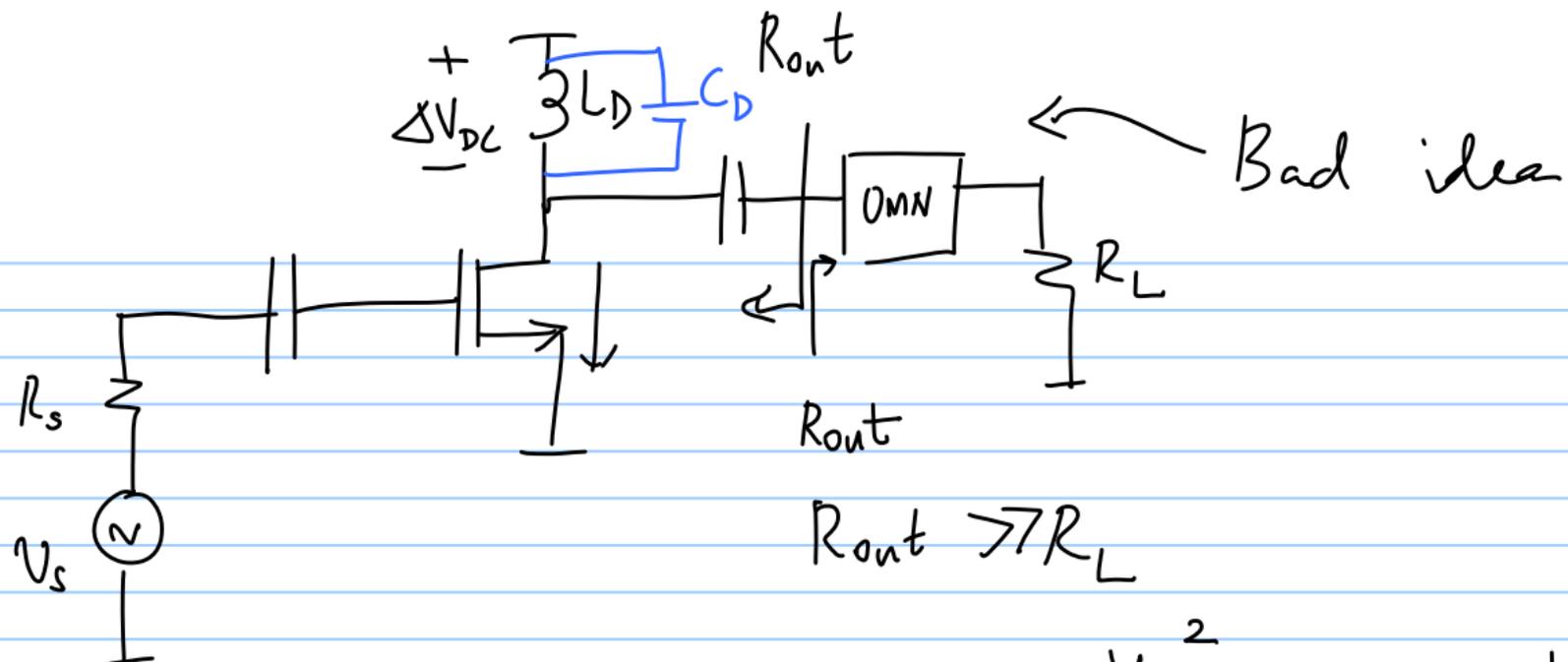


$$R_{out} \gg R_L$$

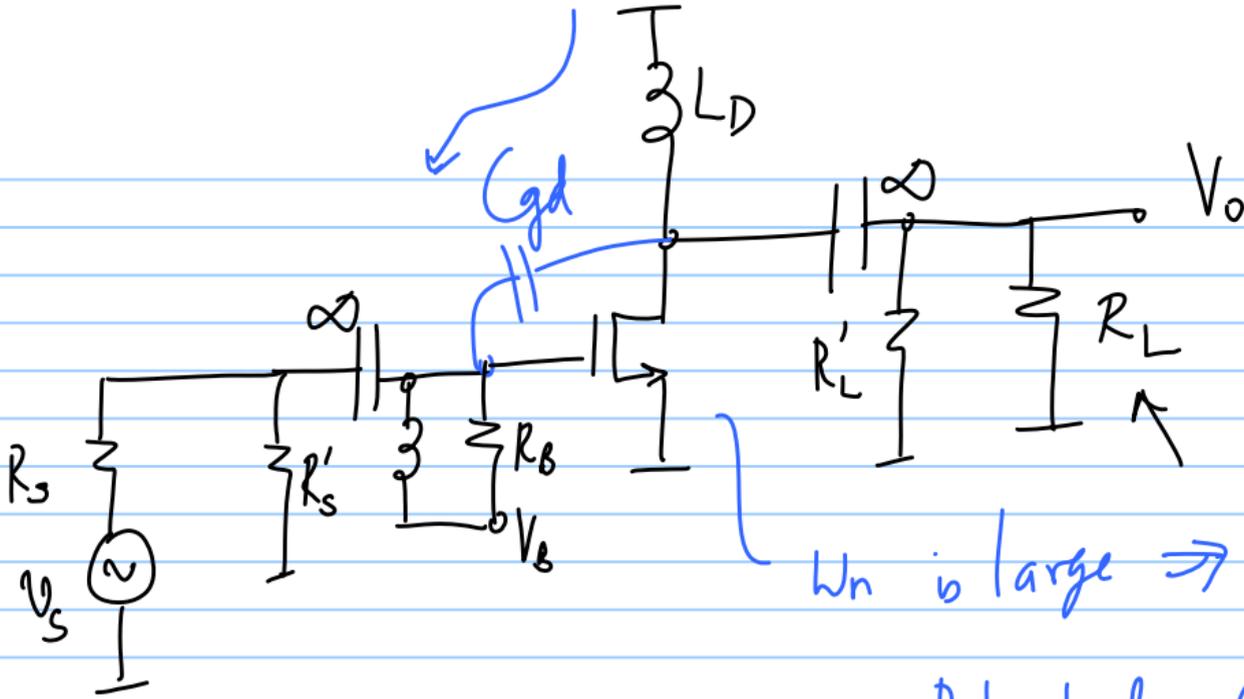
$$P_{out\ max} = \frac{V_{DD}^2}{2R_{out}} \ll \frac{V_{DD}^2}{2R_L}$$



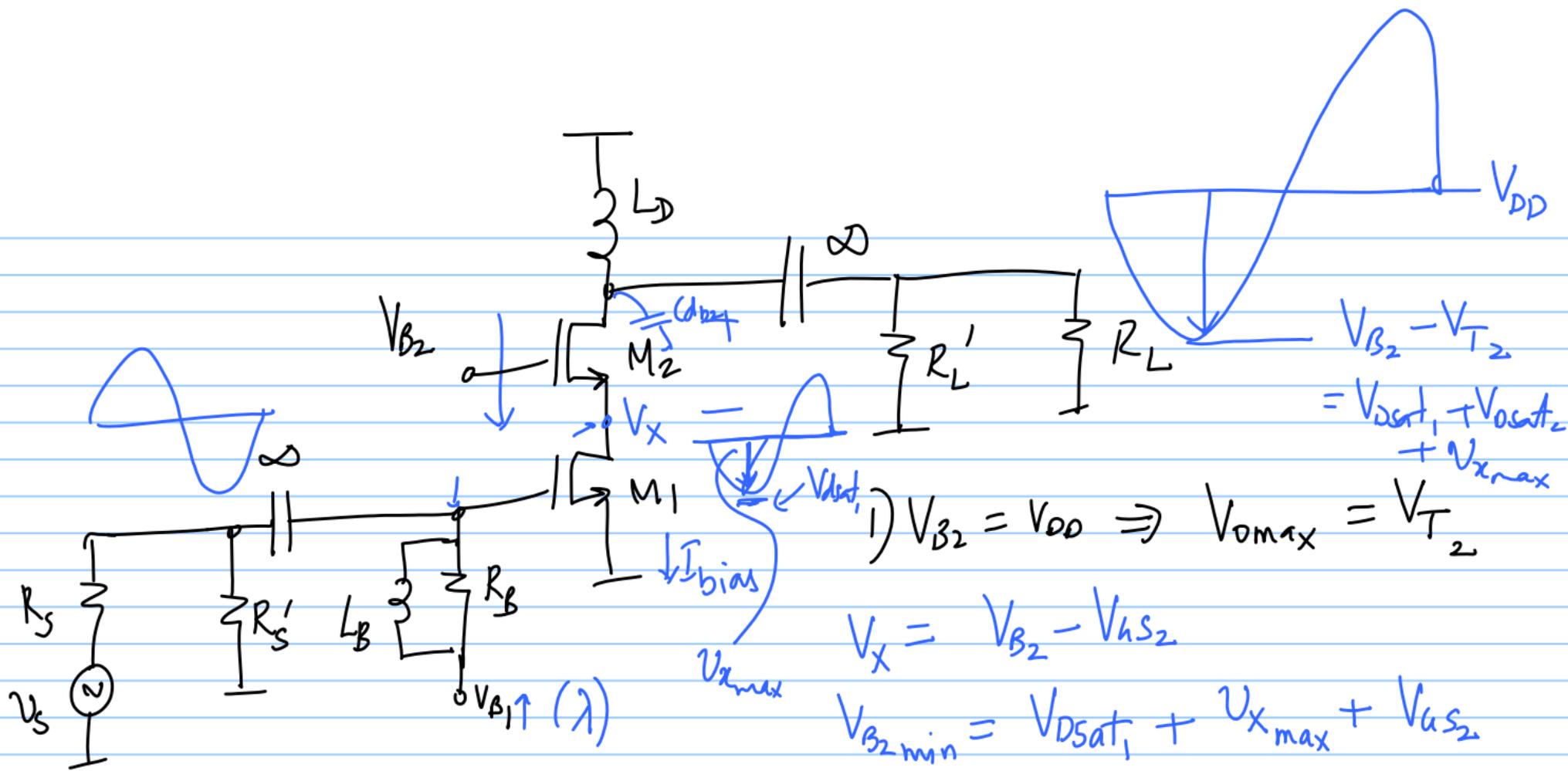W_n is large $\Rightarrow C_{gd}$ is large
 \Rightarrow Potential for instability
 \Rightarrow Add a cascode



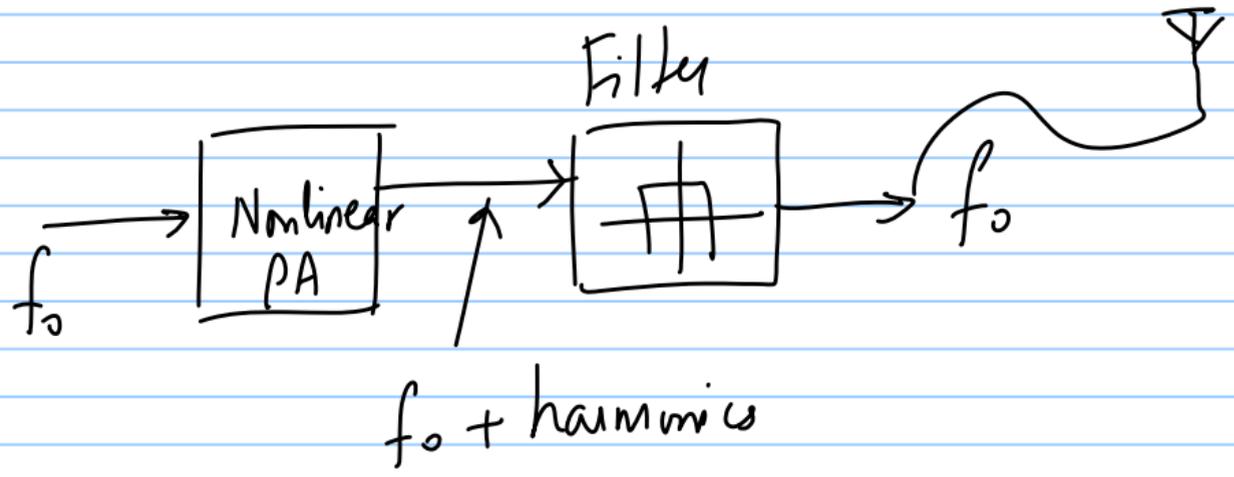
So far: Linear / Class A PAs $\theta_c = 360^\circ$ "conduction angle"



$\theta_c = 180^\circ - 360^\circ \Rightarrow$ Class AB operation

$\theta_c = 180^\circ \Rightarrow$ Class B operation

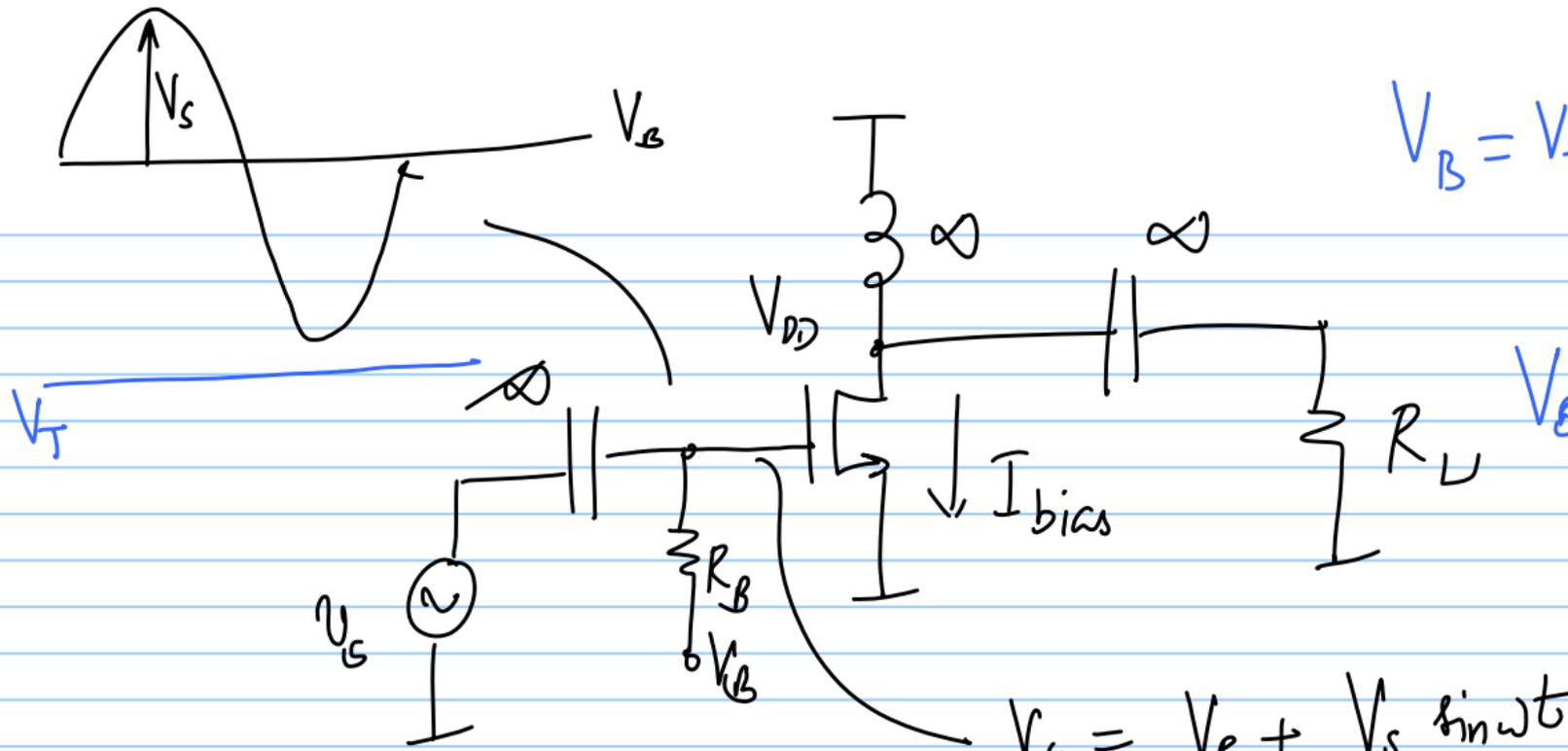$\theta_c < 180^\circ \Rightarrow$ class C operation



$V_B = V_T \Rightarrow$ class B operation

$V_B < V_T$: class C operation

$$V_a = V_B + V_s \sin \omega t$$



linear: $V_a > V_T$ for full cycle

Class E

Add extra circuits {LC} so that

* When $V_{DS} > 0$, $I_D = 0$

* When $I_D > 0$, $V_{DS} = 0$

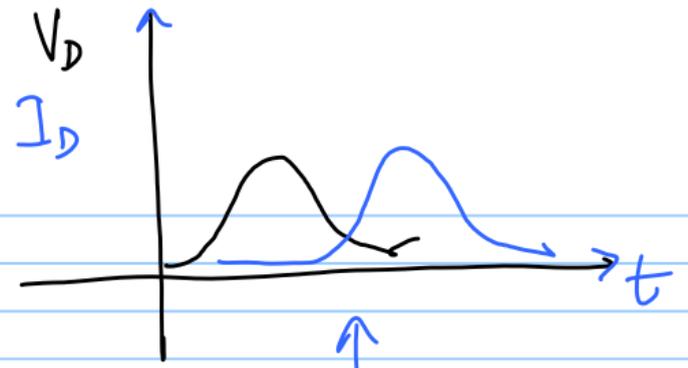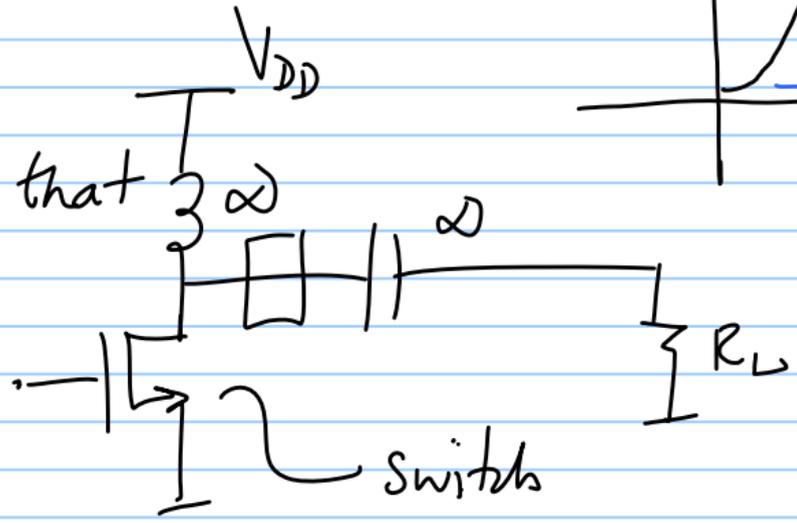

↑
reduce overlap
between V_D & I_D

class D, class F, class G, class J ...