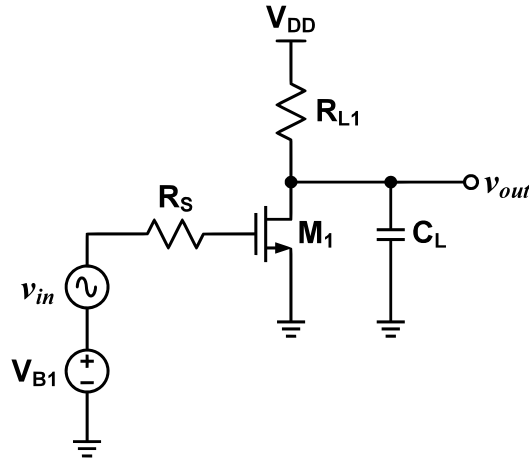



PROBLEM 1. Common Source (CS) Amplifier



Given: $V_{DD} = 1.3\text{V}$, $R_S = 50\Omega$, $R_{L1} = 0.9\text{k}\Omega$ and $C_L = 1\text{pF}$. The operating points of M_1 are as follows: $I_d = 1\text{mA}$, $g_m = 8.2\text{mA/V}$, $g_{ds} = 0.3\text{mA/V}$, $g_{mb} = 2.2\text{mA/V}$, $C_{gs} = 31\text{fF}$, $C_{gd} = 14\text{fF}$, $C_{gb} = 1\text{fF}$, $C_{db} = 28\text{fF}$, $C_{sb} = 31\text{fF}$. Bulk of M_1 is grounded.

- (a) Draw the small signal equivalent model of the above CS amplifier and find $v_{out}(s)/v_{in}(s)$.
- (b) Find DC Gain, poles and zeroes of the transfer function. Use approximations as necessary.
- (c) Plot the magnitude and phase of $v_{out}(s)/v_{in}(s)$ with and without the approximations.


PROBLEM 2. Common Gate (CG) Amplifier

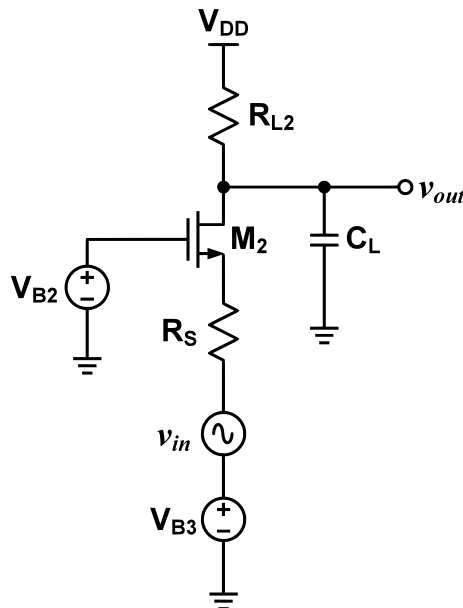

Given: $V_{DD} = 1.3\text{V}$, $R_S = 50\Omega$, $R_{L2} = 0.8\text{k}\Omega$ and $C_L = 1\text{pF}$. The operating points of M_2 are as follows: $I_d = 1\text{mA}$, $V_{ds} = 0.9\text{V}$, $g_m = 8\text{mA/V}$, $g_{ds} = 0.3\text{mA/V}$, $g_{mb} = 2.1\text{mA/V}$, $C_{gs} = 30\text{fF}$, $C_{gd} = 13\text{fF}$, $C_{gb} = 0.8\text{fF}$, $C_{db} = 26\text{fF}$, $C_{sb} = 29\text{fF}$. Bulk of M_2 is grounded.

- Draw the small signal equivalent model of the above CG amplifier and find $v_{out}(s)/v_{in}(s)$.
- Find DC Gain, poles and zeroes of the transfer function. Use approximations as necessary.
- Plot the magnitude and phase of $v_{out}(s)/v_{in}(s)$ with and without the approximations.

PROBLEM 3. Source Follower

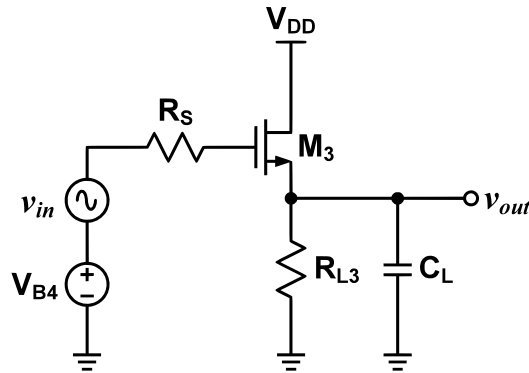

Given: $V_{DD} = 1.3V$, $R_S = 50\Omega$, $R_{L3} = 0.5k\Omega$ and $C_L = 1pF$. The operating points of M_3 are as follows: $I_d = 1mA$, $g_m = 7.4mA/V$, $g_{ds} = 0.3mA/V$, $g_{mb} = 1.8mA/V$, $C_{gs} = 25fF$, $C_{gd} = 11fF$, $C_{gb} = 0.4fF$, $C_{db} = 21fF$, $C_{sb} = 23fF$. Bulk of M_3 is grounded.

- Draw the small signal equivalent model of the above source follower and find $v_{out}(s)/v_{in}(s)$.
- Find DC Gain, poles and zeroes of the transfer function. Use approximations as necessary.
- Plot the magnitude and phase of $v_{out}(s)/v_{in}(s)$ with and without the approximations.