

3/1/20

Note


03-01-2020

Lec 1


2 'similar'

IC - devices can be assumed to be  
nominally identical

Assume no  $L$  (ind) for this course

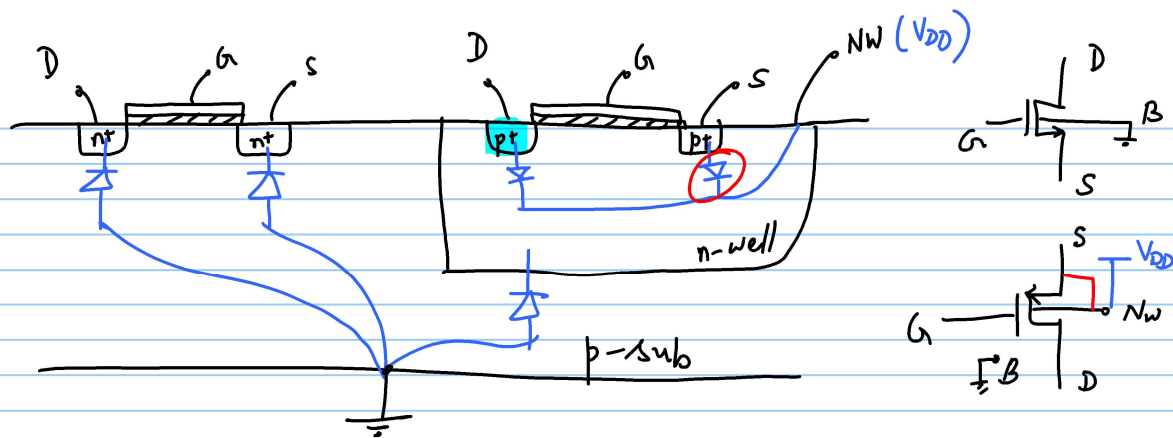


Resistors → mΩ to 100s of kΩ

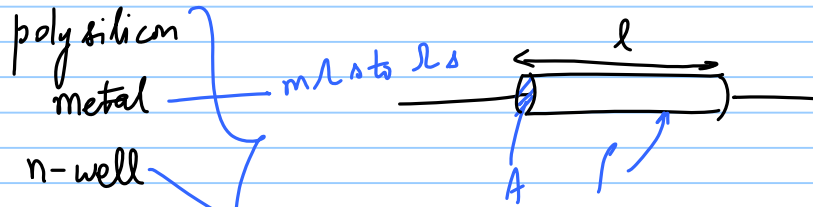

$$R = \frac{\rho l}{A}$$

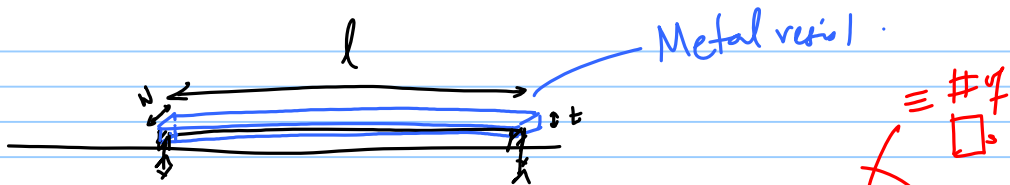larger resistors (10s to 100s of kΩ)  
medium



$$R = \frac{\rho l}{A} = \frac{\rho \cdot l}{w \cdot t} = \left( \frac{\rho}{t} \right) \cdot \frac{l}{w}$$

$\frac{\rho}{t}$  is set by process  
 "sheet resistance"

$\frac{l}{w}$   $\equiv$  # of  $\square$

$\rho / \square$



Value


Power

Accuracy/ Tolerance

Temperature Coefficient ✓


Size

Linearity ✓

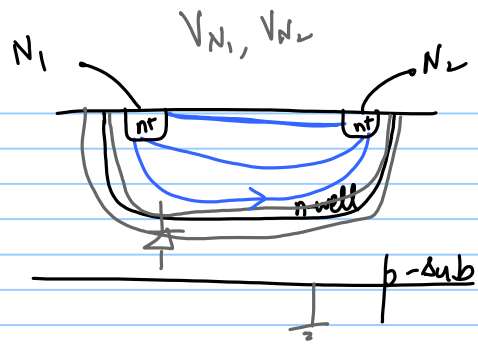


$$V = I \cdot R$$

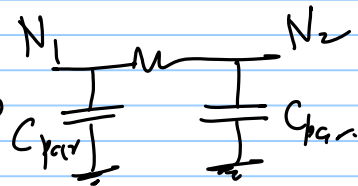
$$I = \frac{V}{R} + ( ) V^2 + ( ) V^3 + \dots$$





# Capacitors

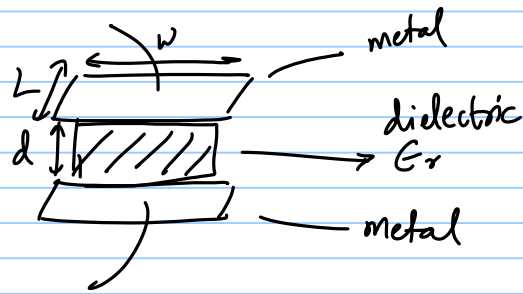

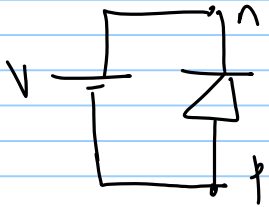
$$C = \frac{\epsilon_r \cdot \epsilon_0 \cdot w \cdot L}{d}$$



$\equiv C_{diode}$

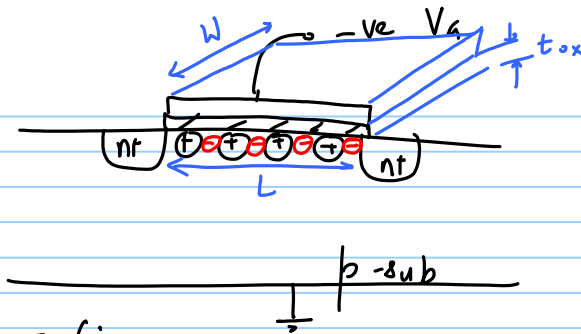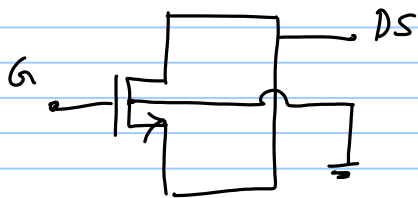

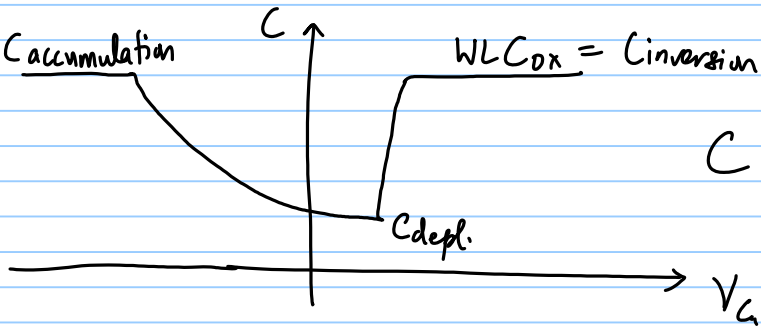$w \cdot L \cdot C_{ox} = C_{accumulation}$







$$C = \frac{\epsilon_0 \epsilon_r \cdot W \cdot L}{t_{ox}} \equiv C_{ox}$$


MIM & MOM


— linear
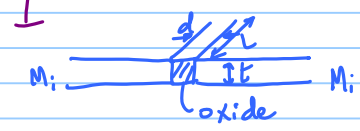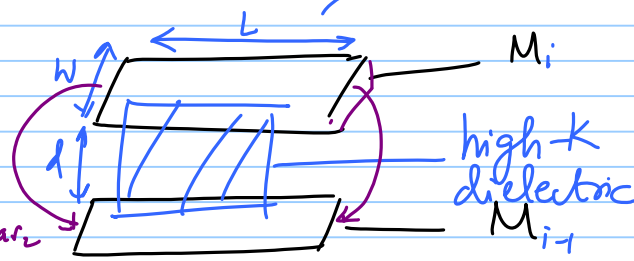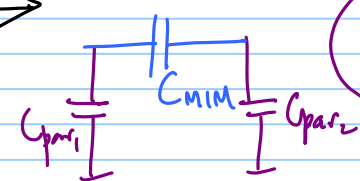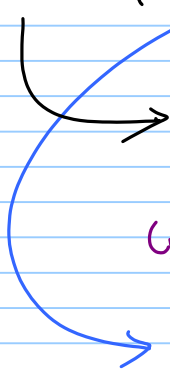
$$C_{ap} = \frac{w \cdot l \cdot \epsilon_0 \cdot k}{d}$$


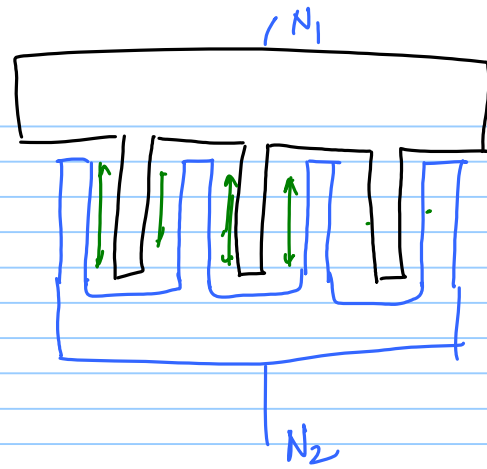
$$C_{non} = \frac{l \cdot t \cdot \epsilon_0 \cdot \epsilon_r}{d_{min}}$$



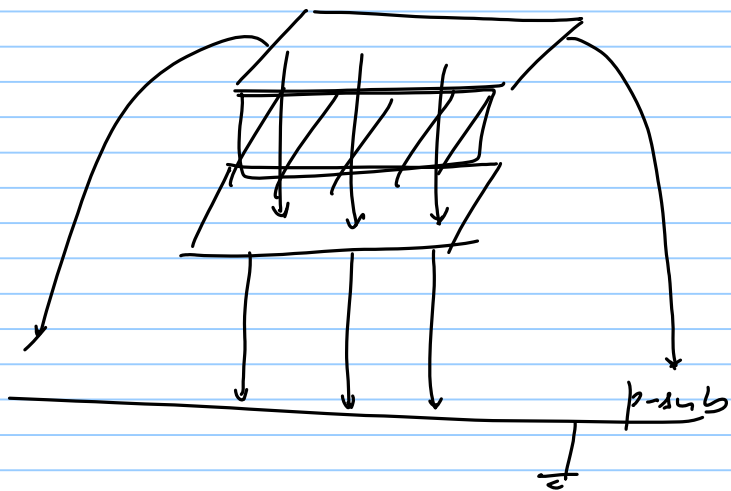


6/1/20

Lec 2

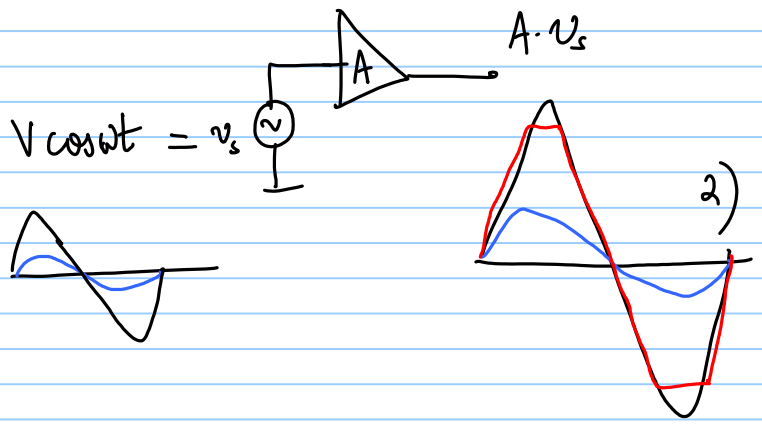
1) As  $v_s$  amplitude  $\uparrow$  : ( $V \uparrow$ )

clipping of sinusoid after violation of swing limits



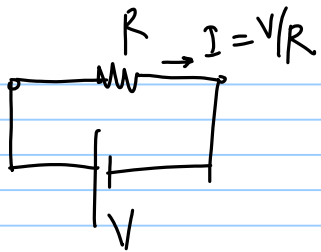
2) As  $V \downarrow$  : reach noise limits






Random motion of charges becomes comparable to deterministic motion

1) Thermal noise of R

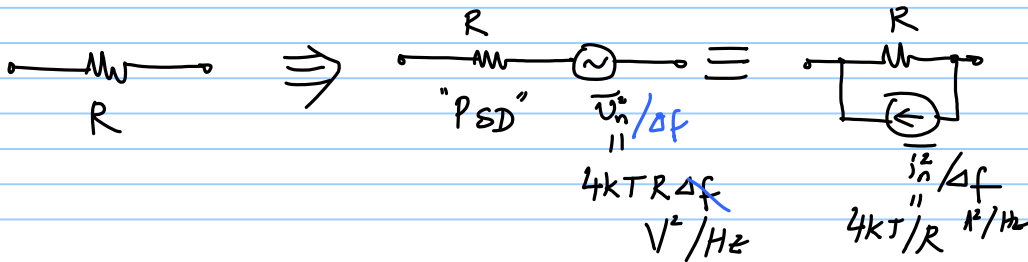

\* "White" noise <sup>constant PSD</sup>

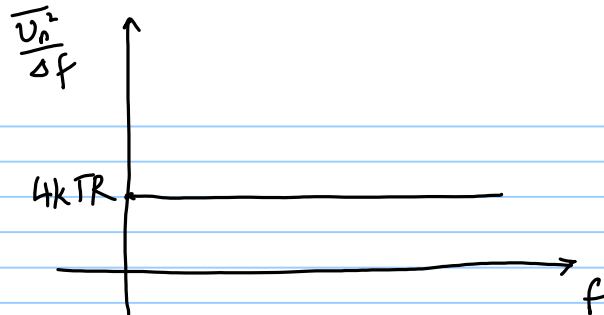\* Either  $\overline{v_n^2}$  or  $\overline{i_n^2}$  should be considered




2)  $\nu$ , C, L, M  $\rightarrow$  No noise  
pure



e.g.  $1\text{ k}\Omega$  Res:


$$\overline{v_n^2} / \Delta f = 16 \times 10^{-18} \text{ V}^2 / \text{Hz} \quad \overline{v_n} / \sqrt{\Delta f} = 4 \text{ nV} / \sqrt{\text{Hz}}$$
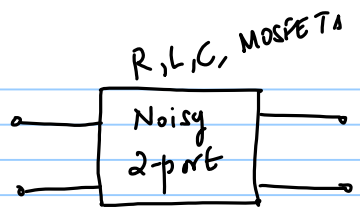
$$\overline{i_n^2} / \Delta f = 16 \times 10^{-24} \text{ A}^2 / \text{Hz} \quad \overline{i_n} / \sqrt{\Delta f} = 4 \text{ pA} / \sqrt{\text{Hz}}$$






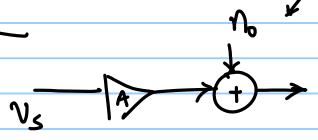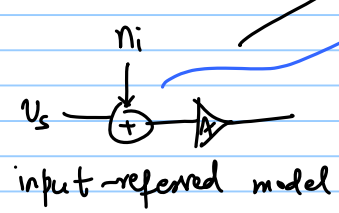
"Input-referred" noise ✓  
"Output-referred" noise



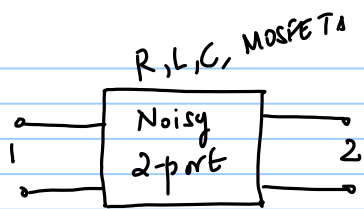


≡

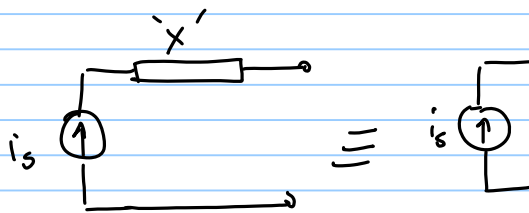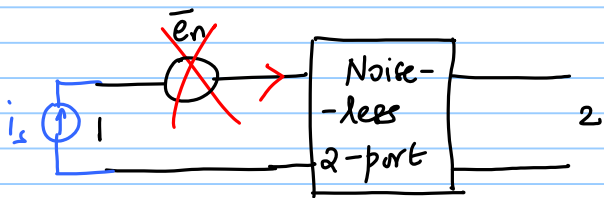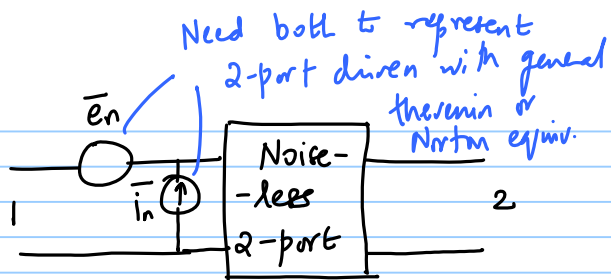

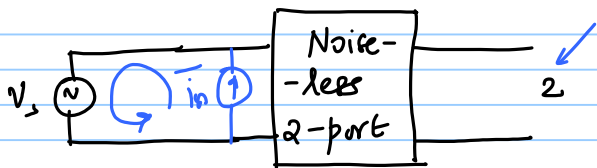


E.g.

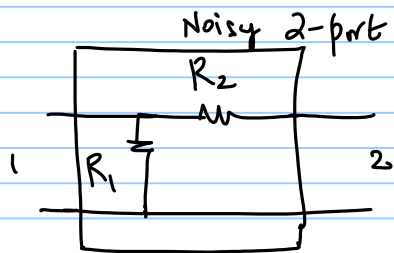


$$\bar{e}_n = ? \quad \bar{i}_n = ?$$

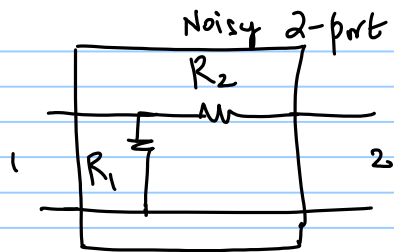\* You need  $\bar{e}_n$  &  $\bar{i}_n$  separately




≡

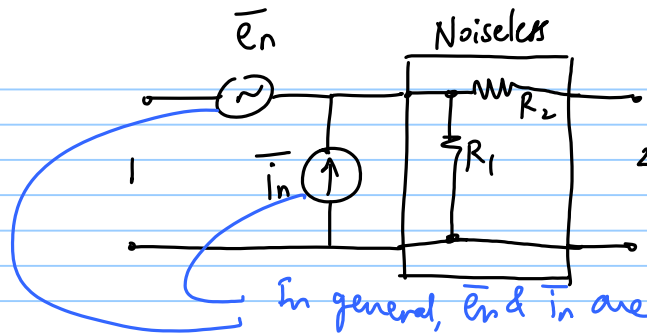


In general,  $\bar{e}_n$  &  $\bar{i}_n$  are partially correlated

Case 1

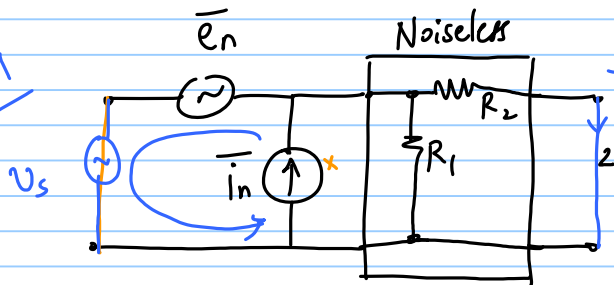

$$\bar{i}_{o1} = f(\bar{e}_n) \text{ only}$$



$$= \frac{\bar{e}_n}{R_2}$$

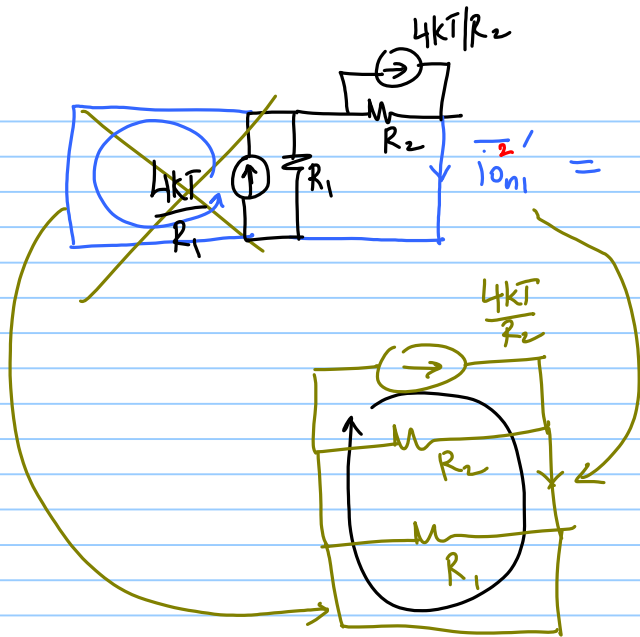

$$\frac{4kT}{R_2}$$

$$\frac{\overline{e_n^2}}{R_2} = \frac{4kT}{R_2}$$

$$\overline{e_n^2} / \Delta f = 4kTR_2$$

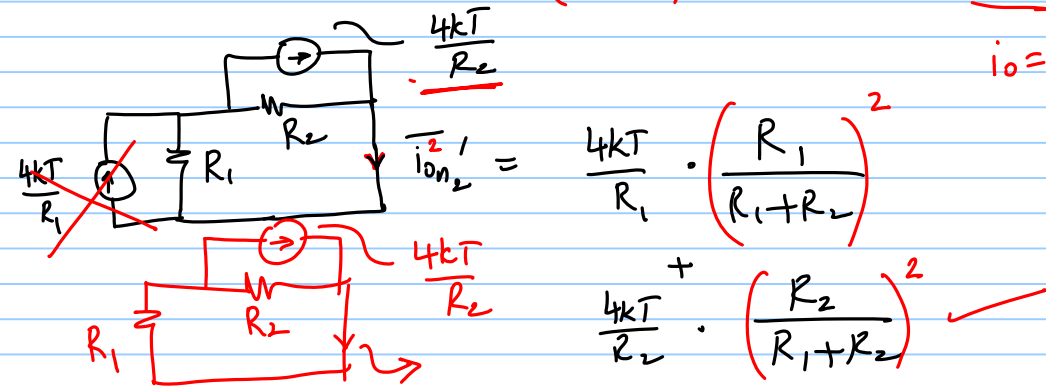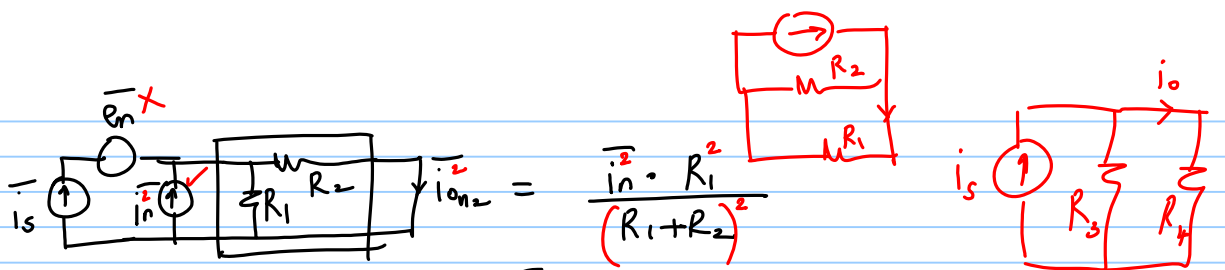



$$\overline{i_n^2} \cdot \left( \frac{R_1}{R_1 + R_2} \right)^2 = \frac{4kT}{R_1} \cdot \left( \frac{R_1}{R_1 + R_2} \right)^2 + \frac{4kT}{R_2} \cdot \left( \frac{R_2}{R_1 + R_2} \right)^2$$


$$\overline{i_n^2} = \frac{4kT}{R_1} + \frac{4kT}{R_2} \cdot \left( \frac{R_2}{R_1} \right)^2$$

mean  
squared  
noise

$$\overline{i_n^2} = \frac{4kT}{R_1} +$$

$$\frac{4kT}{R_2} \left( \frac{R_2}{R_1} \right)^2$$

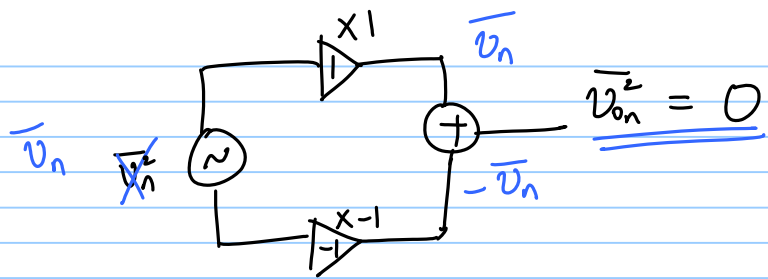
always add  
noise power  
not  $I/V$   
except in cases of noise  
correlation




8/1/20

Lec 3

Noise in MOSFETs (saturation)

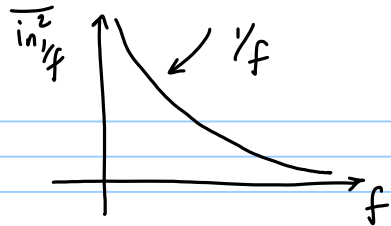


1) Flicker noise or  $1/f$  noise

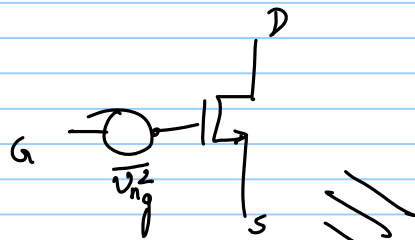

$$\frac{\overline{v_{ng}^2}}{\Delta f} = \frac{K_f}{W \cdot L \cdot C_{ox}^2} \cdot \frac{1}{f}$$



← empirical parameter  
different for nmos & pmos

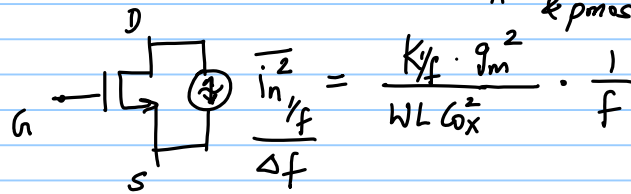large devices  $\leftrightarrow$  low  $1/f$  noise




$$\frac{\overline{i_n^2}}{\Delta f} = \frac{K_f \cdot g_m^2}{W L C_{ox}^2} \cdot \frac{1}{f}$$


2) Drain Thermal noise ("White")

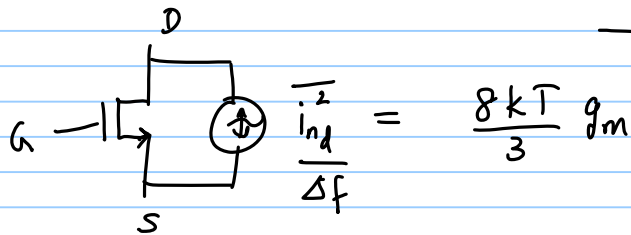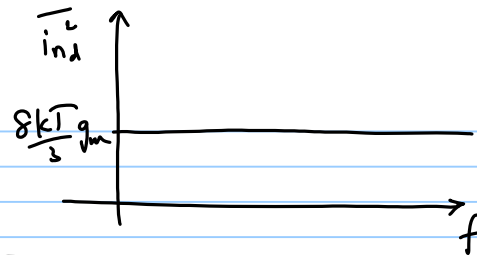

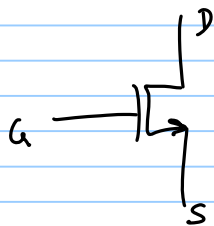3) MOSFET in triode:  $\frac{\overline{i_{nd}^2}}{\Delta f} = 4kTg_{ds}$  X not used in this course




≡

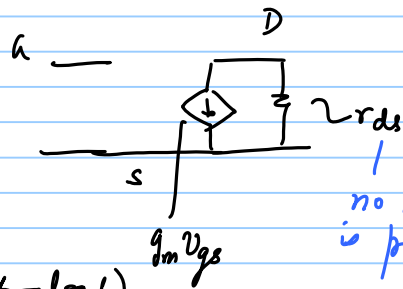


no noise is produced

$\sqrt{i_{nd}^2 + i_{n1/f}^2}$   
(log)

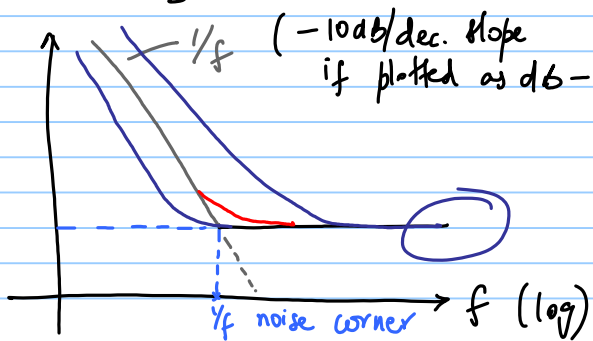

# Common Source Amplifier

E.g. 1)

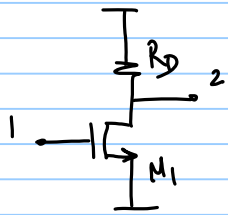

$$\frac{\overline{e_n^2}}{\Delta f} = ?$$



$$\frac{\overline{i_n^2}}{\Delta f} = 0$$

ⓐ low freq. only


part 1: choose to drive with ideal  $v_s$

part 2: choose to measure S.C. current

①

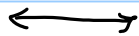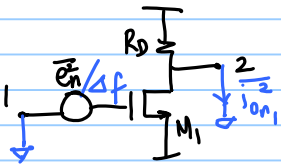

②

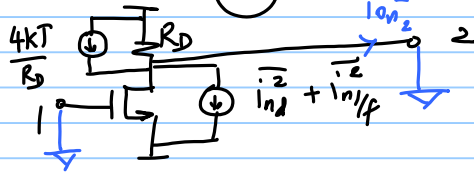

$$(1) : \overline{i_{o_{n1}}^2} = g_{m1}^2 \cdot \overline{e_n^2}$$

$$(2) : \overline{i_{o_{n2}}^2} = \overline{i_{nd}^2} + \overline{i_{n1/f}^2} + \overline{i_{nR_D}^2}$$

$$\overline{i_{o_{n1}}^2} = \overline{i_{o_{n2}}^2}$$



$$\overline{e_n^2} = \frac{\overline{i_{nd}^2} + \overline{i_{n1/f}^2} + \overline{i_{nR_D}^2}}{g_{m1}^2}$$

$$\frac{\overline{e_n^2}}{\Delta f} = \frac{8kT}{3g_{m1}} + \frac{K_{1/f}}{W_L \cdot C_{ox}^2} \cdot \frac{1}{f} + \frac{4kT}{g_{m1}^2 R_D}$$

$$\frac{4kT}{g_{m1}} \cdot \frac{1}{g_{m1} R_D}$$

gain


Eg. 2)

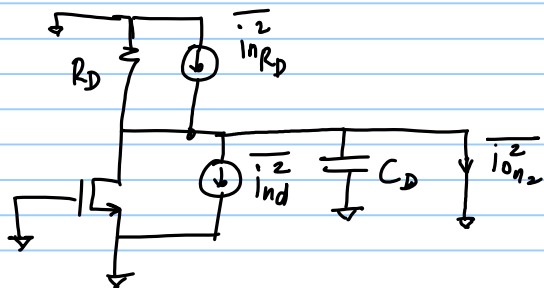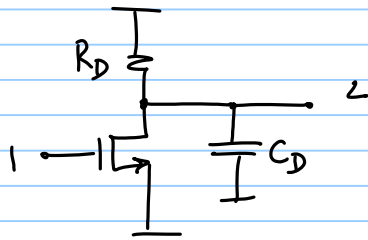



$\bar{e}_n =$  same as before ✓

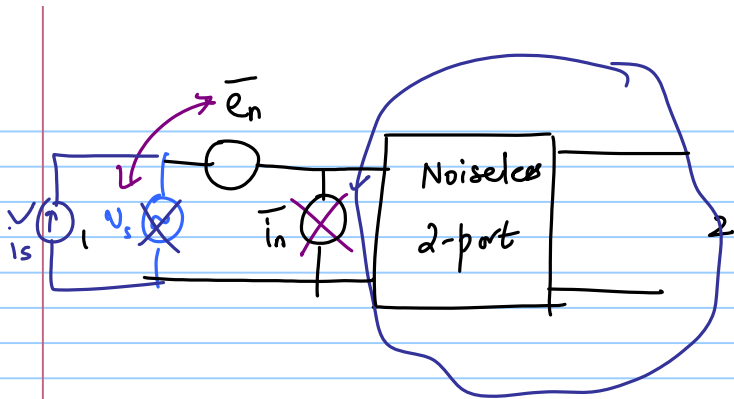HW: Calculate  $\bar{e}_n$  for this circuit using open circuit output voltage









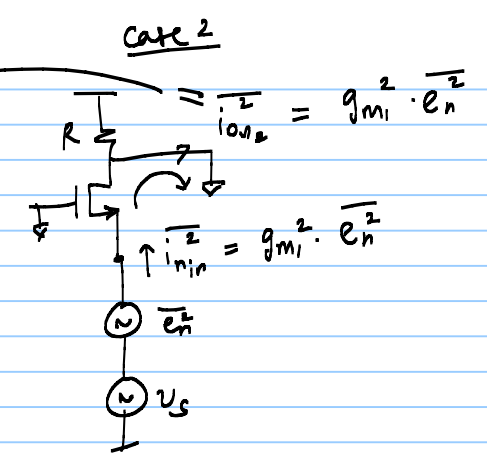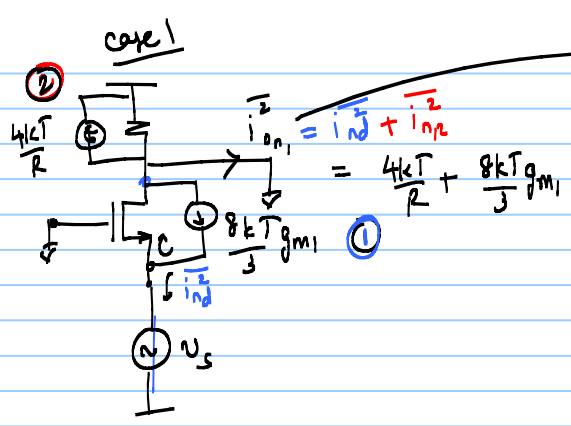

$$e_n^2 = \frac{4kT}{g_{m1}^2 \cdot R} + \frac{8kT}{3g_{m1}}$$
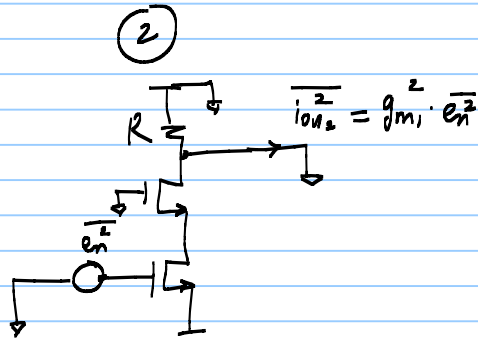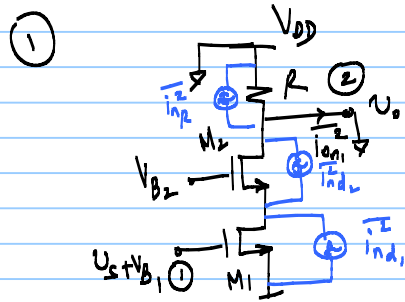
# Cascode Amplifier


$\overline{i_n} = 0$  ;  $\overline{e_n} = ?$




$$\overline{i_{o_{M1}}^2} = (R) + (M_1) + (M_2)$$

R:  $\frac{4kT}{R_1}$        $\frac{8kT}{3} g_{m1}$        $\approx 0$

M<sub>1</sub>:

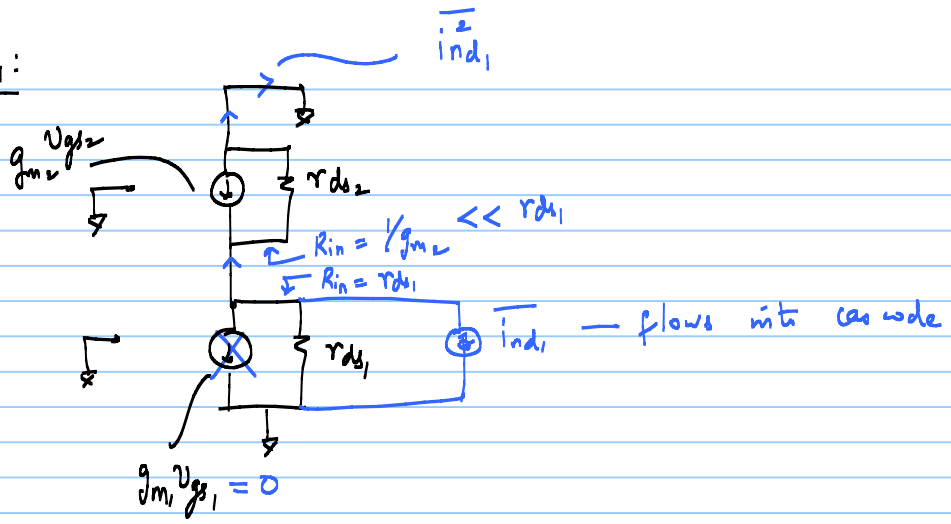

$M_z$ :

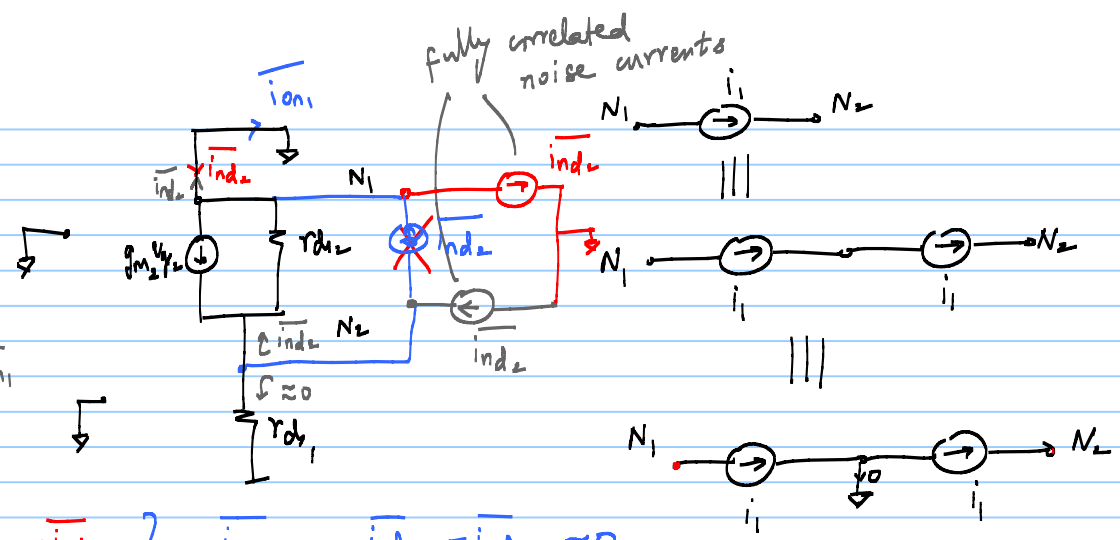

$$\overline{i_{o1}} = \overline{i_{o1}} + \overline{i_{o1}}$$


$$\left. \begin{aligned} \overline{i_{o1}} &= -\overline{i_{d2}} \\ \overline{i_{o1}} &\approx \overline{i_{d2}} \end{aligned} \right\} \begin{aligned} \overline{i_{o1}} &= \overline{i_{d2}} - \overline{i_{d2}} \approx 0 \\ &\text{total due} \\ &\text{to } M_z \end{aligned}$$

$$g_{m1}^2 \cdot \overline{e_n^2} = \frac{4kT}{R} + \frac{8kT}{3} g_{m1}$$


$$\overline{e_n^2} = \frac{4kT}{g_{m1}^2 \cdot R} + \frac{8kT}{3g_{m1}} \quad \left\{ \begin{array}{l} \text{same as} \\ \text{regular CSA} \end{array} \right\}$$

13/1/20

Lec 5

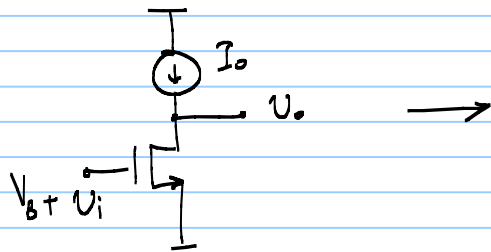

Case 1

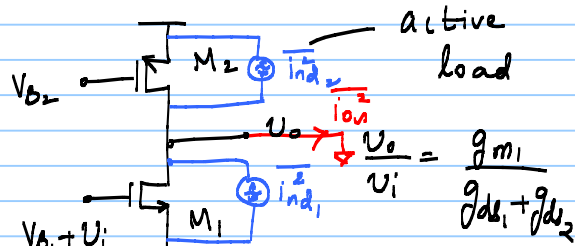


active load

$$\frac{v_o}{v_i} = \frac{g_{m1}}{g_{d1} + g_{d2}}$$

$$\overline{i_{on}^2} = \frac{8kT}{3} g_{m1} + \frac{8kT}{3} g_{m2}$$

$$\overline{e_n^2} = \frac{8kT}{3g_{m1}} + \frac{8kT}{3} \frac{g_{m2}}{g_{m1}^2}$$


Case 2


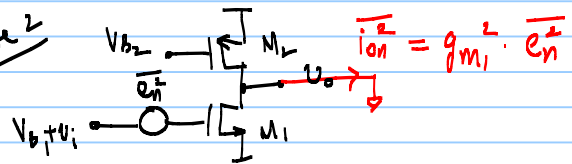


$$\overline{i_{on}^2} = g_{m1}^2 \cdot \overline{e_n^2}$$




For low noise

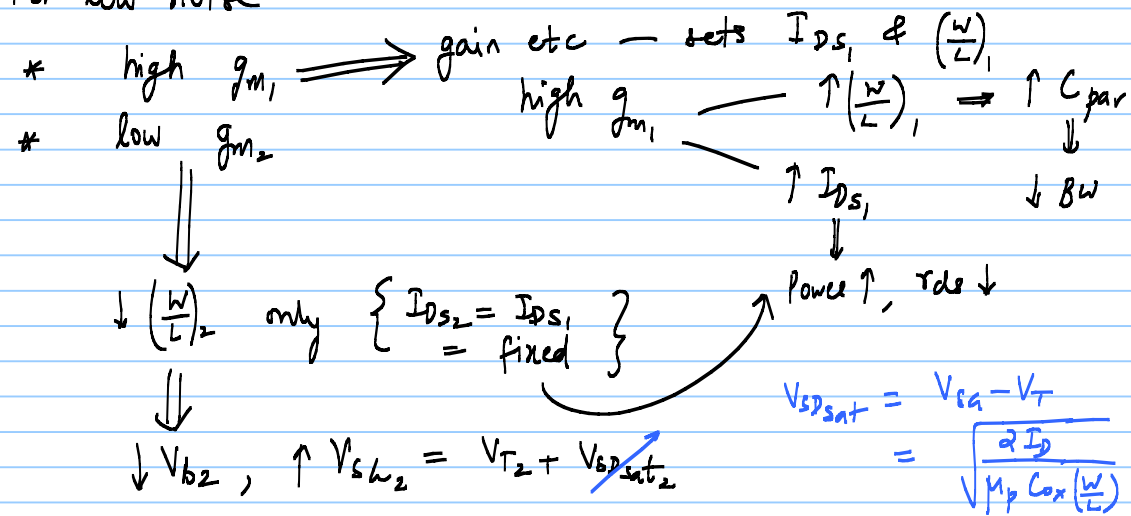

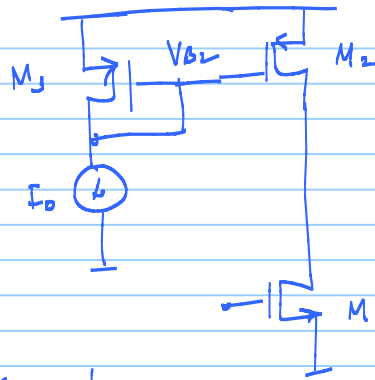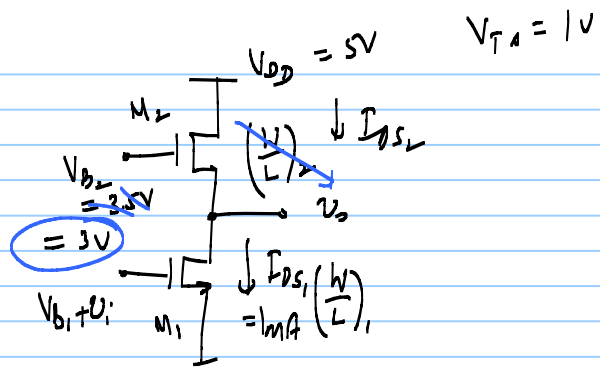

If  $I_{DS}$  is fixed  $\Rightarrow V_{B2}$  can be changed only if  $\left(\frac{w}{L}\right)_2$  is changed


Case 1

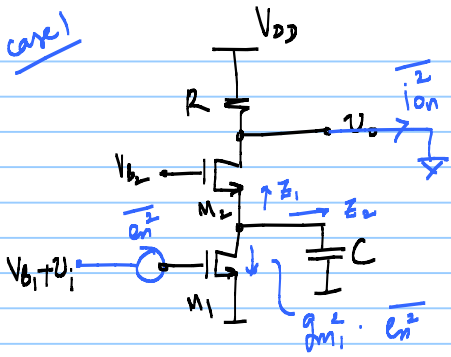

$$e_n^2 = ?$$

$$\frac{Z_2}{Z_1 + Z_2} = \frac{1/j\omega C}{1/g_{m2} + 1/j\omega C} = \frac{g_{m2}}{g_{m2} + j\omega C}$$

Case 2

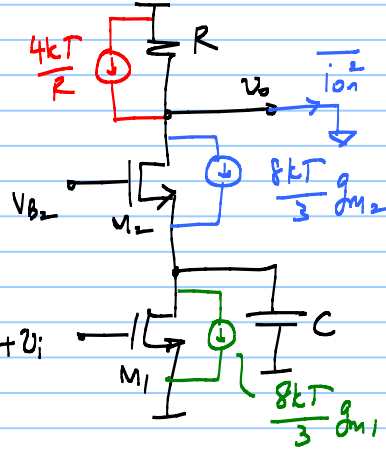

Case 1

$$\begin{aligned} \overline{i_{on}^2} &= g_{m1}^2 \cdot e_n^2 \cdot \left| \frac{Z_2}{Z_1 + Z_2} \right|^2 \\ &= g_{m1}^2 \cdot e_n^2 \cdot \frac{g_{m2}^2}{g_{m2}^2 + \omega^2 C^2} \end{aligned}$$



$$\begin{aligned} \bar{i}_{o_{n2}} &= \frac{-1/g_{m2}}{1/g_{m2} + (r_{ds1} \parallel 1/j\omega C)} \cdot \bar{i}_{d_{n2}} \\ &= \frac{-\bar{i}_{d_{n2}}}{1 + \frac{g_{m2} r_{ds1}}{1 + j\omega C r_{ds1}}} \end{aligned}$$

$$\begin{aligned} &\frac{r_{ds1} \cdot 1/j\omega C}{r_{ds1} + 1/j\omega C} \\ &= \frac{r_{ds1}}{1 + j\omega C r_{ds1}} \end{aligned}$$

$$= -\bar{i}_{d_{n2}} \cdot \frac{1 + j\omega C r_{ds1}}{(1 + g_{m2} r_{ds1}) + j\omega C r_{ds1}}$$


$$\bar{i}_{o_{n2}} = \frac{\frac{g_{m2}}{3} \bar{i}_{d_{n2}}}{(1 + g_{m2} r_{ds1})^2 + \omega^2 C^2 r_{ds1}^2}$$

$$\overline{i_{on}}^2 = \overbrace{\overline{i_{on_1}}^2}^{M_1} + \overbrace{\overline{i_{on_2}}^2}^{M_2} + \overbrace{\overline{i_{on_3}}^2}^R = g_{m_1}^2 \cdot \overline{e_n}^2 \cdot \frac{g_{m_2}^2}{g_{m_2}^2 + \omega^2 C^2}$$

$$\overline{e_n}^2 = \frac{\overline{i_{on_1}}^2 + \overline{i_{on_2}}^2 + \overline{i_{on_3}}^2}{g_{m_1}^2} \cdot \left( \frac{g_{m_2}^2 + \omega^2 C^2}{g_{m_2}^2} \right)$$




Signal

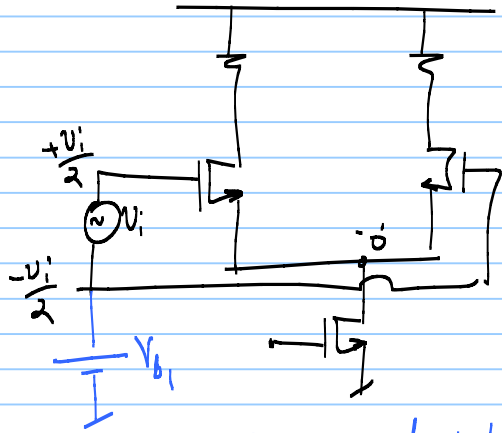

H.C. analysis ✓

Noise analysis

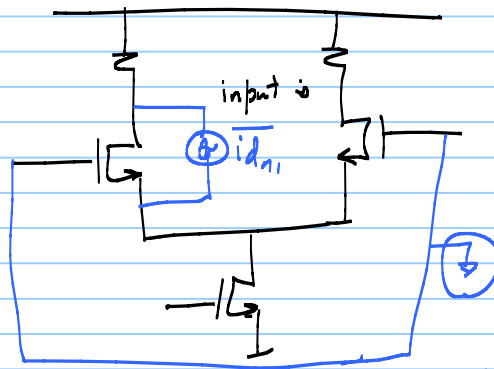


Noise sources are not  
symmetrically applied!  
No H.C. analysis!



17/1/20

Lec 6

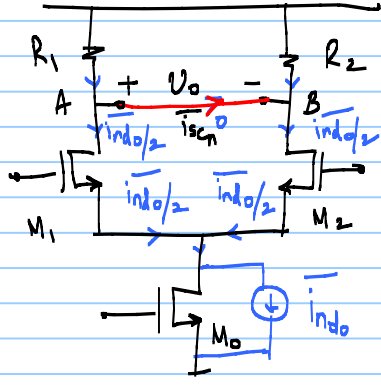

$$\overline{V_{n_a}^2}, \overline{V_{n_b}^2}$$

$$R_1 = R_2 = R$$

1) noise of  $M_0$  :

$$\overline{V_{n_a}} = -\frac{i_{nd_0}}{2} \cdot R_1$$


$$\overline{V_{n_b}} = -\frac{i_{nd_0}}{2} \cdot R_2$$

$\overline{V_{n_a}} = \overline{V_{n_b}}$   
Common mode noise

diff. output noise voltage  $\overline{V_{o,in}} = \overline{V_{n_a}} - \overline{V_{n_b}} = 0$

$\overline{i_{scn}}$  from this point onwards

2) Noise from  $R_1$ :

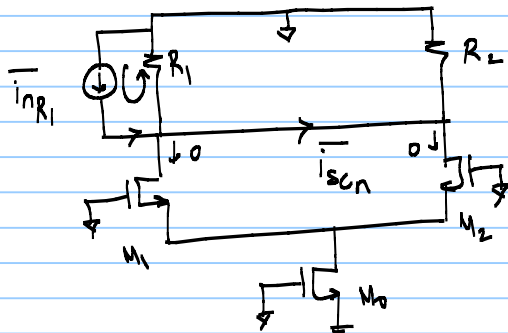


Noise from  $R_2$ :  $\frac{\overline{i_{scn}^2}}{\Delta f} = \frac{kT}{R_2}$

$$\overline{i_{scn}} = \frac{1}{2} \overline{i_{nR1}}$$


$$\frac{\overline{i_{scn}^2}}{\Delta f} = \frac{1}{4} \overline{i_{nR1}^2} = \frac{kT}{R_1}$$

Total noise PSD from resistors =  $\frac{2kT}{R}$


3) Noise from  $M_1$ :

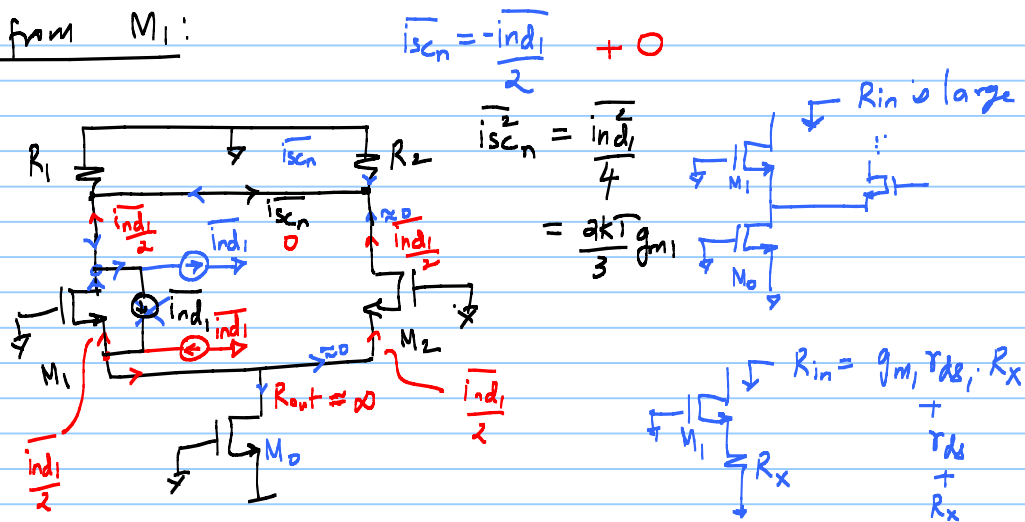


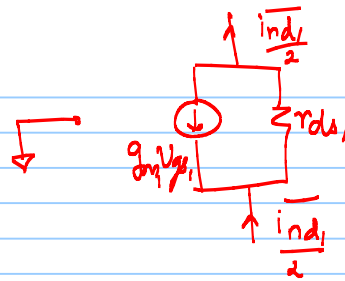Noise of  $M_2$ :  $\overline{i_{sc,n}^2} = \frac{\overline{i_{nd,n}^2}}{4} = \frac{2kT}{3} g_{m2}$


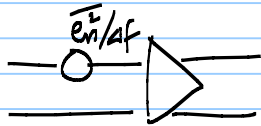
$$\frac{\overline{i_{sc,n,tot}^2}}{\Delta f} = \frac{2kT}{R} + \frac{4kT}{3} g_m$$



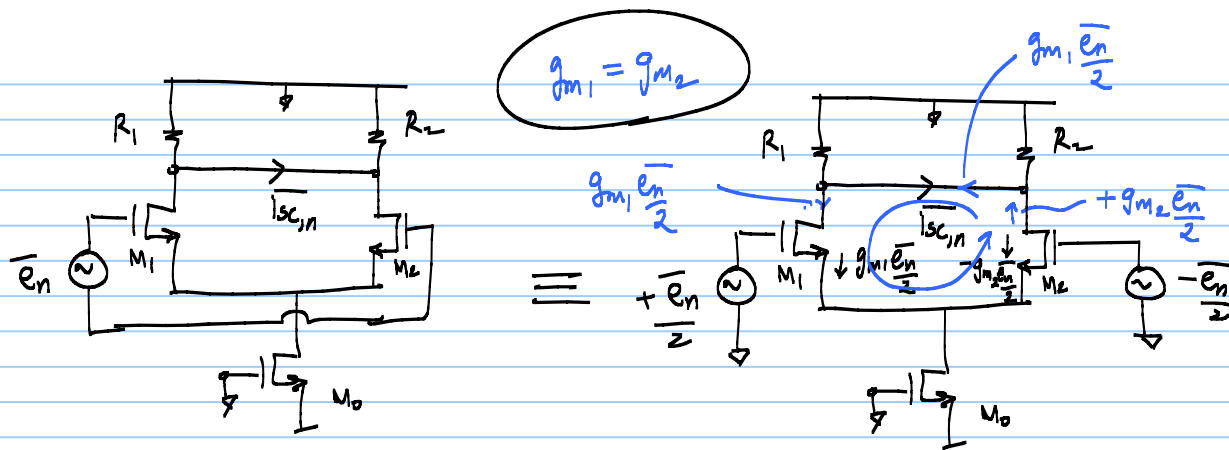

$$\bar{i}_{d1} = g_{m1} \frac{\bar{e}_n}{2} ; \quad \bar{i}_{d2} = -g_{m2} \frac{\bar{e}_n}{2}$$

$$\bar{i}_{sc,n} = -g_{m1} \frac{\bar{e}_n}{2} ; \quad \bar{i}_{sc,n}^2 = \left( \frac{g_{m1}^2}{4} \right) \cdot \frac{\bar{e}_n^2}{\Delta f}$$

Equate  $\overline{i_{scn}^2}$  in the two cases:

$$\frac{g_m^2}{4} \cdot \frac{\overline{e_n^2}}{\Delta f} = \frac{2kT}{R} + \frac{4kT}{3} g_m$$

$$\boxed{\frac{\overline{e_n^2}}{\Delta f} = \frac{8kT}{g_m^2 R} + \frac{16kT}{3g_m}}$$




↔ compare with  $\overline{e_n}$  of CSA:

$$\frac{4kT}{g_m^2 R} + \frac{8kT}{3g_m}$$

low noise:  $\uparrow g_m$ ,  $\uparrow g_m R$

hw: calculate  $\overline{V_{on}^2}$  instead of  $\overline{i_{scn}^2}$


Mismatch

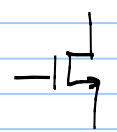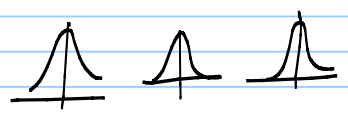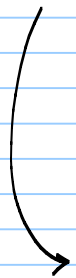

$\mu_n, C_{ox}, V_T \dots$



process variations  
temperature varies etc.

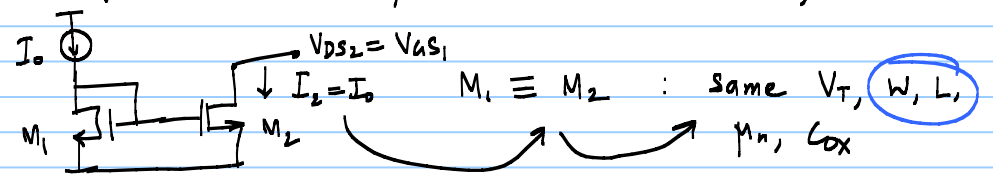2 quantities are expected to be identical, but are not.




$W, L \rightarrow$  design parameters {expected to be equal}

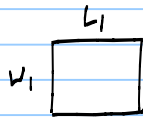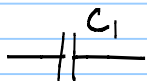$\mu_n, C_{ox}, V_T \rightarrow$  process parameters




$$W_1 L_1 = W_2 L_2$$

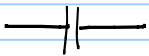



$C_2$

$$C_1 = C_2$$

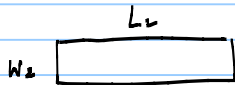

$$C = \frac{C_{ox} k A}{d}$$



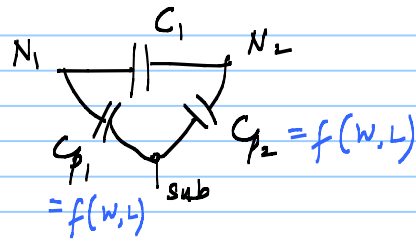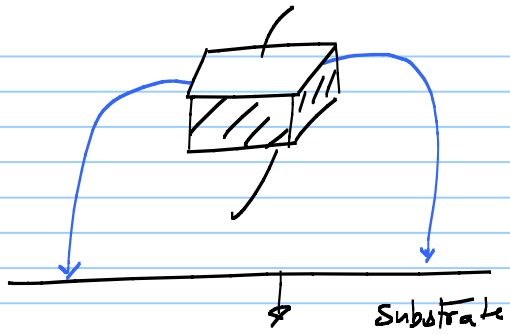



Mismatch 
→ Systematic  
→ Random

20/1/20

### Lec 7


#### Systematic mismatch

e.g. Resistor

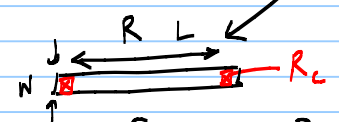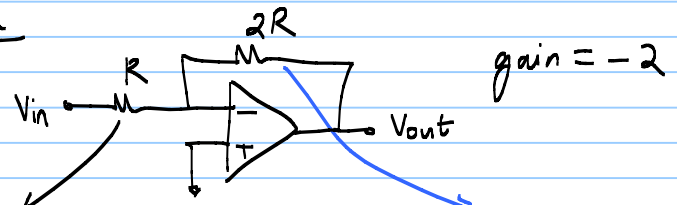


$$R = \left\{ \begin{array}{l} \text{sheet} \\ \text{resistance} \end{array} \right\} \times \left[ \# \text{ of } \square \right]$$

actual Resistance =  $R + 2R_c$

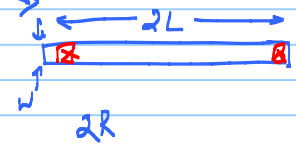



Actual res.  
 $= 2R + 2R_c$   
 $\neq 2 \times \text{resistance}$

Build  $2R$ :

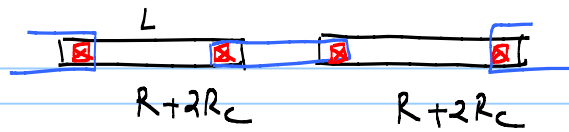
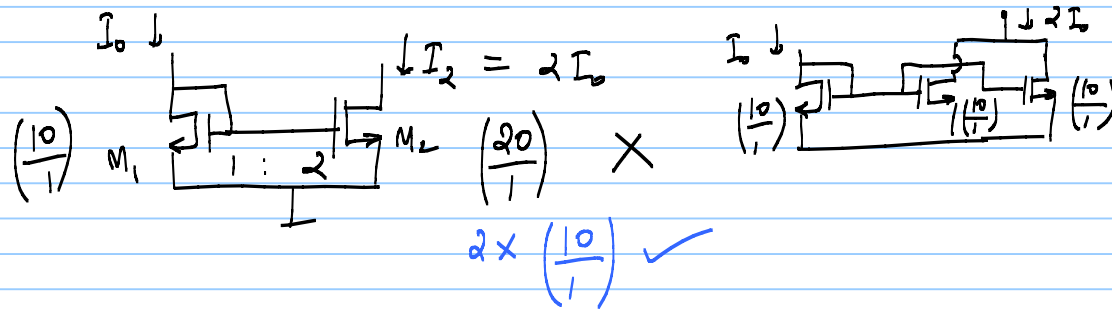
$$\text{total res.} = 2R + 4R_c = 2(R + 2R_c)$$




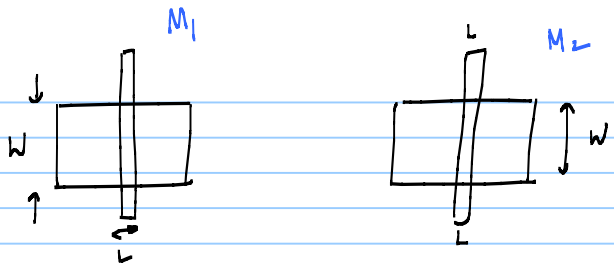

→ T gradient  $\Rightarrow$  properties of  $M_1$  &  $M_2$  will be different



\* place devices as close as possible to each other

T grad. →

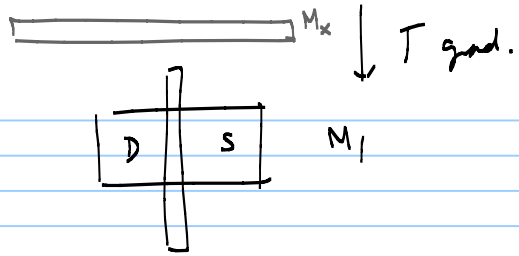


Make  $M_1$  &  $M_2$

Feel same

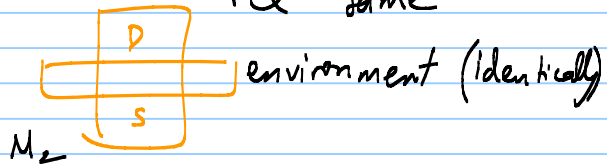
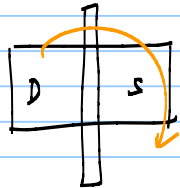


environment (identically)




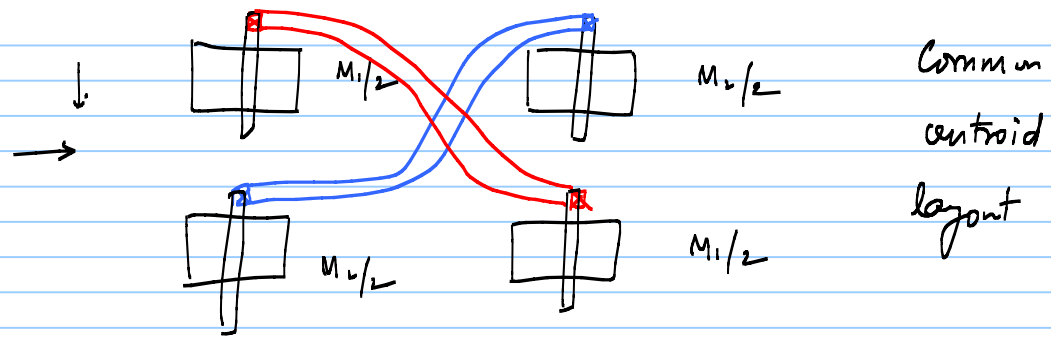

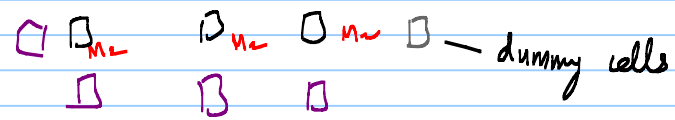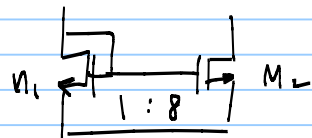$w_f$       width / finger  
 $N_f$       # of fingers  
 ...



## Random mismatch

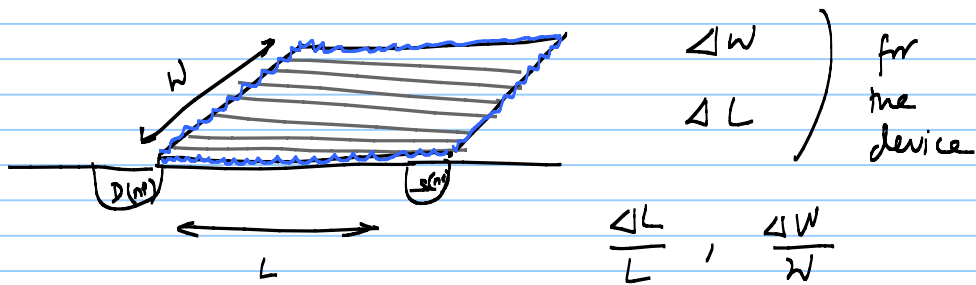

Similar effects for  $R, C, V_T, \dots$

\* Mean = 0,  $\sigma$  describes statistical effects



$$\sqrt{V_T} = \frac{A_{V_T}}{\sqrt{W \cdot L}}$$

empirical parameter

$V_T =$  threshold voltage

$$\sqrt{\beta} = \frac{A_{\beta}}{\sqrt{W \cdot L}}$$

$\beta = \mu C_{ox}$

$$\sqrt{\frac{\Delta R}{R}} = \frac{A_R}{\sqrt{W_R \cdot L_R}}$$

$$\sqrt{\frac{\Delta C}{C}} = \frac{A_C}{\sqrt{W_C \cdot L_C}}$$

Low mismatch (low  $\sigma$ )



\*  $\uparrow W, L \Rightarrow \downarrow \sigma$



\* Area is traded off

with mismatch


\* as Area  $\uparrow$ , distance between devices  $\uparrow$
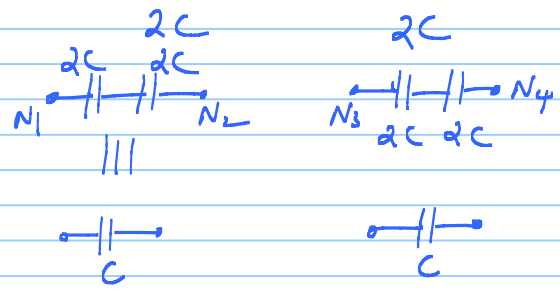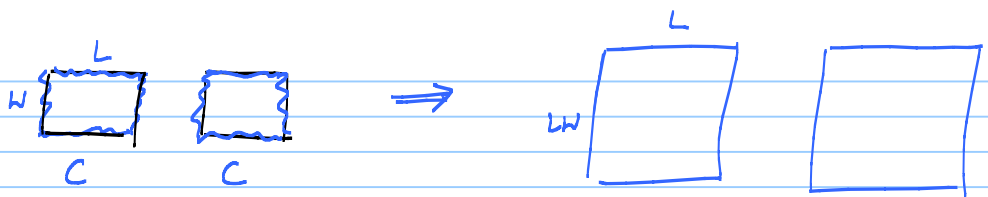
$$\sqrt{\frac{\Delta W/L}{W/L}} = \frac{A_{W/L}}{\sqrt{W \cdot L}}$$



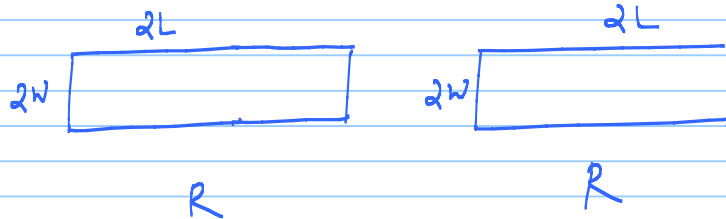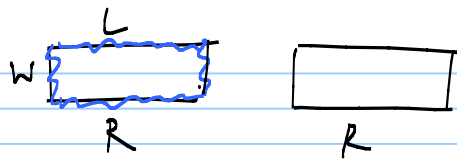

# of  $\square$  is the same

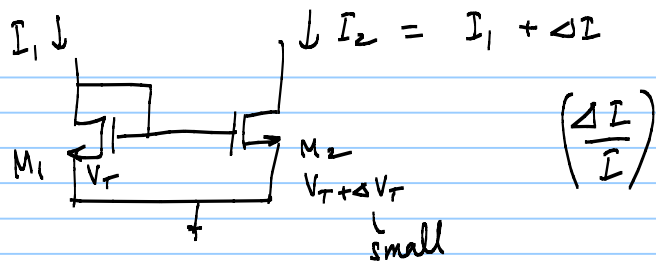

$$\frac{\partial I_D}{\partial V_{GS}} = g_m$$

$$\frac{\partial I_D}{\partial V_T} = -\frac{\partial I_D}{\partial V_{GS}} = -g_m$$

Consider only  $V_T$  mismatch

$$I_D = \frac{1}{2} \mu C_{OX} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2$$

$$\Delta I = \frac{\partial I_D}{\partial V_T} \cdot \Delta V_T = -g_m \cdot \Delta V_T \quad \checkmark$$

$$\sigma_{\Delta I}^2 = g_m^2 \cdot \sigma_{V_T}^2$$

$$\sqrt{\frac{\Delta I}{I}} = \frac{g_m}{I_D} \cdot \sqrt{V_T}$$

nominal

$$g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)$$


$$= \frac{2 I_D}{V_{GS} - V_T} \leftarrow$$

$$= \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right) \cdot I_D}$$

$$\frac{g_m}{I_D} = \frac{4}{V_{DSAT}}$$


$$\sqrt{\frac{\Delta I}{I}} = \frac{\frac{4}{2}}{V_{\text{dsat}}} \cdot \frac{A V_T}{W \cdot L}$$

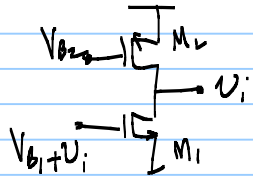larger  $V_{\text{dsat}} \leftrightarrow$  smaller  $\frac{\Delta I}{I}$



No matching  
considerations

Diff.  
Amplifier

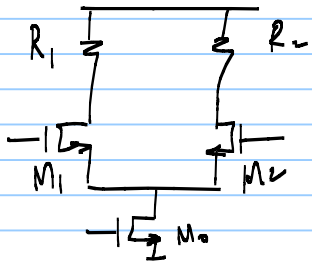

$$M_1 \equiv M_2$$

$$R_1 \equiv R_2$$

$$\bar{I}_{as} = 0$$

Diff. circuit




pull out all mismatches  
as input-referred quantities



input-referred  
offset voltage

$\bar{V}_{os}$


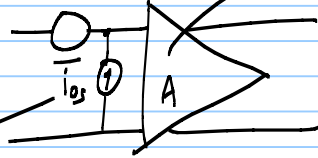


No mismatch


input-referred  
offset current

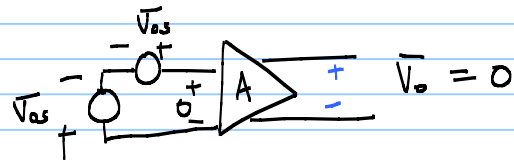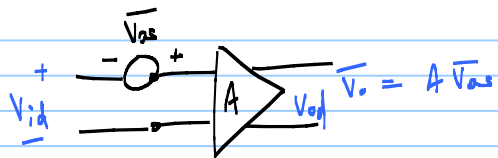$\bar{V}_{os}$  &  $\bar{I}_{os}$   $\rightarrow$  statistical  
quantities





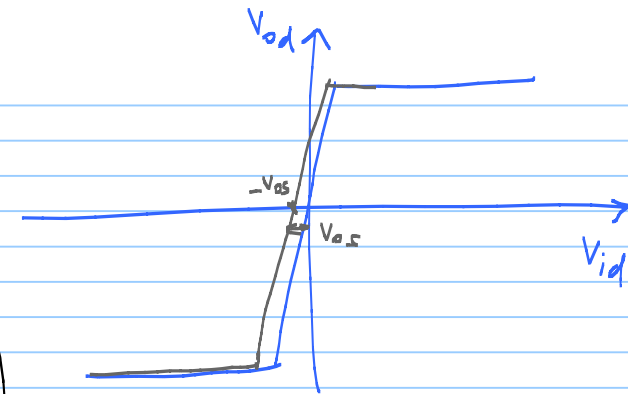
input-referred  
 offset voltage  $\bar{V}_{os}$   
 = voltage that is  
 applied at input so that  
 output voltage offset is  
 zero



23/01/2020

Lec 8

E.g. 1

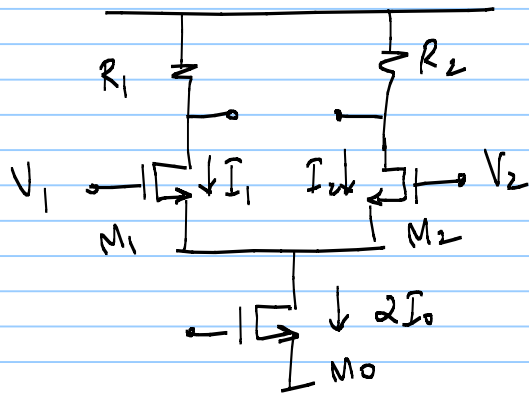

$$R_1 \neq R_2, V_{T1} \neq V_{T2}, \left(\frac{W}{L}\right)_1 \neq \left(\frac{W}{L}\right)_2$$

$$V_{as} = ?$$

$$\rightarrow I_1 \neq I_2$$

$$V_1 - V_2 = V_{as1} - V_{as2} \quad \text{--- (1)}$$

$$I_1 R_1 = I_2 R_2 \quad \text{--- (2)}$$

{output  
offset=0}

$$R = \frac{R_1 + R_2}{2} ; \quad \Delta R = \frac{R_1 - R_2}{2}$$

$$R_1 = R + \Delta R ; \quad R_2 = R - \Delta R$$

$$I = \frac{I_1 + I_2}{2} ; \quad \Delta I = \frac{I_1 - I_2}{2}$$

$$I_1 = I + \Delta I ; \quad I_2 = I - \Delta I$$

$$\left( \frac{W}{L} \right) = \frac{\left( \frac{W}{L} \right)_1 + \left( \frac{W}{L} \right)_2}{2}$$

$$\Delta \left( \frac{W}{L} \right) = \frac{\left( \frac{W}{L} \right)_1 - \left( \frac{W}{L} \right)_2}{2}$$

$$I_1 R_1 = I_2 R_2$$

$$(I + \Delta I)(R + \Delta R) = (I - \Delta I)(R - \Delta R)$$

$$\left(1 + \frac{\Delta I}{I}\right) \left(1 + \frac{\Delta R}{R}\right) = \left(1 - \frac{\Delta I}{I}\right) \left(1 - \frac{\Delta R}{R}\right)$$

$$1 + \frac{\Delta I}{I} + \frac{\Delta R}{R} + \frac{\Delta I \Delta R}{IR} = 1 - \frac{\Delta I}{I} - \frac{\Delta R}{R} + \frac{\Delta I \Delta R}{IR}$$

$$\frac{\Delta I}{I} = \frac{-\Delta R}{R}$$

$$I_D = \frac{\beta}{2} (V_{GS} - V_{T1})^2$$
$$\beta = \mu C_{OX}$$

$$V_1 - V_2 = V_{GS1} - V_{GS2}$$
$$= V_{T1} + \sqrt{\frac{2I_1}{\beta \left(\frac{W}{L}\right)_1}} - \left[ V_{T2} + \sqrt{\frac{2I_2}{\beta \left(\frac{W}{L}\right)_2}} \right]$$

$$V_1 - V_2 = \Delta V_T + \sqrt{\frac{2}{\beta}} \left[ \sqrt{\frac{I + \Delta I}{\left(\frac{W}{L}\right) + \Delta\left(\frac{W}{L}\right)}} - \sqrt{\frac{I - \Delta I}{\left(\frac{W}{L}\right) - \Delta\left(\frac{W}{L}\right)}} \right]$$

$$= \Delta V_T + \sqrt{\frac{2I}{\beta\left(\frac{W}{L}\right)}} \cdot \left[ \sqrt{\frac{1 + \Delta I/I}{1 + \frac{\Delta(W/L)}{W/L}}} - \sqrt{\frac{1 - \Delta I/I}{1 - \frac{\Delta(W/L)}{W/L}}} \right]$$

$$= \Delta V_T + V_{Dsat} \left[ \left(1 + \frac{\Delta I}{2I}\right) \left(1 - \frac{\Delta(W/L)}{2(W/L)}\right) - \left(1 - \frac{\Delta I}{2I}\right) \left(1 + \frac{\Delta(W/L)}{2(W/L)}\right) \right]$$


$$V_1 - V_2 = \Delta V_T + V_{Dsat} \left[ \left( \frac{\Delta I}{I} \right) - \frac{\Delta(W/L)}{(W/L)} \right] \rightarrow \text{true for all } V_1, V_2$$

$$= \Delta V_T + V_{Dsat} \left[ \frac{-\Delta R}{R} - \frac{\Delta(W/L)}{(W/L)} \right]$$

$$V_1 - V_2 = V_{os} \text{ if output offset} = 0$$

$$V_{os} = \Delta V_T - V_{Dsat} \left[ \frac{\Delta R}{R} + \frac{\Delta(W/L)}{(W/L)} \right] \leftarrow \sqrt{V_{os}^2}$$

E.g. 2

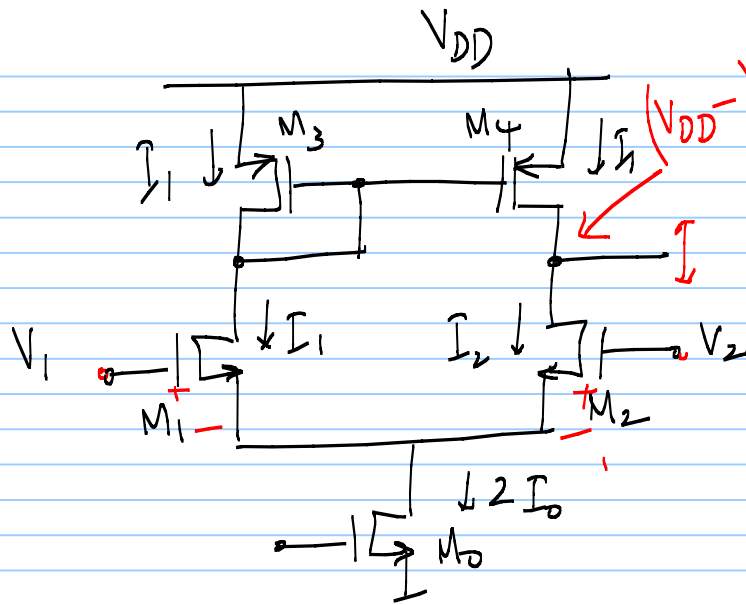


$(V_{DD} - V_{S434}) \quad V_{T1} - V_{T2} = \Delta V_{T12}$

~~$V_{T3} - V_{T4} = \Delta V_{T34}$~~  ✓

$V_{OS} = ?$

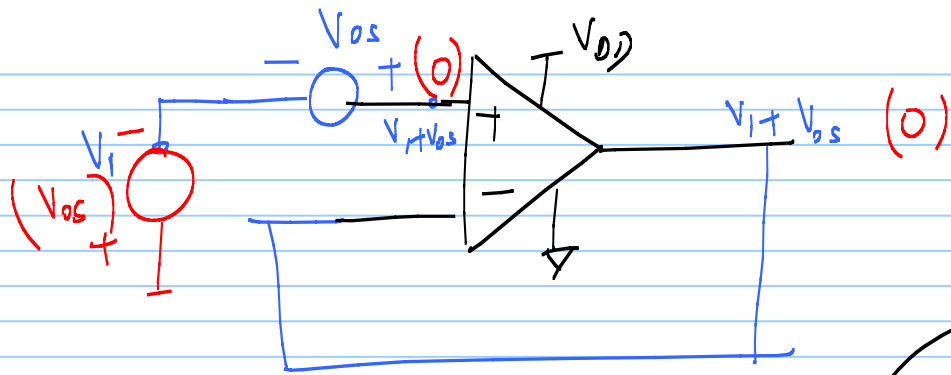- \*  $V_1 - V_2 = 0$
- \*  $V_{GS1} = V_{GS2}$
- \*  $I_1 = I_0 + \Delta I$
- $= I_0 - g_m \frac{\Delta V_{T12}}{2}$
- \*  $I_2 = I_0 - \Delta I$






$2\Delta I$  flows into  $r_{out} \parallel r_{ds3} \parallel r_{ds4}$

$$\Delta V_{out} = 2\Delta I \cdot r_{out} \checkmark$$

$$V_{os} = \Delta V_{in} = -\frac{2\Delta I \cdot r_{out}}{g_m}$$

$$= -\frac{2\Delta I}{g_m} = \Delta V_{T12}$$

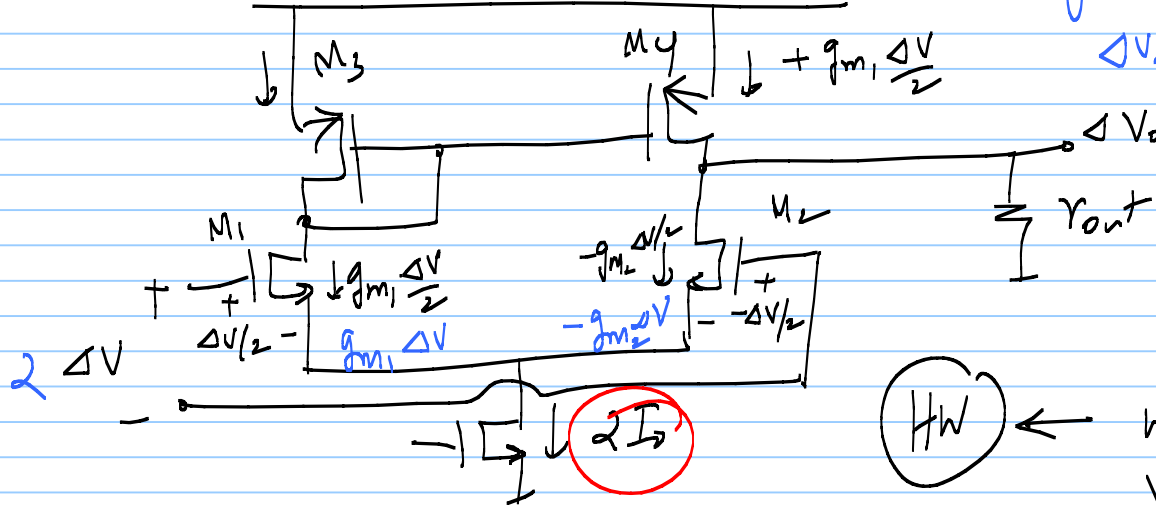apply  $V_{os}$  so that  $\Delta V_{out} = 0$



$$\text{gain} = \frac{\Delta V_o}{2 \Delta V} = g_m r_{out}$$

$$\Delta V_o = 2 g_m r_{out} \Delta V$$

$$\Delta V_o = g_m r_{out} \Delta V$$

$$\text{gain} = \frac{\Delta V_o}{\Delta V} = g_m r_{out}$$

HW


with  $\Delta V_{T3,4}$ ,  
 $V_{os} = ?$

24/1/20


## Lec 9
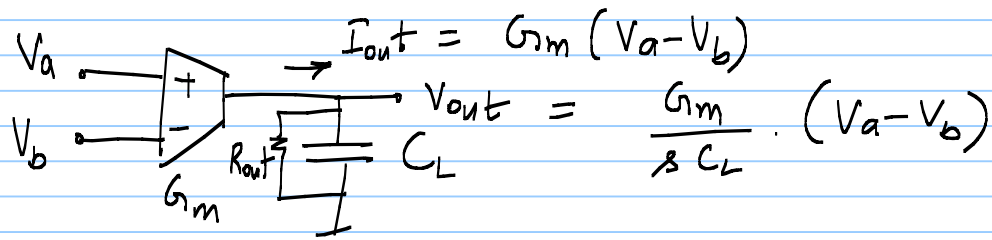
### One-stage Opamp

$$\frac{V_{out}}{V_{id}}(s) = \frac{\omega_u}{s}$$



$$\omega_u = \frac{G_m}{C_L}$$

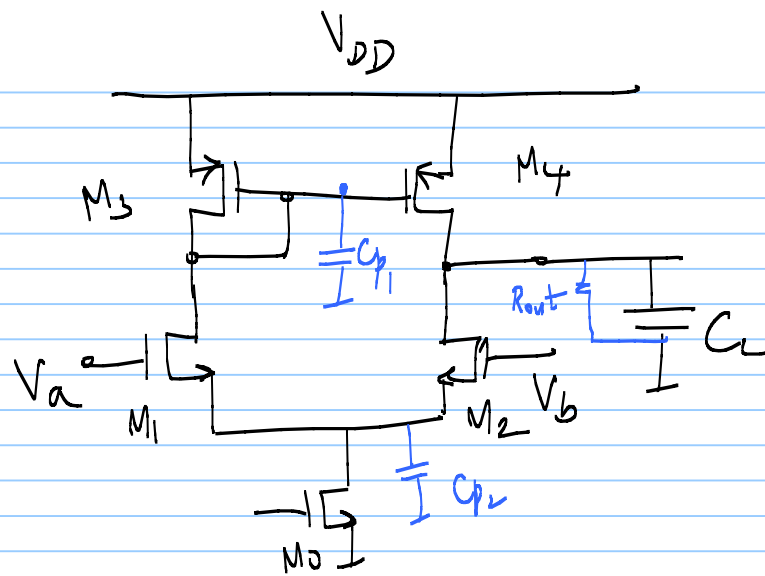


### Data sheet

1) DC gain =  $g_{m1} \overbrace{(r_{ds2} || r_{ds4})}^{R_{out}}$

2)  $G_m = g_{m1}$

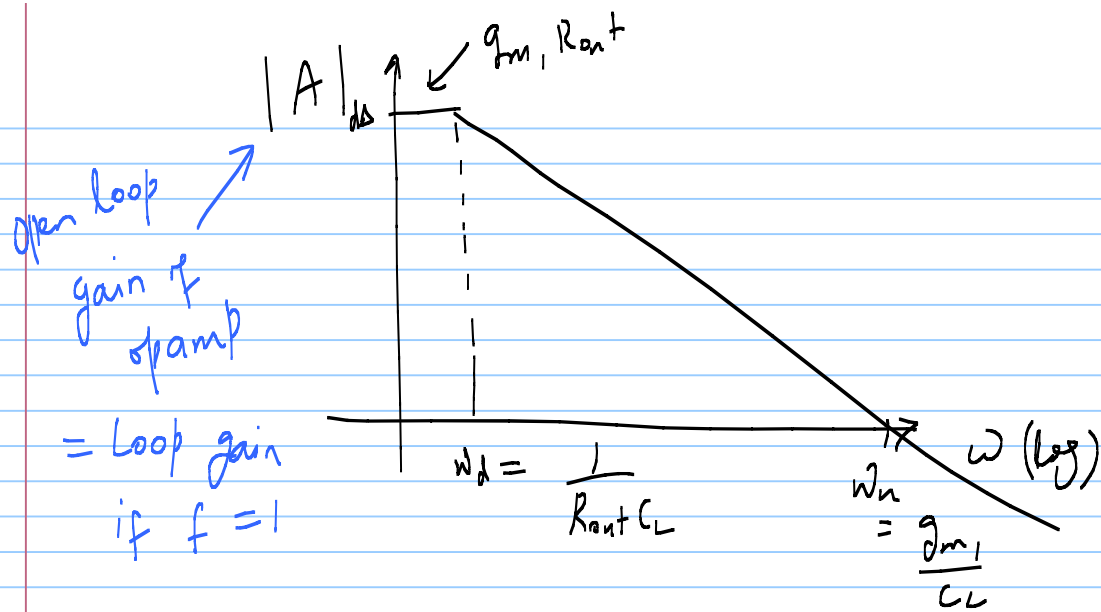3)  $\omega_u = \frac{g_{m1}}{C_L}$  ;


Dominant pole @  $\omega_d = \frac{1}{R_{out} C_L}$



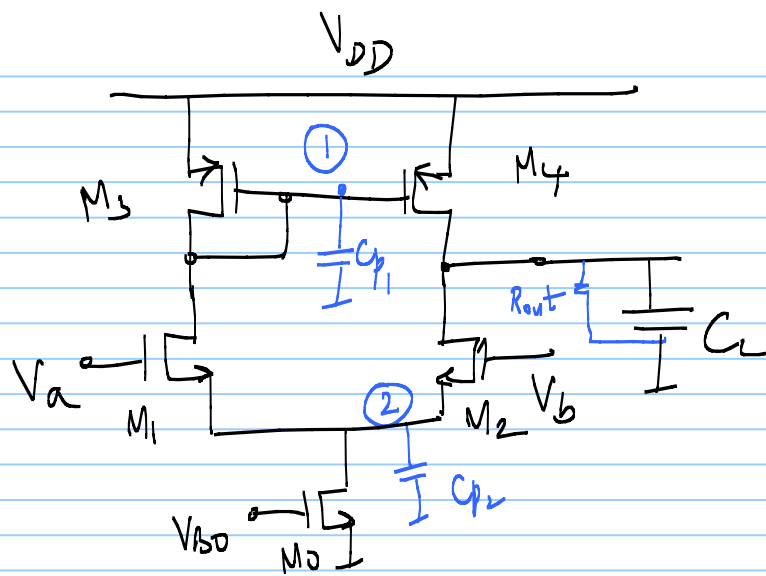4) Non-dominant poles & zeroes?

$$\omega_{p2} = \frac{-g_{m3}}{C_{p1}}$$


$$\omega_z = -\frac{2g_{m3}}{C_{p1}} = 2\omega_{p2}$$



\* Node ② = Virtual ground,  $C_{p2}$  does not affect differential mode operation  
 $C_{p2}$  will affect CM gain & CMRR

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right|$$

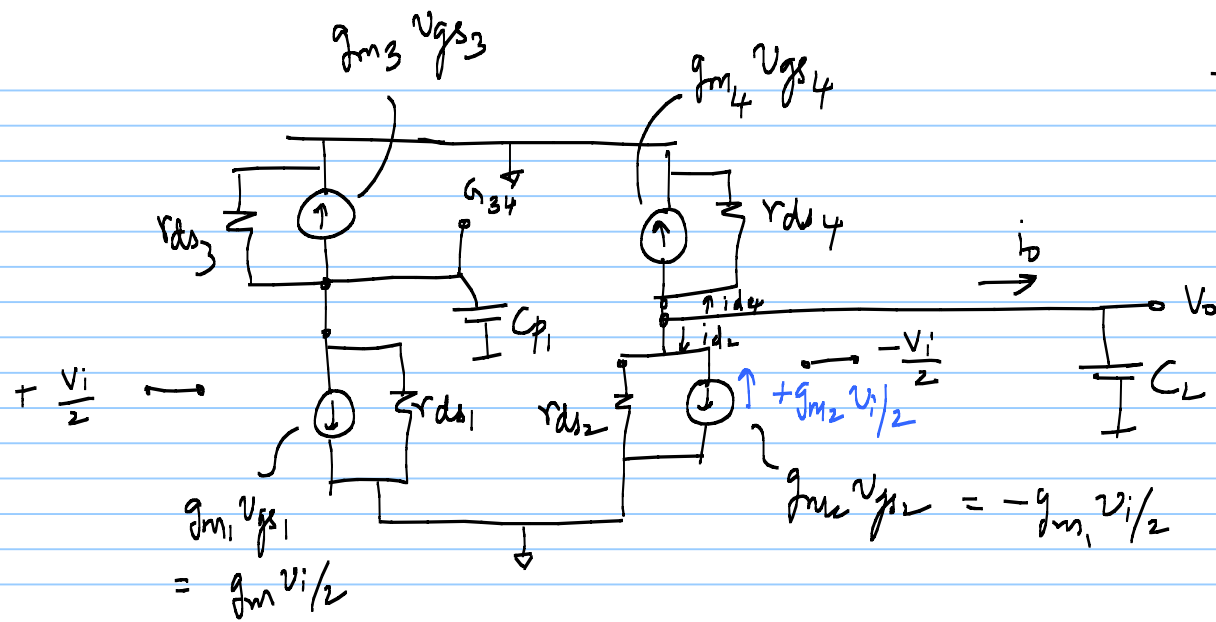\* Node 1 :  $C_{p1}$  could affect  $A_{dm}$



$$\frac{V_o}{V_i}(s) = ?$$

$$i_o = -(i_{d2} + i_{d4})$$

$$= -(g_{m2} v_{gs2} + g_{m4} v_{gs4}) \cdot (r_{ds2} \parallel r_{ds4})$$


$$\frac{-(g_{m2} v_{gs2} + g_{m4} v_{gs4}) \cdot (r_{ds2} \parallel r_{ds4})}{(r_{ds2} \parallel r_{ds4}) + \frac{1}{sC_L}}$$

$$i_o = \left[ - \left( -g_{m2} \frac{v_i}{2} \right) - \left( g_{m4} v_{gs4} \right) \right] \cdot \frac{R_{out}}{R_{out} + \frac{1}{sC_L}}$$

$$v_{gs4} = v_{gs3}$$

assume  $r_{ds1}, r_{ds3} \gg 1/g_{m3}$

$g_m, v_{gs1}$

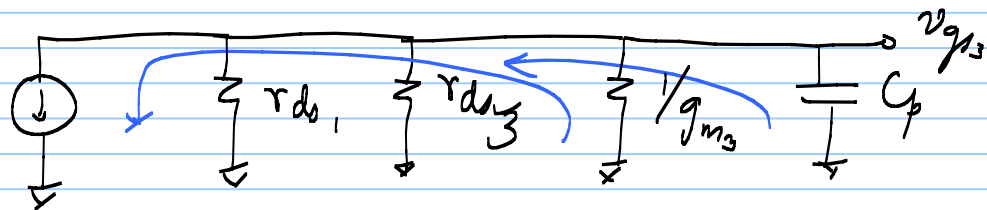



$$v_{gs3} = -g_{m1} \frac{v_i}{2} \times \left( \frac{1}{g_{m3}} \parallel \frac{1}{sC_{p1}} \right)$$

$$= -g_{m1} \frac{v_i}{2} \cdot \frac{\frac{1}{g_{m3}} \times \frac{1}{sC_{p1}}}{\frac{1}{g_{m3}} + \frac{1}{sC_{p1}}} = -g_{m1} \frac{v_i}{2} \frac{1}{g_{m3} + sC_{p1}} = v_{gs4}$$


$$g_{m4} v_{gs4} = -g_{m1} \frac{v_i}{2} \cdot \left( \frac{g_{m4}}{g_{m3} + sC_{p1}} \right)$$

$$i_o = \left[ g_{m2} \frac{v_i}{2} + g_{m1} \frac{v_i}{2} \cdot \left( \frac{g_{m4}}{g_{m3} + sC_{p1}} \right) \right] \frac{R_{out}}{R_{out} + \frac{1}{sC_L}}$$

$$g_{m1} = g_{m2} ; g_{m3} = g_{m4}$$

$$i_o = \frac{g_{m1} v_i}{2} \left[ 1 + \frac{g_{m4}}{g_{m3} + sC_{p1}} \right] = \frac{sC_L R_{out}}{1 + sC_L R_{out}}$$
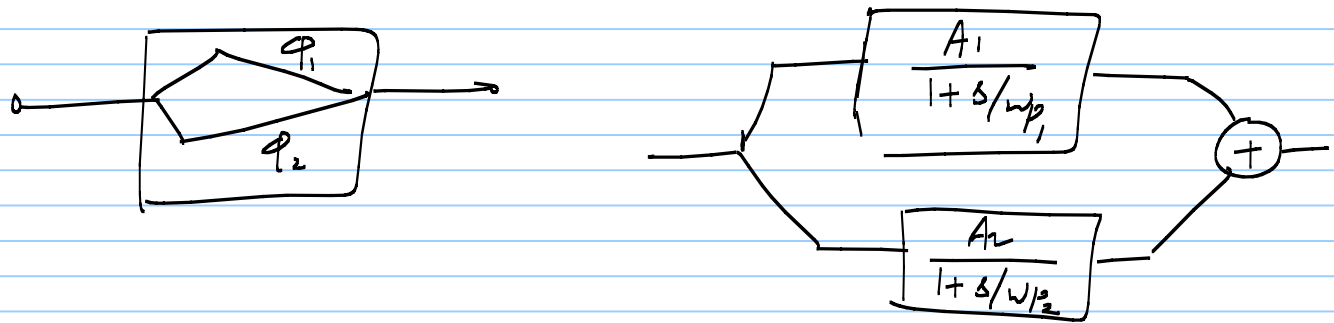
$$V_o = i_o \cdot \frac{1}{sC_L} = \frac{g_{m1} v_i}{2} \cdot \frac{R_{out}}{1 + sC_L R_{out}} \cdot \frac{2g_{m3} + sC_{p1}}{g_{m3} + sC_{p1}}$$





$$\frac{V_o}{V_i}(s) = (D(\text{gain})) \frac{(1 + s/w_z)}{\left(1 + \frac{s}{w_{p1}}\right) \left(1 + \frac{s}{w_{p2}}\right)} \quad w_z = 2w_{p2}$$

$$= g_{m1} R_{out} \cdot \frac{\left(1 + \frac{s}{(2g_{m3}/C_{p1})}\right)}{\left(1 + \frac{s}{(1/C_L R_{out})}\right) \left(1 + \frac{s}{g_{m3}/C_{p1}}\right)}$$

$$\frac{1}{2} \cdot \frac{2g_{m3} + \frac{1}{2}sC_{p1}}{g_{m3} + sC_{p1}} = \frac{1 + \frac{sC_{p1}}{2g_{m3}}}{1 + sC_{p1}/g_{m3}} \quad w_z = -\frac{2g_{m3}}{C_{p1}}; \quad w_{p1} = -\frac{1}{R_{out}C_L}; \quad w_{p2} = -\frac{g_{m3}}{C_{p1}}$$



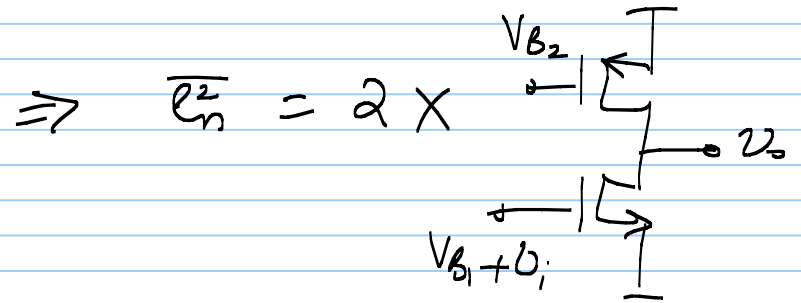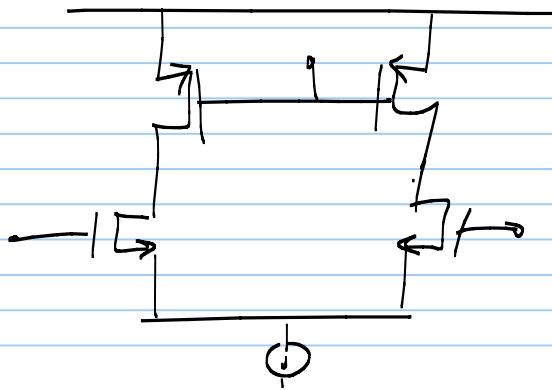7) Noise :  $\bar{i}_n = 0$   
 $\overline{e_n^2} = \text{HW}$






8) Offset

$$V_{os} = \Delta V_{T,1,2} + \frac{g_{m3}}{g_{m1}} \cdot \Delta V_{T,3,4}$$



$$\sigma_{os}^2 = \sigma_{V_{T,1,2}}^2 + \left( \frac{g_{m3}}{g_{m1}} \right)^2 \sigma_{V_{T,3,4}}^2$$

large  $W_1, L_1, W_2, L_2$   
also reduces flicker noise

9) Slew Rate :

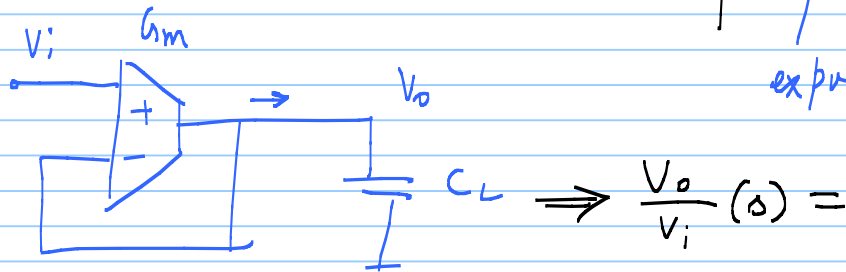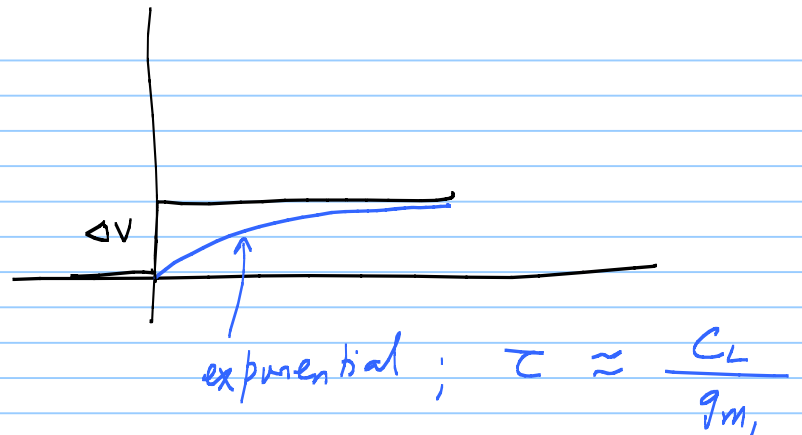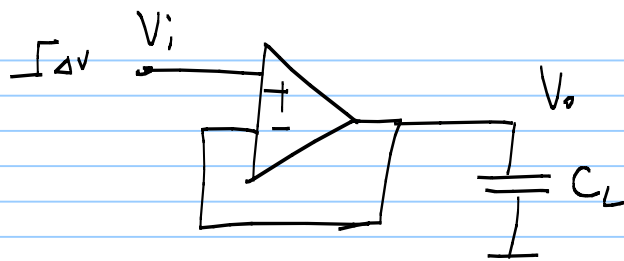





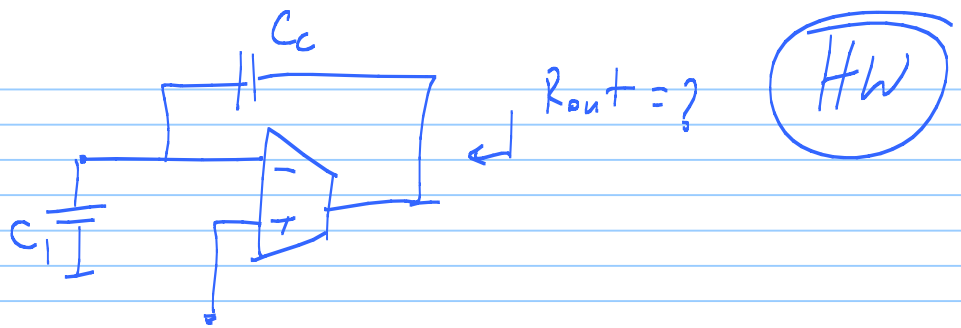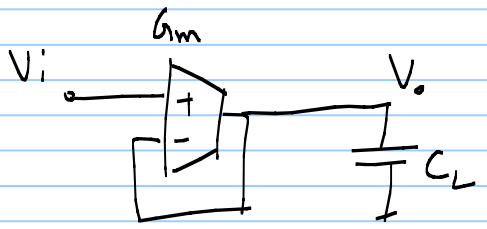

$$(V_i - V_o) \cdot G_m = V_o \cdot s C_L$$
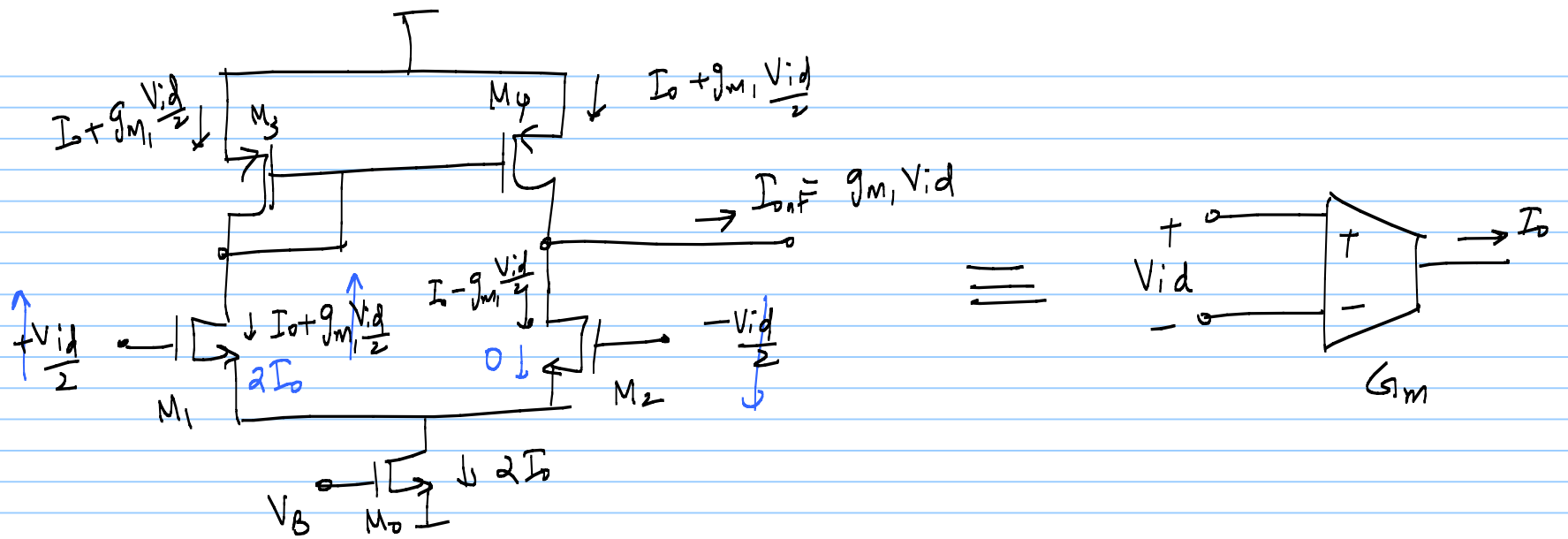
$$\frac{V_o}{V_i}(s) = \frac{1}{1 + s C_L / G_m} \rightarrow \tau = \frac{C_L}{G_m}$$




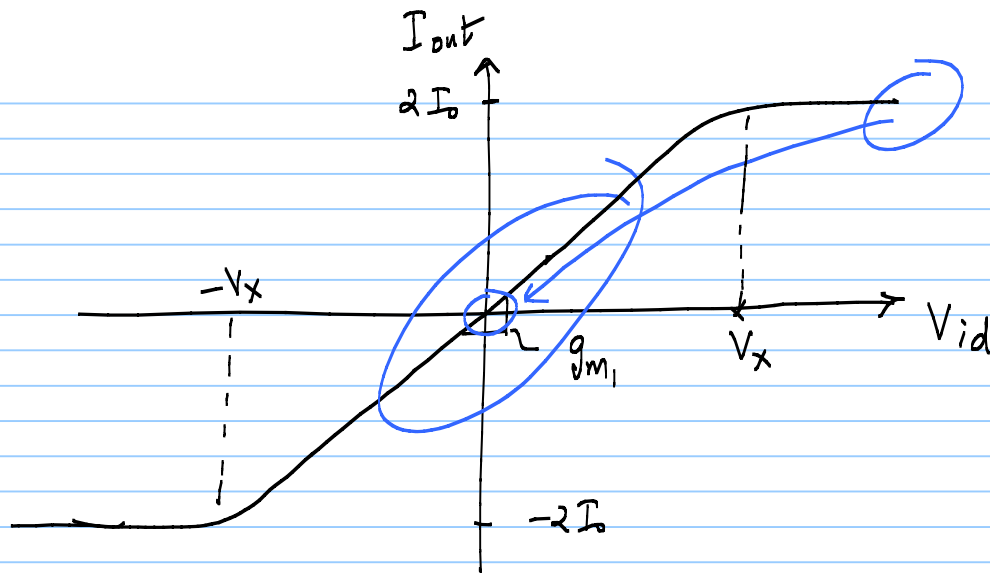

If  $\Delta V$  (or  $V_{id}$ )  $> V_x$ ,

$$I_{out} = 2I_0$$

$$\text{slope} = 0 \quad \{G_m = 0\}$$

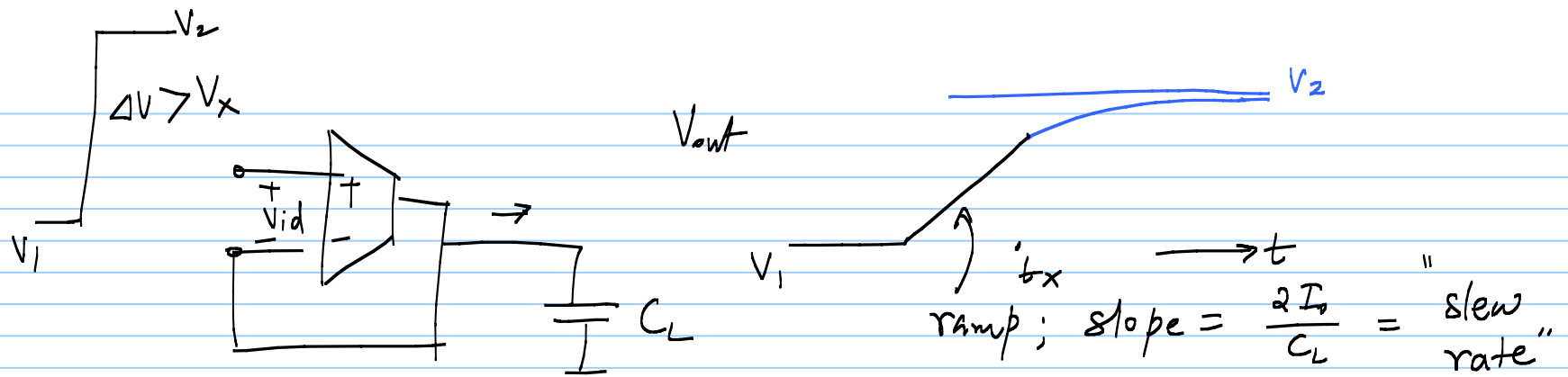


(a)  $t = 0^+$ ,  $V_{id} = \Delta V$  ;  $I_{out} = 2I_o$  ;  $V_{out} = \text{ramp} @ \frac{2I_o}{C_L}$   
 at  $t = t_x$ ,  $\Delta V < V_x$



28/1/20

Lec 10

Telescopic Opamp

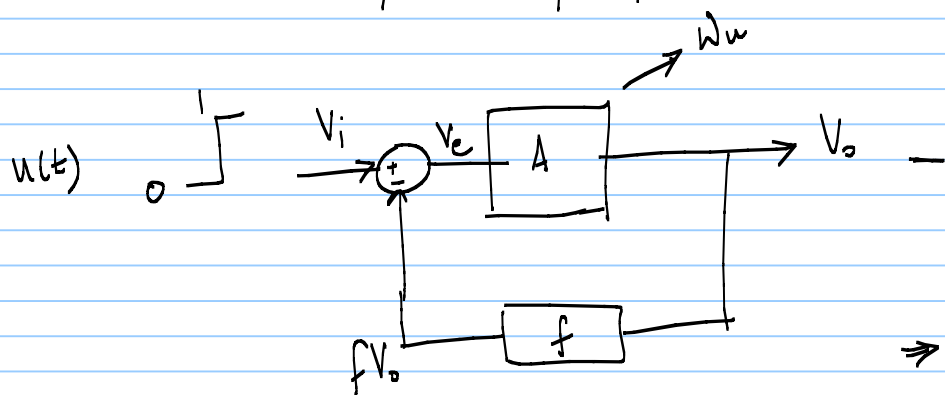


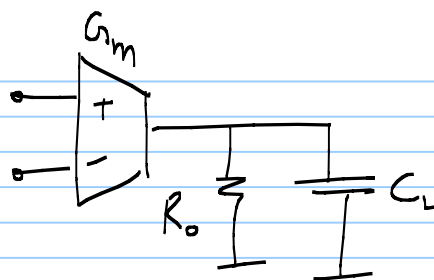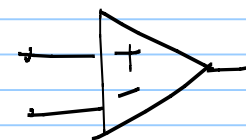
$$V_e(\infty) = 0$$
$$\Rightarrow V_o(\infty) = V_i(\infty) / f = \frac{1}{f} V$$



⇒ 1) Closed loop gain =  $\frac{1}{f}$  in steady state

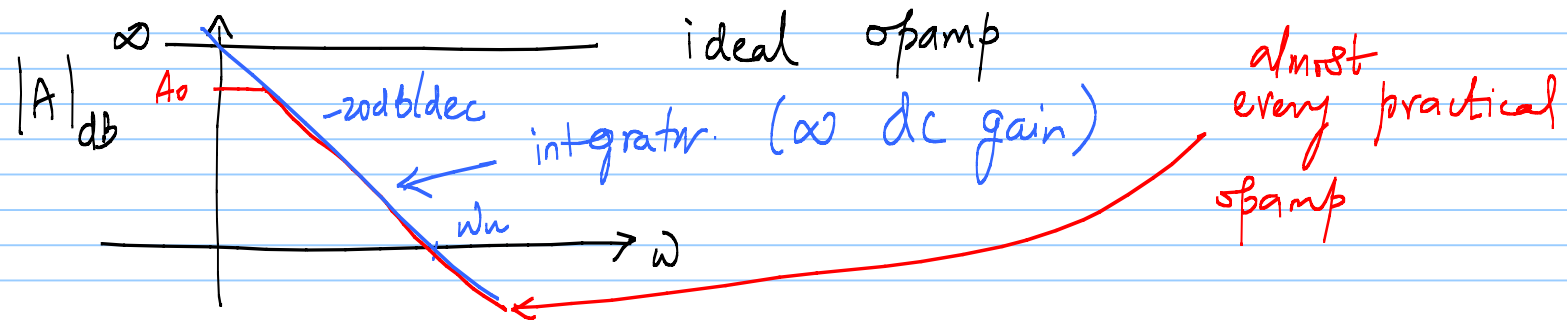
2)  $V_e(\infty) = 0 \Rightarrow$  A should have  $\infty$  DC gain





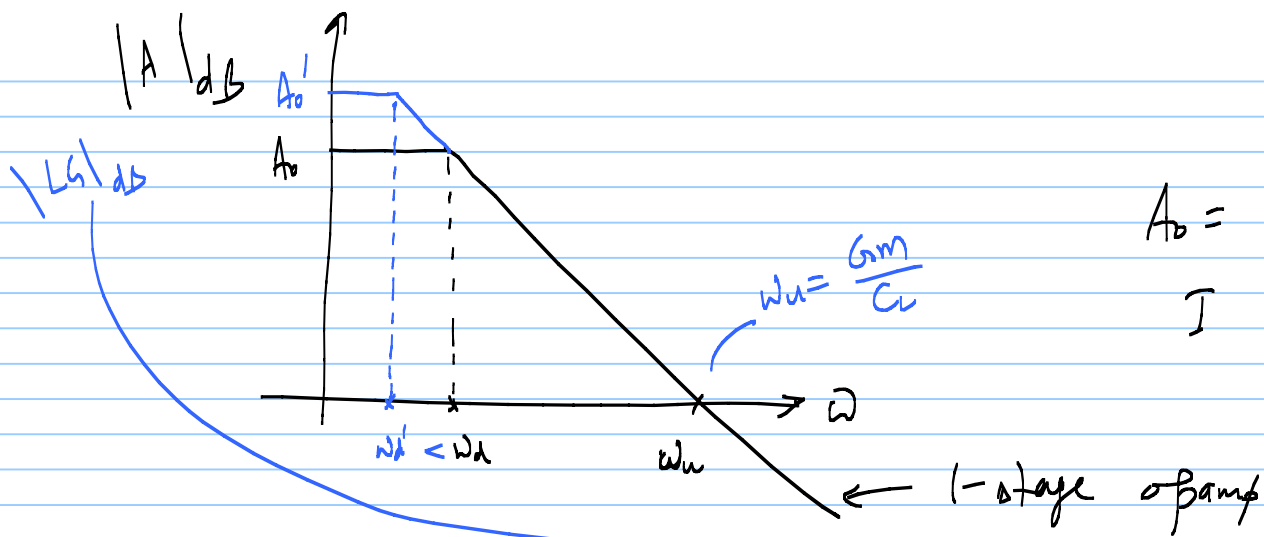

$$A_0 = g_{m1} (r_{ds2} \parallel r_{ds4})$$

I want larger  $A_0$

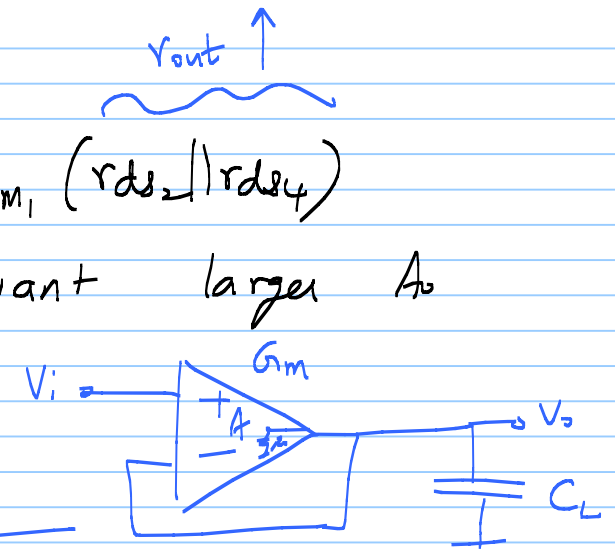

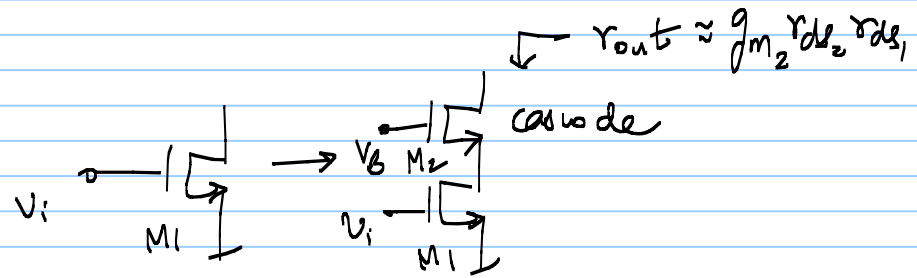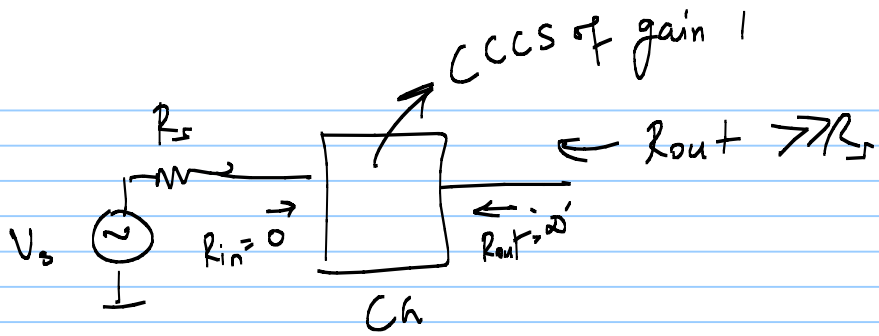





## Datasheet of Telescopic opamp

1) DC gain =  $g_{m1} r_{out} = g_{m1} [(g_{m6} r_{ds6} r_{ds8}) || (g_{m4} r_{ds4} r_{ds2})]$

2)  $G_m = g_{m1}$

3)  $\omega_u = \frac{g_{m1}}{C_L}$  ; dominant pole  $\omega_d = \frac{1}{r_{out} C_L}$


4) ND poles & zeroes : \* 5 nodes of interest

assume node  $N_k \rightarrow \frac{1}{1 + s/p_k}$  ;  $p_k$  depends of  $r$  &  $c$   
@  $N_k$

in general  $p_k$ 's are unique

$+\frac{v}{2} \rightarrow$  encounters effects of  $p_1, p_2, p_3, p_4, p_6$

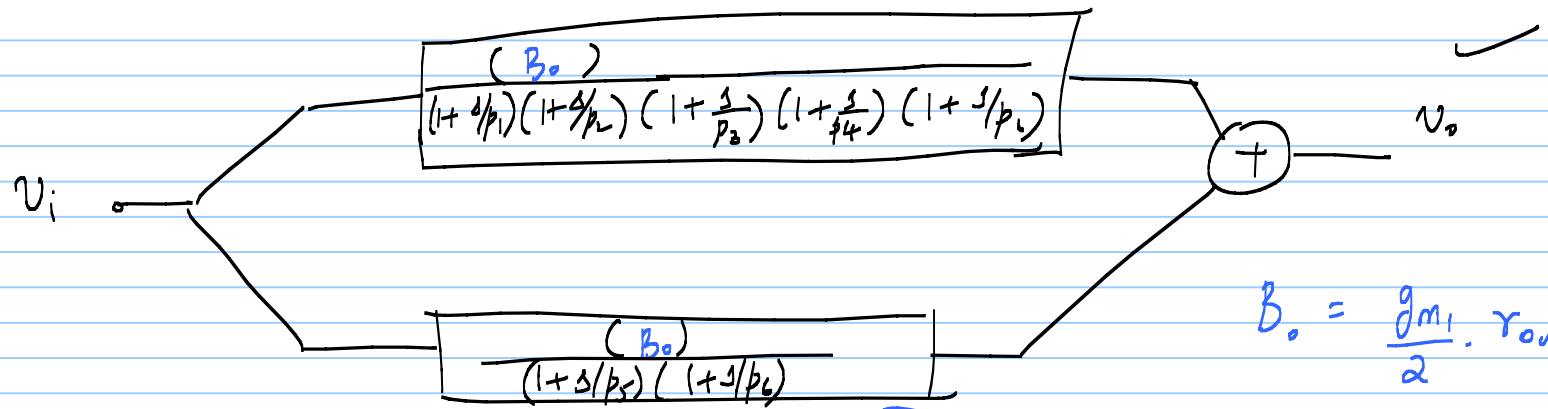$-\frac{v}{2} \rightarrow$  encounters effects of  $p_5, p_6$



$$B_o = \frac{g_{m1} \cdot r_{out}}{2}$$

@ low freq.  $A_o = g_{m1} \cdot r_{out} = 2B_o$

HW

$$\frac{U_o}{U_i} =$$

$$\frac{N(s)}{D(s)}$$

— degree 3 if  $N_1$  &  $N_2$  are symmetric  
— degree 4 if  $N_1$  &  $N_2$  are not symmetric



?? 5 poles if  $N_1$  &  $N_2$  symmetric

6 poles if  $N_1$  &  $N_2$  are asymmetric

29/1/20

Lec 11

$N \Leftrightarrow N_s$  (i.e.  $p_1 = p_s$ )

$$\frac{v_0}{v_1} = \frac{B_0}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right) \left(1 + \frac{s}{p_3}\right) \left(1 + \frac{s}{p_4}\right) \left(1 + \frac{s}{p_6}\right)} + \frac{B_0}{\left(1 + \frac{s}{p_5}\right) \left(1 + \frac{s}{p_6}\right)}$$


$$\frac{V_o}{V_s} = \frac{B_o + B_o \left(1 + s/p_2\right) \left(1 + \frac{s}{p_3}\right) \left(1 + \frac{s}{p_4}\right)}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right) \left(1 + \frac{s}{p_3}\right) \left(1 + \frac{s}{p_4}\right) \left(1 + \frac{s}{p_6}\right)}$$

3 zeros  
5 poles


If  $p_1 \neq p_5$

$$\frac{V_o}{V_i} = \frac{B_o \left(1 + s/p_5\right) + B_o \left(1 + s/p_1\right) \left(1 + s/p_2\right) \left(1 + s/p_3\right) \left(1 + s/p_4\right)}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right) \left(1 + \frac{s}{p_3}\right) \left(1 + \frac{s}{p_4}\right) \left(1 + \frac{s}{p_5}\right) \left(1 + \frac{s}{p_6}\right)}$$

4 zeros  
6 poles

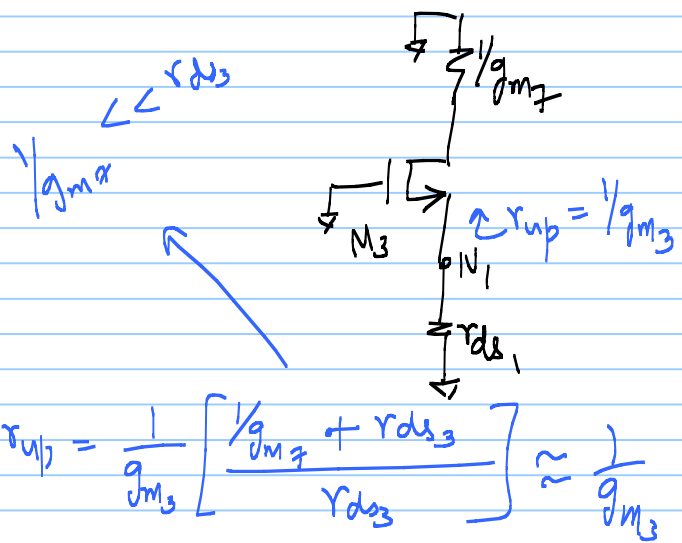

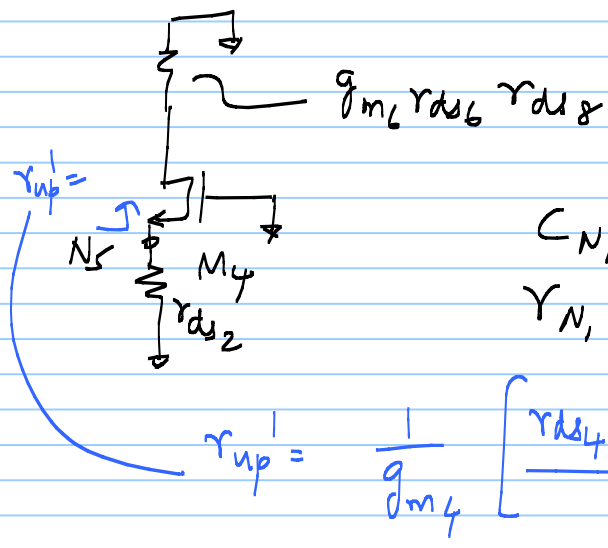
$$r_{up} = \frac{1}{g_{m3}} \left[ \frac{\frac{1}{g_{m7}} + r_{ds3}}{r_{ds3}} \right] \approx \frac{1}{g_{m3}}$$



$$C_{N1} = C_{N5}$$

$$r_{N1} \neq r_{N5}$$

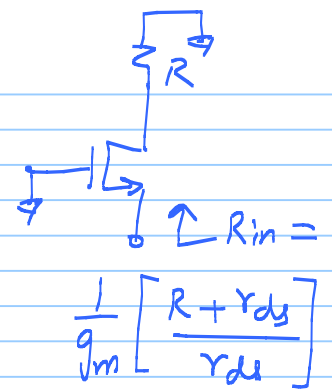

If  $r_{ds} \gg R$ ,

$$R_{in} \approx \frac{1}{g_m}$$



$$r_{up} \approx \frac{g_{m6} r_{ds6} r_{ds4}}{g_{m4} r_{ds4}} \neq \frac{1}{g_{m3}}$$

$N_1$  &  $N_5$  poles are different.

4) ND poles & zeroes  $\rightarrow$  6 poles & 4 zeroes in total


$p_6$  = Dominant pole

$p_1 - p_5$  = ND poles

5) ICMR

$$V_{CMin} (min.) = V_{DSat0} \left| \frac{2I_0}{I_0} \right| + V_{as1} \left| \frac{I_0}{I_0} \right|$$

$$V_{CMin} (max) = V_{B3} - V_{as3} \left| \frac{I_0}{I_0} \right| + V_{T1}$$

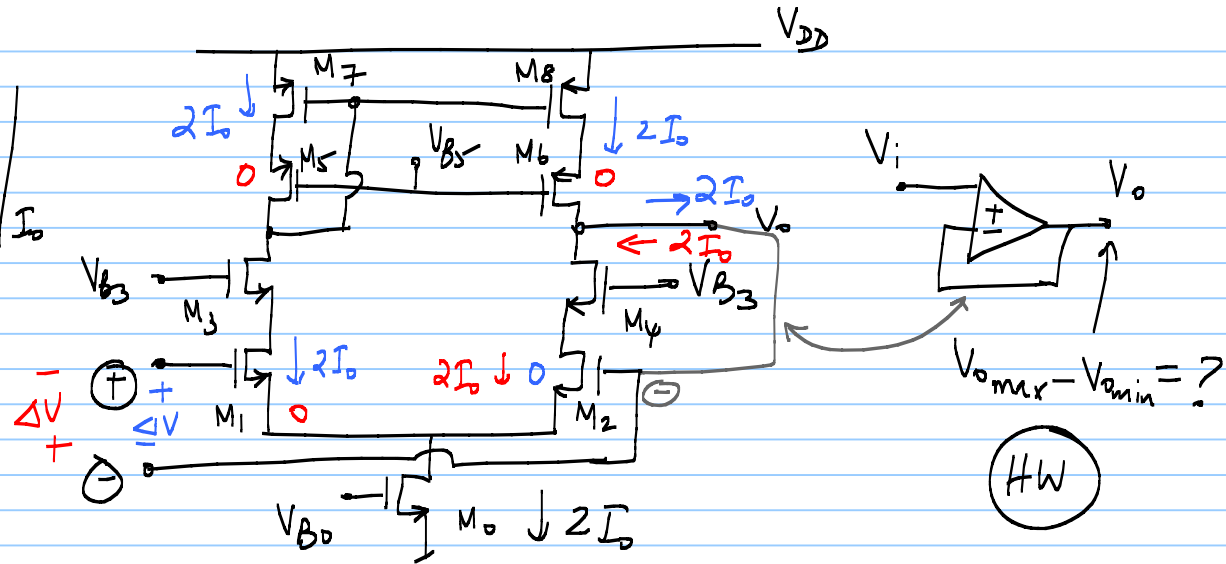

g) OCMR

$$V_{CM_{out}}(\min) = V_{B3} - V_T$$

$$V_{B3}(\min) = V_{CM_{in}} - V_{T2} + V_{A54}$$

$$V_{CM_{out}}(\max) = V_{B5} + V_{T6}$$

7) Noise:  $\bar{i}_n = 0$  @ low freq.


$$\bar{e}_n = \text{same as } \overset{\text{5-transistor}}{\text{1-stage opamp}} = \frac{16kT}{3g_{m1}} + \frac{16kT \cdot g_{m7}}{3g_{m1}^2}$$




\* Noise from  $M_0$  is Common-mode

\* Noise from  $M_3$   $M_4$   $M_5$   $M_6$  — does not affect  $\bar{e}_n$  @  
low freq.; affects  $\bar{e}_n$  @ high freq.


8) Offset :  $\sigma_{os}^2 = ?$  (HW) assume only  $V_T$  mismatch

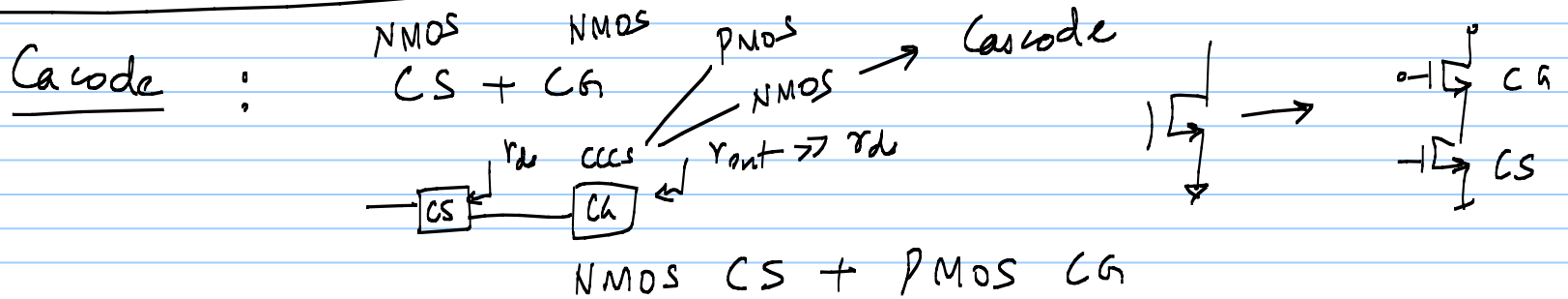9) Slew rate :  $SR = \pm \frac{2I_D}{C_L}$



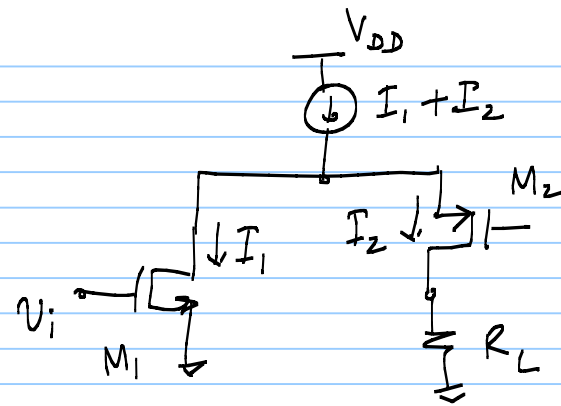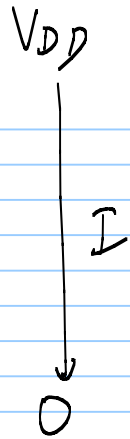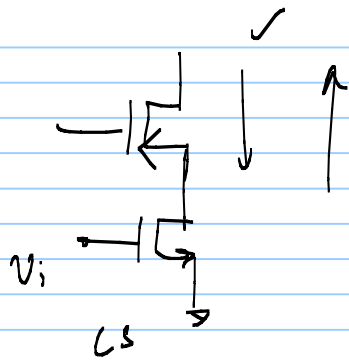

"Folded  
Cascode"  
amplifier

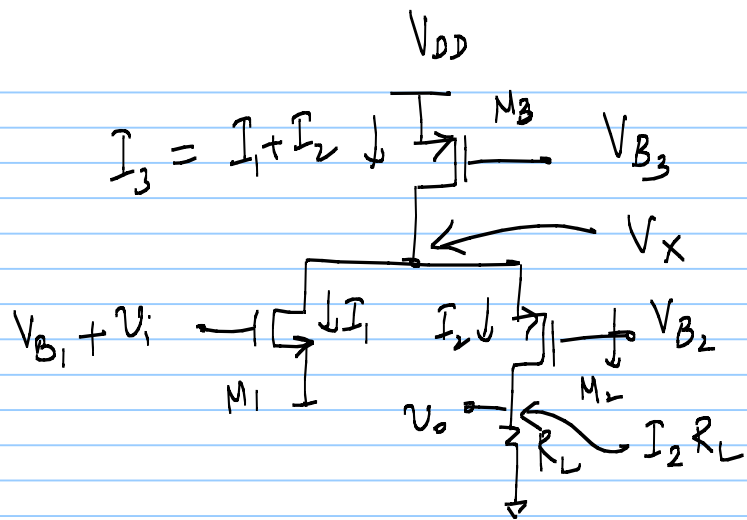

$$V_{S_{q3}} = V_{DD} - V_{B3} \rightarrow \text{cause } I_{D3} = I_1 + I_2$$

$$V_{B1} = V_{GS1} | I_1 ; \quad V_x \text{ is set by } V_{B2} \quad (V_x = V_{B2} + V_{S_{q2}})$$

$$V_x (\text{max}) = V_{DD} - V_{SD_{sat3}} \quad \text{M}_L \text{ in triode}$$

$$V_x (\text{min}) = V_{D_{sat1}} \quad \text{or } ( \quad )$$

~~X~~  $M_2$  goes into triode when  $V_{B_2} = I_2 R_L - V_{T_2}$

$$\min V_X = I_2 R_L - V_{T_2} + V_{S_{G_2}}$$

$$\min V_X = \text{larger of } \left\{ V_{D_{sat_1}}, I_2 R_L + V_{S_{D_{sat_2}}} \right\}$$






4/2/20

## Lec 12

- LT Spice — Circuit simulator that runs on windows
- simulation assignments will start soon.
  - Read the manual & learn to use the simulator


# Folded Cascode

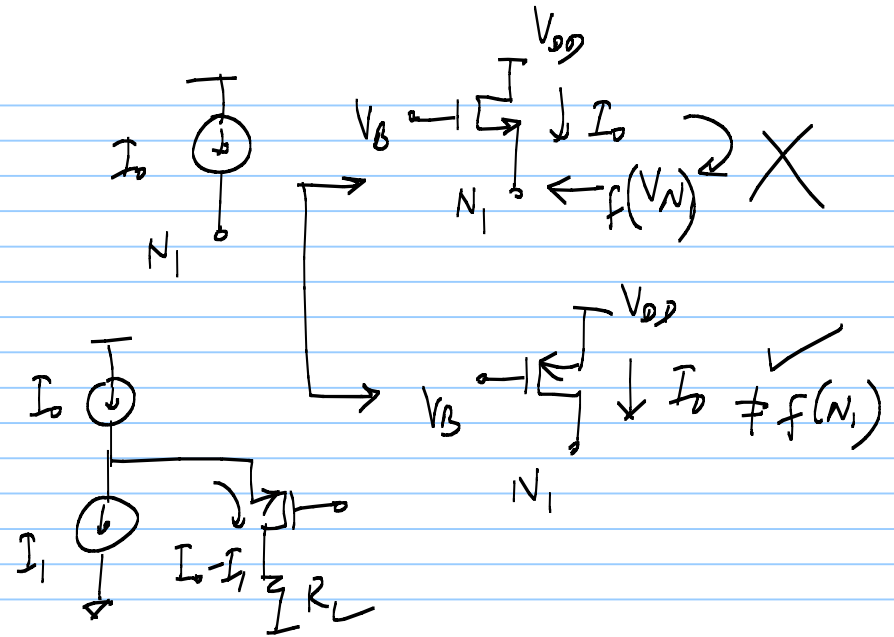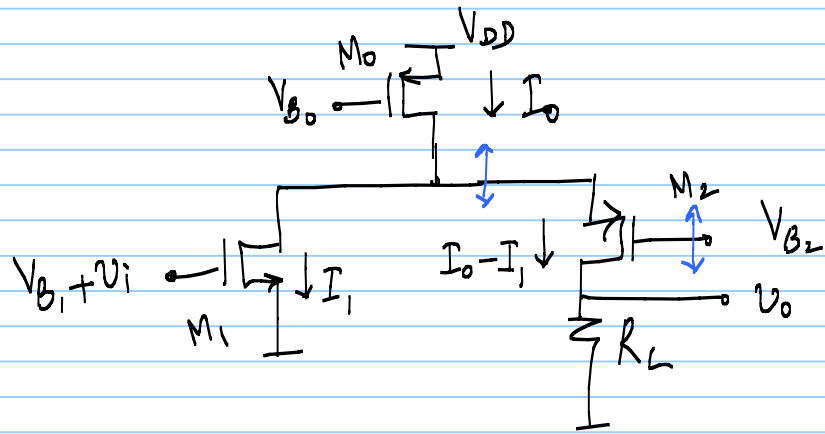

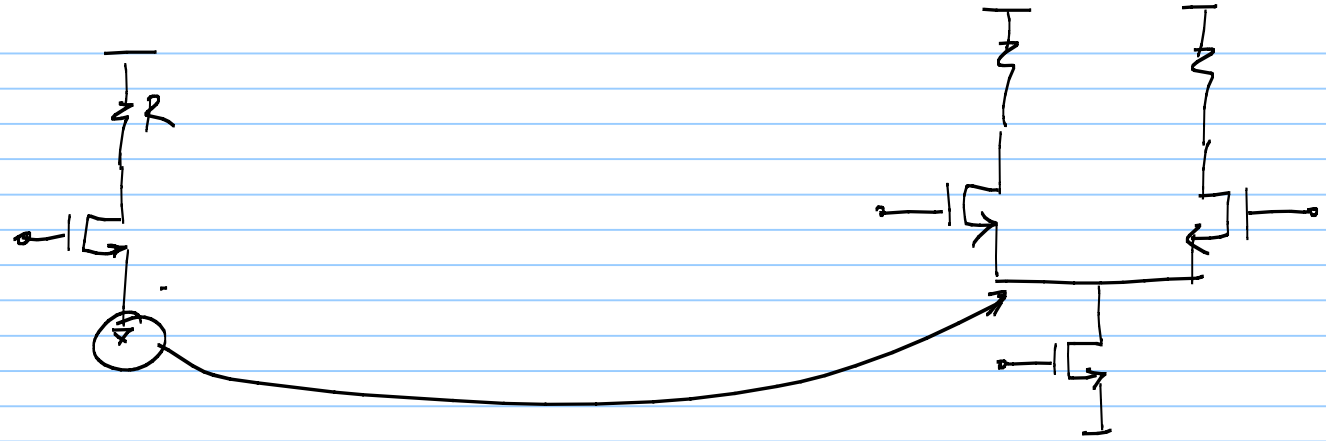





$$\Delta I = g_{m1} \frac{\Delta V}{2}$$

$$I_1 + \Delta I = I_{D1} \downarrow$$

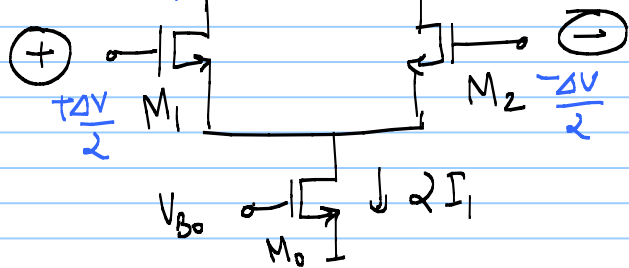

$$I_{D2} = I_1 - \Delta I$$

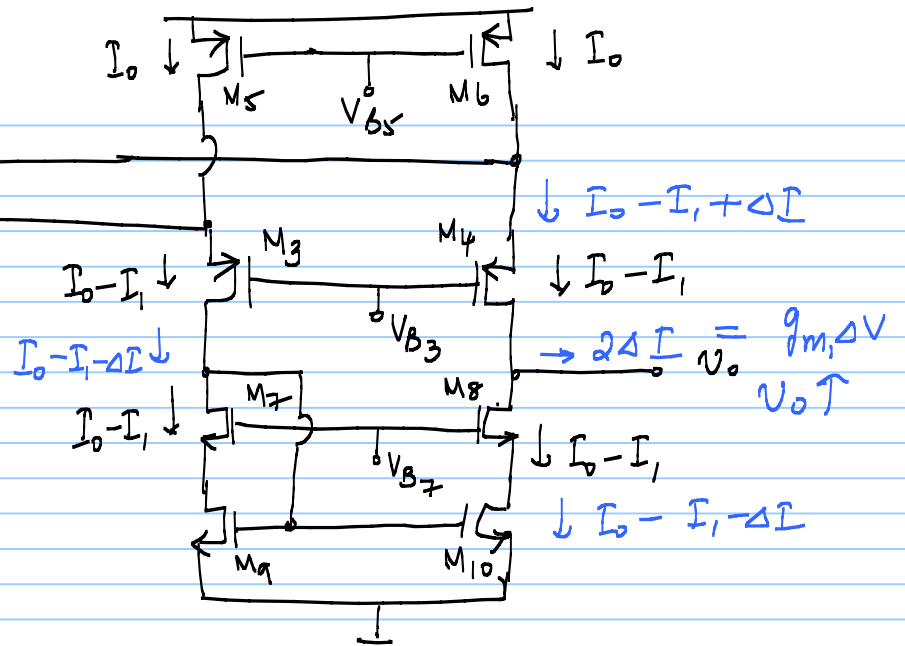

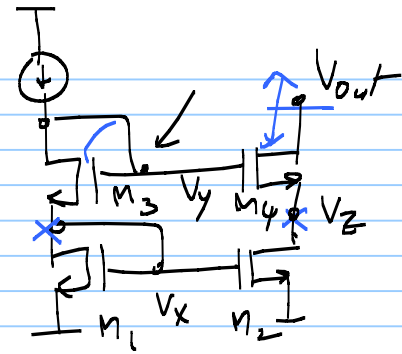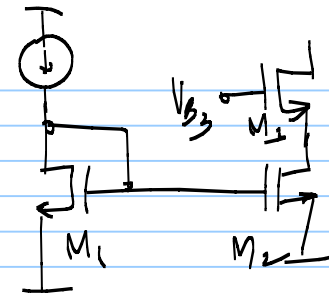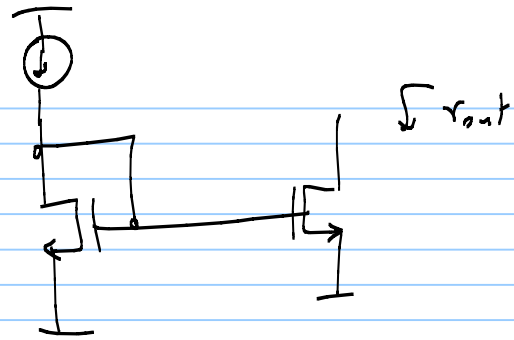


$$\left. \begin{aligned}
 V_y &= V_{GS1} + V_{GS3} ; & V_x &= V_{GS1} \\
 V_z &= V_{GS1} + V_{GS3} - V_{GS4} = V_{GS1}
 \end{aligned} \right\} \begin{aligned}
 V_{out_{min}} &= V_y - V_{T4} \\
 &= V_{GS1} + V_{DSat4}
 \end{aligned}$$

$$I_f \quad \underbrace{V_Z = V_{\text{sat}2}}_2, \quad V_{\text{out min}} = V_{\text{Dsat}2} + V_{\text{Dsat}4}$$

→ we need  $V_y = V_Z + V_{\text{as}4} = V_{\text{Dsat}2} + V_{\text{as}4}$

high  
swing  
cas code  
current mirror

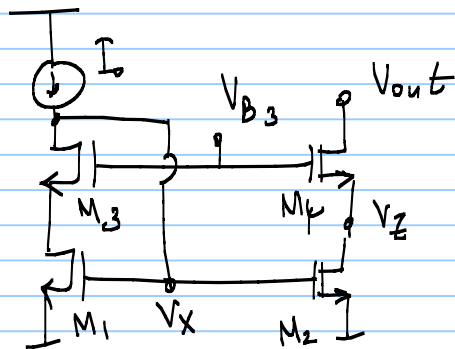

$V_X = V_{\text{as}1}$  through negative f.b.

Set  $V_{B3} \geq V_{\text{Dsat}1} + V_{\text{as}3}$

$$V_{\text{out min}} = V_{B3_{\text{min}}} - V_{T4} = V_{\text{Dsat}1} + V_{\text{Dsat}3}$$


## Datasheet

$$G_m = g_{m1}$$

$$r_{out} = r_{up} \parallel r_{dn}$$

$$= \left[ (g_{m4} r_{ds4}) (r_{ds6} \parallel r_{ds7}) \right] \parallel \left[ (g_{m8} r_{ds8}) (r_{ds10}) \right]$$

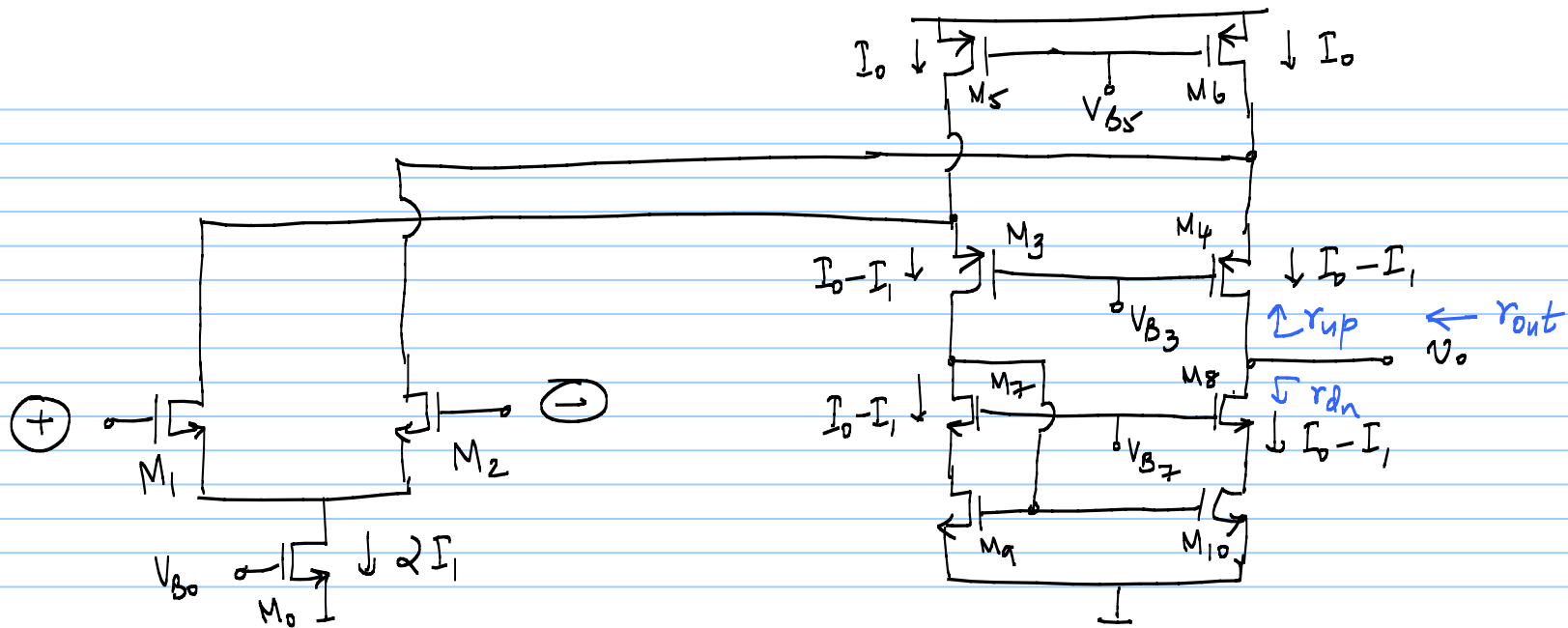1) DC gain =  $g_{m1} r_{out}$   $\rightarrow$  slightly lower than that of telescopic opamp






2)  $G_m = g_{m1}$

3)  $\omega_u = \frac{g_{m1}}{C_L}$  ; Dominant pole  $\omega_d = \frac{1}{r_{out} C_L}$

4) ND poles & zeroes  $\leftarrow$  next class (HW - # of poles & zeroes)

05/02/2020

Lec 13

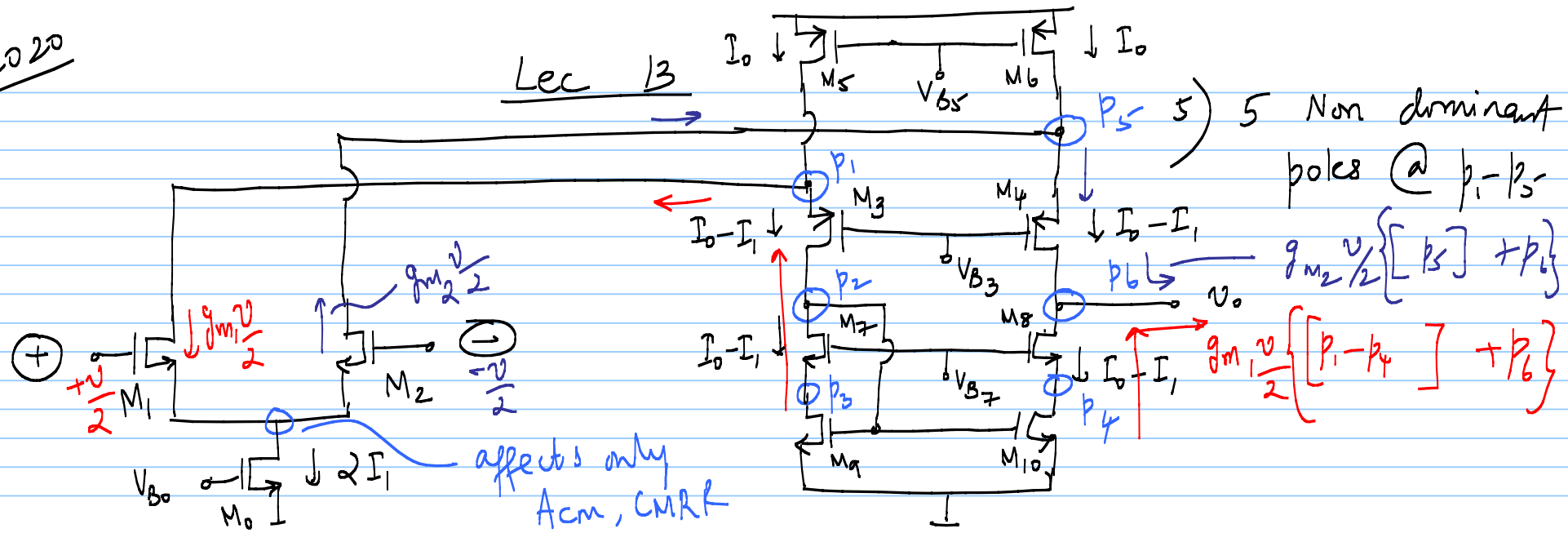

$$6) \quad \underline{ICMR} = \left\{ V_{DSat0} / 2I_1 + V_{AS1} / I_1, \quad V_{B3} + V_{SA3} / I_0 - I_1 + V_{T1} \right\}$$


$$7) \quad \underline{OCMR} = \left\{ \underbrace{V_{B7} - V_{T8}}_{\text{blue wavy}}, \quad \underbrace{V_{B3} + V_{T4}}_{\text{red wavy}} \right\}$$

can be set  $\approx 2V_{DSat}$


$$\text{i.e. } V_{B7} = \underbrace{V_{AS8}}_{I_0 - I_1} + \underbrace{V_{DSat10}}_{I_0 - I_1}$$

$V_{DD} - 2V_{DSat}$
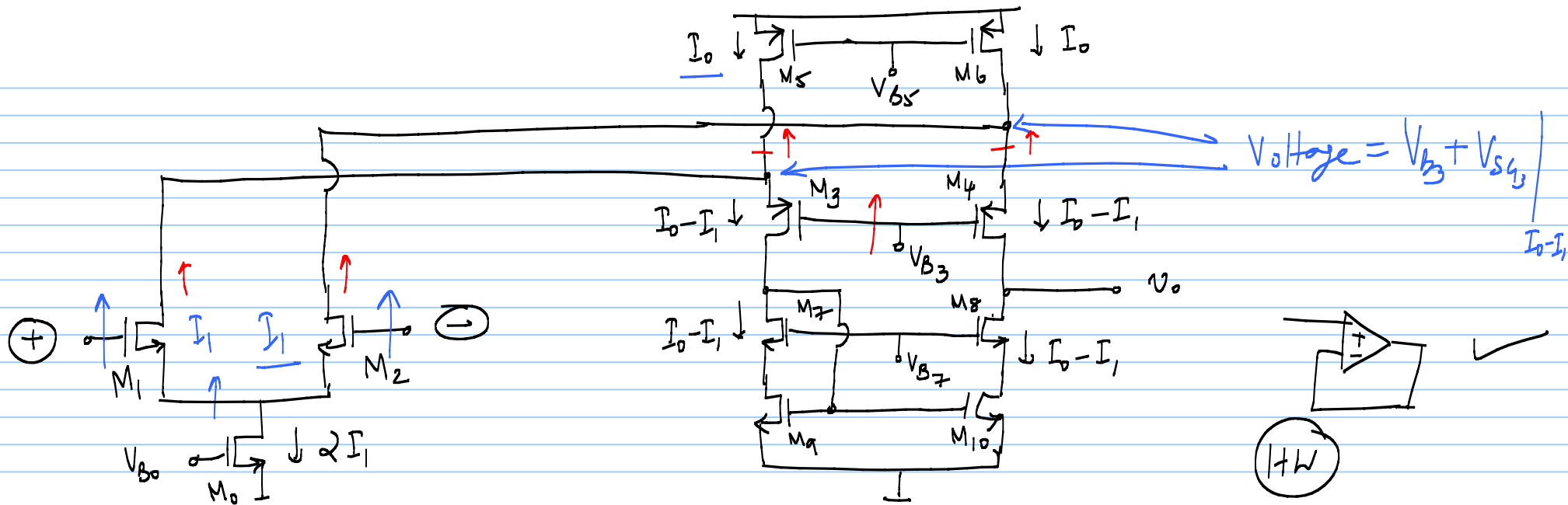
$$\text{i.e. } V_{B3} = V_{DD} - \underbrace{V_{SDSat5}}_{I_0} - \underbrace{V_{SA3}}_{I_0 - I_1}$$





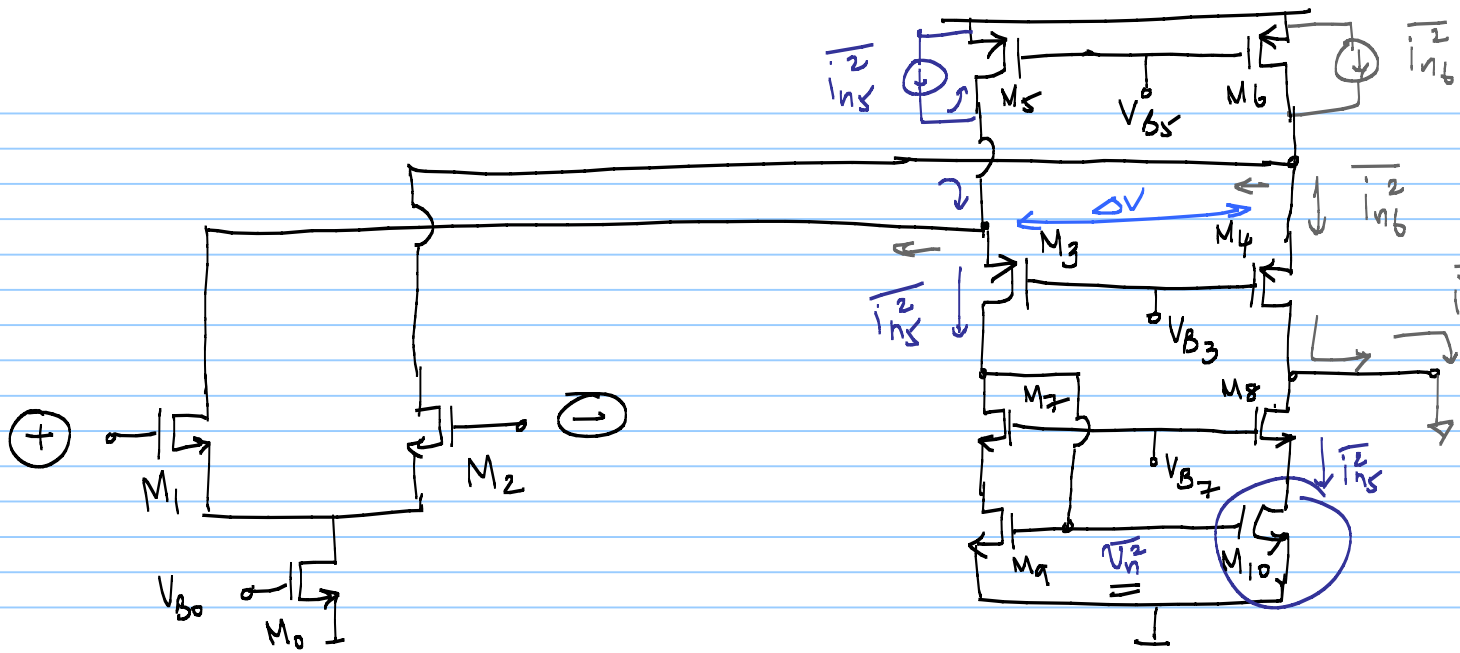


$$i_{scn}^2 = i_{nb}^2 + i_{ns}^2 + i_{n0}^2 + i_{n9}^2$$

if  $\frac{1}{g_{m9}} < r_{d3}$

$$r_{in} = \frac{1}{g_{m3}}$$

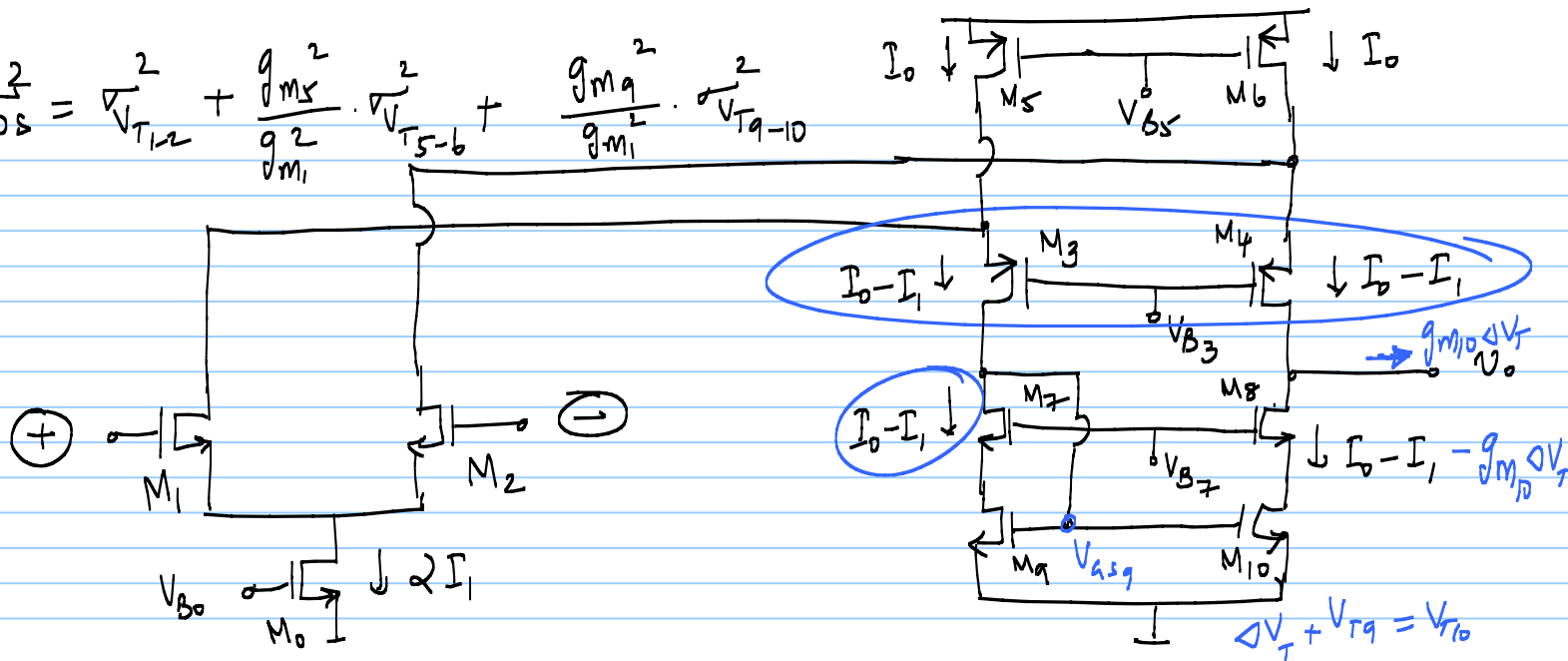9) Offset : 
$$\sqrt{v_{os}^2} = \sqrt{v_{T1,2}^2} + \frac{g_{m5}}{g_{m1}} \cdot \sqrt{v_{T5-6}^2} + \frac{g_{m9}}{g_{m1}} \cdot \sqrt{v_{T9-10}^2}$$










5/7/20

Lec 13

Folded cascode opamp datasheet

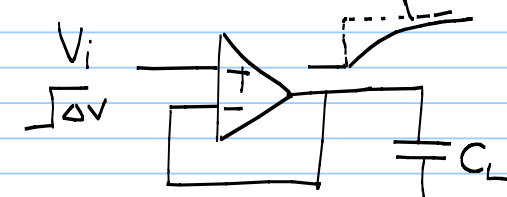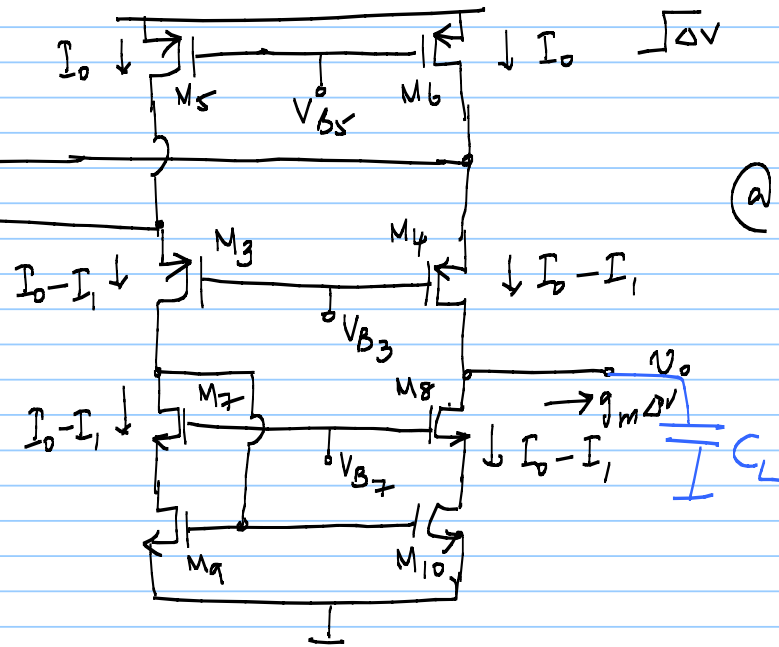
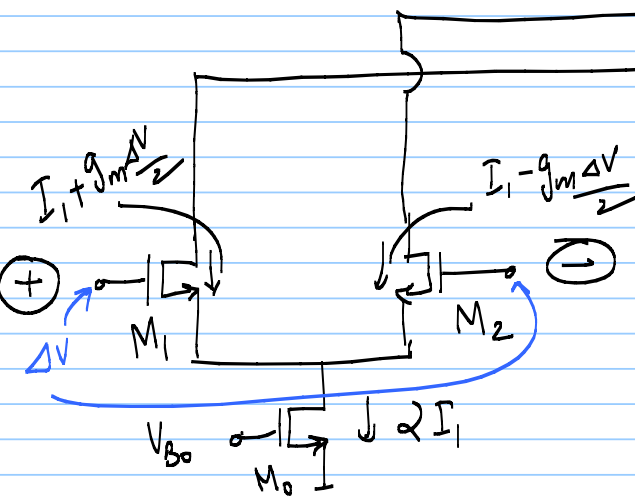
(10) Slew Rate

$$\tau \approx \frac{1}{\omega_u} \quad \tau = \frac{C_L}{g_m}$$



(a)  $t = 0^+$ ,  $\Delta V$  appears as  $V_{id}$   
 $(V_+ - V_-) = \Delta V$

Case 1 :  $I_0 - 2I_1 \geq 0$

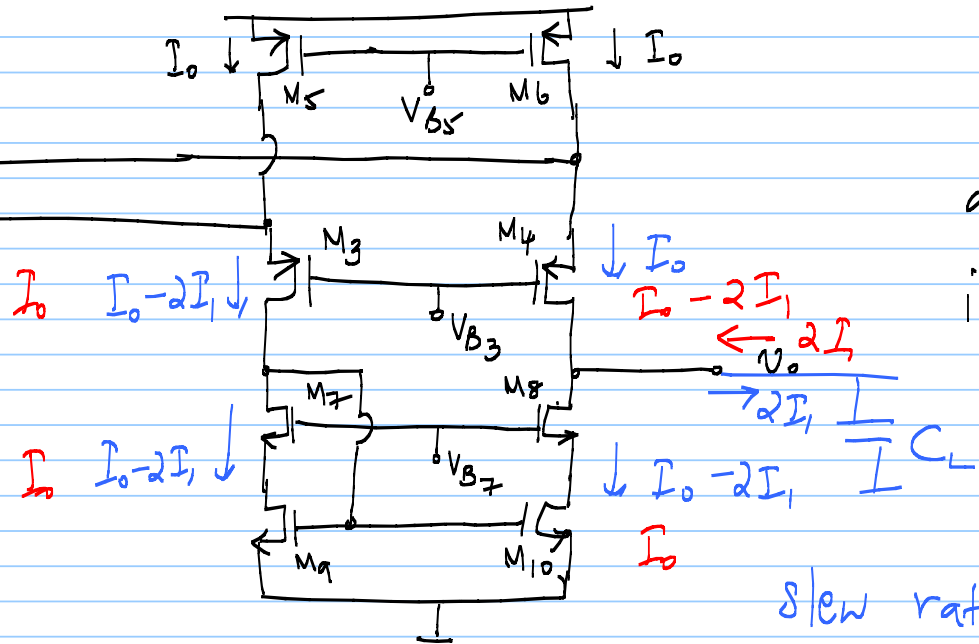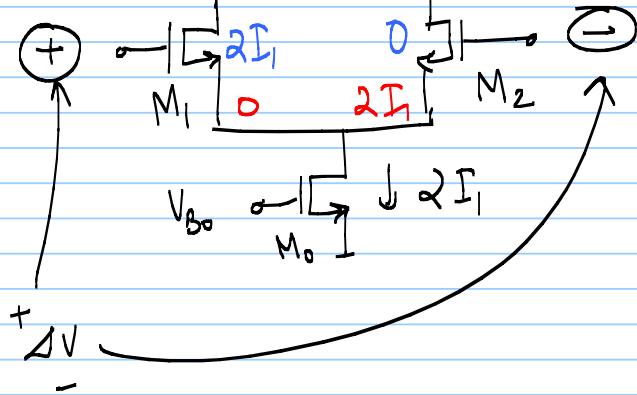



large  $\Delta V$   
applied @  
input

$$\text{slew rate} = \frac{+2I_1}{C_L}$$


$$- \frac{2I_1}{C_L}$$



Case 2:  $I_0 - 2I_1 < 0$

HW

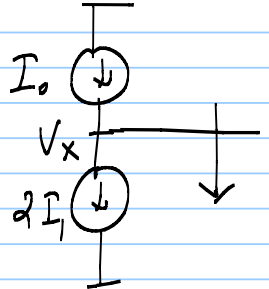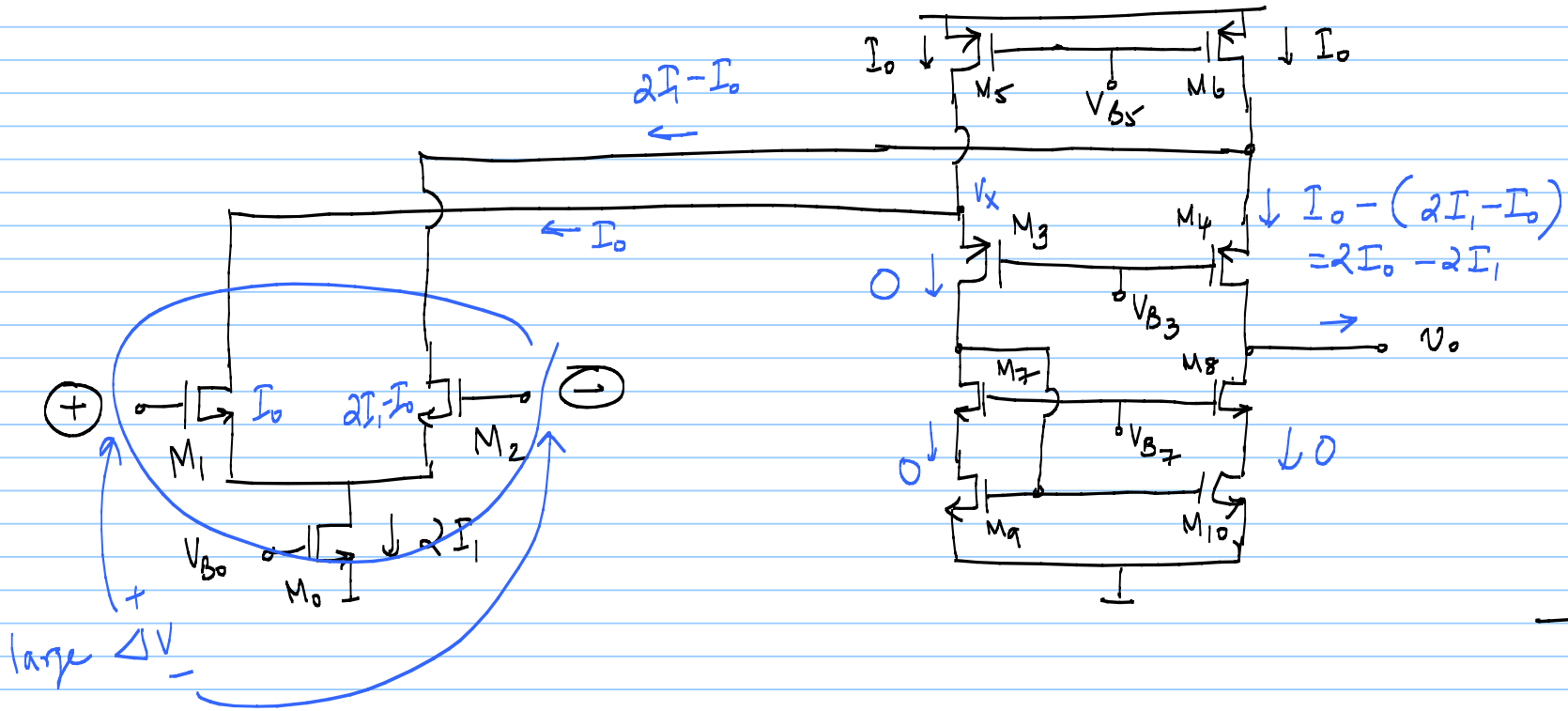

$2I_1 > I_0$

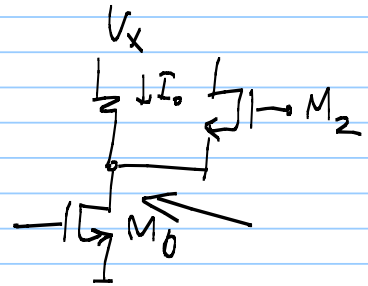

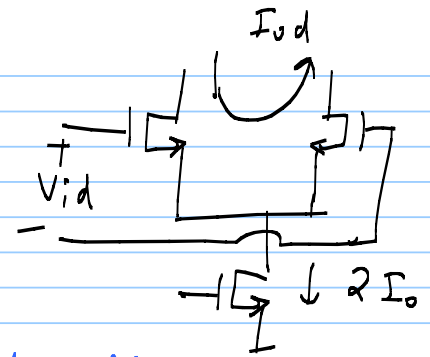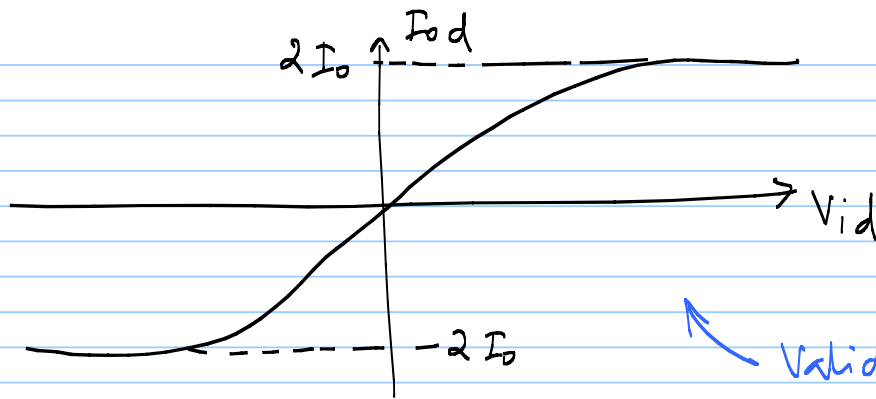



Valid if  $M_1 - M_2$   
are in saturation

7/2/20

Lec 14


$I_0 < 2I_1$

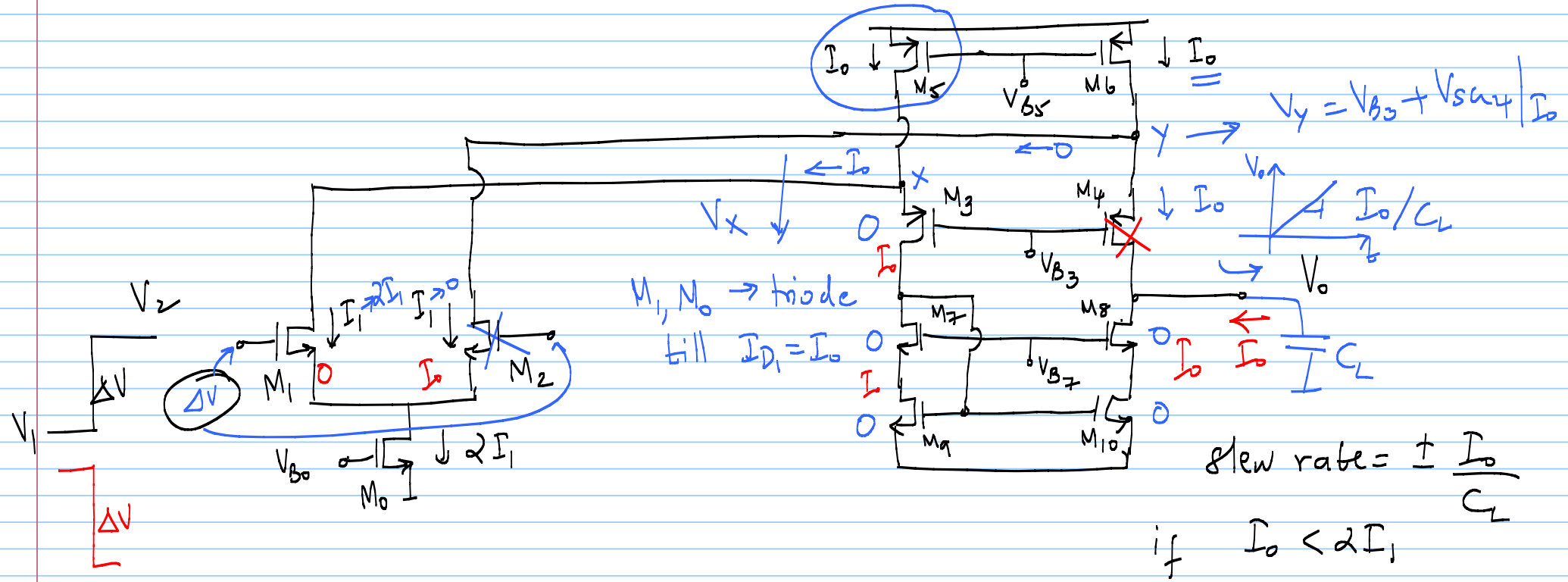

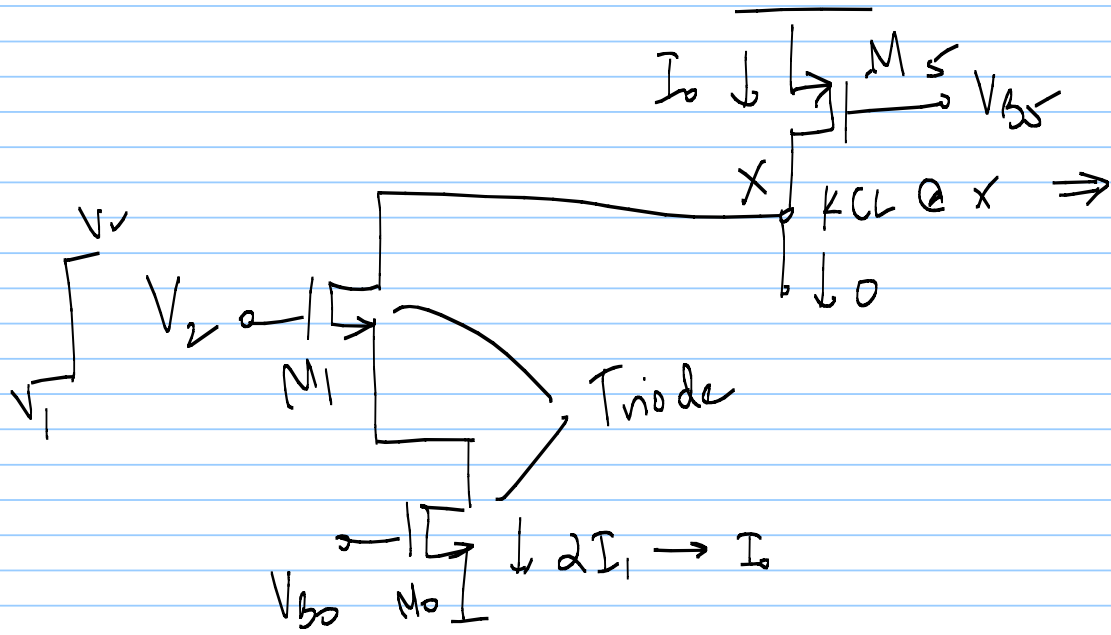


$$\underline{I_0 < 2I_1}$$



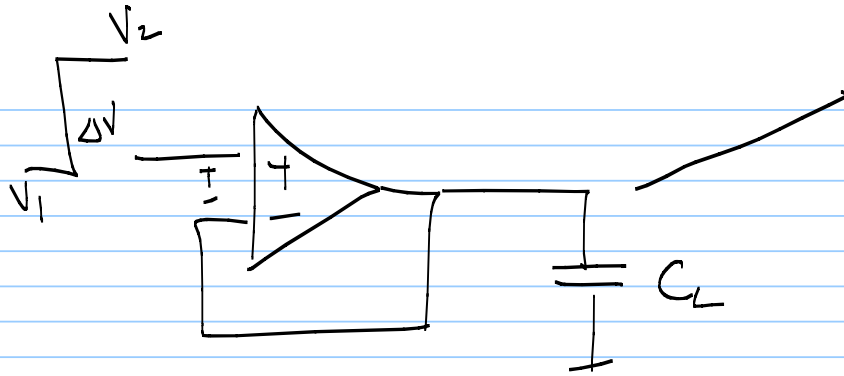

2-stage opamp

Block level picture

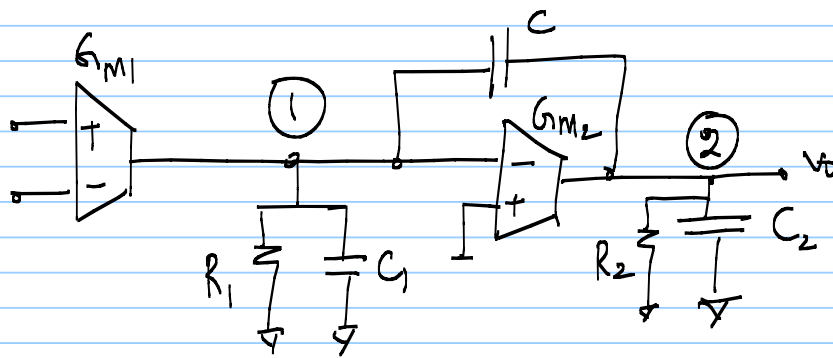

$R_1 \rightarrow r_{out}$  of  $G_{m1}$

$R_2 \rightarrow$  " "  $G_{m2}$



$C_1, C_2 \rightarrow$  total cap @ ①

& ② resp

$\omega_d \leftarrow p_1, p_2, z_1$


Before compensation

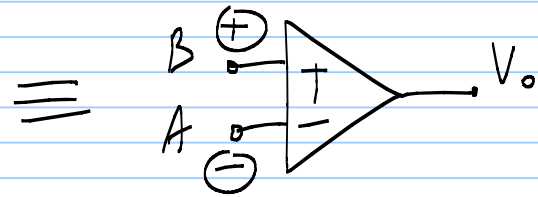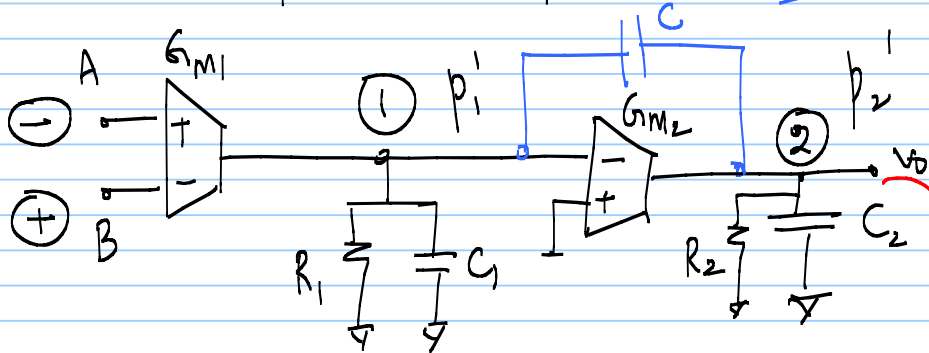Miller effect :  $C_{\text{①}} \approx C_1 + G_{m2}R_2 \cdot C$   
 $\approx G_{m2}R_2 C$



$$A_0 = G_{m1}R_1 G_{m2}R_2$$

pole-splitting

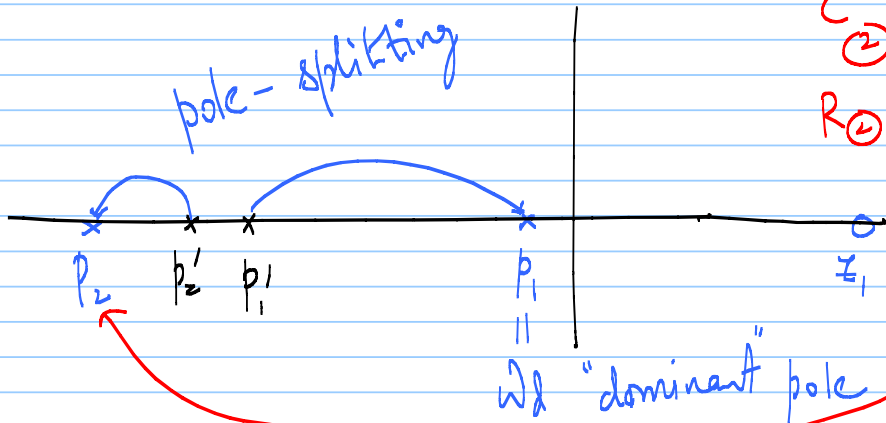

$C_2 \uparrow$  slightly  
 $R_{\text{①}} = r_{\text{out1}} \parallel R_2$

$$p_1' = \frac{1}{R_1 C_1}$$


$$p_1 = \frac{1}{R_1 \cdot G_{m2}R_2 C} = \omega_d$$

$$p_2' = \frac{1}{R_2 C_2}$$

$$p_2 = \dots$$




a) high freq.:

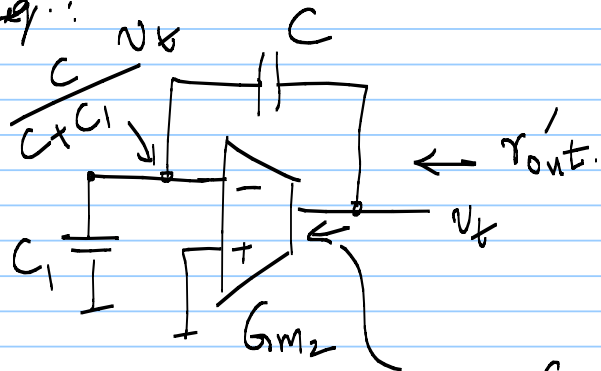


$$i_b = \frac{G_{m2} \cdot C}{C + C_1} \cdot v_b$$
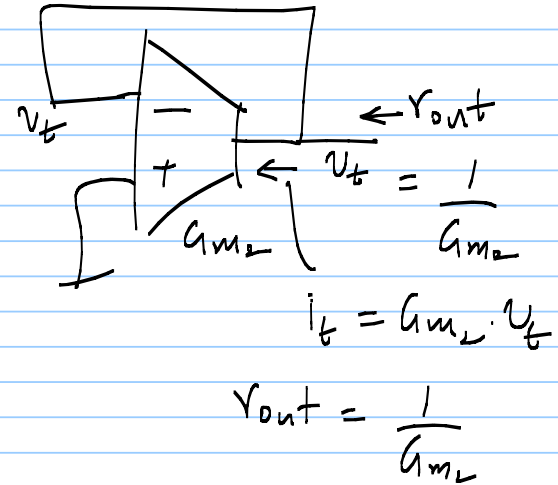
$$r'_{out} = \frac{v_b}{i_b} = \left( \frac{C + C_1}{C} \right) \cdot \frac{1}{G_{m2}}$$



$$r_{out} = \frac{1}{G_{m2}}$$


Zero :  $Z_1 = + \frac{G_{m2}}{C}$

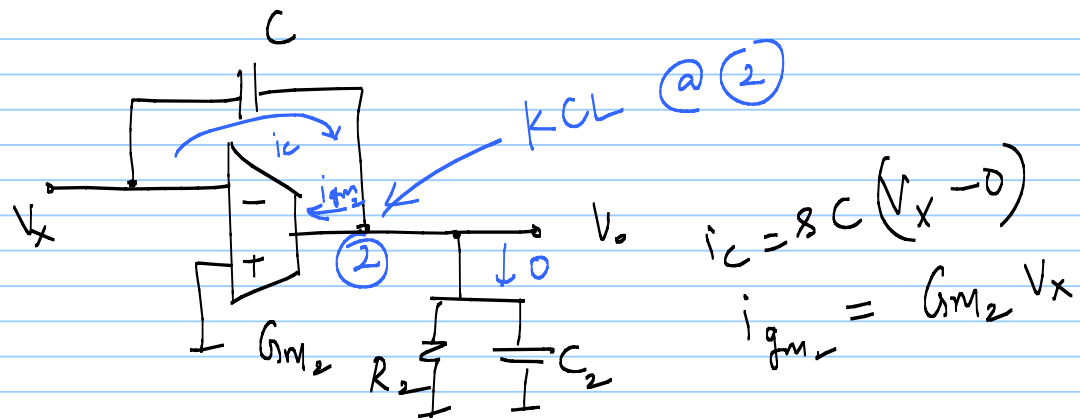

$i_c = i_{gm_2} @ Z_1 : Z_1 = \frac{G_{m2}}{C}$

$\omega_u = \frac{G_{m1}}{C} = \omega_d \cdot A_0$

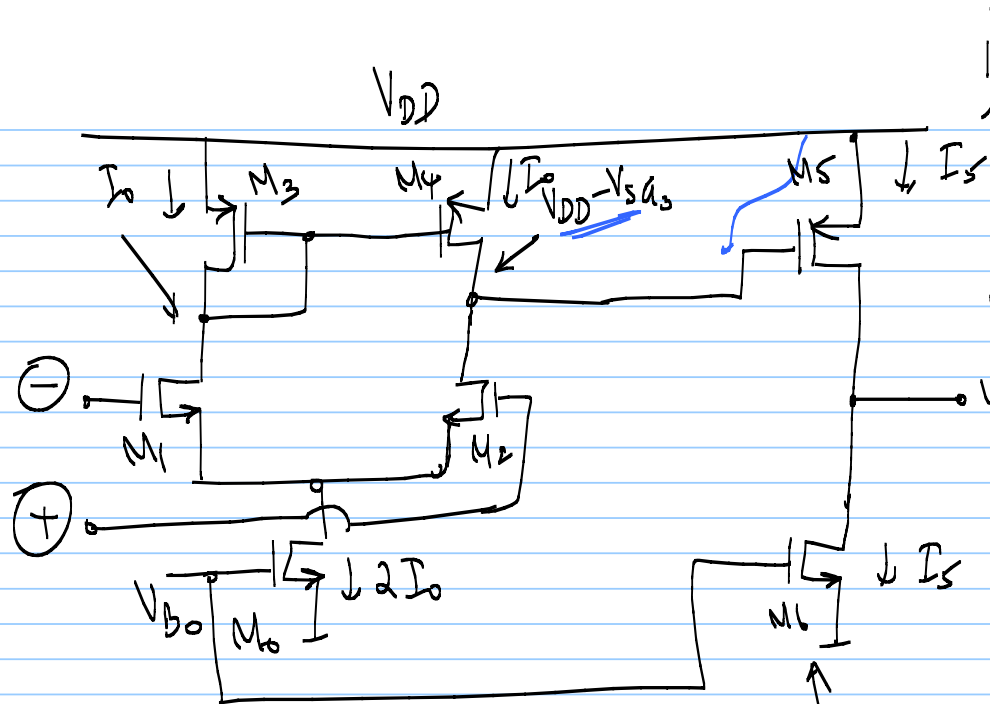Normally  $Z_1, p_2 \gg \omega_u \Rightarrow 1) G_{m2} \gg G_{m1}$



1) choose  $\left(\frac{W}{L}\right)_6$  so that  $I_{D6} = I_5$  <sup>desired</sup>  
 $(W/L)_6 : (W/L)_5 = I_5 : 2I_0$


2)  $V_{DD} - V_{sa3} = V_{DD} - V_{sc5}$

$$V_{sa3} = V_{sc5}$$

$$V_{dsat6} = V_{dsat5}$$

$$\sqrt{\frac{2I_0}{\beta(W/L)_3}} = \sqrt{\frac{2I_5}{\beta(W/L)_5}}$$
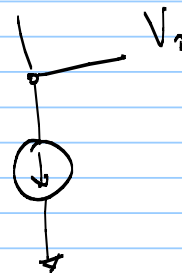
$$\left. \begin{aligned} G_{m1} &= g_{m1} \\ G_{m2} &= g_{m5} \end{aligned} \right) g_{m5} \Rightarrow g_m$$




$$\frac{I_0}{(W/L)_3} = \frac{I_5}{(W/L)_5}$$

11/2/20



Lec 15

Datasheet of 2-stage opamp

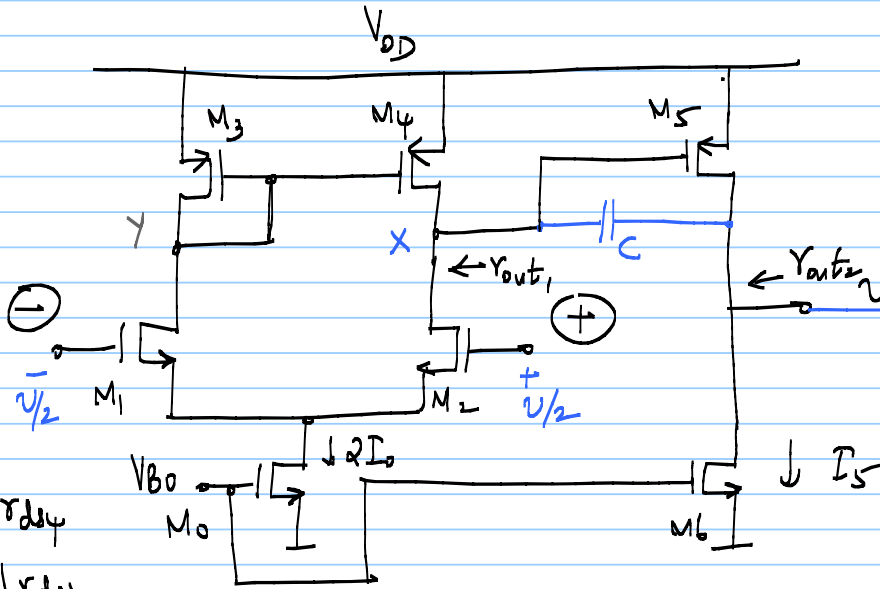

$r_{out1} = r_{ds2} || r_{ds4}$

$r_{out2} = r_{ds5} || r_{ds6}$

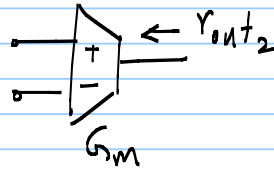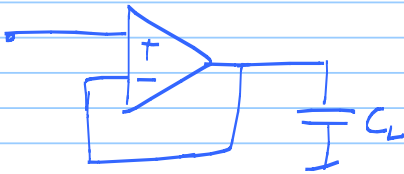

1)  $G_m = ?$

$v_x = -g_{m1} (r_{out1}) \cdot v$

$i_{out} = +g_{m1} r_{out1} g_{m5} \cdot v$

$G_m = g_{m1} r_{out1} g_{m5}$

2) DC gain  $A_0 = (g_{m1} r_{out1}) (g_{m5} r_{out2})$

If  $R_L$  exists,

$A_0 = (g_{m1} r_{out1}) (g_{m5} (r_{out2} || R_L))$

$$3) \quad \omega_u = \frac{G_{m1}}{C} = \frac{g_{m1}}{C} ; \quad \omega_d = \frac{1}{R_1 \cdot (G_{m2} R_2 \cdot C)} = \frac{1}{r_{out1} \cdot (g_{m5} r_{out2} \cdot C)}$$

4) ND poles & zeroes:

$p_2$  @ output node

$p_3$  @ node Y

$z_1$  @  $\frac{G_{m2}}{C} = \frac{g_{m5}}{C}$  (RHP)

$z_2$  due to  $+v_x$  through X path (LHP)  
 $-v_x$  through Y-X path (LHP)

2 poles & 2 zeroes that are ND.


5) ICMR

$$V_{CM,in} = \left\{ V_{as1} / I_0 + V_{Dsat0} / 2I_0, \quad V_{DD} - V_{as3} / I_0 + V_{T1} \right\}$$


6) OCMR

$$V_{CM,out} = \left\{ V_{B0} - V_{T6}, \quad V_{DD} - V_{Dsat5} / I_5 \right\}$$

7)  $e_n^2 =$

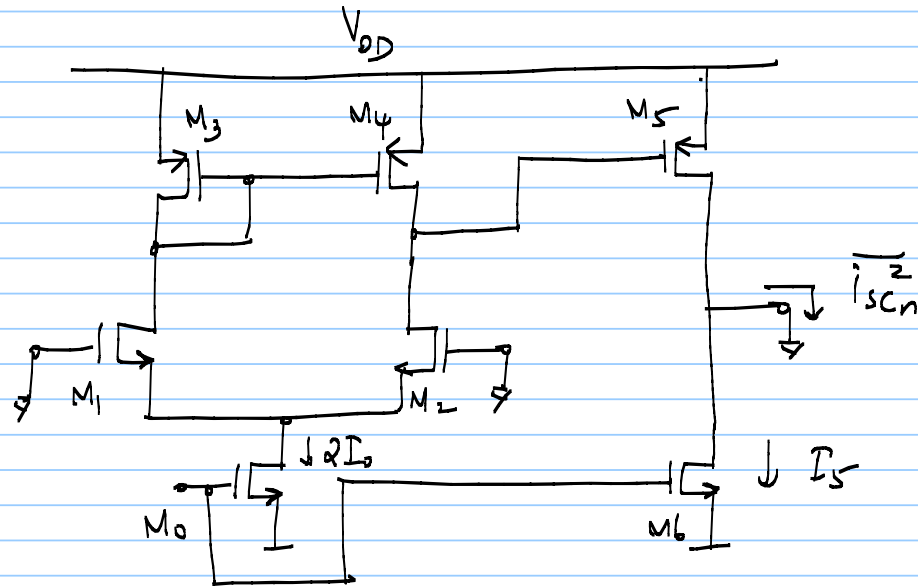
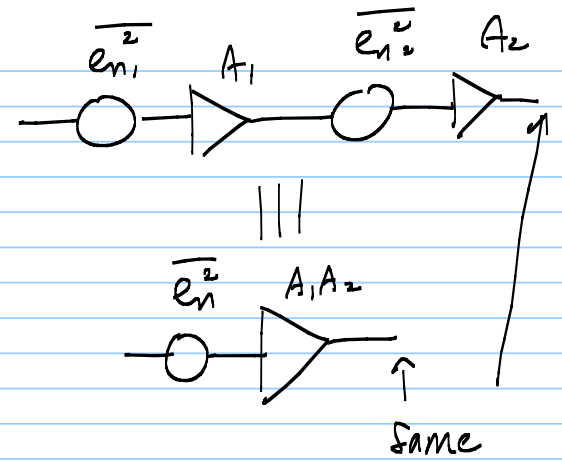
$$\frac{\overline{e_{n1}^2}}{\Delta f} = \frac{16kT}{3} \left[ \frac{1}{g_{m1}} + \frac{g_{m3}}{g_{m1}^2} \right]; \quad A_1 = g_{m1} r_{out1}$$



$$\overline{e_n^2} \cdot (A_1 A_2)^2 = \overline{e_{n1}^2} \cdot (A_1 A_2)^2 +$$

$$\overline{e_{n2}^2} \cdot (A_2)^2$$


$$\overline{e_n^2} = \overline{e_{n1}^2} + \frac{1}{A_1^2} \cdot \overline{e_{n2}^2}$$

$$\overline{e_{n2}^2} = \frac{8kT}{3} \left[ \frac{1}{g_{m5}} + \frac{g_{m6}}{g_{m5}^2} \right]; \quad A_2 = g_{m5} r_{out2}$$

$$\overline{e_n^2} = \overline{e_{n1}^2} + \frac{1}{A_1^2} \cdot \overline{e_{n2}^2}$$

$$\overline{e_n^2} = \frac{16kT}{3} \left[ \frac{1}{g_{m1}} + \frac{g_{m3}}{g_{m1}^2} \right] + \underbrace{\left( \frac{1}{g_{m1} r_{out1}} \right)^2}_{\text{wavy line}} \cdot \underbrace{\frac{8kT}{3} \left[ \frac{1}{g_{m5}} + \frac{g_{m6}}{g_{m5}^2} \right]}_{\text{wavy line}}$$

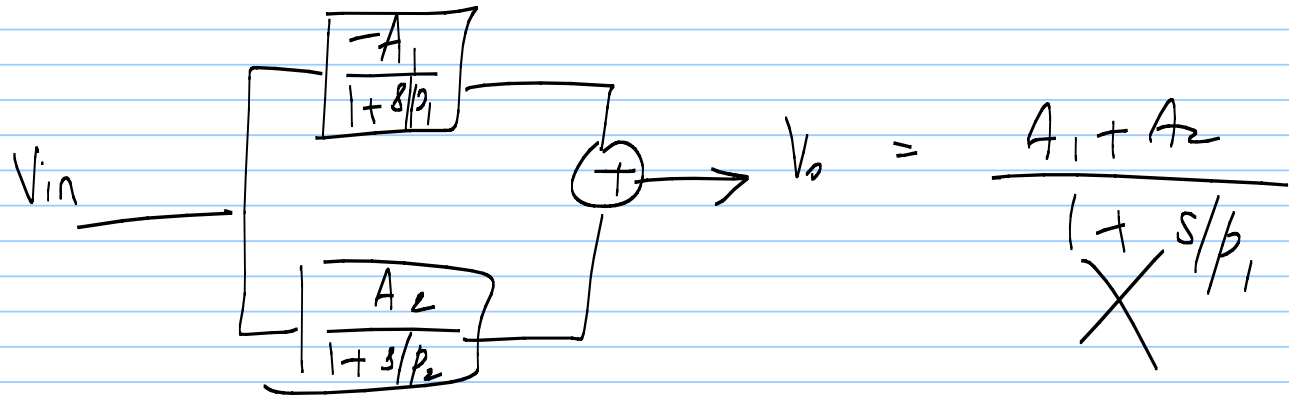$g_{m5} \gg g_{m1} \quad (\text{to keep } z_1 \gg \omega_u)$   
 $\hookrightarrow \overline{e_{n2}^2} \ll \overline{e_{n1}^2}$   
 $\overline{e_n^2} \approx \overline{e_{n1}^2}$



$$V_o = \frac{A_1 + A_2}{1 + s/p_1}$$

~~$1 + s/p_2$~~





12/2/20

Lec 16

8) Offset voltage

$$r_{os}^2 = r_{V_{T1-2}}^2 + \frac{g_{m3}^2}{g_{m1}^2} r_{V_{T3-4}}^2$$

9) Slew rate

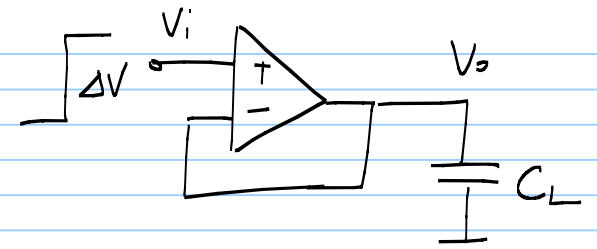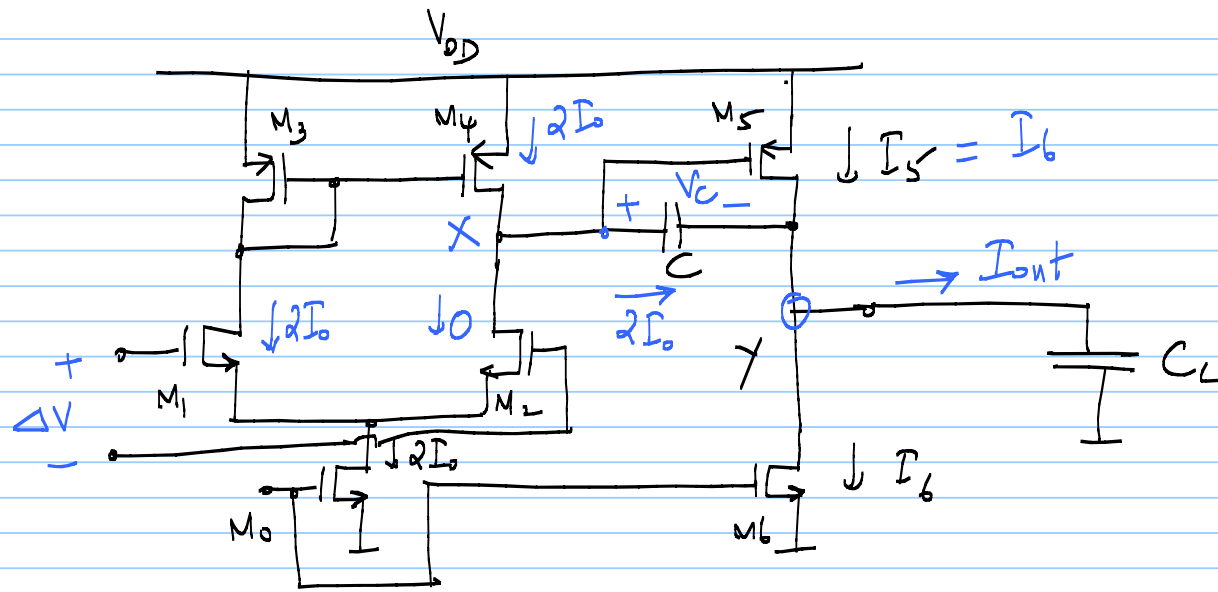

$$\left. \frac{dV_o}{dt} \right|_{t=0^+} = ?$$

$$\frac{dV_c}{dt} = \frac{2I_o}{C}$$

$$\text{KCL @ } Y : 2I_o + I_{S'} = I_{out} + I_o \quad @ \quad t = 0^+$$

$$V_{G5} = V_X ; \quad V_X(0^+) = V_X(0^-)$$

$$I_5(0^+) = I_5(0^-) = I_6 \Rightarrow I_{out} = 2I$$

$$\left. \frac{dV_o}{dt} \right|_{t=0^+} = \frac{2I_6}{C_L}$$

$$SR = \pm \frac{2I_6}{C_L}$$

$$G_{m2} \gg G_{m1}$$

$$(Z_1 \gg \omega u)$$

$$g_{m5} \gg g_{m1}$$

$$\text{normally } I_{5,6} \gg 2I_6$$

## Design Example

Specs :  $A_0 \geq 80 \text{ dB}$  ;  $f_u \geq 5 \text{ MHz}$  ;  $V_{opp} \geq 4 \text{ V}$


$SR \geq 10 \text{ V}/\mu\text{s}$  ;  $PM \geq 60^\circ$  (unity gain)

Design parameters :  $V_{DD} = 5 \text{ V}$  ,  $C_L = 10 \text{ pF}$  ,  $\mu_n C_{ox} = 50 \mu\text{A}/\text{V}^2$

$\mu_p C_{ox} = 25 \mu\text{A}/\text{V}^2$  ,  $V_{Tn} = V_{Tp} = 1 \text{ V}$  ,

$L_{min} = 2 \mu\text{m}$  ,  $C_{ox} = 1.5 \text{ fF}/\mu\text{m}^2$

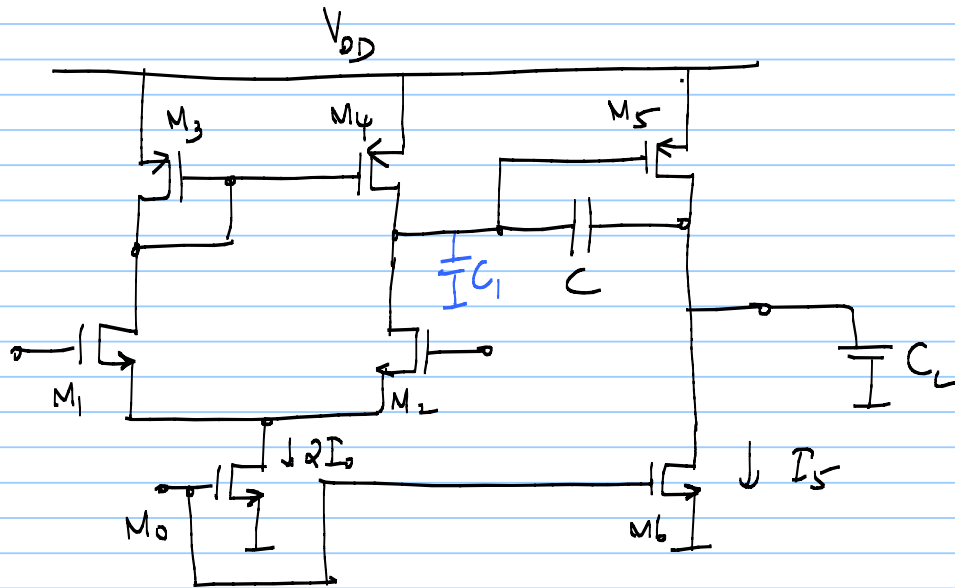$(\lambda L)_n = 0.04 \mu\text{m}/\text{V}$  ;  $(\lambda L)_p = 0.1 \mu\text{m}/\text{V}$



$$SR = \frac{2I_0}{C_L} / \frac{2I_0}{C}$$

$$10V/\mu s = \frac{2I_0}{10pF}$$

$$2I_0 = 100\mu A \leftarrow \text{overdesigned}$$

$$I_0 = 50\mu A$$

$$PM = 60^\circ$$

$$Z_1 \gg \omega_n \Rightarrow g_{m5} \gg g_{m1} \quad \text{e.g. } g_{m5} = 10 g_{m1}$$

$$\text{Assume } C_1 \ll C \Rightarrow \beta_2 = \frac{g_{m5}}{C_L} = \sqrt{3} \omega_u = \sqrt{3} \times 2\pi \times 5e^6$$

$$g_{m5} = \sqrt{3} \times 2\pi \times 5 \times 10^6 \times 10 \times 10^{-12} = 543.8 \mu S$$

$$g_{m1} = 54.4 \mu S$$

$$g_{m1} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_0} \Rightarrow \left(\frac{W}{L}\right)_1 = 0.6$$

$$\omega_u = \frac{g_{m1}}{C} \Rightarrow C = 1.73 \text{ pF}$$


$$\begin{aligned} SR &= \frac{2I_0}{C} = \frac{100 \mu A}{1.73 \text{ pF}} \\ &= 57.8 \text{ V}/\mu s \end{aligned}$$

$$V_{opp} = 4V \Rightarrow V_{o_{max}} = 4.5V ; V_{o_{min}} = 0.5V$$

$$V_{D_{sat}_s} = 0.5V \quad V_{D_{sat}_b} = 0.5V$$

$$V_{SQ_5} = 1.5V$$
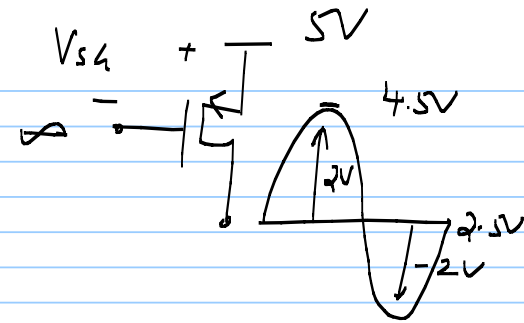
$$\left. \begin{array}{l} g_{m5} = 543.8 \mu S \\ V_{DSAT5} = 0.5V \end{array} \right\} \begin{array}{l} I_5 = 135 \mu A \\ \left(\frac{W}{L}\right)_5 = 43.2 \end{array}$$



$$I_6 = I_5 ; \quad V_{DSAT6} = 0.5V$$

$$\Rightarrow \left(\frac{W}{L}\right)_6 = \frac{1}{2} \left(\frac{W}{L}\right)_5 = 21.6$$

$$\Rightarrow \left(\frac{W}{L}\right)_6 = \frac{2I_6}{I_5} \cdot \left(\frac{W}{L}\right)_6 = \frac{100 \mu A}{135 \mu A} \cdot 21.6 = 16$$

$$V_{SG_{3,4}} \Big|_{I_D} = V_{SG5} \Big|_{I_S} \Rightarrow \frac{I_D}{(W/L)_3} = \frac{I_S}{(W/L)_5}$$

$$\Rightarrow \left(\frac{W}{L}\right)_{3,4} = \frac{50 \mu A}{135 \mu A} \cdot 43.2 = 16$$

$$A_0 = 80 \text{ dB} \Rightarrow A_1 \cdot A_2 = 10^4$$

$$g_{m1} \underset{r_{out1}}{(r_{ds2} \parallel r_{ds4})} \cdot g_{m5} \underset{r_{out2}}{(r_{ds5} \parallel r_{ds6})} = 10^4$$

If  $L = L_{min}$ , what are  $r_{ds}$  values?



$$L_{1,2} = L_{3,4} = L_5 = L_6 = 2 \mu\text{m}$$

$$L_5 = L_{3,4}$$

$$r_{ds} = \frac{1}{\lambda I}$$

$$\lambda_n = 0.02 / \text{V}$$

$$\lambda L = L_{\text{cut.}}; L = L_{\text{min.}}$$

$$\lambda_p = 0.05 / \text{V}$$

$$r_{ds_{1,2}} = 1 \text{ M}\Omega$$

$$r_{ds_{3,4}} = 0.4 \text{ M}\Omega$$

$$r_{ds_5} = 0.148 \text{ M}\Omega$$

$$r_{ds_6} = 0.37 \text{ M}\Omega$$

$$Y_{\text{out}_1} = 0.29 \text{ M}\Omega; Y_{\text{out}_2} = 0.11 \text{ M}\Omega$$

$$A_1 = 54.4 \mu\text{s} \times 0.29 \text{ M}\Omega = 15.8$$

$$A_2 = 543.8 \mu\text{s} \times 0.11 \text{ M}\Omega = 59.8$$

$$A_0 = A_1 A_2 = 944.8 \text{ V/V}$$

$$\text{Set } r_{d_{3,4}} = 1 \text{ M}\Omega \Rightarrow L_{3,4} = 5 \mu\text{m} = L_5$$


$$r_{d_{55}} = 0.37 \text{ M}\Omega$$

$$A_1 = g_{m_1} \cdot (0.5 \text{ M}\Omega) = 27.2$$

$$A_2 = g_{m_5} \cdot (0.185 \text{ M}\Omega) = 100.6$$

14/2/2020

Lec 17

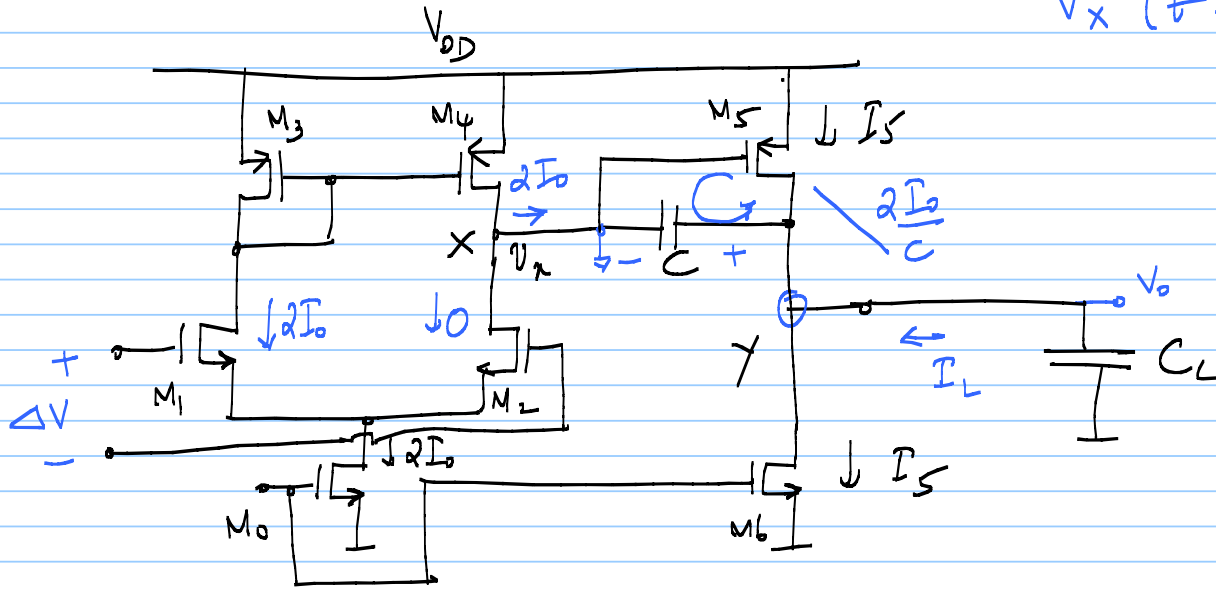

$$V_x(t=0^+) = V_x(t=0^-)$$

$$\left. \frac{dV_o}{dt} \right|_{t=0^+} = \frac{2I_0}{C_L}$$

\$v\_x \approx 0\$ after a short period of time due to fast neg. f.b. loop around \$M\_5\$

$$-\frac{I_L}{C_L} = \frac{dV_o}{dt} \Rightarrow I_L = \frac{2I_0}{C} \cdot C_L \Rightarrow \frac{dV_o}{dt} = -\frac{2I_0}{C}$$

$$\begin{aligned} \text{KCL @ } Y \Rightarrow I_{D5} &= I_S - 2I_0 - I_L \\ &= I_S - 2I_0 \left[ 1 + \frac{C_L}{C} \right] \end{aligned}$$


$$SR = \frac{2I_0}{C} = 57.8 \text{ V}/\mu\text{s}$$

We wanted  $10 \text{ V}/\mu\text{s}$

$2I_0$  can be reduced from  $100 \mu\text{A}$  to

$$\frac{1}{5.78} \times 100 \mu\text{A} = 17.3 \mu\text{A}$$

$$r_{ds} = \frac{1}{\lambda I}$$

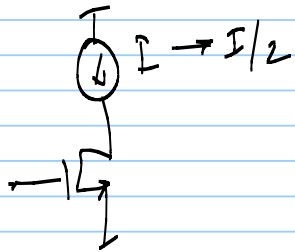

$$\text{gain} = g_m r_{ds}$$

$$\hookrightarrow = g_m' r_{ds}' = \frac{g_m}{\sqrt{2}} \cdot 2r_{ds} = \sqrt{2} g_m r_{ds}$$

With all  $L = L_{min}$ ,  $A_1 = 15.8$ ,  $A_2 = 59.8$

$$\text{If } Q \text{ falls to } 17.3 \mu\text{A}, \quad A_1' = \sqrt{5.78} A_1 \\ = 38 \text{ V/V}$$

$$\text{New } A_0 = A_1 A_2 = 2272.4$$

$$f_u' = \frac{g_{m1}'}{2\pi C} = \frac{f_u}{\sqrt{5.78}} = 2.1 \text{ MHz} \rightarrow \text{set } g_{m1}' = g_m \text{ by } \uparrow \left(\frac{W}{L}\right)_1 \\ \text{by } \sqrt{5.78} \quad \boxed{g_{m1} \approx 59.8 \mu\text{S}}$$

$$\Rightarrow \text{set } \left(\frac{W}{L}\right)_1 = 1.44$$

$$\Rightarrow A_1 = 5.78 \times 15.8 = 91.3 \text{ V/V}; \quad A_2 = 59.8 \text{ V/V}$$

$$A_0 = A_1 A_2 = 5459.7 \text{ V/V}$$

$$r_{ds1,2} = 5.78 \times 1 \text{ M}\Omega = 5.78 \text{ M}\Omega$$

$$r_{ds5} = 0.148 \text{ M}\Omega$$

$$r_{ds3,4} = 5.78 \times 0.4 \text{ M}\Omega \\ = 2.3 \text{ M}\Omega$$

$$r_{ds6} = 0.37 \text{ M}\Omega$$

$$\lambda_n = 0.04 \\ \lambda_p = 0.02 \text{ V}$$

$$L_{3,4} = L_5 = 5 \mu\text{m} \Rightarrow$$

$$r_{ds3,4} = 5.78 \text{ M}\Omega \quad \left\{ \lambda_p = 0.02 \right\}$$

$$r_{ds5} = 0.37 \text{ M}\Omega$$

$$\lambda_n = 0.02 \text{ V} \quad \left. \begin{array}{l} \lambda_p = 0.05 \text{ V} \\ \text{for } L_{\text{min}} = 2 \mu\text{m} \end{array} \right\}$$

$$r_{out1}' = 2.89 \text{ M}\Omega$$

$$A_1' = g_{m1}' \quad r_{out1}' = 172.8 \text{ V/V}$$

$$r_{out2}' = 0.185 \text{ M}\Omega$$

$$A_2' = g_{m2} \quad r_{out2}' = 110.63 \text{ V/V}$$

$$A_0' = A_1' A_2' = 19116.9 \text{ V/V} \quad \checkmark$$

\* check  $C_{gs5} \ll g_{m5} \cdot R_{out2} \cdot C$

\* check Mirror pole ( $M_{3,4}$ )  $\gg \omega_n$

$$\approx \frac{g_{m3,4}}{2C_{gs3,4}}$$

18/2/20


# Lec 18

Process variations - how to tackle?

$$b_{n-1} b_{n-2} \dots b_0 = 10 \dots 0$$


$$R_{nm} = 1k\Omega$$

$R, C, RC, g_m, \dots$

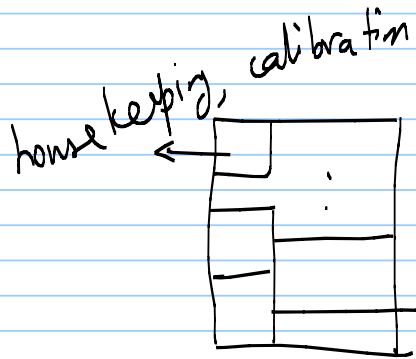

R-tuner, RC-tuner  
C-tuner,
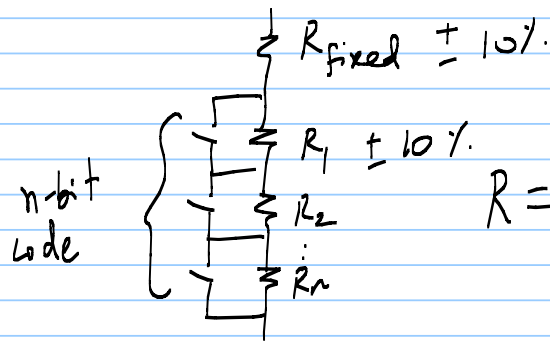
$$R = 1k\Omega \pm 10\% \Rightarrow 900\Omega \text{ to } 1.1k\Omega$$




$$R = R_{fixed} + K_{var.}$$

$$f(b_{n-1} b_{n-2} \dots b_0)$$

$$\left\{ 990 - 1010 \Omega \right\}$$




# Pole zero cancellation compensation

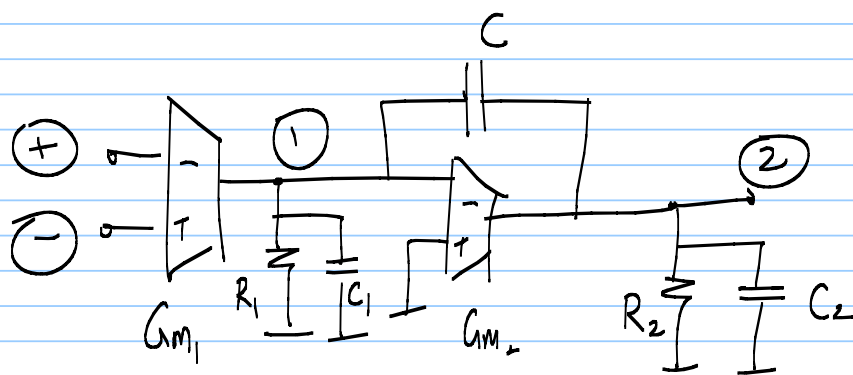

$$p_1 \approx \frac{-1}{R_1 \cdot (G_{m2} R_2) C}$$

$$p_2 \approx \frac{-1}{\left[ R_2 \parallel \left( \frac{C}{C+C_1} \right) \cdot \frac{1}{G_{m2}} \right] \cdot \left[ C_2 + \frac{C C_1}{C+C_1} \right]}$$

$$z_1 = + \frac{G_{m2}}{C} \rightarrow$$

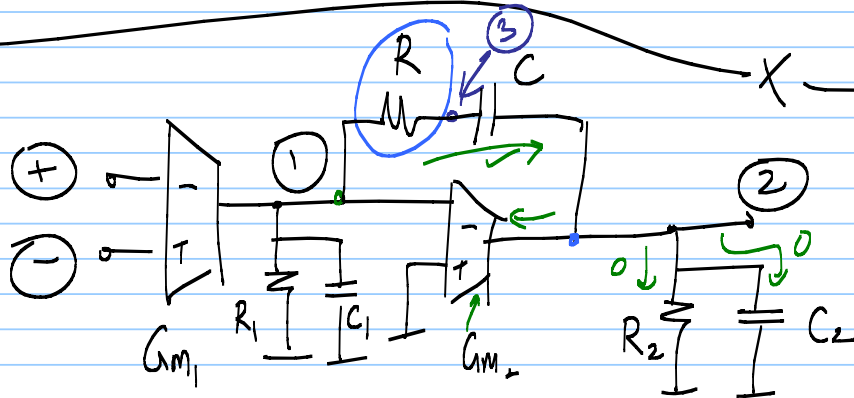


$$p_1 \approx \frac{-1}{R_1 (G_{m2} R_2) C}$$

$$p_2 \approx \frac{-G_{m2}}{C_1 C_2 + C C_1 + C C_2}$$

$$z_1 = \frac{+1}{C \left( \frac{1}{Gm_2} - R \right)} ; p_3 \approx \frac{-1}{R \cdot C_1}$$

1) Push  $z_1$  to  $\infty$

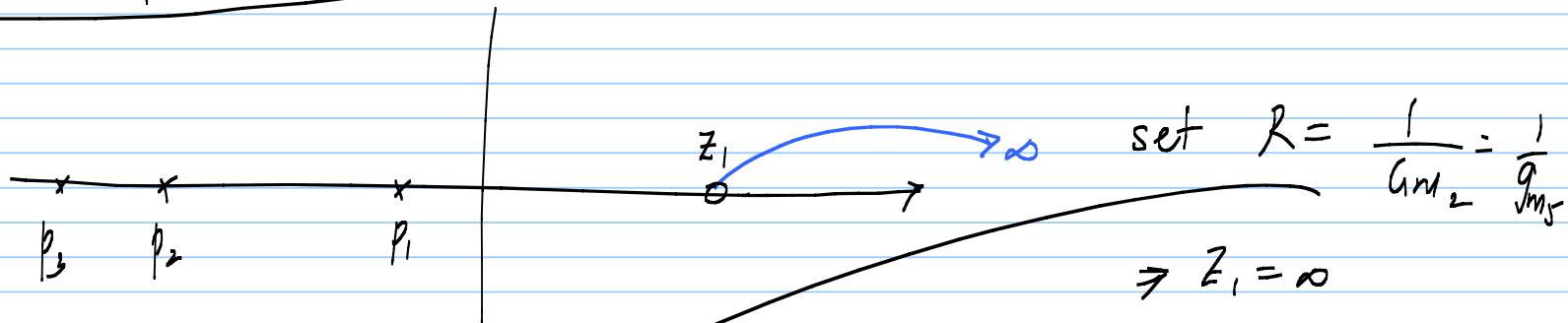

$p_1 =$  stays the same

$p_2 =$  " "

$$p_3 = \frac{-1}{RC_1} = - \frac{Gm_2}{C_1}$$


2) What happens if  $R > \frac{1}{G_{m2}} \Rightarrow$  zero moves into LHP

$\Rightarrow$  option of cancelling  $p_2$  or  $p_3$   
 $\uparrow$   
first ND pole

If you cancel  $p_2$ , PM improves or BW improves

$$z_1 = p_2 \Rightarrow \frac{1}{C\left(\frac{1}{G_{m2}} - R\right)} = \frac{-G_{m2}}{\sum C_i C_j} \Rightarrow \text{gives value of } R$$

$$R = f(G_{m2})$$

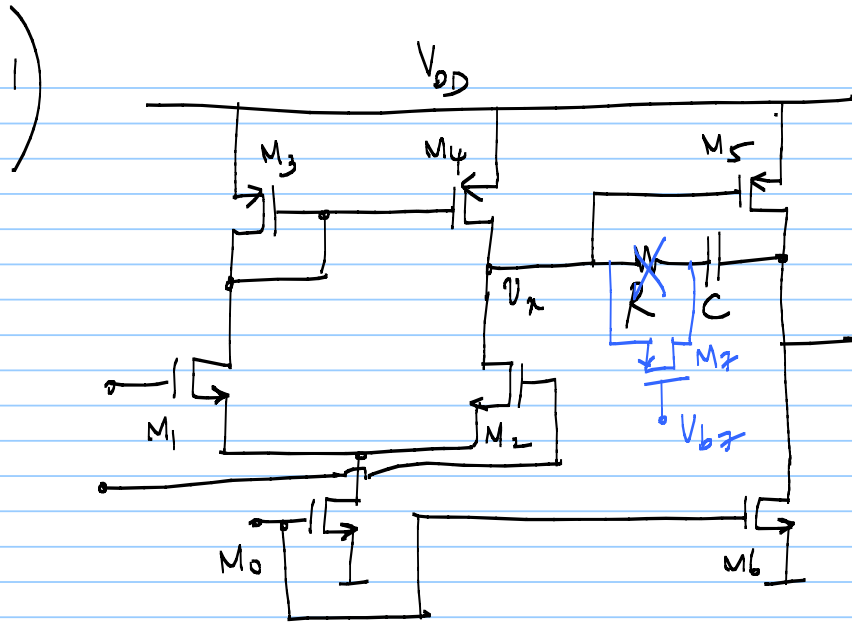



set  $R$  to depend on  $g_{m2}$   
or  $g_{m5}$

$M_7$  is in triode region

$$R_{M7} = r_{ds7} = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_7 (V_{sg7} - V_{T7} - V_{sd7})}$$

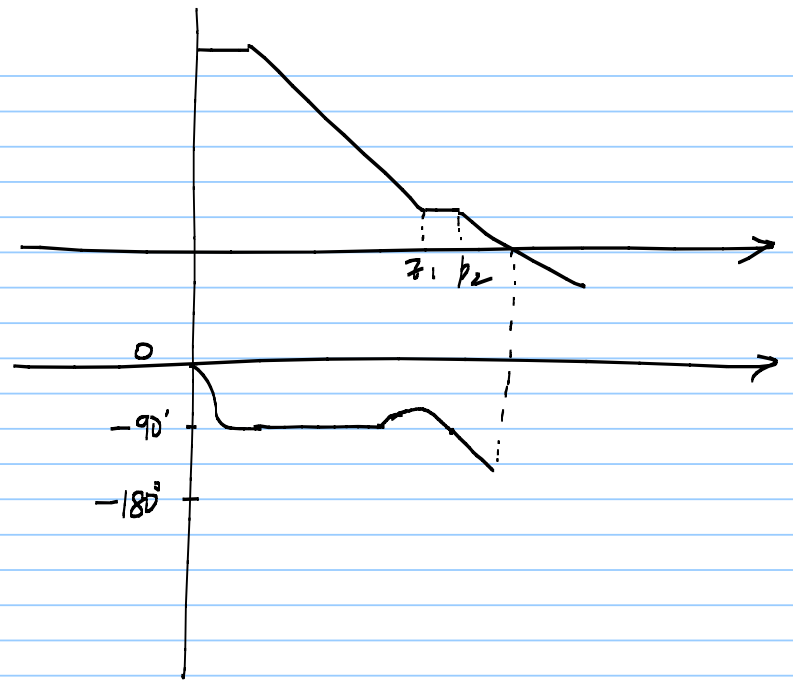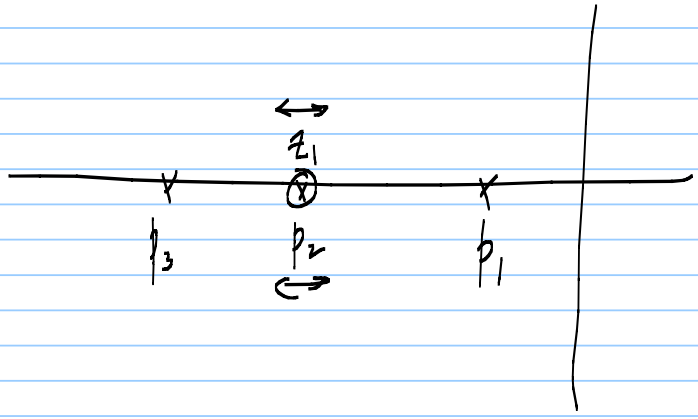
$$g_{m5} = \mu_p C_{ox} \left(\frac{W}{L}\right)_5 (V_{sg5} - V_{T5})$$





19/2/20

Lec 19

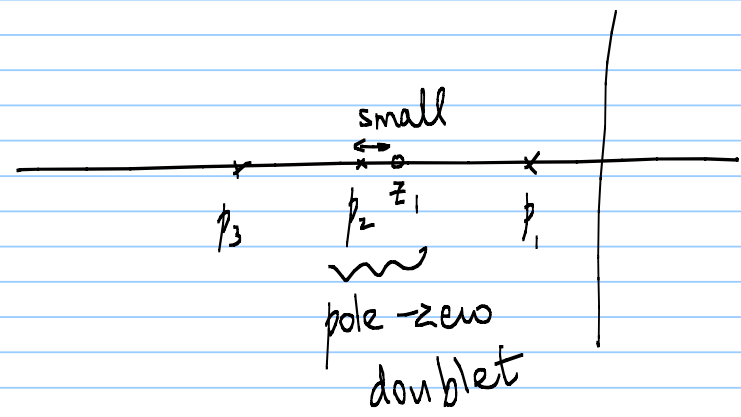

causes very slow-settling component in step response





$$V_{B7} = V_{DD} - V_{S95} - V_{S97}$$

$$V_E = V_{DD} - V_{S99} - V_{S10}$$

set  $V_{B7} = V_E$

e.g.  $V_{S99} = V_{S95}$      i.e.  $\frac{I_5}{(W/L)_5} = \frac{I_8}{(W/L)_9}$

$$V_{S97} = V_{S10}$$

choose  $M_{10}$  so that its  $g_{m10} = g_{ds7}$   
 if  $\left(\frac{W}{L}\right)_7 = \left(\frac{W}{L}\right)_{10}$

as Temp  $\uparrow$


$$I_D = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right) (V_{S99} - V_T)^2$$

$\Rightarrow V_E = (V_{DD} - V_{S99} - V_{S10})$  has to decrease

$V_{SG5}$  also increase due to  $\downarrow$  in  $\mu p$

$V_{SG7} \uparrow \Rightarrow g_{ds7}$  is constant  $\Rightarrow R$  is constant

Case 2 :

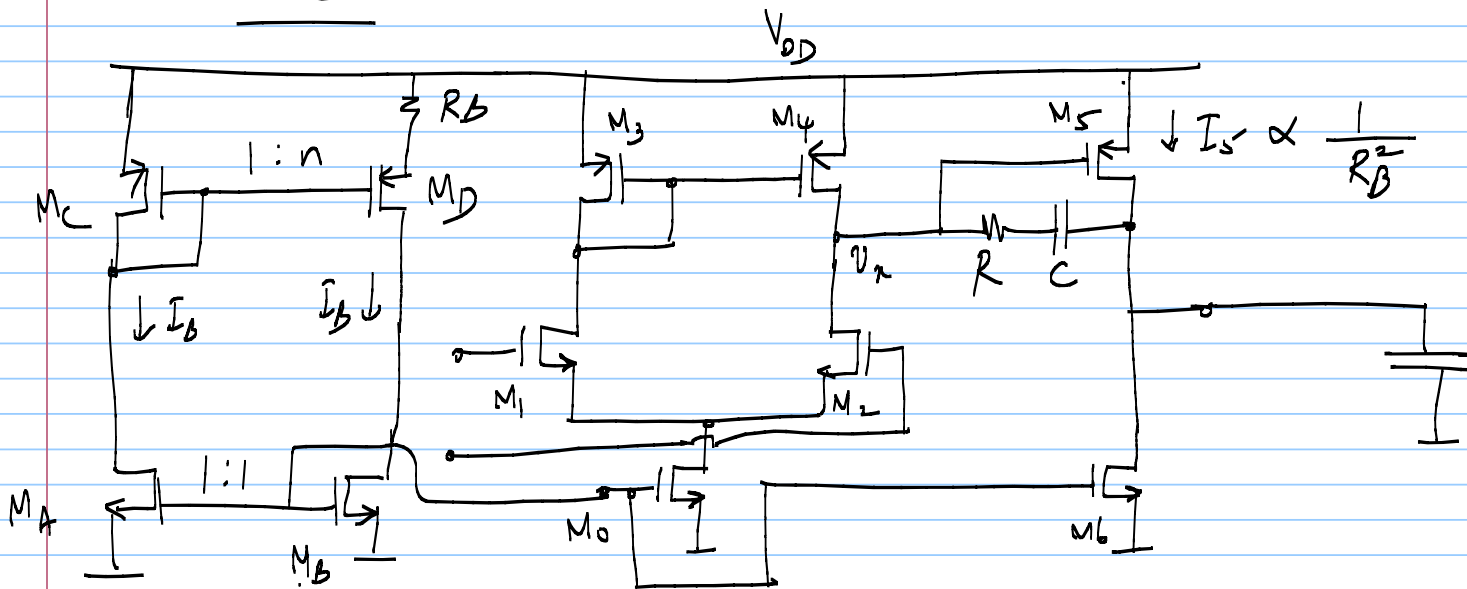

We want  $R \propto \frac{1}{g_{m5}}$


We can also use a

passive  $R$ , and

force  $g_{m5}$  to

track  $\frac{1}{R}$

$\Rightarrow$  change  $I_S$

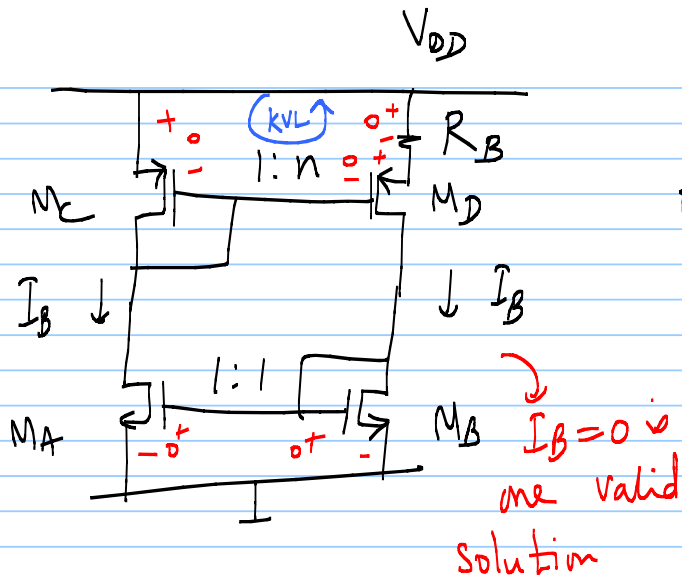

## Constant $g_m$ bias circuit

KVL around  $M_C M_D$  loop:

$$V_{S_{AC}} = V_{S_{AD}} + I_B \cdot R_B$$

$$V_{T_C} + V_{ov_C} = V_{T_D} + V_{ov_D} + I_B \cdot R_B$$

$$V_{ov_C} = \sqrt{n} \cdot V_{ov_D}$$

$$V_{ov_C} = \frac{V_{ov_C}}{\sqrt{n}} + I_B R_B$$

$$g_m = \frac{2 I_{bias}}{V_{S_{A}} - V_T} = \frac{2 I_{bias}}{V_{ov}} \Rightarrow \frac{2 I_B}{g_{m_C}} = \frac{1}{\sqrt{n}} \frac{2 I_B}{g_{m_C}} + I_B R_B$$

$$\text{If } I_B \neq 0 ; \quad \frac{2}{g_{m_C}} = \frac{1}{\sqrt{n}} \frac{2}{g_{m_C}} + R_B \quad \left\{ \text{Need a startup circuit} \right\}$$


$$g_{m_c} = \frac{2(1 - \frac{1}{\sqrt{n}})}{R_B} \quad \leftarrow \text{set } g_{m_s} \text{ based on this}$$

$$\sqrt{2\beta_p \left(\frac{W}{L}\right)_c I_B} = \frac{2(1 - \frac{1}{\sqrt{n}})}{R_B}$$

$$I_B \propto \frac{1}{\beta_p R_B^2}$$

Choose  $R_B$  &  $R$  to be same type of resistor!

### 3-stage opamp

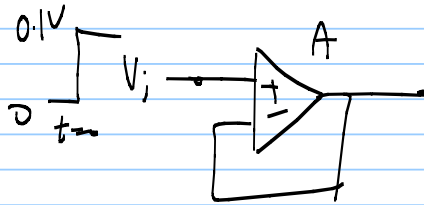

$$0.1V \quad + \quad \frac{A}{1+A} \cdot V_i$$



$$- \quad -$$

Ideal Opamp  $\rightarrow$   $R_{in} = \infty$  VCVS  
 $R_o = 0$   
 $A = \infty$

\* reduce  $V_e$  even further

Ideal OTA  $\rightarrow$   $R_{in} = \infty$  VCCS  
 $R_o = \infty$   
 $G_m = \infty$


### 2-stage opamp

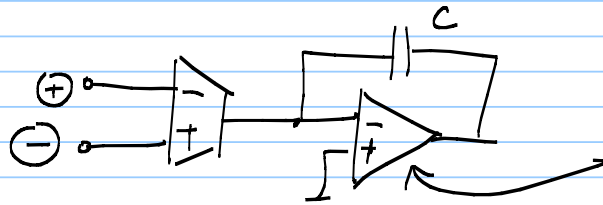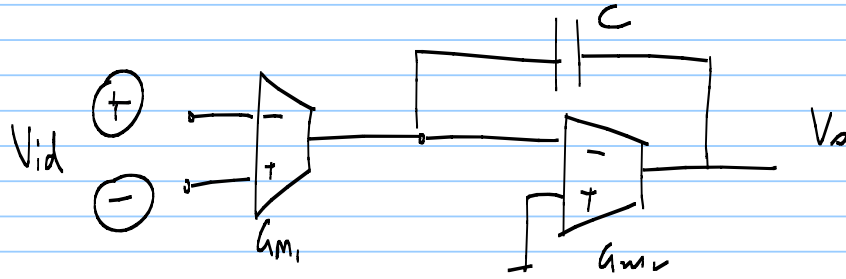

Replace  $G_{m2}$  by

2-stage opamp

## Nested Miller 3-stage opamp

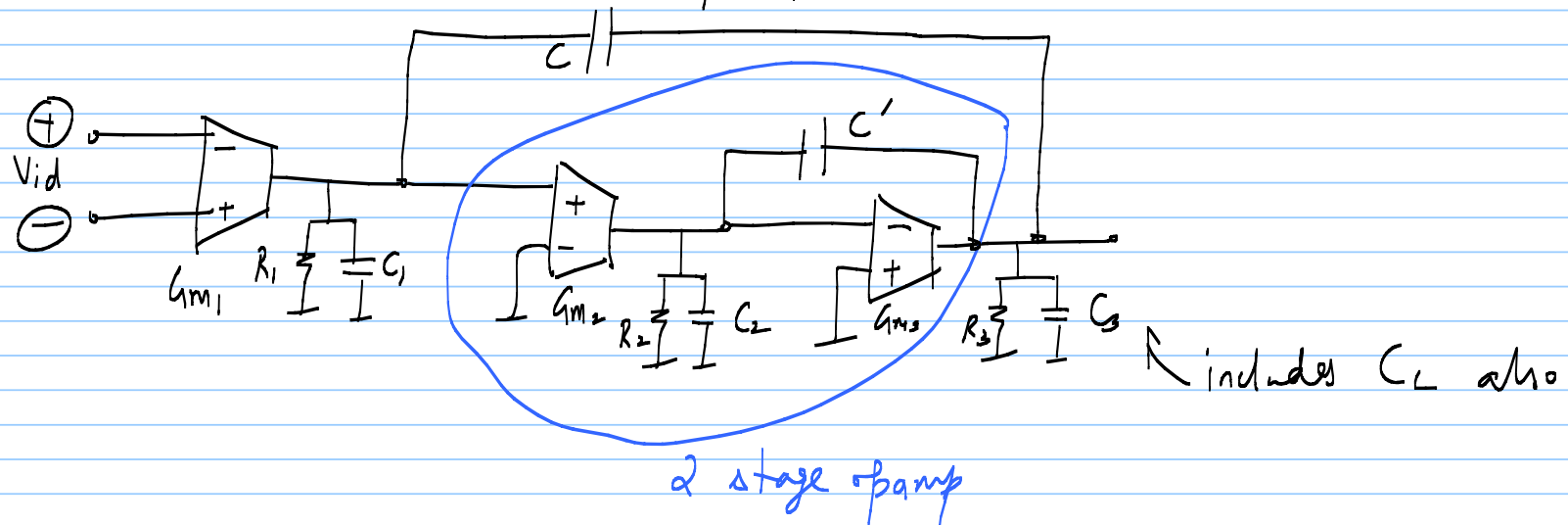

$$\text{DC gain } A_0 = (G_{m1} R_1) (G_{m2} R_2) (G_{m3} R_3)$$

$$\omega_u = \frac{G_{m1}}{C} ; \quad \omega_d = p_1 = \frac{\omega_u}{A_0}$$

2 ND poles :  $p_2, p_3$  ; at least 2 zeros

## Conditions for a 'good' design:

1)

$$\frac{G_{m2}}{C'} \gg \omega_u$$

↪ VGF of inner opamp


⇒ Speed of 3-stage opamp is typically lower than that of 2-stage opamp.

2)




$$p_3 \gg \underbrace{\frac{G_{m2}}{C'}}_{\omega_u}$$

20/2/2020

Lec 20


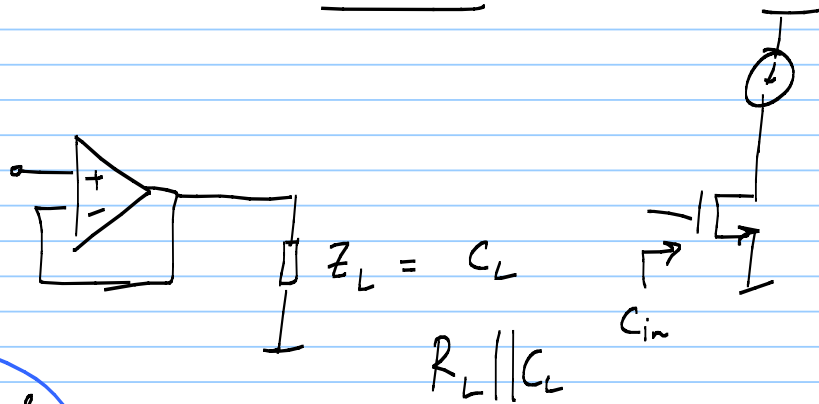


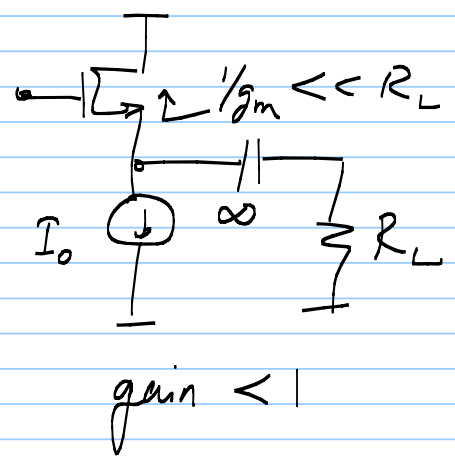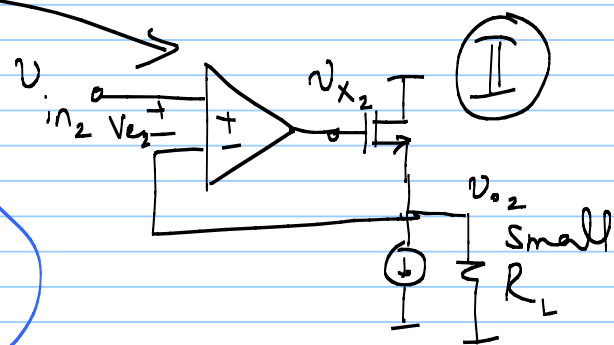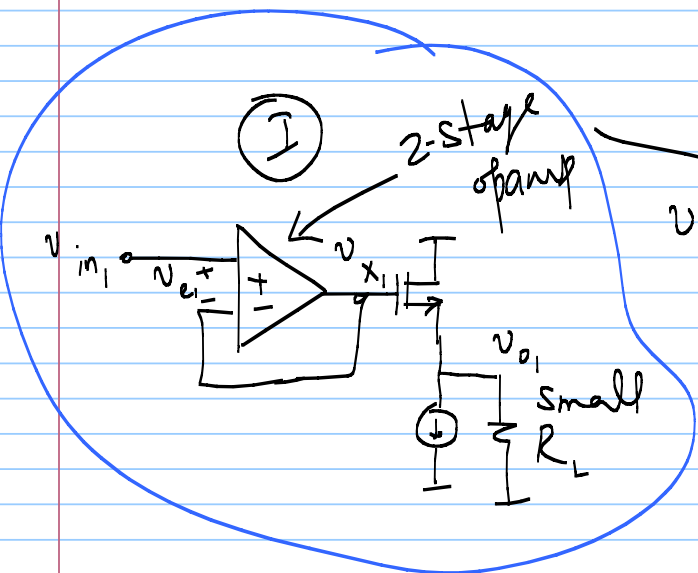
drive small  $R_L$   
 $\Downarrow$   
 CDA





" " 3-stage amp

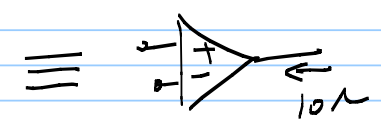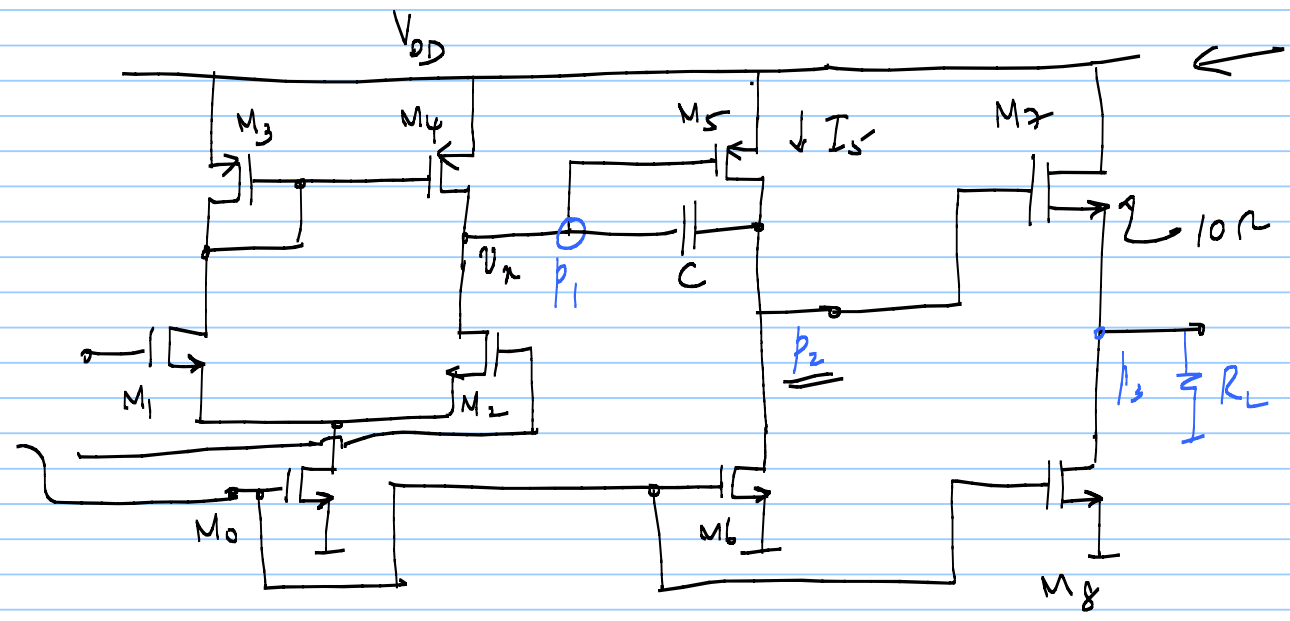

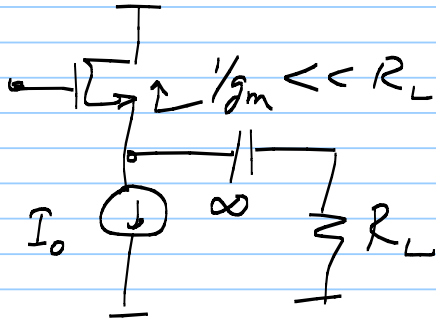

gain  $< 1$

$$g_m R_L = 10$$


$$\text{gain} = \frac{g_m R_L}{1 + g_m R_L} = \frac{10}{11} \approx 0.91$$

Case I:  $v_{x_1} = v_{in_1} - v_{e_1}$   
 $v_{o_1} = 0.91 v_{x_1}$


Case II:  $v_{o_2} = v_{in_2} - v_{e_2}$   
 $v_{x_2} = 1.1 v_{o_2}$  ✓

$v_{e_1}$  vs  $v_{e_2} \leftarrow$  will be about the same


# Stability in case II

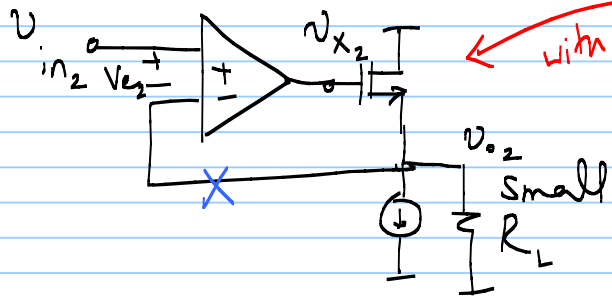

with CDA

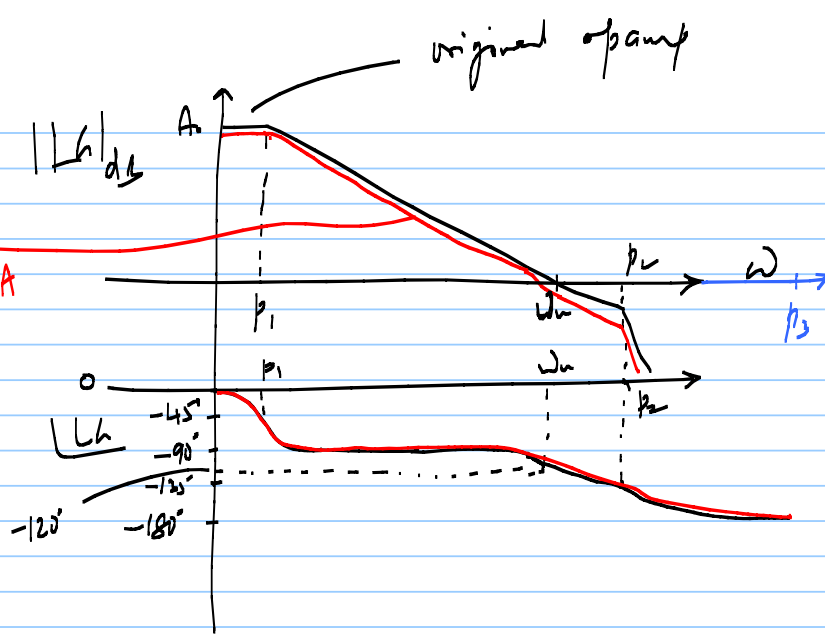

e.g.  $PM = 60^\circ$

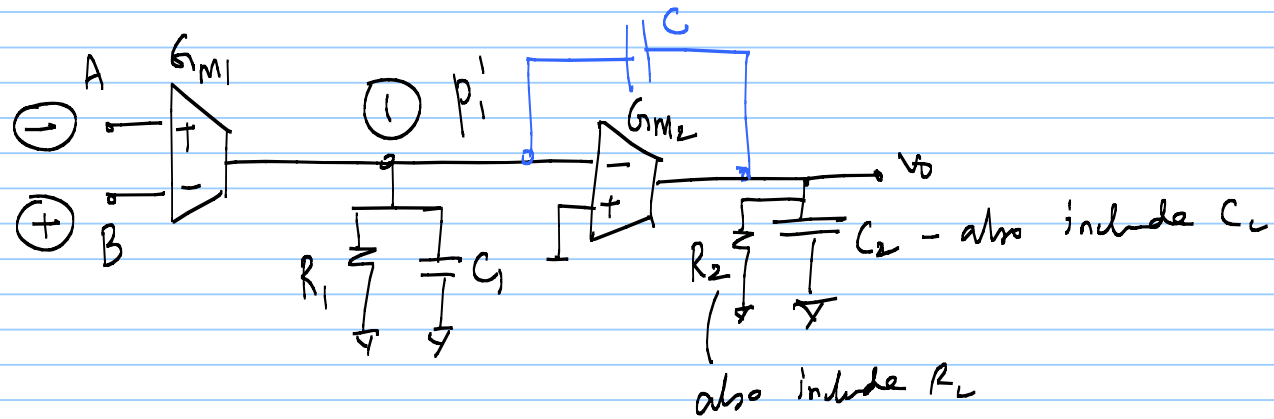


In our example,

$$G_{m2} = g_{m5} \approx 574 \mu S \approx 0.5 \text{ mS}$$

If  $R_L = 2 \text{ k}\Omega$  is the load

$$\Rightarrow A_2 = G_{m2} (R_L \parallel R_c) = 0.5 \text{ mS} \times (130 \text{ k}\Omega \parallel 2 \text{ k}\Omega) \approx 1$$

$$A_1 \approx 170$$

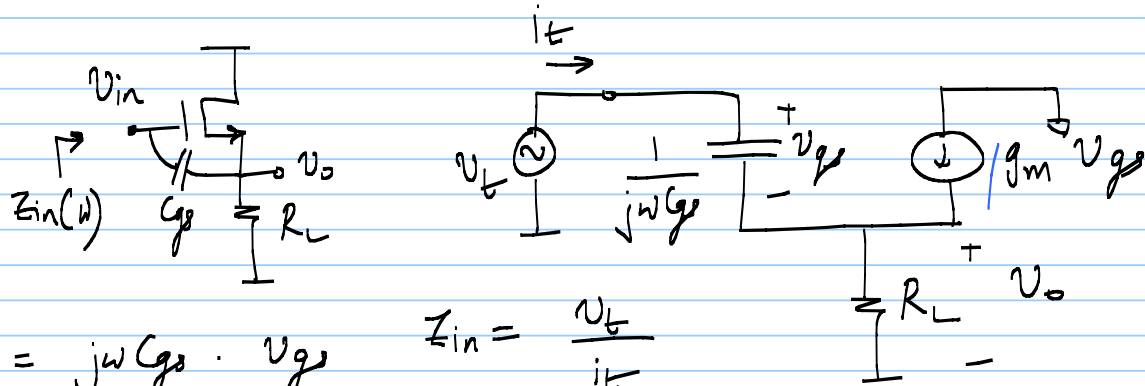


$$i_t = j\omega C_{gs} \cdot v_{gs} \quad Z_{in} = \frac{v_t}{i_t}$$

$$v_t = v_{gs} + v_o$$


$$= v_{gs} + [j\omega C_{gs} \cdot v_{gs} + g_m v_{gs}] \cdot R_L$$

$$v_t = v_{gs} [1 + g_m R_L + j\omega C_{gs} R_L]$$
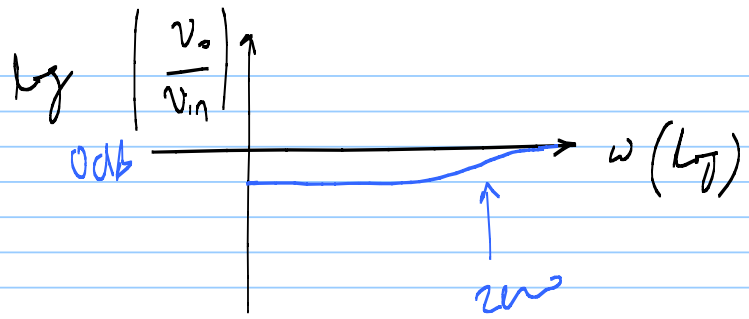
$$= \frac{1 + g_m R_L + j\omega C_{gs} R_L}{j\omega C_{gs}} \cdot i_t \Rightarrow Z_{in}(j\omega) = \frac{1 + g_m R_L + j\omega C_{gs} R_L}{j\omega C_{gs}}$$





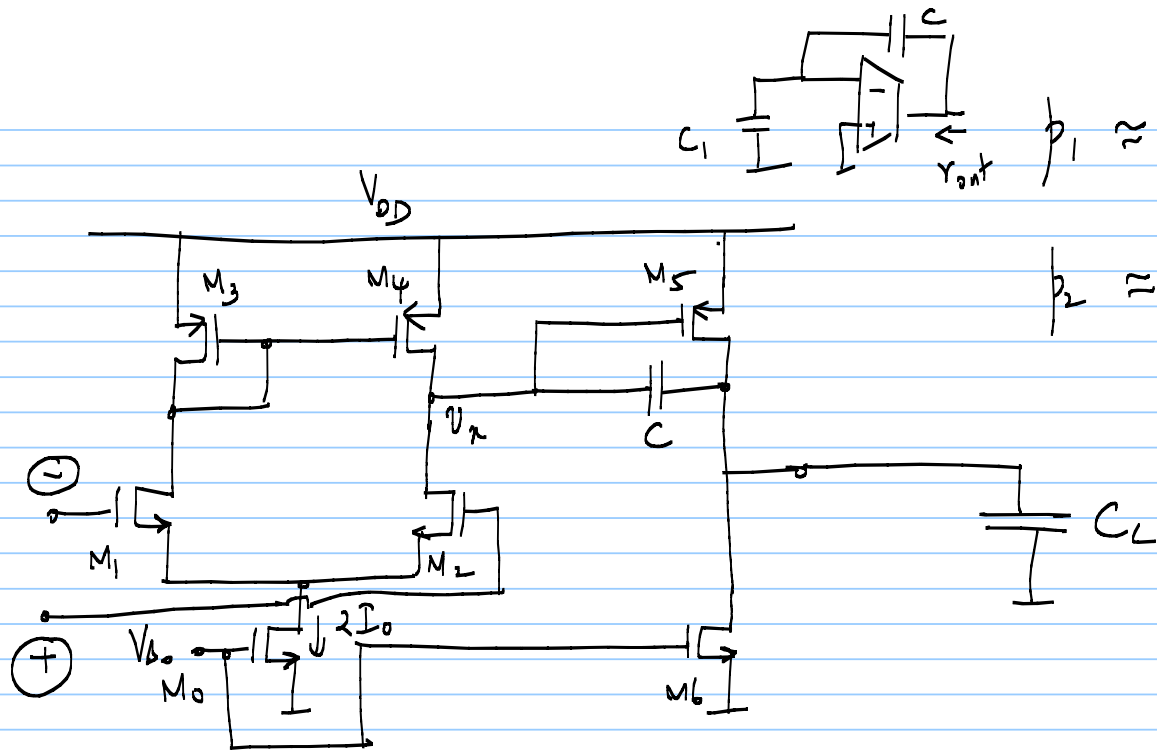

$$p_1 \approx \frac{-1}{r_{out1} \cdot (g_{m5} r_{out2}) C}$$

$$p_2 \approx \frac{-1}{\left(\frac{C+C_1}{C} \cdot \frac{1}{g_{m5}}\right) C_L}$$

$$Z_1 = \frac{+g_{m5}}{C}$$


$$\omega_u = \frac{g_{m1}}{C}$$

$$r_{out} = \frac{(C+C_1)}{C} \cdot \frac{1}{g_{m2}} \quad \checkmark$$

set  $g_{m5} \gg g_{m1}$
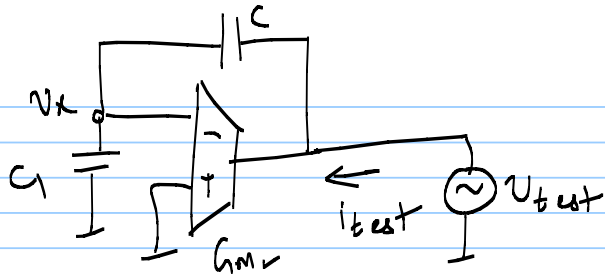
$$\frac{C}{C+C_1} \cdot \frac{1}{g_{m2}} \quad \times$$






$$v_x = \frac{C}{C + C_1} \cdot v_{test}$$


$$i_{test} = G_{mL} \cdot v_x = \frac{G_{mL} \cdot C}{C + C_1} \cdot v_{test}$$


$$Y_{out} = \left( \frac{C + C_1}{C} \right) \cdot \frac{1}{G_{mL}}$$
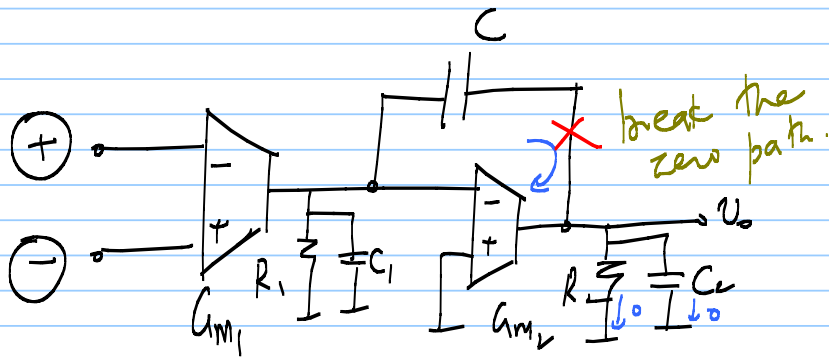
$$Z_i = + \frac{G_{mL}}{C} \quad \times$$





a)  $Z_i ; v_o = 0$

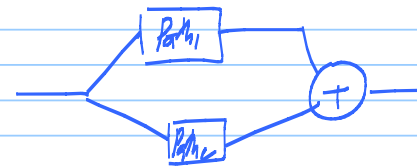

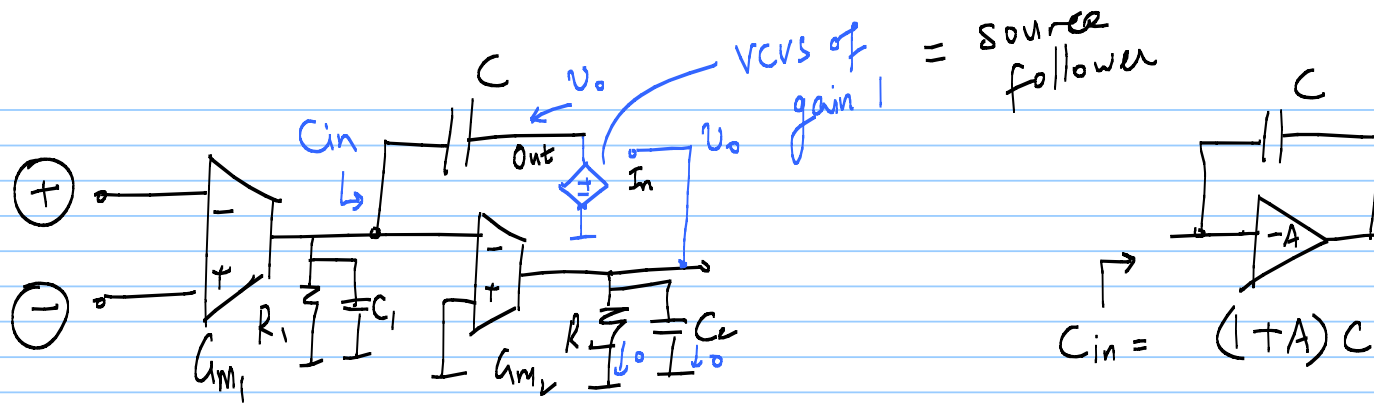

$$C_{in} = (1 + G_{m2}R_2)C$$

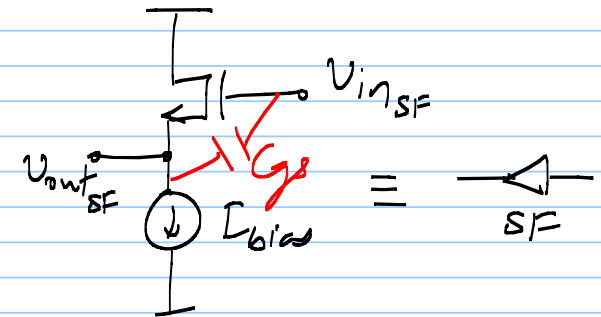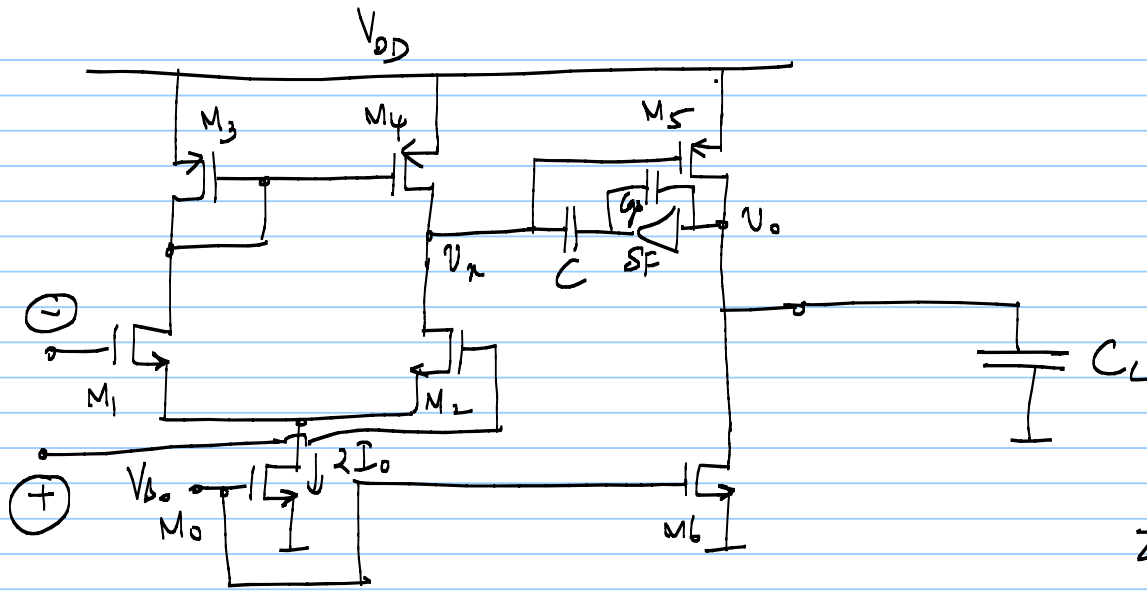


$$Z_{\text{zero}} = \frac{+g_{m5}}{\left( \frac{C \cdot C_{gs}}{C + C_{gs}} \right)} \rightarrow \omega_n$$

26/2/20

Lec 22

Fully Differential Opamps

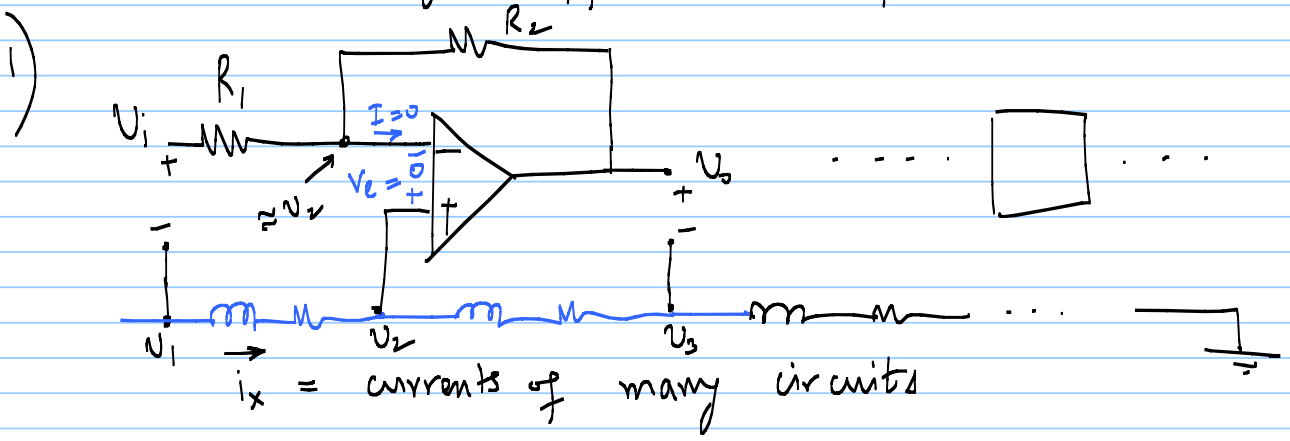




We want  $\frac{v_0}{v_i} = -\frac{R_2}{R_1} + ( )$

$i_x =$  currents of many circuits

$v_1, v_2, v_3 =$  functions of  $i_x$

$v_0 =$  function of  $i_x$

2)

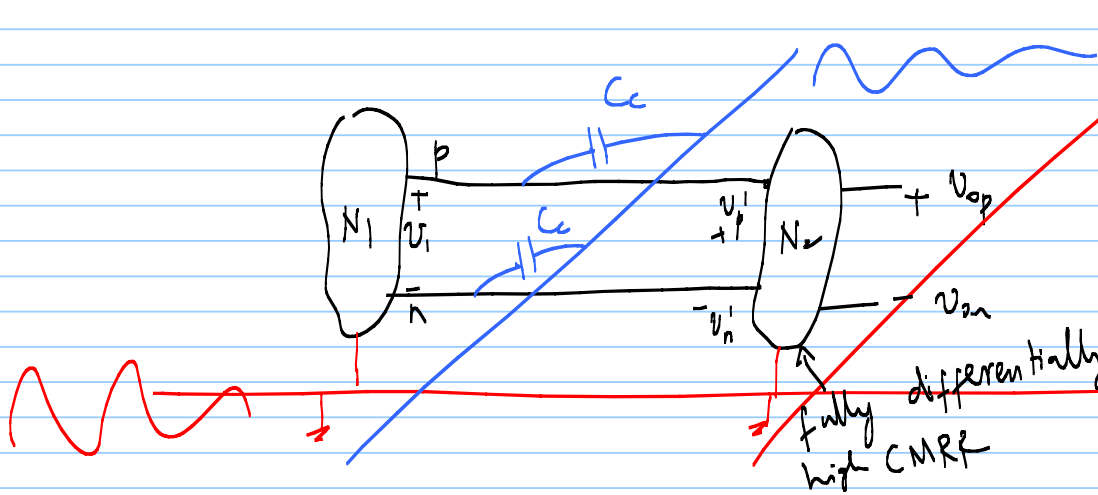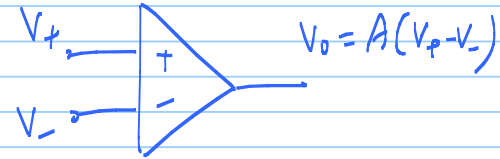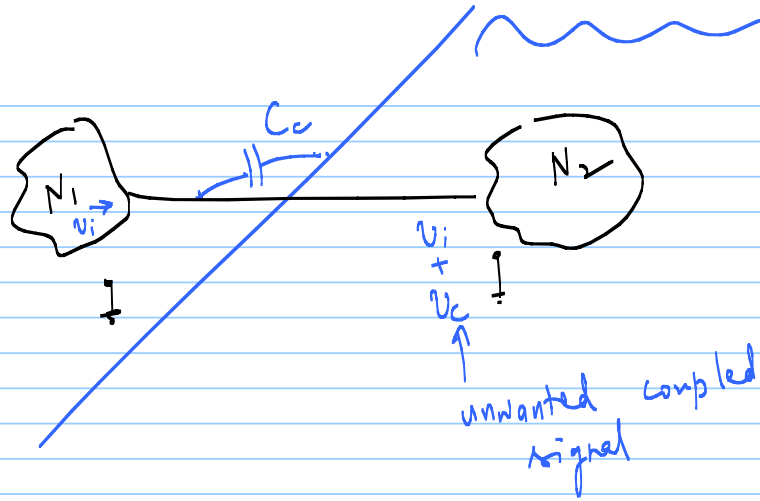

$$v_p - v_n = v_i$$


$$v_p' = v_p + v_c$$

$$v_n' = v_n + v_c$$

$$v_i' = v_p - v_n$$

common-mode signal to  $p$  &  $n$  lines

fully differentially, high CMRR

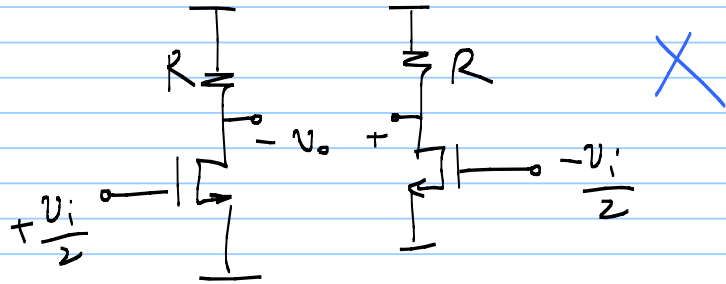


$$A_{dm} = \frac{v_o}{v_i} = g_m R$$

$$A_{cm} = A_{dm}$$

$$CMRR = 1 = 0 \text{ dB}$$

"pseudo-differential" amplifier

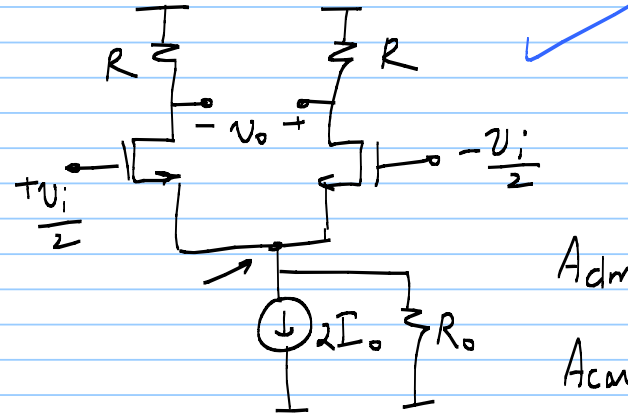


$$A_{dm} = \frac{v_o}{v_i} = g_m R$$

$$A_{cm} = \frac{g_m R}{1 + 2 g_m R_0}$$

high CMRR


"fully differential" amplifier

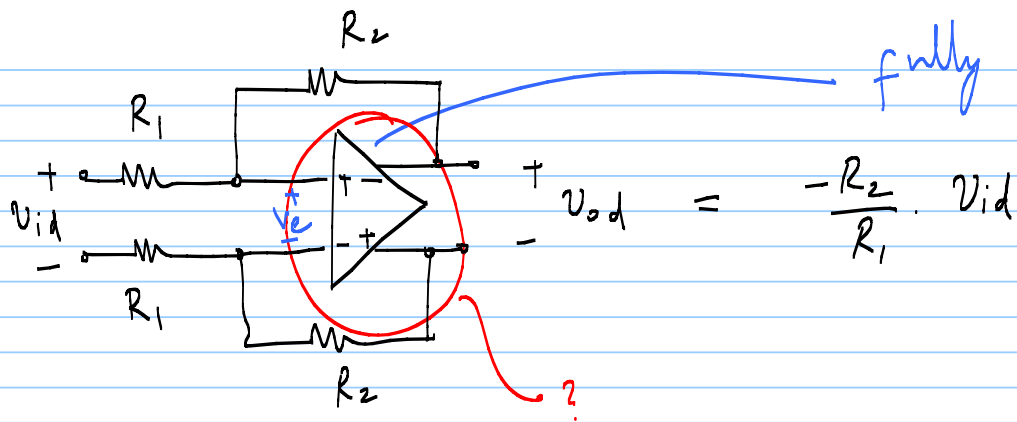


$$R_{in} = \infty$$

$$R_o = \text{large (OTA)}$$
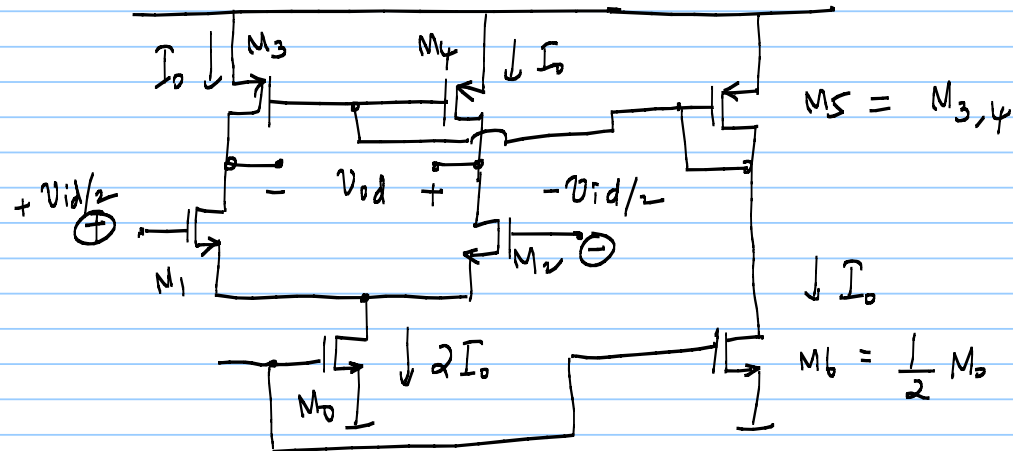
$$A = \text{large} \Rightarrow V_e \rightarrow 0$$



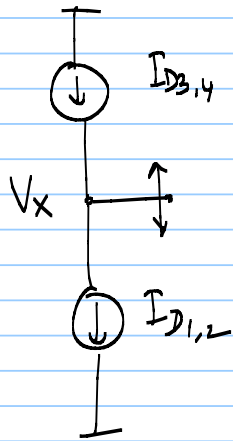Slight mismatches in  $M_0 - M_6$  or  $M_5 - M_{3,4}$  will cause  $I_{D3,4}$  &  $I_{D1,2}$  to be different



$$I_f \quad I_{D_{3,4}} > I_{D_{1,2}} \Rightarrow V_x \uparrow$$


$$\quad \quad \quad < \quad \quad \quad \Rightarrow V_x \downarrow$$

$M_{1,2}$  or  $M_{3,4}$  could move into triode region

\* Output common-mode is not set properly.

$$V_{ocm} = \frac{V_{o+} + V_{o-}}{2}$$





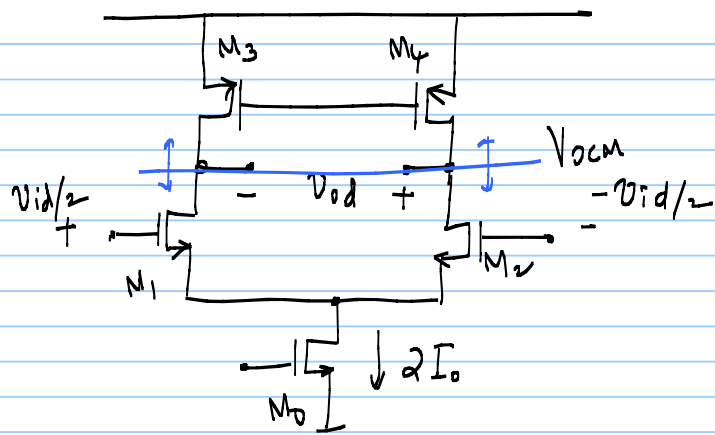


Use Negative f.b. to set Vocm


- \* Sense Vocm
- \* Compare Vocm to desired value Vref
- \* Employ feedback to drive Vocm → Vref

1) Sense Vocm:

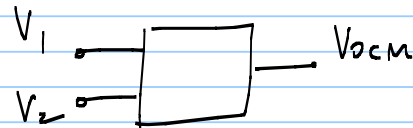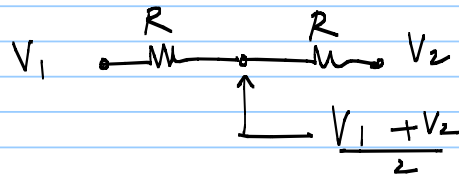


2) Compare Vocm to Vref:

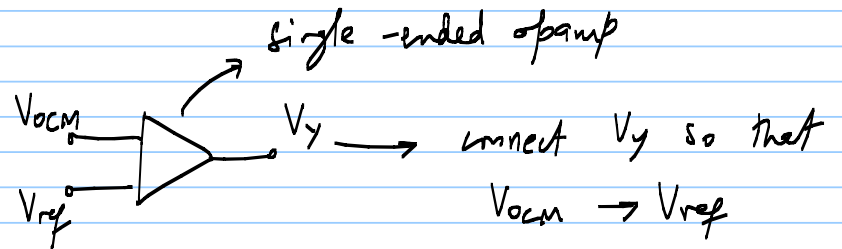

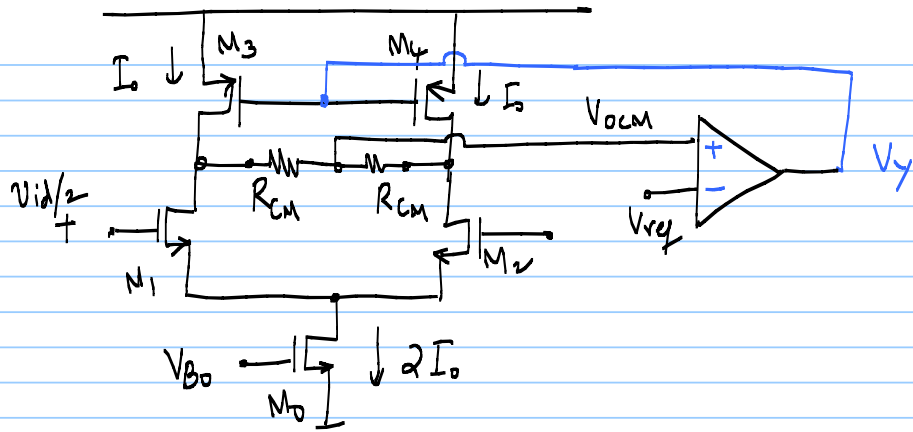


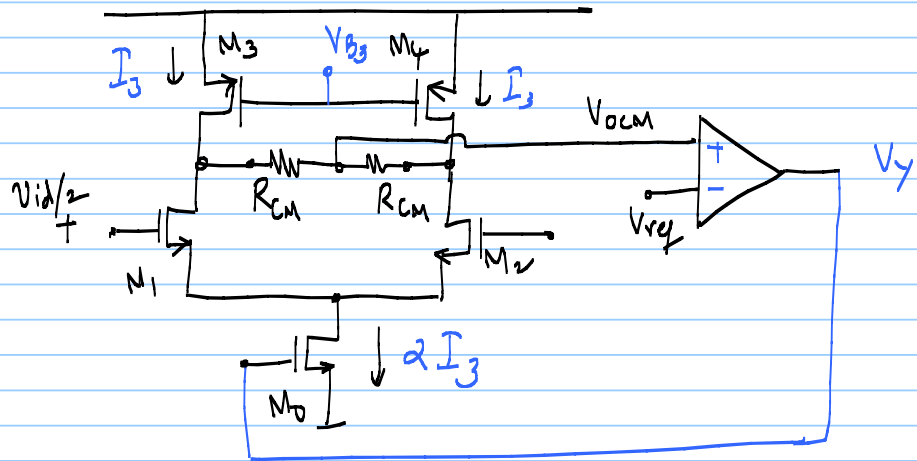
→ Set  $M_0$  current & f.b. to  $V_{a3,4}$



27/2/20

Lec 23

CMFB network

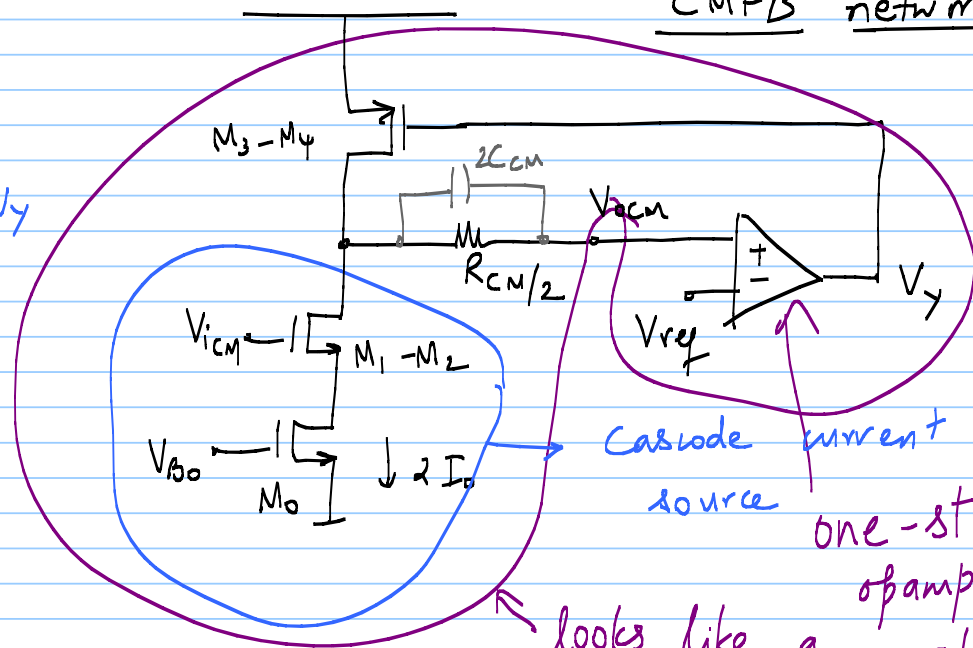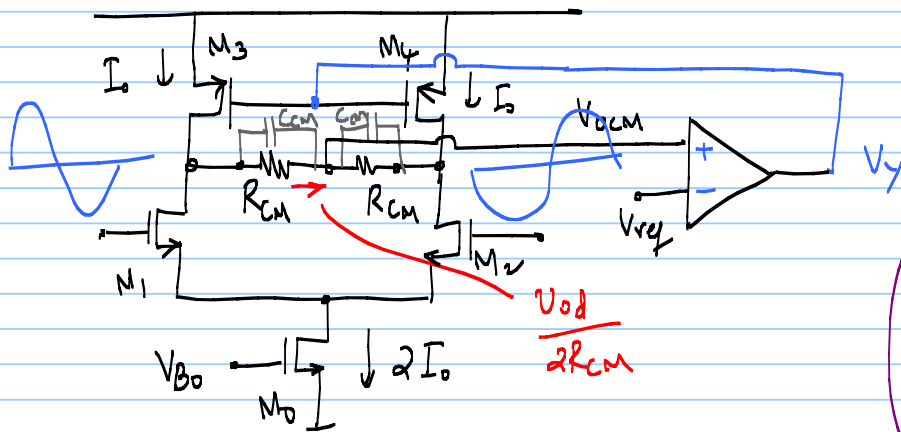


differ. gain  $\frac{V_{od}}{V_{id}} = g_{m1} (r_{ds2} \parallel r_{ds4} \parallel R_{cm})$

$R_{cm}$  - chosen to be much larger than  $r_{ds2}, r_{ds4}$


$R_{cm} \sim M \Omega$  is possible  $\rightarrow$  comes with parasitic cap.  $C_{cm}$

one-stage opamp  
looks like a 2-stage opamp


Cascode current source

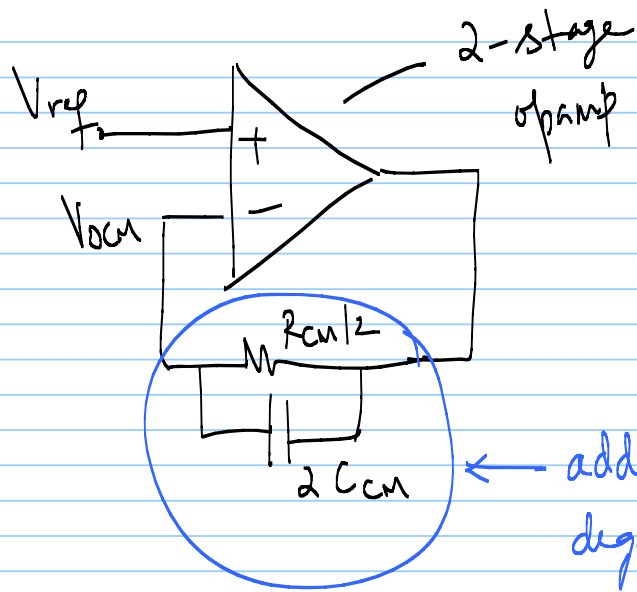

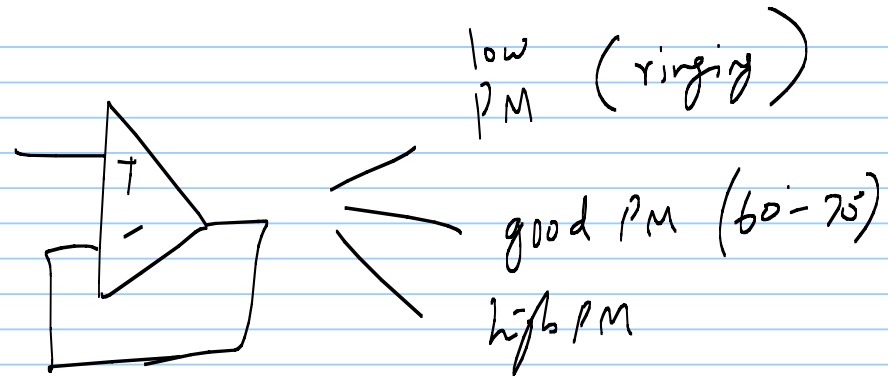← adds phase shift,  
degrades PM further



\* You have to compensate the CMFB loop

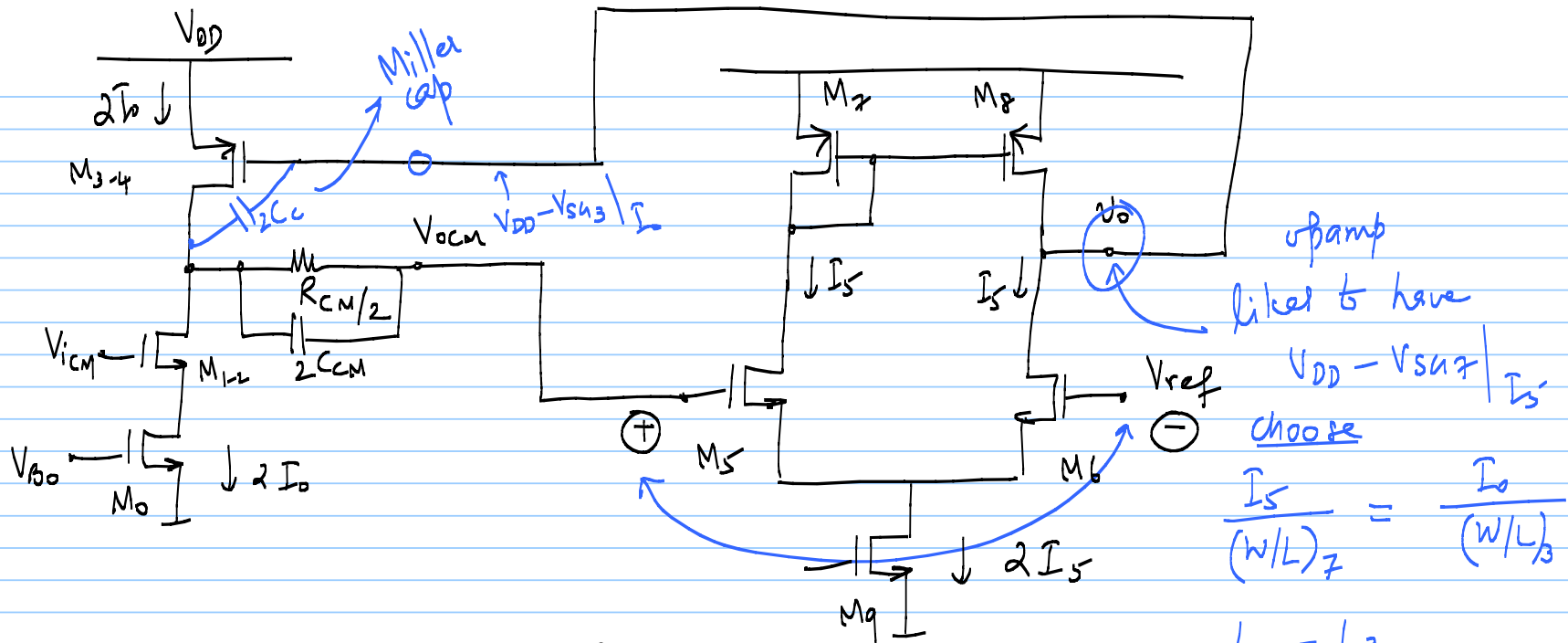

$$\frac{I_5}{(W/L)_7} = \frac{I_0}{(W/L)_3}$$


$$L_7 = L_3$$

Normally  $I_5 \ll I_0$


CMFB :

$$\omega_{u_{CM}} = \frac{g_{m5}}{2C_C}$$

$$DC \text{ gain} = g_{m5} (r_{ds6} || r_{ds8}) \cdot g_{m_{3-4}} (r_{ds_{3-4}} || (g_{m_{1-2}} r_{ds_{1-2}} \cdot r_{ds0}))$$

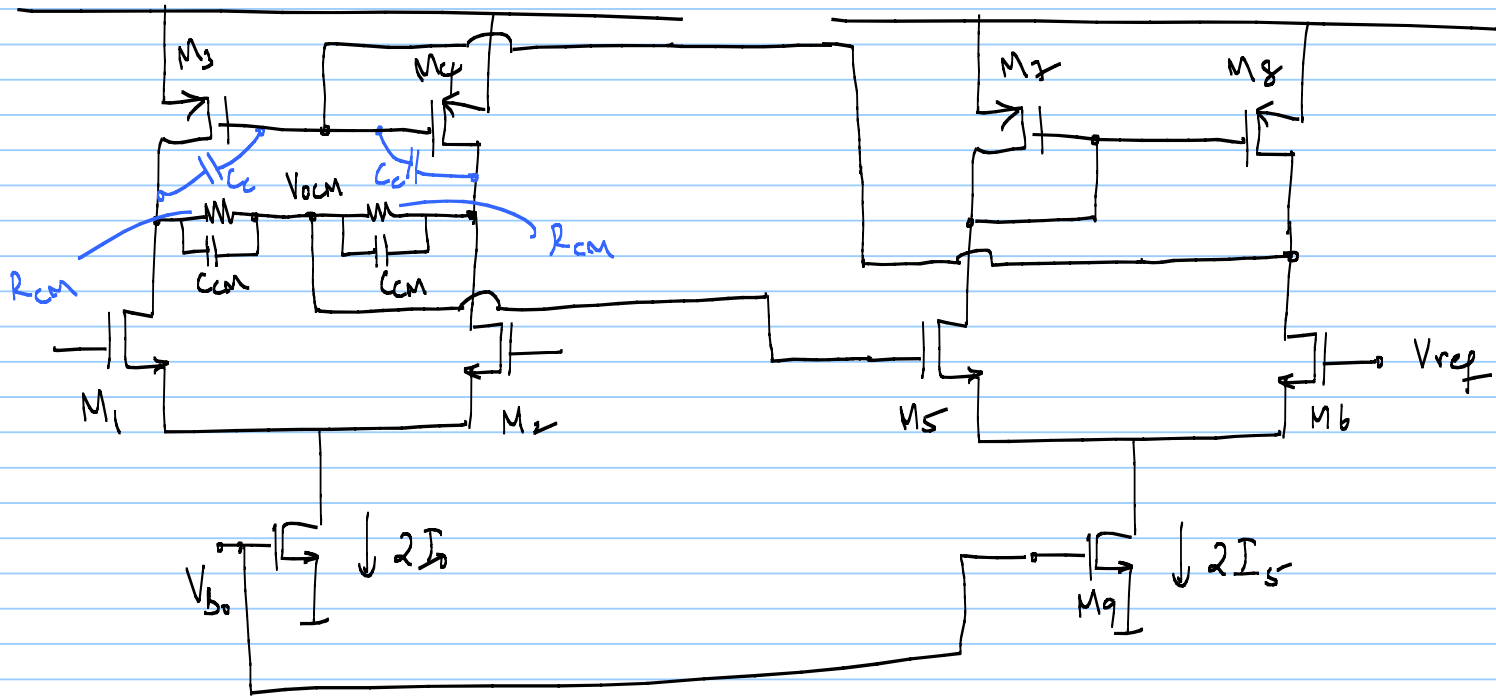


1)

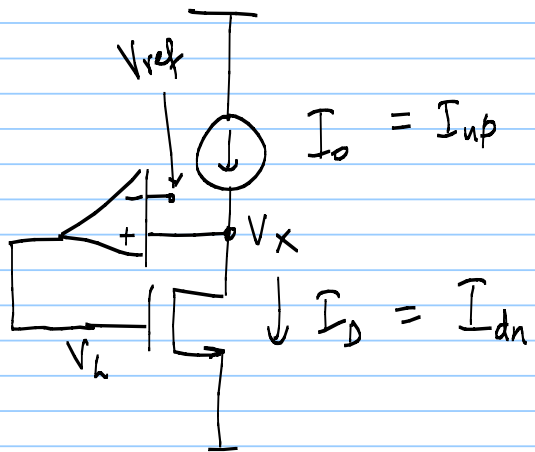


$$V_x = V_{ref}$$

2)

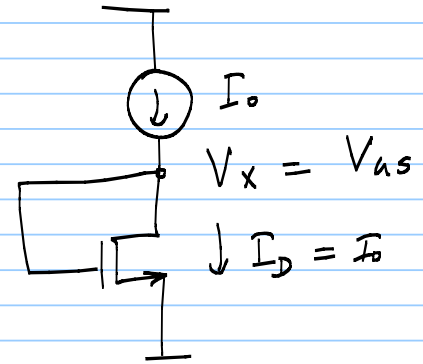

$$V_x = V_{as}$$

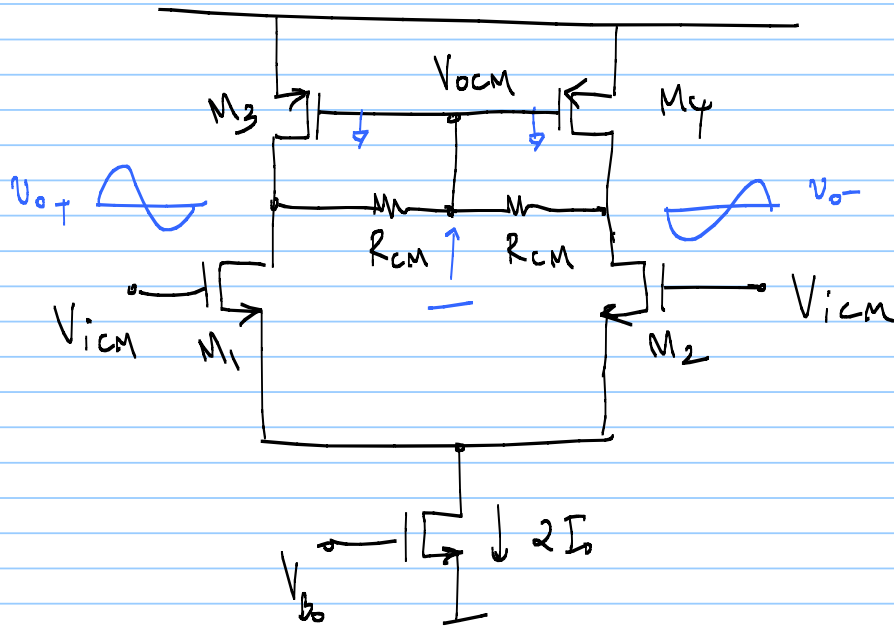


$$V_{OCM} = V_{DD} - V_{SA3} | I_b$$

$$\frac{v_{od}}{v_{id}} = g_{m1} (r_{ds2} || r_{ds4} || R_{CM})$$

$R_{CM}$  CM det.  
is linear



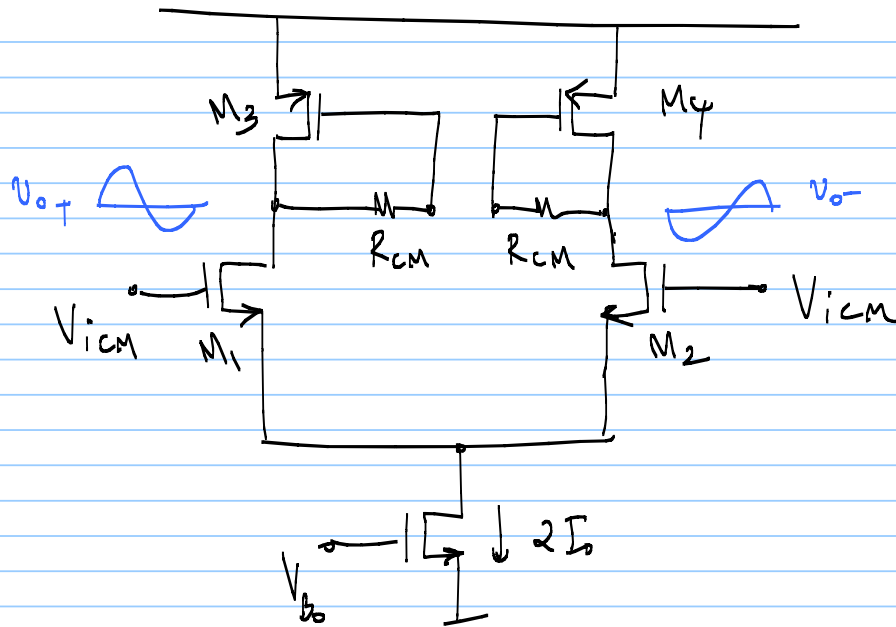

$$V_{OCM} = V_{DD} - V_{S_{M3}} \Big| I_0$$


$$\frac{v_{od}}{v_{id}} \approx \frac{g_{m1}}{g_{m3}}$$




1)  $V_{op}, V_{on}$  — 100s of mV to V of swing  $\leftarrow$   $V_{se}$  Resistive CM detector

$V_{op1}, V_{on1}$  — mV to 10s of mV of swing  $\leftarrow$  can use active

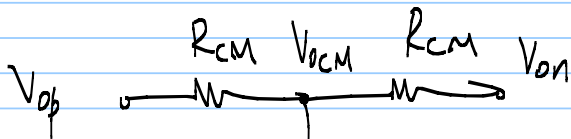2) Two-stage opamp — resistive loads  $\leftarrow$  you get gain from 1st stage  
 large gain, small error voltages  
 we active CM detector with  $R_{in} = \infty$



goes to  $V_{a7,8}$   
 $\rightarrow$  \* choose PMOS input pair + NMOS CM load  
 \* NMOS CM has same current density as  $M_7 - M_8$   
 $\sim V_{DD}/2$

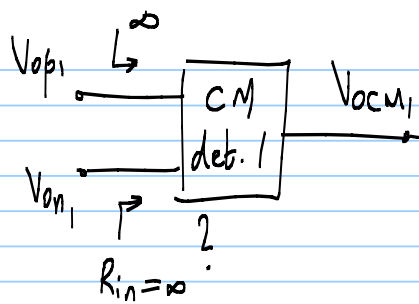



OTA1

→ NMOS input pair + PMOS CM load  
and ensure PMOS CM has same  
current density as  
M3 - M4




→ choose  $V_{ref1} = V_{DD} - V_{GS5} | I_5$

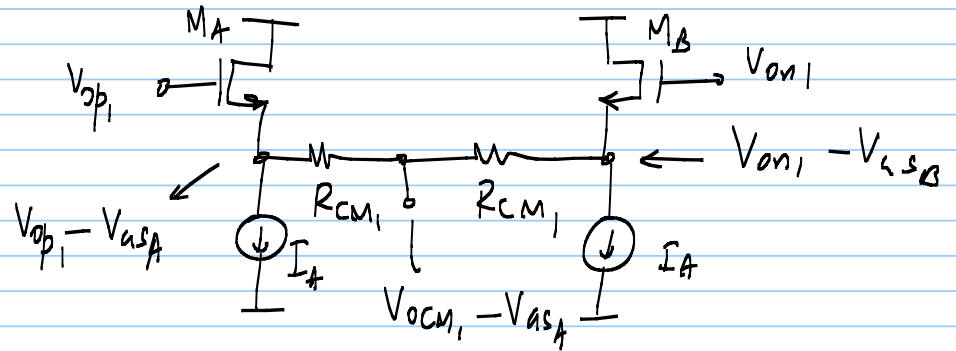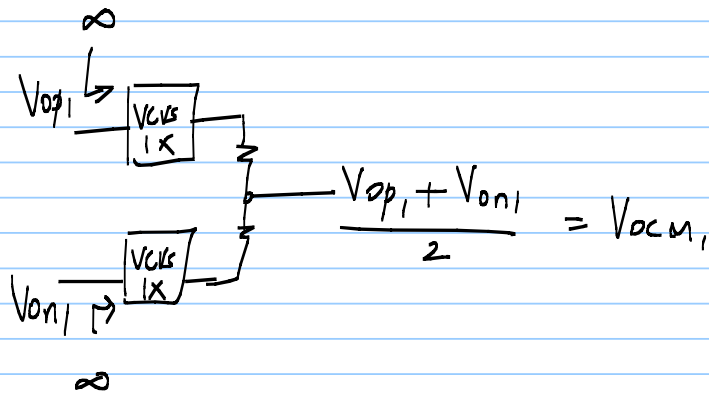so that M5 & M6 have a current  $I_5$  each




# Method 1

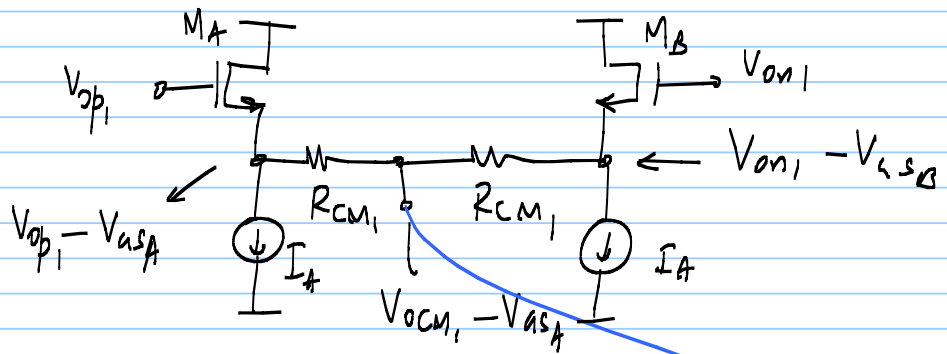


Ensure that

$$V_{asa} / I_A = V_{asc} / I_c$$

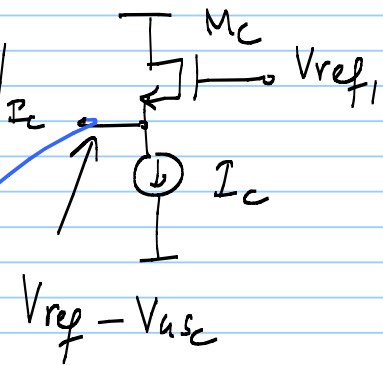

↓ to  $V_{a3,4}$

Method 2 :

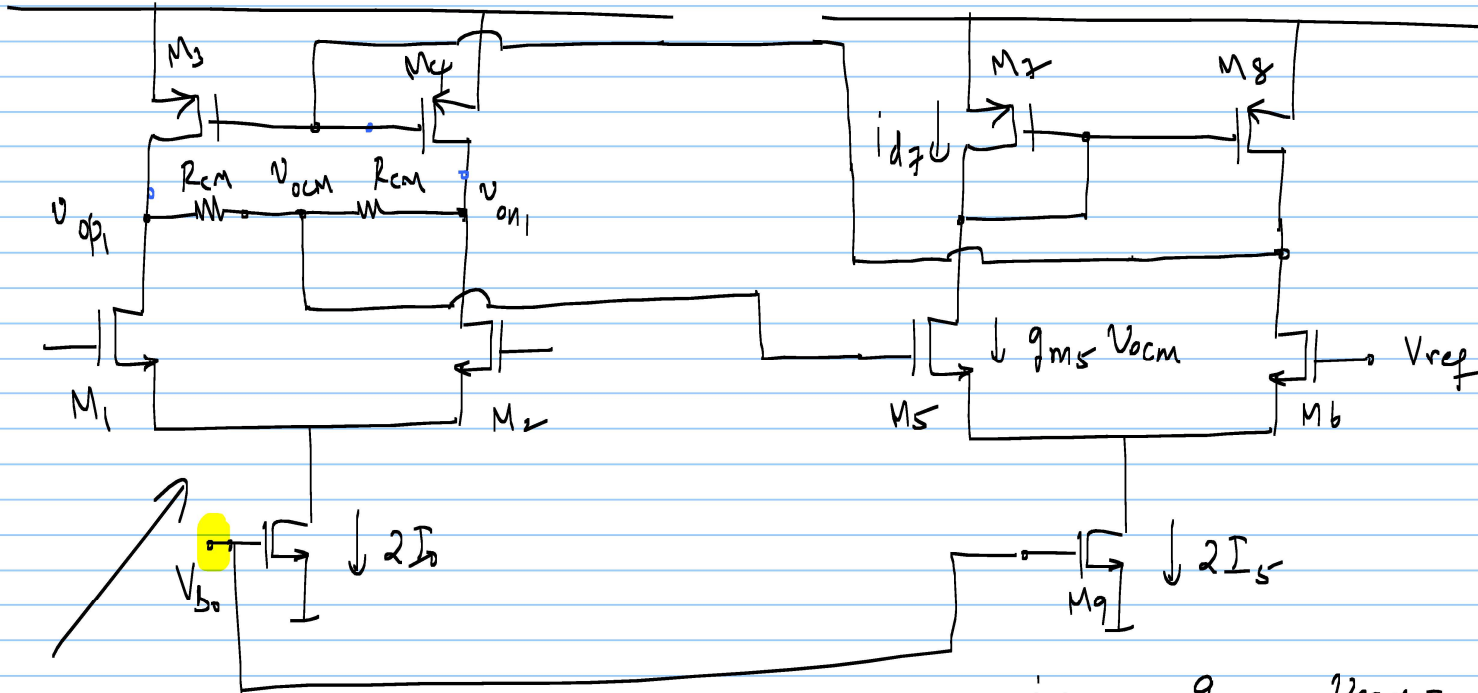


1st stage of

2-stage of amp

$$i_{d5} = g_{m5} \cdot V_{ocm} = g_{m5} \left( \frac{V_{op1} + V_{on1}}{2} \right)$$

$$= i_{d7}$$

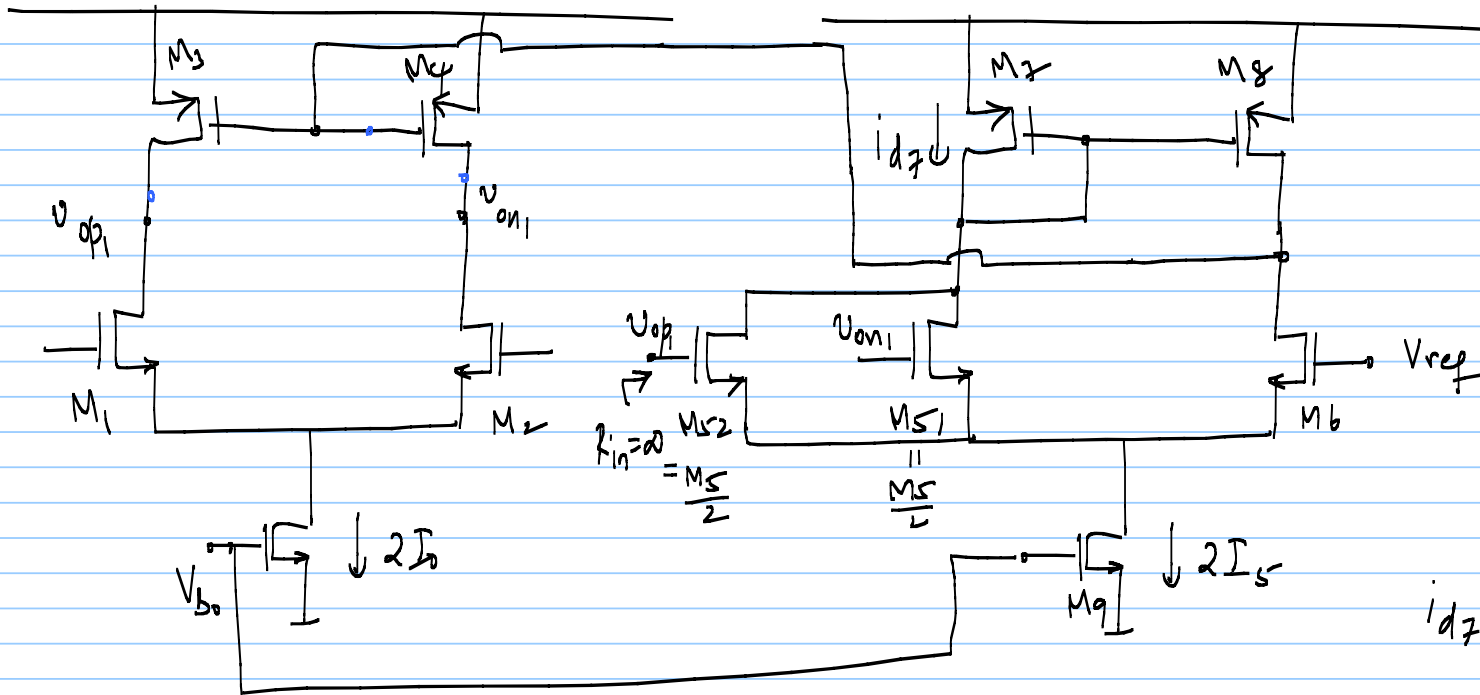

$$i_{d_{s2}} = g_{m_{s2}} \cdot v_{op1}$$

$$i_{d_{s1}} = g_{m_{s1}} \cdot v_{on1}$$

$$g_{m_{s1}} = g_{m_{s2}} = \frac{g_{m_S}}{2}$$

$$i_{d7} = i_{d_{s1}} + i_{d_{s2}}$$



$$= \frac{g_{m_S}}{2} (v_{op1} + v_{on1})$$

Same as before

4/3/20  
1st way

Lec 25

CMFB for 2-stage Fully diff. opamp

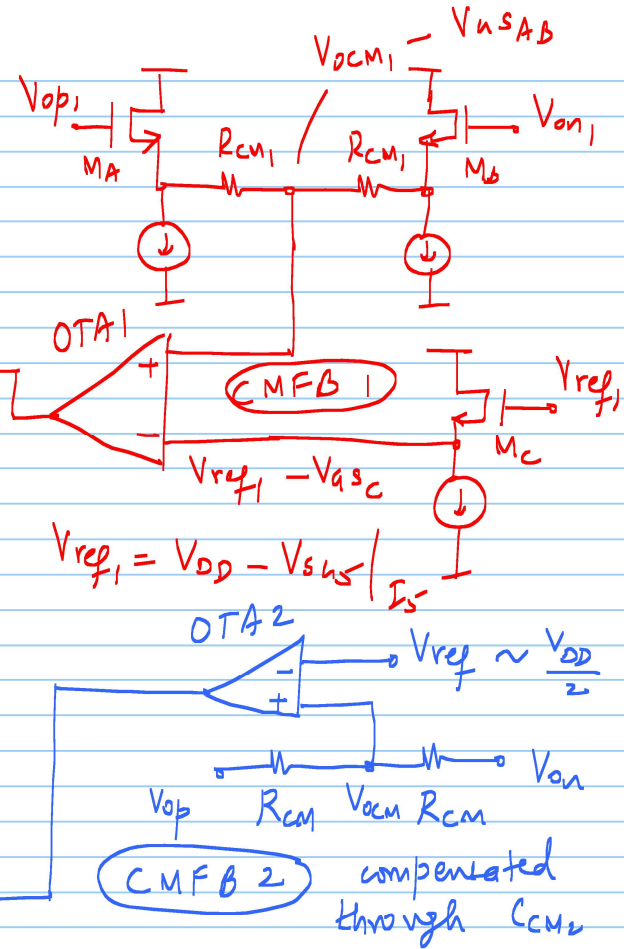
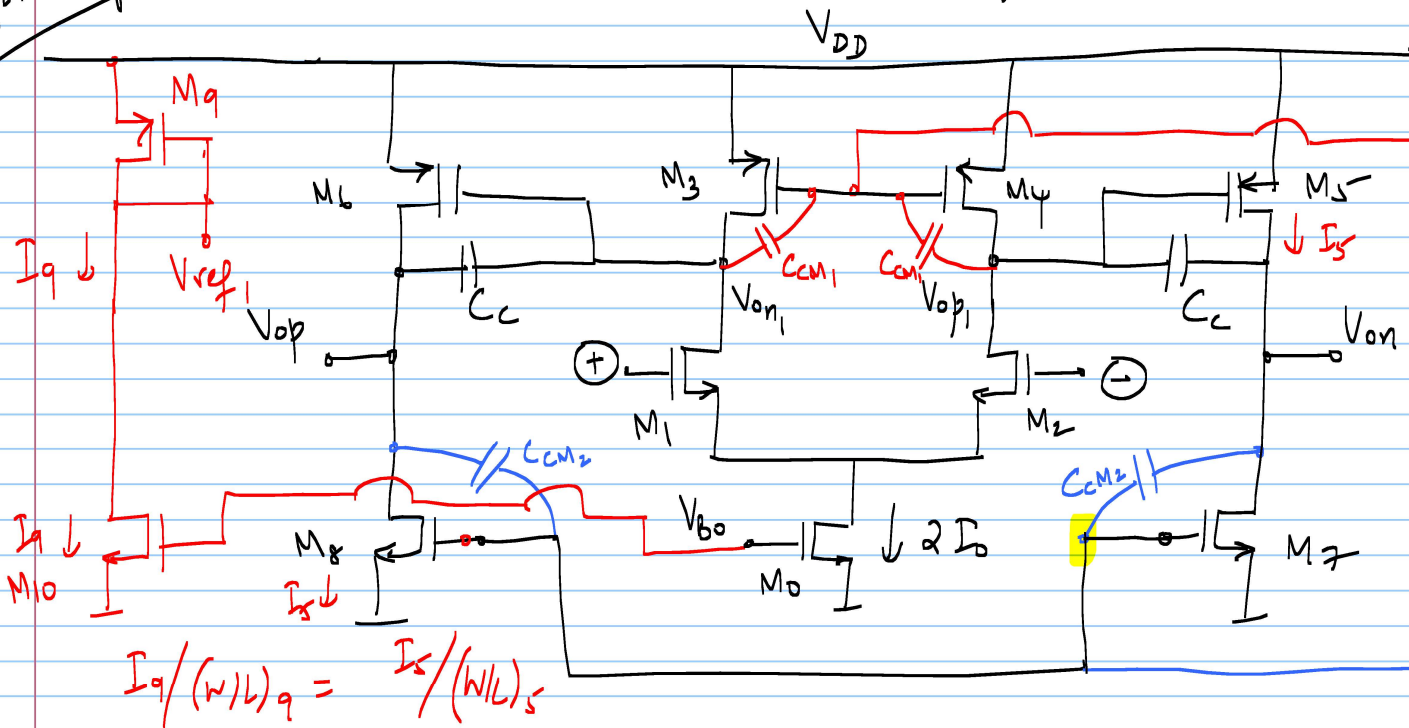








3 stage loop

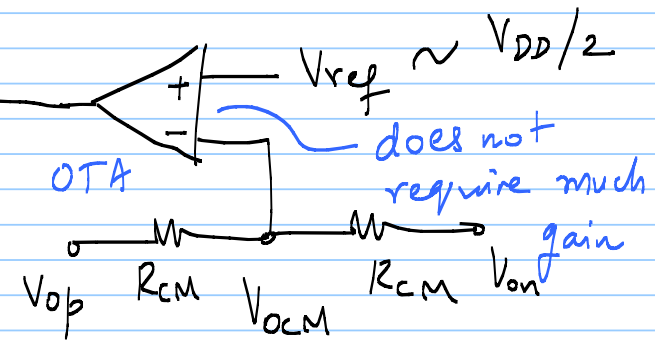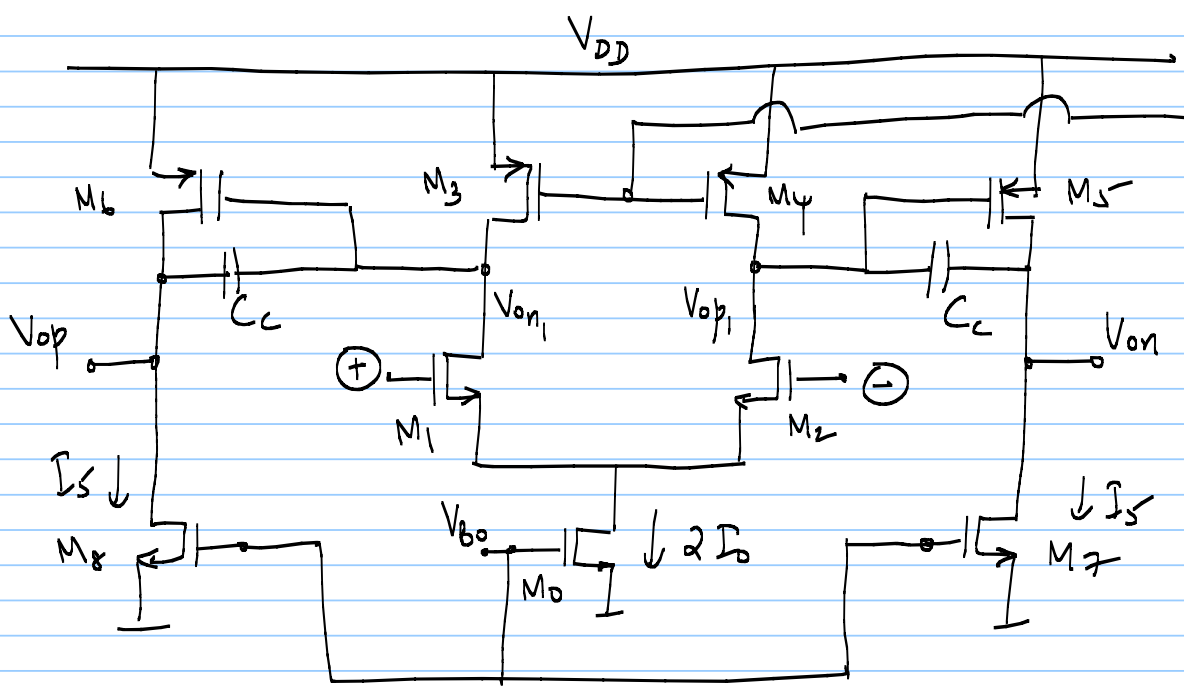$C_c$  can be chosen to compensate the CMFB loop also




\* CMFB will set  $V_{u34}$  so that  $\frac{V_{op1} + V_{on1}}{2} = \frac{V_{DD} - V_{th5}}{I_S}$


Quiz 1 discussion

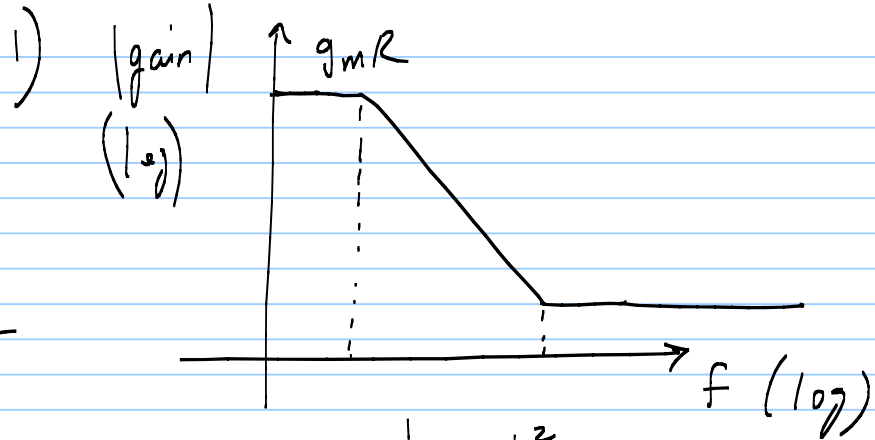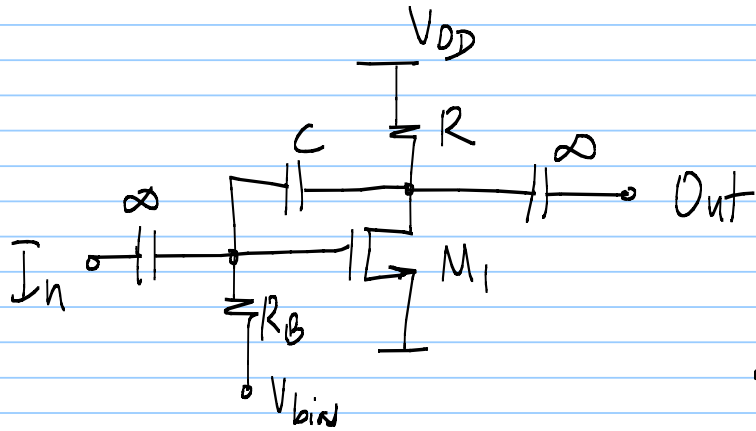

2)  $\overline{e_n^2} = \frac{|\overline{i_{sc}}|^2}{|I_{out}/v_{in}(0)|^2}$

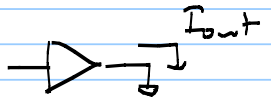


3)  $\overline{i_n^2} = \frac{|\overline{i_{sc}}|^2}{|I_{out}/I_{in}(0)|^2}$

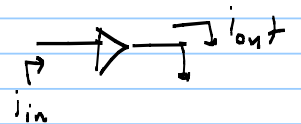

4)  $R_B$  adds no component to  $\overline{e_n}$

Quiz 2 discussion

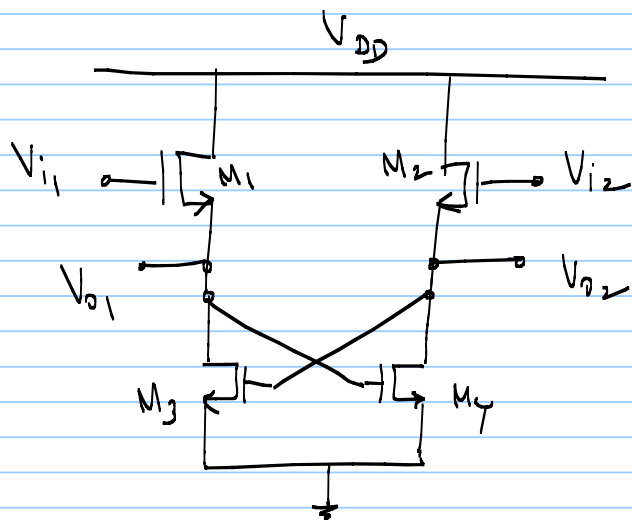


1)  $V_{icm}$  so that bias current = 1mA

$$V_{icm} = V_{as1} + V_{as4} = V_{as2} + V_{as3}$$



$$\left(\frac{W}{L}\right) = 80/2$$

$$V_{icm} = 2V_{as} \Big|_{1mA} = 4V$$

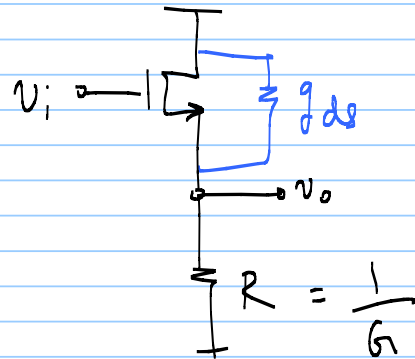2)  $\frac{v_{out1} - v_{out2}}{v_{in1} - v_{in2}} = g_m$


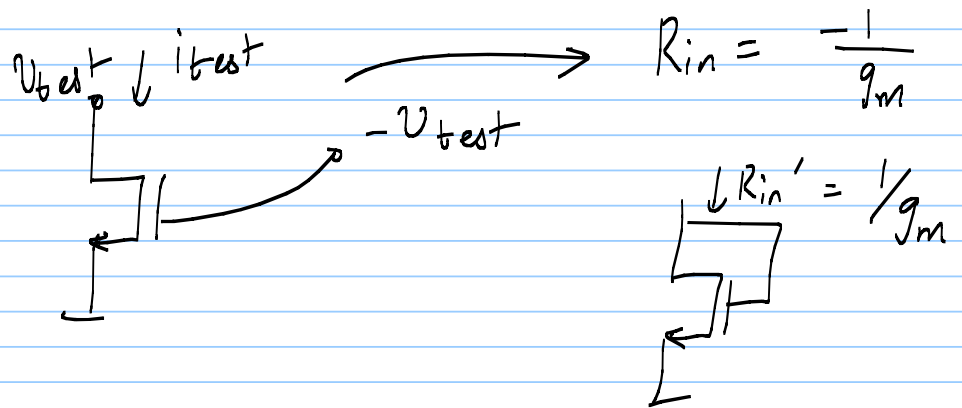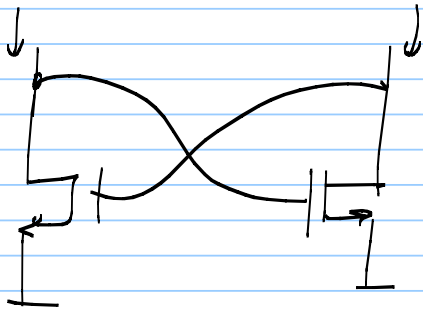
$$\frac{v_o}{v_i} = \frac{g_m R}{1 + g_m R} = \frac{g_m}{g_m + G + g_{ds}}$$



$$\frac{V_{od}}{V_{id}} = \frac{g_{m1}}{g_{m1} + g_{m1} - g_{m3} + g_{ds3}} = \frac{g_{m1}}{2g_{ds1}}$$

3)  $\overline{e_n}$  : calculate  $\frac{i_{sc}^2}{|g_m|^2} \approx \frac{V_{on}^2}{|A|^2}$

4)  $\Delta V_{T_{1-2}} \leq 100\text{mV}$  &  $\Delta V_{T_{3-4}} \leq 100\text{mV}$



worst case :

$$\left. \begin{array}{l} V_{T1} = V_{T2} + 0.1\text{V} \\ V_{T4} = V_{T3} + 0.1\text{V} \end{array} \right\} \begin{array}{l} V_{i1} = V_{ds1} + V_{ds4} \\ V_{i2} = V_{ds3} + V_{ds2} \end{array}$$

5/3/20


# Body Effect

## Lec 26

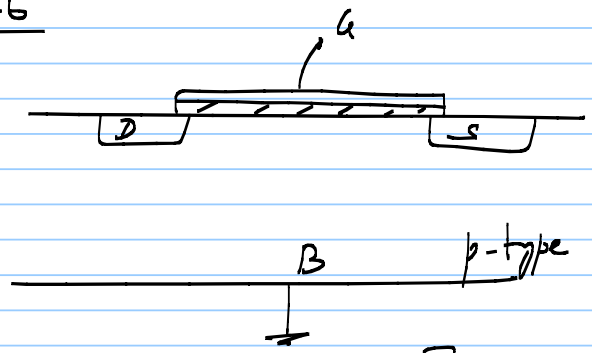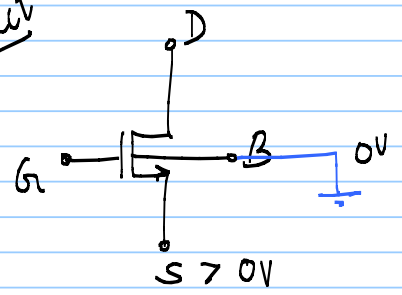


$$V_T = V_{T0} + \gamma \left[ \sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F} \right]$$

$$V_{SB} > 0 \Rightarrow V_T > V_{T0}$$

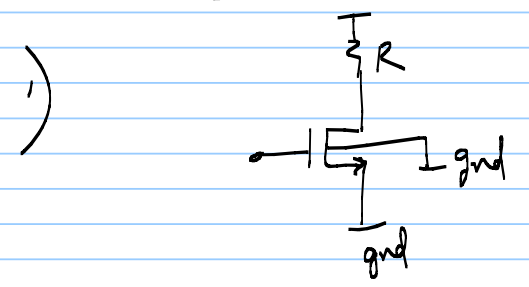


$$V_{SB} = 0, V_T = V_{T0}$$

2)

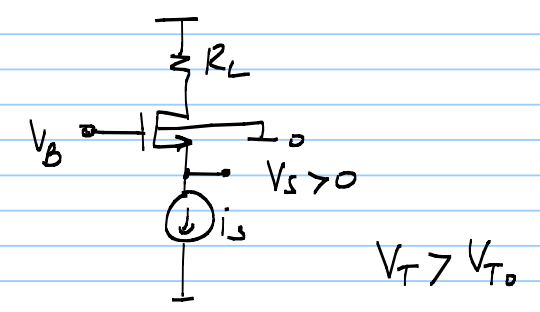


$$V_T > V_{T0}$$

3)

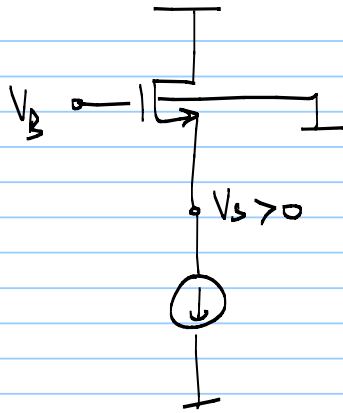


$$V_T > V_{T0}$$

4)

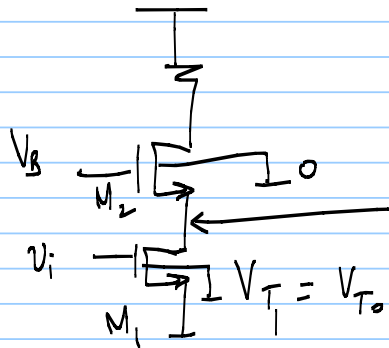

$$V_{s2} > 0 \Rightarrow V_{T2} > V_{T0}$$


5)

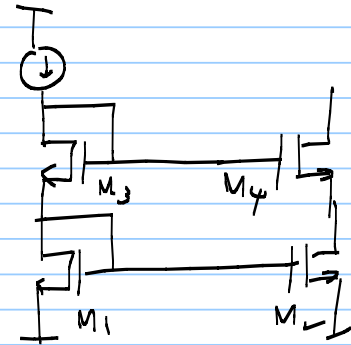


$$V_{T3,4} > V_{T1,2}$$



6)

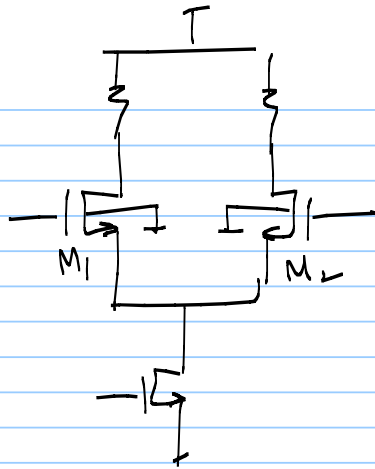

$$V_{T_{1,2}} > V_{T_0}$$


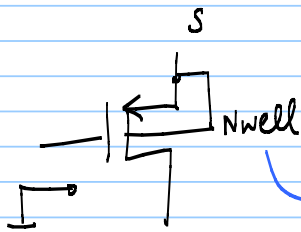


$$V_{sb} = 0 \Rightarrow V_{Tp} = V_{Tp_0}$$

has relatively larger parasitic caps



$$V_{Tp} > V_{Tp_0}$$

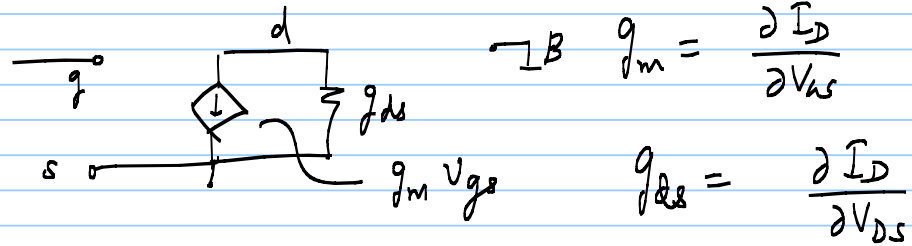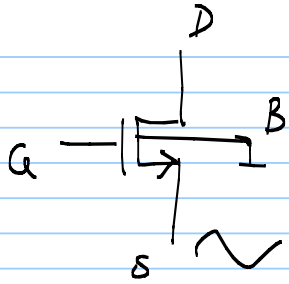

$$I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

$$\frac{\partial I_D}{\partial V_{SB}} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) \times 2 (V_{GS} - V_T) \times -1 \cdot \frac{\partial V_T}{\partial V_{SB}} = -g_m \cdot \frac{\partial V_T}{\partial V_{SB}}$$

$$\frac{\partial I_D}{\partial V_{SB}} = \frac{\partial I_D}{\partial V_T} \cdot \frac{\partial V_T}{\partial V_{SB}}$$

$\parallel$   
 $-\partial I_D / \partial V_{GS}$

$$V_T = V_{T0} + \gamma \left[ \sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F} \right]$$



$$\frac{\partial V_T}{\partial V_{SB}} = \frac{\gamma}{2} \cdot \frac{1}{\sqrt{2\phi_F + V_{SB}}}$$

$$\frac{\partial I_D}{\partial V_{SB}} = - \frac{g_m \gamma}{2} \cdot \frac{1}{\sqrt{2\phi_F + V_{SB}}} = - \alpha g_m$$

normally  $\alpha \ll 1$


DC value
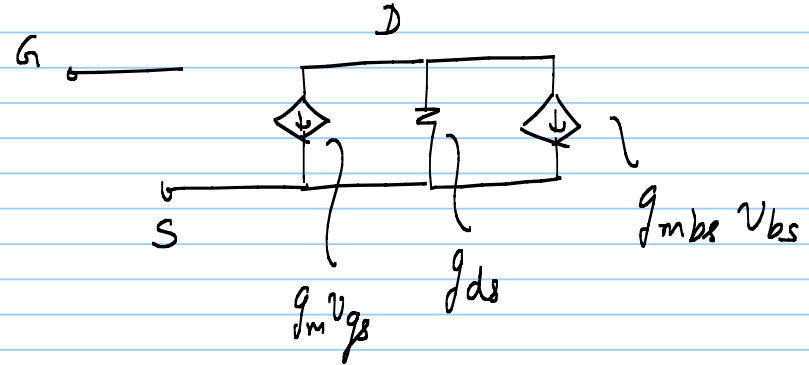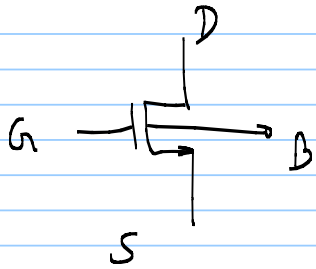
$$g_{mbs} = \frac{\partial I_D}{\partial V_{BS}} = \alpha g_m$$



$$g_m \gg g_{mbs} \gg g_{ds}$$

### Transit frequency

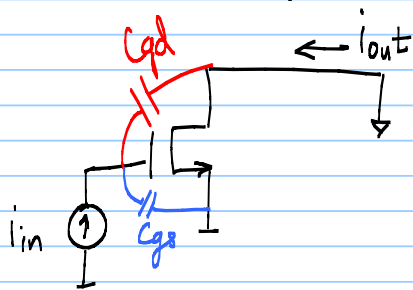

$$i_{out} = g_m \cdot v_{gs} = g_m \cdot i_{in} \cdot \frac{1}{j\omega C_{gs}}$$

$$\left| \frac{i_{out}}{i_{in}} \right| = \frac{g_m}{\omega C_{gs}} \rightarrow = 1 \quad @ \quad \begin{matrix} \omega = \omega_T \\ f = f_T \end{matrix}$$

$$\omega_T = \frac{g_m}{C_{gs}} ; \quad f_T = \frac{g_m}{2\pi C_{gs}}$$

Note: with  $C_{gd}$ ,

$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}}$$

$$\omega_T = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right) (V_{ds} - V_T)}{\frac{2}{3} W L C_{ox}} = \frac{3}{2} \frac{\mu_n (V_{ds} - V_T)}{L^2}$$

### High speed

- 1) NMOS cks  $\leftarrow \mu_n > \mu_p$
- 2) Small  $L$  { but, leads to lower  $g_m V_{ds}$  }
- 3) larger  $(V_{ds} - V_T)$  { but, leads to lower swings }

Short-channel effect - Velocity saturation

$$v_{el.} = \mu_n E$$


$$I_D = \frac{W C_{ox}}{2} (V_{as} - V_T) v_{sat} \quad \text{in saturation region}$$

velocity


$$g_m = \frac{\partial I_D}{\partial V_{as}} = \frac{W C_{ox}}{2} \cdot v_{sat}$$

$$\omega_T = \frac{g_m}{C_{gs}} = \frac{\frac{W C_{ox}}{2} v_{sat}}{\frac{2}{3} W L C_{ox}} = \frac{3}{4} \frac{v_{sat}}{L}$$

## Noise in an RC LPF

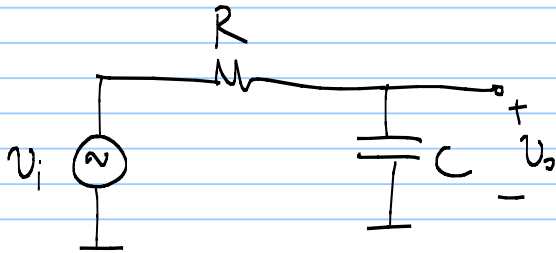
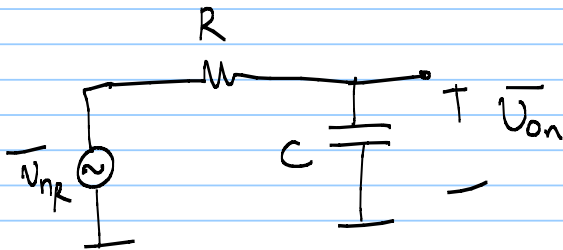
$$\frac{v_o}{v_i} = \frac{1}{1 + j\omega CR}$$



$$\overline{v_{on}^2} = \overline{v_{nr}^2} \cdot \left| \frac{1}{1 + j2\pi f CR} \right|^2$$

$$= \frac{4kTR}{1 + 4\pi^2 f^2 C^2 R^2}$$

$$\underline{\text{Total integrated noise}} = \int_0^{\infty} \frac{4kTR}{1 + 4\pi^2 f^2 C^2 R^2} \cdot df$$

$$\text{Set } x = 2\pi f CR$$

$$= \int_0^{\infty} \frac{4kTR}{1+x^2} \cdot \frac{dx}{2\pi CR}$$

$\int_0^{\infty} \frac{1}{1+x^2} dx = \frac{\pi}{2}$

$$\text{Total integrated noise} = \frac{4kTR}{2\pi CR} \cdot \frac{\pi}{2} = \frac{kT}{C}$$

← Build LPF with small R, large C keeping RC constant



$$g_m = \frac{2 I_D}{V_{ov}} \Rightarrow \frac{g_m}{I_D} = \frac{2}{V_{ov}}$$

Assumes pure  
square law operation

From 17/3/20 :

Tue 3:30 - 4:45 pm

Thu 3:30 - 4:45 pm

Fri 3:30 - 4:45 pm


Next week :

Wed (11/3) 3:30 - 4:45 pm

Thu (12/3) 3:30 - 4:45 pm

11/3/2020

Lec 27

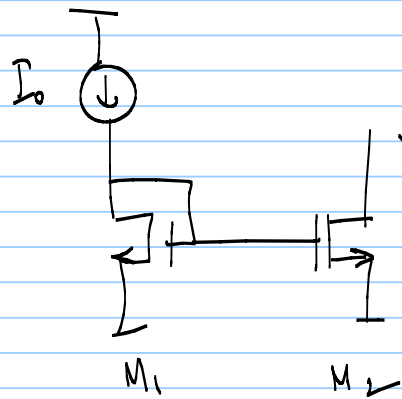


$$\Delta I = -g_{m2} \cdot \Delta V_T$$

$\Delta V_T = \text{small signal}$

$$V_{T2} = V_{T1} + \Delta V_T$$

$$I_D = \frac{1}{2} \mu C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 \leftarrow$$

$$\times (1 + \lambda V_{DS})$$

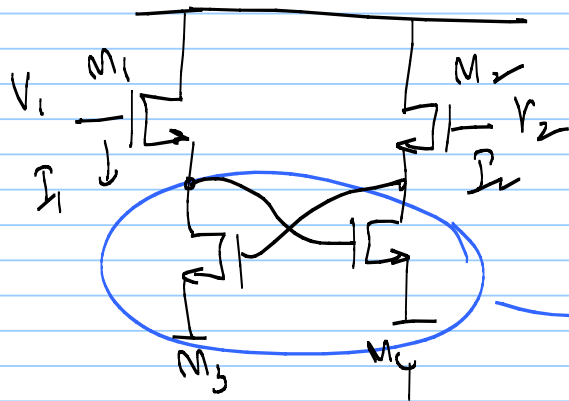

$$I_1 = I_2 = 0 \quad V_{T1} + V_{os1}$$


$$V_1 = V_{gs1} + V_{as1} \quad V_{T2} + V_{os2}$$

$$V_2 = V_{gs2} + V_{as2}$$

→ +ve feedback

Use CLM in DC eqn or small-signal analysis


## Switched capacitor Circuits

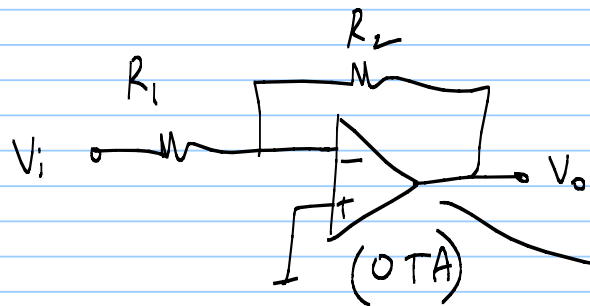



$$\frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

we wanted high gain,  $\infty R_{in}$  & 0  $R_{out}$

|||

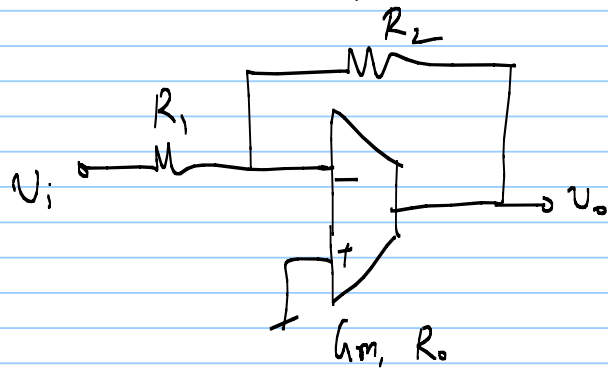

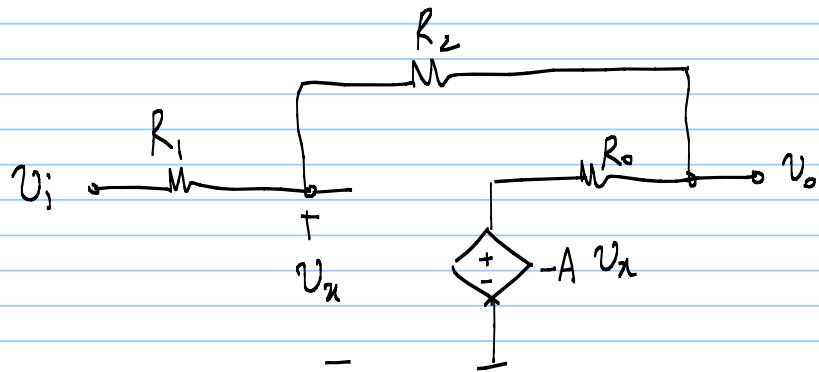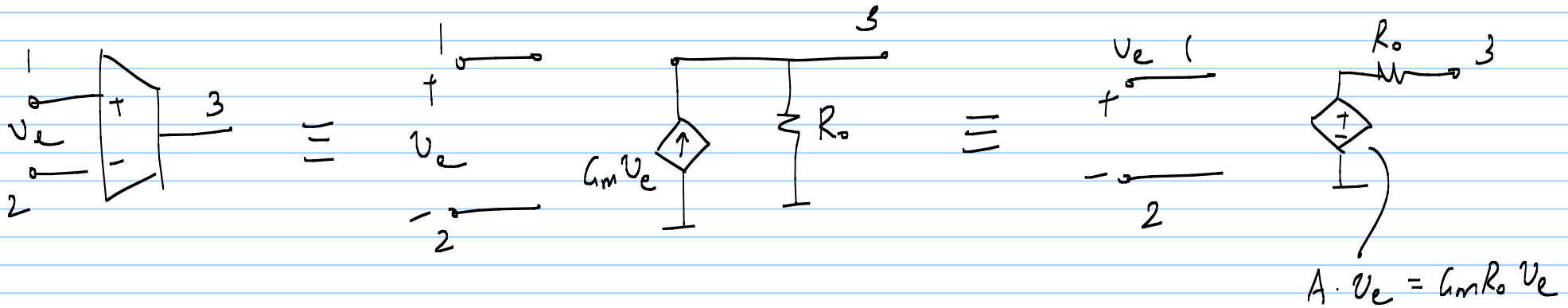we got high gain,  $\infty R_{in}$ , but large  $R_{out}$



$$\frac{V_o}{V_i} = \frac{-R_2}{R_1} \circ \text{—————}$$

$$v_x = v_i + \frac{v_o - v_i}{R_1 + R_2} \cdot R_1$$

$$-Av_x - R_o \left[ \frac{v_o - v_i}{R_1 + R_2} \right] = v_o$$

$$-A \left[ v_i + \frac{v_o - v_i}{R_1 + R_2} \cdot R_1 \right] - R_o \cdot \left[ \frac{v_o - v_i}{R_1 + R_2} \right] = v_o$$

$$\frac{v_o}{v_i} = \frac{-R_2}{R_1} \cdot \frac{1 - \frac{R_o}{AR_2}}{1 + \frac{R_1 + R_2 + R_o}{AR_1}} = \frac{-R_2}{R_1} \cdot \frac{A - \frac{R_o}{R_2}}{1 + A + \frac{R_2}{R_1} + \frac{R_o}{R_1}}$$

Opamp with gain  $A$  and  $R_o = 0$ : 
$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} \cdot \frac{A}{1+A+\frac{R_2}{R_1}}$$


1)  $R_1$  &  $R_2$  load OTA : gain error

choose large  $R_1$  &  $R_2$

2)  $R_{in}$  of closed loop amplifier =  $R_1$  : loads previous stage

3)  $R_1$  &  $R_2$  add thermal noise

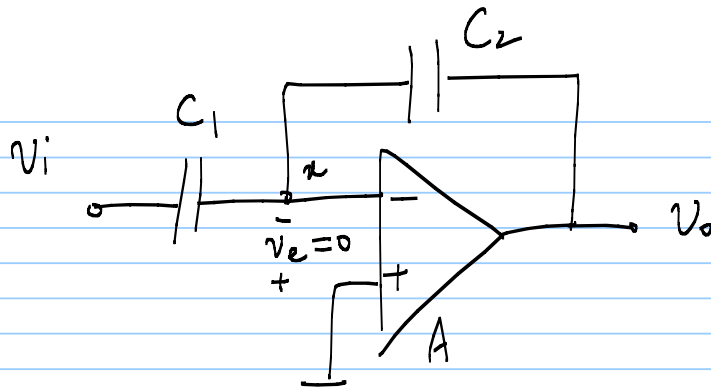4) large area for  $R_1$  &  $R_2$ , large parasitics



ideal  $v\beta$  amp


$$\frac{V_o}{V_i} = -\frac{C_1}{C_2}$$

OTA: no steady state current drawn from OTA ✓

Issues:

$V_{em} + 0$   
(DC) (ac)

1) Gain is a function of  $f_{ev}$ ?

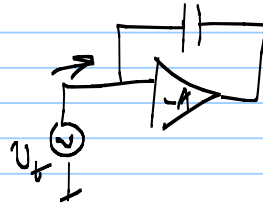


$R_{in} = \infty$  ✓

noise = 0 ✓

2) DC gain = 0 ; Use only for ac signals

3) No DC feedback !  $V_n$  is undefined




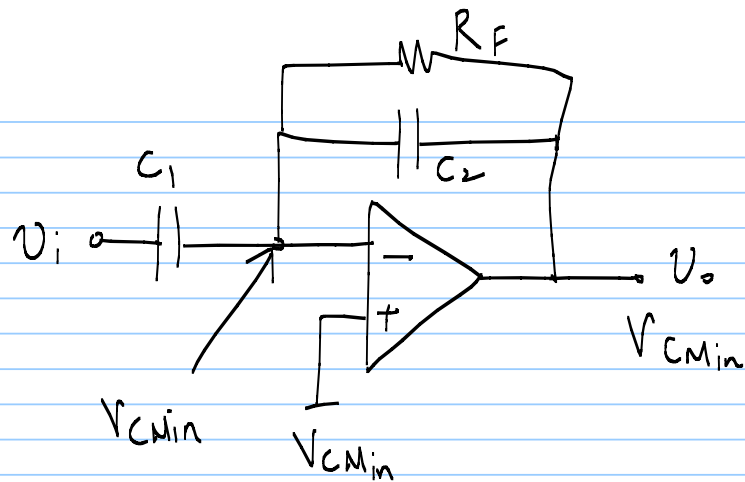


$$\frac{V_o}{V_i}(\omega) \approx - \frac{R_F \cdot \frac{1}{sC_2}}{R_F + \frac{1}{sC_2}} \cdot \frac{1}{sC_1} = - \frac{sC_1 R_F}{1 + sC_2 R_F}$$


$$= - \frac{sC_1}{\frac{1}{R_F} + sC_2}$$

1) No longer a wide band amplifier

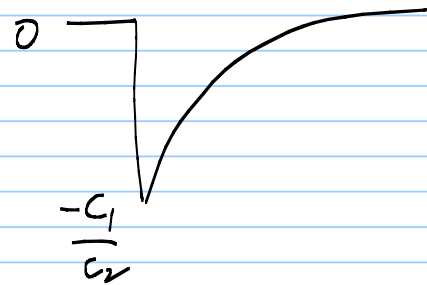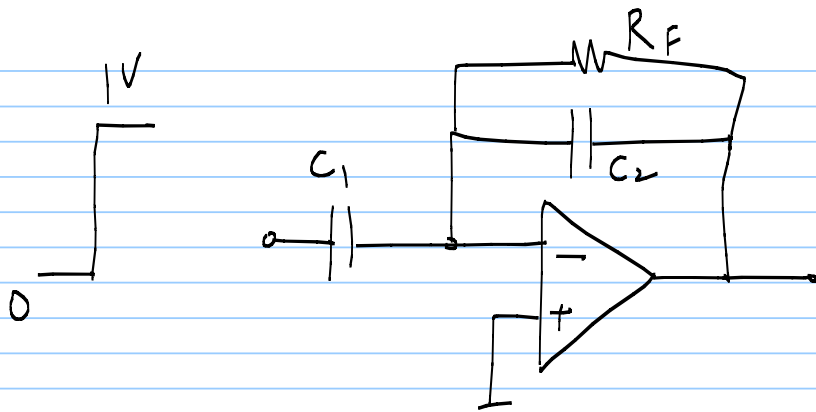
2) Choose large  $R_F$ :  $\frac{V_o}{V_i} \approx - \frac{C_1}{C_2}$



Avoid large  $R_F$ !

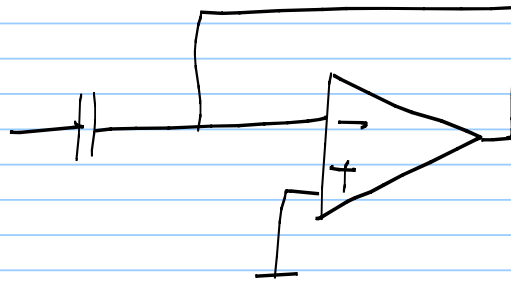


- sets DC f.b.
- but no ac gain

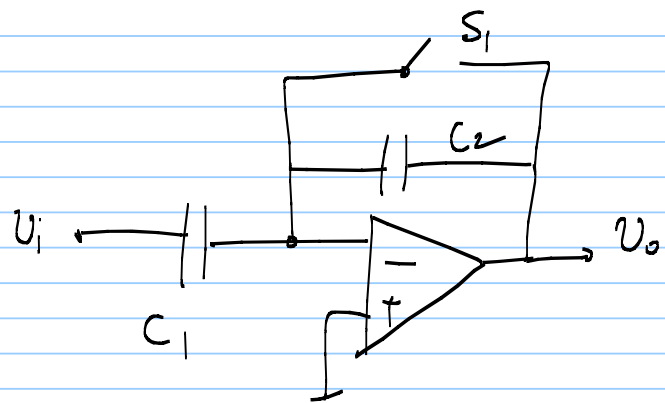

→


phase 1 : close  $S_1$

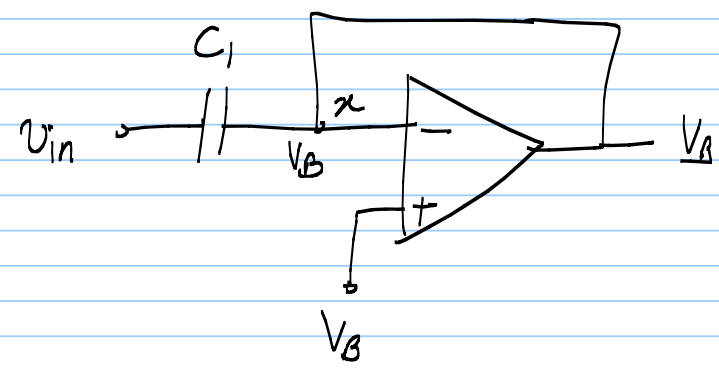

$$U_{C_1} = U_{in}$$

↓


phase 2 : open  $S_1$

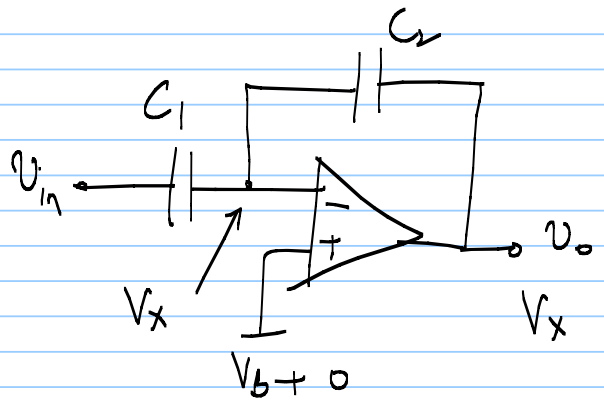


$V_x$  stays the same (charge is held)

12/3/20

Lec 28

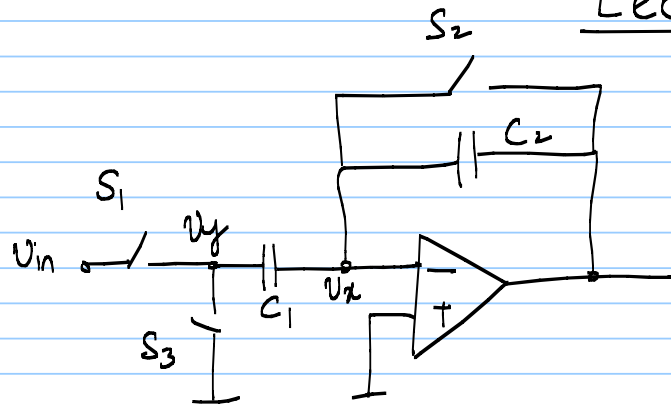

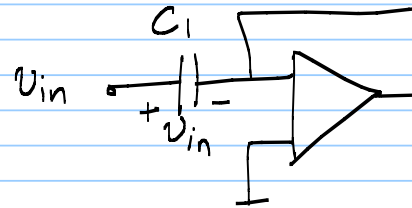Phase 1 : close  $S_1$  &  $S_2$ , open  $S_3$




$$v_y = v_{in}$$

$$v_x = 0$$

$$v_{c_1} = v_{y-x} = v_{in}$$

"sampling mode"

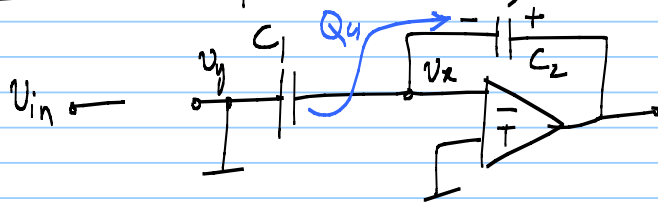Phase 2 : open  $S_1$  &  $S_2$ , close  $S_3$  @  $t = t_0$



$$v_y = 0, \quad v_x = 0, \quad v_{xy} = 0$$

$$\text{at } t = t_0 - \delta t, \quad Q_{c_1}(t_0 - \delta t) = c_1 v_{in}(t_0)$$

$$\text{at } t = t_0 + \delta t, \quad Q_{c_1}(t_0 + \delta t) = 0$$



$$Q_{C_2}(t + \delta t) = Q_{C_1}(t - \delta t) = C_1 V_{in}(t_0)$$

$$V_{C_2} = \frac{C_1}{C_2} V_{in}(t_0)$$

$$V_{out} = \frac{C_1}{C_2} V_{in}(t_0) \quad : \text{ amplifier with gain } \frac{C_1}{C_2}$$

Build discrete time amplifiers using switches, OTAs & capacitors

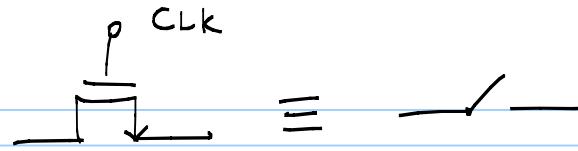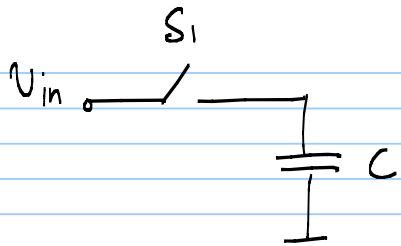
↳ sampling phase ✓  
↳ amplification phase



CLK =  $V_{DD}$   $\Rightarrow$  switch is ON


CLK = 0  $\Rightarrow$  switch is OFF

Case 1)

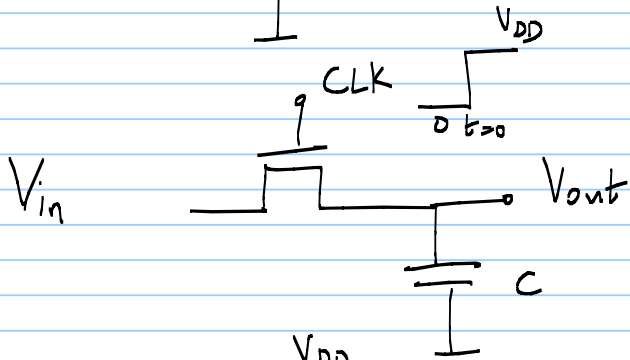

$$V_C(t=0^+) = V_{DD}$$

$$V_{in} = 0$$

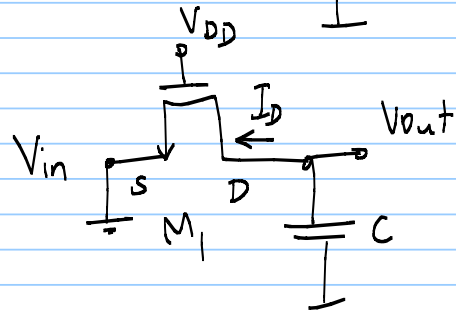

@  $t = 0^+$ ,  $V_{gs} = V_{DD}$  } MOSFET is  
 $V_{ds} = V_{DD}$  } in saturation

$$I_D = \frac{\beta}{2} (V_{DD} - V_T)^2 = -C \frac{dV_{out}}{dt}$$

$$\beta = \mu_n C_{ox} \left( \frac{W}{L} \right)$$

$$V_{out}(t) = V_{DD} - \frac{\beta}{2C} (V_{DD} - V_T)^2 \cdot t$$

@  $t = t_1$ ,  $M_1$  goes into triode :  $V_{out} = V_{DD} - V_T$

$$V_{DD} - V_T = V_{DD} - \frac{\beta}{2C} (V_{DD} - V_T)^2 \cdot t_1$$

$t > t_1$  :

$$I_D = \beta \left( (V_{DD} - V_T) \cdot V_{out} - \frac{V_{out}^2}{2} \right) = -C \frac{dV_{out}}{dt}$$

$V_{out}(t) = ?$

$$\frac{dV_{out}}{(V_{DD} - V_T) V_{out} - \frac{V_{out}^2}{2}} = \frac{-\beta}{C} dt$$

$$\frac{dV_{out}}{2(V_{DD}-V_T)V_{out} - V_{out}^2} = \frac{-\beta}{2C} dt$$

$$\frac{dV_{out}}{[2(V_{DD}-V_T) - V_{out}]V_{out}} = \frac{-\beta}{2C} dt$$

$$\left[ \frac{1}{V_{out}} + \frac{1}{2(V_{DD}-V_T) - V_{out}} \right] \cdot \frac{dV_{out}}{2(V_{DD}-V_T)} = \frac{-\beta}{2C} dt$$

$$\ln(V_{out}) - \ln[2(V_{DD}-V_T) - V_{out}] = -\frac{\beta(V_{DD}-V_T)}{C} \cdot t$$

$$\ln \left[ \frac{V_{out}}{2(V_{DD}-V_T) - V_{out}} \right] = -\frac{\beta}{C} (V_{DD}-V_T) \cdot t$$



$$\frac{V_{out}}{2(V_{DD}-V_T) - V_{out}} = \exp\left(\frac{-\beta}{C}(V_{DD}-V_T) \cdot t\right)$$

$$V_{out} = 2(V_{DD}-V_T) \cdot \exp\left(\frac{-\beta}{C}(V_{DD}-V_T) \cdot t\right)$$

$$- V_{out} \cdot \exp\left(\frac{-\beta}{C}(V_{DD}-V_T) \cdot t\right)$$

$t > t_1$

$$V_{out}(t) = \frac{2(V_{DD}-V_T) \cdot \exp\left(\frac{-\beta}{C}(V_{DD}-V_T) \cdot t\right)}{1 + \exp\left(\frac{-\beta}{C}(V_{DD}-V_T) \cdot t\right)}$$


replace with  $t-t_1$



$$\frac{1}{V_{DD} - V_{out} - V_T} - \frac{1}{V_{DD} - V_T} = \frac{\beta \cdot t}{2C}$$

$$V_{out} = V_{DD} - V_T - \frac{1}{\frac{\beta t}{2C} + \frac{1}{V_{DD} - V_T}}$$

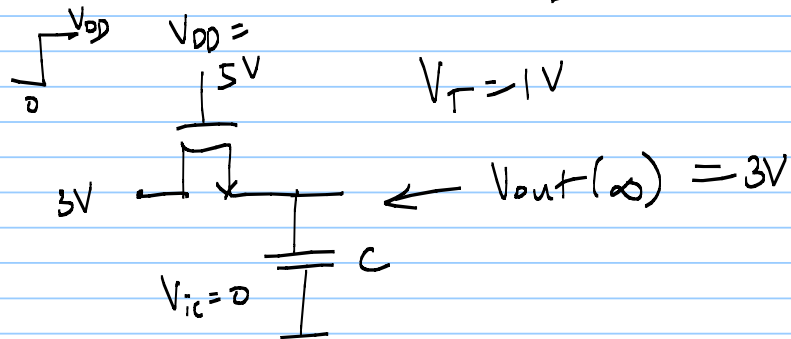(a)  $t = \infty$  :  $V_{out} = V_{DD} - V_T$




@  $t = 0^+$ , M<sub>1</sub> is in triode



$R_{on}$  in Triode

$$I_D = \beta \left( (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right)$$

$$R_{on} = r_{ds} = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{1}{\beta (V_{GS} - V_T - V_{DS})}$$

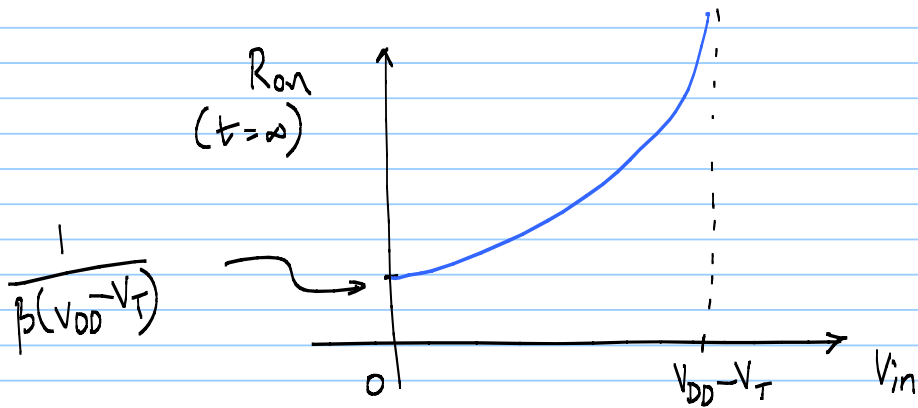


Case 1:  $V_{in} = 0$

Case 2:  $V_{in} = V_{DD}$

Case 3:  $V_{in} = 0 < V_{in} < V_{DD}$

Case 4:  $V_{in} = V_{DD} - V_T$


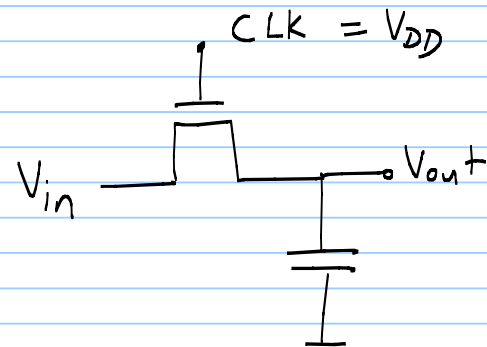


$$V_{out}(\infty) = V_{DD} - V_T$$


$$V_{DS}(\infty) = 0$$

$$V_{GS}(\infty) = V_T$$

Why  $R_{on}(t \rightarrow \infty)$  ←

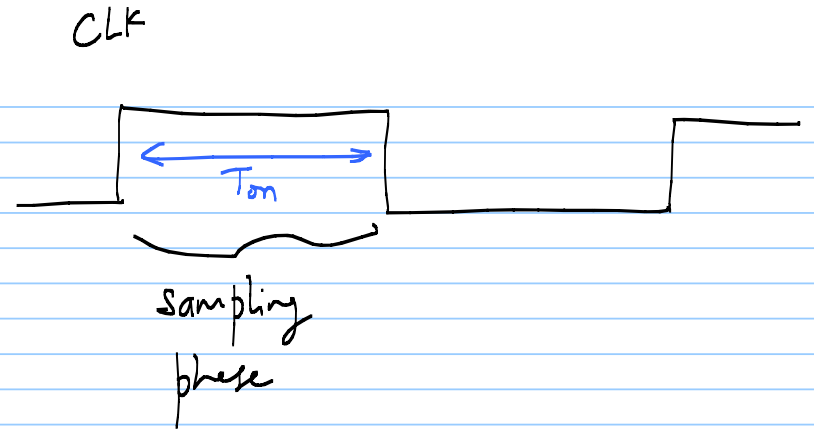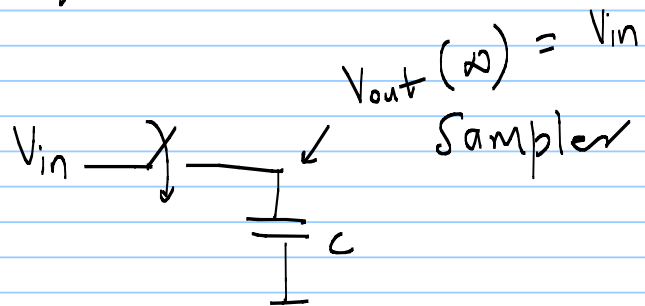

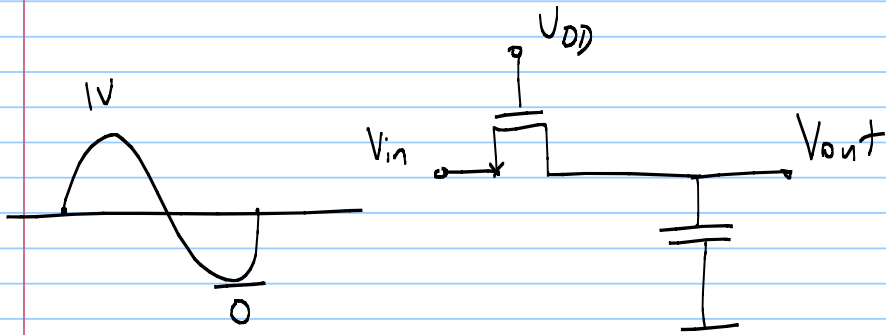within  $T_{on}$ , we want  $V_{out} = V_{in} - \delta V$   
precision specification




# Lec 29

Note Title

24-03-2020

24/3/20


## Switched Capacitor Circuits

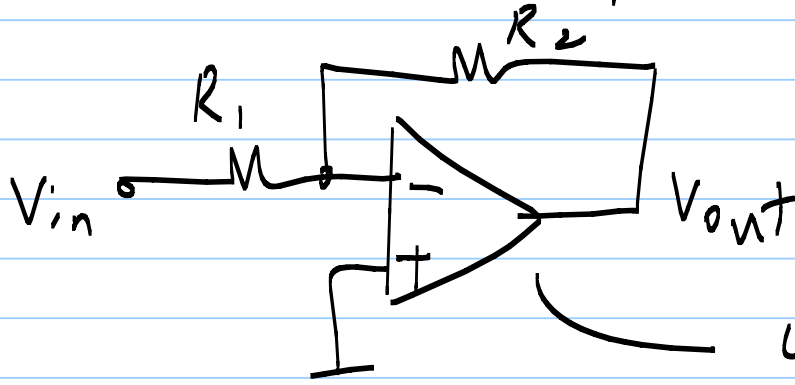

OTA,  $R_{out}$  high

$R_{in} \neq \infty$  (loading on previous stage)

$R_1, R_2$  - thermal noise

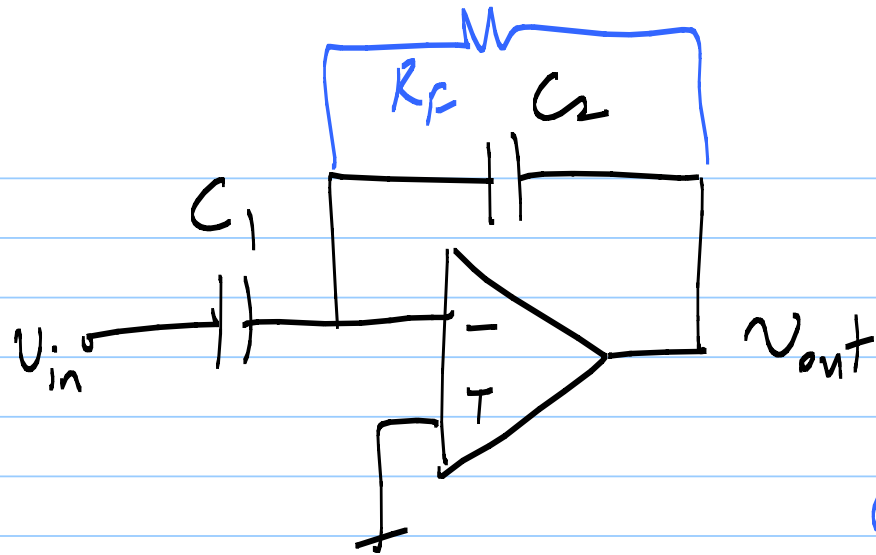

choose large  $R_F \gg \frac{1}{sC_2}$



$$\frac{U_o}{U_i} = -\frac{C_1}{C_2}$$

\* No DC feedback


Discrete time amplification

sampling phase

amplification phase

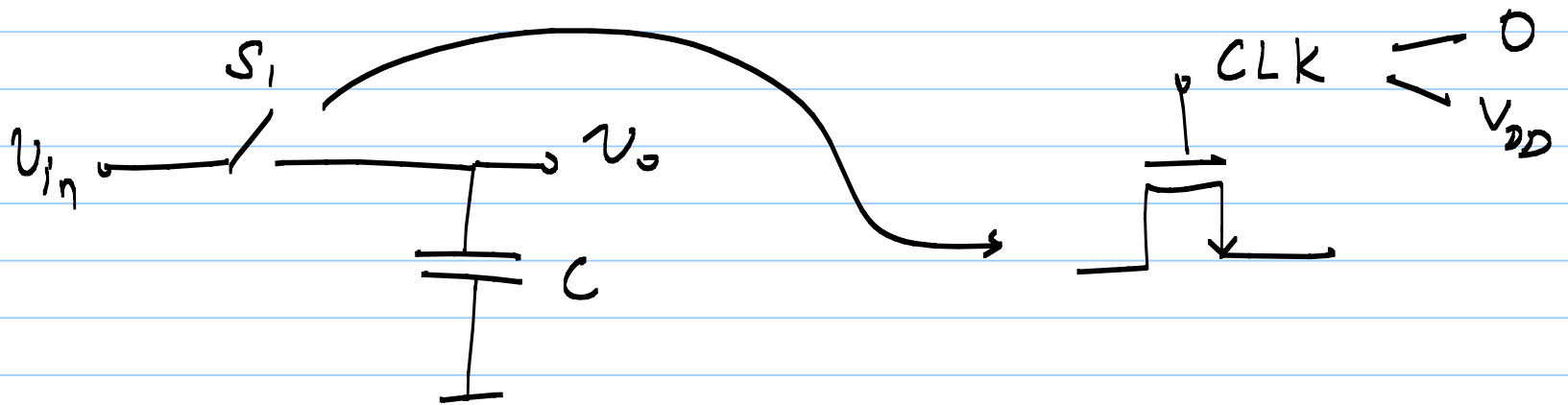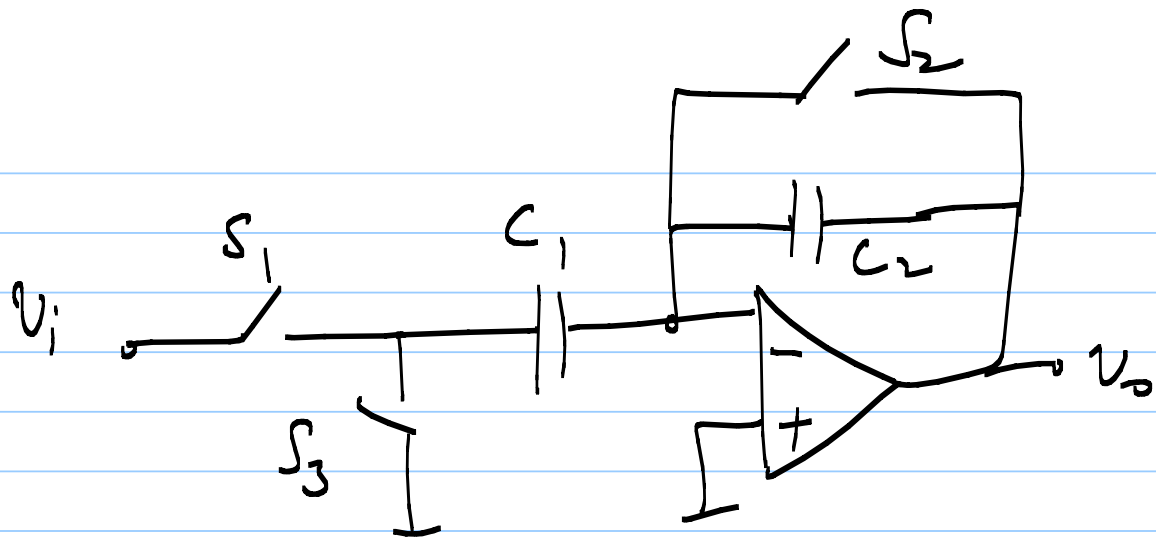




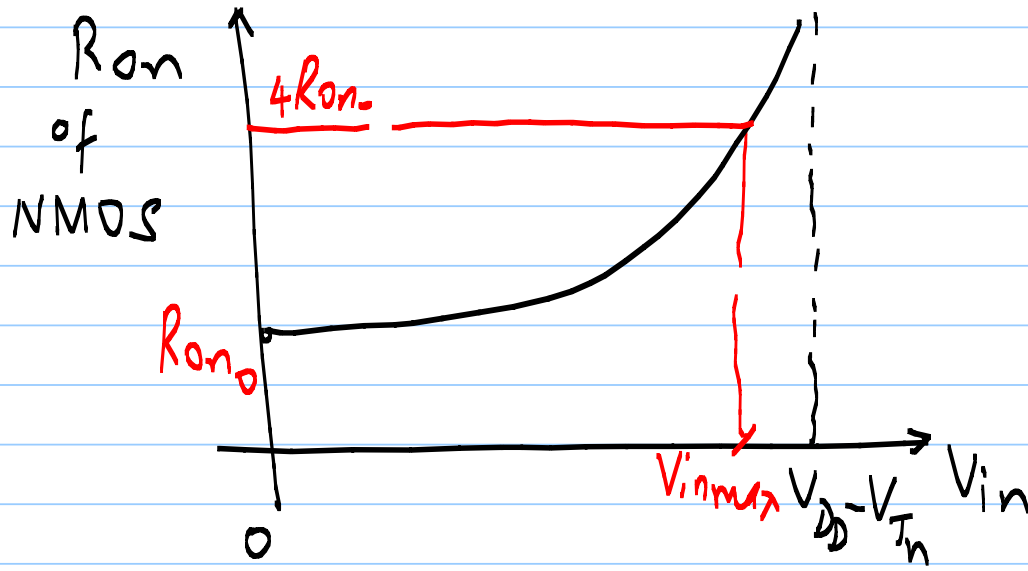

$$\beta_n = \mu_n C_{ox} \left(\frac{W}{L}\right)_n$$
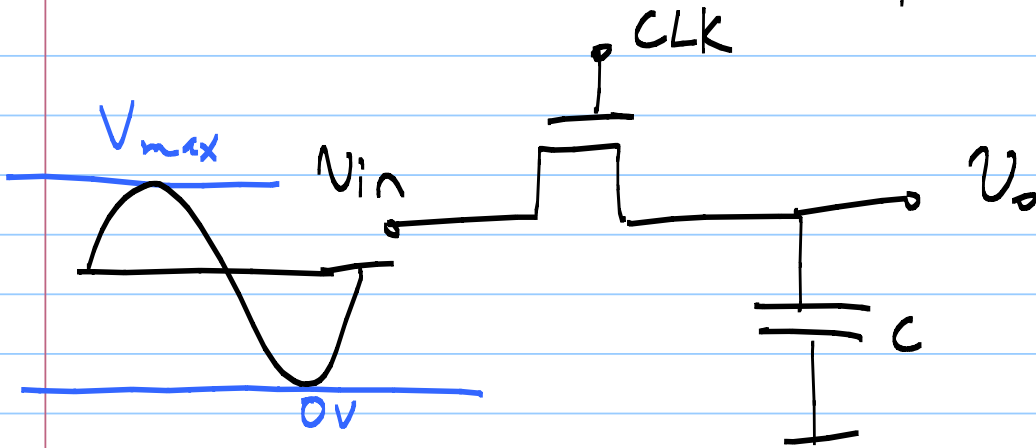
$$R_{on} = r_{ds} = \frac{1}{\beta_n (V_{gs} - V_T)}$$






$$R_{max} = 4 \times R_{on}(V_{in} = 0)$$

$$\frac{1}{\beta_n (V_{DD} - V_{in_{max}} - V_{Tn})} = \frac{4}{\beta_n (V_{DD} - V_{Tn})}$$

$$\Rightarrow V_{in_{max}} = \frac{3}{4} (V_{DD} - V_{Tn}) \approx 3V$$

5V
1V

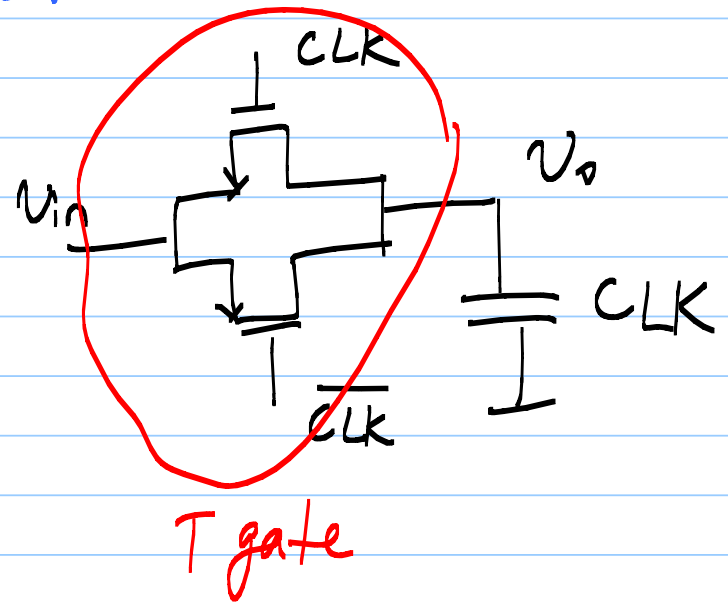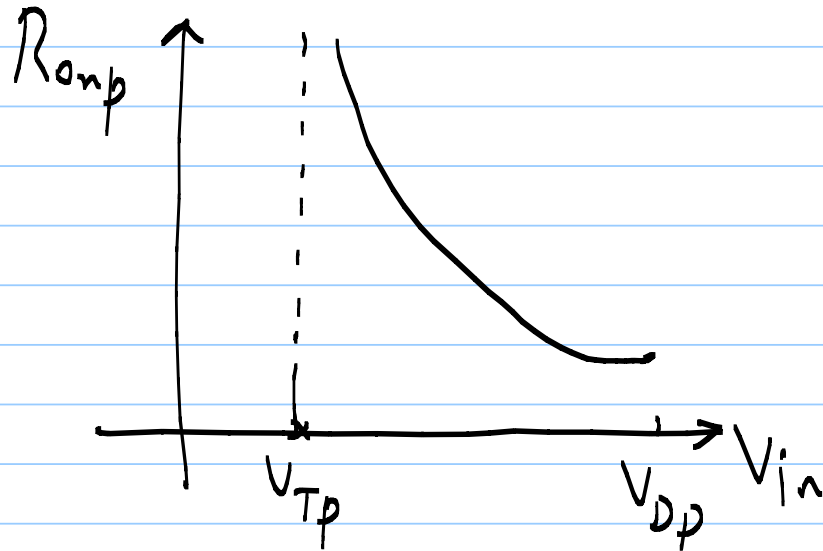

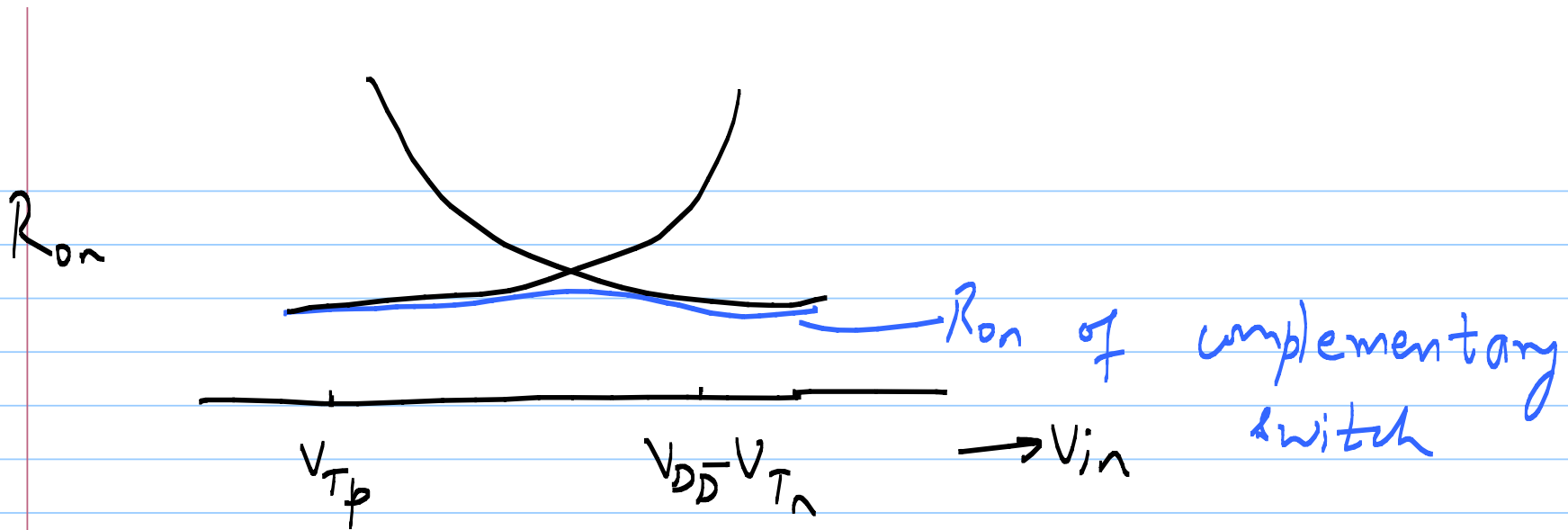


$$R_{on} = R_{onn} \parallel R_{onp}$$

$$= \frac{1}{\beta_n (V_{DD} - V_{in} - V_{TN})} \parallel \frac{1}{\beta_p (V_{in} - V_{TP})}$$


$$= \frac{1}{\beta_n (V_{DD} - V_{TN}) - \beta_p (V_{TP}) - \underbrace{(\beta_n - \beta_p) \cdot V_{in}}}$$

$$I_f \quad \beta_n = \beta_p \quad \text{i.e.} \quad \mu_n C_{ox} \left(\frac{W}{L}\right)_n = \mu_p C_{ox} \left(\frac{W}{L}\right)_p$$

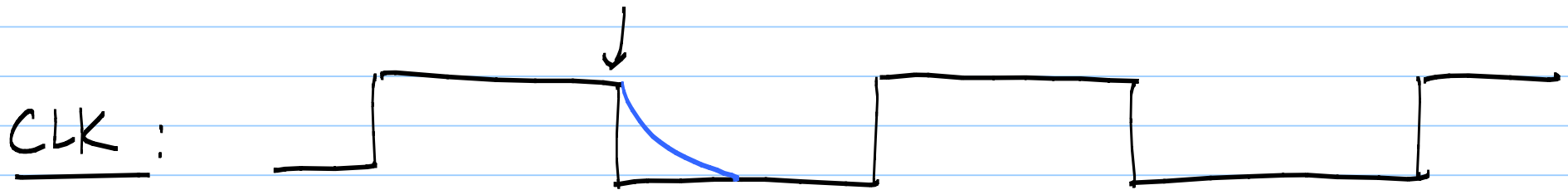$\Rightarrow R_{on}$  is independent of  $V_{in}$





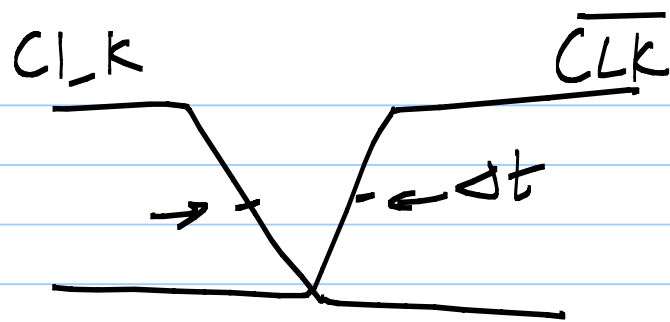Higher speed  $\Rightarrow$  low  $R_{on}$  and/or  $C$   
large  $(W/L)$




NMOS  
turns  
off first

Good  
clock  
signals

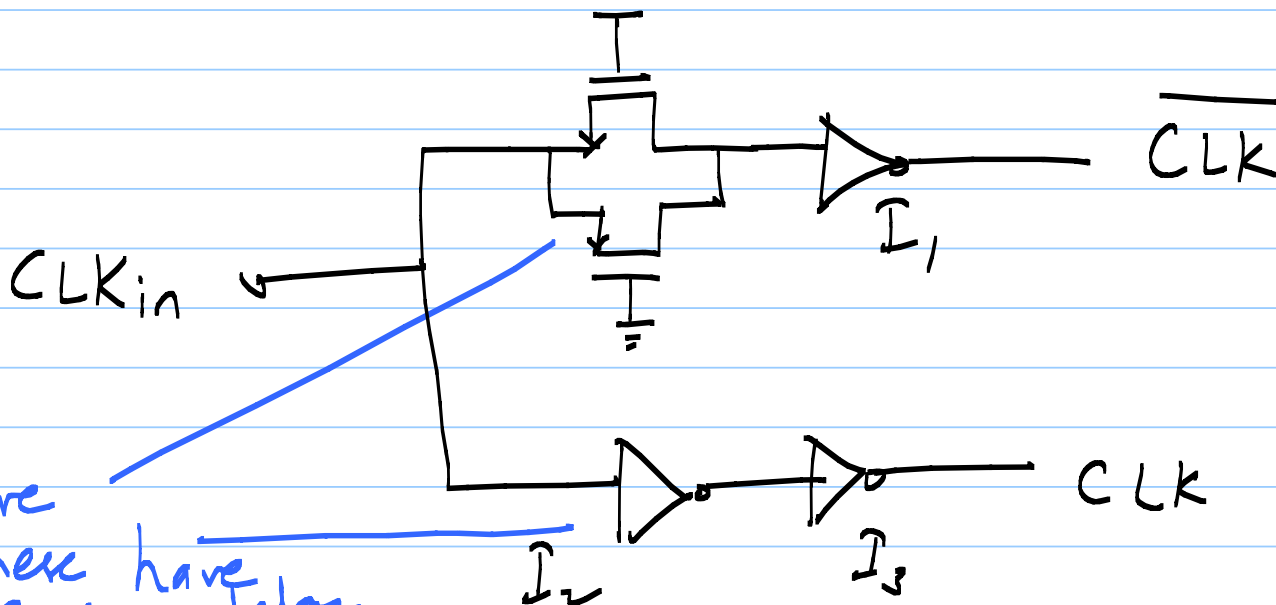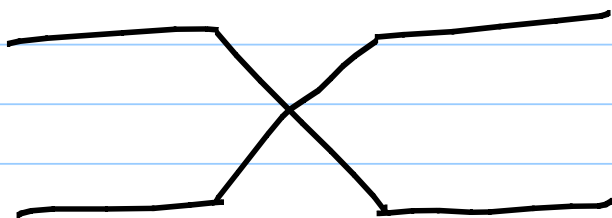

ensure  
that these have  
same delay

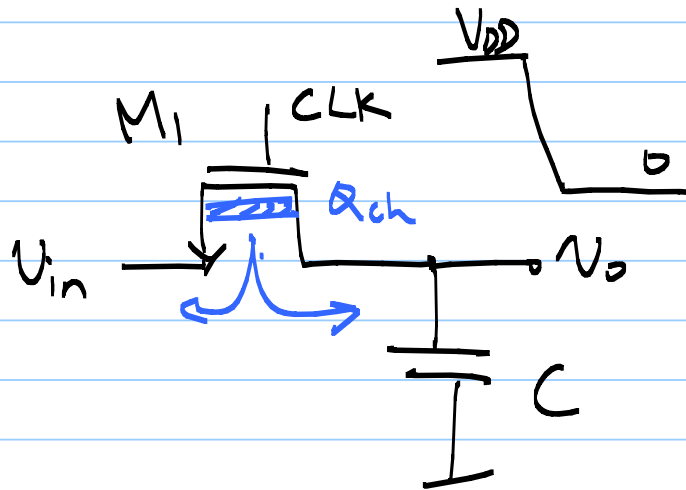

$$Q_{ch} = WL C_{ox} (V_{DD} - V_{in} - V_{Tn})$$

estimate  $\frac{Q_{ch}}{2}$  each goes into  $V_{in}$  &  $V_{out}$  nodes.

$$\Delta V_{out} = \frac{WL C_{ox} (V_{DD} - V_{in} - V_{Tn})}{2C}$$



Worst case: all of  $Q_{ch}$  goes into  $C$

$$\Delta V_{out} = \frac{WL C_{ox} (V_{DD} - V_{in} - V_{Tn})}{C}$$

$$V_{out} = V_{in} - \Delta V_{out}$$

$$= V_{in} - \frac{WL C_{ox} (V_{DD} - V_{in} - V_{Tn})}{C}$$
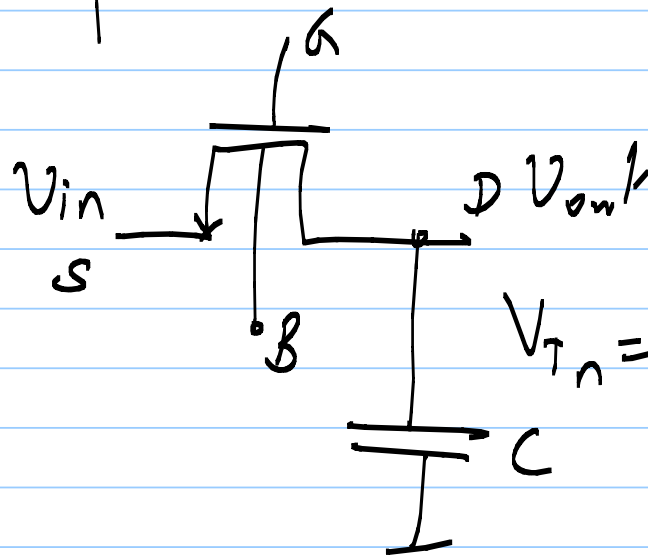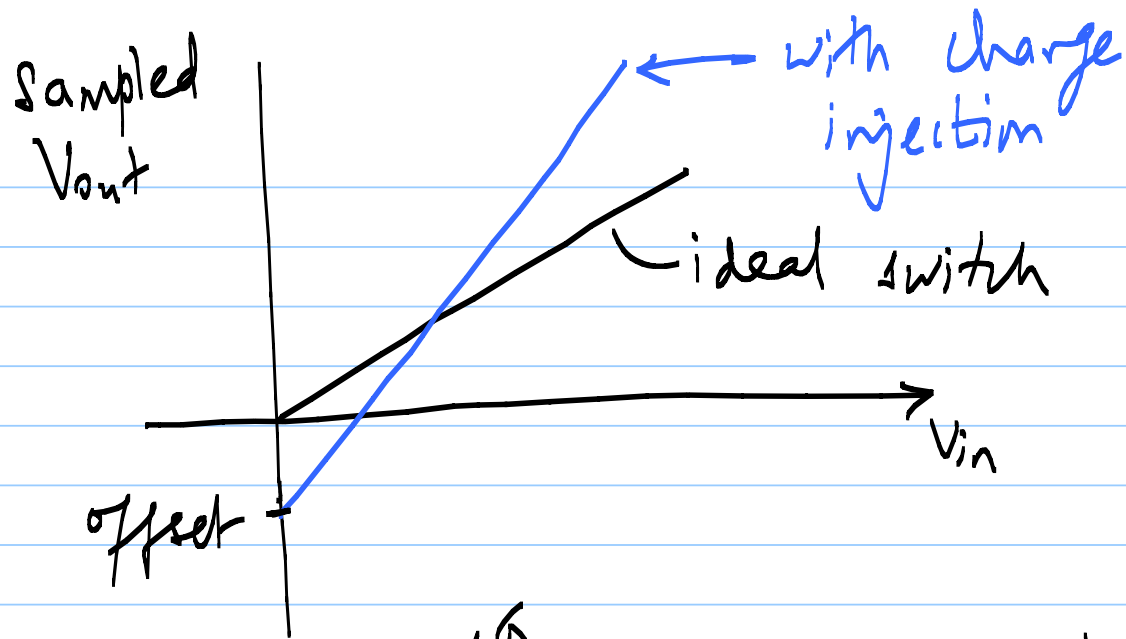
$$= V_{in} \underbrace{\left(1 + \frac{WL C_{ox}}{C}\right)}_{\text{gain error}} - \underbrace{\frac{WL C_{ox} (V_{DD} - V_{Tn})}{C}}_{\text{offset}}$$



$\Rightarrow V_{Tn}$  is not constant

$$V_{Tn} = V_{Tn0} + \gamma \left( \sqrt{2\phi_B + \underbrace{V_{SB}}_{V_{in}}} - \sqrt{2\phi_B} \right)$$

$$V_{out} = V_{in} - \frac{WLCo_x}{C} \left[ V_{DD} - V_{in} - V_{T0} - \gamma \sqrt{2\phi_B + V_{in}} + \gamma \sqrt{2\phi_B} \right]$$



$$= V_{in} \left( 1 + \frac{WL C_{ox}}{C} \right) + \gamma \frac{WL C_{ox}}{C} \cdot \underbrace{\sqrt{2\phi_B + V_{in}}}_{\text{non-linearity}}$$

$$- \underbrace{\frac{WL C_{ox}}{C} (V_{DD} - V_{Tn0} + \gamma \sqrt{2\phi_B})}_{\text{effect}}$$

gain error

FOM  $F = \frac{1}{\tau \cdot \Delta V}$

$$\tau = R_{on} \cdot C = \frac{C}{\beta_n (V_{DD} - V_{in} - V_{Tn})}$$


$$\Delta V = \frac{WL C_{ox}}{C} (V_{DD} - V_{in} - V_{Tn})$$

$$\tau \cdot \Delta V = \frac{C}{\mu_n C_{ox} \left(\frac{W}{L}\right) (V_{DD} - V_{in} - V_{Tn})} \cdot \frac{WL C_{ox}}{C} (V_{DD} - V_{in} - V_{Tn})$$

$$F = \frac{1}{C \cdot \Delta V}$$

$$= \frac{\mu_n}{L^2}$$

Clock feedthrough

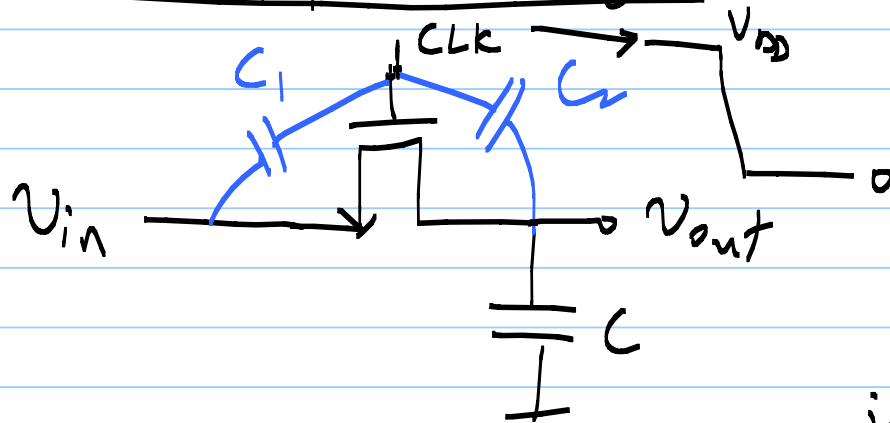


$$\Delta V_{out} = \frac{V_{DD} \cdot C_2}{C + C_2}$$

independent of  $V_{in}$

26/3/20

Lec 30

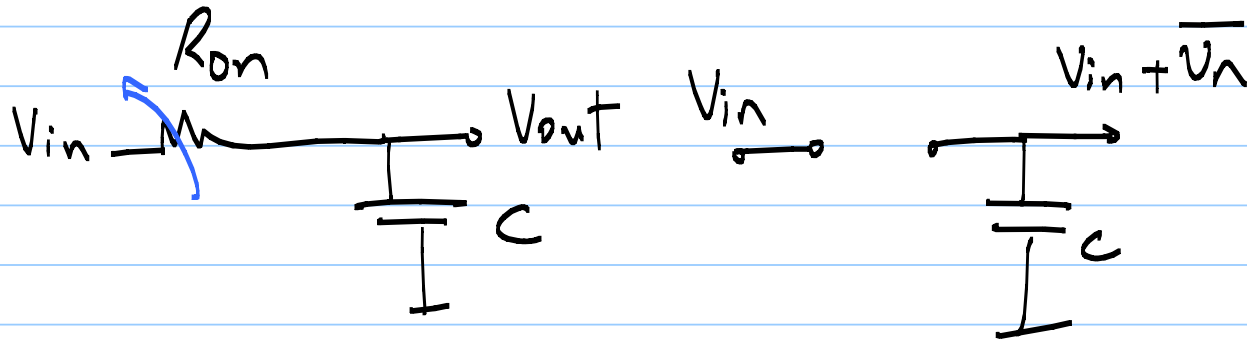


$$\text{integrated } \overline{v_{on}^2} \approx \frac{kT}{c}$$

high precision  $\Rightarrow$  low noise  $\Rightarrow$  C should be as large as possible

$\Rightarrow$  loading on preceding circuit

## Charge injection - mitigation


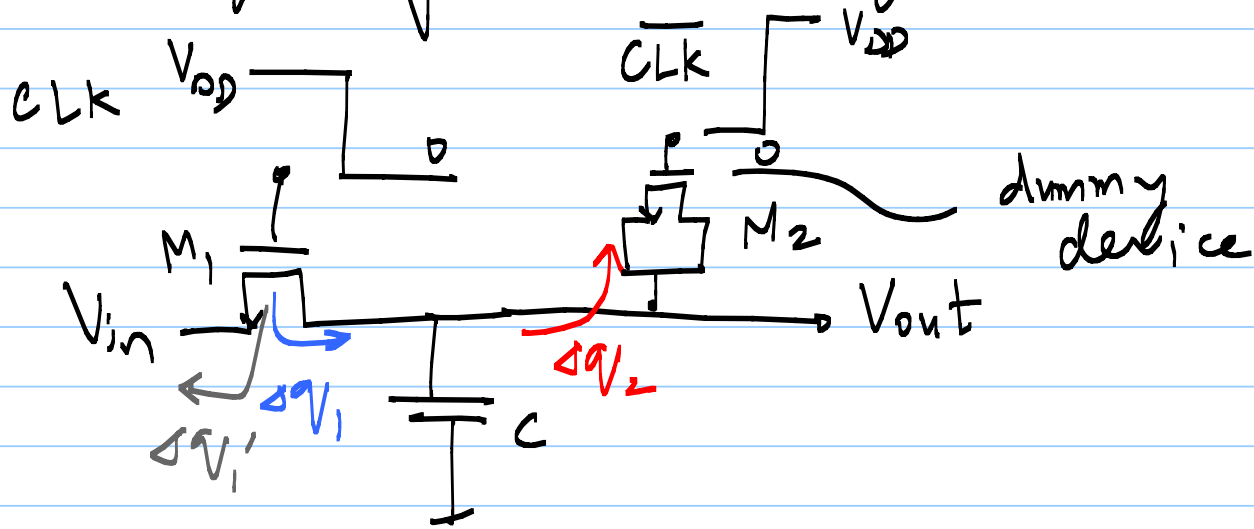



$$\Delta q_1 = \frac{W_1 L_1 C_{ox} (V_{DD} - V_{in} - V_{Tn1})}{2}$$

$$\Delta q_2 = W_2 L_2 C_{ox} (V_{DD} - V_{in} - V_{Tn2})$$

$$L_1 = L_2, \quad W_2 = 0.5 W_1 \Rightarrow \Delta q_2 = \Delta q_1$$

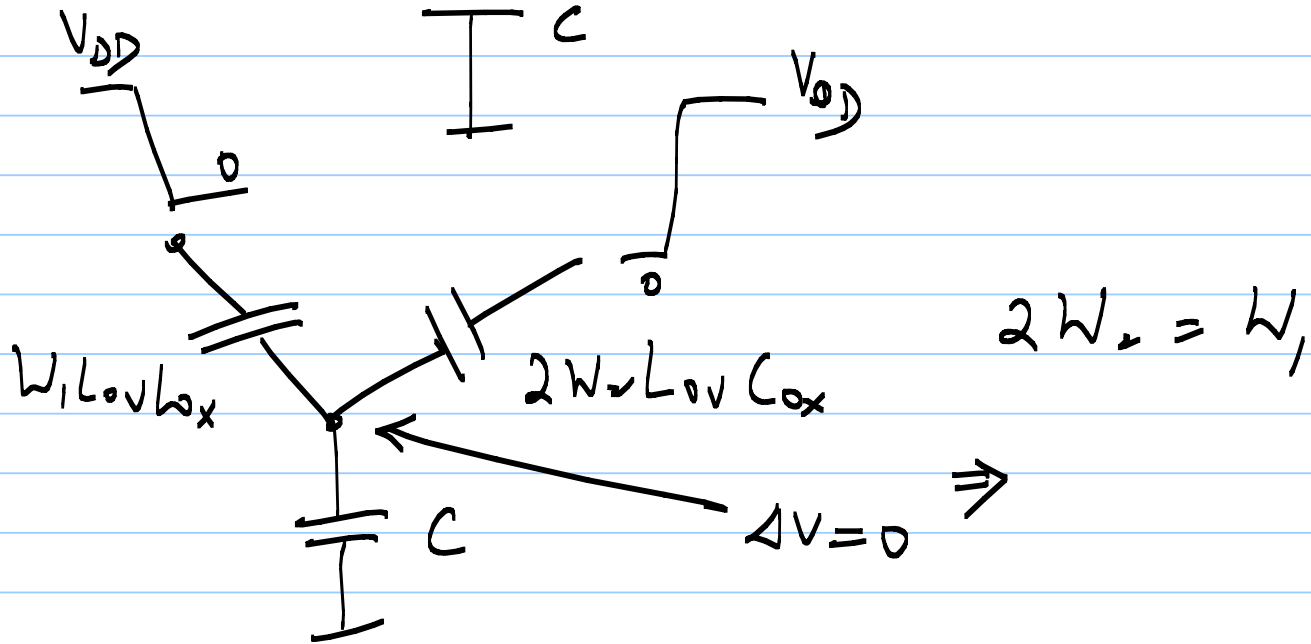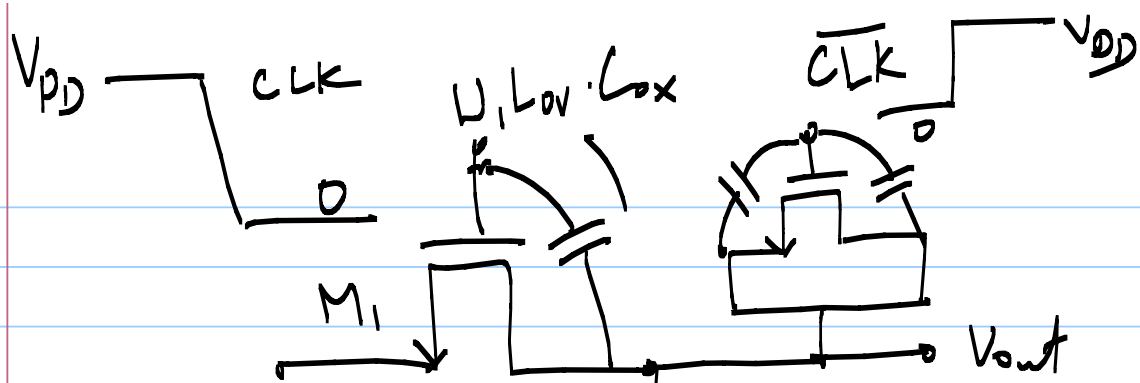\* will work well why if  $\Delta q_1 = \Delta q_1'$



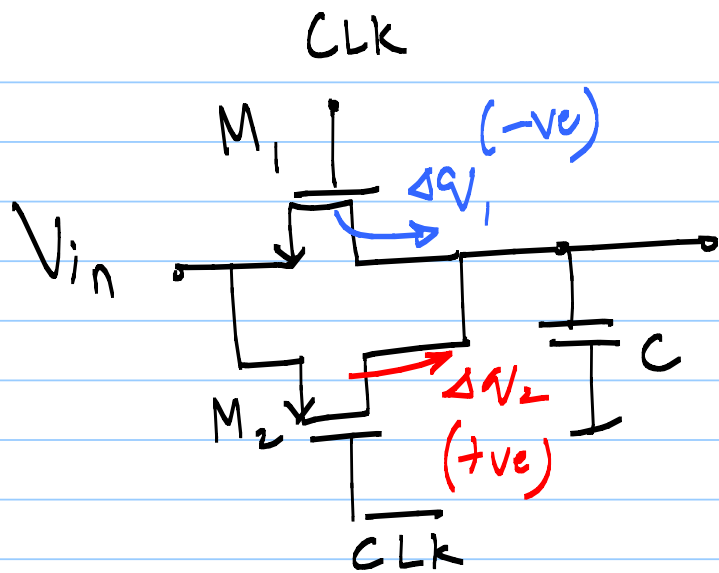

$$\Delta Q_1 = W_1 L_1 C_{ox} (V_{DD} - V_{in} - V_{Tn})$$

$$\Delta Q_2 = W_2 L_2 C_{ox} (V_{in} - V_{Tp})$$

for charge cancellation,  $\Delta Q_1 = \Delta Q_2$


$$W_1 L_1 C_{ox} (V_{DD} - V_{in} - V_{Tn}) = W_2 L_2 C_{ox} (V_{in} - V_{Tp})$$

$\Rightarrow$  valid for only one value of  $V_{in}$

\* CLK feedthrough - does not cancel completely

$$C_{ovp} \neq C_{ovn}$$

# Differential Circuit

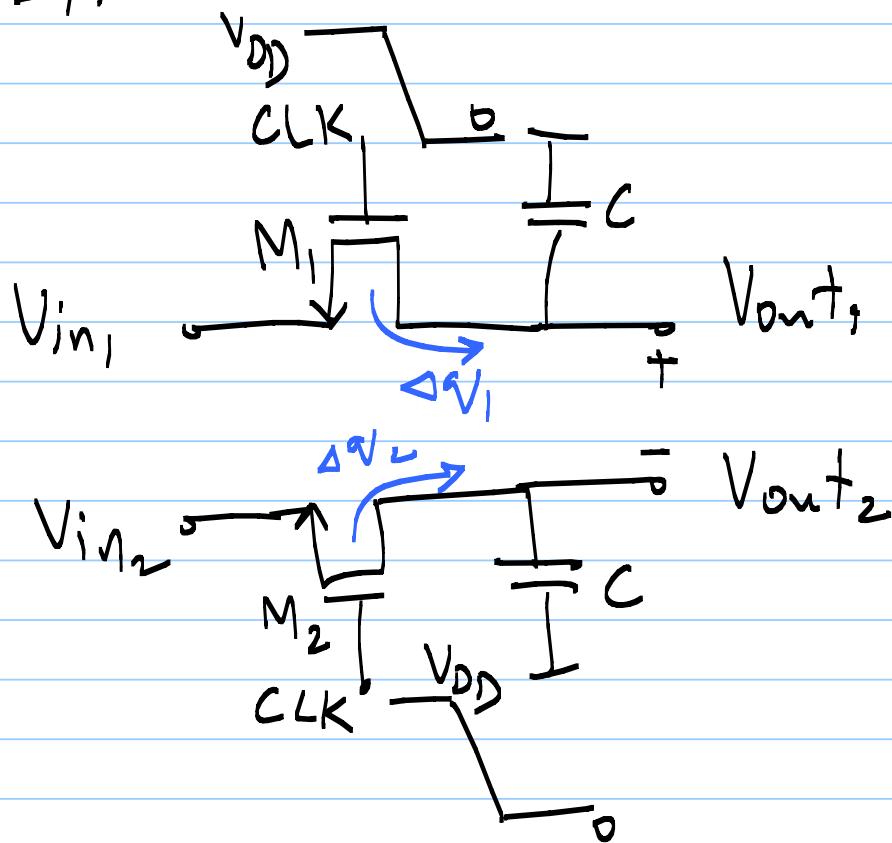

$$\Delta Q_1 = WL C_{ox} (V_{DD} - V_{in1} - V_{Tn})$$

$$\Delta Q_2 = WL C_{ox} (V_{DD} - V_{in2} - V_{Tn})$$

We want  $\Delta Q_1 = \Delta Q_2$  for diff. charge cancellati<sub>on</sub>.

$\Delta Q_1 = \Delta Q_2$  only if  $V_{in1} = V_{in2}$  { which is not true for diff. oper<sup>n</sup> }


$$\Delta V_1 - \Delta V_2 = WL C_{ox} \left[ (V_{in2} - V_{in1}) + (V_{Tn2} - V_{Tn1}) \right]$$

$$= WL C_{ox} \left[ \underbrace{(V_{in2} - V_{in1})} + \gamma \left( \sqrt{2\phi_f + V_{in2}} - \sqrt{2\phi_f + V_{in1}} \right) \right]$$


effects get cancelled

## SC amplifiers


1) Unity gain buffer

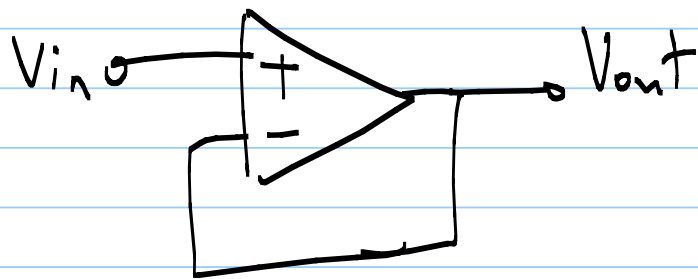


CT version

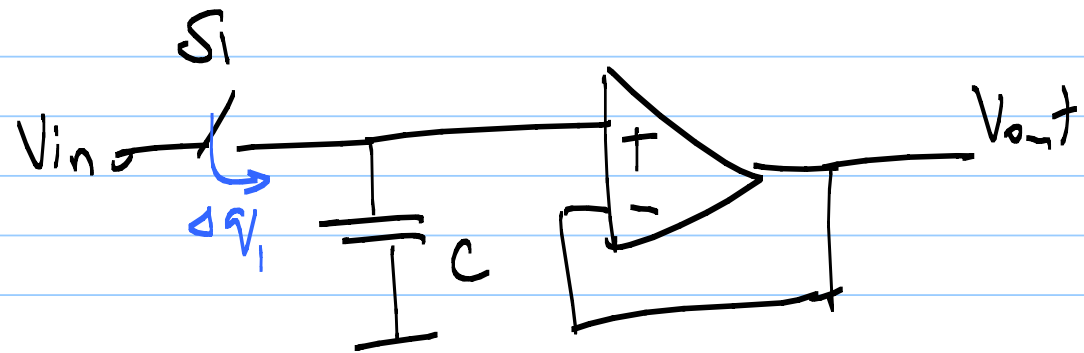



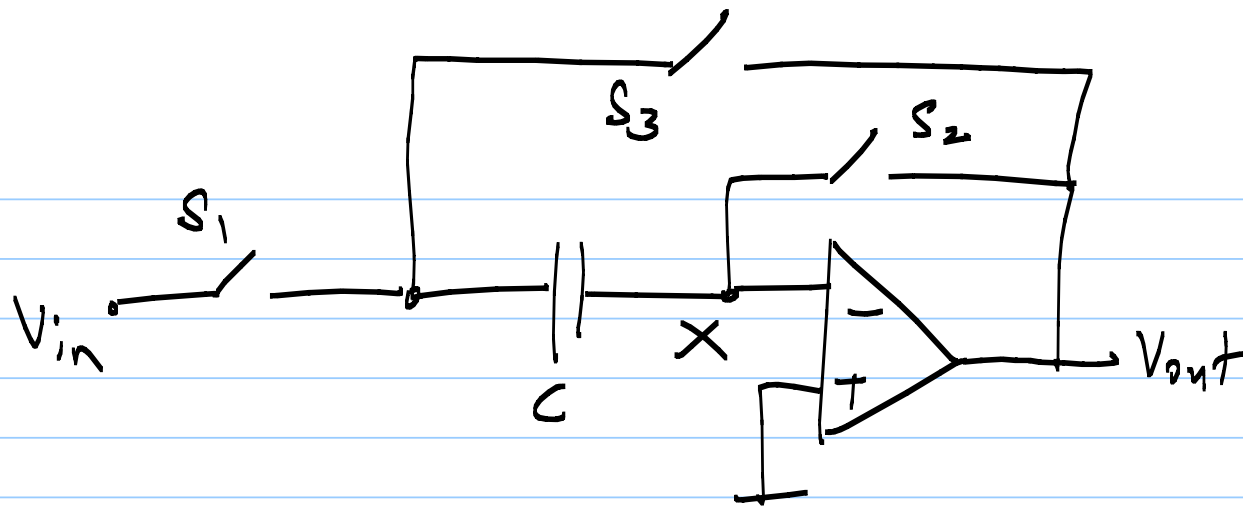

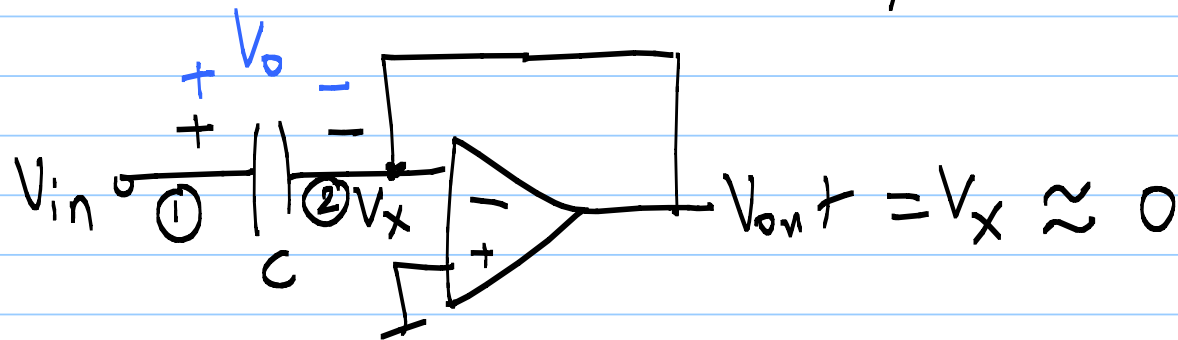
1) Sampling mode!  $S_1, S_2$  ON;  
 $S_3$  OFF



$V_{in} = V_C$  will track  $V_{in}$

@  $t = t_0$ ,  $\left. \begin{array}{l} \text{open } S_1 \ \& \ S_2 \\ \text{close } S_3 \end{array} \right\} \text{ say } V_{in} = V_0$


## 2) Amplification mode

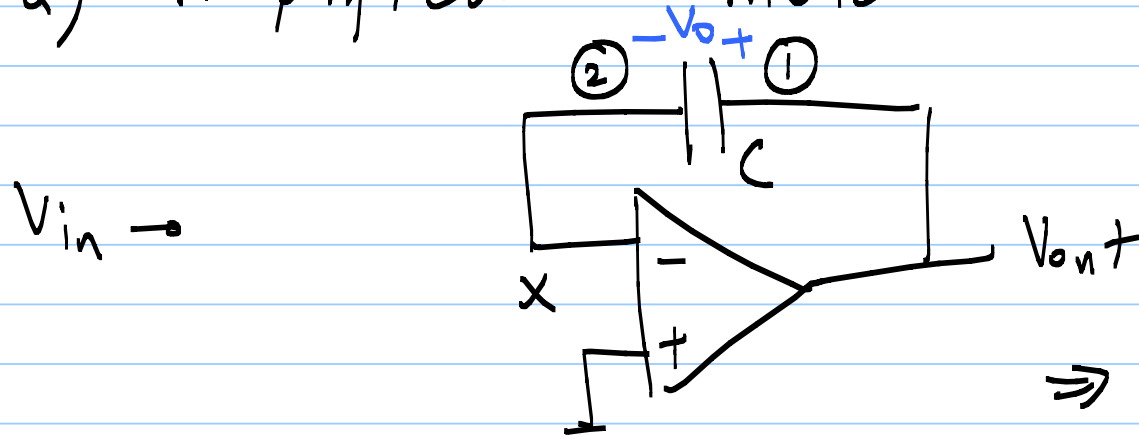

$V_x \approx 0$  due to ac -ve f.b. through C

$$\Rightarrow V_{out} = V_0$$

### Charge injection:

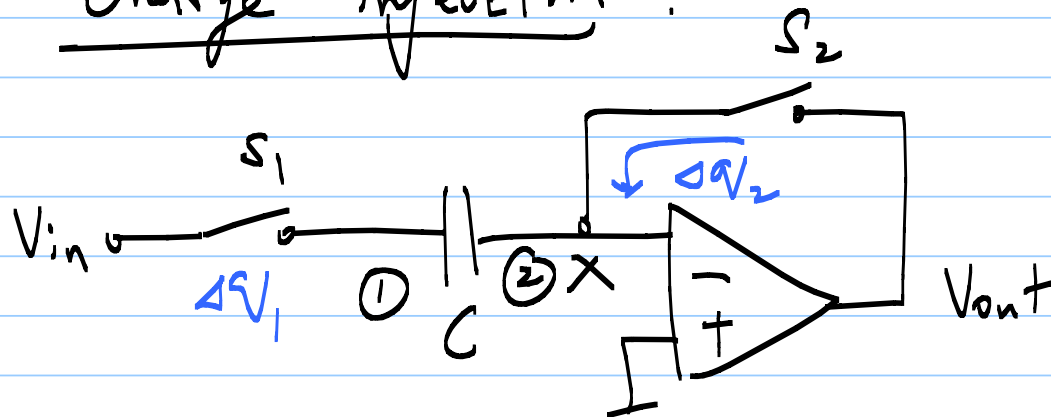


turn off  $S_2$  slightly before  $S_1$

$$\Delta V_c = \frac{\Delta Q_2}{C} \rightarrow \text{independent of } V_{in} \text{ because } x \text{ is a virtual ground}$$

$$\Delta Q_2 = WL C_x (V_{DD} - V_x - V_{Tn}) \Rightarrow \text{leads to offset}$$

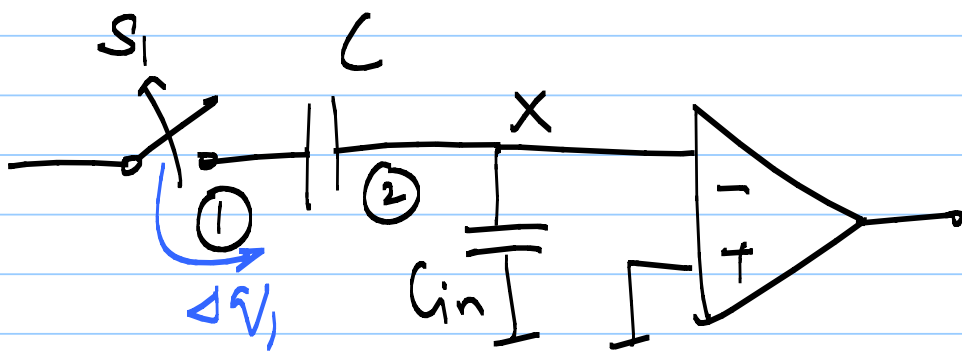→ Can be tackled using differential operation




$C$  &  $C_{in}$  both have charges  $\Delta Q_1$

↓  $S_3$  closed

assume

$$V_{in}(t_0) = V_0 = 0$$

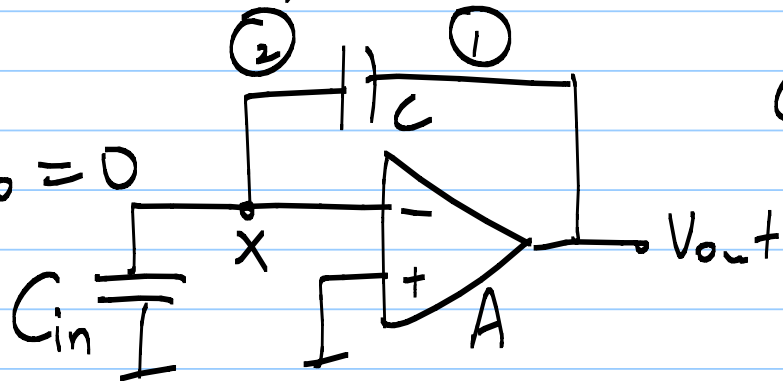

$$C_{in} V_x - (V_{out} - V_x) C = 0 \quad \text{--- (1)}$$

$$V_x = -\frac{V_{out}}{A} \quad \text{--- (2)}$$


$$\textcircled{1}: + (C_{in} + C) V_x - V_{out} C = 0$$

$$- (C_{in} + C) \cdot \frac{V_{out}}{A} - V_{out} C = 0$$

$$\Rightarrow V_{out} = 0 \quad (\text{independent of } s q_1)$$


S<sub>3</sub> turns on

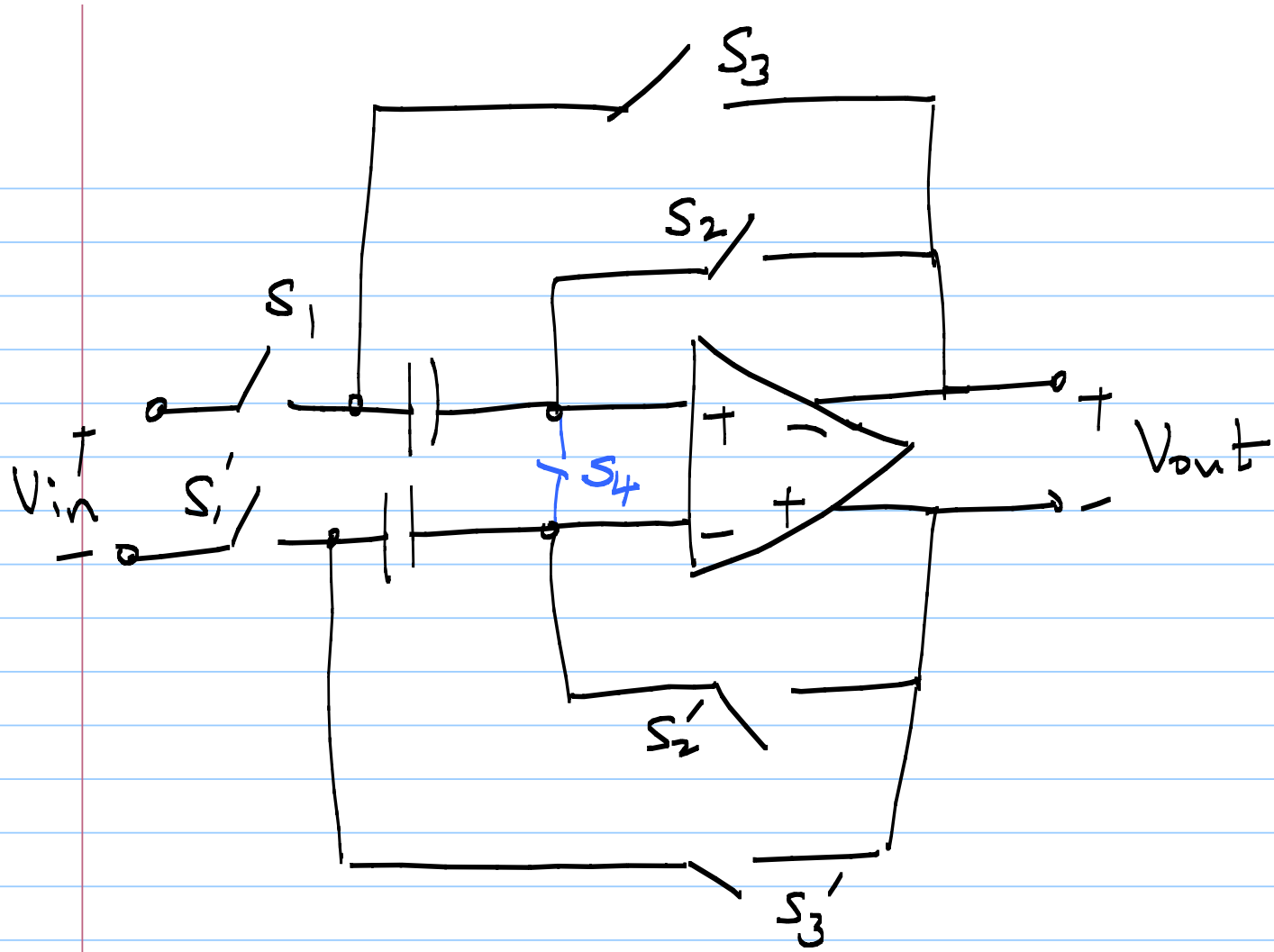$\Rightarrow$  channel charge needs to  
come from somewhere




27/3/20

Lec 31

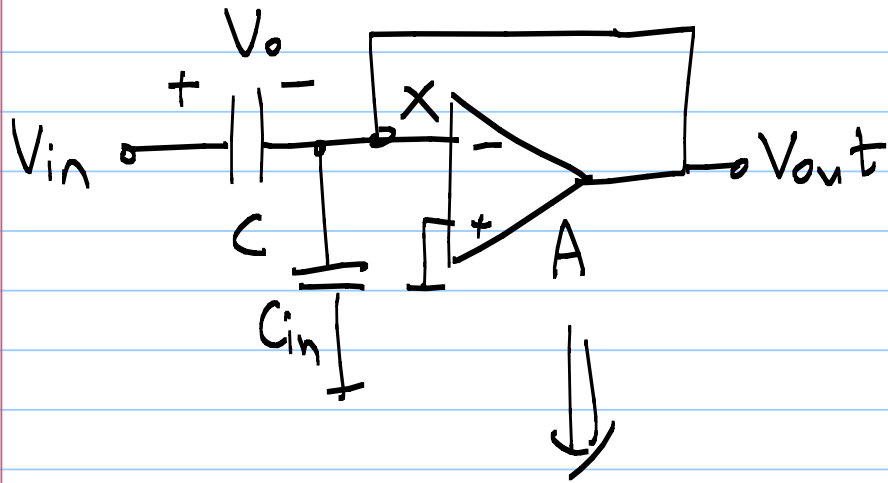

Sampling mode

Ampl. mode

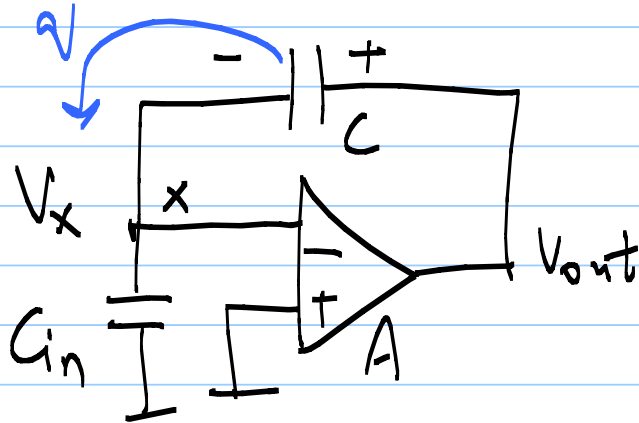

$V_x \neq 0$  (A is finite)

$C_{in}$  has been charged

to  $C_{in} \cdot V_x$

\* charge is conserved @ x  $\Rightarrow$  charge  $in C = C V_0 + C_{in} V_x$

⇒ Voltage across C

$$= \frac{C V_o + C_{in} V_x}{C}$$

$$V_x = V_{out} - \left[ \frac{C V_o + C_{in} V_x}{C} \right] \quad \text{--- (1)}$$

$$V_x = -\frac{V_{out}}{A} \quad \text{--- (2)}$$

$$-\frac{V_{out}}{A} = V_{out} - V_o - \frac{C_{in}}{C} \cdot \left( -\frac{V_{out}}{A} \right)$$

$$V_{out} \left[ 1 + \frac{1}{A} \left( 1 + \frac{C_{in}}{C} \right) \right] = V_o$$

$$V_{out} = \frac{V_o}{1 + \frac{1}{A} \left( \frac{C_{in}}{c} + 1 \right)}$$

$$\approx V_o \left[ 1 - \frac{1}{A} \left( \frac{C_{in}}{c} + 1 \right) \right]$$

error



$$\text{If } \frac{C_{in}}{c} \ll 1 \Rightarrow V_{out} \approx V_o \left( 1 - \frac{1}{A} \right)$$

\* minimise  $C_{in} \Rightarrow$  tradeoff precision with offset, power, noise etc.



Speed :

1) Sampling mode

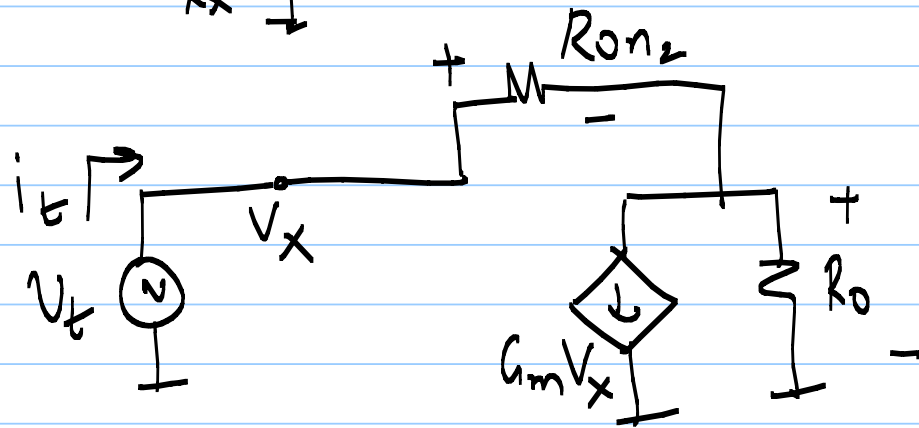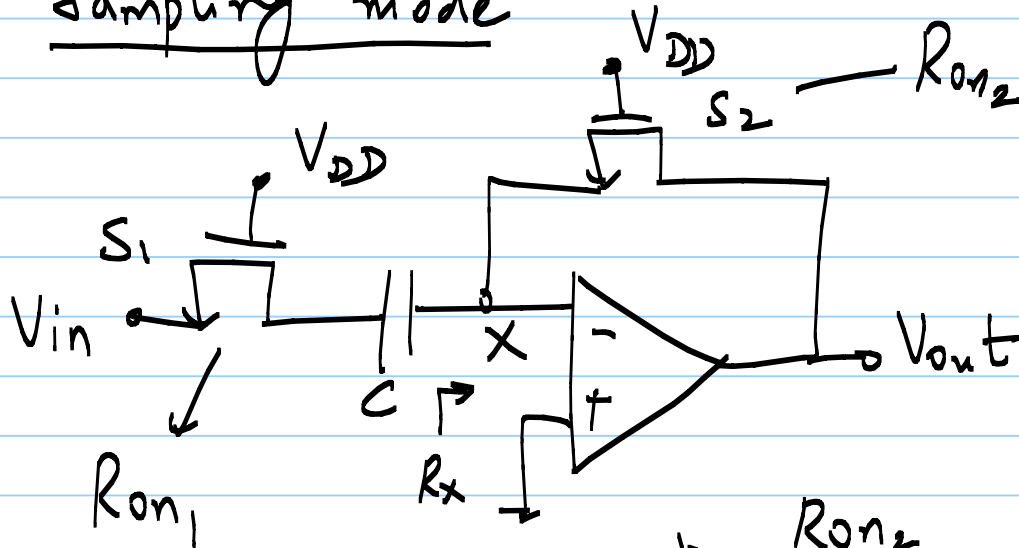

$$R_x = \frac{V_t}{i_t}$$

$$(i_t - G_m \cdot V_t) R_o + i_t \cdot R_{on2} = V_t$$

$$R_x = \frac{R_o + R_{on2}}{1 + G_m R_o}$$

$$R_o \Rightarrow R_{on2}$$


$$G_m R_o \gg 1$$

$$R_x \approx \frac{1}{G_m}$$

$$\tau_{\text{sampl.}} = \left( R_{on1} + \frac{1}{G_m} \right) \cdot C$$


small enough  
for  $V_c$  to settle  
to desired precision

## 2) Amplification mode ( $t = t_0$ )

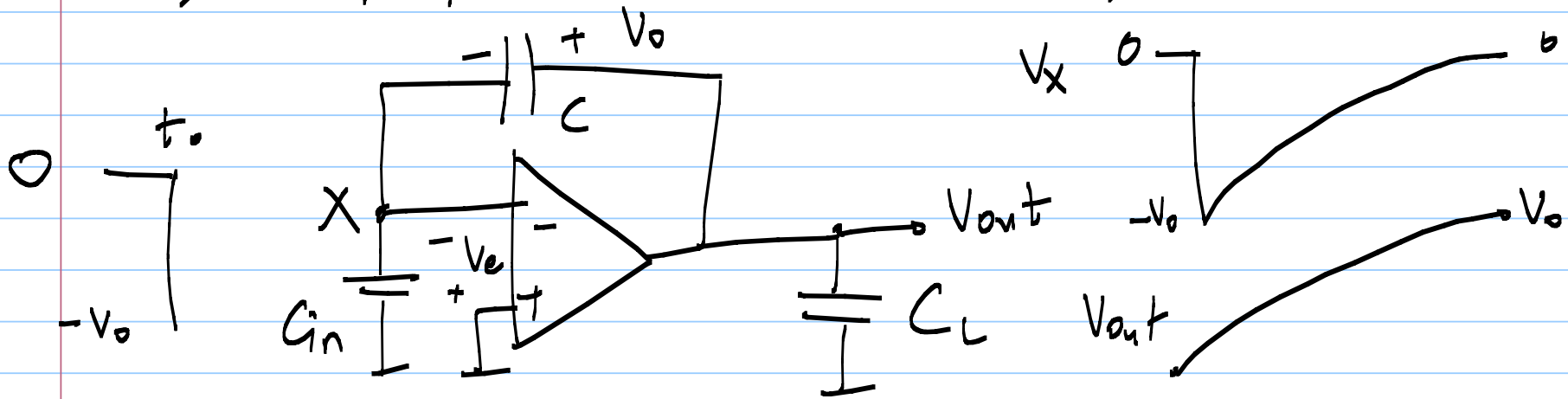

\*  $V_{out} \approx 0$  at beginning of ampl. phase ( $t = t_0^+$ )

\*  $V_e(t = t_0^+) = V_o$

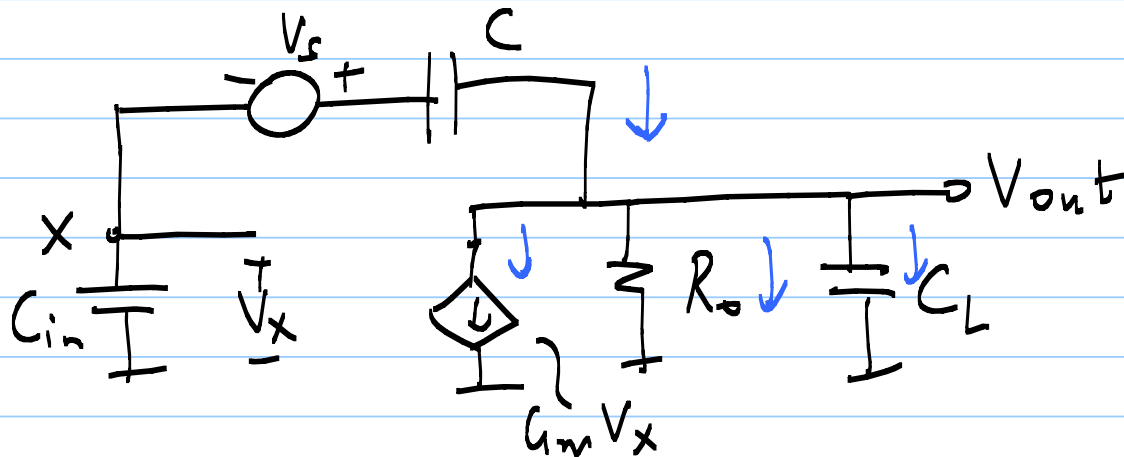

we want

$$\frac{V_{out}}{V_s} (s)$$

$$V_{out} \left( \frac{1}{R_o} + sC_L \right) + G_m V_x = (V_S + V_x - V_{out}) sC \quad \text{--- (3)}$$

$$i_{C_{in}} = V_x \cdot sC_{in} \rightarrow \text{also flows through } C$$

$$V_{out} = \frac{V_x \cdot sC_{in}}{sC} + V_x + V_S \quad \text{--- (4)}$$

$$V_{out} - V_S = V_x \left( 1 + \frac{C_{in}}{C} \right)$$

$$V_x = \left( \frac{C}{C + C_{in}} \right) (V_{out} - V_S) \quad \leftarrow \text{ply into (3)}$$

$$V_{out} \left( \frac{1}{R_o} + sC_L \right) + \frac{G_m C}{C + C_{in}} (V_{out} - V_s)$$

$$= \left[ V_s - V_{out} + \left( \frac{C}{C + C_{in}} \right) (V_{out} - V_s) \right] sC$$

$$\frac{V_{out}}{V_s}(s) = R_o \frac{(G_m + sC_{in}) C}{R_o (C_L C_{in} + C C_{in} + C C_L) s + G_m R_o C + C + C_{in}}$$

Assume

$$G_m R_o C \gg C + C_{in}$$


$$\frac{V_{out}}{V_s}(s) = \frac{(G_m + sC_{in}) C}{G_m C + s(C_L C_{in} + C C_{in} + C C_L)}$$

$$\tau_{amp.} = \frac{C_L C_{in} + C C_{in} + C C_L}{G_m C}$$


$$\tau_{\text{amp.}} = \frac{1}{g_m} \left[ C_{in} + \left( 1 + \frac{C_{in}}{C} \right) C_L \right]$$

larger  $C_{in}$   
 $\rightarrow$  lower speed


C  $\rightarrow$

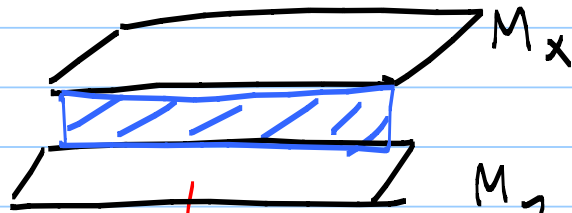


MIM capacitor

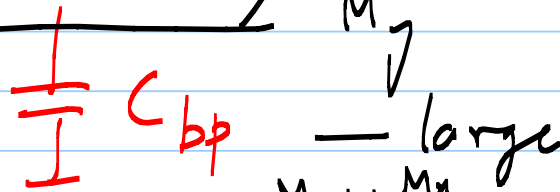

$C_{in} + C_{bp}$

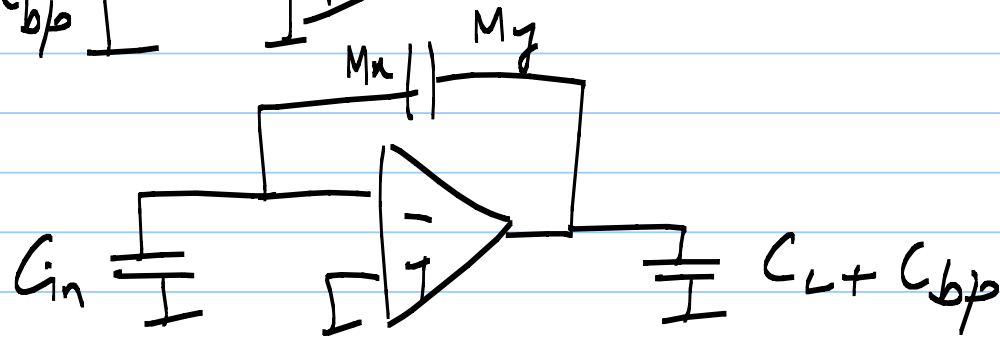


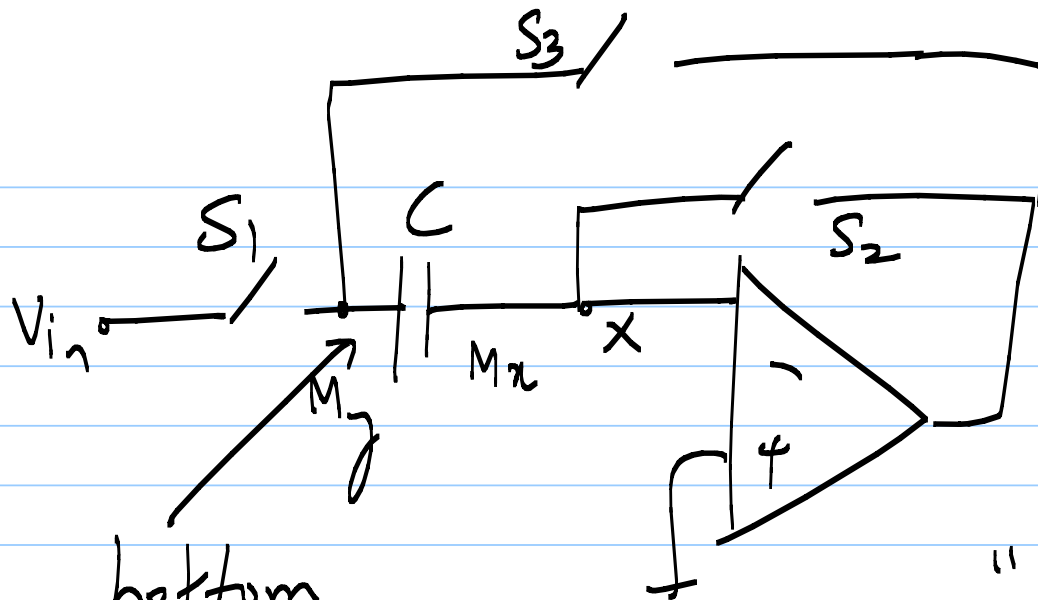


bottom  
plate

" bottom plate  
sampling "

# Non-inverting amplifier


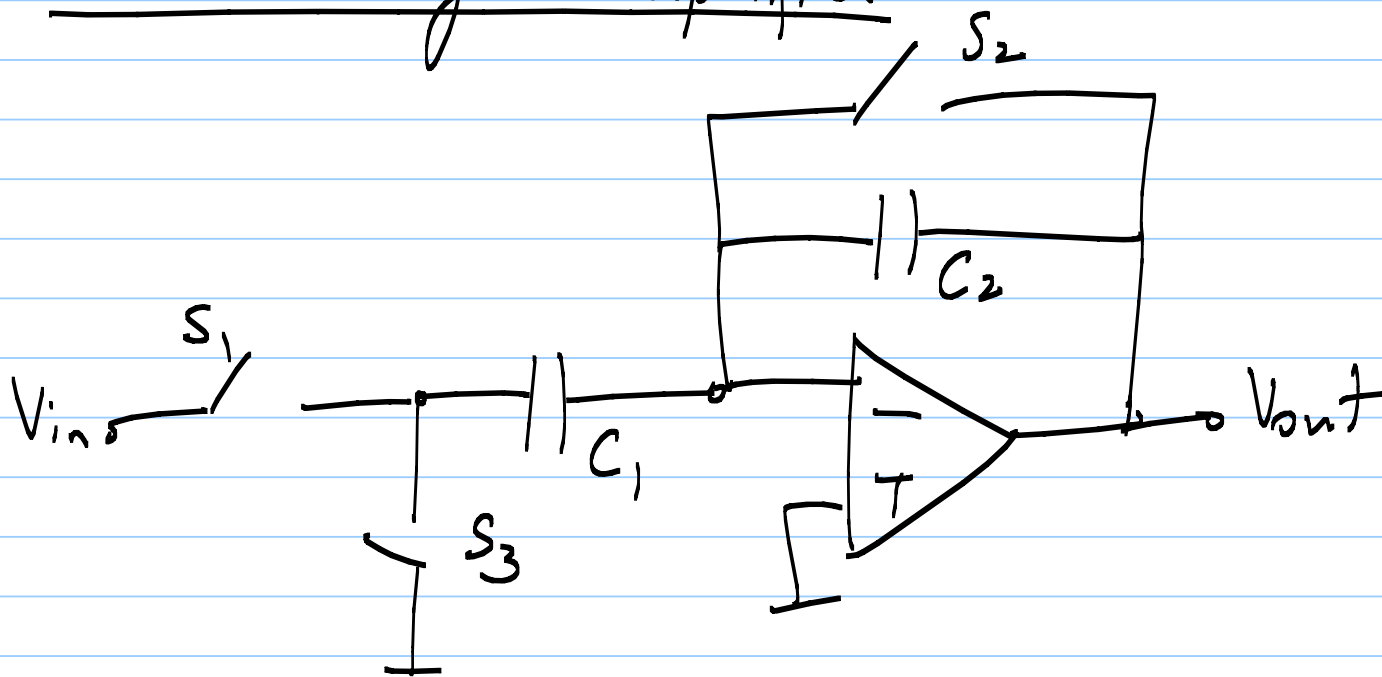


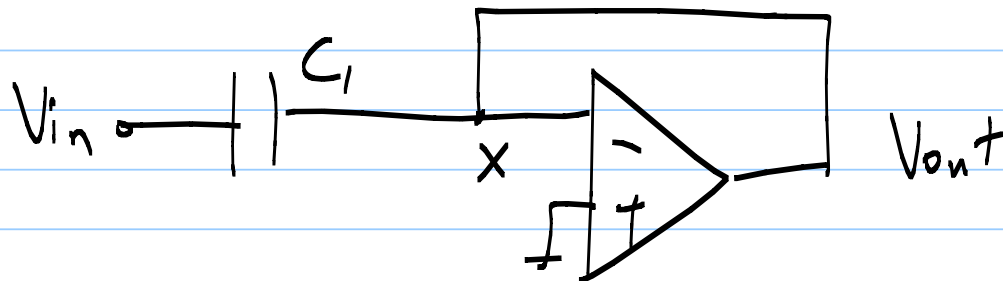Sampling  $\rightarrow S_1, S_2$  on ;  $S_3$  off




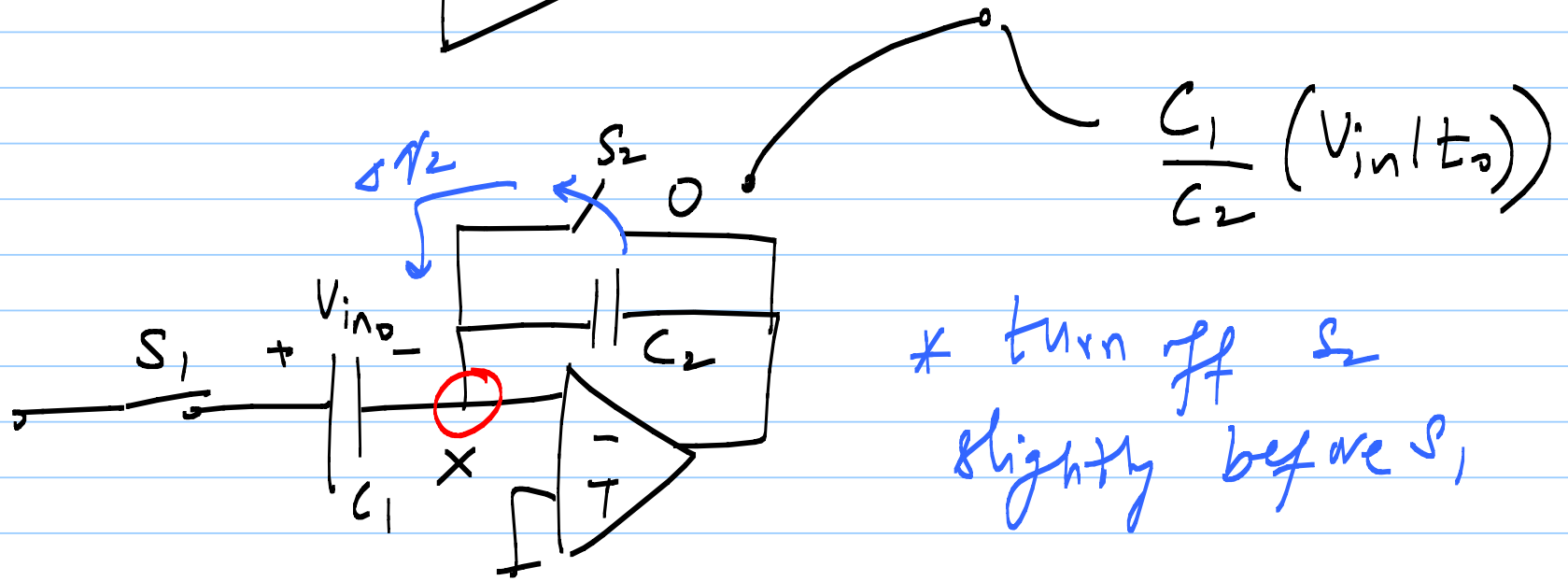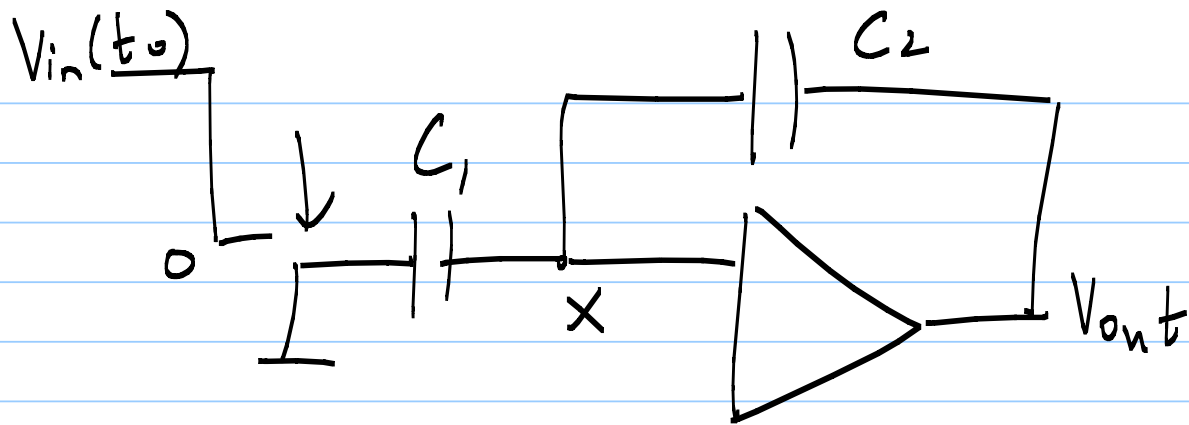Ampl. mode :  $S_1, S_2$  off ;  $S_3$  on








$$\frac{C_1}{C_2} (V_{in}(t_0))$$

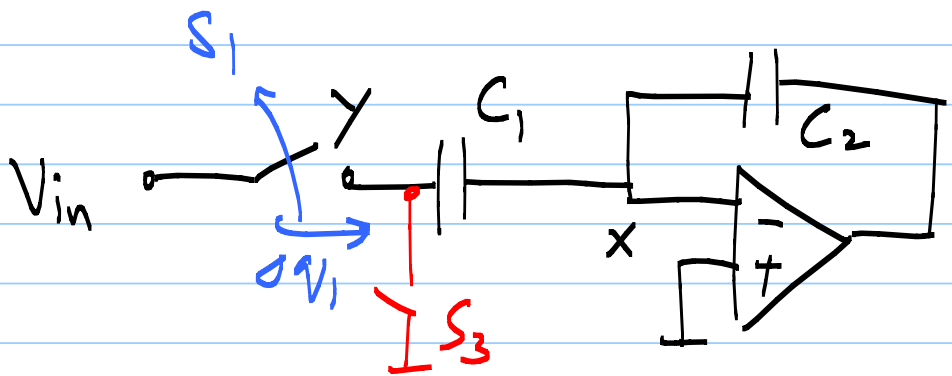

$$\Delta V_y = \frac{\Delta V_1}{C_1}$$
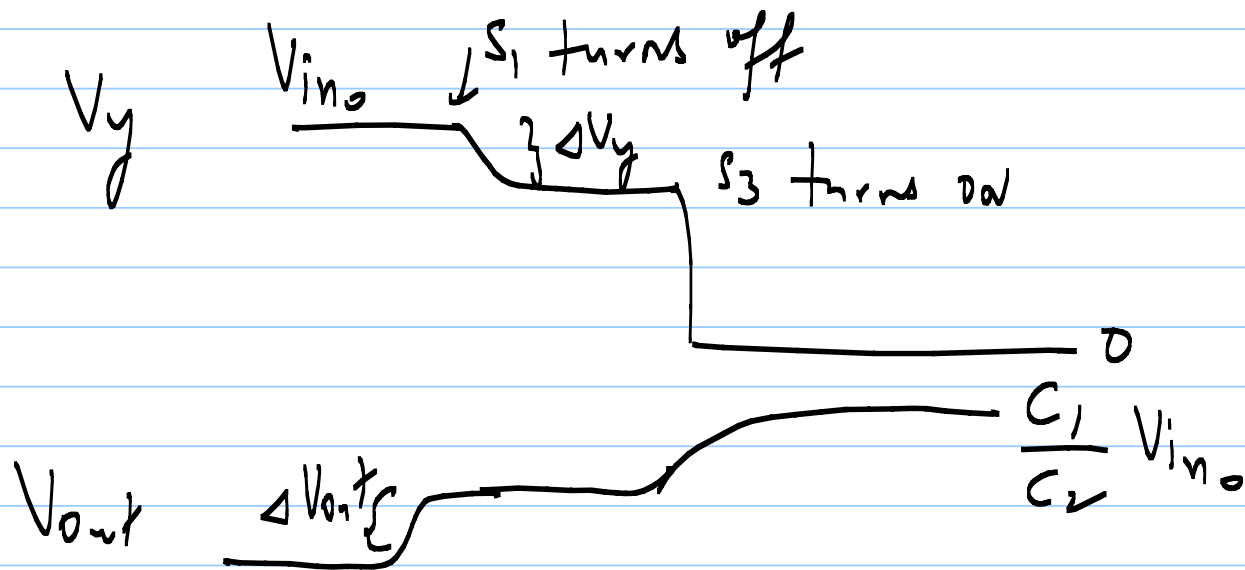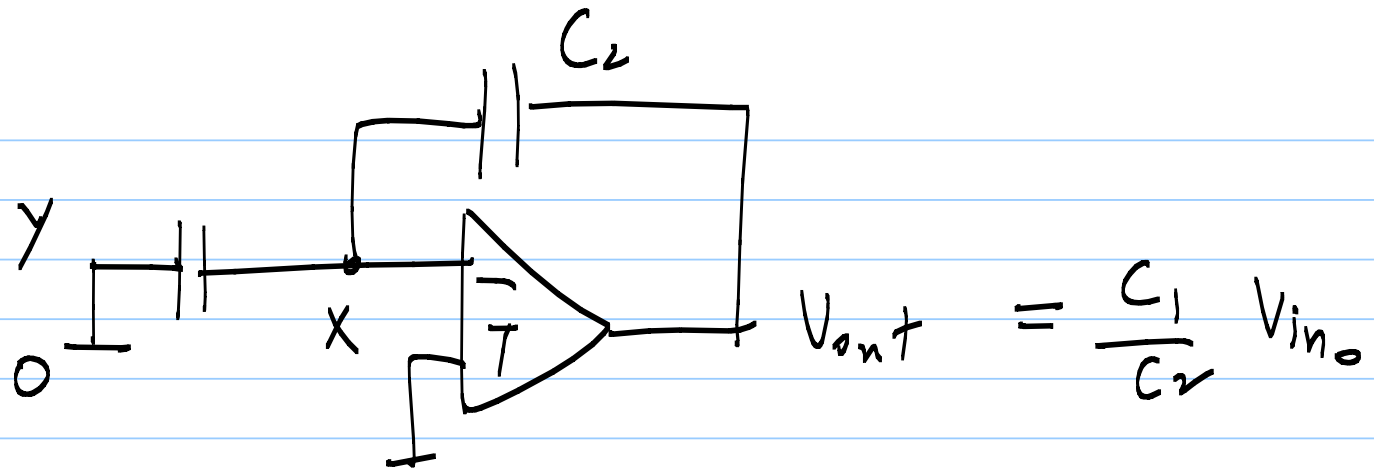
$$\Delta V_{out} = \Delta V_y \cdot ( )$$



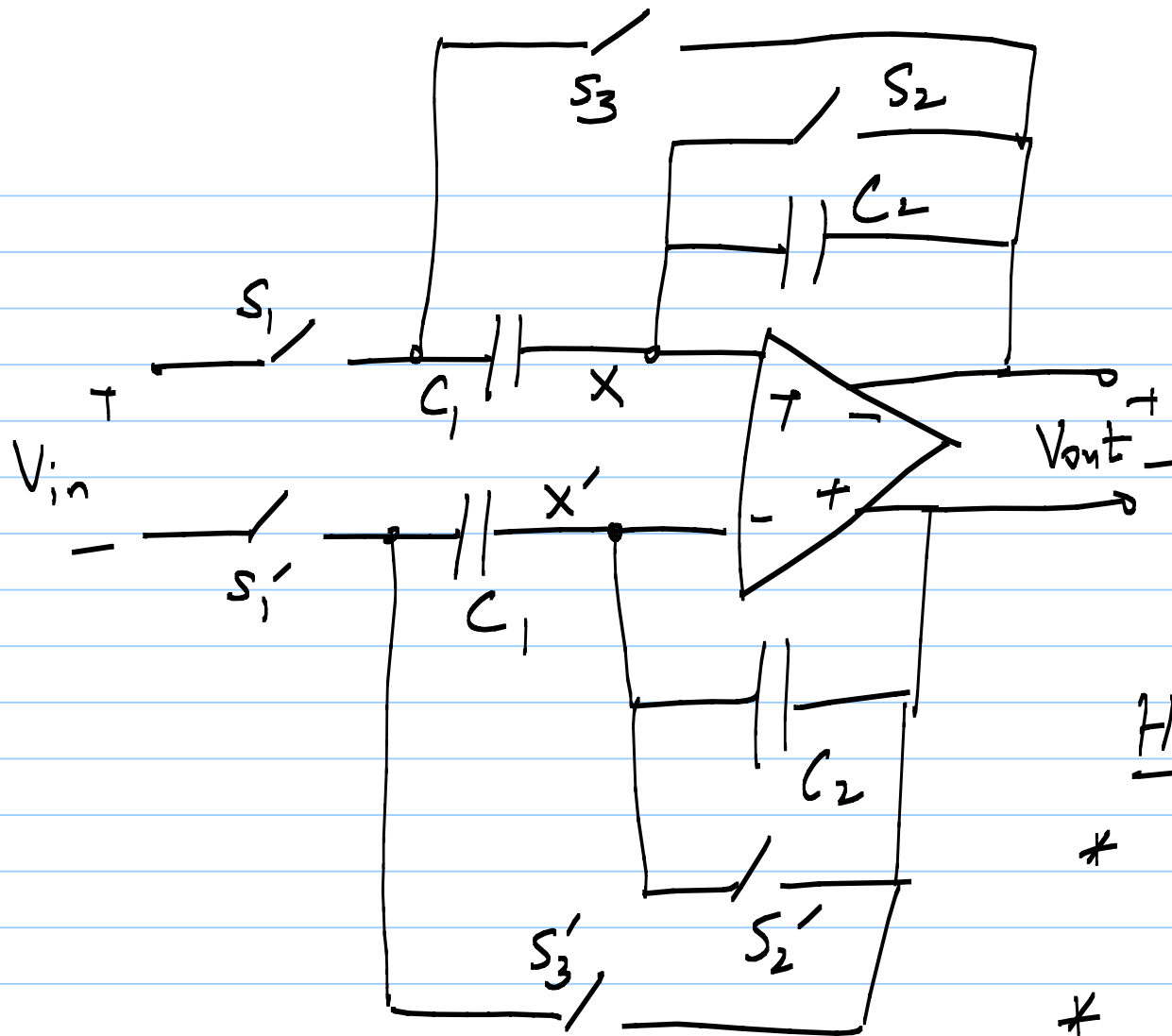


HW

- \* Finite  $A$  & non-zero  $C_{in}$
- \* gain error
- \*  $\tau_{\text{sampl}}$  &  $\tau_{\text{ampl}}$ .


31/3/20

Lec 32

1) Precision

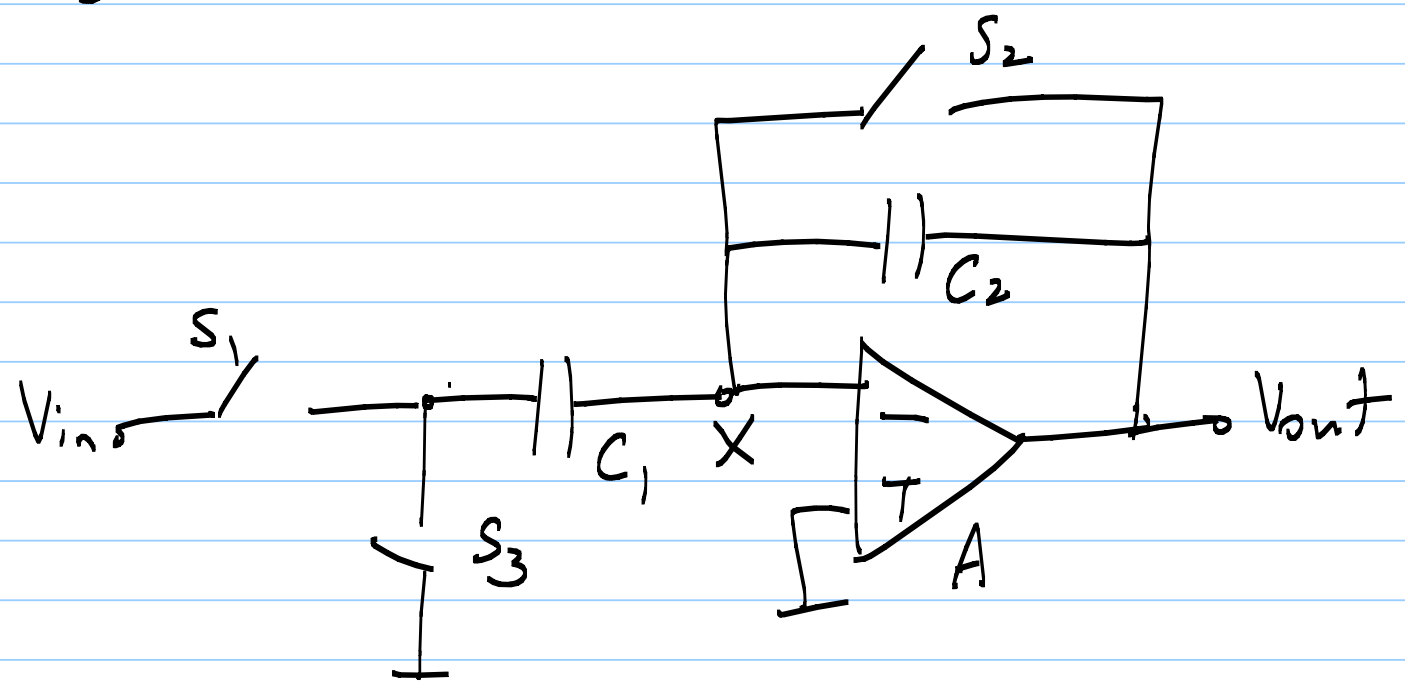

In ampl. mode:

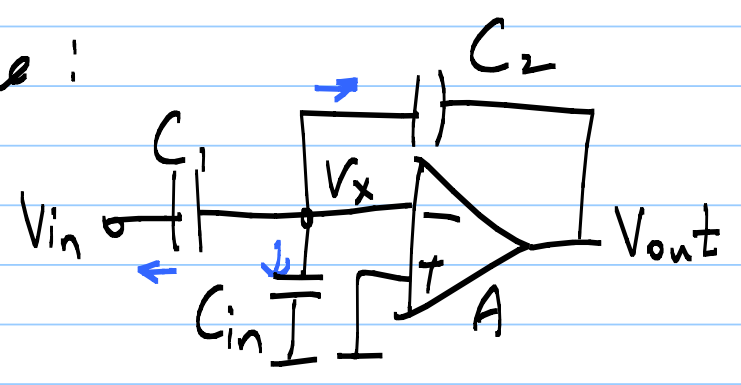

$$V_x = -\frac{V_{out}}{A}$$

KCL @ x:

$$(V_x - V_{in}) \cdot C_1 + V_x \cdot C_{in} + (V_x - V_{out}) \cdot C_2 = 0$$

$$\left(-\frac{V_{out}}{A} - V_{in}\right) \cdot C_1 - \frac{C_{in} V_{out}}{A} - V_{out} \left(1 + \frac{1}{A}\right) \cdot C_2 = 0$$

$$-V_{in} \cdot C_1 = V_{out} \left( C_2 + \frac{C_2}{A} + \frac{C_{in}}{A} + \frac{C_2}{A} \right)$$


$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{C_1}{C_2 + \frac{1}{A} (C_1 + C_2 + C_{in})}$$

$$= \frac{C_1}{C_2} \cdot \frac{1}{1 + \frac{1}{A} \cdot \frac{1}{C_2} (C_1 + C_2 + C_{in})}$$


$$\left| \frac{V_{out} t}{V_{in}} \right| \approx \frac{C_1}{C_2} \left[ 1 - \underbrace{\frac{1}{A} \frac{C_1 + C_2 + C_{in}}{C_2}} \right]$$

gain error  
(increases with  $C_1/C_2$ )

2) Speed in ampl. mode

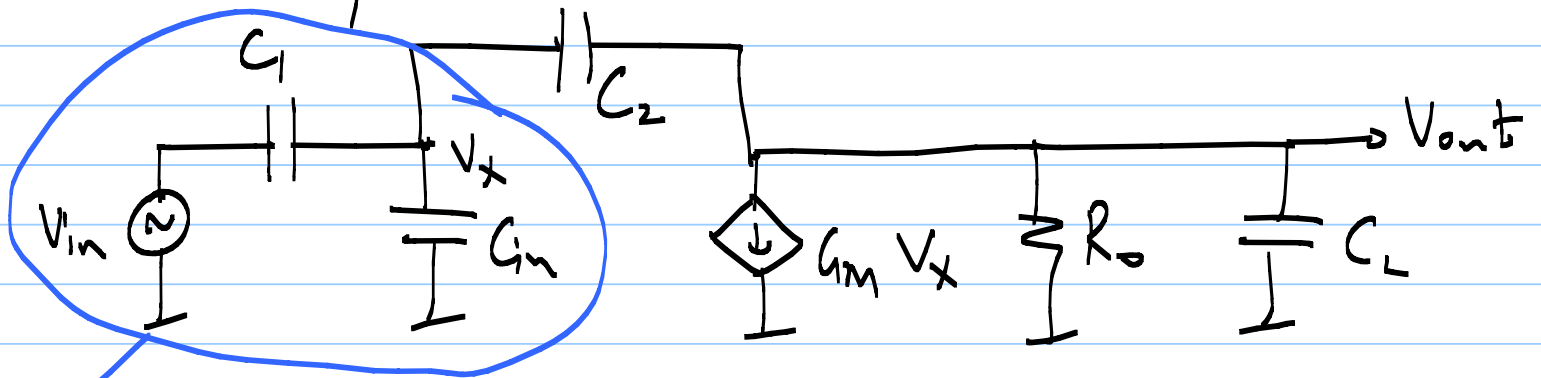

Replace with thevenin eq. ckt @ x

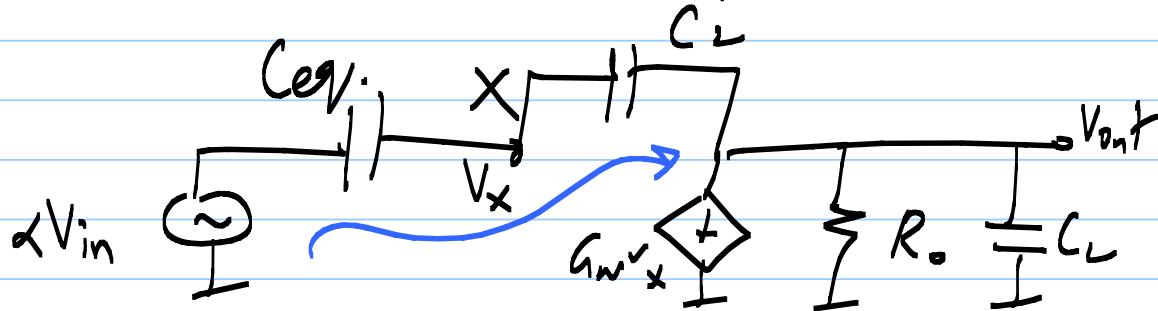

$$\alpha = \frac{g_m}{C_1 + C_{in}} ; \quad C_{eq.} = C_1 + C_{in}$$

$$V_x = (\alpha V_{in} - V_{out}) \cdot \frac{C_{eq.}}{C_2 + C_{eq.}} + V_{out}$$

KCL @ output node

$$g_m V_x + V_{out} \left[ \frac{1}{R_o} + sC_L \right] = sC_2 \cdot \underbrace{(V_x - V_{out})}_{\substack{= \\ \frac{C_{eq.}}{C_2 + C_{eq.}} (\alpha V_{in} - V_{out})}}$$

$$\left( \alpha V_{in} - V_{out} \right) \frac{C_{eq.}}{C_2 + C_{eq.}} + V_{out} \quad G_m$$

$$V_{out} \left( \frac{1}{R_o} + s C_L \right) = \left( \alpha V_{in} - V_{out} \right) \frac{C_{eq.}}{C_2 + C_{eq.}} \cdot s C_2$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{-C_{eq.} \frac{C_1}{C_1 + C_{in}} (G_m - s C_2) \cdot R_o}{s R_o [C_2 C_{eq.} + C_2 C_L + C_L C_{eq.}] + \frac{C_2 G_m R_o}{C_{eq.} + C_2}}$$

$$\text{If } G_m R_o \gg 1 \Rightarrow G_m R_o C_2 \gg C_{eq.} + C_2$$




$$\frac{V_{out}}{V_{in}}(s) \approx \frac{-C_{eq} \frac{C_1}{C_1 + C_{in}} (g_m - s C_2)}{s(C_2 C_{eq} + C_L C_{eq} + C_L C_2) + g_m C_2}$$

$$\tau_{amp.} = \frac{C_2 C_{eq} + C_L C_{eq} + C_L C_2}{g_m C_2}$$


$$\tau_{amp.} = \frac{C_1 + C_2 + C_{in}}{C_2} \cdot \frac{C_L + \frac{C_L (C_{in} + C_1)}{C_2 + C_{in} + C_1}}{g_m}$$

← equivalent resistance
→ eq. cap.

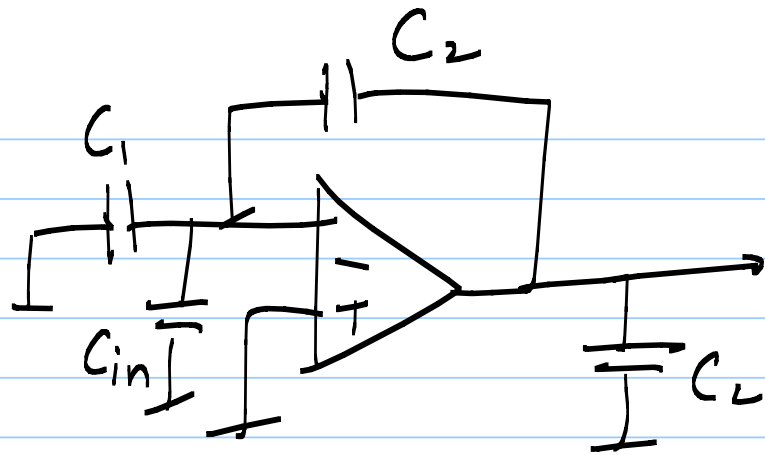

## Switched - capacitor integrator

CT integrator:

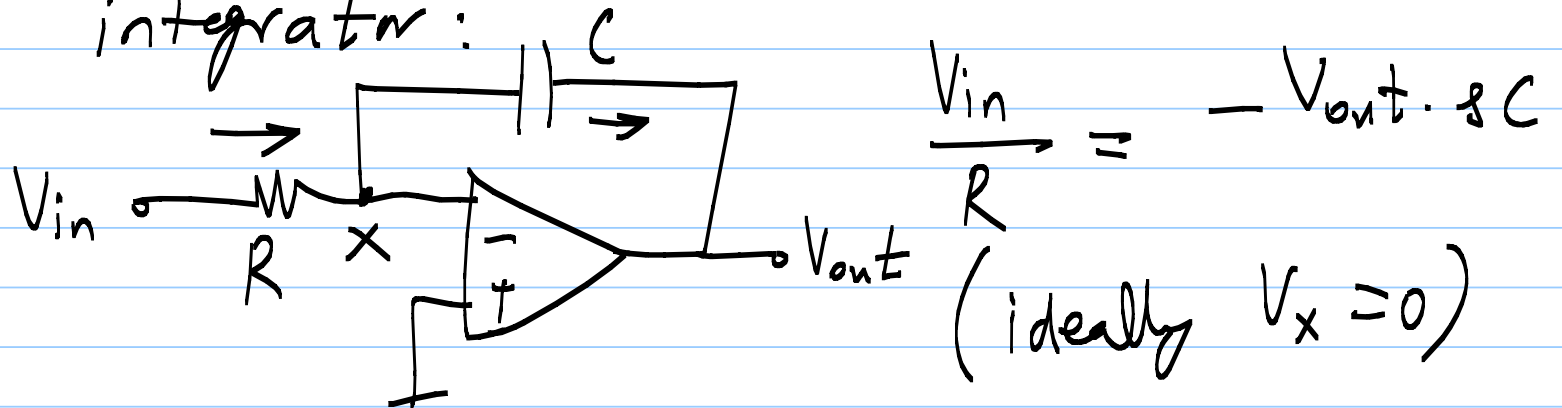

$$\frac{V_{out}}{V_{in}}(s) = \frac{-1}{sCR}$$

$$V_{out}(t) = \frac{-1}{RC} \int_{-\infty}^t V_{in} dt$$

### Issues



1)  $R_{in} = R$  { loads previousckt }

2)  $\frac{V_{out}}{V_{in}}(\omega) = \frac{-1}{\omega} \cdot \frac{1}{RC}$


R & C  
Vary independ-  
-ently

±20%      ±15%

3) R adds thermal noise

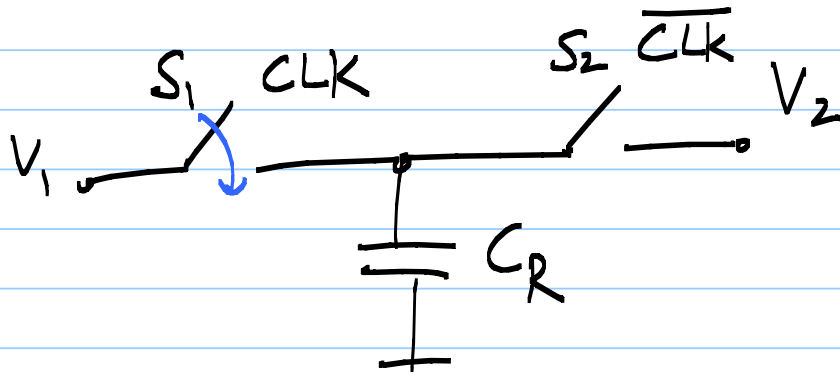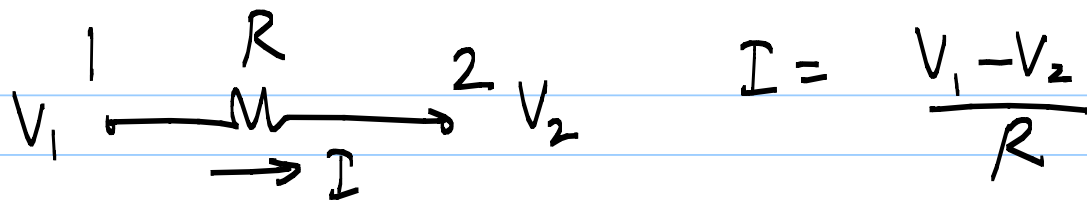


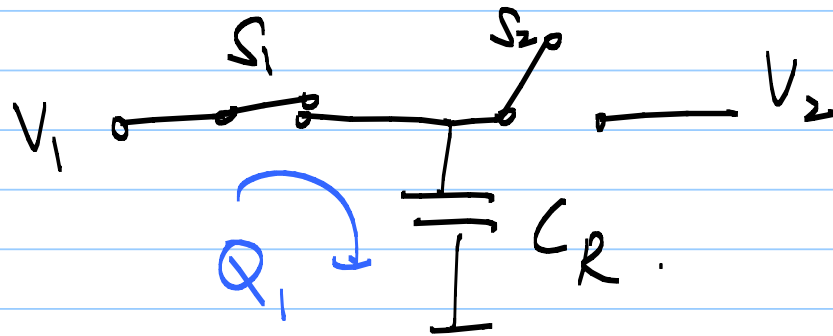phase 1 : CLK ON,  $S_1$  is ON  
 $S_2$  is OFF



$Q_1$  from  $V_1 = C_R \cdot V_1$

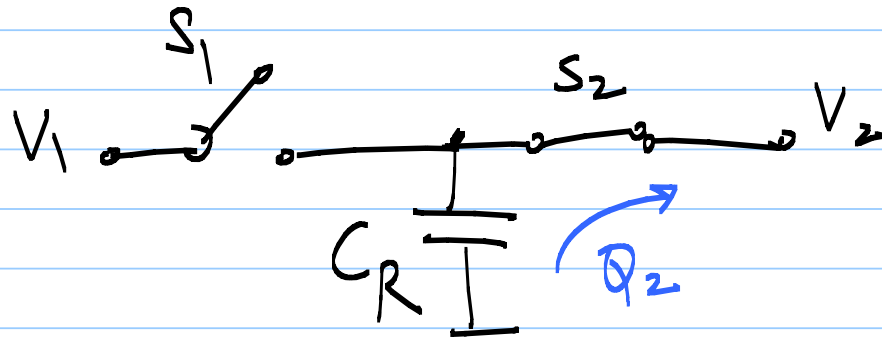phase 2 :  $\overline{\text{CLK}}$  ON,  $S_1$  OFF  
 $S_2$  ON



new charge on  $C_R = C_R \cdot V_2$

net charge moved from  $V_1$  to  $V_2$  :

$$= C_R (V_1 - V_2)$$

Done over a time period  $= T = \frac{1}{f_{\text{CLK}}}$

$$I_{\text{avg.}} = \frac{C_R (V_1 - V_2)}{T}$$


$$I_{avg} = f_{CLK} \cdot C_R (V_1 - V_2)$$

Compare with resistor



$$I_R = \frac{V_1 - V_2}{R}$$



Switched Cap. Res. =  $\frac{1}{f_{CLK} \cdot C_R}$

Discrete time  
integrator :

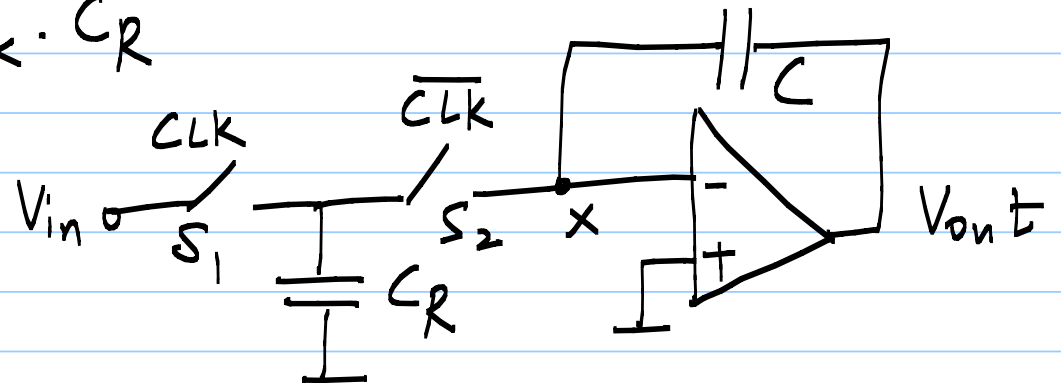

e.g. if  $V_{in}$  is constant:

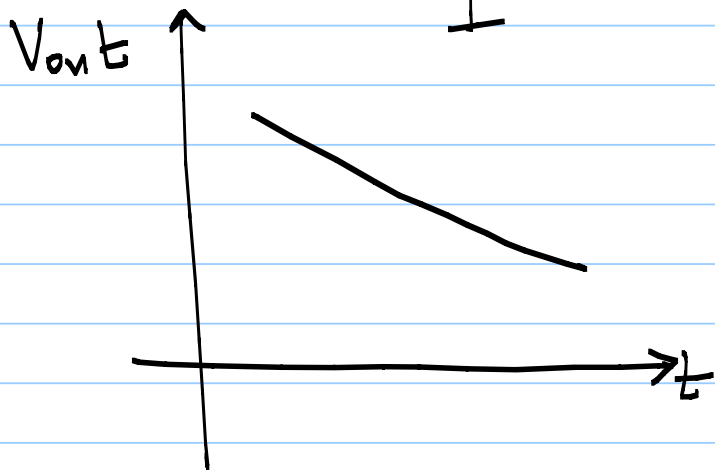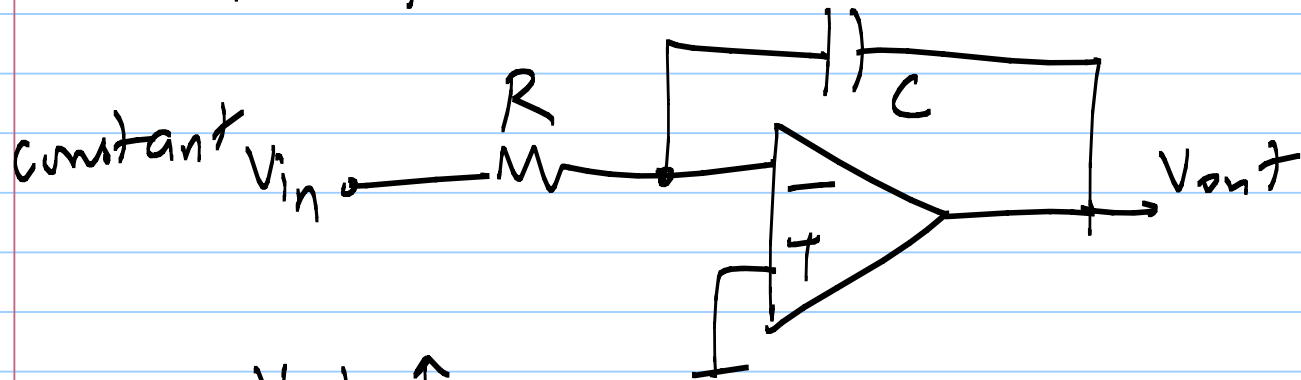

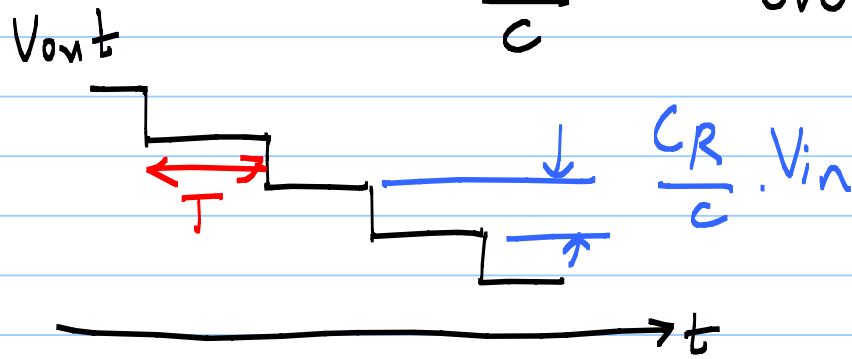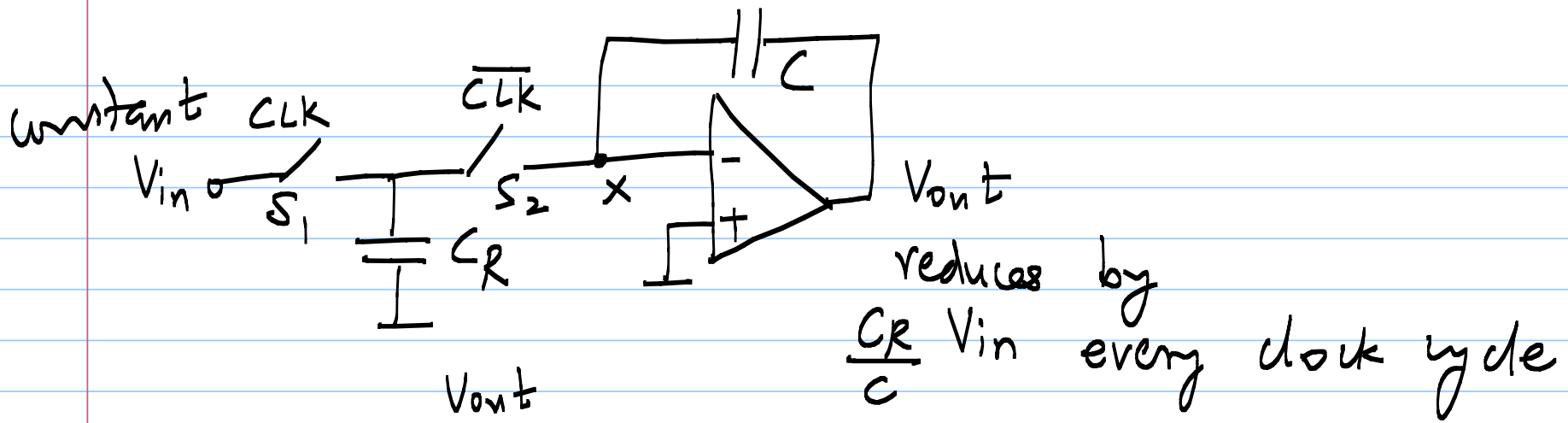

- \* gain of integrator  $\propto \frac{CR}{C}$
  - \* presents cap. input impedance
- ratio caps tracks very well across PVT





$$V_{out}(kT_{CLK}) = V_{out}((k-1)T_{CLK}) - V_{in}((k-1)T_{CLK}) \cdot \frac{CR}{C}$$

$\Rightarrow$  z-domain analysis

02/04/20

Lec 33

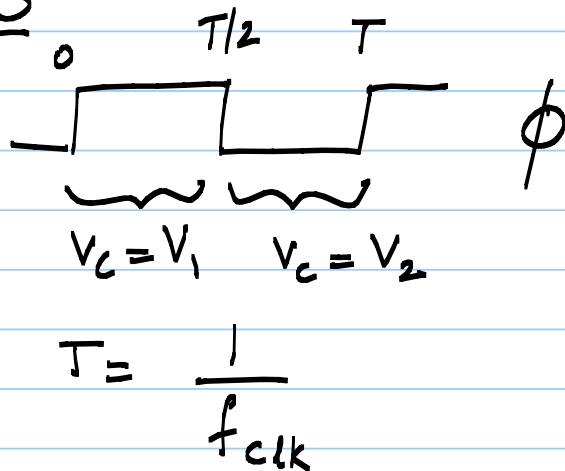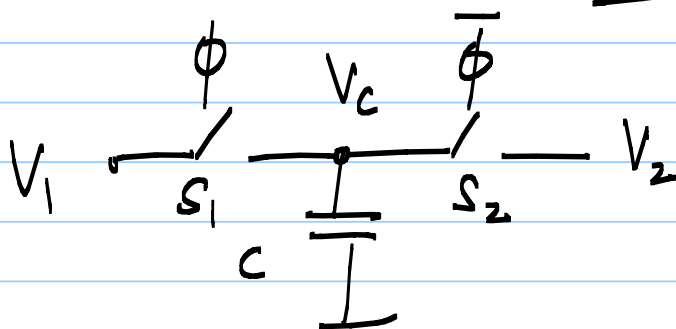

$\phi: t = 0 \text{ to } T/2$   
 $Q_c = CV_1$

$\bar{\phi}: t = T/2 \text{ to } T$   
 $Q_c = CV_2$

$\Delta Q_c = C(V_1 - V_2) =$  charge transferred from  $V_1$  to  $V_2$

$\Delta t = T - 0 = T$

$$I_{avg} = \frac{\Delta Q_c}{\Delta t} = \frac{C(V_1 - V_2)}{T}$$


$$\left\{ \text{CT current } I = \frac{dQ}{dt} \right\}$$



$$I_R = \frac{V_1 - V_2}{R} = I_{avg}'$$


$$I_{avg}' = I_{avg} \Rightarrow \frac{C(V_1 - V_2)}{T} = \frac{V_1 - V_2}{R}$$
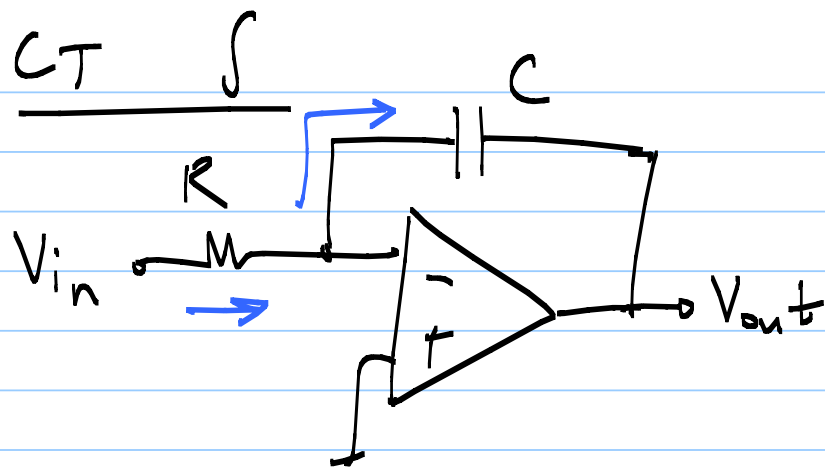
$$R = \frac{T}{C} = \frac{1}{C f_{clk}}$$



$$\frac{V_{in}}{R} = -V_{out} \cdot sC \Rightarrow \frac{V_{out}}{V_{in}} = \frac{-1}{sCR}$$

DT S

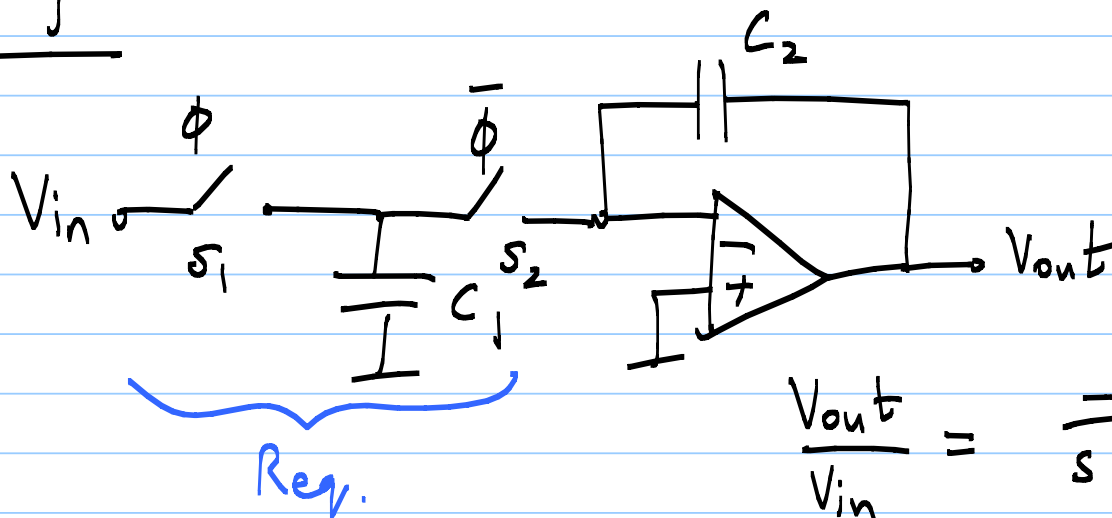

$$\frac{V_{out}}{V_{in}} = \frac{-1}{sC_2 R_{eq.}} = \frac{-C_1 f_{clk}}{sC_2}$$

ratio of caps  
very tightly controlled across PVT

1)  $\phi: 0 \leq t \leq T/2$


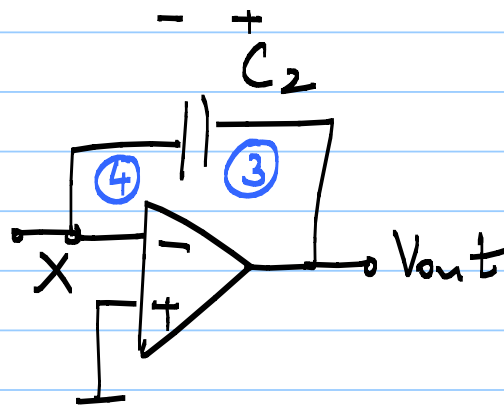
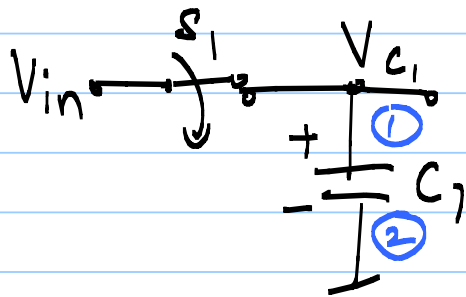


plate (1) of  $C_1$ :  $q_1 = C_1 \cdot V_{in}(T/2)$

plate (3) of  $C_2$ :  $q_2 = C_2 \cdot V_{out}(T/2) = C_2 V_{out}(0)$

{ No charge transferred from  $V_{in}$  so far }

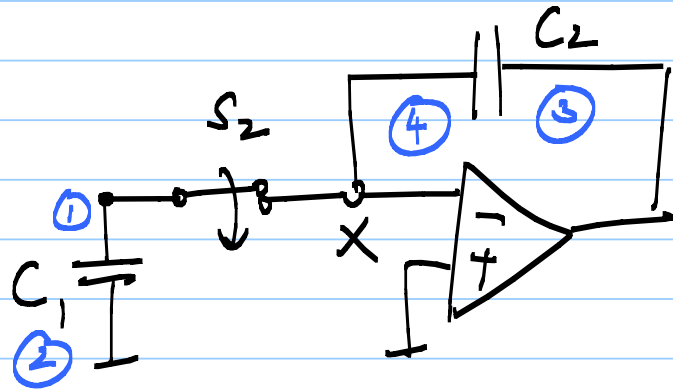2)  $\bar{\phi} : T/2 \leq t \leq T \quad V_x \approx 0$



Total charge on plates  
① & ④ is conserved

$$C_1 V_{in}(T/2) - C_2 V_{out}(0) = 0 - C_2 V_{out}(T)$$

$\swarrow$  plate ④ is -ve plate of  $C_2$

$$V_{out}(T) = V_{out}(0) - \frac{C_1}{C_2} V_{in}(T/2)$$

$\parallel$   $\parallel$   $\parallel$   
 $V_{out}(3T/2) \quad V_{out}(T/2) \quad V_{in}(0)$

(or)  $V_{out}(3T/2) = V_{out}(T/2) - \frac{C_1}{C_2} V_{in}(T/2)$

In general, we can write

$$V_{out}(nT) = V_{out}((n-1)T) - \frac{C_1}{C_2} V_{in}((n-1)T)$$

In z-domain:

$$V_{out}(z) = z^{-1} \cdot V_{out}(z) - \frac{C_1}{C_2} \cdot z^{-1} \cdot V_{in}(z)$$

where  $z = e^{j\omega_d T}$  ;  $T = \frac{1}{f_{clk}}$

$\omega_d = DT$  freq.

$$\frac{V_{out}}{V_{in}}(z) = -\frac{C_1}{C_2} \cdot \frac{z^{-1}}{1-z^{-1}} = -\frac{C_1}{C_2} \cdot \frac{1}{z-1}$$

$$= -\frac{C_1}{C_2} \cdot \frac{1}{e^{j\omega_d T} - 1}$$

$$e^{j\omega_d T} = 1 + j\omega_d T + \frac{(j\omega_d T)^2}{2!} + \dots$$

$$\frac{V_{out}}{V_{in}}(z) = -\frac{C_1}{C_2} \cdot \frac{1}{j\omega_d T + \frac{(j\omega_d T)^2}{2!} + \dots}$$

If  $\omega_d T$  is very small,

$$\begin{aligned} \frac{V_{out}}{V_{in}}(z) &\approx -\frac{C_1}{C_2} \cdot \frac{1}{j\omega_d T} \\ &= -\frac{C_1}{T} \cdot \frac{1}{C_2} \cdot \frac{1}{j\omega_d} \\ &= \frac{1}{\text{Rev}} \end{aligned}$$



$$\frac{V_{out}}{V_{in}}(z) \approx \frac{-1}{j\omega_d \cdot R_{eq} C_2}$$

In general,

$$H(s) \rightarrow H(z)$$

Non linear transformation: complex s-plane

forward :  $s = \frac{2}{T} \frac{z-1}{z+1}$  mapped to  
complex z-plane

reverse :  $z = \frac{2 + sT}{2 - sT}$

$$H(s) = \frac{-1}{sRC} \quad \left\{ H(j\omega) = \frac{-1}{j\omega RC} \right\}$$

We want

$$H_d(j\omega_d) = H(s)$$

$$= H \left[ \frac{2}{T} \cdot \frac{z-1}{z+1} \right]$$

$$= H \left[ \frac{2}{T} \frac{e^{j\omega_d T} - 1}{e^{j\omega_d T} + 1} \right]$$

$$= H \left[ j \cdot \frac{2}{T} \frac{(e^{j\omega_d T/2} - e^{-j\omega_d T/2})/2j}{(e^{j\omega_d T/2} + e^{-j\omega_d T/2})/2} \right]$$

$$= H \left[ j \cdot \frac{2}{T} \cdot \tan \left( \frac{\omega_d T}{2} \right) \right]$$

$$\text{We want } H\left(j \cdot \frac{2}{T} \cdot \tan\left(\frac{\omega_d T}{2}\right)\right) = H(j\omega)$$

$$\text{i.e. DT } H_d(j\omega_d) = \text{CT } H(j\omega)$$



$$\text{If } \frac{\omega_d T}{2} \ll 1 \Rightarrow \tan\left(\frac{\omega_d T}{2}\right) \approx \frac{\omega_d T}{2}$$

$$H\left(j \cdot \frac{2}{T} \tan\left(\frac{\omega_d T}{2}\right)\right) \approx H\left(j \cdot \frac{2}{T} \cdot \frac{\omega_d T}{2}\right) \\ = H(j\omega_d) = H(j\omega)$$


$$\boxed{\omega_d T \ll T}$$

# High Speed Amplifiers

1) CSA

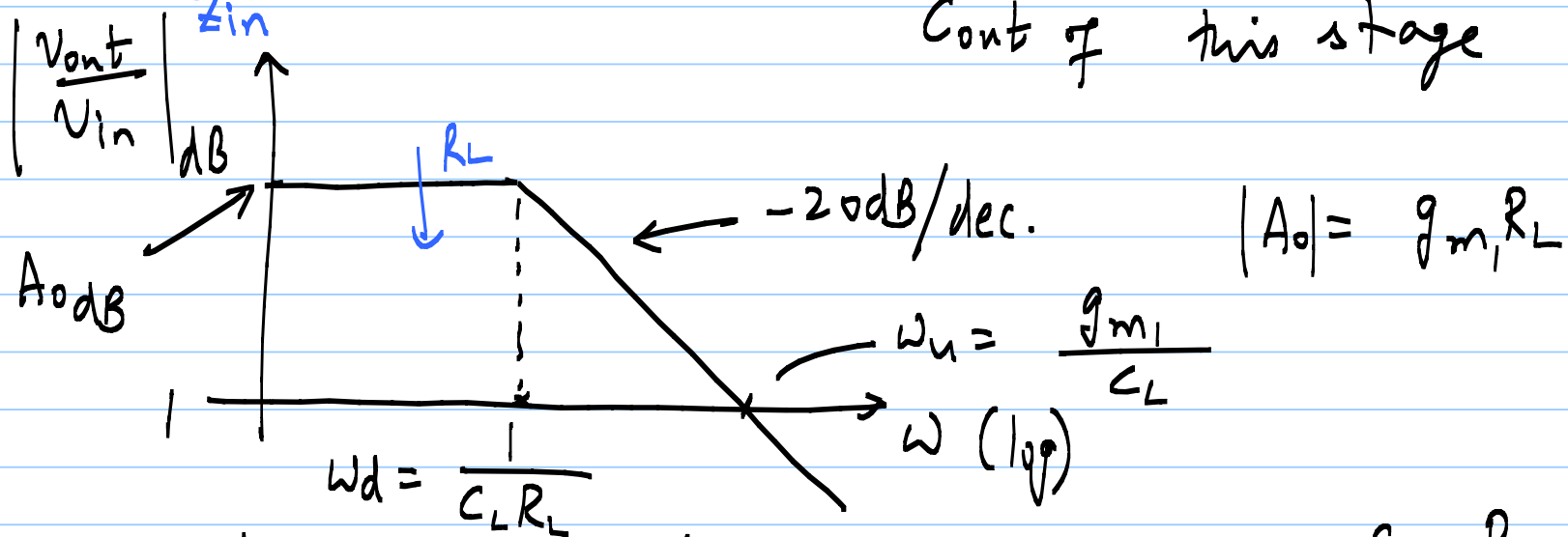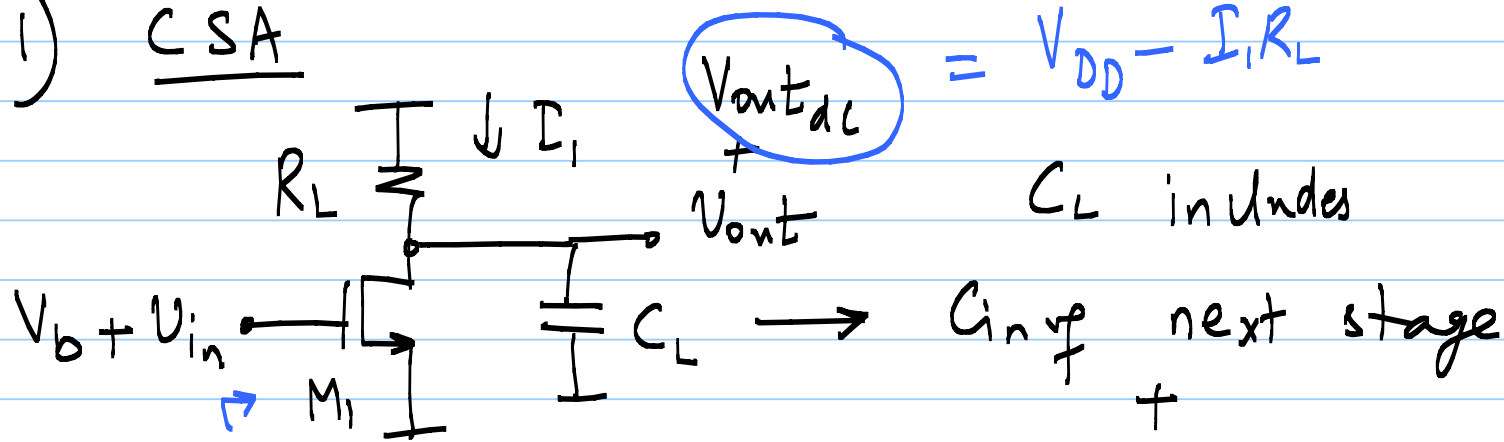
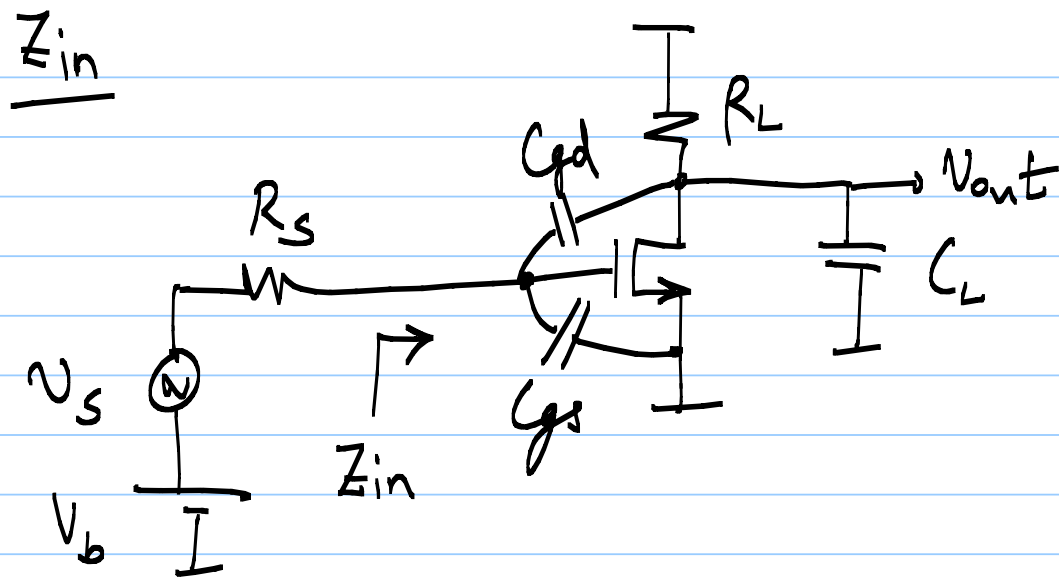
$$\frac{V_{out}}{V_{in}} = -g_{m1} \left( R_L \parallel \frac{1}{j\omega C_L} \right) = \frac{-g_{m1} R_L}{1 + j\omega C_L R_L}$$



$$\text{gain} = -A = -g_m R_L$$

$L \sim L_{\min}$  for high speed

$C_{gd}$  is significant compared to  $C_{gs}$

e.g. in deep submicron processes,

@  $L_{\min}$ ,  $C_{gd} \approx 50\%$  of  $C_{gs}$


$$Z_{in} \approx \frac{1}{s(C_{gs} + C_{gd}(1+A))} = \frac{1}{sC_{gs} \left[ 1 + \frac{C_{gd}}{C_{gs}}(1+g_m R_L) \right]}$$

e.g.  $g_m R_L = 3$

$$Z_{in} \approx \frac{1}{sC_{gs}(1 + 0.5(4))} = \frac{1}{3sC_{gs}}$$

input cap has almost tripled

2) Add a cascode device (Cascode CSA)

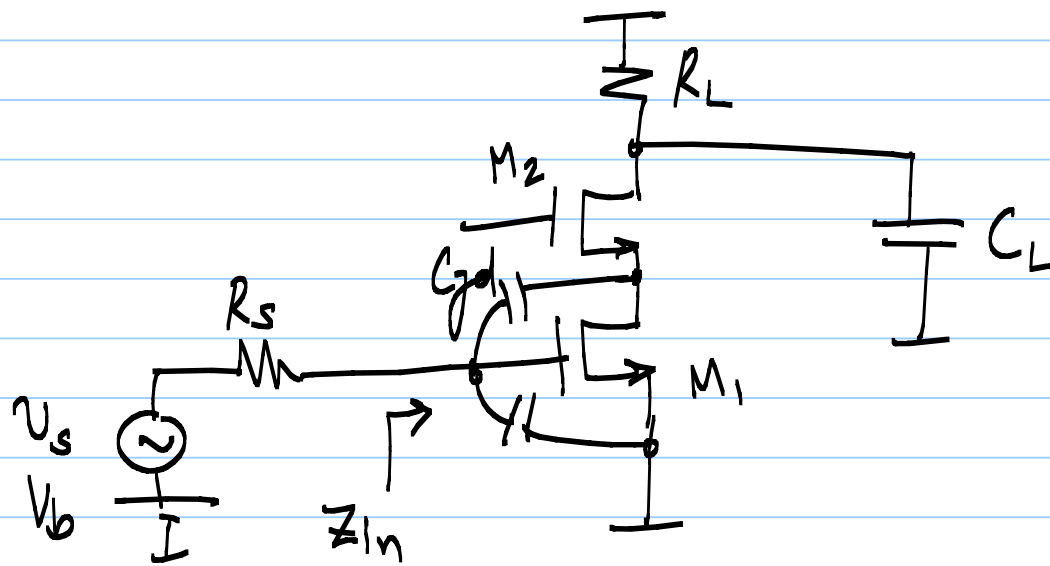

$M_2 = M_1$   
 gain from gate of  $M_1$  to drain of  $M_1$   
 $= -\frac{g_{m1}}{g_{m2}} \approx -1$

$$Z_{in} \approx \frac{1}{sC_{gs} [1 + 0.5(2)]} \approx \frac{1}{2sC_{gs}}$$

←  $C_{in}$  has reduced by about 30%.


Issue: Reduced swing at  $V_{out}$

### 3) Source coupled amplifier

\* Miller effect  $\rightarrow$  sending signal through Drain of  $M_1$

\* Avoid drain node

\* Send signal through source node

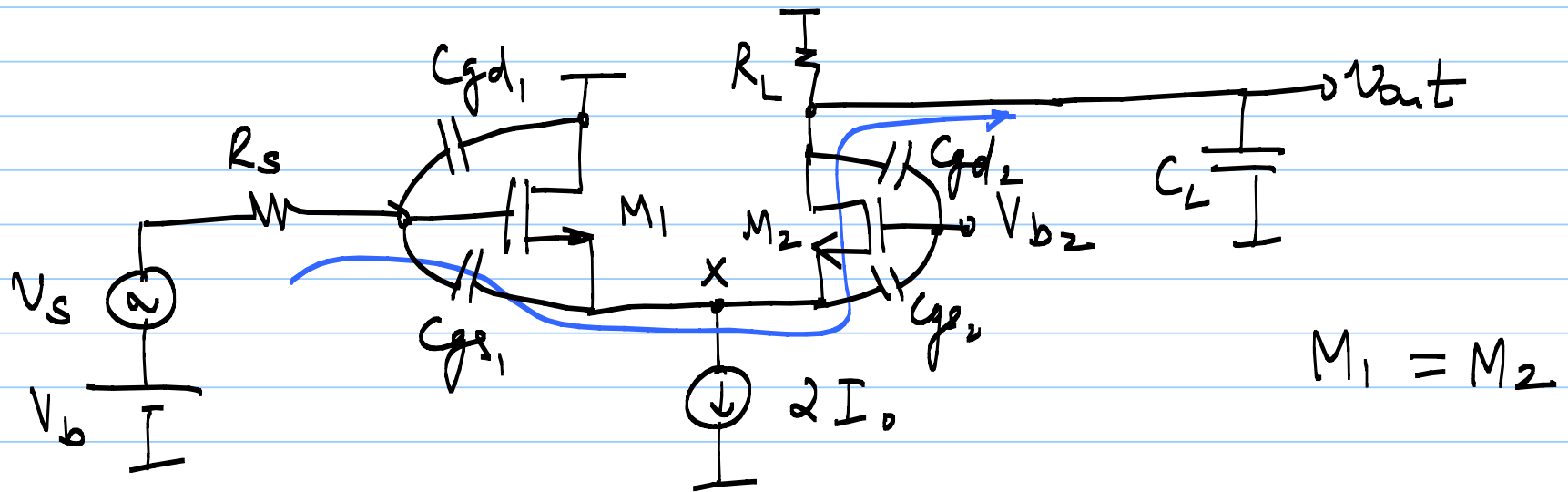

\*  $C_{gd1}$  — is not Miller  
multiplied

\* effect of  $C_{gs1}$  is halved

—  $C_{gs1}$  in series with  $C_{gs2}$

$$* Z_{in} \approx \frac{1}{s(C_{gd} + \frac{C_{gs1}}{2})} = \frac{1}{sC_{gs} \left(0.5 + \frac{C_{gd}}{C_{gs}}\right)}$$


$$Z_{in} \approx \frac{1}{sC_{gs}}$$

\* Issues : 1) parasitic cap @ node x is high  
2) power consumed is now  $2x$



3/4/20

Lec 34

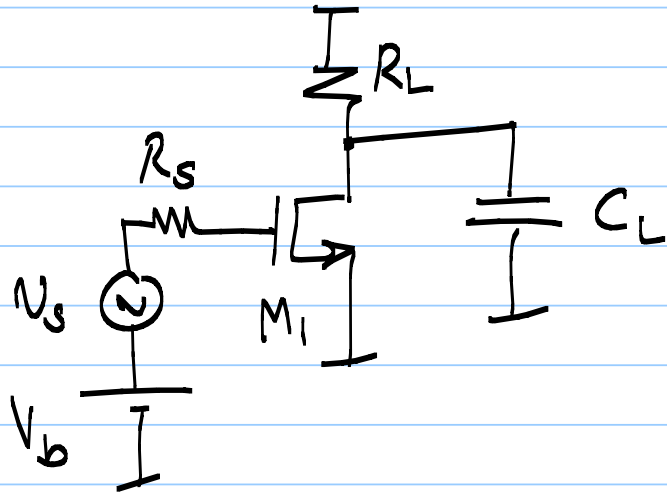


DC gain

$$A_o = -g_m R_L$$

$$\omega_{3dB} = \frac{1}{R_L C_L}$$

$$\omega_u = \frac{g_m}{C_L}$$

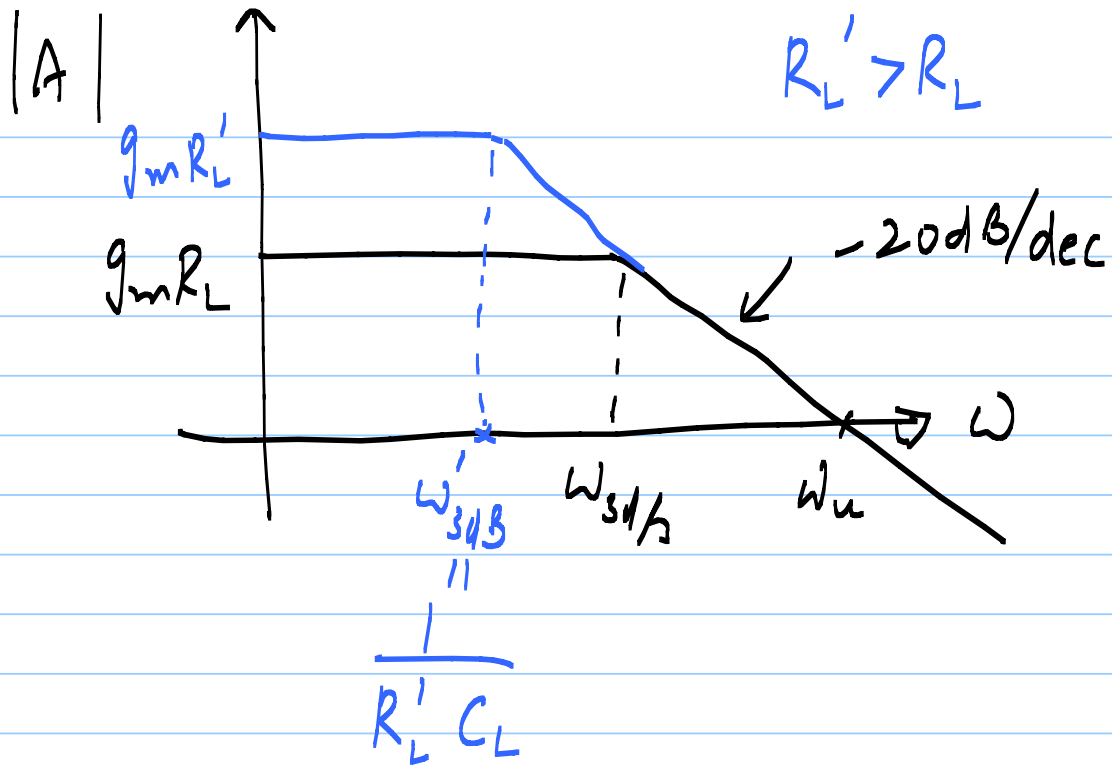

We want to increase  $\omega_u = \frac{g_m}{C_L}$

eg. load this amplifier with another identical amplifier


$$C_L \propto W$$

$$g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)$$

$$\omega_u = \frac{g_m}{C_L} \propto \frac{(V_{GS} - V_T)}{L}$$

\* to maximize  $\omega_u$   $\left\{ \begin{array}{l} \rightarrow L = L_{min} \\ \rightarrow \text{bias } M. @ \text{ max } (V_{GS} - V_T) \end{array} \right.$

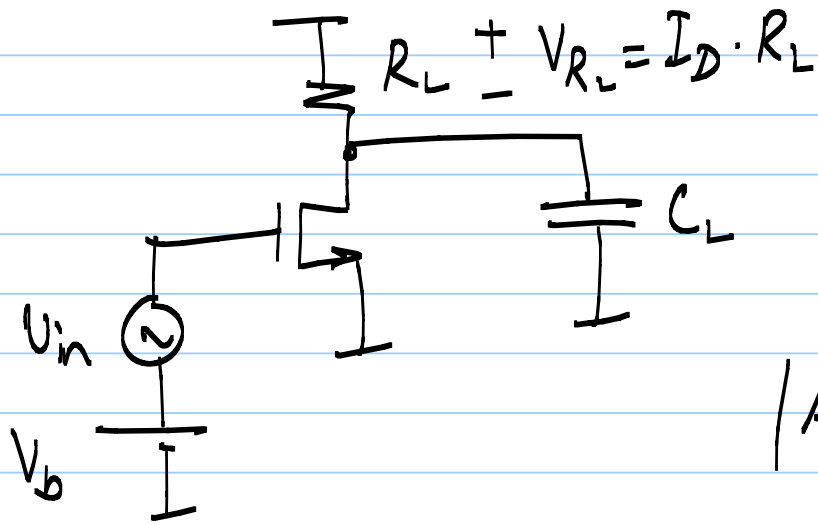\* In velocity saturation:  $\uparrow V_{GS} - V_T$  does not  $\uparrow g_m$



$$g_m = \frac{2I_D}{V_{GS} - V_T}$$


$$|A| = g_m R_L = \frac{2I_D}{V_{GS} - V_T} \cdot R_L$$

$$= \frac{2V_{R_L}}{V_{GS} - V_T}$$


$$\max A \approx \frac{2V_{DD}}{V_{GS} - V_T}$$

high  $\omega_u \rightarrow$  large  $V_{GS} - V_T \rightarrow$  small  $A_{\max}$

#### 4) Neutralisation

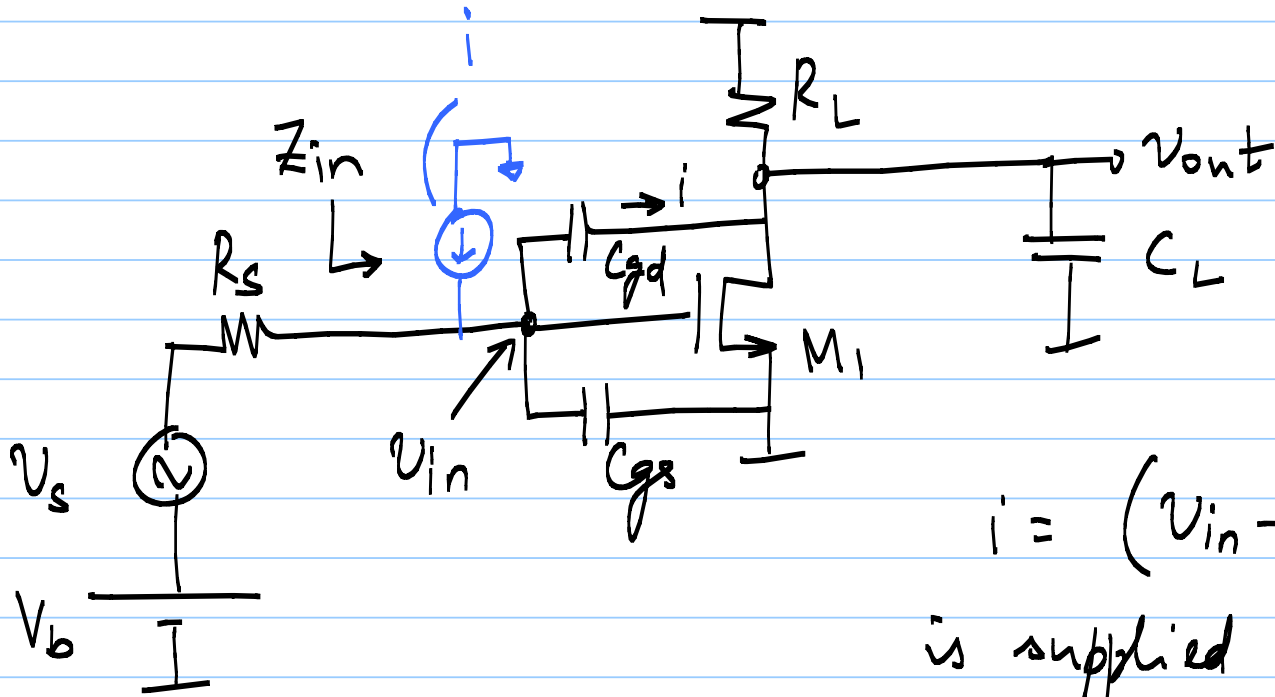
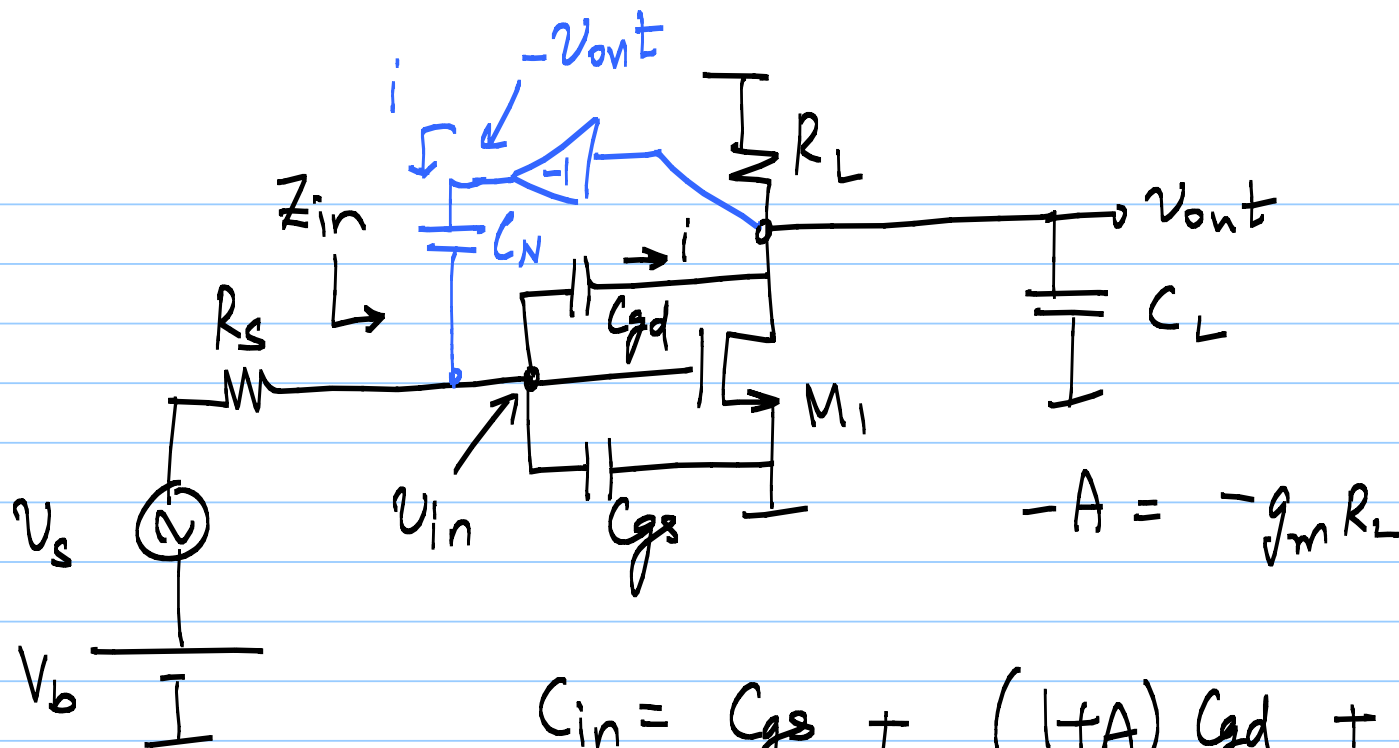
$$i = (v_{in} - v_{out}) s C_{gd}$$
  
is supplied by  $v_s$   
for the original amplifier



$$i = (v_{in} - v_{out}) s C_{gd}$$

$$C_{in} = C_{gs} + (1+A) C_{gd} + (1-A) C_N$$

\* Choose  $C_N = C_{gd}$

$$C_{in} \approx C_{gs} + (1+A) C_{gd} + (1-A) C_{gd}$$

$$= C_{gs} + 2 C_{gd} \quad \left\{ \begin{array}{l} \text{Same as that} \\ \text{for cascode} \end{array} \right.$$

$$* C_N < C_{gd}$$

↳ not fully neutralised

$$↳ C_{in} > C_{gs} + 2C_{gd}$$

$$* C_N > C_{gd}$$

$$C_{in} = C_{gs} + (1+A)C_{gd} + (1-A)C_N$$

$$= C_{gs} + (1+g_m R_L)C_{gd} + (1-g_m R_L)C_N$$




adds -ve cap

→ can reduce effect of  $C_{gs}$

\* If  $C_N$  becomes too large →  $C_{in}$  is -ve

↳ Can degrade stability


↳ Can present inductive input impedance

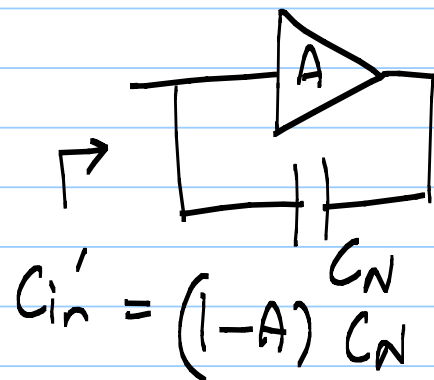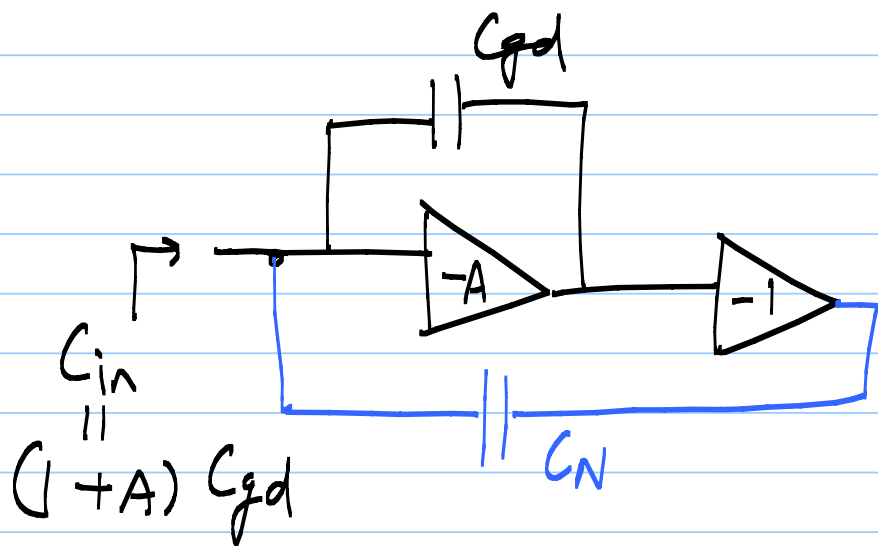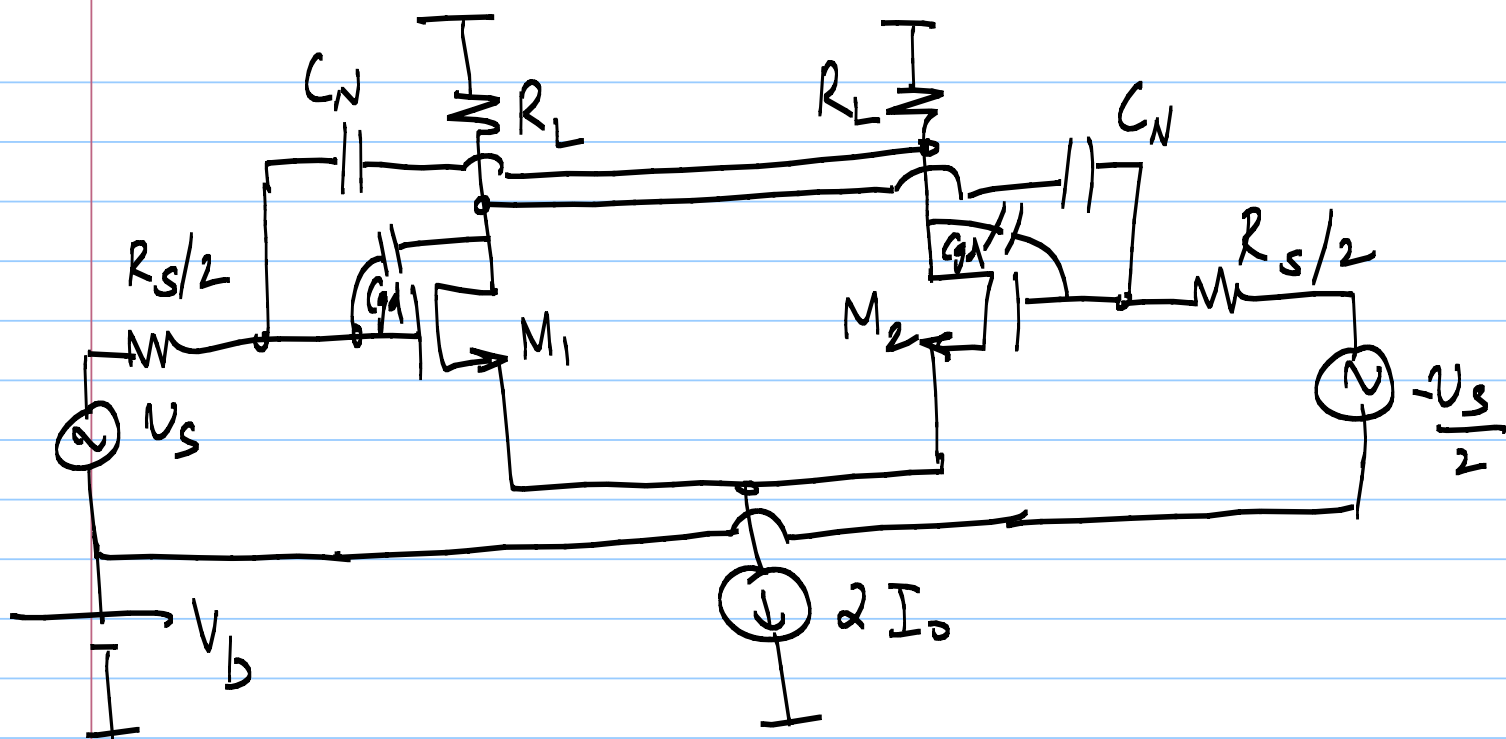


$$C_{in}' = (1-A) C_N$$



# Bandwidth Extension

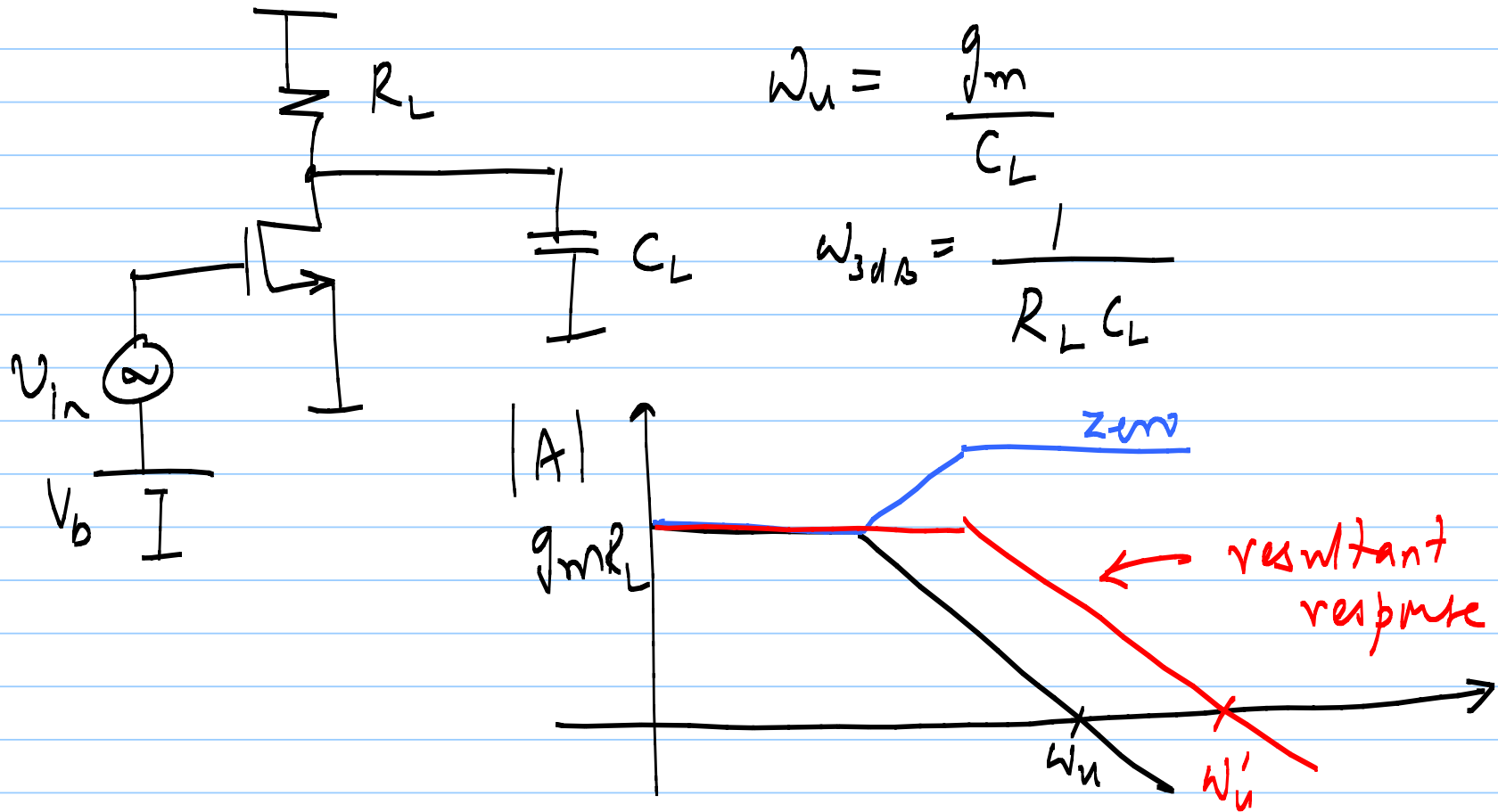

Use an inductor to add a zero

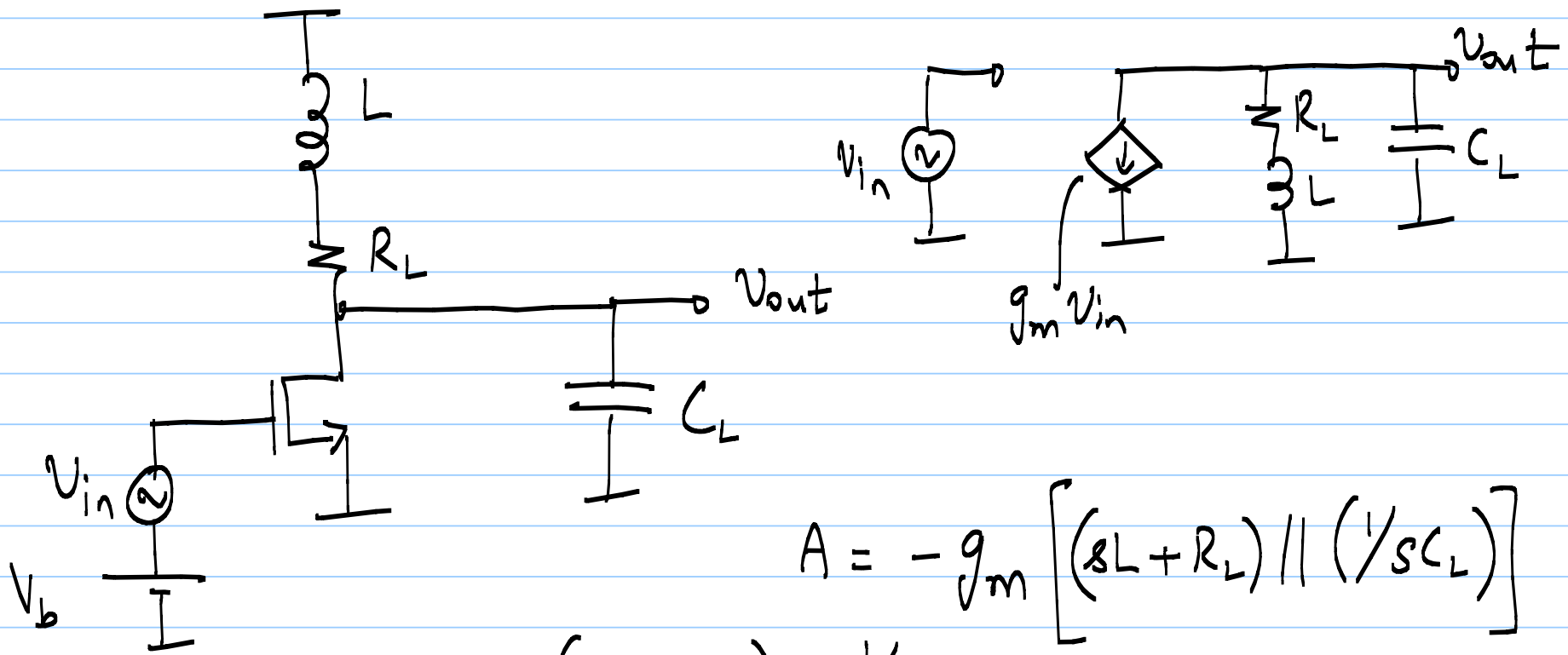

$$A = -g_m \frac{(sL + R_L) \cdot \frac{1}{sC_L}}{sL + R_L + \frac{1}{sC_L}}$$

$$= -g_m \frac{sL + R_L}{s^2 LC_L + sR_L C_L + 1}$$

$$A = -g_m \left[ (sL + R_L) \parallel \left( \frac{1}{sC_L} \right) \right]$$

$$A = -g_m R_L \frac{s \left( \frac{L}{R_L} \right) + 1}{s^2 L C_L + s R_L C_L + 1}$$

2 time constants:

$$\tau_0 = R_L C_L = \frac{1}{\omega_0} \quad ; \quad \tau_1 = \frac{L}{R_L}$$

$$\text{set } m = \frac{\tau_0}{\tau_1} = \frac{R_L C_L}{L/R_L} = \frac{R_L^2 C_L}{L}$$

$$A = -g_m R_L \frac{s \tau_1 + 1}{s^2 \cdot \tau_1^2 \cdot m}$$

$$\tau_1^2 = \frac{L^2}{R_L^2} \quad ; \quad \tau_1^2 \cdot m = \frac{L^2}{R_L^2} \cdot \frac{R_L^2 C_L}{L} = L C_L$$

replace  $\tau_1 = \tau_0/m = \frac{1}{m \omega_0}$  and set  $s = j\omega$

$$|A| = g_m R_L \cdot \left| \frac{j \frac{\omega}{m\omega_0} + 1}{-\left(\frac{\omega}{m\omega_0}\right)^2 \cdot m + j \left(\frac{\omega}{m\omega_0}\right) \cdot m + 1} \right|$$

Let new  $\omega_{3dB} = \omega_1$     { old  $\omega_{3dB} = \omega_0$  }

$$\left| \frac{j \frac{\omega_1}{m\omega_0} + 1}{-\left(\frac{\omega_1}{m\omega_0}\right)^2 \cdot m + j \frac{\omega_1}{\omega_0} + 1} \right| = \frac{1}{\sqrt{2}}$$

\* we want to find  $\frac{\omega_1}{\omega_0}$  and maximize it

set  $\alpha = \frac{\omega_1}{\omega_0} =$  "BW extension ratio"

$$\left| \frac{\sqrt{\frac{\alpha}{3}} + 1}{\sqrt{\alpha} + 1 - \left(\frac{\alpha}{3}\right)^2 \cdot 3} \right| = \frac{1}{\sqrt{2}}$$

$$\frac{1 + \frac{\alpha^2}{m^2}}{\alpha^2 + \left(1 - \frac{\alpha^2}{m}\right)^2} = \frac{1}{2}$$

$$2 + \frac{2\alpha^2}{m^2} = \alpha^2 + 1 + \frac{\alpha^4}{m^2} - \frac{2\alpha^2}{m}$$

$$\frac{\alpha^4}{m^2} + \alpha^2 \left(1 - \frac{2}{m} - \frac{2}{m^2}\right) - 1 = 0$$

$$x^4 + x^2(m^2 - 2m - 2) - m^2 = 0$$

$$x^2 = \frac{(2 + 2m - m^2) + \sqrt{(2 + 2m - m^2)^2 + 4m^2}}{2} \quad \begin{array}{l} \text{larger} \\ \text{root} \end{array}$$

$$= \left( -\frac{m^2}{2} + m + 1 \right) + \sqrt{\left( -\frac{m^2}{2} + m + 1 \right)^2 + m^2}$$


$$x = \frac{\omega_1}{\omega_0} = \sqrt{\left( -\frac{m^2}{2} + m + 1 \right) + \sqrt{\left( -\frac{m^2}{2} + m + 1 \right)^2 + m^2}}$$

\*  $m$  sets amount of  
BW extension


\*  $L = \frac{R_L^2 C_L}{m}$  is the  
desired inductor value

7/4/20

# Lec 35

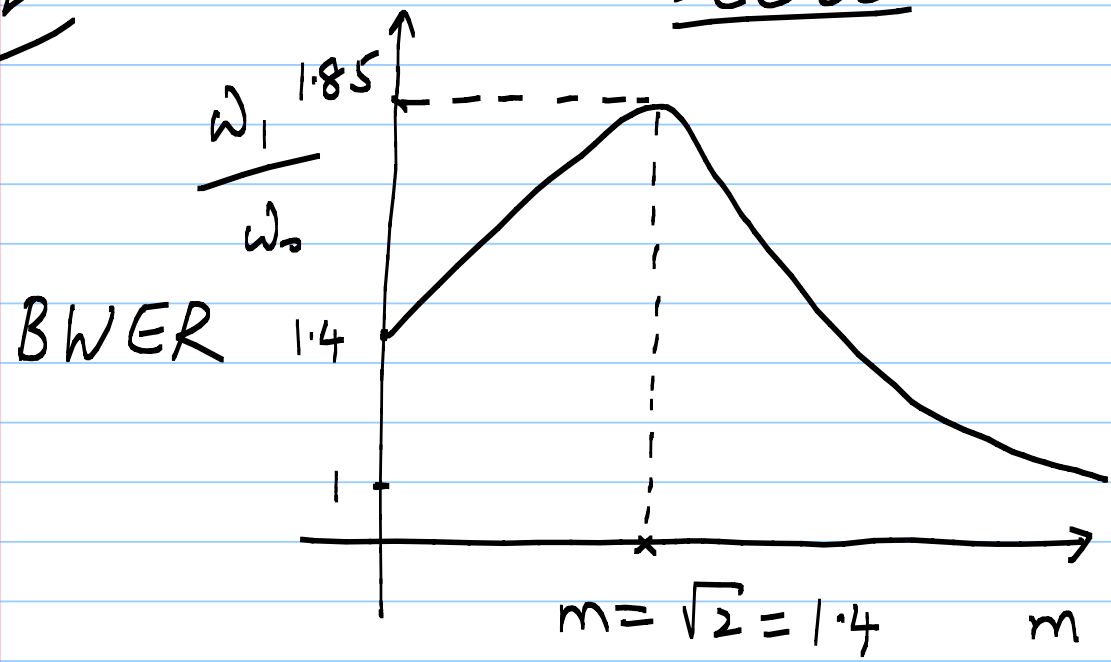

highest BWER = 1.85x  
@  $m = 1.41$

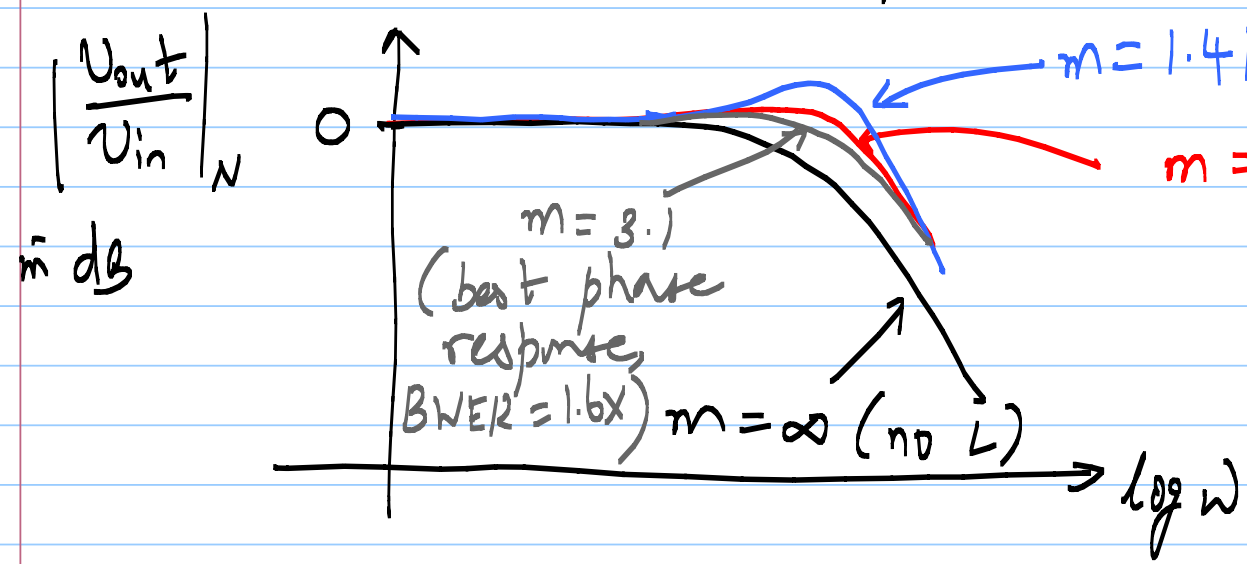


$m = 1.41$  (maximum BW, BWER = 1.85)  
 $m = 2.41$  (maximally flat, BWER = 1.72x)



$$T_D(\omega) = - \frac{d\phi(\omega)}{d\omega}$$

If delay is constant over as wide a BW  
as possible  $\rightarrow$  maximally flat time delay  
(best phase response)

## 2) Bridged Shunt Peaking

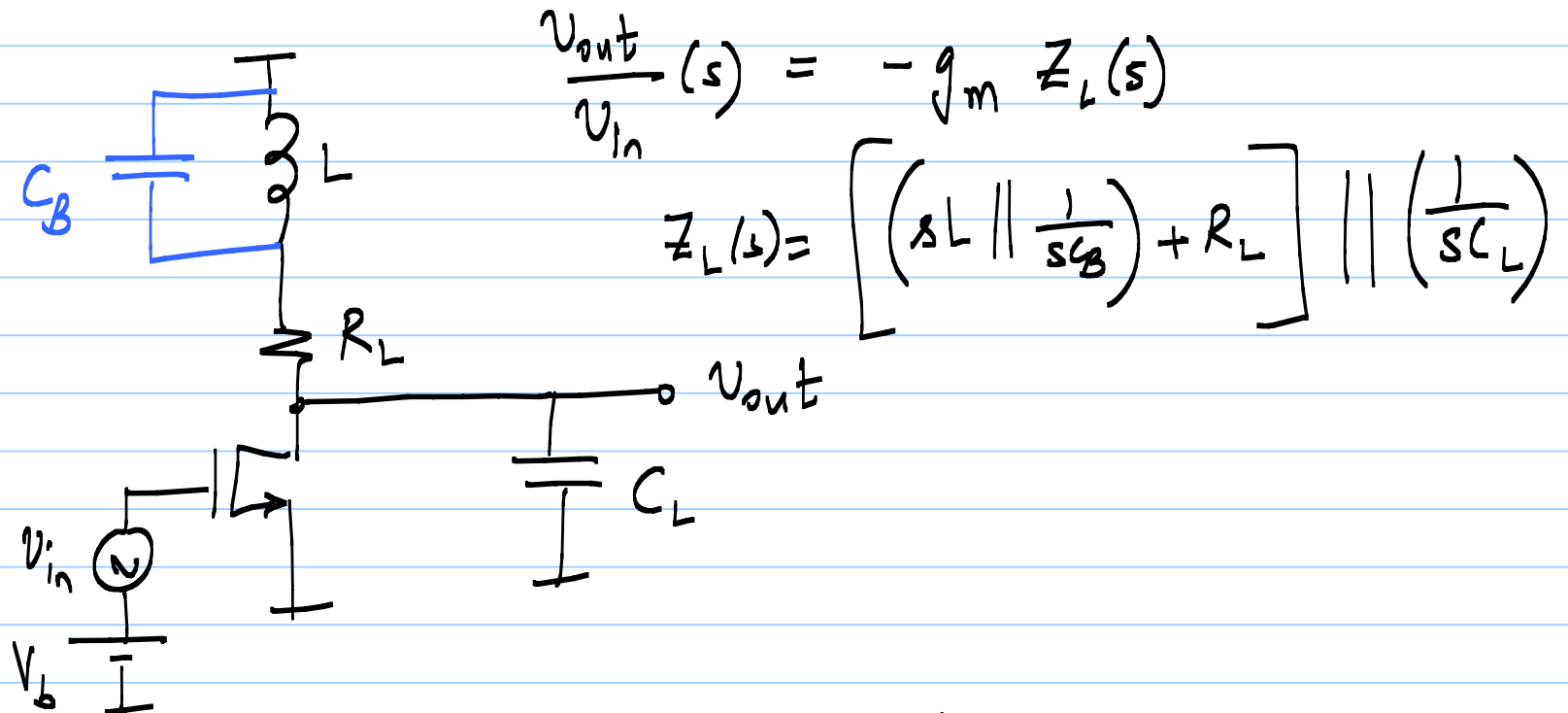

$$\frac{v_{out}}{v_{in}}(s) = -g_m Z_L(s)$$

$$Z_L(s) = \left[ \left( sL \parallel \frac{1}{sC_B} \right) + R_L \right] \parallel \left( \frac{1}{sC_L} \right)$$

$$Z_L(s) = \left[ R_L + \left( \frac{sL \cdot \frac{1}{sC_B}}{sL + \frac{1}{sC_B}} \right) \right] \parallel \left( \frac{1}{sC_L} \right)$$

$$Z_L(s) = \left[ R_L + \left( \frac{sL}{1+s^2LC_B} \right) \right] \parallel \frac{1}{sC_L}$$

$$= \left[ \frac{R_L + sL + s^2LC_B R_L}{1+s^2LC_B} \right] \parallel \left( \frac{1}{sC_L} \right)$$

$$= \frac{(R_L + sL + s^2LC_B R_L)}{1+s^2LC_B} \times \frac{1}{sC_L}$$

$$\frac{R_L + sL + s^2LC_B R_L}{1+s^2LC_B} + \frac{1}{sC_L}$$

$$Z_L(s) = \frac{R_L + sL + s^2 L C_B R_L}{1 + s C_L R_L + s^2 (L C_L + L C_B) + s^3 L C_B C_L R_L}$$

← 2 zeroes

Parameterize:

$$m = \frac{R_L^2 C_L}{L} ; \quad \omega_0 = \frac{1}{R_L C_L} ; \quad k_B = \frac{C_B}{C_L}$$

$$Z_L(s) = R_L \frac{1 + \frac{sL}{R_L} + s^2 L C_B}{1 + s C_L R_L + s^2 L (C_L + C_B) + s^3 L C_B C_L R_L}$$

$$\frac{L}{R_L} = \frac{1}{R_L/L} = \frac{1}{\frac{R_L^2 C_L}{L} * \frac{1}{R_L C_L}} = \frac{1}{m \omega_0}$$

$$L C_B = \frac{1}{1/(L C_B)} = \frac{1}{\frac{R_L^2 C_L}{L} * \frac{1}{R_L^2 C_L C_B}}$$

$$= \frac{1}{m \cdot \frac{1}{R_L^2 C_L^2} \cdot \frac{C_L}{C_B}} = \frac{1}{m \cdot \omega_0^2 \cdot \frac{1}{k_B}}$$

$$= \frac{k_B}{m \omega_0^2}$$

$$L(C_L + C_B) = \frac{1}{\frac{1}{L(C_L + C_B)}} = \frac{1}{\frac{R_L^2 C_L}{L} \cdot \frac{1}{R_L^2 C_L} \cdot \frac{1}{(C_L + C_B)}}$$

$$= \frac{1}{m \cdot \frac{1}{R_L^2 C_L^2} \cdot \frac{1}{(1 + C_B/C_L)}} = \frac{k_B + 1}{m \omega_0^2}$$

$$L C_b C_L \cdot R_L = L \cdot \frac{C_b}{C_L} \cdot R_L C_L^2 = L \cdot k_B \cdot \frac{1}{R_L} \cdot (C_L^2 R_L^2)$$

$$= \frac{k_B}{\omega_0^2} \cdot \frac{L}{R_L} = \frac{k_B}{\omega_0^2} \cdot \frac{1}{m \omega_0} = \frac{k_B}{m \omega_0^3}$$

$$\frac{U_{out}}{U_{in}}(s) = -g_m R_L \cdot \underbrace{Z_N(s)}_{\text{normalized impedance}}$$

$$Z_N(s) = \frac{1 + \left(\frac{1}{m}\right) \frac{s}{\omega_0} + \left(\frac{k_B}{m}\right) \frac{s^2}{\omega_0^2}}{1 + \frac{s}{\omega_0} + \left(\frac{k_B + 1}{m}\right) \frac{s^2}{\omega_0^2} + \left(\frac{k_B}{m}\right) \frac{s^3}{\omega_0^3}}$$

$$m = \frac{R_L^2 \cdot C_L}{L}$$

$$k_B = 0, m = \infty \Rightarrow \text{BWER} = 1X$$

$$k_B = 0, m = 1.41 \Rightarrow 1.83X, 1.5 \text{ dB peaking}$$

$$k_B = 0.3, m = 2.4 \Rightarrow 1.83X, \text{ maximally flat}$$

\* as  $k_B \uparrow$  ( $C_L \uparrow$ ), change  $m$  to keep BWER  
at  $1.83X \Rightarrow$  amount of peaking reduces

e.g. final BW =  $1.5 \text{ GHz} = f_1$

phase modulation  $\rightarrow$  best group delay case

$$\Rightarrow m = 3.1$$

say  $C_L = 1.5 \text{ pF}$ ;  $\min R_L = 10 \Omega$   
(limited by power  
consumption)

original BW  $f_0 = \frac{1}{2\pi R_L C_L} = 1.06 \text{ GHz}$


$m = 3.1 \Rightarrow L = \frac{R_L^2 C_L}{3.1} = 4.8 \text{ nH}$

$f_1 = 1.6 f_0 = 1.7 \text{ GHz}$

$Q = \frac{\omega_0 L}{R_L} = 0.5 @ 1.7 \text{ GHz}$  much lower than  $Q$   
of inductor itself



3) Create zero without L

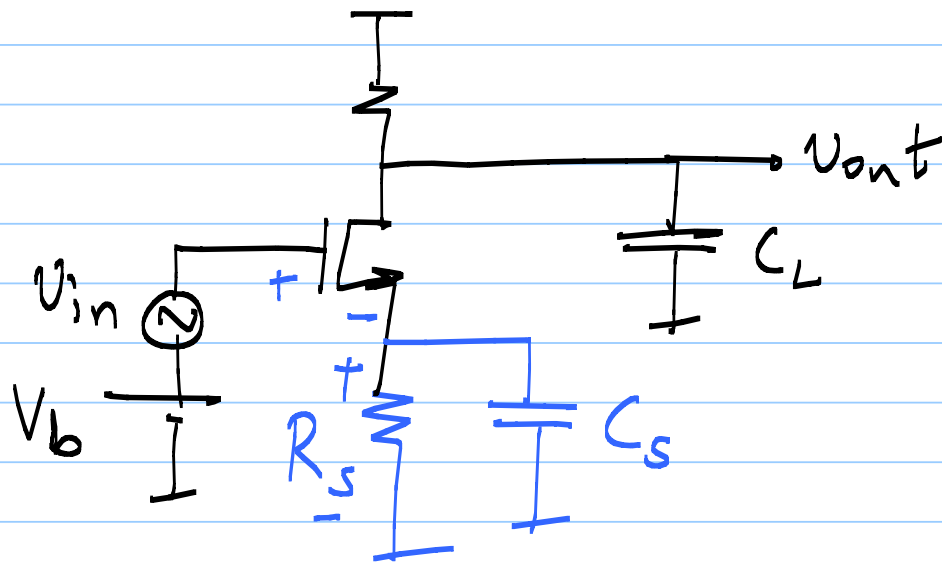

Zero  $\rightarrow$  low gain @  
low freq.,  
high gain @  
higher freq.

$$\text{gain @ low freq.} = \frac{g_m R_L}{1 + g_m R_s}$$

$$Z_L = R_L \parallel \frac{1}{sC_L} \quad ; \quad Z_s = R_s \parallel \frac{1}{sC_s}$$


$$\frac{V_{out}}{V_{in}}(s) = - \frac{g_m Z_L}{1 + g_m Z_s + sC_{gs} Z_s}$$

$$I_f \quad \omega \ll \omega_T \quad \Rightarrow \quad g_m \rightarrow sC_g$$

$$\frac{V_{out}}{V_{in}}(s) \approx -g_m R_L \frac{1 + sR_s C_s}{(1 + sR_L C_L)(1 + sR_s C_s + g_m R_s)}$$

$$Z_{env} @ \frac{1}{R_s C_s}$$
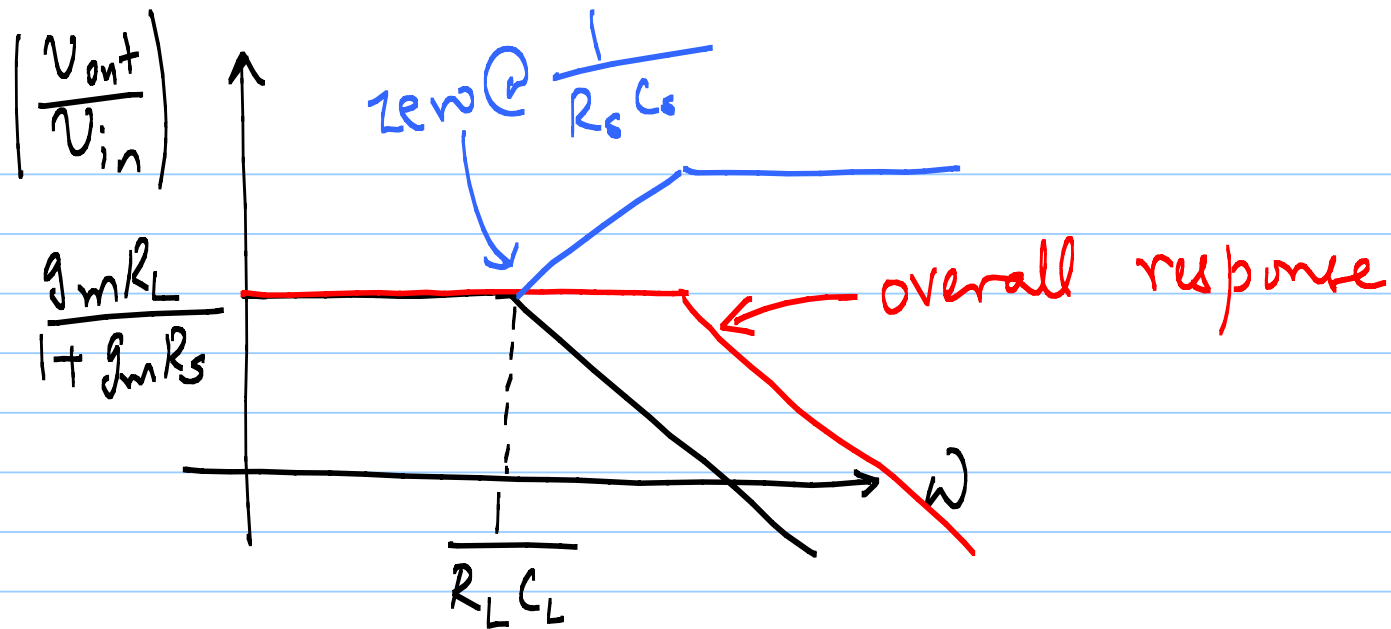
$$2^{nd} \text{ pole } @ \frac{1 + g_m R_s}{R_s C_s}$$



\* Cancel pole @  $\frac{1}{R_L C_L}$  by zero @  $\frac{1}{R_s C_s}$

$$\Rightarrow \boxed{R_s C_s = R_L C_L}$$

$$\frac{V_{out}}{V_{in}} = - \frac{g_m R_L}{1 + s R_s C_s + g_m R_s}$$

$$\text{new BW} = \frac{1 + g_m R_s}{R_s C_s} = \frac{1 + g_m R_s}{R_L C_L}$$

$$\text{dc } A_o = \frac{g_m R_L}{1 + g_m R_s}$$

But : If we had designed original CSA  
for same DC gain


Choose  $R_L' = \frac{R_L}{1 + g_m R_s}$

$$\text{BW} = \omega_2 = \frac{1}{R_L' C_L} = \frac{1 + g_m R_s}{R_L C_L} = \text{same as zero-peaked amplifier}$$

9/4/20

Lec 36

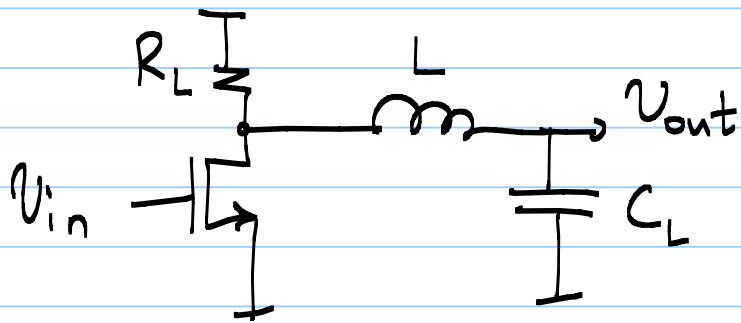4) Series peaking (neglect drain parasitics)



$$\frac{V_{out}(s)}{V_{in}}(s) = -g_m R_L \cdot Z_N(s)$$

$$\omega_0 = \frac{1}{R_L C_L} ; m = \frac{R_L^2 C_L}{L}$$

$$Z_N(s) = \frac{1}{1 + \frac{s}{\omega_0} + \frac{s^2}{m\omega_0^2}}$$


\* inferior to shunt  
peaking due to  
lack of zero

\* maximum BWFR = 1.41X @ m=2

## 5) Series peaking with cap. load splitting

\*  $C_L =$  drain parasitic + input cap of next stage

$$C_L = C_1 + C_2$$

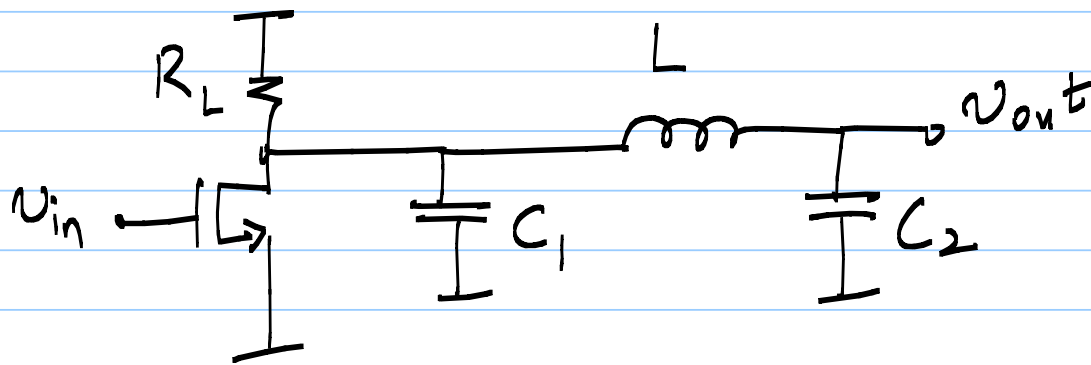

$$\omega_0 = \frac{1}{R_L C_L}$$

$$m = \frac{R_L^2 C_L}{L}$$

$$K_c = \frac{C_1}{C_2}$$

\* no zeroes

\* 3<sup>rd</sup> order system

$$Z_N(s) = \frac{1}{1 + \frac{s}{\omega_0} + \left(\frac{1-k_c}{m}\right) \frac{s^2}{\omega_0^2} + \left[\frac{k_c(1-k_c)}{m}\right] \frac{s^3}{\omega_0^3}}$$

$$k_c = 0, m = 2 \Rightarrow \text{BWER} = 1.41x$$

$$k_c = 0.3, m = 2.4 \Rightarrow \text{BWER} = 2.52x, \text{ no peaking}$$

$$k_c = 0.4, m = 1.9 \Rightarrow \text{BWER} = 2.75x, \text{ 1 dB peaking}$$


$$k_c = 0.4, m = 2.5 \Rightarrow \text{BWER} = 3.17x, \text{ 3 dB peaking}$$

Can you combine shunt & series peaking?

Yes
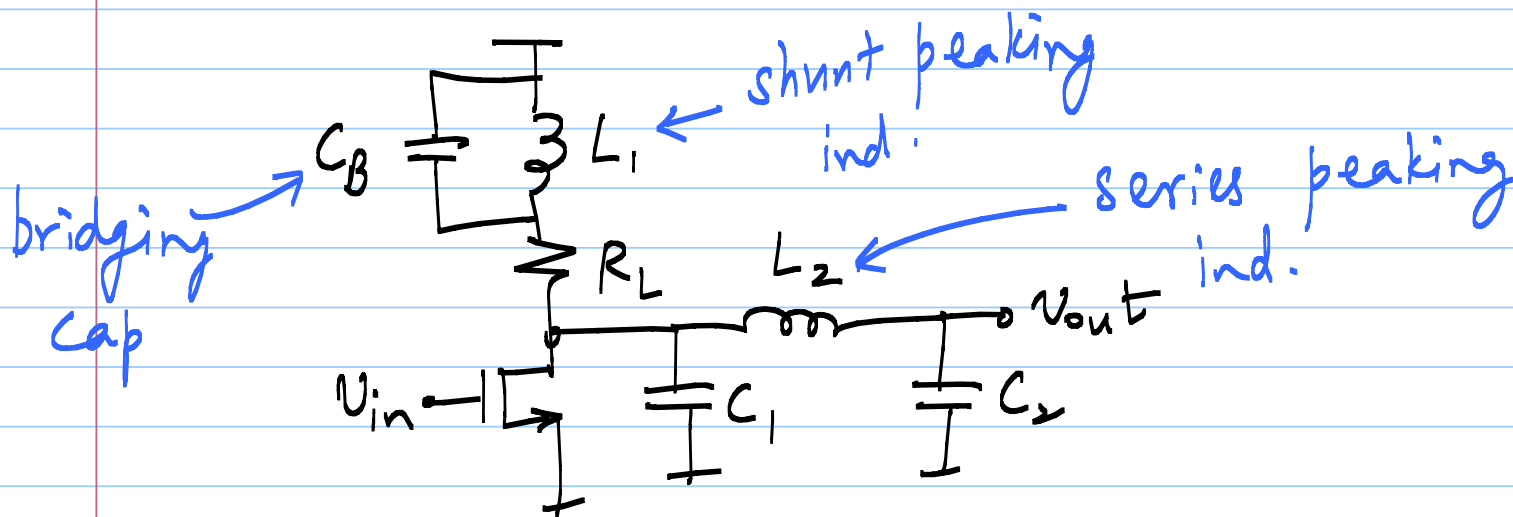
## 6) Bridged shunt-series peaking

\* add 2 zeroes to  $Z_N(s)$  in (5) above  
shunt  $L + C_B$



$$\omega_0 = \frac{1}{R_L C_L}$$

$$C_L = C_1 + C_2$$

$$k_C = \frac{C_1}{C_L}$$

$$m_1 = \frac{R_L^2 C_L}{L_1}$$

$$m_2 = \frac{R_L^2 C_L}{L_2}$$

$$Z_N(s) = \frac{\text{2 zeroes}}{\text{5 poles}}$$

$$k_B = \frac{C_B}{C_L}$$



$$Z_N(s) = \frac{1 + \left(\frac{1}{m_1}\right) \frac{s}{\omega_0} + \left(\frac{k_B}{m_1}\right) \frac{s^2}{\omega_0^2}}{1 + \frac{s}{\omega_0} + \left[\frac{1+k_B}{m_1} + \frac{1-k_c}{m_2}\right] \frac{s^2}{\omega_0^2} + \left[\frac{k_B}{m_1} + \frac{k_c(1-k_c)}{m_2}\right] \frac{s^3}{\omega_0^3} + \left[\frac{(k_c+k_B)(1-k_c)}{m_1 m_2}\right] \frac{s^4}{\omega_0^4} + \left[\frac{k_B k_c (1-k_c)}{m_1 m_2}\right] \frac{s^5}{\omega_0^5}}$$

\*  $k_c = 0.4$ ,  $m_1 = 8$ ,  $m_2 = 2.4$ ,  $k_B = 0.3$  :


BWER =  $3.92x$ , 0 dB peaking

\*  $k_c = 0.4$ ,  $m_1 = 6$ ,  $m_2 = 2.4$ ,  $k_B = 0.2$  :

BWER =  $4x$ , 2 dB peaking

## 7) Shunt + double series peaking


revisit basic shunt peaking

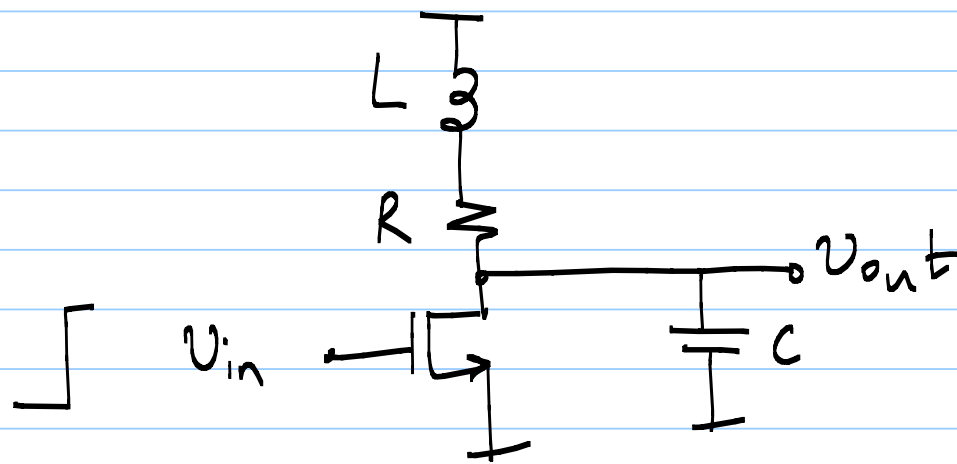

\* BW can be inferred from step response

faster step response  $\leftrightarrow$  higher BW

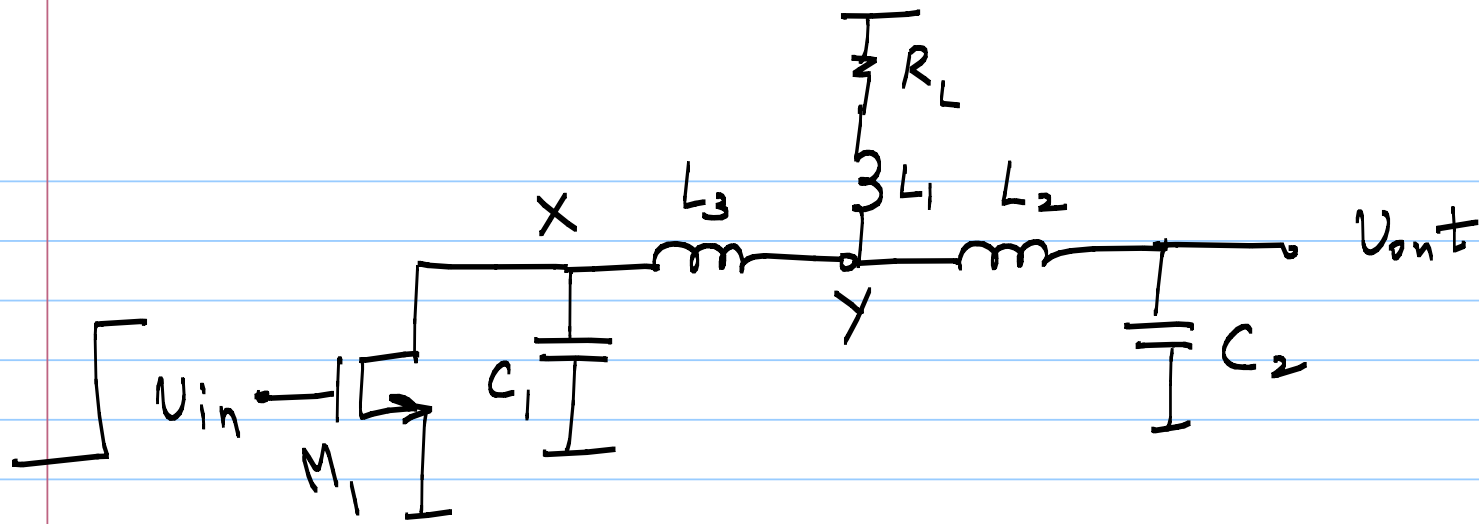- \*  $L$  delays current flow through  $R$ 
  - $\rightarrow$  more current available to charge  $C$
  - $\rightarrow$  lower rise time, higher BW



- \*  $L_1$  delays current through  $R_L$
- \*  $L_3$  delays current to rest of the network
- \*  $M_1$  drive only self cap.  $C_1$  for some time  
 → rise time @  $x$  (drain of  $M_1$ ) improves
- \* After some time,  $V_y$  rises
- \* Finally,  $V_{out}$  starts to rise (as current starts to flow through  $L_2$ )

10/4/20

Lec 37

\* Shunt + double series peaking network trades off increased delay for improved BW

8) T-coil BW enhancement


\* Realize  $L_1-L_2-L_3$  as a transformer

→ smaller die area

→ Eq. det is the same

\* Use a symmetric Xfmr

\* Works well if  $C_1 \ll C_2$

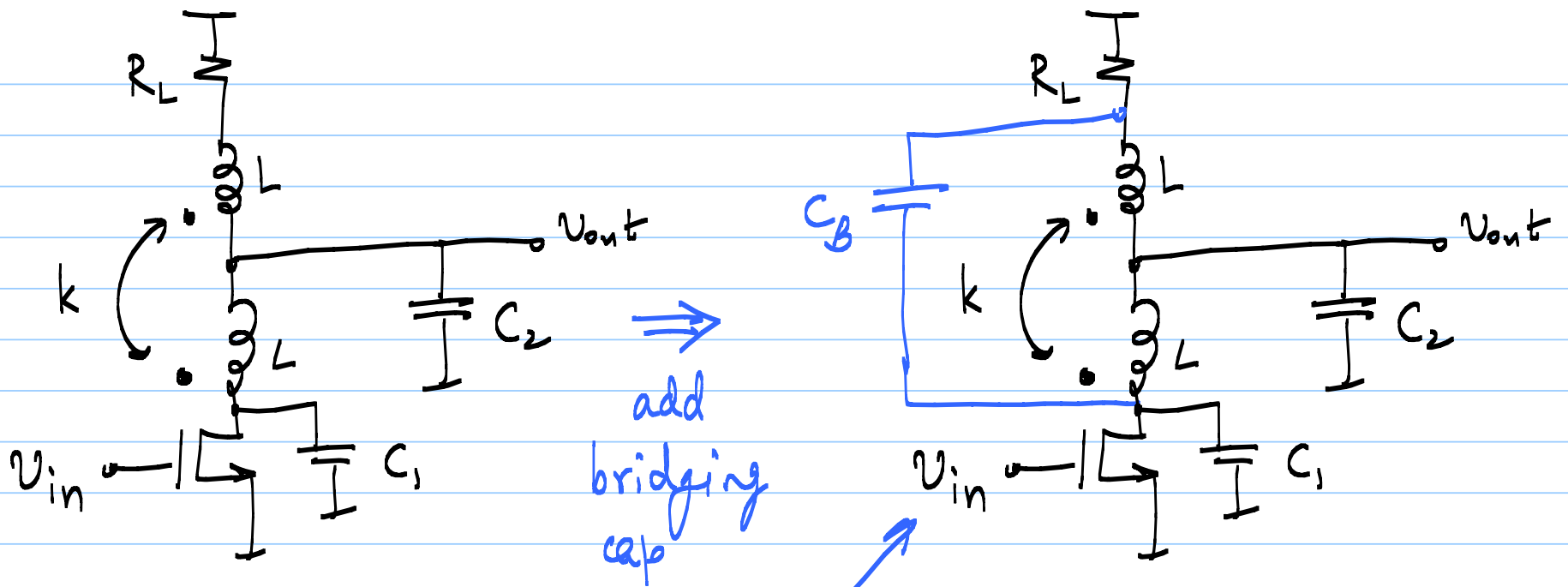

9) Bridged T-coil BW enhancement

- \*  $C_B$  creates parallel resonance across  $X_{fm} r$
- \* Circulating currents allow faster charging of node voltages ( $\uparrow$  BW)

$$Z_N(s) = \frac{1}{1 + 2 \zeta \left( \frac{s}{\omega_n} \right) + \frac{s^2}{\omega_n^2}}$$

$$L = \frac{R_L^2 C_L}{2(1+k)} = \text{primary \& secondary self-ind.}$$

$$C_B = \frac{C_L}{4} \frac{1-k}{1+k}$$

$k$  - decides magnitude response

\*  $k = \frac{1}{3} \Rightarrow$  Butterworth response (maximally flat)

$$\left( \zeta = \frac{1}{\sqrt{2}} \right)$$

$$BWER = 2\sqrt{2} = 2.83 \times$$

\*  $k = \frac{1}{2} \Rightarrow$  maximally flat group delay

$$\text{BWER} = 2.7 \times$$

\*  $C_2 \gg C_1$

\* If  $C_1 \gg C_2$ , interchange T-wind connections

e.g. min.  $R_L = 100 \Omega$ ,  $C_L = 1.5 \text{ pF}$

$$f_0 = \frac{1}{2\pi R_L C_L} = 1.06 \text{ GHz}$$

phase modulated data  $\Rightarrow k = \frac{1}{2}$

$$L = \frac{R_L^2 C_L}{2(1+k)} = 5 \text{ nH}$$

$$C_B = \frac{C_L}{4} \frac{1-k}{1+k} = 125 \text{ fF}$$

Can be  
absorbed as


$$\begin{aligned} \text{new BW} &= 2.7 \times 1.06 \text{ GHz} \\ &= 2.86 \text{ GHz} \end{aligned}$$

parasitic cap of  
Xfmr

⇒ no increase in power



10) Asymmetric T-coil

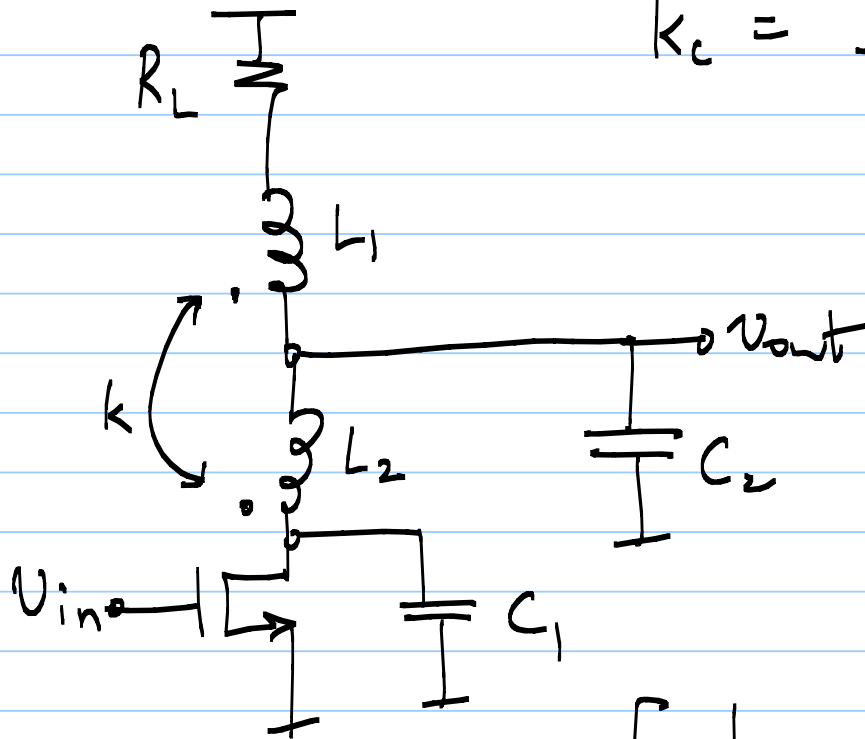

$$k_c = \frac{C_1}{C_L} ; m_1 = \frac{R_L^2 C_L}{L_1} ;$$

$$m_2 = \frac{R_L^2 C_L}{L_2} ;$$

$k_m =$  Xfmr coupling factor

$$= \frac{M}{\sqrt{L_1 L_2}}$$


$$Z_N(s) = \frac{1 + \left[ \frac{1}{m_1} + \frac{k_m}{\sqrt{m_1 m_2}} \right] \frac{s}{\omega_0}}{1 + \frac{s}{\omega_0} + \left[ \frac{1}{m_1} + \frac{k_c}{m_2} + \frac{2k_c k_m}{\sqrt{m_1 m_2}} \right] \frac{s^2}{\omega_0^2} + \left[ \frac{k_c(1-k_c)}{m_2} \right] \frac{s^3}{\omega_0^3} + \left[ \frac{k_c(1-k_c)(1-k_m^2)}{m_1 m_2} \right] \frac{s^4}{\omega_0^4}}$$

## BW enhancement ( $f_T$ doublers)

$$\text{MOSFET } \omega_T = \frac{g_m}{C_{gs} + C_{gd}} \approx \frac{g_m}{C_{gs}}$$

$$\uparrow \omega_T \Rightarrow \uparrow I_D, \downarrow W \\ (\uparrow V_{as} - V_T)$$

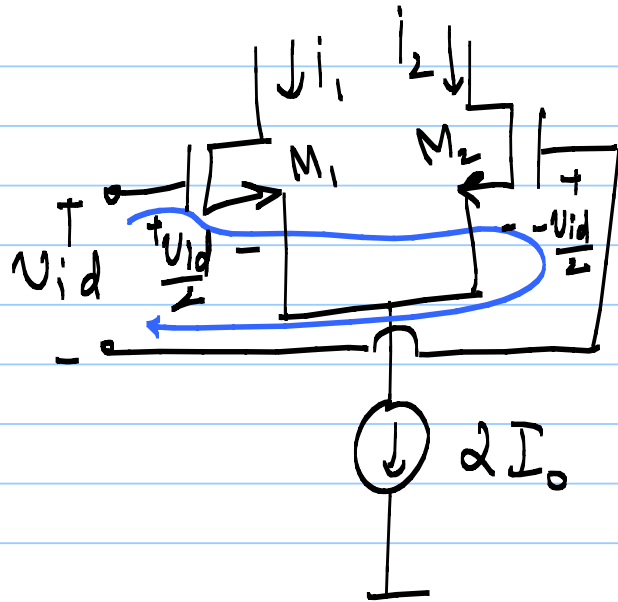$\Rightarrow$  you will hit velocity sat.



$$i_d = i_1 - i_2 = g_m V_{id}$$


$$C_{in} = C_{gs1} \text{ series } C_{gs2}$$

$$= \frac{C_{gs}}{2}$$

$$\text{eq. } f_T = \frac{2g_m}{C_{gs}}$$

\* Diff. amp. acts as an  $f_T$  doubler

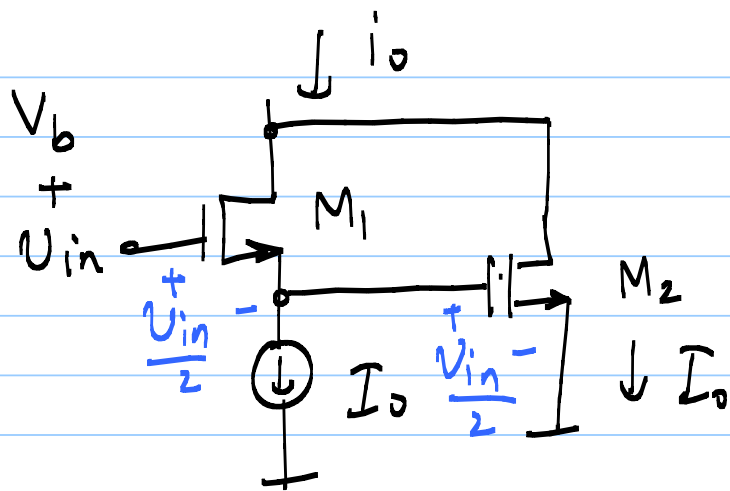\* Single ended In & out  $\Rightarrow$  interchangy G & S  
of  $M_2$



$$M_1 = M_2$$

$$I_{D1} = I_{D2}$$


$$C_{in} = C_{gs}/2$$

$$i_1 = i_2 = g_m \frac{V_{in}}{2}$$

$$i_o = i_1 + i_2$$

$$f_T = \frac{2g_m}{C_{gs}}$$

### Battjes $f_T$ doubler

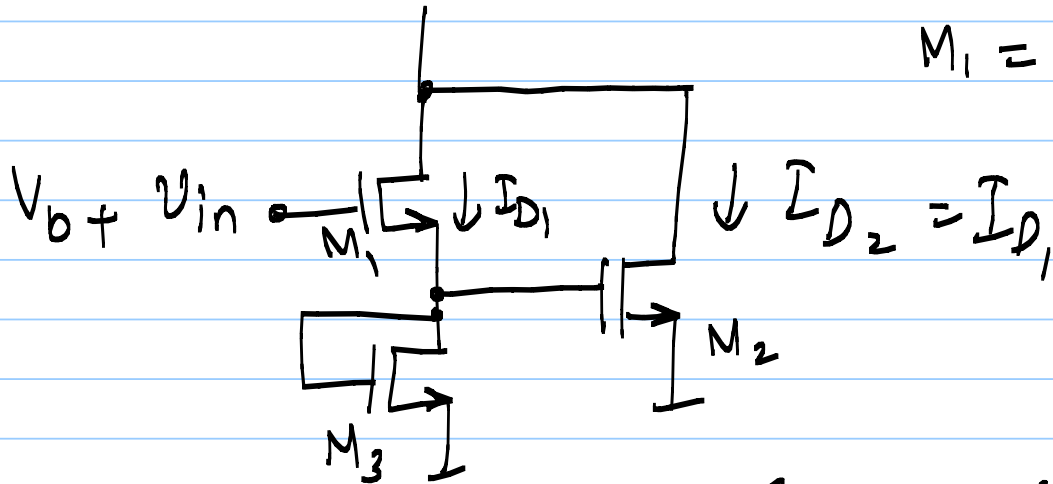

$$M_1 = M_2 = M_3$$

$$f_T \approx 1.5 \times$$

improvement  
due to  $C_{gs}$  &  $C_{db}$  of  $M_3$

$$C_{in} \approx C_{gs1} \text{ ser. } (C_{gs2} + C_{gs3}) \approx \frac{1}{1.5} C_{gs}$$

## Cascaded Amplifiers.

each stage :  $H(s) = \frac{A_0}{s\tau + 1}$        $\tau = \frac{1}{\omega_0}$

$H_N(s) = \frac{1}{s\tau + 1}$       normalized TF

Cascade  $n$  v amplifiers identical

cascaded gain (normalized)  $A_N(s) = \left[ \frac{1}{s\tau + 1} \right]^n \Rightarrow$  3 dB BW of cascade

$$|A_N(j\omega)| = \frac{1}{\sqrt{2}}$$

$$\left| \frac{1}{j\omega\tau + 1} \right|^n = \frac{1}{\sqrt{2}}$$

$$\left( \frac{1}{\sqrt{(\omega\tau)^2 + 1}} \right)^n = \frac{1}{\sqrt{2}}$$

$$\left( (\omega\tau)^2 + 1 \right)^n = 2$$

BW shrinkage



$$\omega = \frac{1}{\tau} \sqrt{2^{1/n} - 1} = \omega_0 \sqrt{2^{1/n} - 1}$$

$$n \rightarrow \infty \Rightarrow \omega \rightarrow 0$$

$$2^{1/n} = \exp(\ln(2^{1/n})) = \exp\left[\frac{1}{n} \ln 2\right]$$

If  $n$  is large,

$$\exp\left[\frac{1}{n} \ln 2\right] \approx 1 + \frac{1}{n} \ln 2$$

$$\omega = \omega_0 \sqrt{2^{1/n} - 1} \approx \omega_0 \sqrt{\frac{1}{n} \ln 2} \approx \frac{0.833 \omega_0}{\sqrt{n}}$$

Optimum gain per stage

Let overall desired gain =  $G$   
of cascade

gain of each stage =  $G^{1/n}$

$$\omega_u = G^{1/n} \cdot \omega_0$$

$$\omega_0 = \frac{\omega_u}{G^{1/n}}$$

$$\omega_{3dB} \approx \frac{\omega_0 \cdot \sqrt{\ln 2}}{\sqrt{n}} \approx \frac{\omega_u}{G^{1/n}} \frac{\sqrt{\ln 2}}{\sqrt{n}}$$

we want to maximise  $\omega_{3dB}$

$\Rightarrow$  minimise  $\frac{1}{\omega_{3dB}}$



$$\frac{d}{dn} \left[ \frac{1}{\omega_{3dB}} \right] = 0$$

$$\frac{d}{dn} \left[ \frac{1}{\omega_u \sqrt{\ln 2}} \cdot \sqrt{n} \cdot G^{1/n} \right] = 0$$

$$\frac{d}{dn} \left[ \sqrt{n} G^{1/n} \right] = 0$$

$$\Rightarrow \ln [G^{1/n}] = \frac{1}{2} \Rightarrow \boxed{G^{1/n} = \sqrt{e}} \quad \begin{array}{l} \text{gain} \\ \text{per} \\ \text{stage} \end{array}$$

$$\boxed{n = 2 \ln G} \quad \# \text{ of stages}$$

$$\omega_{3dB} = \omega_u \sqrt{\frac{\ln 2}{2e \ln G}} \approx \frac{0.357 \omega_u}{\sqrt{\ln G}}$$


14/4/20

## Lec 38

### Phase locked loops (PLL)


First part of the course - closed loop voltage amp.


$$V_o = k V_i$$

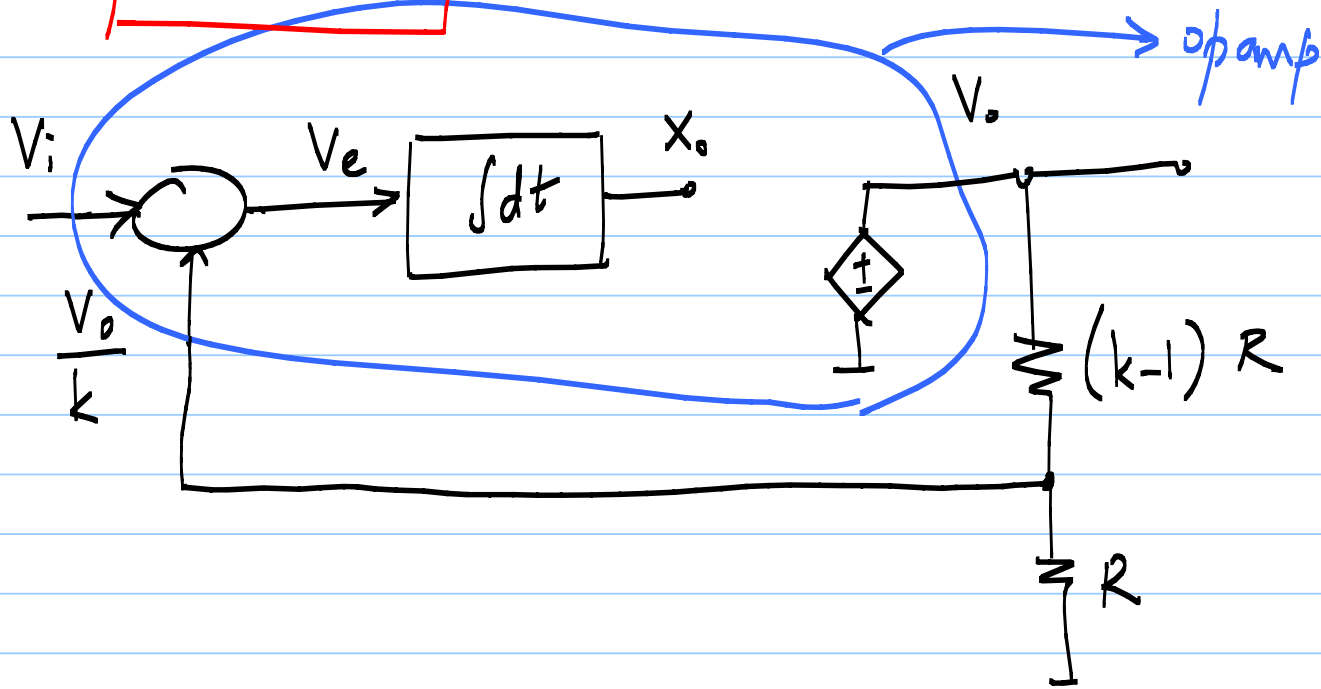

Frequency Multiplier

$$f_{out} = N f_{in}$$

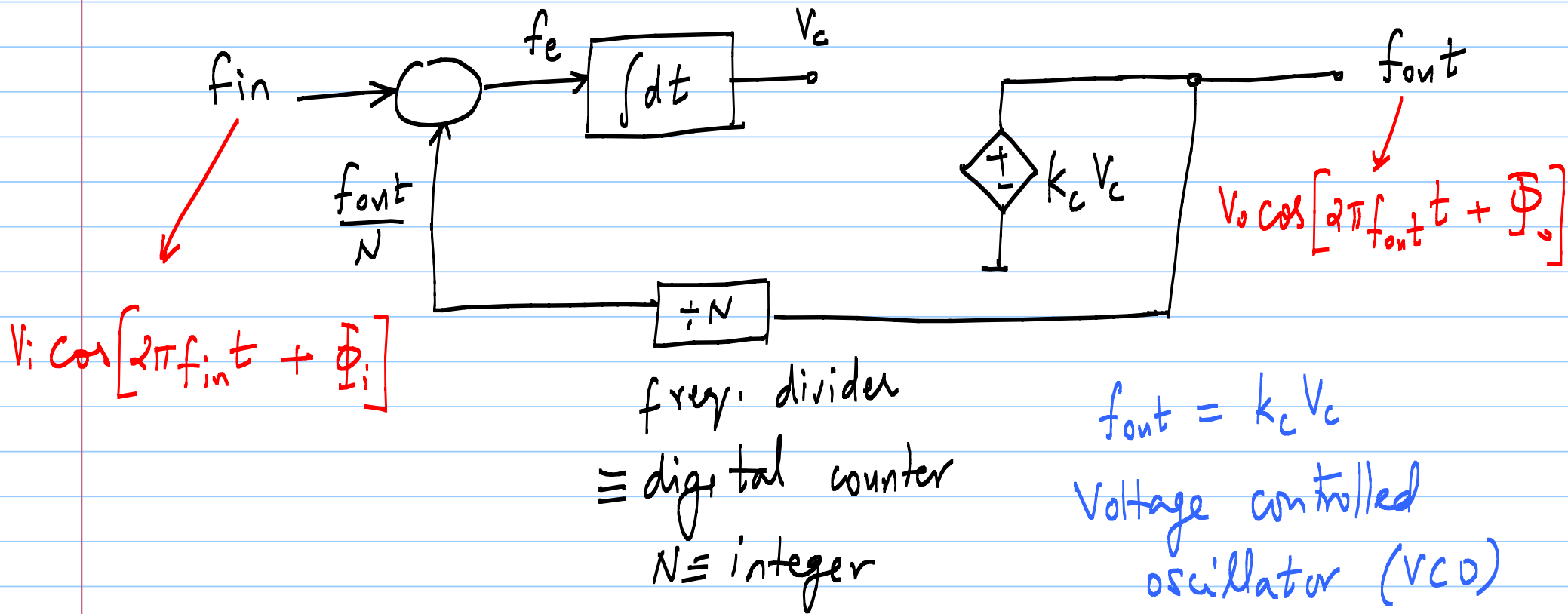

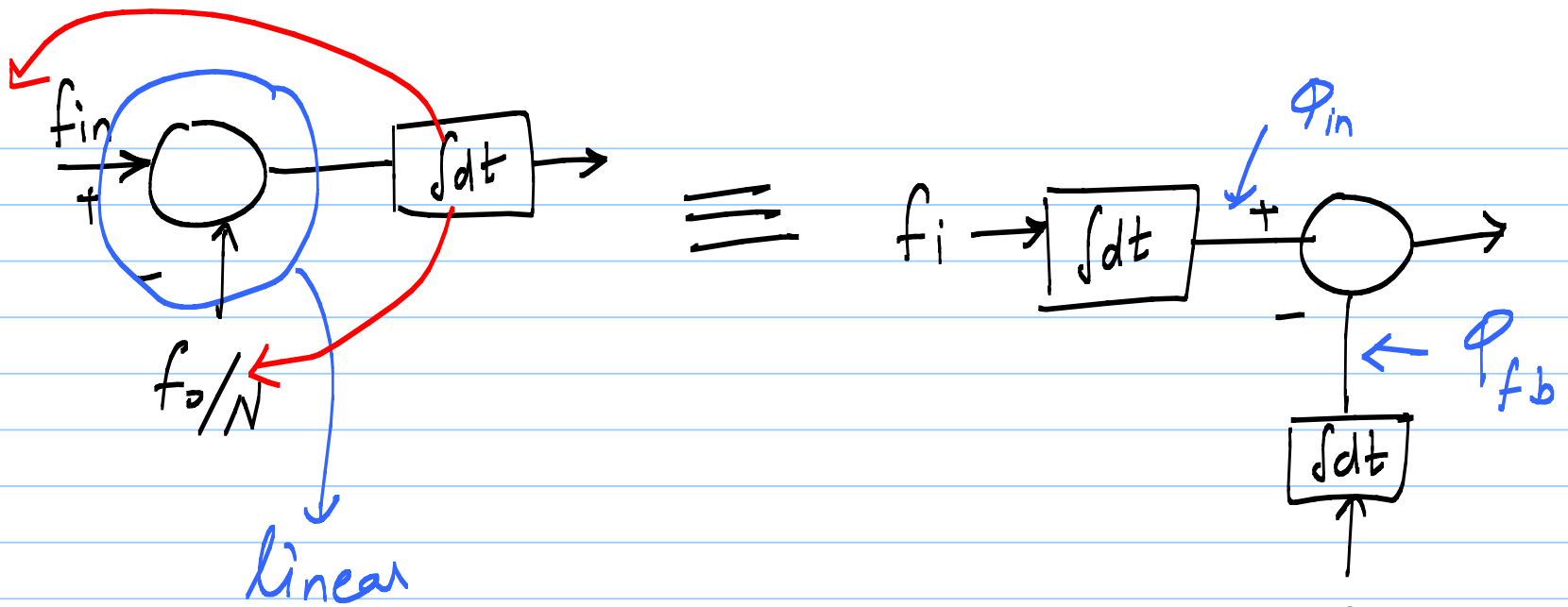


$$f_{fb} = f_{out}/N$$

"phase detector"

VCO

$$f_{out} = K_c V_c$$

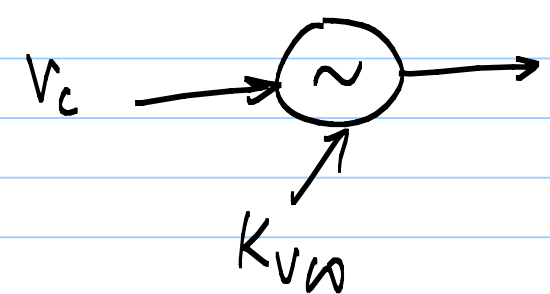

$$\cos(\omega_{out} t)$$

(periodic @  $2\pi$ )

$$f_{out} = \underbrace{f_{free}}_{\text{constant}} + K_{vco} \cdot V_c$$



constant

units of Hz/V


$$\phi_{out} = 2\pi \int f_{out} dt$$

$$= 2\pi \int (f_{free} + K_{VCO} \cdot V_c) dt$$

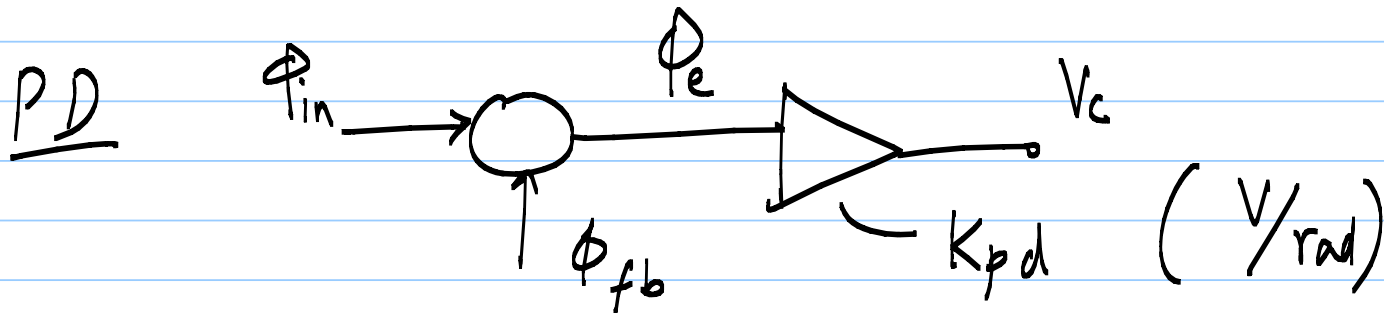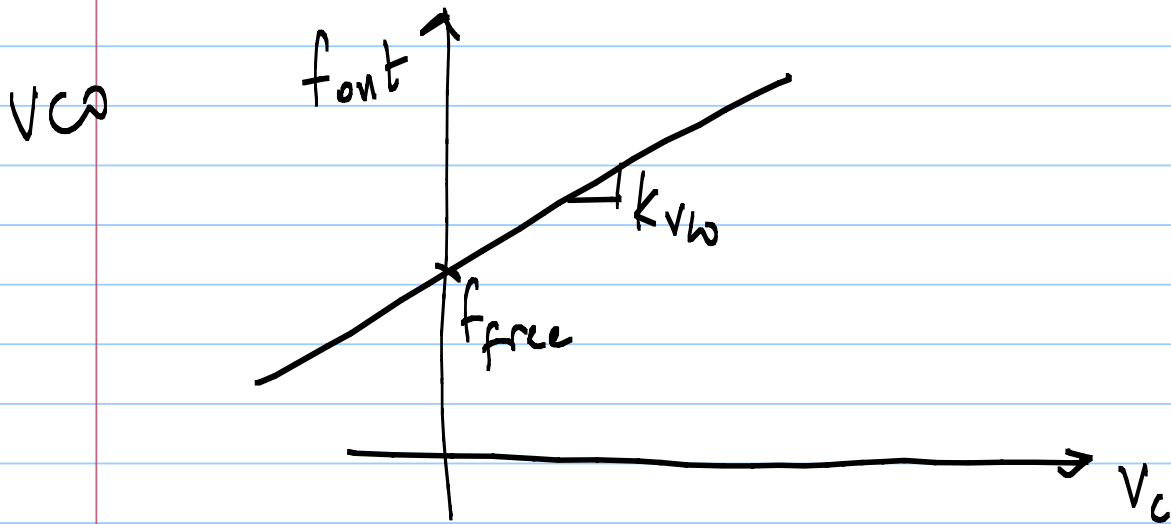
$$= 2\pi f_{free} \cdot t + 2\pi K_{VCO} \int_{-\infty}^t V_c dt + \phi_0$$




Freq. divider

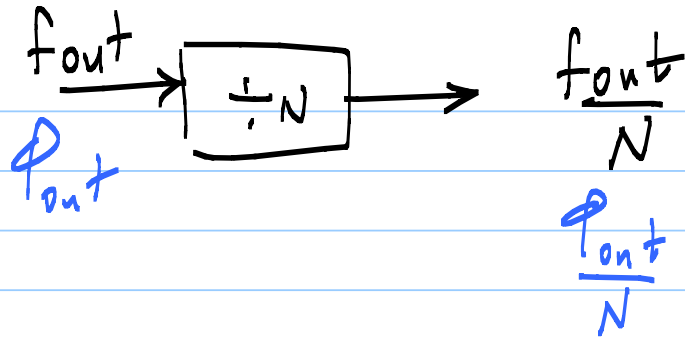


Linear model of PLL

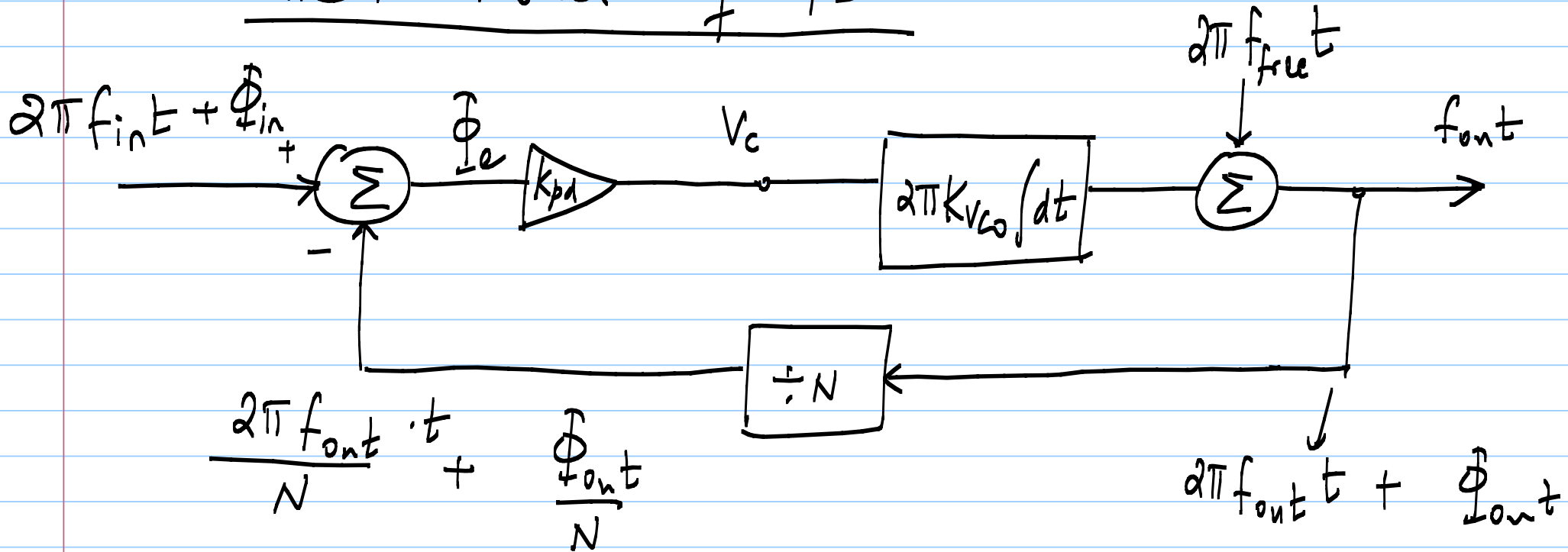

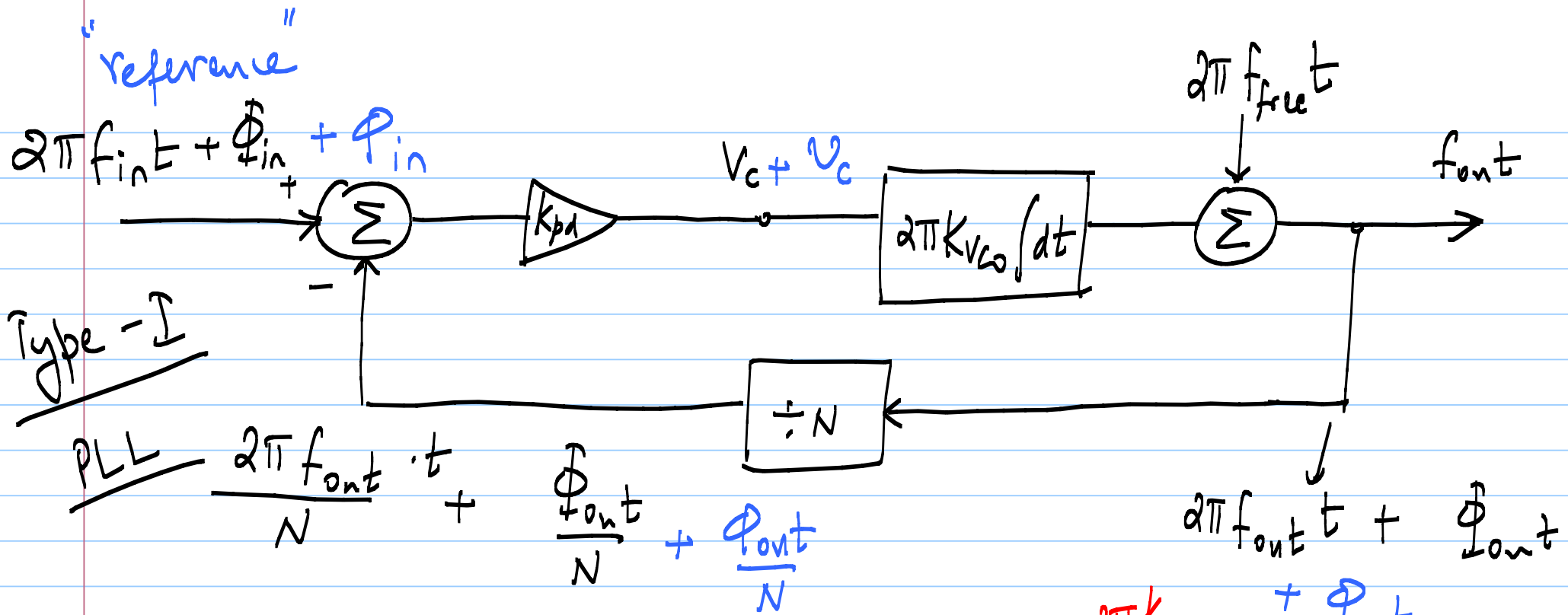In steady state (lock) :  $f_{in} = \frac{f_{out}}{N}$



Incremental picture

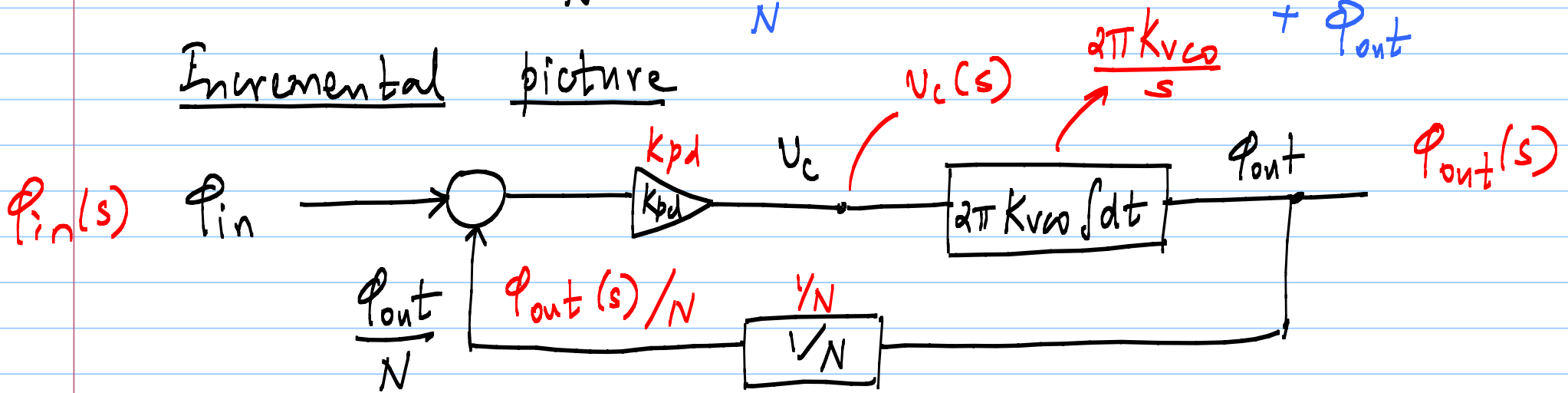

Loop gain  $L(s) = \frac{2\pi K_{pd} K_{v\omega}}{Ns}$


closed loop gain  $\frac{\phi_{out}(s)}{\phi_{in}(s)} = N \cdot \frac{L(s)}{1+L(s)}$

$$\frac{\phi_{out}}{\phi_{in}}(s) = N \cdot \frac{1}{1 + \frac{N}{2\pi K_{pd} K_{v\omega}} \cdot s}$$

closed loop -3dB BW  $f_{-3dB} = \frac{K_{pd} K_{v\omega}}{N}$
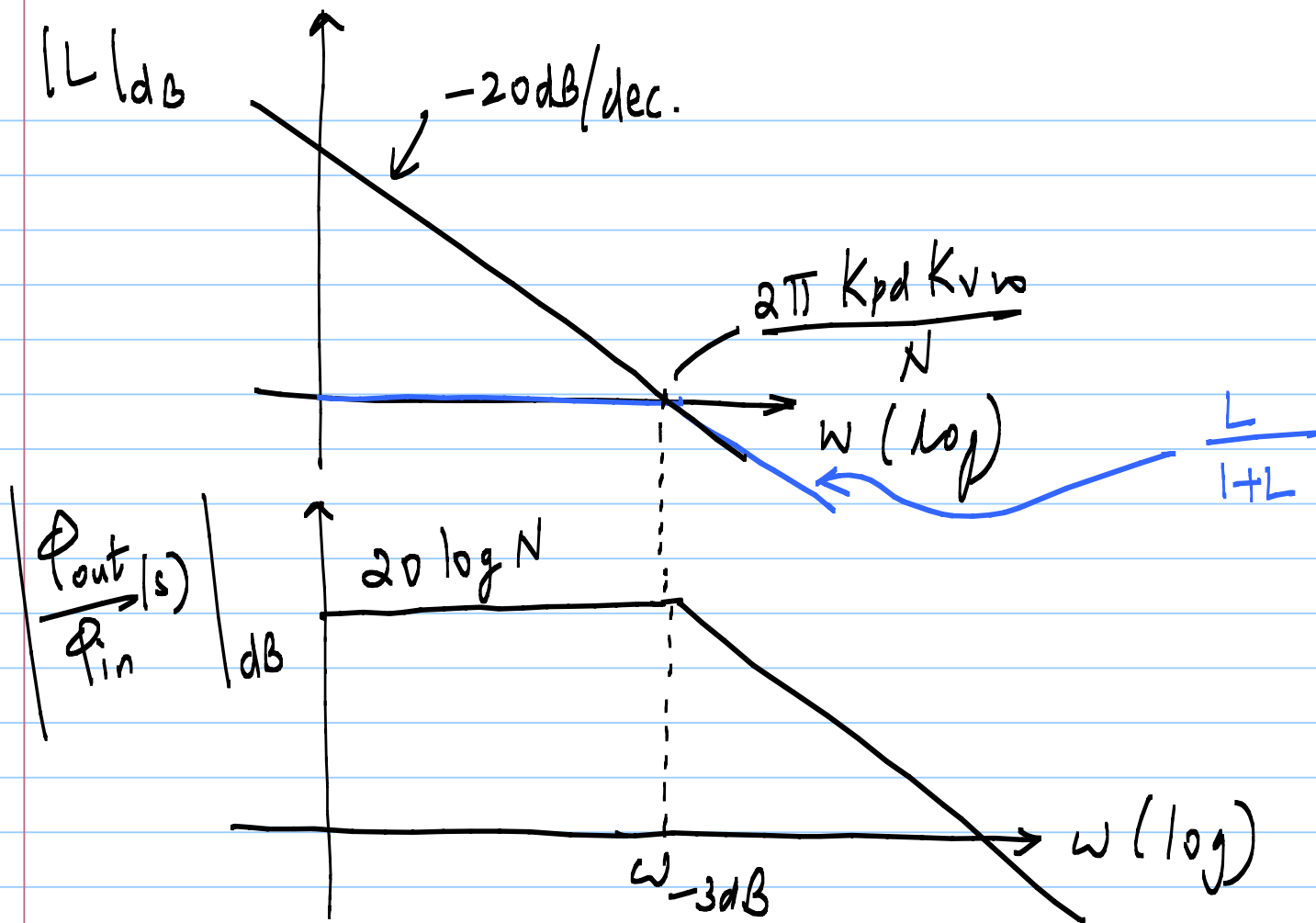
$$\omega_{-3dB} = \frac{2\pi K_{pd} K_{v\omega}}{N}$$





In steady state

$$f_{in} = \frac{f_{out}}{N}$$

in general,  
 $f_{out} > f_{free}$   
i.e.  $V_c > 0$

$$V_c = \frac{(N f_{in} - f_{free})}{K_{vw}}$$

in lock  $f_{out} = f_{free} + K_{vw} \cdot V_c$

We also know that

$$V_c = K_{pd} \left[ \Phi_{in} - \frac{\Phi_{out}}{N} \right]$$

In general,  $f_{out} \neq f_{free}$ ;  $V_c > 0$

$\Phi_{in} \neq \frac{\Phi_{out}}{N}$   $\left\{ \text{though } f_{in} = \frac{f_{out}}{N} \right\}$

⇒ Type-I PLL

$f_e = 0$  in steady state

but  $\phi_e \neq 0$

16/4/20

Lec 39

$$V_c = \frac{N f_{in} - f_{free}}{K_{v\omega}} \text{ in steady state}$$

input phase error


$$\Phi_e = \frac{V_c}{K_{pd}} = \frac{N f_{in} - f_{free}}{K_{pd} K_{v\omega}} \neq 0$$

\* All real PD also have a periodic term

in addition to  $\Phi_e$

$\Rightarrow V_c$  will also have a periodic component

PLL (VCO)  
Output Ampl.

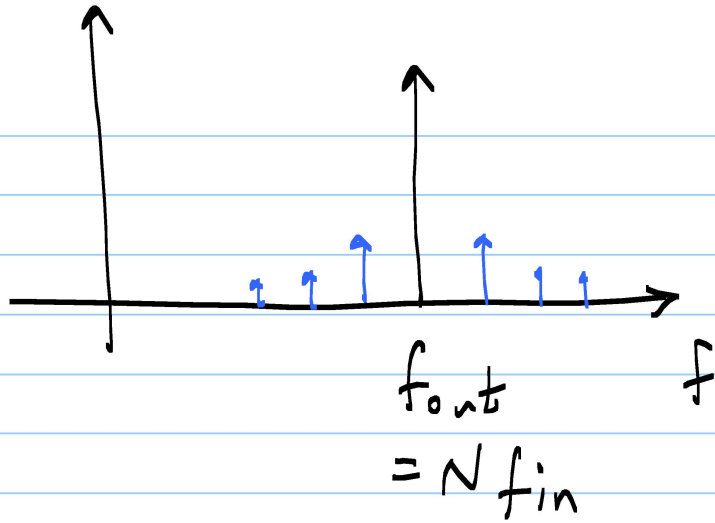


"Spurious" tones @

$$N f_{in} \pm k f_{in}$$

$\equiv$  "reference feedthrough"

$$f_{3dB} \ll f_{in}$$

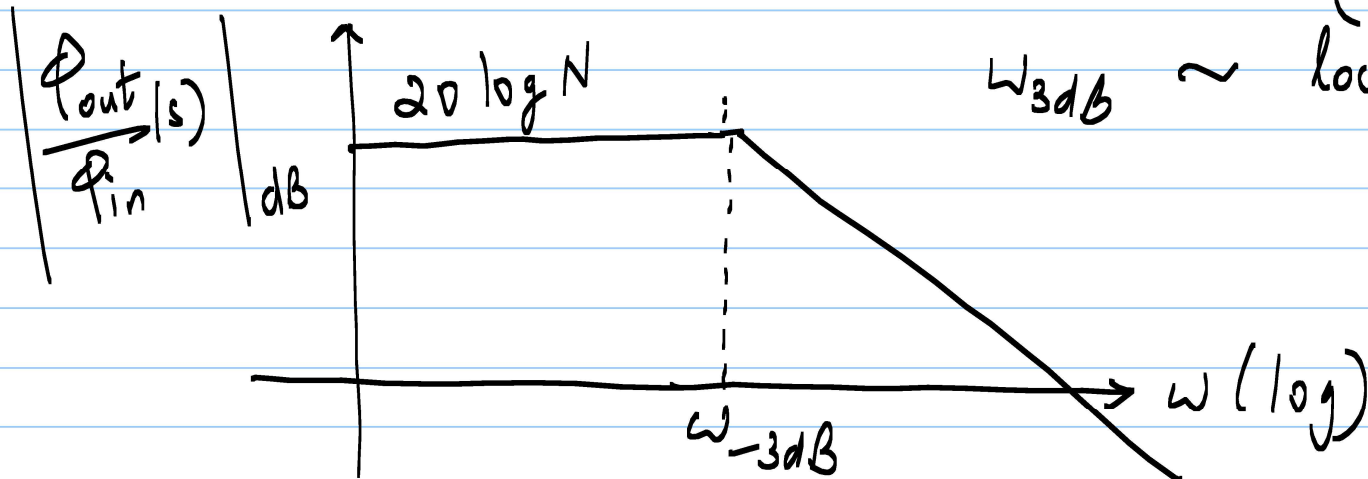

(related to)  
 $\omega_{3dB} \sim$  lock range of the PLL

$$\omega_{-3dB} = \frac{2\pi K_{pd} K_{vco}}{N}$$


$$N = \frac{f_{out}}{f_{in}}$$


↑ lock range  $\leftrightarrow$  you have to ↑  $K_p K_v \omega$

↑  $f_{-3dB}$  → write reference feedthrough

\* Ideally, we want to ↑  $K_p K_v \omega$  only @ dc

⇒ use an integrator (in the limit)

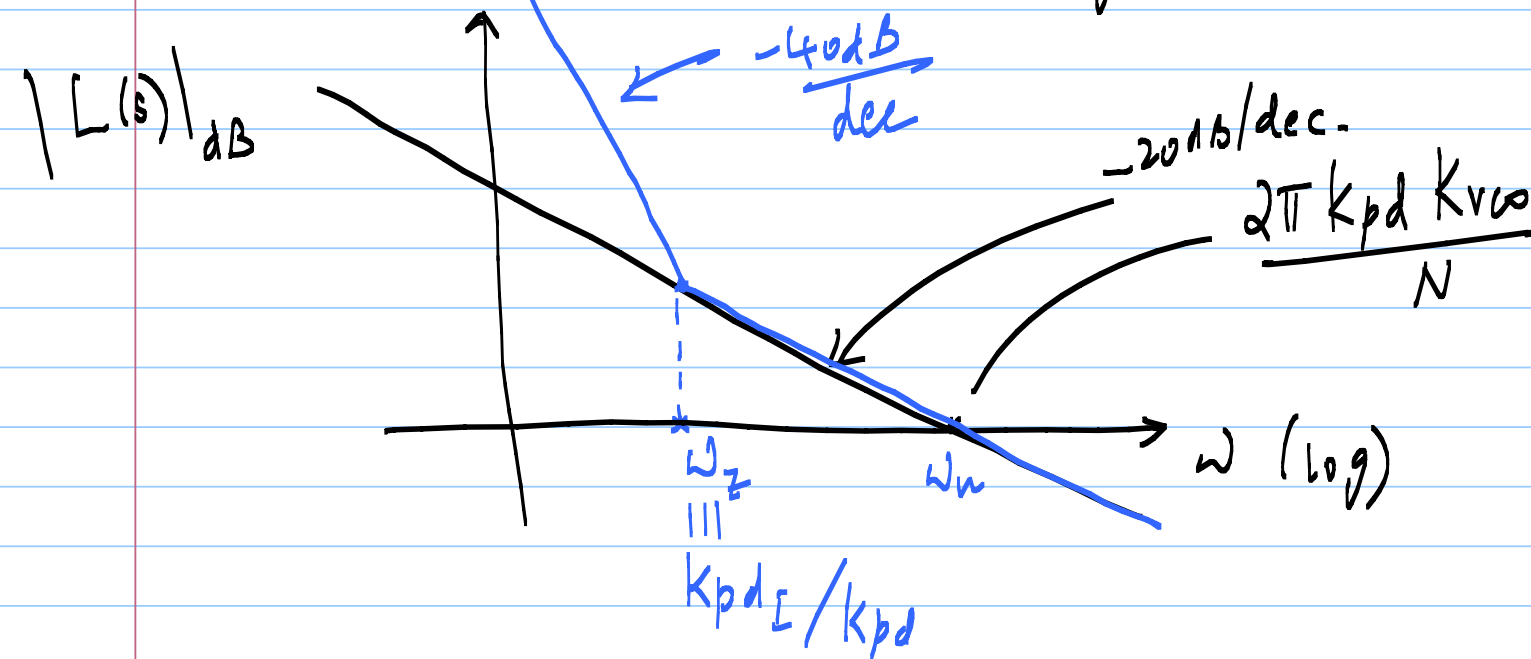

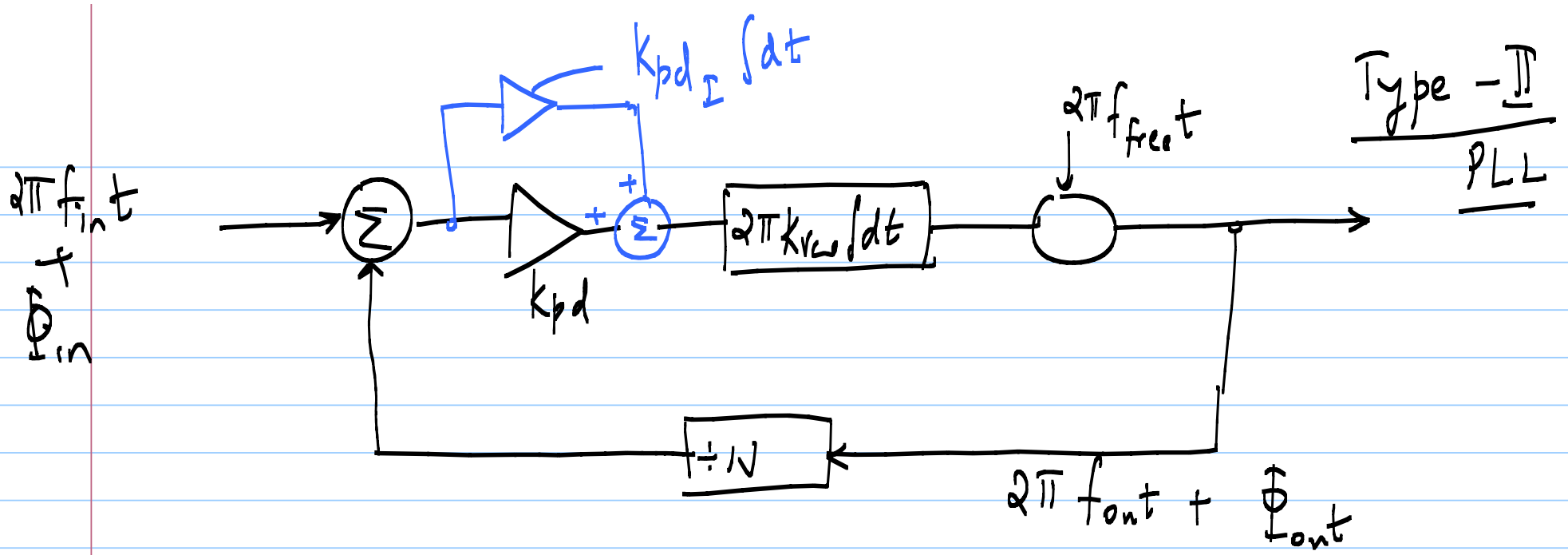

Type - II  
PLL

$$L(s) = \frac{2\pi K_{vco}}{Ns} \left[ K_{pd} + \frac{K_{pd_I}}{s} \right]$$

$$= \frac{2\pi K_{pd_I} \cdot K_{vco}}{Ns^2} \left[ 1 + \frac{K_{pd} \cdot s}{K_{pd_I}} \right]$$


$\omega_z$  is set using  $K_{pd_I}$

$$\frac{\varphi_{out}}{\varphi_{in}}(s) = N \frac{1 + s \cdot \left( \frac{K_{pd}}{K_{pdI}} \right)}{1 + s \cdot \frac{K_{pd}}{K_{pdI}} + s^2 \cdot \frac{N}{2\pi K_{pdI} K_{v\omega}}}$$


$$\omega_n = \sqrt{\frac{2\pi K_{pdI} K_{v\omega}}{N}} \quad ; \quad Q = \frac{\sqrt{(N K_{pdI}) / (2\pi K_{v\omega})}}{K_{pd}}$$

$$\zeta = \frac{1}{2Q}$$




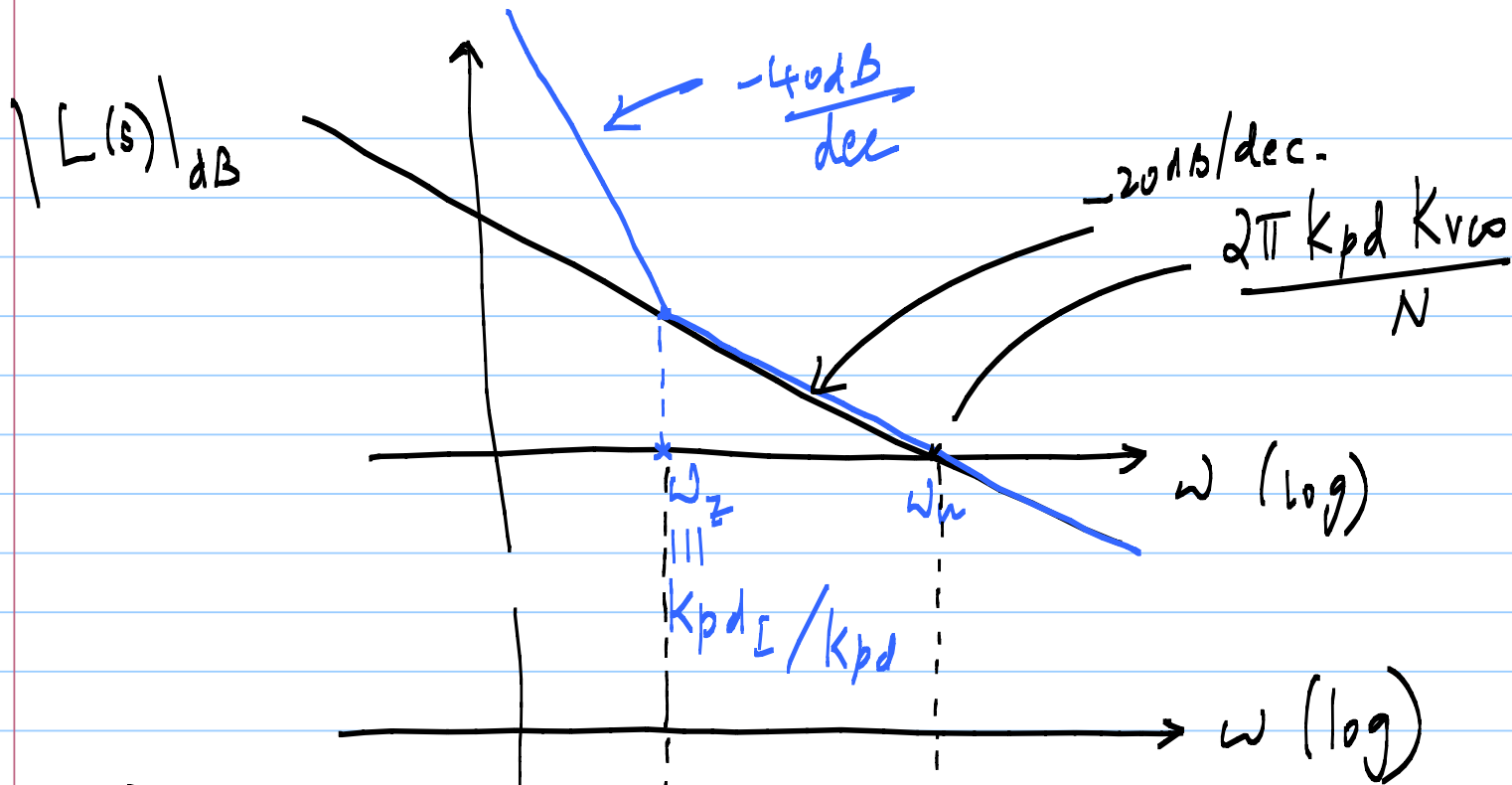

## Phase detector

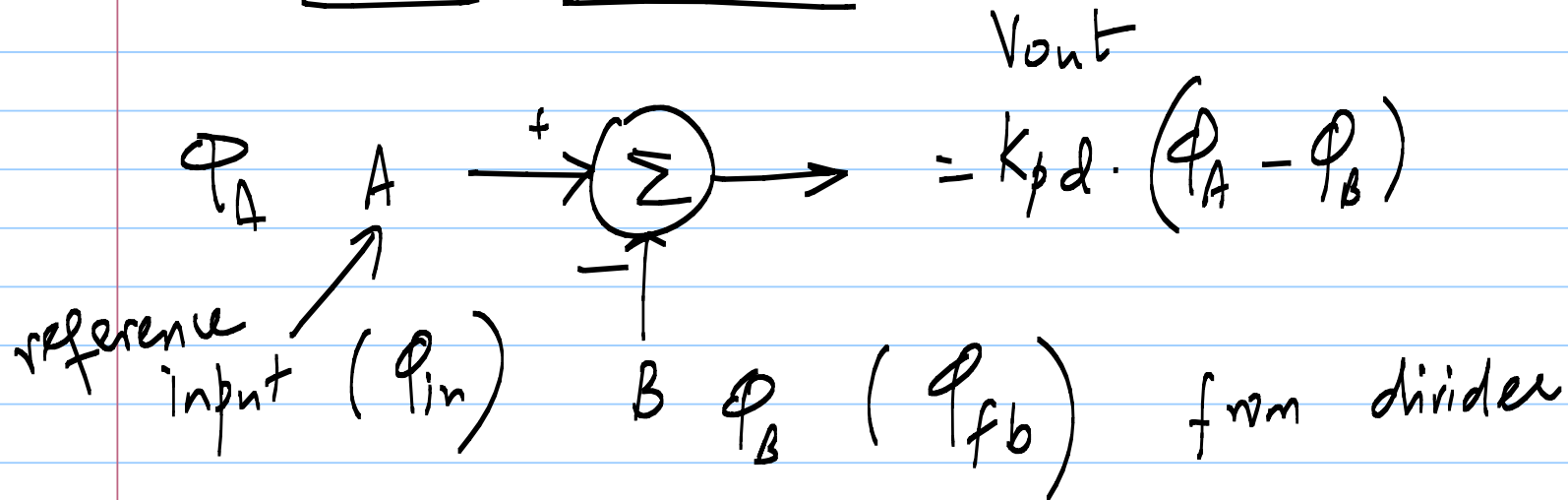

## Multiplier PD

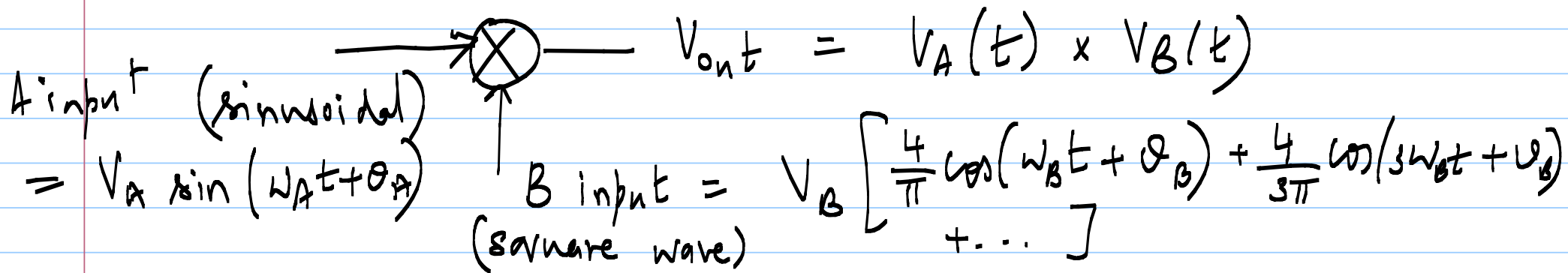

$$V_{out}(t) = V_A V_B \cdot \frac{4}{\pi} \sin(\omega_A t + \theta_A) \cdot \cos(\omega_B t + \theta_B)$$

$$+ V_A V_B \cdot \frac{4}{3\pi} \sin(\omega_A t + \theta_A) \cdot \cos(\omega_B t + \theta_B)$$

+ ...

$$= \frac{2}{\pi} V_A V_B \left[ \sin((\omega_A + \omega_B)t + \theta_A + \theta_B) \right.$$

$$\left. + \sin((\omega_A - \omega_B)t + \theta_A - \theta_B) \right.$$

+ ... ]

desired  
output  $\Delta f$


desired  
output  $\Delta \phi$


\*  $\omega_A + \omega_B$ ;  $\omega_A \pm k\omega_B$  for  $|k| > 1$  are undesired periodic terms @ PD output

\* LPF the PD output to reduce magnitude of undesired terms

- \* XOR gate can also act as a PD
  - \* Divider output is a square wave
  - \* reference input can be converted into a square wave easily
- Can you use a digital clock PD?
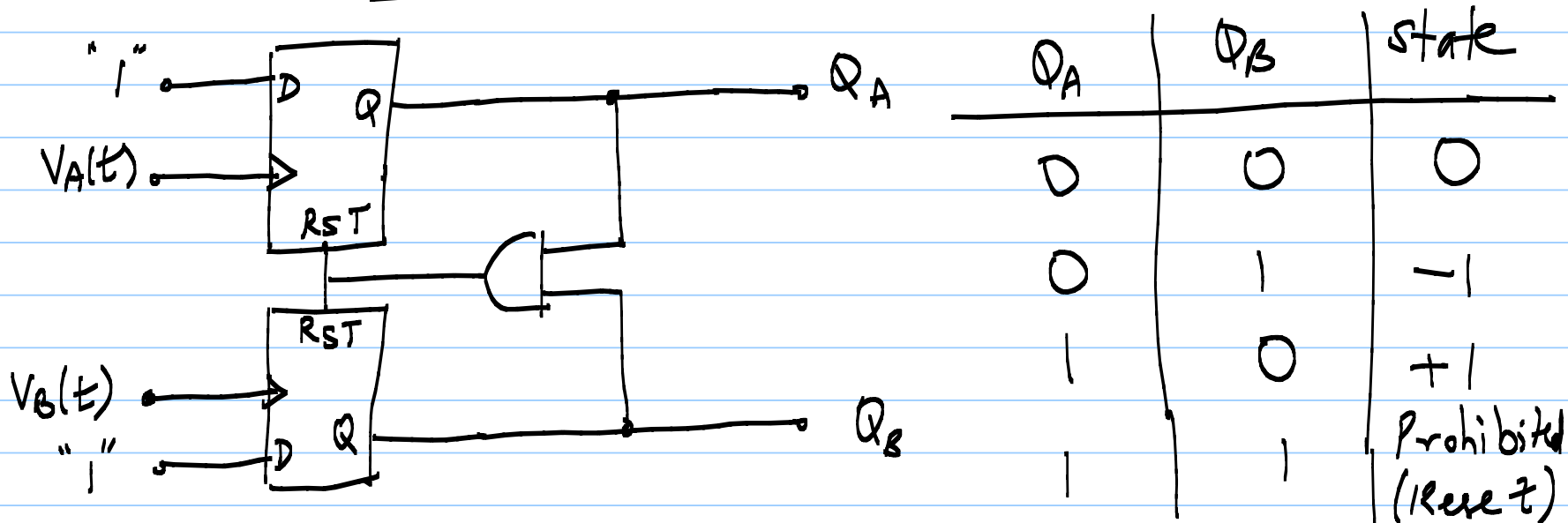
### Tristate Phase-frequency detector (PFD)




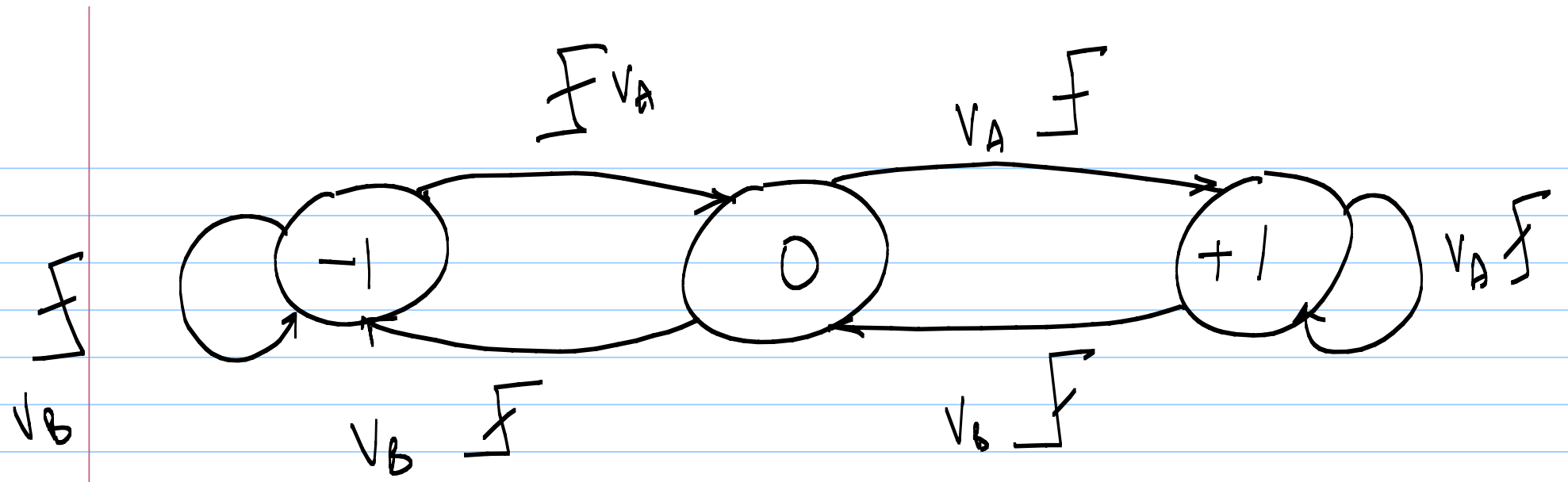

17/4/20


# Lec 40

## PFD Characteristics

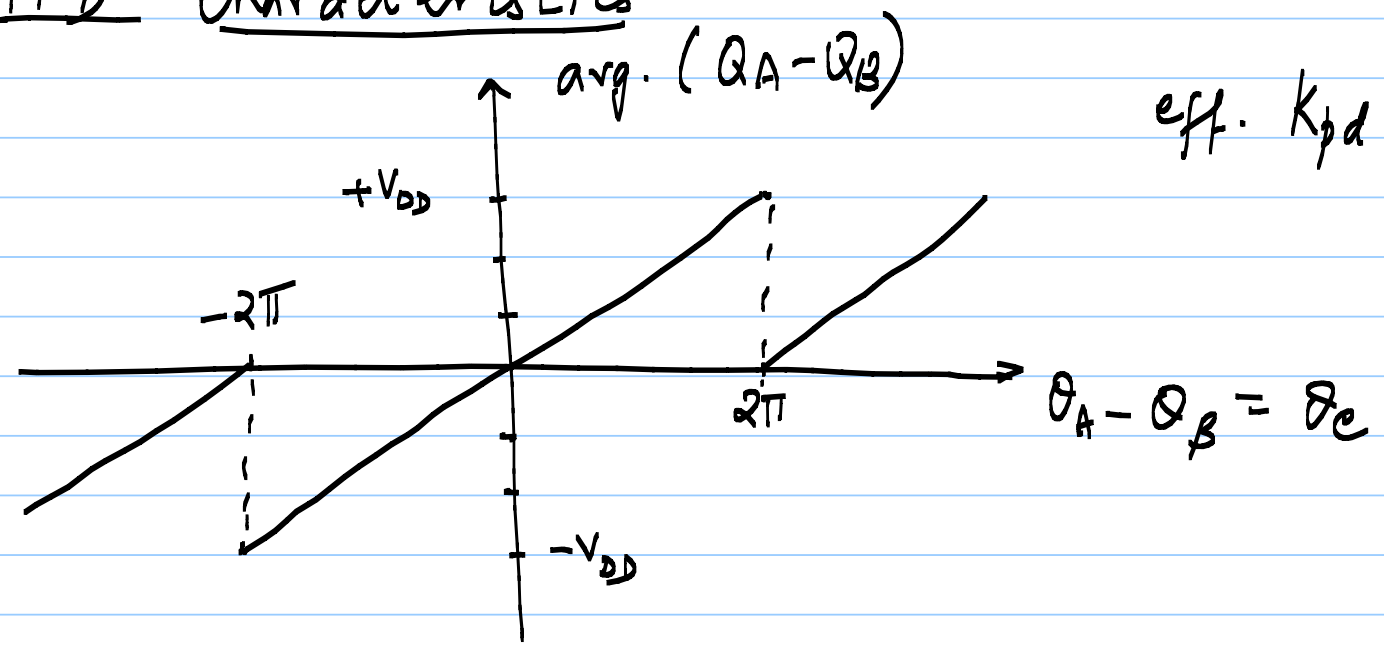



$$\begin{aligned} \text{eff. } K_{pd} &= \frac{2V_{DD}}{4\pi} \\ &= \frac{V_{DD}}{2\pi} \end{aligned}$$

$\phi_e > 0$

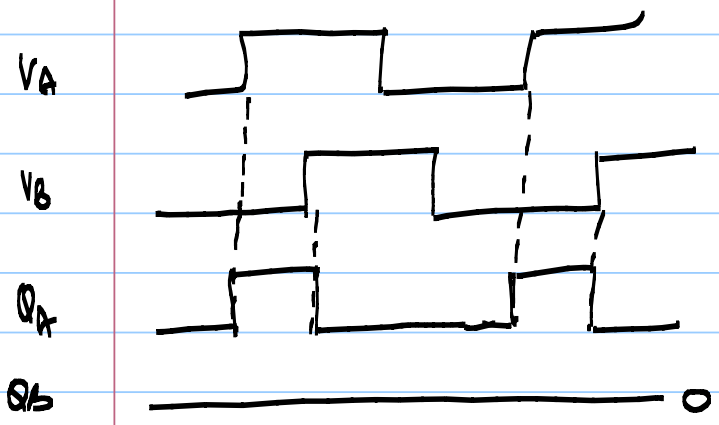

$\phi_e < 0$

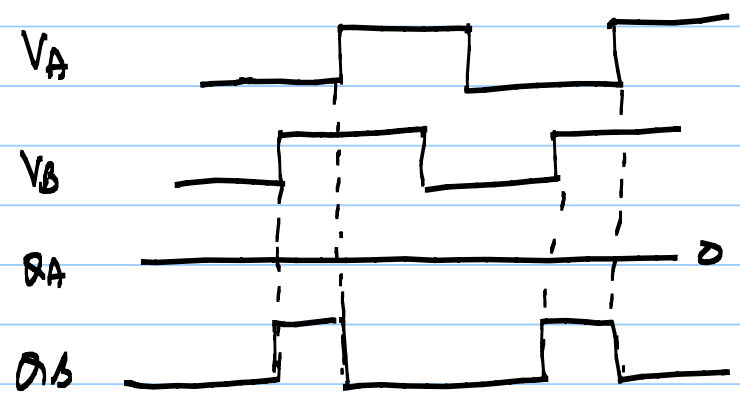

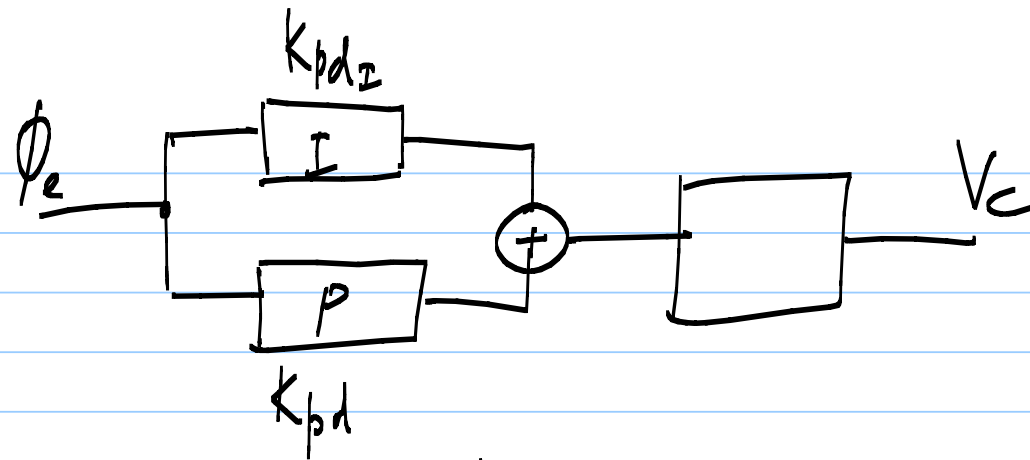

\* We have 2 outputs  $Q_A$  &  $Q_B$


we need  $\text{avg}(Q_A - Q_B)$

\*  $K_{pd}$  &  $K_{pdI}$  are required

— pass the same  $I$  through  $R$  &  $C$


Resistor  
 $V = IR$

capacitor  
 $V = \frac{1}{C} \int I dt$

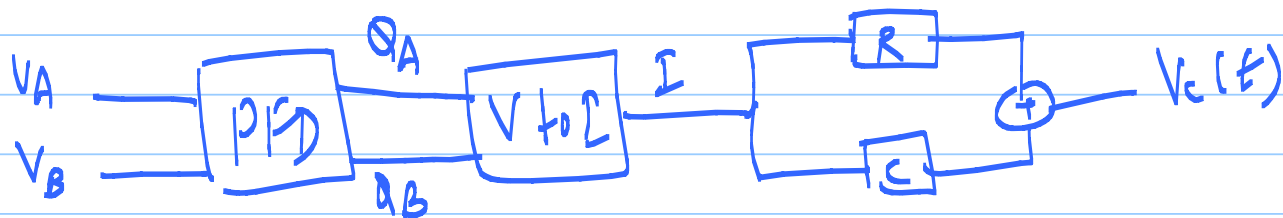

# Charge pump


$\theta_e > 0$        $\theta_e < 0$

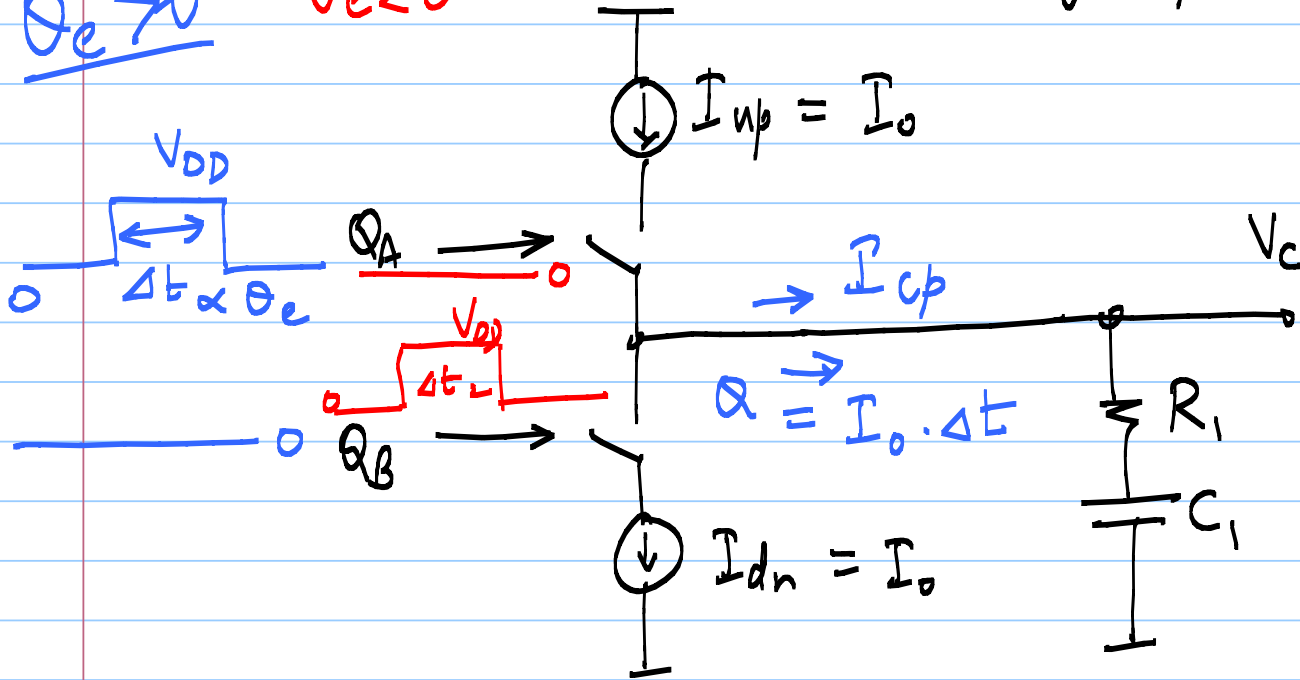

\*  $I_{cp}$  is a PWM current with avg. value  $\propto \theta_e$


PFD  
CP

Characteristic

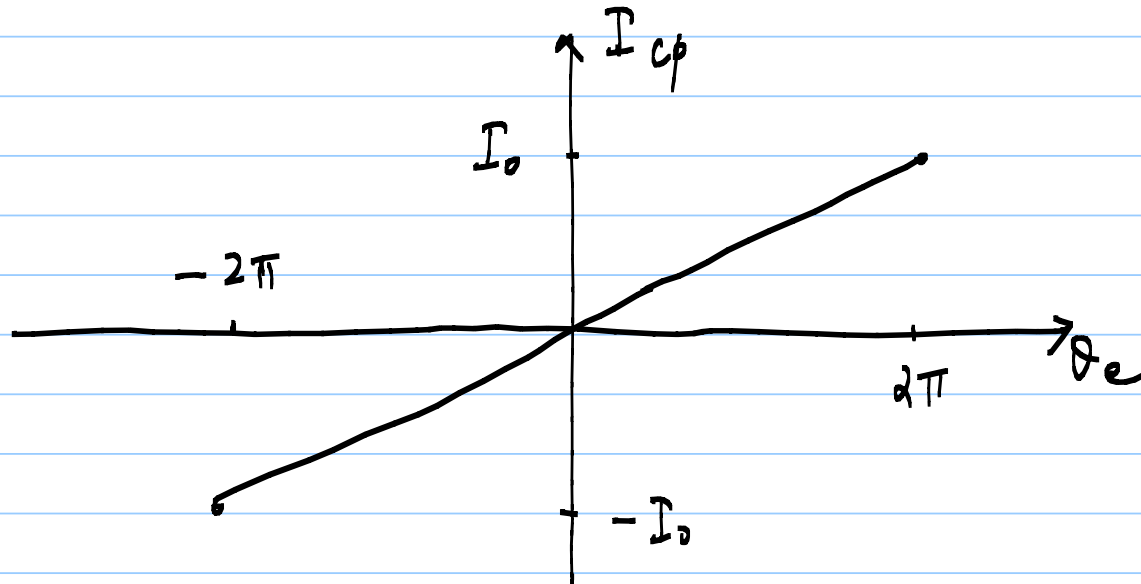


$$\text{gain} = \frac{I_0}{2\pi}$$




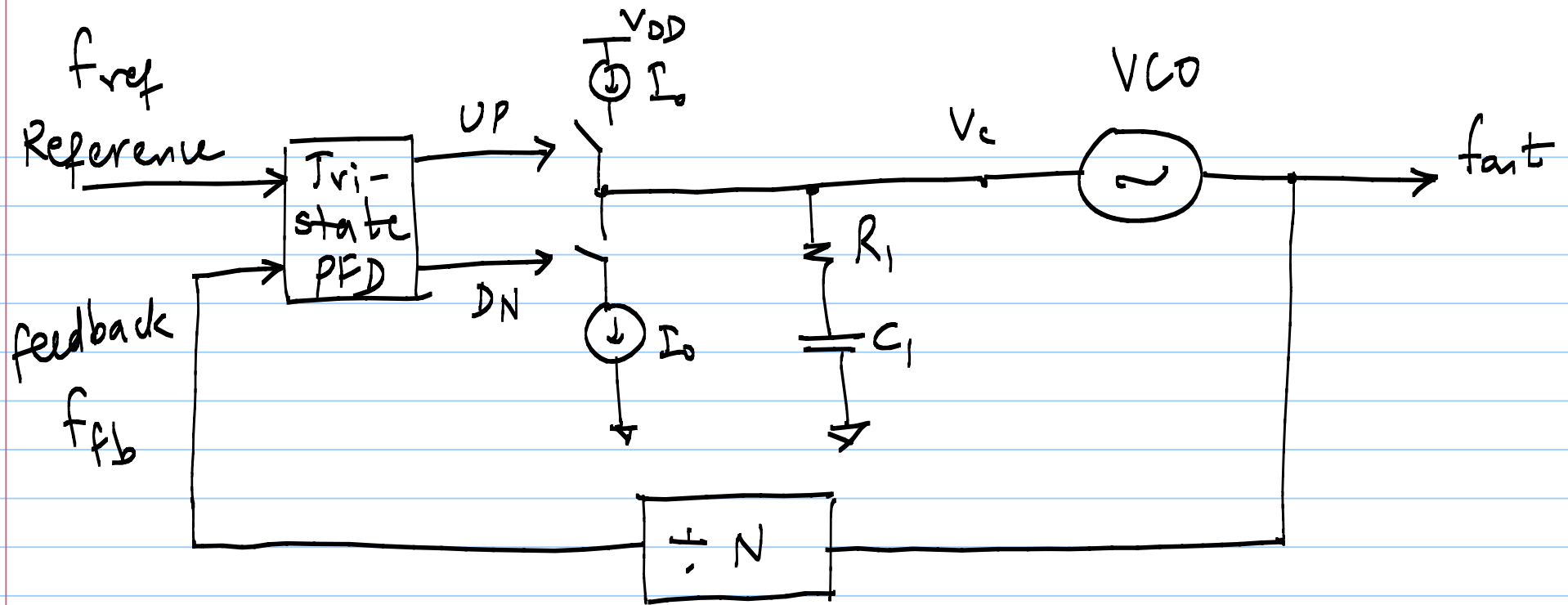




### LC-VCO

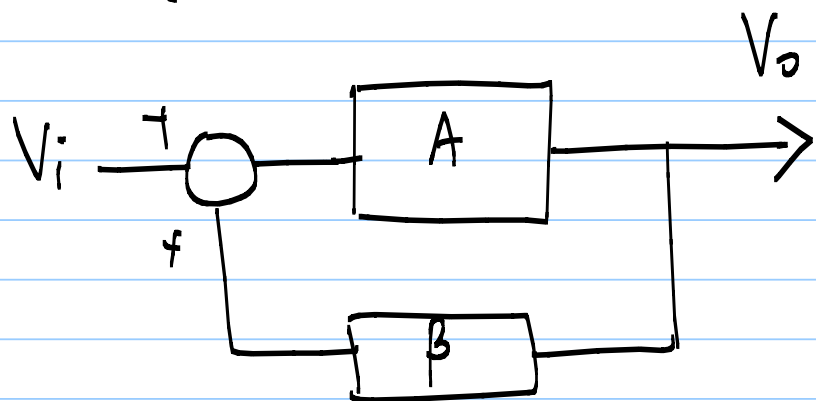


$$\left. \begin{array}{l} |L_A(j\omega)| \geq 1 \\ \angle L_A(j\omega) = 360^\circ \end{array} \right\} \text{instability}$$

for stable osc:  $|L_A(j\omega_0)| = 1$ ,  $\angle L_A(j\omega_0) = 360^\circ @ \omega_0$

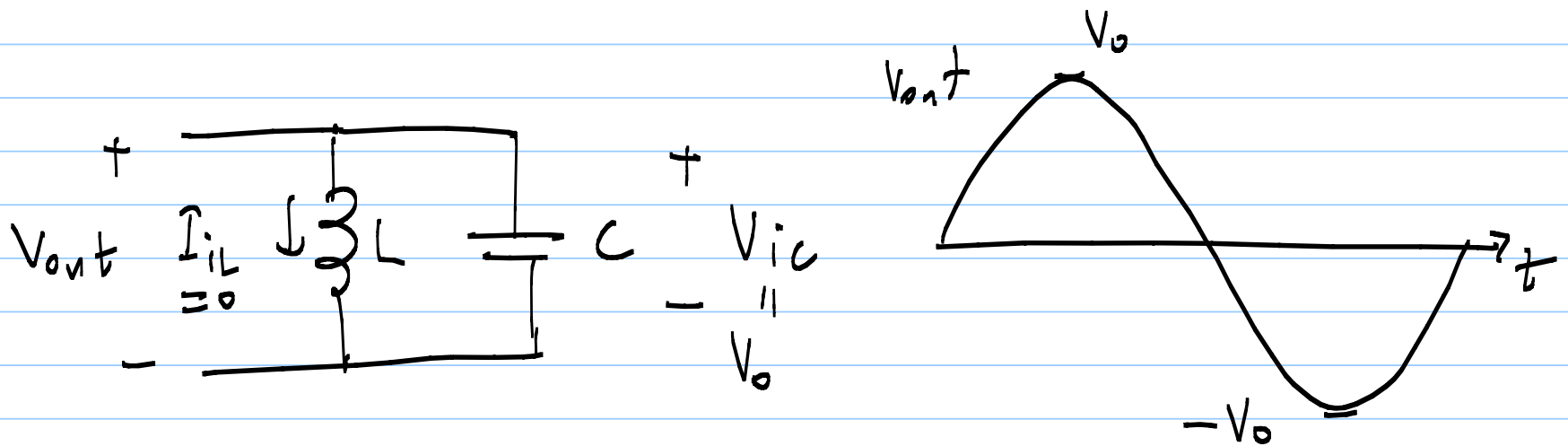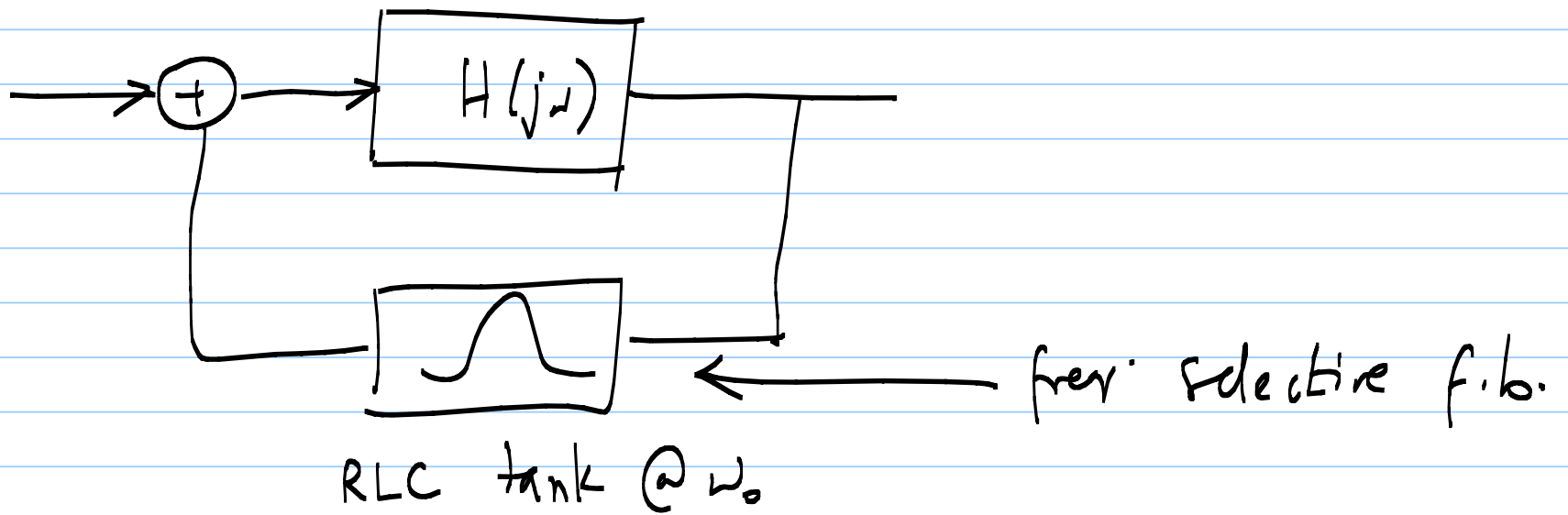

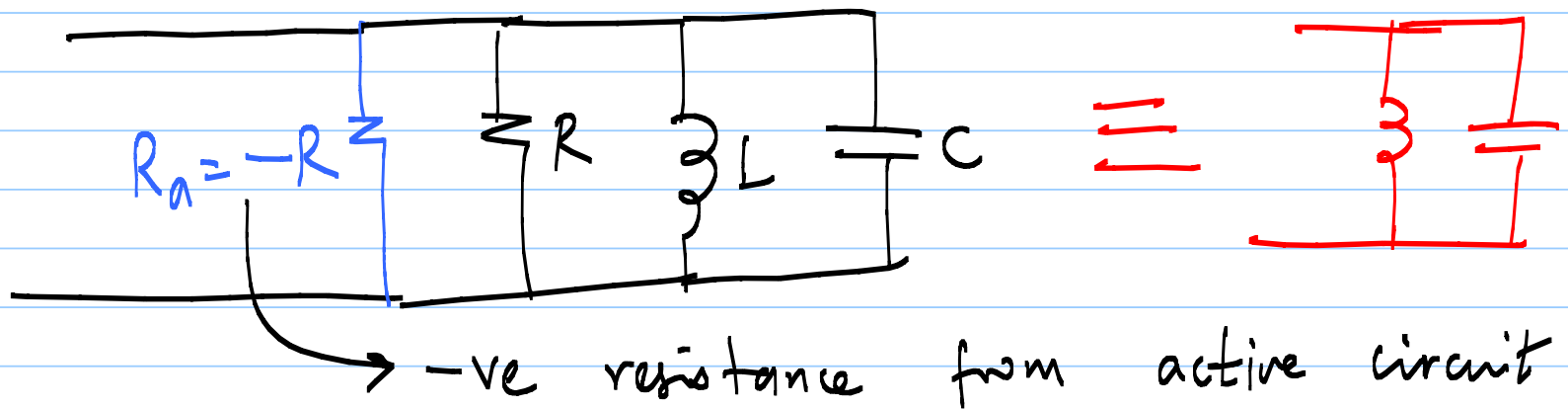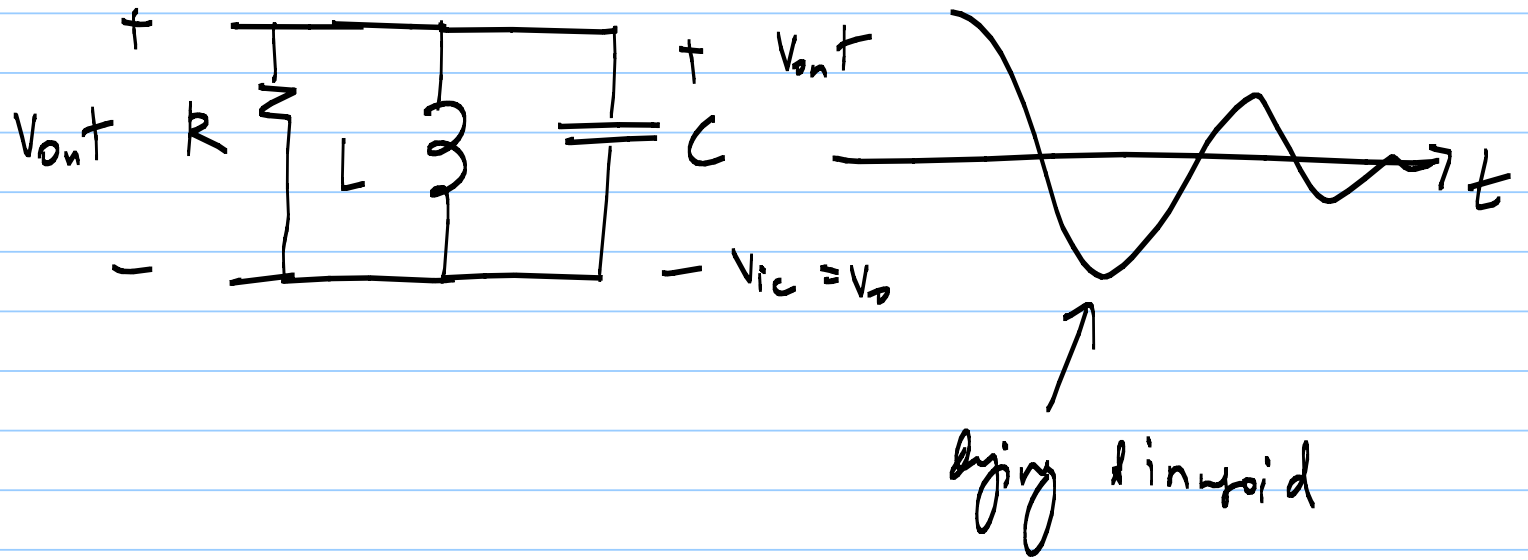


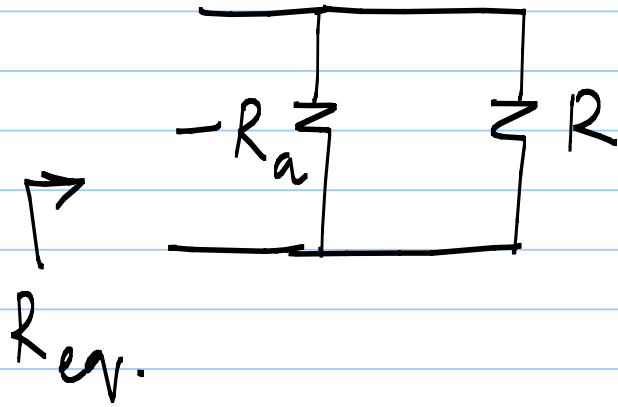

$$R_{eq.} = \frac{-R R_a}{R - R_a}$$


$$= \frac{R R_a}{R_a - R}$$

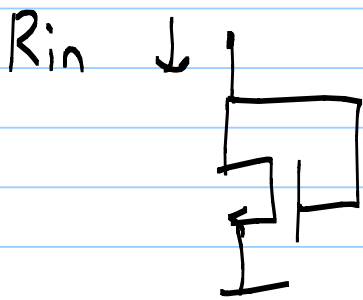- 1)  $R_a = R \Rightarrow R_{eq.} = \infty$  (ideal LC tank)
- 2)  $R_a > R \Rightarrow R_{eq.} > 0$  (dying oscillations)
- 3)  $R_a < R \Rightarrow R_{eq.} < 0$  (growing oscillations)




$$R_{in} = \frac{1}{g_m}$$

(-ve f.b.)

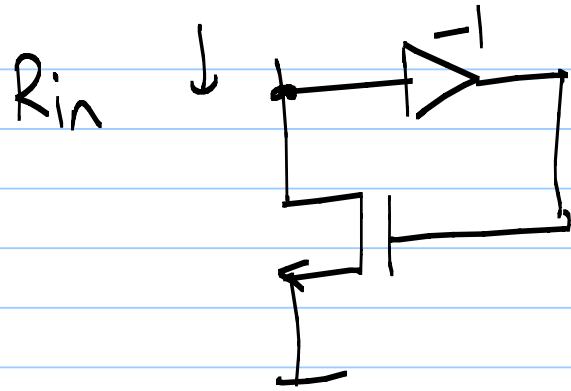


+ve f.b.

$$R_{in} = -\frac{1}{g_m} \{HW\}$$

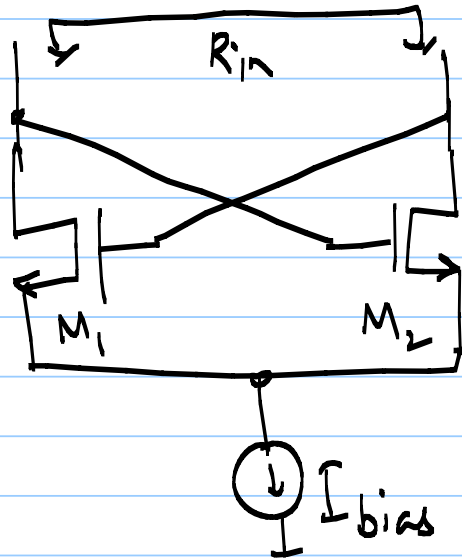

$$R_{in} = -\frac{2}{g_m}$$

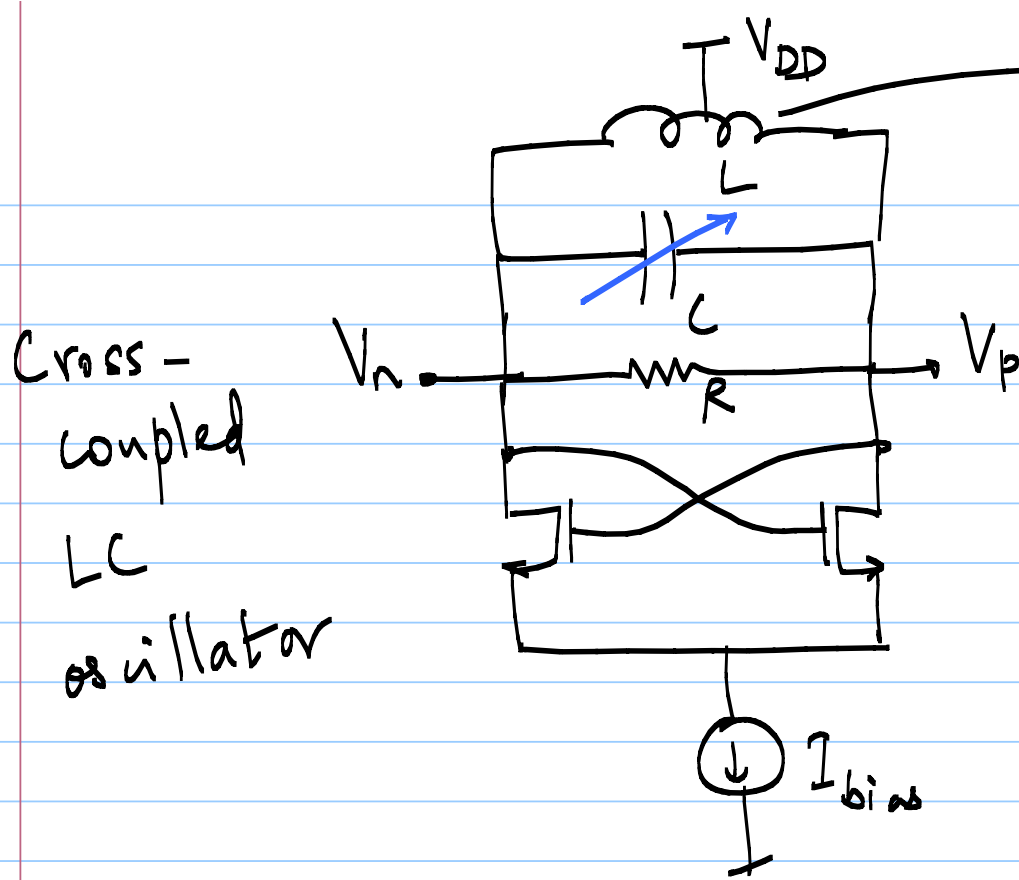

Spiral

In steady state,

$$|R| = \left| \frac{-2}{g_m} \right|$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

tuning C through  $V_c$   
(varactor)