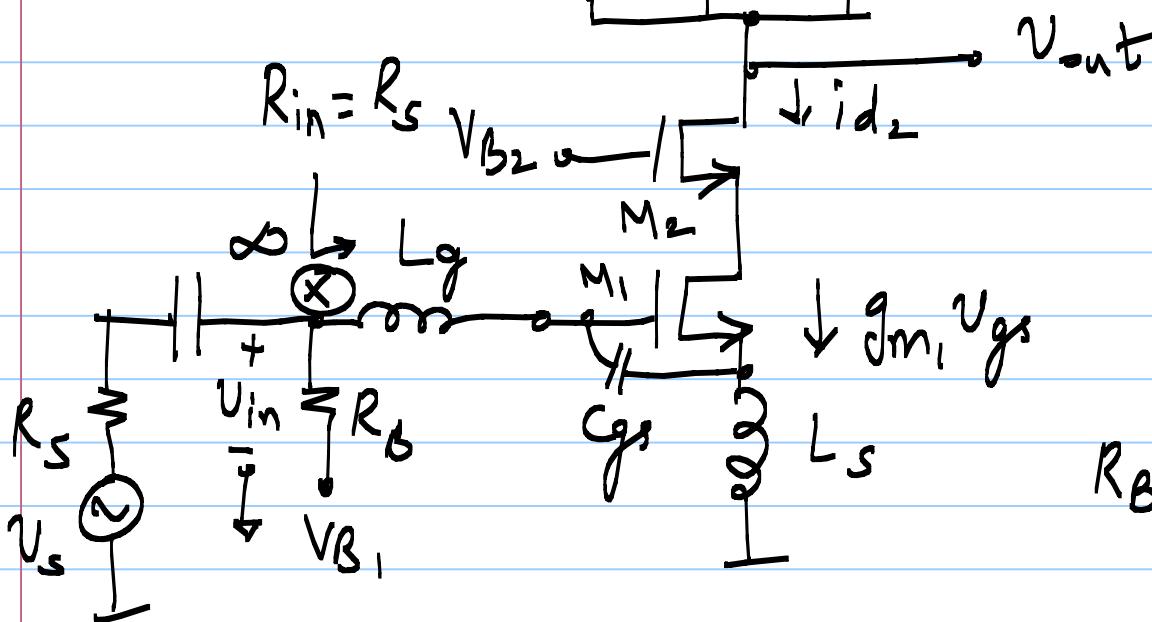


12/2/20


Lec 13




$$\omega_T L_s = R_{in} = R_s$$

$$V_{in} = \frac{V_s}{2}$$

Thevenin  
equivalent  
at X

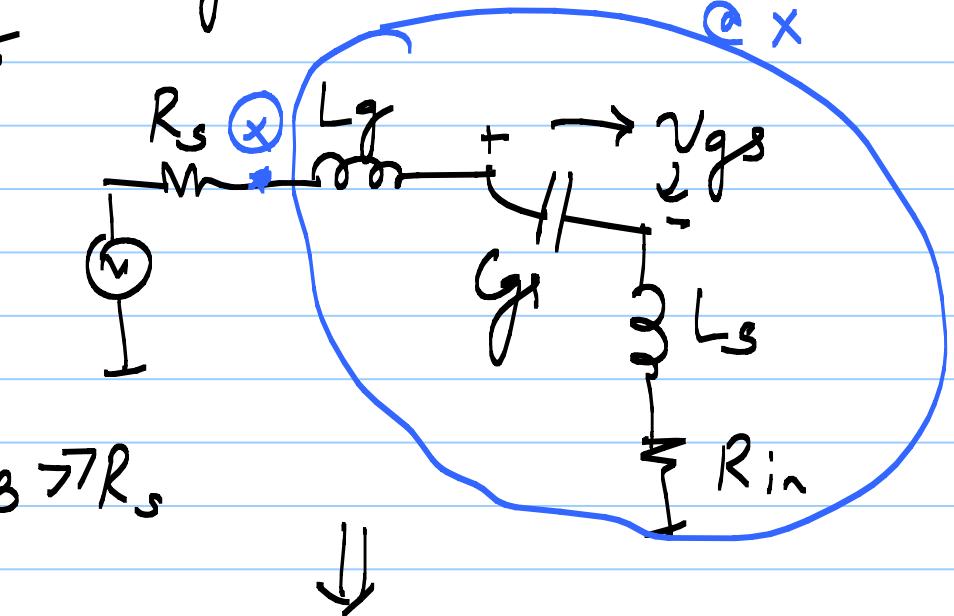
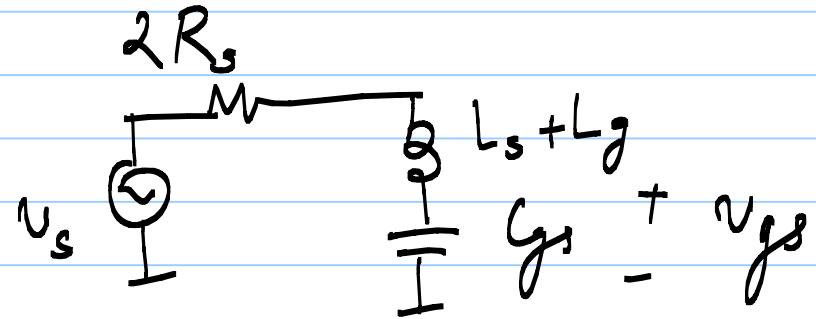
$$Q_{in} = \frac{1}{2R_s(\omega(g_s))} = \frac{\omega(L_s + L_g)}{2R_s}$$



$$v_{gs} = Q_{in} \cdot v_s = 2 Q_{in} \cdot v_{in}$$


$$i_{d_1} = g_m, v_{gs} = i_{d_2}$$

$$v_{out} = -i_{d_2} R_d = -g_m, R_d \cdot v_{gs}$$

$$\left| \frac{v_{out}}{v_s} \right| = g_m, R_d \cdot Q_{in}$$

passive voltage gain

$$\left| \frac{v_{out}}{v_{in}} \right| = 2 g_m, R_d \cdot Q_{in}$$

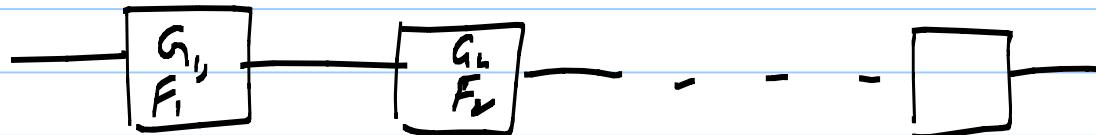


Large  $Q_{in} \Rightarrow$  large gain

↳ small  $g_s \rightarrow$  small  $\omega$ ,  
large  $I_{bias}$


↳ large  $\omega_T \rightarrow$  smaller  $L_s$

larger  $L_g$

NF should improve [Friis eq.]

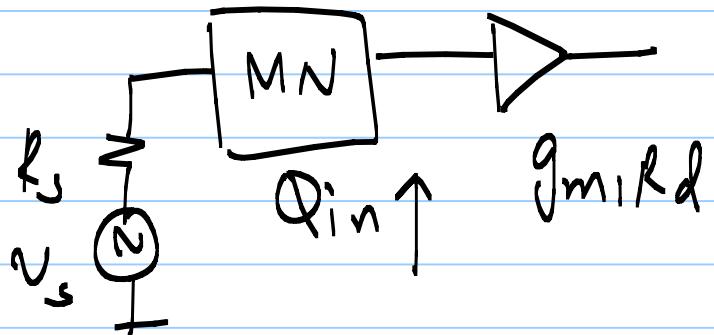

NF:

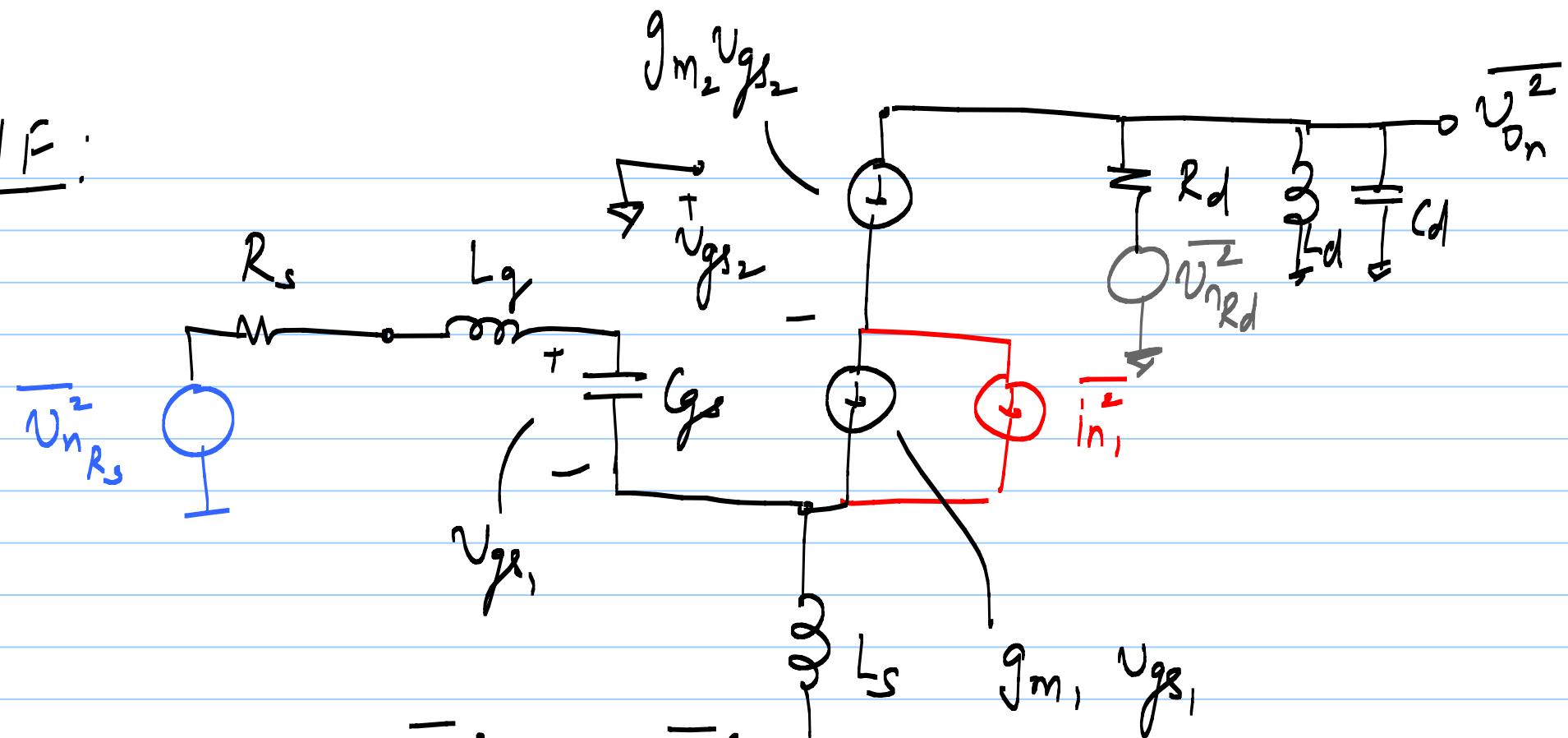

$$F = 1 + \frac{\bar{V}_{o_n}^2 M_1}{\bar{V}_{o_n}^2 R_s} + \frac{\bar{V}_{o_n}^2}{\bar{V}_{o_n}^2 R_1}$$

$$\frac{\bar{V}_{o_n}^2}{\Delta f} = \left| \frac{V_{out}}{V_{in}} \right|^2 \cdot \bar{V}_{n_{R_s}}^2 = Q_{in}^2 g_{m1}^2 R_d^2 \cdot 4kT R_s$$

$$\frac{\overline{v_{on}^2}_{Rd}}{\Delta f} = \frac{\overline{v_n^2}_{Rd}}{\Delta f} = 4kT R_d$$

$$\frac{\overline{v_{onM_1}^2}}{\Delta f} = ?$$


$\overline{i_{n_1}}$

$\overline{i_{n_2}}$

pair of correlated  
noise sources

$$\overline{v_{onM_1}} \text{ due to } \overline{i_{n_1}} = -\overline{i_{n_1}} \cdot R_d$$
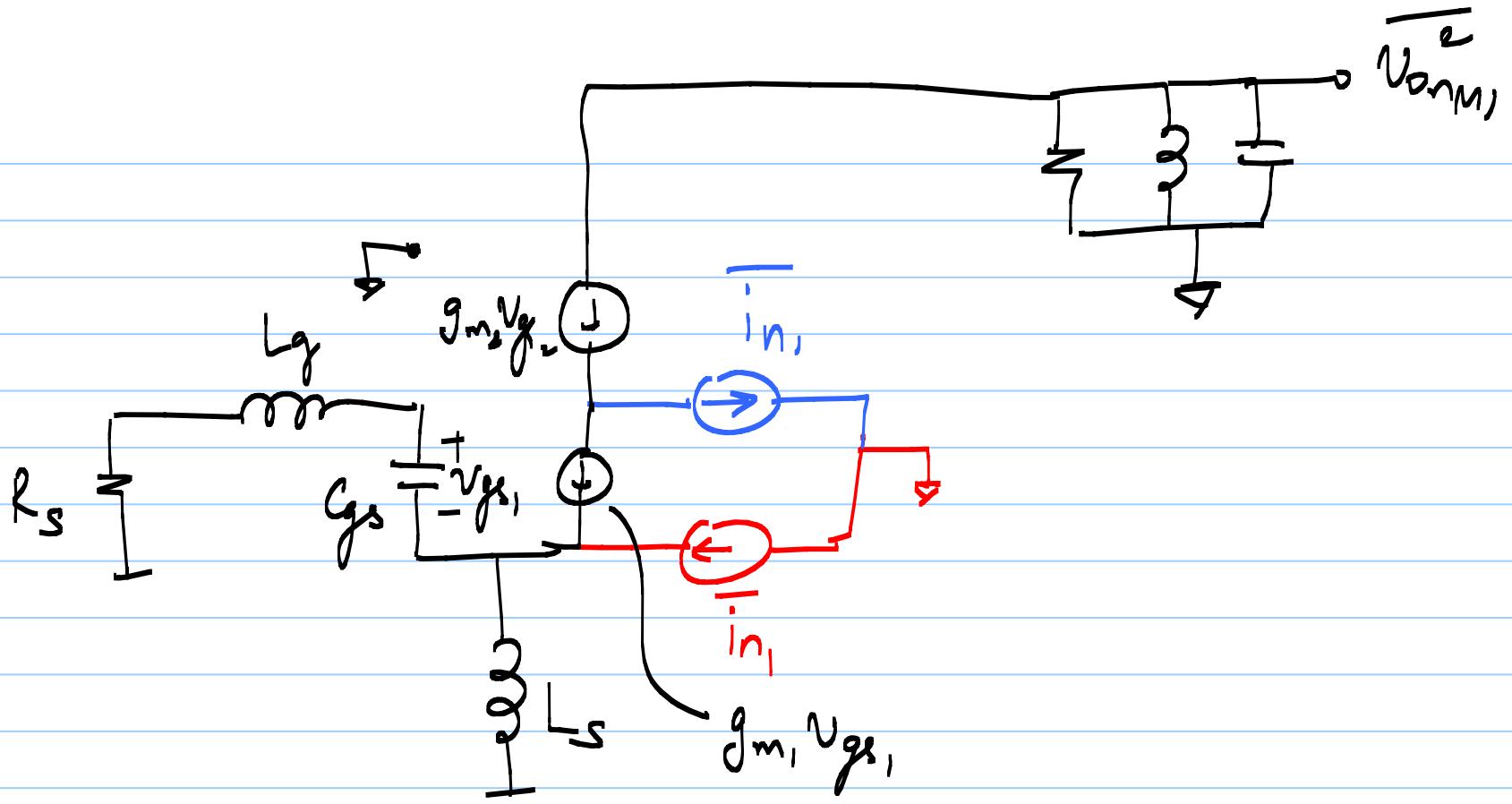
$$\overline{v_{onM_1}} \text{ due to } \overline{i_{n_2}} =$$



$$\begin{aligned} \overline{v_{onM_1}} &= \left[ \frac{R_d}{1 + R_d g_m} \right]^2 \cdot \overline{i_{n_1}}^2 \quad \cancel{\text{?}} \\ &= \left[ \overline{i_{n_1}} \times (g_m R_s + 1) \cdot R_d - \overline{i_{n_1}} \cdot R_d \right]^2 ?? \end{aligned}$$