
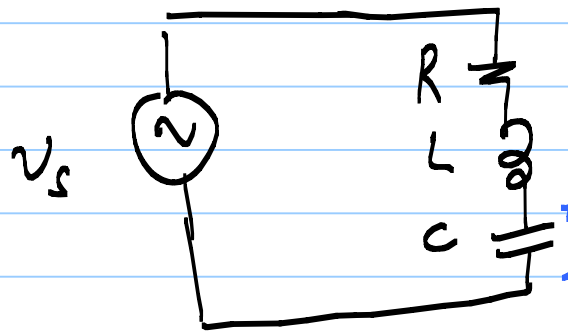


19/2/20

Lec 15

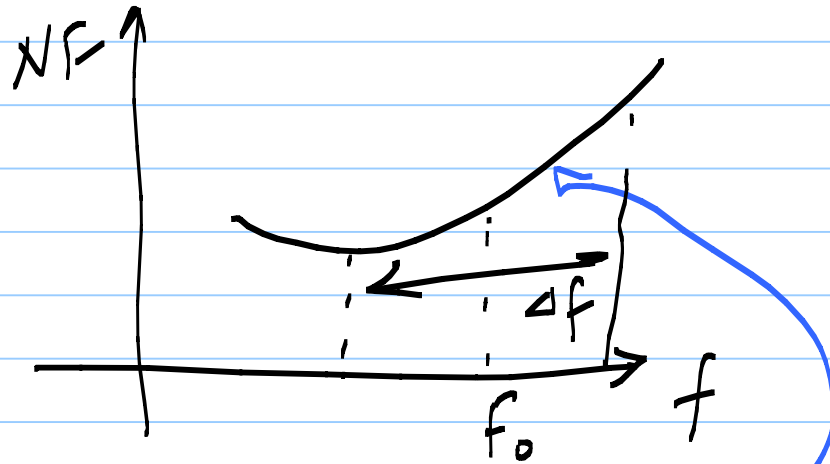

$$Q_{\omega_0} = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R}$$

If you go outside band:


$v_s \downarrow$

effect of R_d noise

Induced gate noise: (See 2011 lectures)

- * depends on δ (empirical parameter)
- * coloured noise
- * \uparrow with operating freq.
- * partially correlated with drain thermal noise
- * depends on C_{gs} & r_g
- * $|S_{11}|_{min}$ & f_{min} need not occur at same frequency

LNA Design procedure

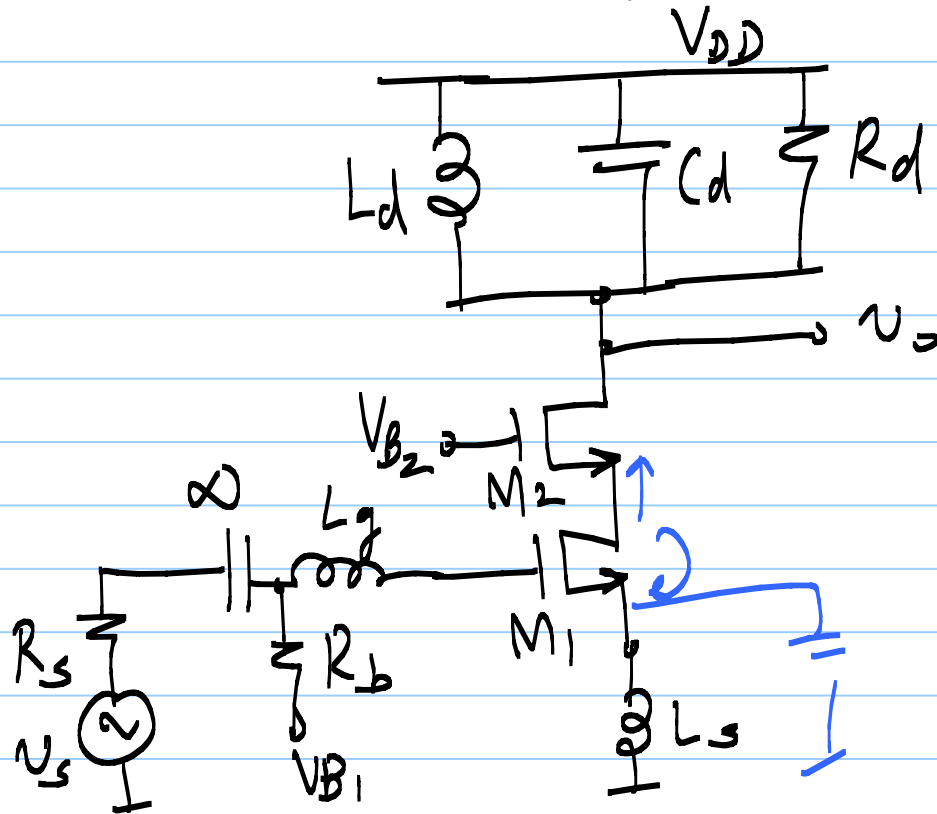

@ drain :

$$f_0 = \frac{1}{2\pi \sqrt{L_d C_d}}$$

larger R_d

- larger gain
- lower NF
- should meet LNA BW requirements

1) Choose L_d , C_d & R_d to set f_0 and Q_{drain}

$$C_d = C_{\text{par } M_2} + C_{\text{load}} + C_{\text{variable}}$$

2) Set Q_{in} based on BW requirement

$$Q_{\text{in}} = \frac{1}{2W_0 C_{gs} R_s}$$

3) Set $L = L_{\text{min}}$

Set W based on C_{gs} from (2)

$$4) \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_1 ; V_{B2} = V_{DD}$$

5)

$$\omega_T L_S = R_S$$

maximise ω_T to minimise NF

$$\omega_T = \left. \begin{array}{l} \frac{g_m}{C_{gs}} \propto \sqrt{W} \\ \frac{g_m}{C_{gs}} \propto W \end{array} \right\} \begin{array}{l} \text{minimise } W \\ L = L_{\min} \end{array}$$

$\propto \sqrt{I} \Rightarrow$ maximise I_{bias}

maximise $(V_{as} - V_T)$

e.g. $f_T = 300 \text{ GHz}$

$$L_S = \frac{R_S}{2\pi f_T} = 26.5 \text{ pH}$$

L_S of $\sim 100 \text{ pH}$ can be reliably achieved with good accuracy at a few GHz

⇒ choose $f_T \approx 75 \text{ GHz}$

6) Choose L_g for $f_0 = \frac{1}{2\pi \sqrt{C_{gs}(L_s + L_g)}}$

7) Set $I_{bias} = \text{max allowed current}$