

EE6320 Homework 5: Due Sunday 02/05/2021

1. A class-A power amplifier is shown in figure 1 below. The device bias current is chosen to be exactly equal to the peak signal current so that the transistor just touches cut-off at the negative end of the input signal cycle and just touches linear region at the positive end of the input signal cycle. Neglect the saturation voltage $V_{D,SAT}$ of the transistor in relation to V_{DD} (so that the drain output voltage V_X swings between 0 and V_{DD}). Assume that L_1 is very large and that the matching network is ideal.

(a) Prove that the drain efficiency of the class-A PA is exactly 50%

(b) Prove that other (“wasted”) 50% of the supply power is dissipated in M_1 .

2. A cascoded class-A power amplifier is shown in figure 2 below. Assume that M_1 and M_2 are biased such that M_1 is biased at the edge of triode region. Determine the maximum possible drain efficiency. In this problem, do not ignore the saturation voltage $V_{D,SAT}$ of the transistors. Assume that L_1 is very large and that the matching network is ideal.

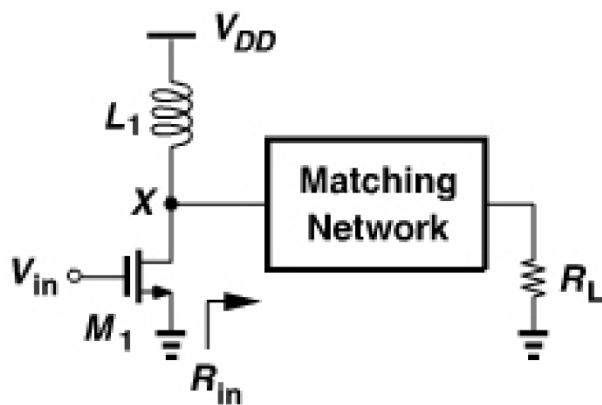


Figure 1

 


Figure 2