

HW7 solutions (draft)

Q1)

(a)

$$\begin{aligned} X(s) &= \frac{s+2}{s^2+8s+15} \\ &= \frac{s+2}{(s+3)(s+5)} \end{aligned}$$

Separating the terms in $X(s)$ using partial fractions

$$\begin{aligned} X(s) &= \frac{1}{2} \left(\frac{3}{s+5} - \frac{1}{s+3} \right) \\ \implies x(t) &= \frac{1}{2} \left(3e^{-5t} - e^{-3t} \right) u(t) \end{aligned}$$

(b)

$$X(s) = \frac{s+1}{(s+2)^2(s+3)}$$

Using partial fractions on $X(s)$

$$X(s) = \frac{A}{s+3} + \frac{B}{s+2} + \frac{C}{(s+2)^2}$$

Solving for A , B and C ,

$$X(s) = \frac{-2}{s+3} + \frac{2}{s+2} + \frac{-1}{(s+2)^2}$$

Using the differentiation property of Laplace transform,

$$\begin{aligned} t \times y(t) &\longleftrightarrow -\frac{dY(s)}{ds} \\ te^{-2t} &\longleftrightarrow \frac{1}{(s+2)^2} \end{aligned}$$

$$\implies x(t) = \left(-2e^{-3t} + 2e^{-2t} - te^{-2t} \right) u(t)$$

(c)

$$\begin{aligned} X(s) &= \frac{2s^2 + s + 1}{s(s+2)} \\ &= 2 - \frac{3s-1}{s(s+2)} \end{aligned}$$

Using partial fractions to separate $X(s)$

$$\begin{aligned} X(s) &= 2 - \frac{1}{2} \left(\frac{-1}{s} + \frac{7}{s+2} \right) \\ \Rightarrow x(t) &= 2\delta(t) + \frac{u(t)}{2} - \frac{7}{2}e^{-2t}u(t) \end{aligned}$$

(d)

$$X(s) = \frac{2s+1}{(s+2)(s^2+1)^2}$$

Using partial fractions to split $X(s)$

$$X(s) = \frac{A}{s+2} + \frac{Bs+C}{s^2+1} + \frac{Ds+E}{(s^2+1)^2}$$

Solving for A, B, C, D and E ,

$$X(s) = \frac{-3}{25(s+2)} + \frac{3s-6}{25(s^2+1)} + \frac{3s+4}{5(s^2+1)^2} \quad (1)$$

Using the differentiation property of Laplace transform,

$$\begin{aligned} t \times y(t) &\longleftrightarrow \frac{dY(s)}{ds} \\ t \sin(t) &\longleftrightarrow -\frac{d}{ds} \left(\frac{1}{s^2+1} \right) = \frac{2s}{(s^2+1)^2} \end{aligned} \quad (2)$$

$$\begin{aligned} \text{Similarly } t \cos(t) &\longleftrightarrow -\frac{d}{ds} \left(\frac{s}{s^2+1} \right) = \frac{1}{s^2+1} - \frac{2}{(s^2+1)^2} \\ \Rightarrow t \cos(t) - \sin(t) &\longleftrightarrow -\frac{2}{(s^2+1)^2} \end{aligned} \quad (3)$$

Using the results (2) and (3) in (1),

$$\begin{aligned} x(t) &= \left[\frac{-3}{25}e^{-2t} + \frac{3}{25}\cos(t) - \frac{6}{25}\sin(t) + \frac{3}{10}t\sin(t) - \frac{2}{5}t\cos(t) + \frac{2}{5}\sin(t) \right] u(t) \\ &= \left[\frac{-3}{25}e^{-2t} + \frac{3}{25}\cos(t) + \frac{4}{25}\sin(t) + \frac{3}{10}t\sin(t) - \frac{2}{5}t\cos(t) \right] u(t) \end{aligned}$$

(e)

$$\begin{aligned} X(s) &= \frac{1}{10^4 s^2 + 10^2 s + 1} \\ &= \frac{1}{10^4 (s^2 + 10^{-2} s + 10^{-4})} \\ &= \frac{1}{10^4 \left[\left(s + \frac{1}{200} \right)^2 + \left(\frac{\sqrt{3}}{200} \right)^2 \right]} \\ &= \frac{200}{10^4 \times \sqrt{3}} \frac{\frac{\sqrt{3}}{200}}{\left[\left(s + \frac{1}{200} \right)^2 + \left(\frac{\sqrt{3}}{200} \right)^2 \right]} \end{aligned}$$

Using the relation,

$$\begin{aligned} e^{-\alpha t} \sin(\omega t) u(t) &\longleftrightarrow \frac{\omega}{(s + \alpha)^2 + \omega^2} \\ x(t) &= \frac{e^{\left(\frac{-t}{200}\right)} \sin\left(\frac{\sqrt{3}t}{200}\right)}{50\sqrt{3}} u(t) \end{aligned}$$

Q2)

(a)

Using final value theorem, we can get $v_c(0^+)$ as

$$\begin{aligned} v_c(0^+) &= \lim_{s \rightarrow \infty} s V_c(s) \\ &= \lim_{s \rightarrow \infty} s \frac{as + b}{s^2 + cs + d} \\ &= \lim_{s \rightarrow \infty} \frac{as^2 + bs}{s^2 + cs + d} \\ &= \lim_{s \rightarrow \infty} \frac{a + \frac{b}{s}}{1 + \frac{c}{s} + \frac{d}{s^2}} \\ &= a \end{aligned}$$

(b)

Since $i(t) = C \frac{dV_c}{dt}$, we get $I(s) = CsV_c(s) - Cv_c(0)$.

$$\begin{aligned} I(s) &= Cs \frac{as + b}{s^2 + cs + d} - Ca \\ &= \frac{sC(b - ac) - Cad}{s^2 + cs + d} \end{aligned}$$

Using initial value theorem,

$$\begin{aligned} i(0^+) &= \lim_{s \rightarrow \infty} s I(s) \\ &= \lim_{s \rightarrow \infty} \frac{s^2 C(b - ac) - sCad}{s^2 + cs + d} \\ &= \lim_{s \rightarrow \infty} \frac{C(b - ac) - \frac{Cad}{s}}{1 + \frac{c}{s} + \frac{d}{s^2}} \\ &= C(b - ac) \end{aligned}$$

(c)

Since $v_L(t) = L \frac{di}{dt}$, we get $V_L(s) = L (sI(s) - i(0))$.

$$\begin{aligned} I(s) &= L \left(\frac{s^2 C(b - ac) - sCad}{s^2 + cs + d} - C(b - ac) \right) \\ &= LC \left(\frac{s(ac^2 - bc - ad) - bd + acd}{s^2 + cs + d} \right) \end{aligned}$$

Using initial value theorem,

$$\begin{aligned} v_L(0^+) &= \lim_{s \rightarrow \infty} sV_L(s) \\ &= \lim_{s \rightarrow \infty} LC \left(\frac{s^2(ac^2 - bc - ad) + s(-bd + acd)}{s^2 + cs + d} \right) \\ &= \lim_{s \rightarrow \infty} LC \left(\frac{(ac^2 - bc - ad) + \frac{(-bd + acd)}{s}}{1 + \frac{c}{s} + \frac{d}{s^2}} \right) \\ &= LC(ac^2 - bc - ad) \end{aligned}$$


Q3)

At steady state, capacitor is open and the two resistances are in parallel (and $R_{eq} = 1 || (1/2) = 1/3$), and

$$v_2 = \frac{I_0}{3}$$

This means, $v_c(0^-) = I_0/3$.

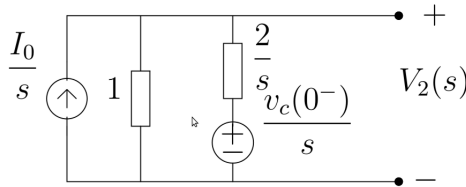At $t = 0$, the switch K is opened. The new circuit in the transform domain is Now,




$$\begin{aligned} \frac{V_2(s) - \frac{V_c(0^-)}{s}}{2/s} + \frac{V_2(s)}{1} &= \frac{I_0}{s} \\ V_2(s) \left(\frac{s}{2} + 1 \right) &= \frac{I_0}{s} + \frac{V_c(0^-)}{2} \\ V_2(s) \left(\frac{s+2}{2} \right) &= I_0 \left(\frac{6+s}{6s} \right) = \frac{I_0}{3} \left[\frac{3}{s} - \frac{2}{s+2} \right] \end{aligned}$$

Therefore, $v_2(t) = I_0 \left(1 - \frac{2}{3}e^{-2t} \right) u(t)$ whose values agree with the intuition for the initial and final times.

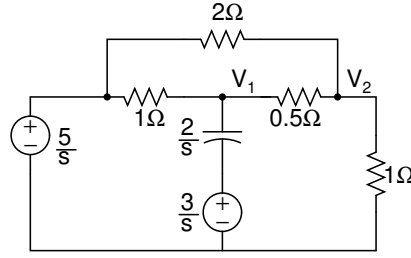Q4)

At $t = 0^-$, the capacitor holds a potential same as that of the drop between the 0.5Ω and 1Ω resistors. $v_c(0^-) = \frac{0.5+1}{1+0.5+1} \times 5 = 3V$.

At $t = 0$, when the switch K is closed the circuit in transform domain becomes:



Using KCL at node V_1 ,

$$\frac{V_1 - \frac{5}{s}}{1} + \frac{V_1 - V_2}{0.5} + \frac{V_1 - \frac{3}{s}}{\frac{2}{s}} = 0 \quad (4)$$

$$\Rightarrow V_2 = -\frac{10 + 3s}{4} + \left(\frac{s + 6}{4}\right) V_1 \quad (5)$$

Using KCL for node V_2 ,

$$\frac{V_2 - \frac{5}{s}}{2} + \frac{V_2 - V_1}{0.5} + \frac{V_2}{1} = 0$$


$$\Rightarrow V_2 = \frac{5}{7s} + \frac{4}{7} V_1 \quad (6)$$

From equations (5) and (6),

$$V_1(s) = \frac{3(s + \frac{30}{7})}{s(s + \frac{26}{7})}$$

$$I_c(s) = \frac{V_1(s) - \frac{3}{s}}{\frac{2}{s}} = \frac{\frac{6}{7}}{s + \frac{26}{7}}$$
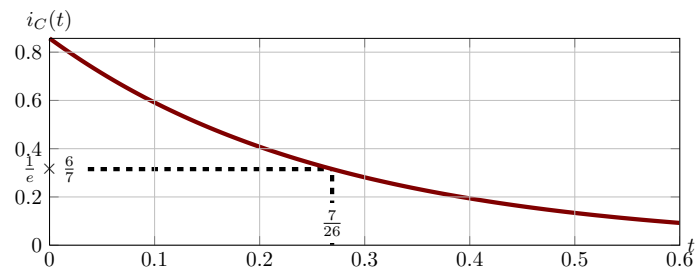
$$\Rightarrow i_c(t) = \frac{6}{7} e^{-\frac{26t}{7}} u(t)$$



Therefore the time constant is $\frac{7}{26}$.

Q5)

At steady state,

$$i(t) = \frac{100}{|Z|} \sin 314t - \theta$$

where $Z = |Z| \angle \theta$ where $|Z| = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$ and $\theta = \tan^{-1} \frac{(\omega L - \frac{1}{\omega C})}{R}$ and $R = 10^3 \Omega$, $L = 1 \text{ H}$, $C = 1/2 \mu\text{F}$ and $\omega = 314 \text{ rad/s}$. Then, $Z \approx 6137 \angle -80^\circ$.

When the switch is closed at $t = 0$, $i_L(0^-) = i(t = 0)$ and $v_C(0^-) = v_C(t)|_{t=0} = \frac{100}{|Z| \cdot \omega C} \sin 314t - \theta - 90^\circ|_{t=0}$. So, $i_L(0^-) = 0.016$ A and $v_C(0^-) = -18.02$ V. The transformed circuit is as shown below:

Using $\omega_0^2 = \frac{1}{LC} \approx 1414$ rad/s,

$$\begin{aligned} I(s) \left(sL + \frac{1}{sC} \right) &= \frac{100\omega}{s^2 + \omega^2} + Li_L(0^-) - \frac{v_C(0^-)}{s} \\ \Rightarrow I(s) &= \frac{100s\omega}{L(s^2 + \omega^2)(s^2 + \omega_0^2)} + \frac{i_L(0^-)s}{(s^2 + \omega_0^2)} - \frac{v_C(0^-)}{L(s^2 + \omega_0^2)} \\ &= \frac{100\omega}{L(\omega_0^2 - \omega^2)} \left[\frac{s}{s^2 + \omega^2} - \frac{s}{s^2 + \omega_0^2} \right] + \frac{i_L(0^-)s}{(s^2 + \omega_0^2)} - \frac{v_C(0^-)}{L(s^2 + \omega_0^2)} \end{aligned}$$


$$\begin{aligned} \Rightarrow i(t) &= A \cos \omega t - B \cos \omega_0 t + i_L(0^-) \cos \omega_0 t - \frac{v_C(0^-)}{L\omega_0} \sin \omega_0 t \\ &= 0.0165 \cos \omega t - 0.0165 \cos \omega_0 t + 0.016 \cos \omega_0 t + 0.012 \sin \omega_0 t \end{aligned}$$

for $t > 0$. Notice that there are no decaying terms as there is no resistive element in the circuit for all $t > 0$. Check to see if $B = i_L(0^-)$ in which case there will be some cancellation.

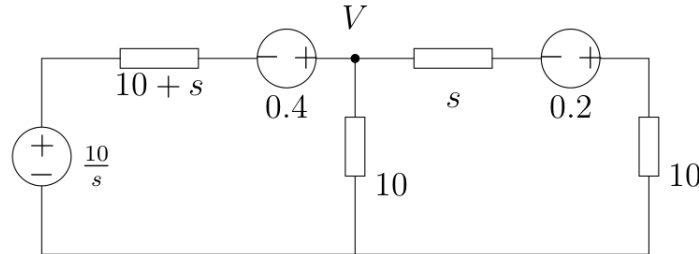Q6)

At steady-state, with the inductances acting as short-circuits, $i_{L_1} = 0.4$ A and $i_{L_2} = 0.2$ A.

At $t = 0$, the 10Ω resistance is shorted. The transform of the resulting circuit is shown below.



Applying KCL at node V,

$$\begin{aligned} \frac{V - \frac{10}{s} - 0.4}{10 + s} + \frac{V}{10} + \frac{V + 0.2}{10 + s} &= 0 \\ V \left[\frac{1}{10 + s} + \frac{1}{10} + \frac{1}{10 + s} \right] &= \frac{0.2(s + 50)}{s(s + 10)} \\ \Rightarrow V &= \frac{2(s + 50)}{s(s + 30)} = \frac{\frac{10}{3}}{s} - \frac{\frac{4}{3}}{s + 30} \end{aligned}$$

And, to compute the current,

$$\begin{aligned} I_R(s) &= \frac{V + 0.2}{10 + s} = \frac{0.2s^2 + 8s + 100}{s(s + 10)(s + 30)} \\ &= \frac{\frac{1}{3}}{s} - \frac{\frac{1}{5}}{s + 10} + \frac{\frac{1}{15}}{s + 30} \\ \Rightarrow i_R(t) &= \left(\frac{1}{3} - \frac{1}{5}e^{-10t} + \frac{1}{15}e^{-30t} \right) u(t) \end{aligned}$$

which checks out OK with initial and final currents.

Q7)

Writing KVL around the 2 loops;

$$v_1(t) = L_1 \frac{di_1(t)}{dt} + v_a(t) + M \frac{di_2(t)}{dt} \quad (7)$$

$$v_a(t) = L_2 \frac{di_2(t)}{dt} + M \frac{di_1(t)}{dt} \quad (8)$$

$$i_1(t) - i_2(t) = C \frac{dv_a(t)}{dt} \quad (9)$$

Substitute the component values and substitute $j\omega$ for differentiation since it is sinusoidal steady state.

$$v_1(t) = j\omega i_1(t) + v_a(t) + 0.25j\omega i_2(t) \quad (10)$$

$$v_a(t) = j\omega i_2(t) + 0.25j\omega i_1(t) \quad (11)$$

$$i_1(t) - i_2(t) = j\omega v_a(t) \quad (12)$$

Therefore,

$$v_a(t) = \frac{v_1(t)}{2 - 0.75\omega^2} \quad (13)$$

Since the input signal has a frequency of 1 rad/s ,

$$v_a(t) = 1.6\cos(t) \quad (14)$$

Q8


Given the values $L = 10mH$, $C = 100\mu F$ and $R = 10k\Omega$
Initial conditions are 0.

In the s-domain,

$$L \rightarrow sL$$

$$C \rightarrow \frac{1}{sC}$$

$$R \rightarrow R$$

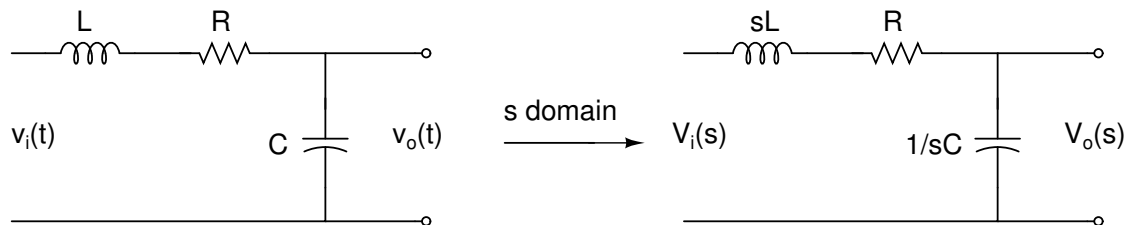

Applying voltage divider rule to the circuit $V_o(s)$ will be

$$V_o(s) = \frac{\frac{1}{sC}}{R + sL + \frac{1}{sC}} V_i(s)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{s^2LC + sRC + 1}$$

Substituting RLC values, we get

$$\frac{V_o(s)}{V_i(s)} = \frac{10^6}{s^2 + 10^6 s + 10^6}$$