

EE5311- Digital IC Design

Module 3 - The Inverter

Janakiraman V

Assistant Professor
Department of Electrical Engineering
Indian Institute of Technology Madras
Chennai

September 3, 2018


Learning Objectives

- ▶ Explain the functioning of a CMOS inverter
- ▶ Explain the Voltage Transfer Characteristics of an inverter
- ▶ Derive an expression for the trip point of an inverter
- ▶ Derive an expression for the delay of an inverter driving a load
- ▶ Derive expressions for Static, Dynamic and Short Circuit power of an inverter.

Outline

- ▶ Switch Model
- ▶ Transfer Characteristics
- ▶ Switching Threshold
- ▶ Noise Margin
- ▶ Supply Voltage Scaling
- ▶ Propagation Delay
- ▶ Power
 - ▶ Dynamic
 - ▶ Short circuit
 - ▶ Leakage

Inverters - Robust Configuration

 

- ▶ Pull down to *GND* with NMOS
- ▶ Pull up to V_{DD} with PMOS

Load Line

 


Figure: The CMOS Inverter

$$I_{DSp} = -I_{DSn}$$

$$V_{GSn} = V_{in}$$

$$V_{GSp} = V_{in} - V_{DD}$$

$$V_{DSn} = V_{out}$$

$$V_{DSp} = V_{out} - V_{DD}$$

Load Line

 


Figure: Solid lines- NMOS, Dashed lines - PMOS

Voltage Transfer Characteristics

 


Figure: VTC of a CMOS Inverter

Region	NMOS	PMOS
1	Off	Lin
2	Sat	Lin
3	Sat	Sat
4	Lin	Sat
5	Lin	Off

Switching Threshold

 


Figure: Switching Threshold

- ▶ Both NMOS and PMOS are in saturation
- ▶ Assume velocity saturation

Switching Threshold

$$I_{DSp} = -I_{DSn}$$

$$V_{GSn} = V_{in}$$

$$V_{GSp} = V_{in} - V_{DD}$$

$$V_{DSn} = V_{out}$$

$$V_{DSp} = V_{out} - V_{DD}$$

$$V_{in} = V_{out}$$

- ▶ Both NMOS and PMOS are in saturation
- ▶ Assume velocity saturation

Switching Threshold

Ignoring channel length modulation

$$I_{DSn} = k'_n \frac{W_n}{L} \left(V_M - V_{Tn} - \frac{V_{DSATn}}{2} \right) V_{DSATn}$$

$$I_{DSP} = k'_p \frac{W_p}{L} \left(V_M - V_{DD} - V_{Tp} - \frac{V_{DSATp}}{2} \right) V_{DSATp}$$

$$V_M = \frac{V_{Tn} + \frac{V_{DSATn}}{2} + r(V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2})}{1+r}$$

$$r = \frac{k'_p (W_p/L) V_{DSATp}}{k'_n (W_n/L) V_{DSATn}} = \frac{W_p v_{satp}}{W_n v_{satn}}$$

$$V_M \approx \frac{r}{r+1} V_{DD}$$

Switing Threshold

 


Figure: VTC Trip Point

Ratio of $\frac{W_p}{W_n}$ determines V_M

Switing Threshold Without Velocity Saturation

$$V_M = \frac{V_{Tn} + r(V_{DD} + V_{Tp})}{1 + r}$$

$$r = \sqrt{\frac{-k_p}{k_n}}$$

Left as an exercise

Noise Margin

 


Figure: Noise Margin of a CMOS Inverter

- ▶ Logic levels from the driver should be recognized by the load
- ▶ Points of slope -1 provide the noise margin levels

$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

Noise Margin Approximation

 


Figure: Noise Margin approximation of a CMOS Inverter

- Extend the tangent at V_M
- Slope is the gain (g) of the VTC

$$NM_H = V_{DD} - V_{IH} = V_{DD} - V_M + \frac{V_M}{g}$$

$$NM_L = V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

Noise Margin Calculations

- ▶ Need to consider channel length modulation
- ▶ Slope is the gain ($g = \frac{dV_{out}}{dV_{in}}$) of the VTC

$$I_{DSn} = I_{DSn}^{no-clm}(1 + \lambda_n V_{out})$$



$$I_{DSP} = I_{DSP}^{no-clm}(1 + \lambda_p(V_{out} - V_{DD}))$$

$$g = -\frac{1}{I_D(V_M)} \frac{k_n V_{DSATn} + k_p V_{DSATp}}{\lambda_n - \lambda_p}$$

$$g \approx \frac{1 + r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$

$$r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}}$$

Pass Transistors

  

$$v_C(t) = \min(V_G - V_{Tn}, V_D)$$

$$v_C(t) = \max(V_G - V_{Tp}, V_D)$$

Switch Model

 


Figure: The CMOS Inverter

- ▶ The high and low logic levels are V_{DD} and $GND(0)$
- ▶ Logic levels are independent of sizes - Ratioless Logic
- ▶ Low output impedance ($k\Omega$) - Immune to noise
- ▶ Large input impedance - Infinite fanout
- ▶ No conduction path from supply to ground in steady state

Switch Model Dynamic Behaviour

 


Figure: Dynamic Behaviour of CMOS Inverter

$$\tau_{rise} = R_p C_L$$

$$\tau_{fall} = R_n C_L$$

Delay

- ▶ Propagation Delay - 50% input to 50% output
 - ▶ Rise delay. Output goes from $L \uparrow H$ - t_{pLH}
 - ▶ Fall delay . Output goes from $H \downarrow L$ - t_{pHL}
 - ▶ Propagation delay is defined as $t_p = \frac{t_{pHL} + t_{pLH}}{2}$
- ▶ Slew
 - ▶ Rise time - Time taken for output to go from 10% to 90%
 - ▶ Fall time - Time taken for output to go from 90% to 10%

Delay

 


Figure: Delay

$$t_{pHL} = R_{eqn} C_L$$

$$t_{pLH} = R_{eqp} C_L$$

$$t_p = C_L \frac{R_{eqn} + R_{eqp}}{2}$$

Transistor Sizing - Symmetric delay

- ▶ Rising propagation delay should be identical to falling propagation delay.
- ▶ This also ensures a symmetric VTC

$$t_{pHL} = t_{pLH}$$


$$R_{eqn} = R_{eqp}$$

$$\frac{C_L V_{DD}}{2I_{DSATn}} = \frac{C_L V_{DD}}{2I_{DSATp}}$$

$$W_n \mu_n = W_p \mu_p$$

$$W_p \approx 2W_n$$

Transistor Sizing - Minimum delay

 

$$t_p = C_L \frac{R_{eqn} + R_{eqp}}{2}$$

$$t_p = (0.5)[(1 + \beta)(C_{gn2} + C_{dn1}) + C_{wire}]R_{eqn}(1 + \frac{\alpha}{\beta})$$

$$\alpha = \frac{R_{eqp}}{R_{eqn}} @ W_p = W_n; \beta = \frac{W_p}{W_n}$$

$$\frac{\partial t_p}{\partial \beta} = 0$$

$$\beta_{opt} = \sqrt{\alpha \left(1 + \frac{C_{wire}}{C_{dn1} + C_{gn2}} \right)}$$

Power Dissipation

Energy lost as heat dissipation in the devices

- ▶ Dynamic - Charge/ Discharging of capacitance
- ▶ Short Circuit - Conductive path from $V_{DD} \rightarrow GND$
- ▶ Static - Leakage even when no activity happens

Dynamic Power

 


Figure: Capacitor charge and discharge

$$E_{VDD} = \int_0^{\infty} i_{VDD}(t) V_{DD} dt$$
$$E_C = \int_0^{\infty} i_{VDD}(t) V_{out}(t) dt$$

Dynamic Power

$L \uparrow H$

$$E_{VDD} = \int_0^{\infty} i_{VDD}(t) V_{DD} dt$$

$$E_{VDD} = \int_0^{\infty} C_L \frac{dv_{out}}{dt} V_{DD} dt$$

$$E_{VDD} = \int_0^{V_{DD}} C_L V_{DD} dv_{out}$$

$$E_{VDD} = C_L V_{DD}^2$$

$$E_C = \frac{C_L V_{DD}^2}{2}$$

Dynamic Power

- ▶ $L \uparrow H$ - Load capacitor charges and dissipates $\frac{C_L V_{DD}^2}{2}$ in PMOS
- ▶ $H \downarrow L$ - Load capacitor discharges and dissipates $\frac{C_L V_{DD}^2}{2}$ in NMOS
- ▶ Note that the energy dissipated is independent of size
- ▶ Depends on
 - ▶ Probability of switching ($P_{0 \rightarrow 1}$) - Activity factor
 - ▶ Frequency of operation (f)

$$P_{dyn} = C_L V_{DD}^2 f_{0 \rightarrow 1}$$

$$P_{dyn} = C_L V_{DD}^2 P_{0 \rightarrow 1} f$$

Short Circuit Power

 


Figure: Both NMOS and PMOS conduct

$$E_{sc} = V_{DD} \frac{I_{peak} t_{sc}}{2} + V_{DD} \frac{I_{Peak} t_{sc}}{2}$$

$$P_{sc} = t_{sc} V_{DD} I_{peak} f$$

$$t_{sc} = \frac{V_{DD} + V_{Tp} - V_{Tn}}{V_{DD}} t_s$$

Static Power

 


Figure: NMOS or PMOS leaks current


$$P_{stat} = I_{stat} V_{DD}$$

$$P_{tot} = P_{dyn} + P_{sc} + P_{stat}$$

$$P_{tot} = (C_L V_{DD}^2 + V_{DD} I_{peak} t_s) f_{0 \rightarrow 1} + V_{DD} I_{leak}$$

Stacking Effect

 
- ▶ The intermediate node : $0 < V_X < V_{DD}$
- ▶ Exponentially reduces the leakage of the series stack ($I_2 \ll I_1$)
- ▶ Increase in V_{TH} of the top transistor due to body effect




Process Variations

- ▶ Impossible to manufacture tiny dimensions accurately
- ▶ Variations are not avoidable
- ▶ Process Parameters : T_{OX} , N_A , L_e x_j , μ_n , μ_p see variations
- ▶ Performance Parameters: Currents and Voltages
- ▶ Process variation information (μ, σ) are provided to designers
- ▶ Performance parameter variation in simulation should match measured variations

Process Variations

 


Global Variations

 

WAFER : 200mm (8 in) or 300mm (12 in)

- ▶ All transistors within a chip affected in the same way
- ▶ Transistors in different chips across the wafer affected differently

Global Variations

 


- ▶ Manufacturing process of (N and P)MOS are different
- ▶ Transistors end up being Fast (F), Slow (S) or Typical (T)
- ▶ All N can get biased in one direction
- ▶ All P can get biased in another
- ▶ Corner simulation (N,P) : (TT, FS, FF, SF, SS)

Local Variations


- ▶ Transistors sitting right next to each other will be different
- ▶ Happens mainly due to Random Dopant Fluctuation
- ▶ Large transistors are affected less than small ones
 $(\sigma_{Local} \propto \frac{1}{\sqrt{LW}})$
- ▶ Requires large number of statistical simulations to ensure correct functionality

Ring Oscillators

 - ▶ Excellent process monitors
- ▶ Good representative of all digital circuits
- ▶ Can be added by the FAB in Kerf regions or by designers in their chip
- ▶ Measure the frequency of oscillations to determine the global process corner
- ▶ Can be added in multiple corners of a large chip to measure any across chip variation



Ring Oscillators

 

$$T_P \approx 2x(2N + 1)\tau_{inv}$$

- ▶ $EN = 0$ prevents any oscillations - Saves dynamic power
- ▶ Usually a couple of 100 INV long
- ▶ Very high frequency of oscillations
- ▶ Divided several times before being brought out of the chip

References

The material presented here is based on the following books/
lecture notes

1. Digital Integrated Circuits Jan M. Rabaey, Anantha Chandrakasan and Borivoje Nikolic 2nd Edition, Prentice Hall India