


# Learning Objectives for SRAM

- Articulate memory hierarchy and the value proposition of SRAMs in the memory chain + utilization in current processors
- Explain SRAM building blocks and peripheral operations and memory architecture (with physical arrangement)
- Articulate commonly used SRAM cells (6T vs 8T), their advantages and disadvantages
- Explain the operation of a non-conventional SRAM cells, and their limitations
- Explain commonly used assist methods
- Explain how variations impact memory cells


# Topics

- ❑ Introduction to memory
- ❑ SRAM : Basic memory element
- ❑ Operations and modes of failure
- ❑ Cell optimization
- ❑ SRAM peripherals
- ❑ Memory architecture and folding

# Memory Classification revisited

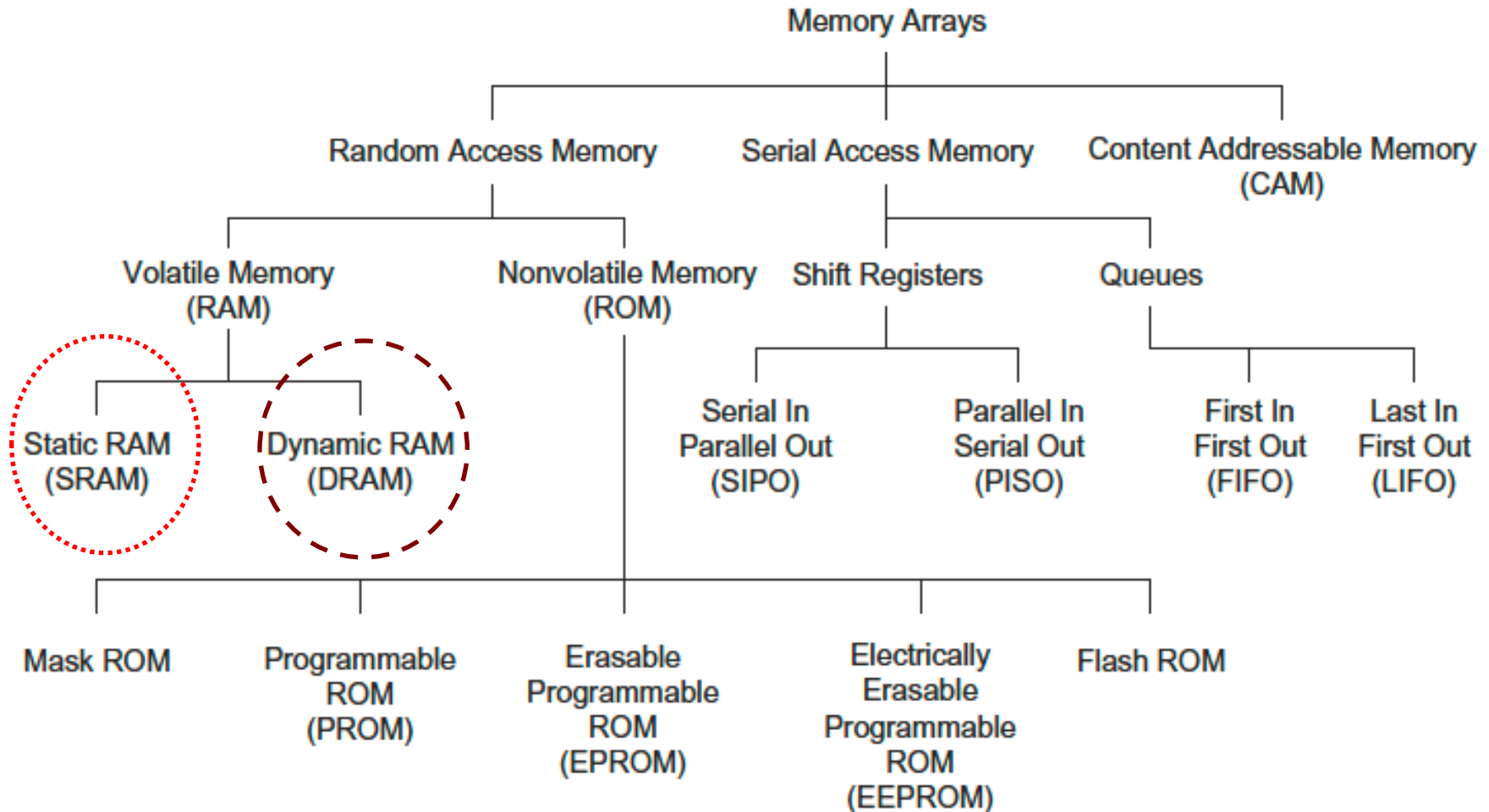

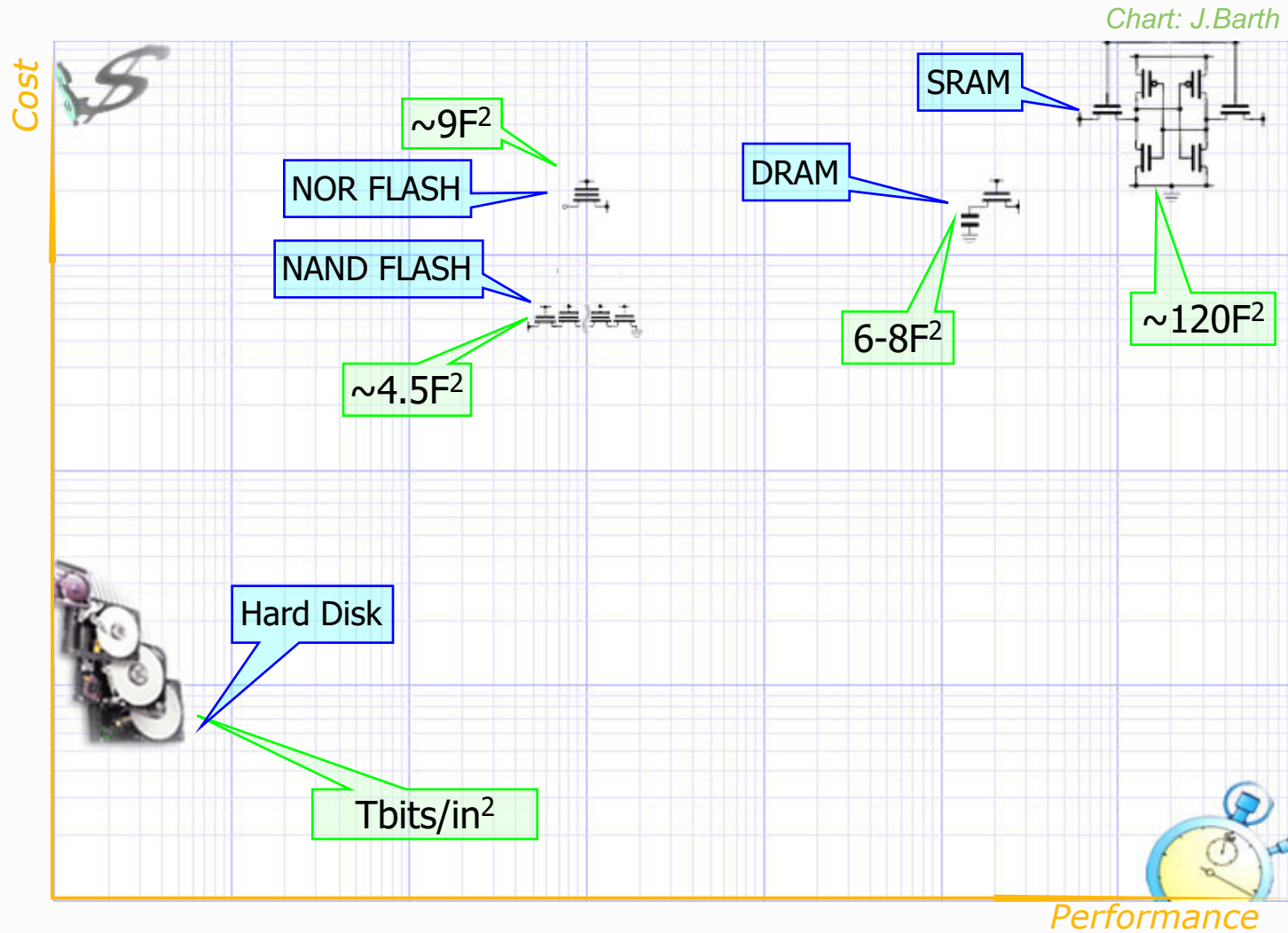
# Technology choices for memory hierarchy



 
# Cache Sizes


AMD Zen  
ISSCC 2017  
512kB L2\$,  
8MB L3\$



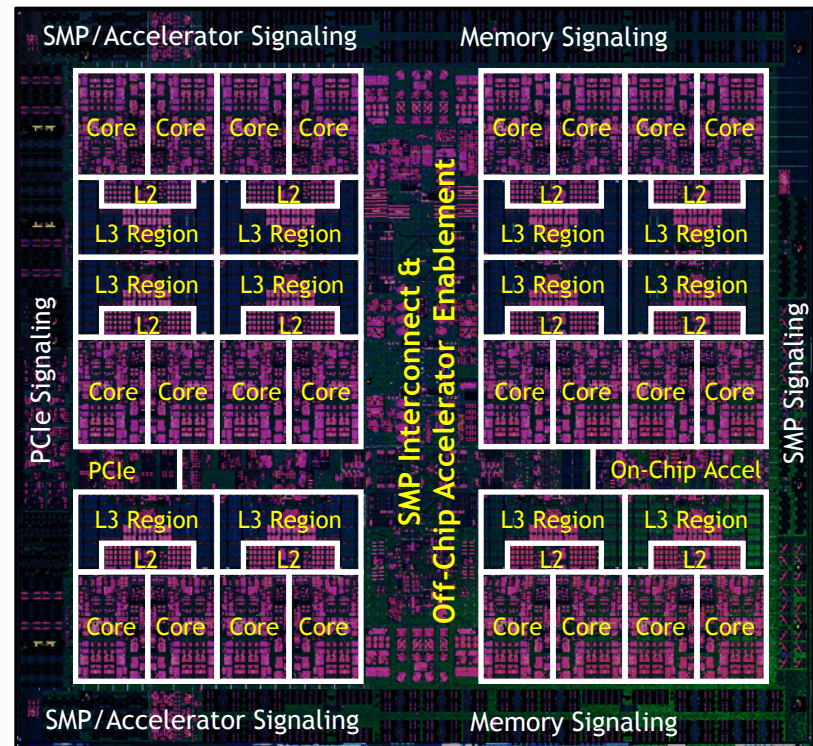IBM POWER9  
Hotchips 2016  
32kB L1 I\$ and D\$,  
120MB e-DRAM L3\$


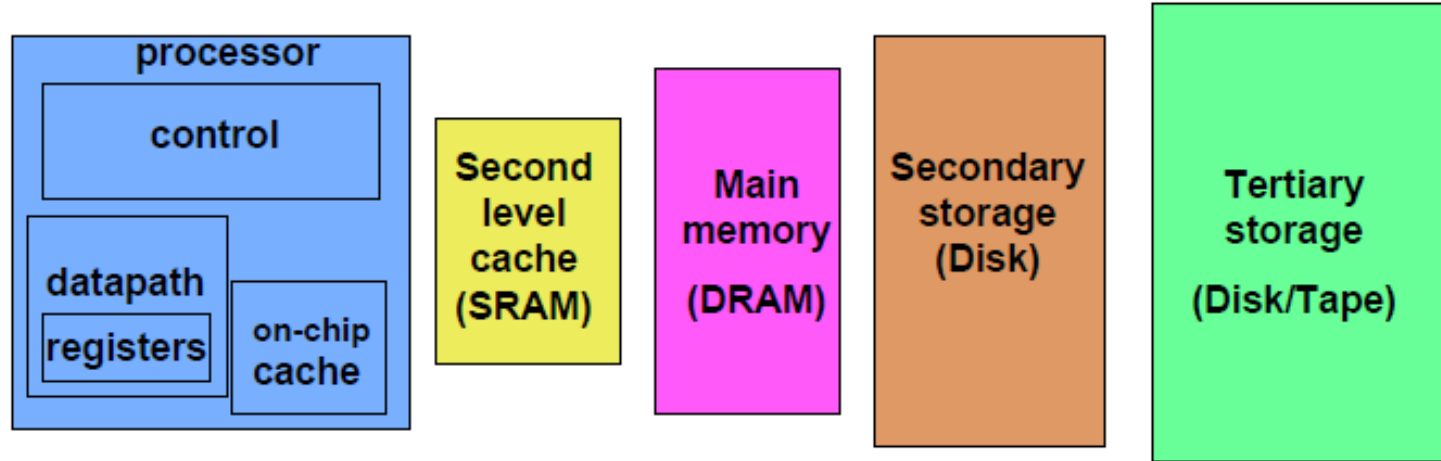
# Cache size impacts cycles-per-instruction



Speed	1ns	10ns	100ns	10ms	10sec
Size	B	KB	MB	GB	TB

For a 5GHz processor, scale the numbers by 5x

Several memory blocks in a typical processor core: I\$, D\$, Address translation tables, Branch history tables, all in the KB - low MB range

# Question 1


- ❑ SRAMs are preferred for L1 Cache over eDRAMs
- a) Refresh operation of e-DRAM causes undesirable performance penalty
- b) e-DRAMs is too slow for high speed operation
- c) SRAMs are compact and can easily fit near functional blocks
- d) e-DRAMs requires multiple supply voltages

# Topics


- ❑ Introduction to memory
- ❑ SRAM : Basic memory element
- ❑ Operations and modes of failure
- ❑ Cell optimization
- ❑ SRAM peripherals
- ❑ Memory architecture and folding




# Basic Memory Element

 


# Access ways

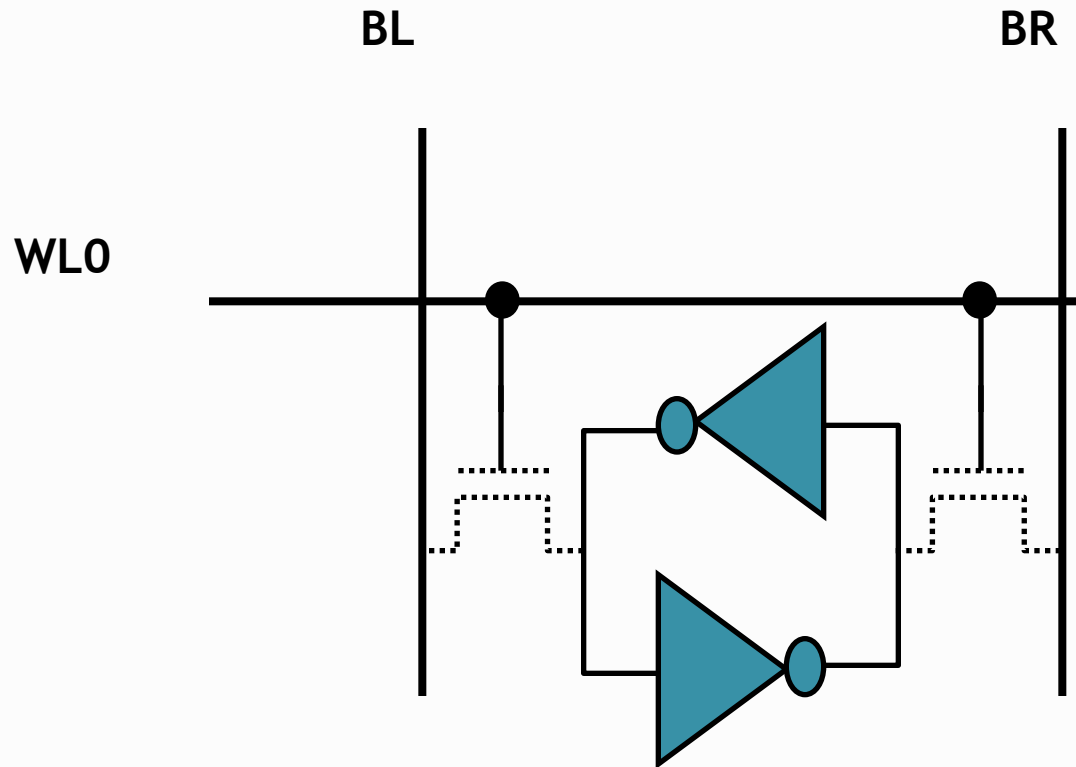


# No Operation (Hold)

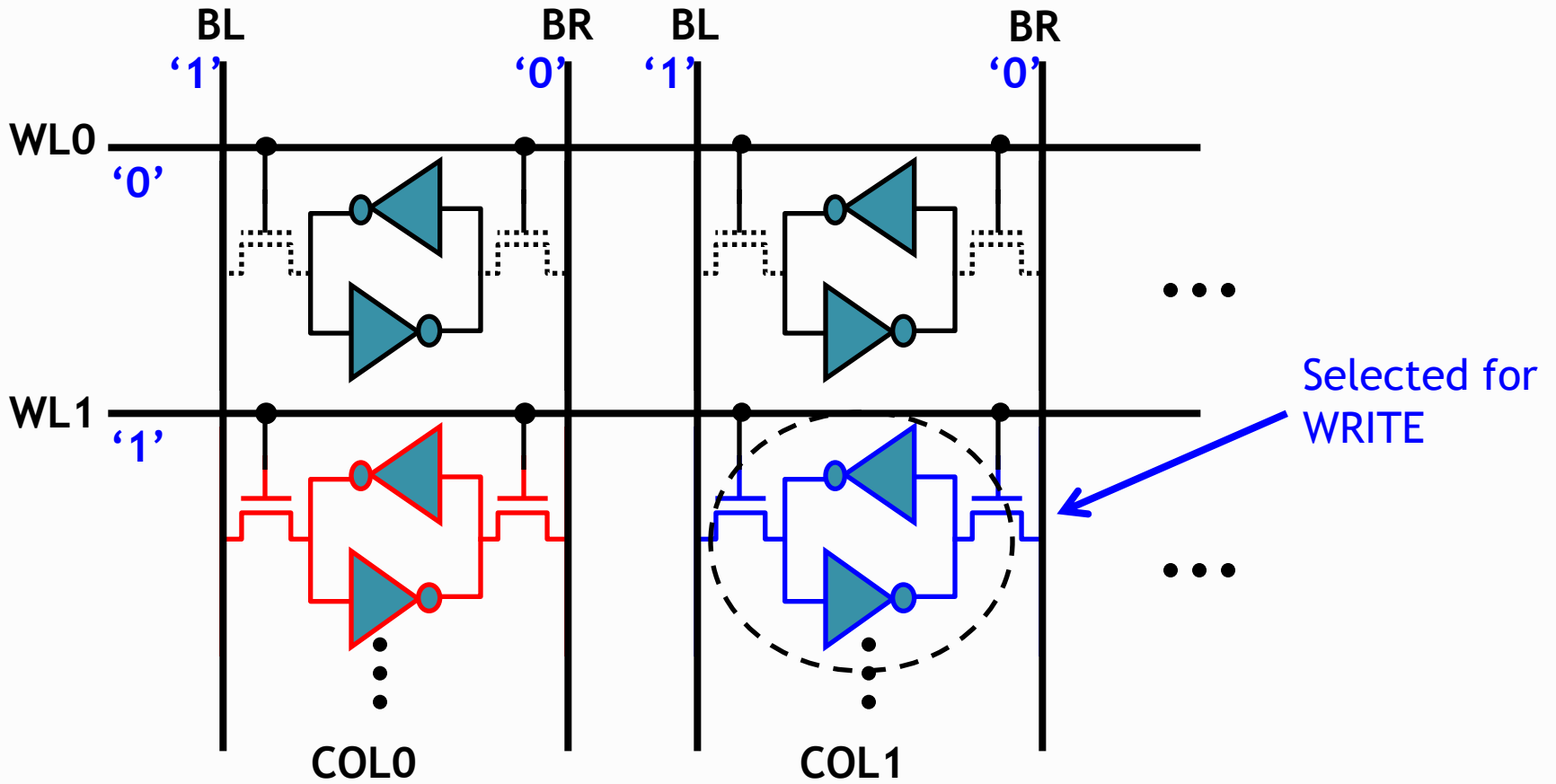



# Hold Margin

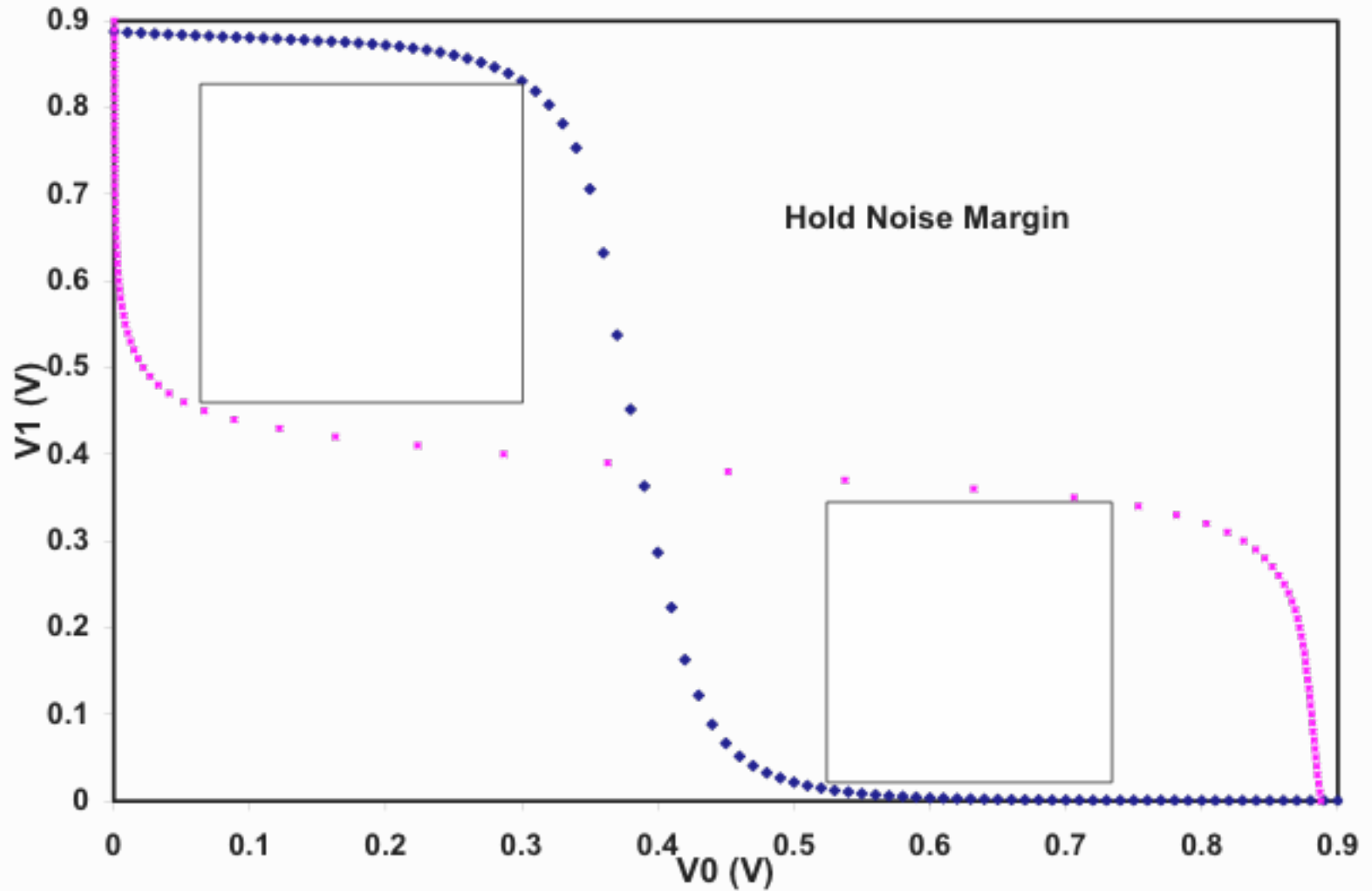

# Hold Failure

 

$$P_{HF} = P(V_{DDHmin} > V_{HOLD})$$

  


Hold Failure => Flipping of cell data in the Hold mode with the application of a lower supply voltage.

## Question 2




### Hold Margin for an SRAM cell

- a) Is always greater than read margin
- b) Can be improved by making the access transistor bigger
- c) Defines the minimum supply voltage required to perform a read operation
- d) Depends on the number of cells on the bit line

# Read Operation

 

# Read Failure

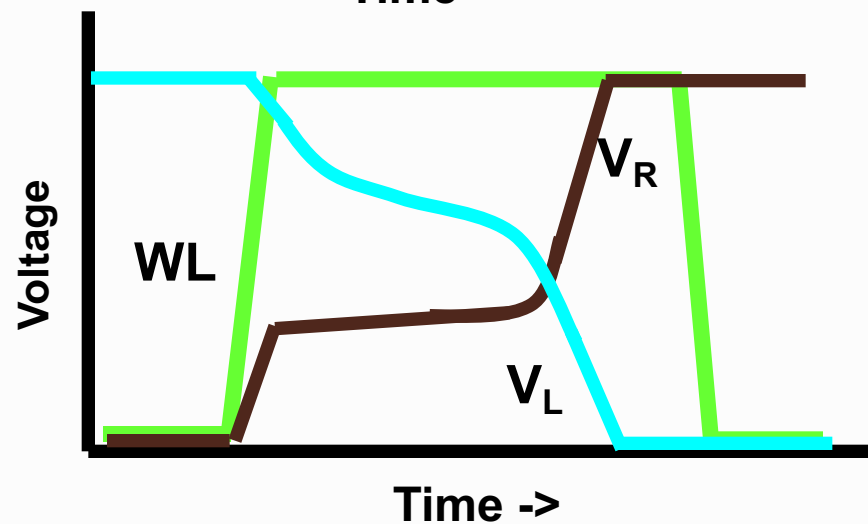 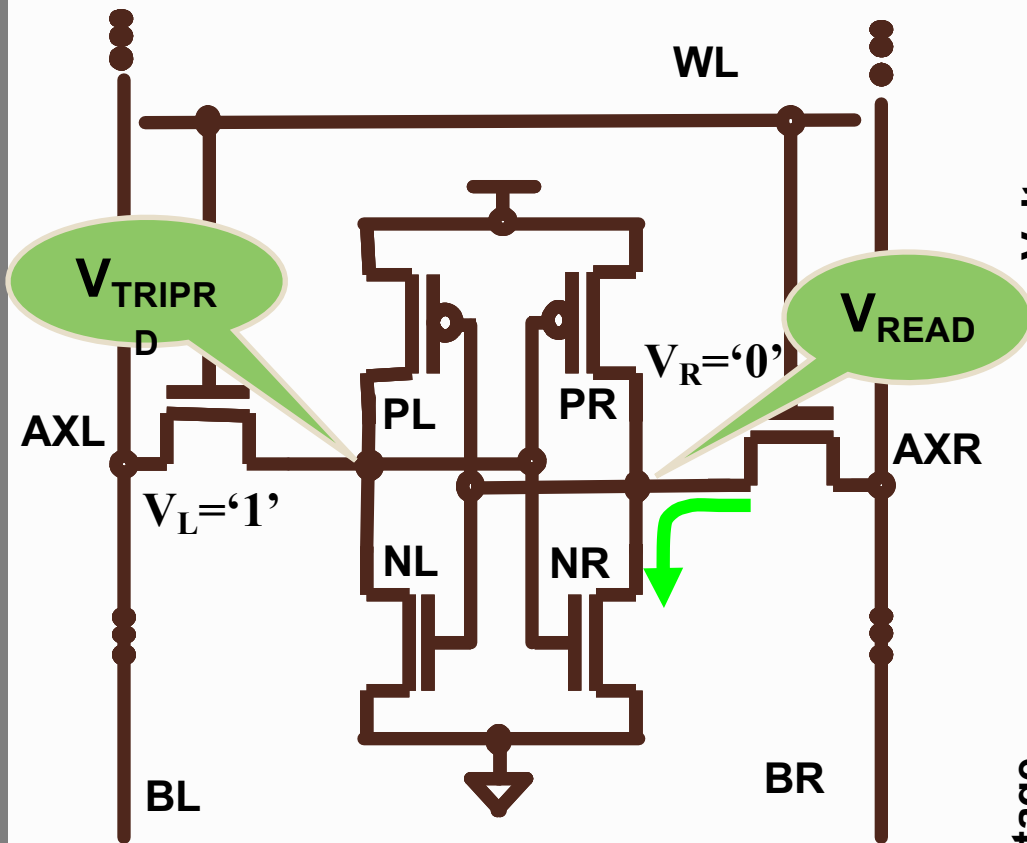


$$P_{RF} = P(V_{READ} > V_{TRIPRD})$$


Read failure => Flipping of Cell Data while Reading






# Hold vs Read Margin

 

# Write Operation

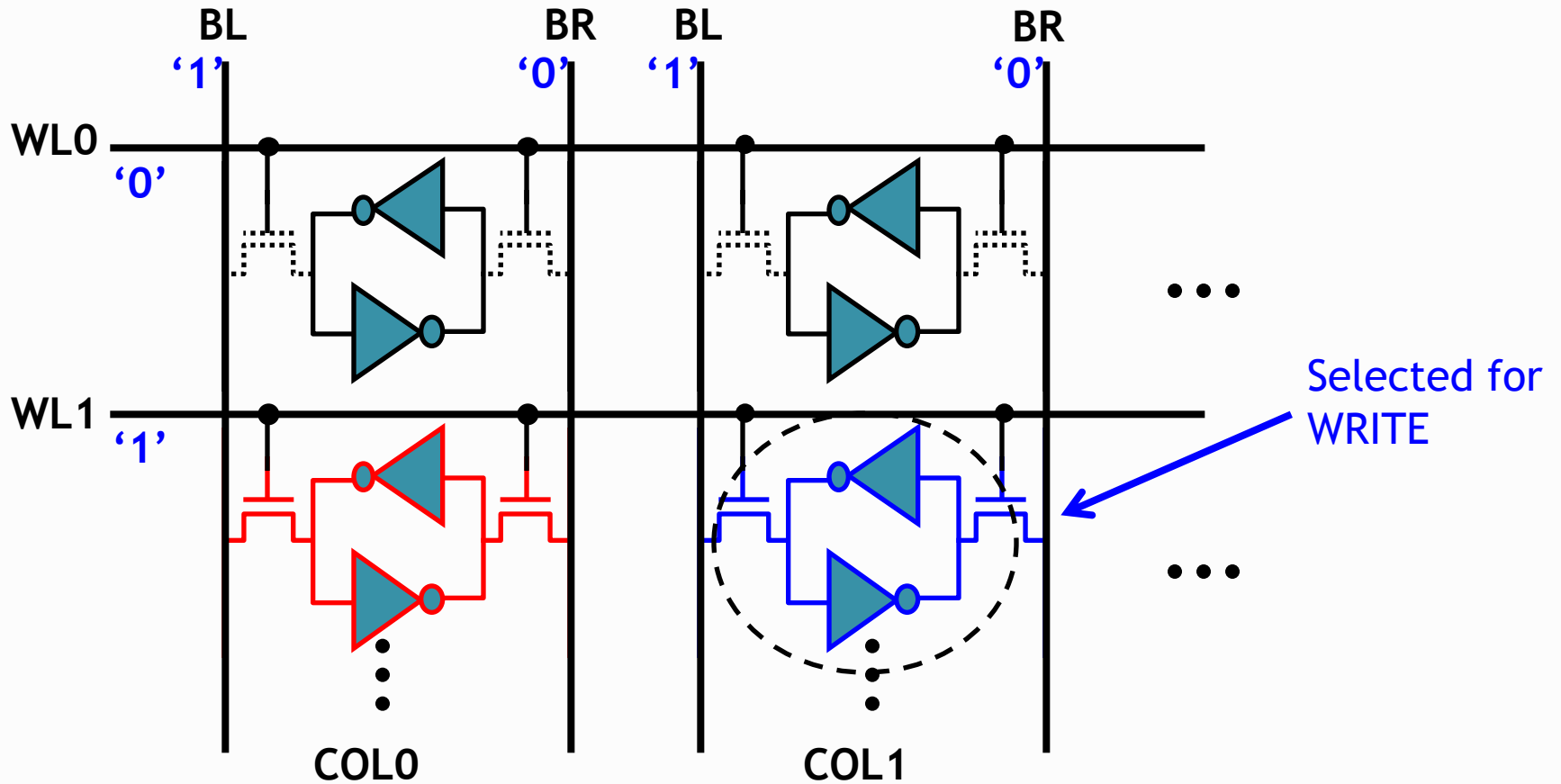


# Write Failure

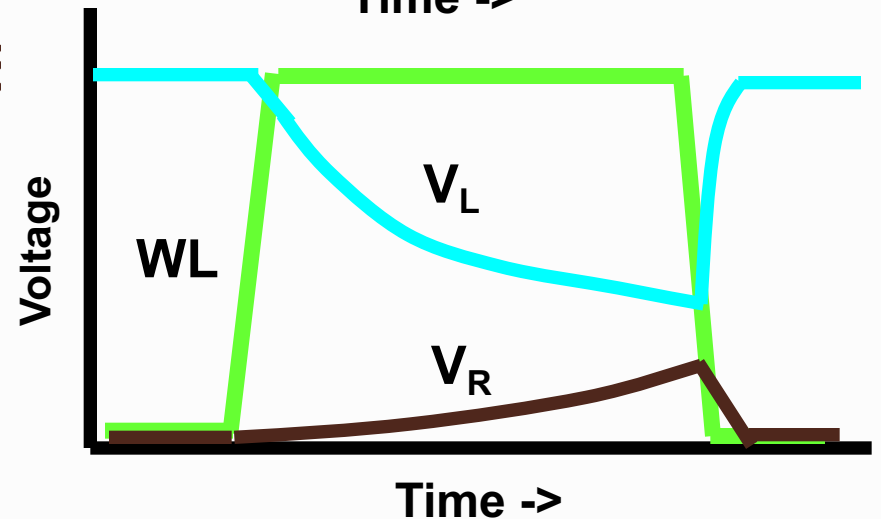  



$$P_{WF} = P(T_{WRITE} > T_{WL})$$

Write Failure => Unsuccessful write to the cell.

# Write Margin

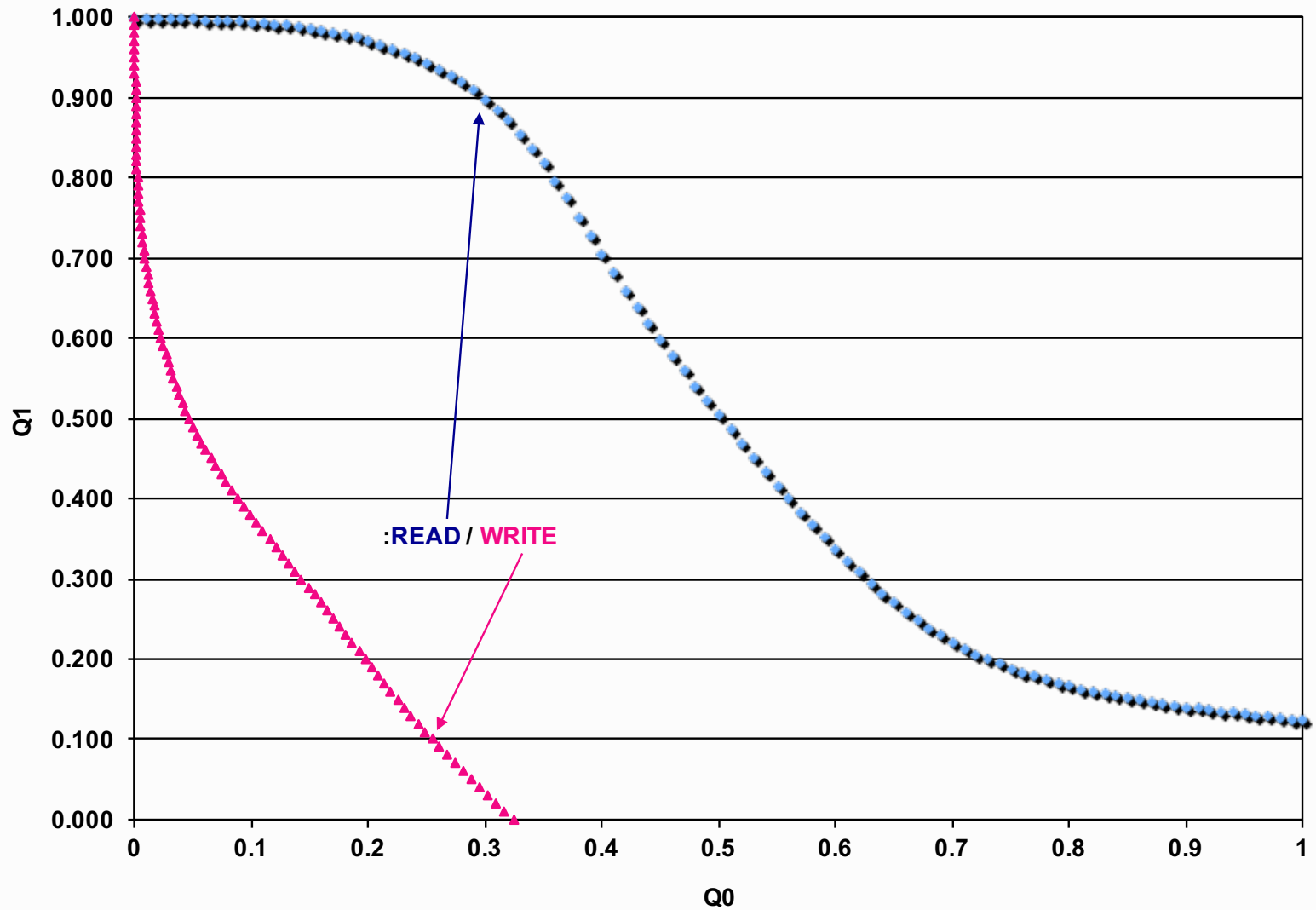

# Access Failure

 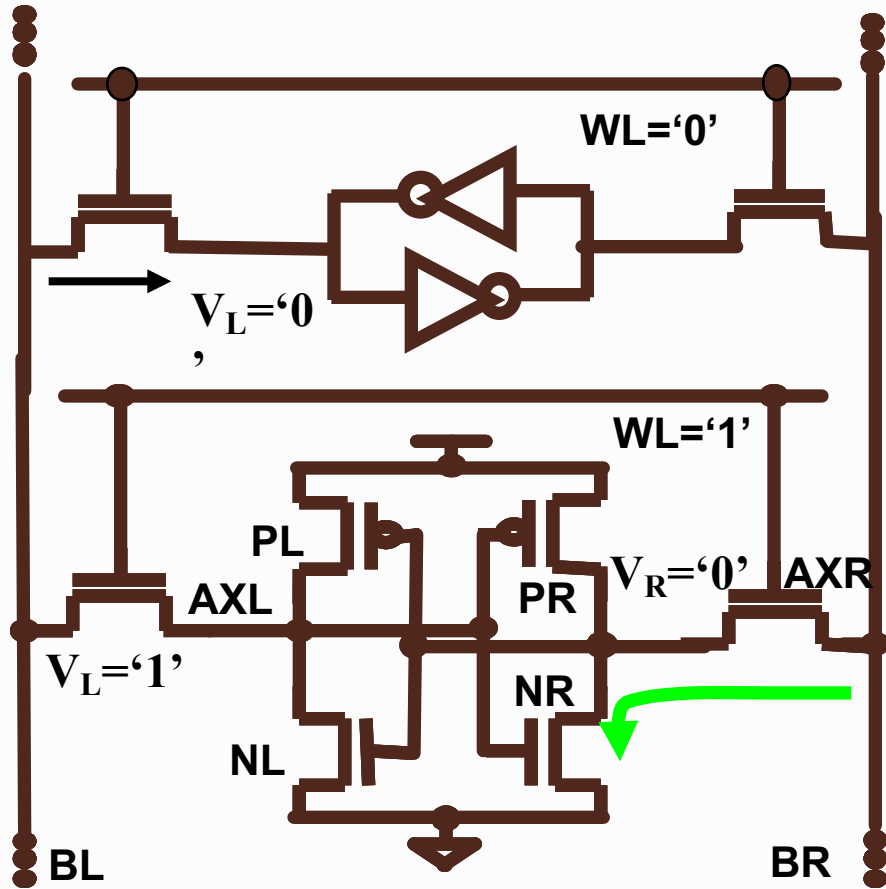

$$P_{AF} = P(T_{ACCESS} > T_{MAX})$$


**Access Failure :** Time required to produce a pre-specified bit-differential is higher than a maximum allowed time.

## Question 2b

### Write Margin for an SRAM cell

- a) Is always greater than read margin
- b) Can be improved by making the access transistor bigger
- c) Defines the minimum supply voltage required to perform a read operation
- d) Depends on the number of cells on the bit line

# The Balancing Act

 


**Large N:** Better READ performance. If too large, trip voltage of inverter becomes so low that cell becomes unstable.

**Large A:** Better Performance. If too large, storage node voltage goes high during READ, causing cell flip


**Large P:** Increase stability. If too large, hard to WRITE.

Need to balance all : **NR:XR:PR** ~ 2:1:1


# Workhorse 6T-Cell

 

Access Xr: On  
 Data driven on bit - lines  
 Data Flipped by over-  
 coming pull-up / pull -  
 down Xrs

 

Access Xr: On  
 BL, Blb pre-conditioned,  
 and then floated, one  
 line discharges thru the  
 cell (Iread), voltage  
 sensed, Data Retained

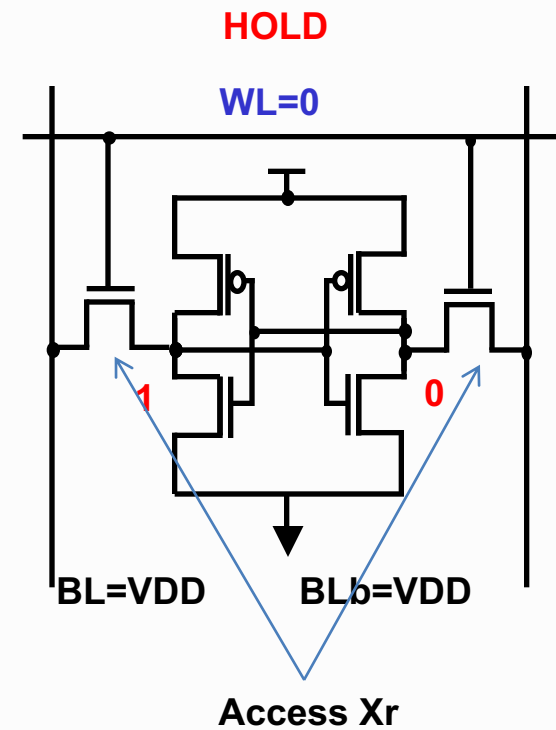


Access Xr : Off  
 Data Retained, due  
 to back-to-back  
 inverters




# Thin Cell (Litho-Friendly)

Cell area vital for density

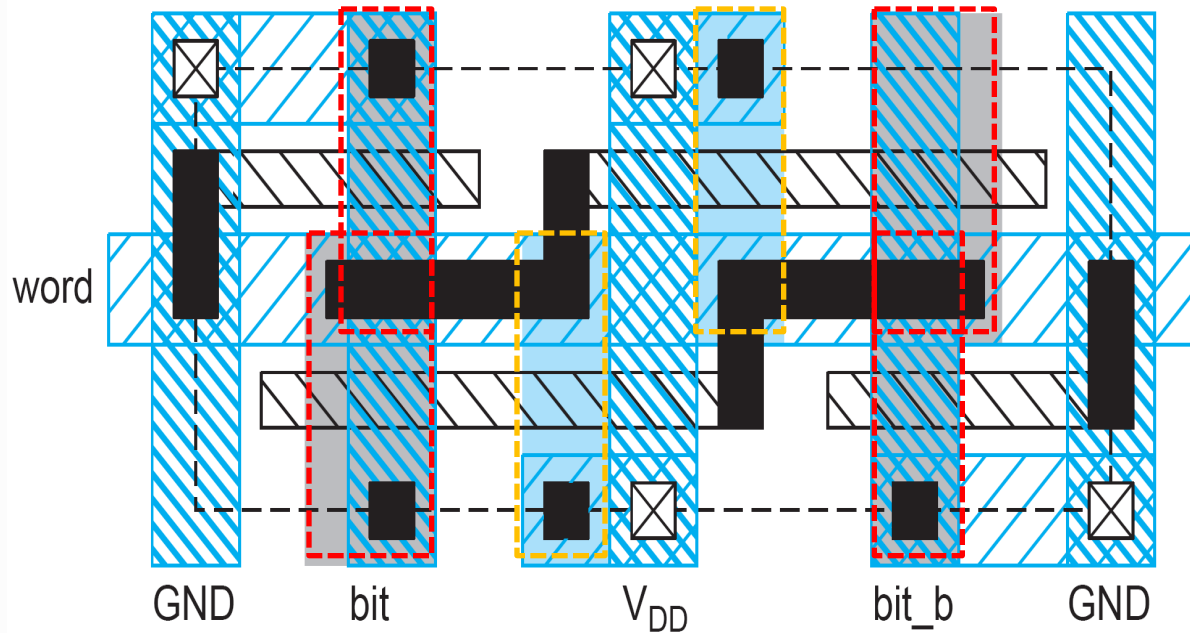

Flip

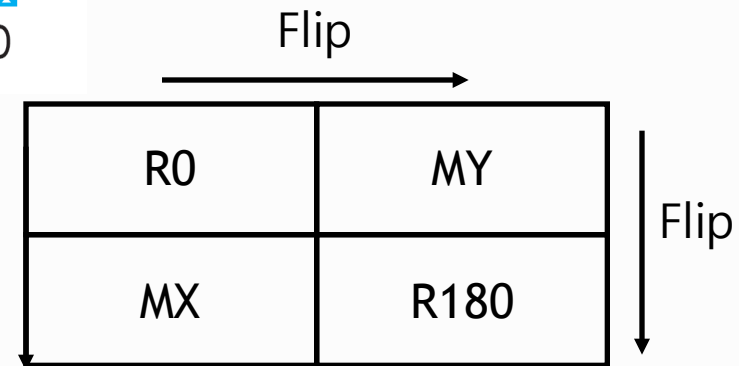

## Question 2c

Decreasing the size of only one side of NFET transistors will improve the cell

- a) Cell density
- b) Read margin
- c) Write margin
- d) Hold margin

# Topics

- ❑ Introduction to memory
- ❑ SRAM : Basic memory element
- ❑ Operations and modes of failure
- ❑ Cell optimization
- ❑ SRAM peripherals
- ❑ Memory architecture and folding


# Decoders and Drivers

WL driver	cell	cell	cell	cell
WL driver	cell	cell	cell	cell


•  
•  
Word line driver layout needs to be pitch  
matched to SRAM cell  
•

WL driver	cell	cell	cell	cell
WL driver	cell	cell	cell	cell
Decoder and Control	Column Circuitry			


# Column Circuitry for Read and Write

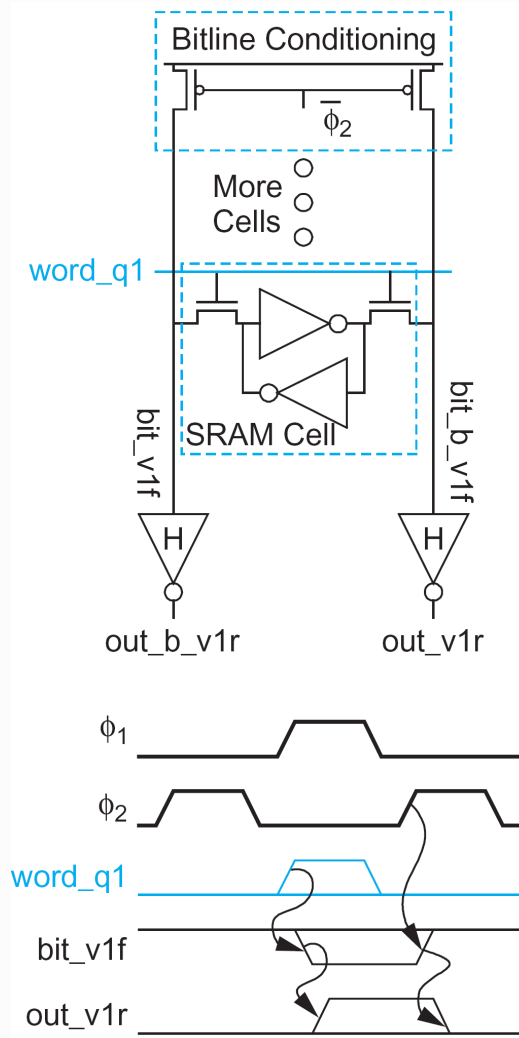

**READ**

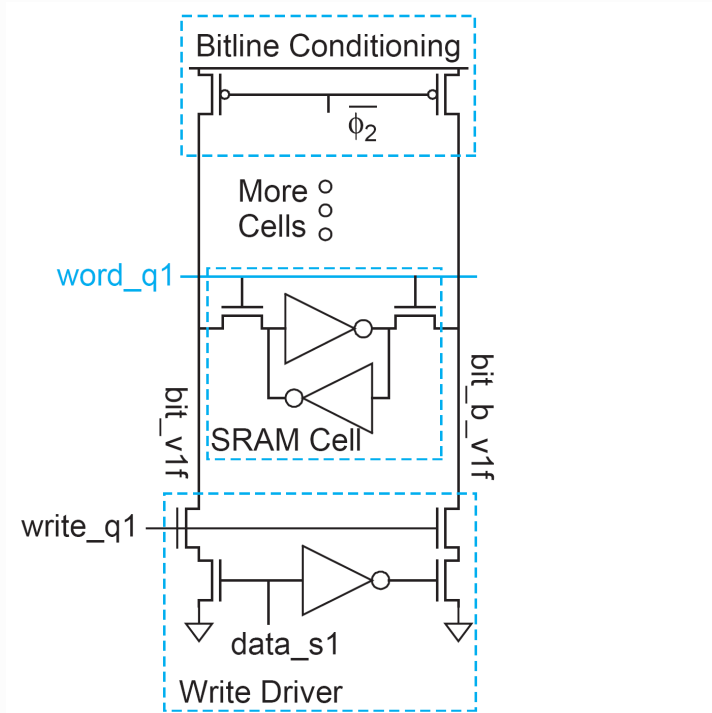


(a)

 

(b)

**WRITE**


# Sense Amplifiers

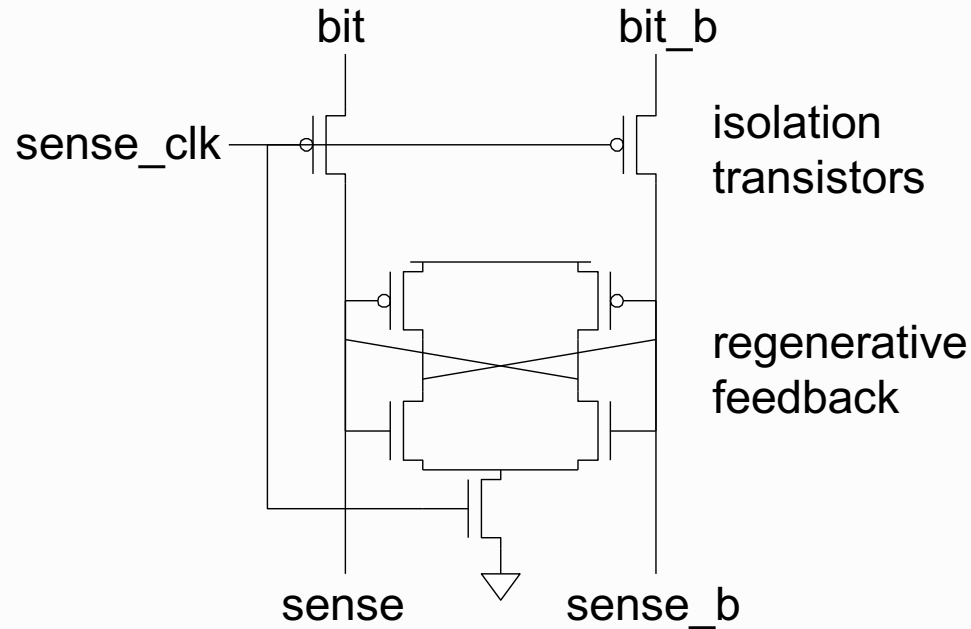

Sense-amp provide necessary gain (small input  $\rightarrow$  large output) for read  
If sense\_clk arrives too early  $\rightarrow$  False read may happen due to too small difference  
If sense\_clk arrives too late  $\rightarrow$  Too slow

Isolation transistors: Disconnects sense amp to cutoff large bit line capacitance once sensing starts


# Hierarchical Bit-lines

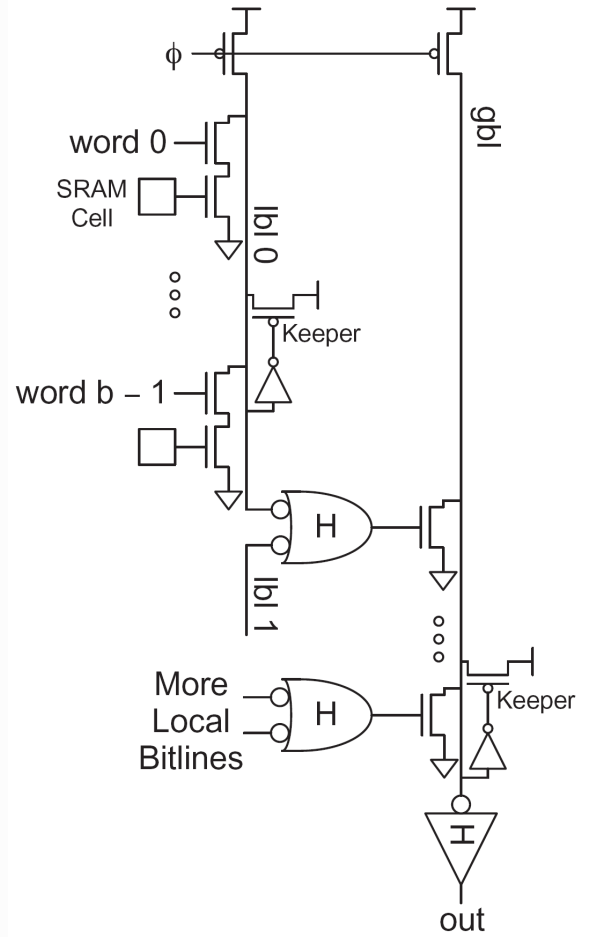


Hierarchical Bit-lines

# Pre-Conditioning

Precharge

 

Equalizer

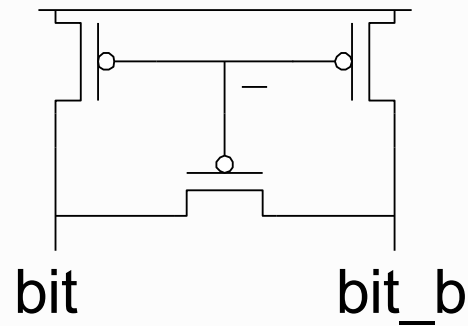

Pre-Conditioning



## Question 3

### Equalizer is required


- a) Both the bitlines are pre-charged at the same time
- b) To ensure that the bit-lines are conditioned suitably for write operation
- c) To minimize offset between the bitlines prior to read operation
- d) To improve the hold and read margin of the memory cells

# Topics

- ❑ Introduction to memory
- ❑ SRAM : Basic memory element
- ❑ Operations and modes of failure
- ❑ Cell optimization
- ❑ SRAM peripherals
- ❑ Memory architecture and folding
 
# Memory Architecture

- $2^n$  words of  $2^m$  bits each, If  $n \gg m$ , fold by  $2^k$  into fewer rows of more columns



- Good regularity - easy to design
- Utilization = Cell Area / (Cell + Periphery Area)

# Why memory is folded?

- To improve aspect ratio by column multiplexing
  - E.g.: 2Kword x 16 can be arranged as 256 rows and 128 columns
  - 8:1 MUX are used to read 16 desired columns out of 128
- To improve soft-error immunity
  - bits of a word are not placed next to each other
    - Single-bit soft-error can be corrected by ECC


# Column Select and Half-Select Issue



● selected column

○ non-selected column

 Prevents multiple-bit soft error  
Better aspect ratio



## Class Exercise

- ❑ Build a schematic of a 6T - SRAM cell with minimum sized PFETs, Pull down = 3\*PFET size, and Access transistor = 2\* PFET size. Simulate it and plot butterfly curve for margins
- ❑ Change Pull down size to 4\*PFET size and re-simulate
- ❑ Change Access transistor size to 3\*PFET size and re-simulate
- ❑ Change pull up device size to 2 original size and re-simulate

## Next Class

- Alternative Cell Types (6 to 10T), Asymmetric Cells, Sub-threshold Cells, Low - leakage cells