
 


High-Performance SRAM Design


Rahul Rao

IBM Systems and Technology Group

Exercise

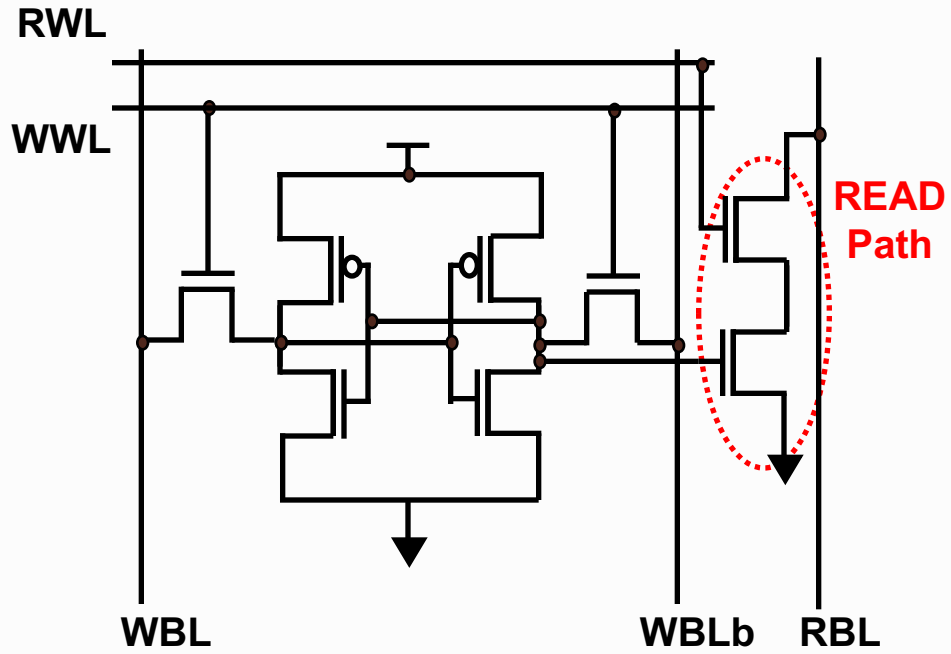

Worst case read condition

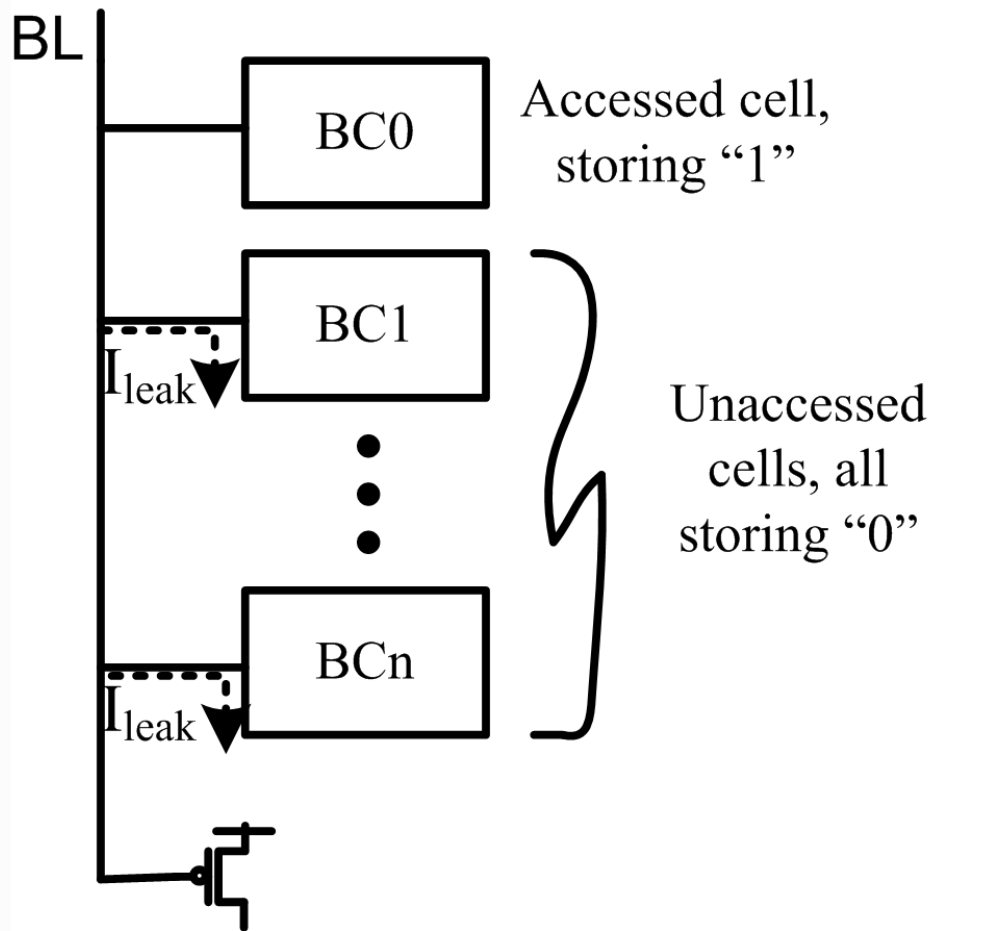

: Worst case Bitline Leakage when reading a "1"

Data Independent Leakage Cell


 
 
 
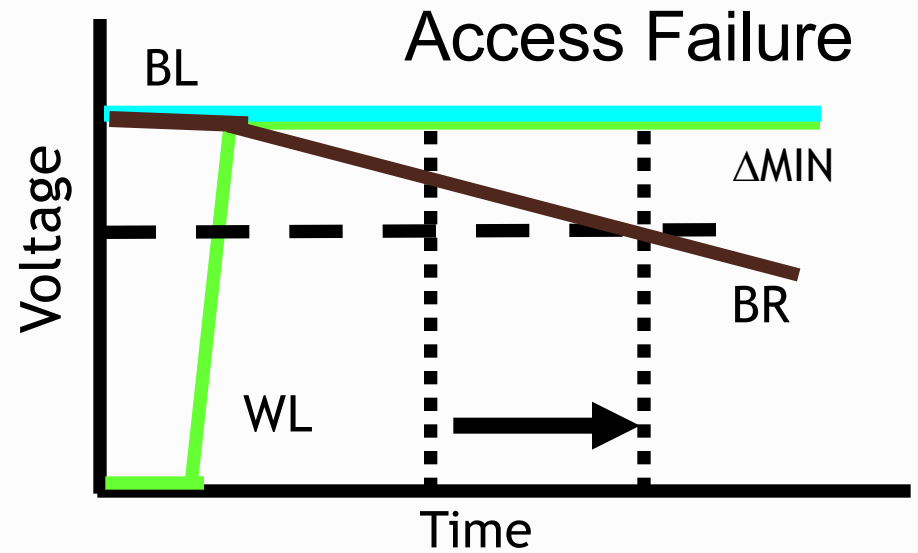


Figure 9 (c): Schematic of Ten transistors with M9 and M10 added to schematic of eight transistor to lower leakage power

Mechanisms of Parametric Failures

 

Question



- ❑ Which of the following are true for the 6-T SRAM cell
 - a) A cell with poor READ margin is unlikely to have access failure
 - b) Differential read means there is no worst case data condition for read
 - c) The worst case write condition is having cells with alternate 0s and 1 along the column
 - d) Access fails can be minimized by running the array at a slower frequency

Topics


- ❑ Introduction to memory
- ❑ SRAM basics and bitcell array (refresher)
- ❑ Current Challenges
- ❑ Alternative Cell Types (6 to 10T), Asymmetric Cells, Sub-threshold Cells, Low - leakage cells
- ❑ Impact of Variation, Assist Circuits
- ❑ BTI and impact on SRAMs
- ❑ Power

Sources of Manufacturing Variations


Variation in Process Parameters

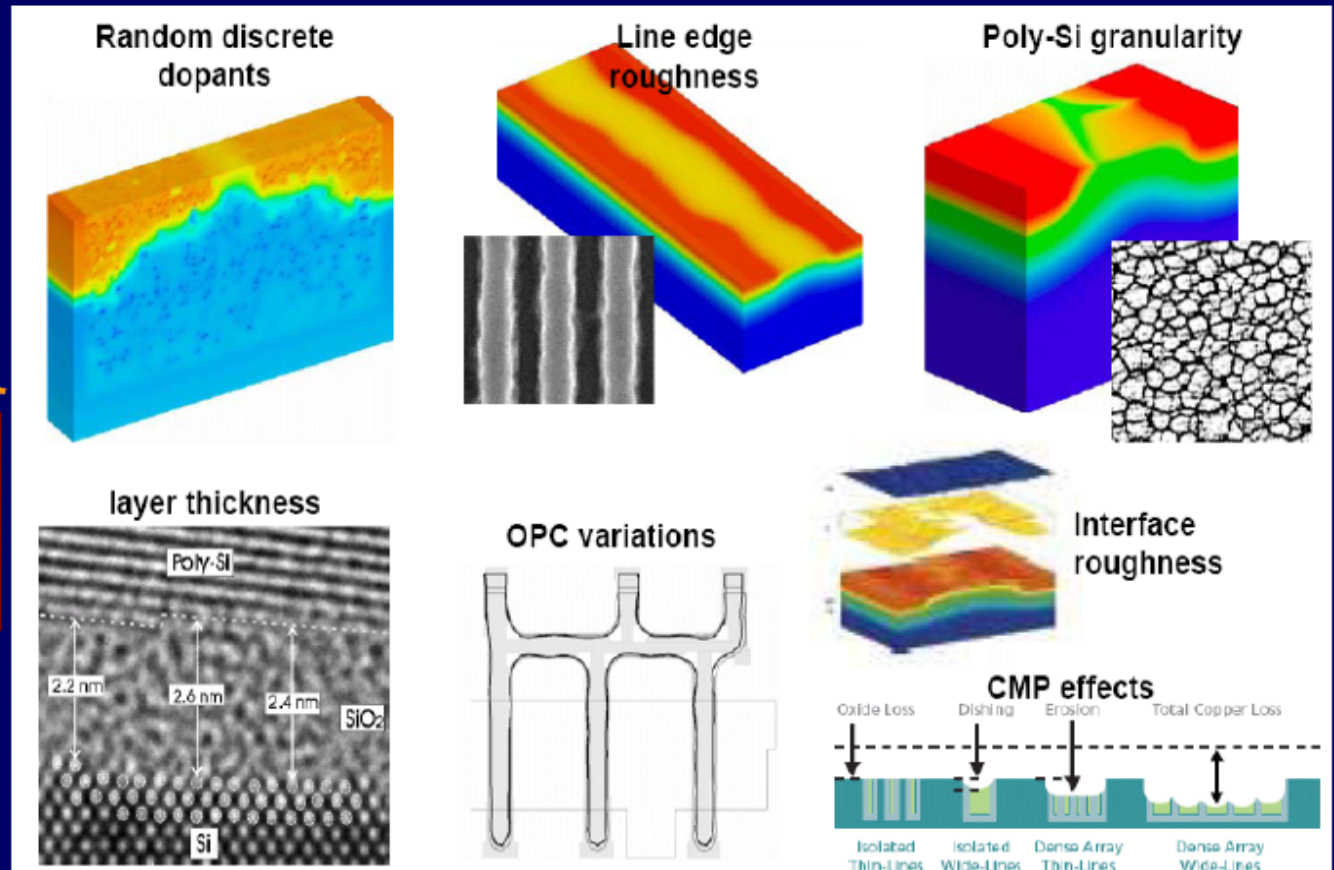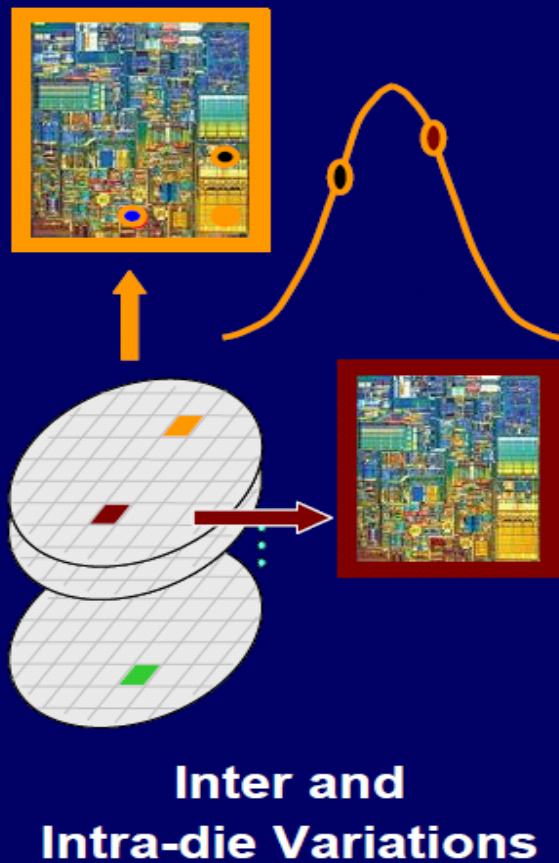

Impact of Manufacturing Variations


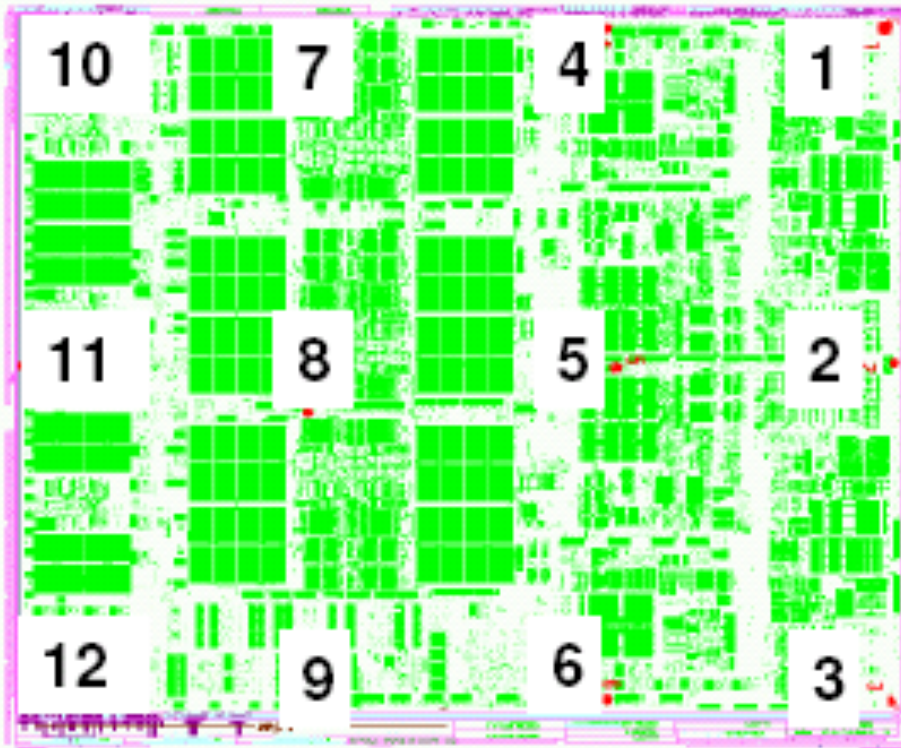


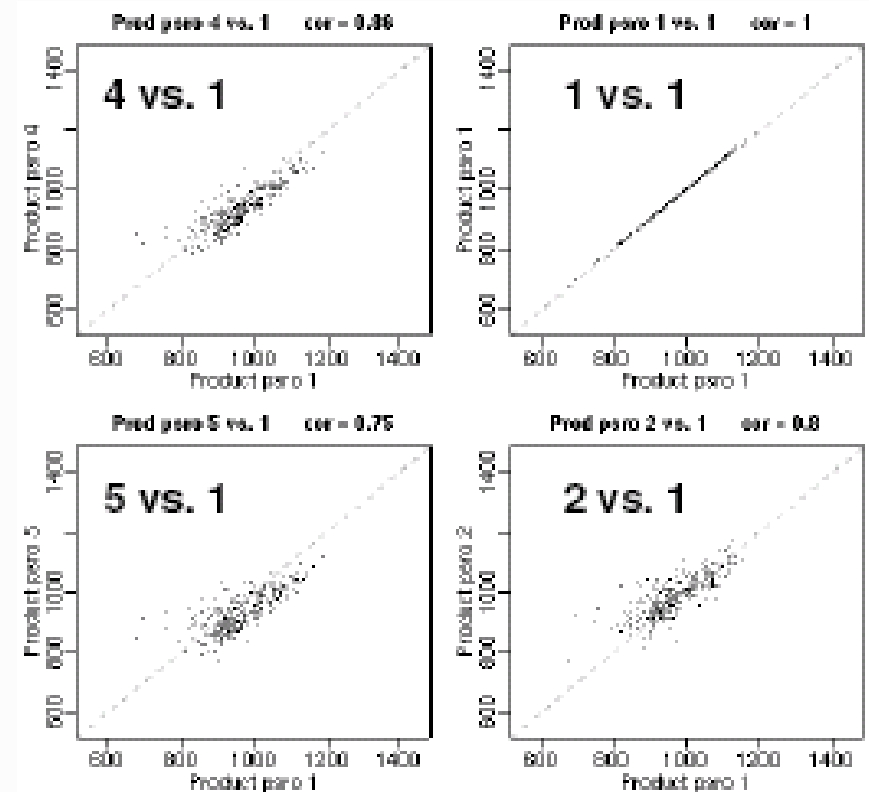Location of Identical Ring Oscillators on a Die



Frequency Correlation
(averaged over 300 die)

Environmental Variations

  

Temperature Variation

- Switching Characteristics of Blocks
- Material Properties: Thermal Coefficient
- Cooling and Packaging Solutions
- Workload and Thermal Management Policies

Delay and leakage increase with temperature




Power Supply Variation

- IR drop: Leakage, Power grid robustness
- Ldi/dt: Transient activity, decoupling capacitors
- Power Efficient Design Strategies: Clock Gating, Power Gating




Delay increases with power supply droop

Global and Local Variations




Random Dopant Fluctuation

  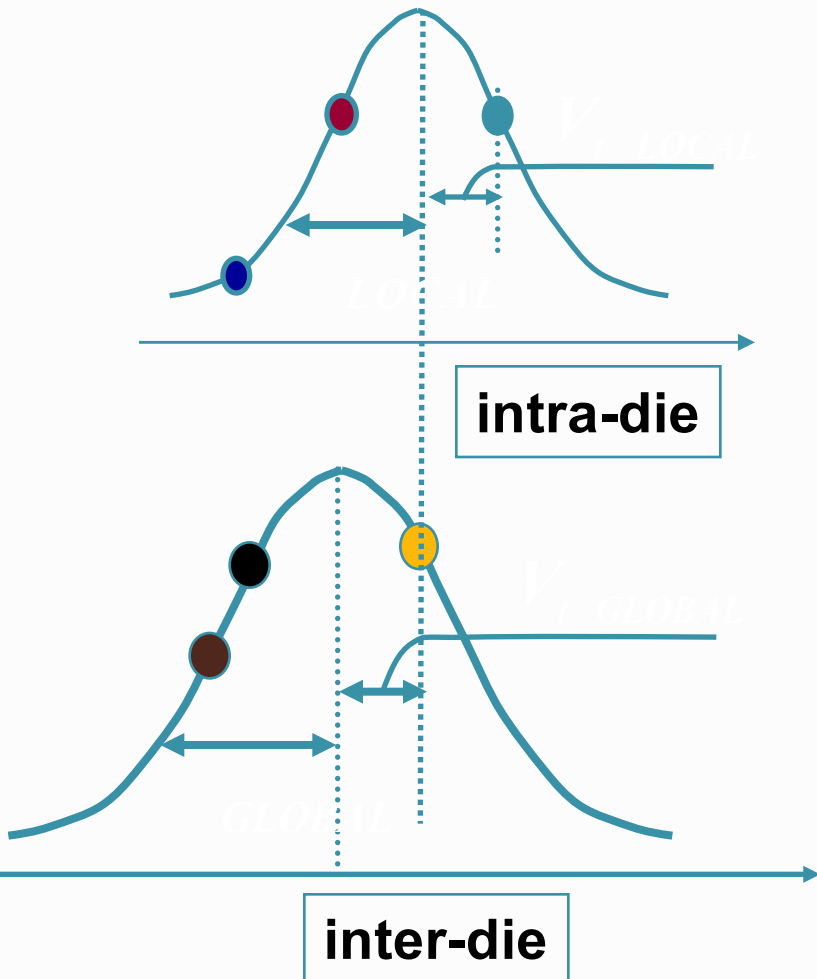




Hold Failure

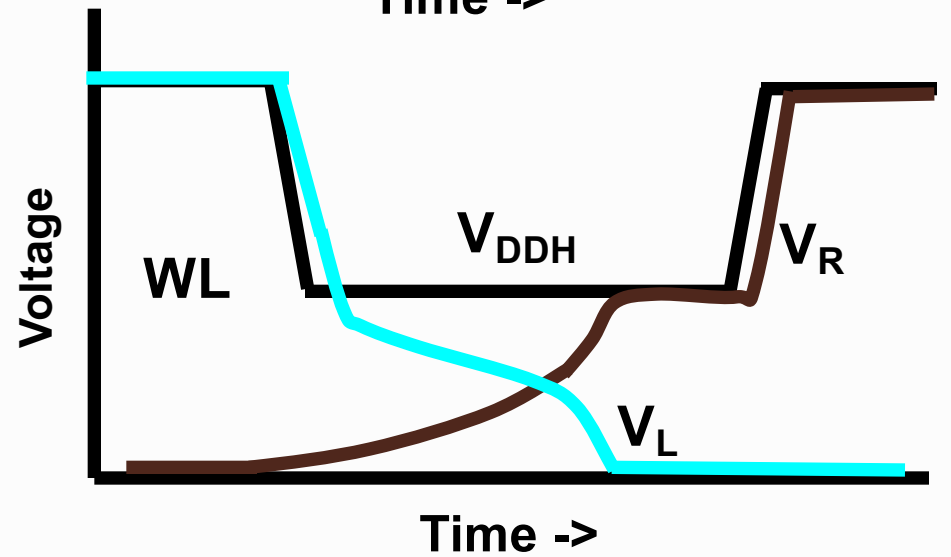 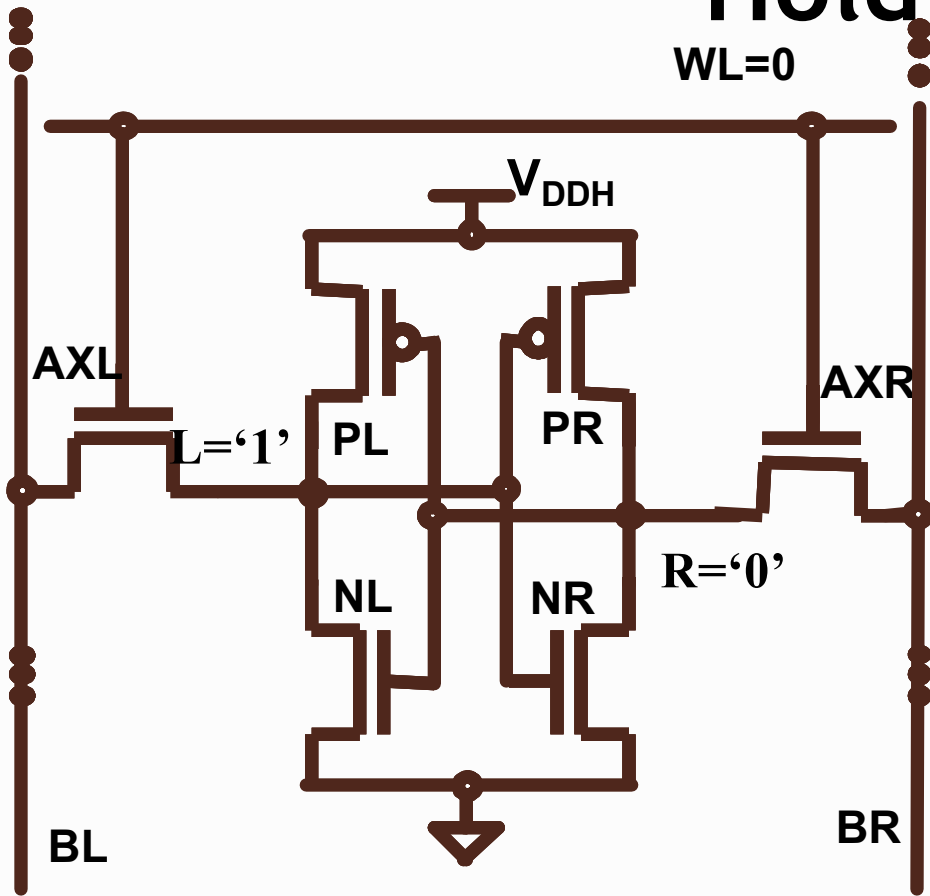



Read Failure

   

Write Failure

  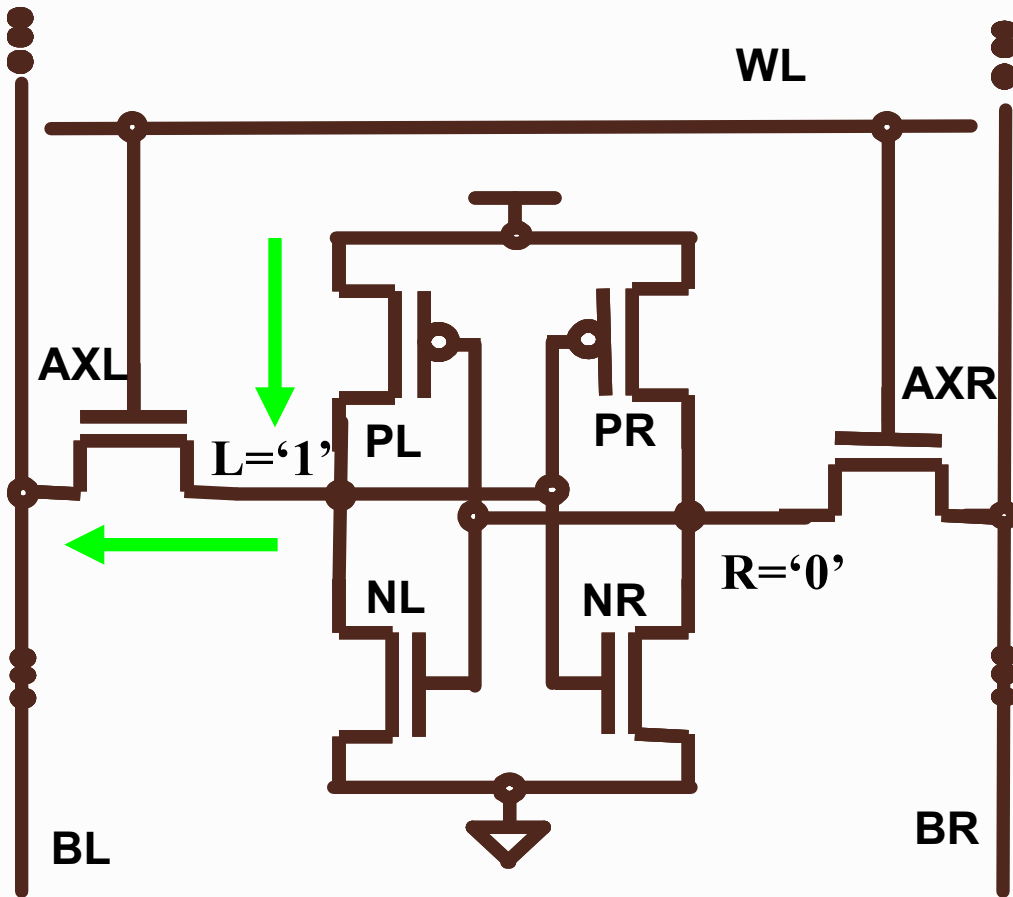


Access Failure

 
 


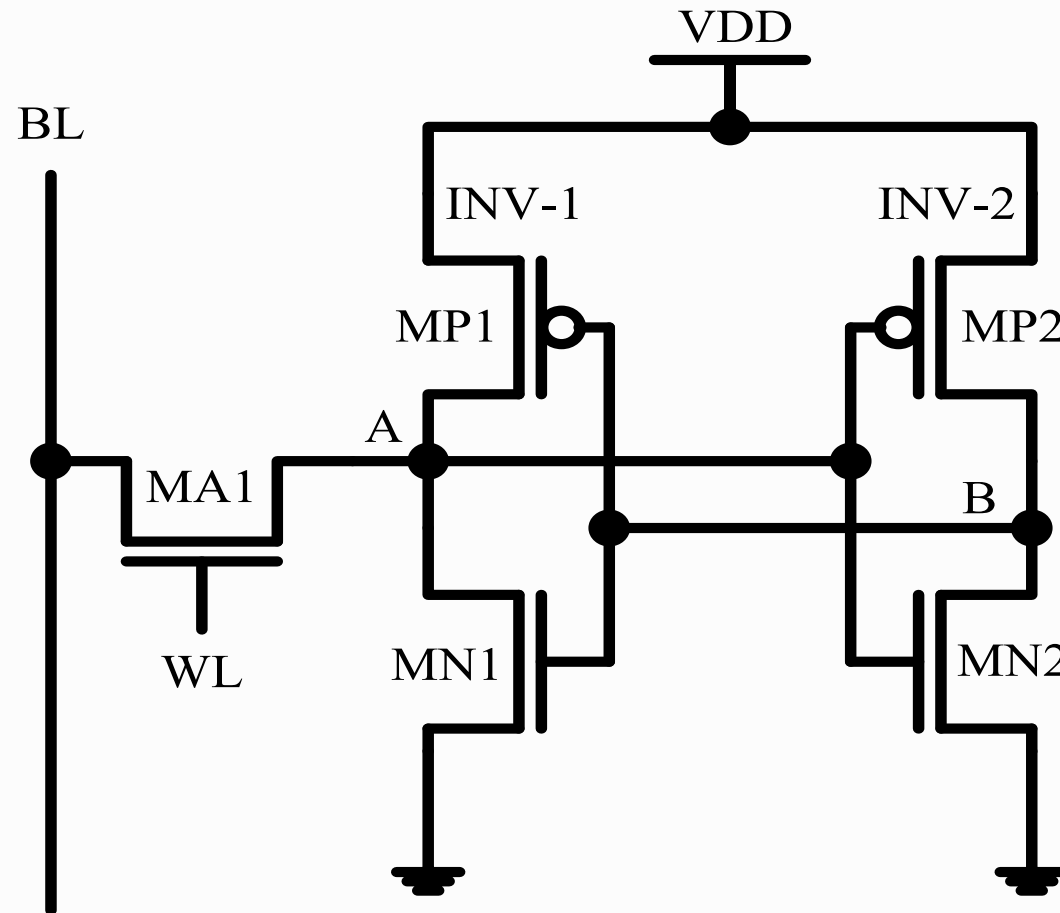Question


- Mark worst case V_T variation condition for each device for write failure



Inter-die Variation & Cell Failures

  

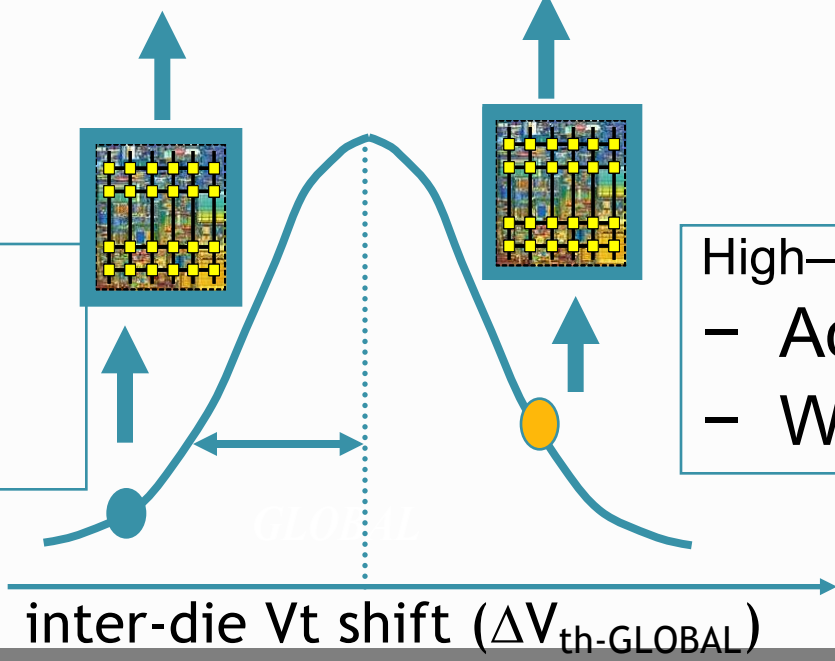Low-Vt Corners
- Read failure \uparrow
- Hold failure \uparrow





High-Vt Corners
- Access failure \uparrow
- Write failure \uparrow

Failures in SRAM Array

Overall Cell Failure:

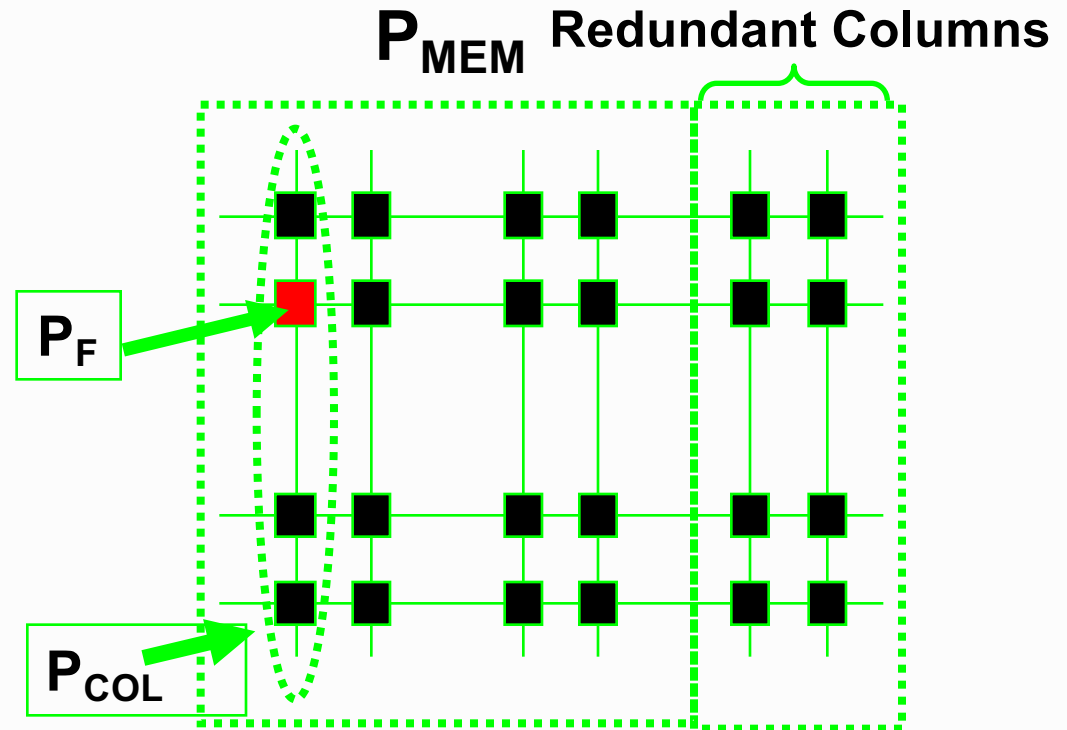
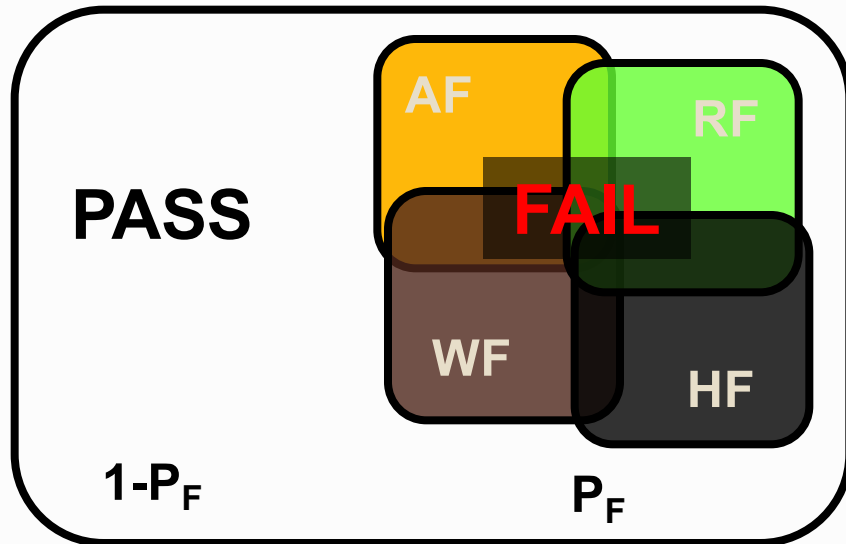
$$P_F = P[\text{Fail}] = P A_F \cup R_F \cup W_F \cup H_F$$



- P_{COL} : Probability that any of the cells in a column fail

$$P_{COL} = 1 - (1 - P_F)^{N_{ROW}}$$

Impact of Redundancy on Memory Failure

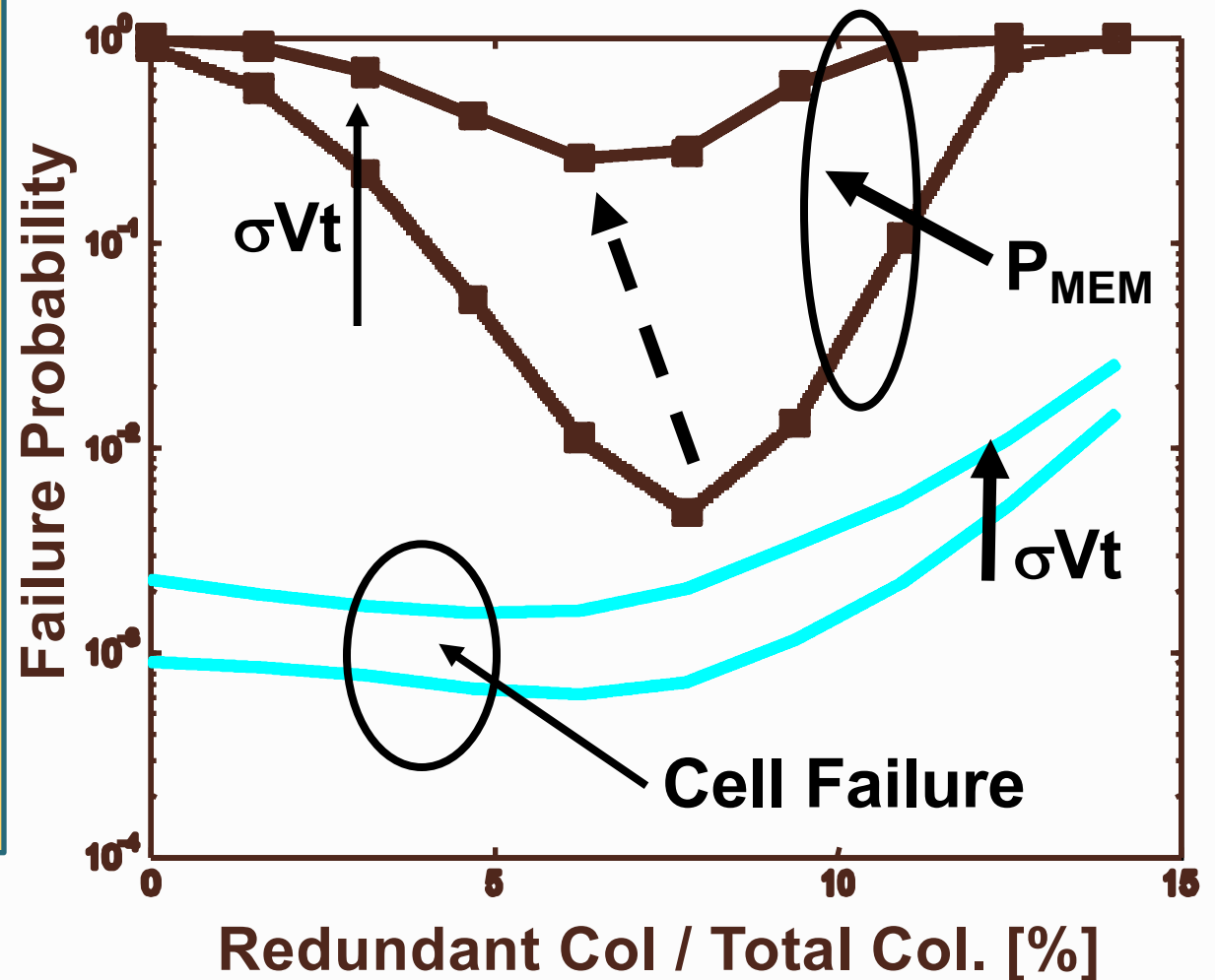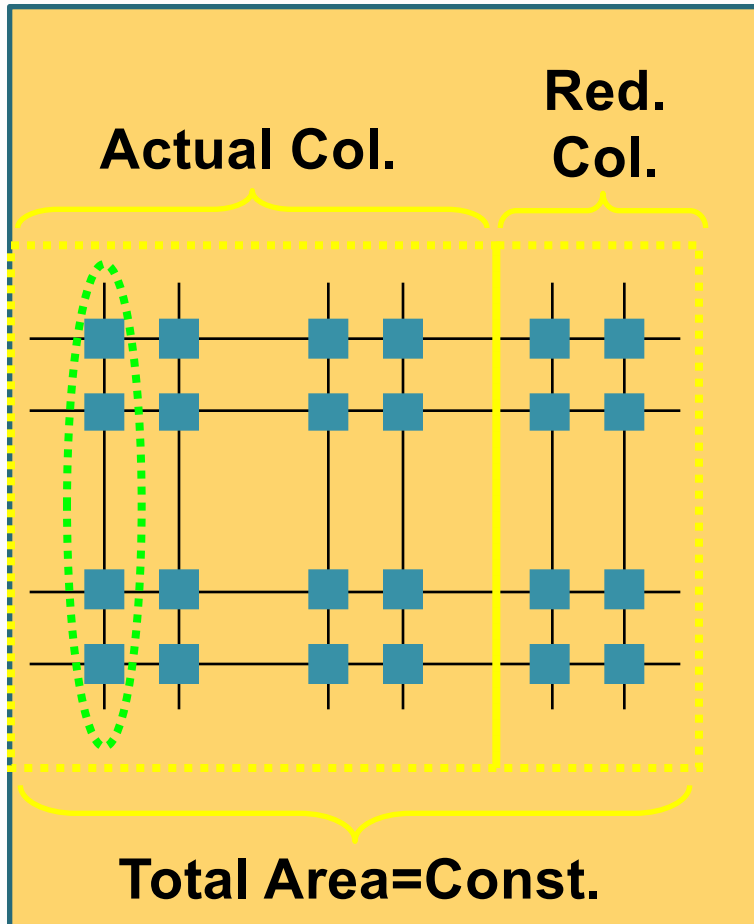


Larger redundancy

(1) more column to replace (less memory failure).

(2) smaller cell area (larger cell failure).

Transistor Sizing


 


Question

Array redundancy


- a) Improves cell stability
- b) Degrades cell performance (i.e increases read and write times)
- c) Does not require any change to cell peripheral circuits
- d) Row redundancy is better than column redundancy

Example: Multi-VCC for SRAM Cell

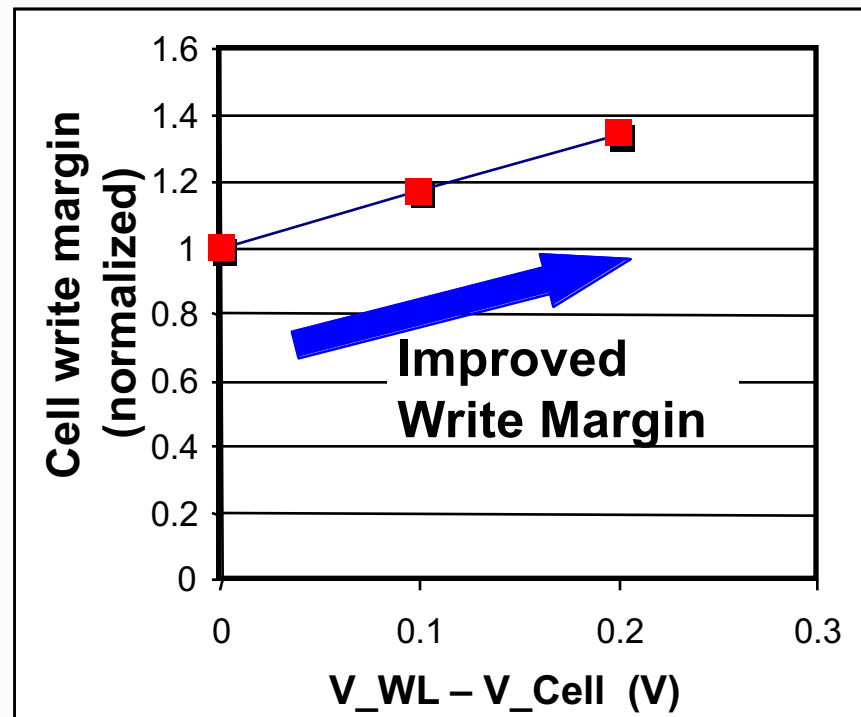 



- Create differential voltage between WL and Cell to decouple the Read & Write
 - Write: $V_{WL} > V_{Cell}$
 - Read: $V_{WL} < V_{Cell}$

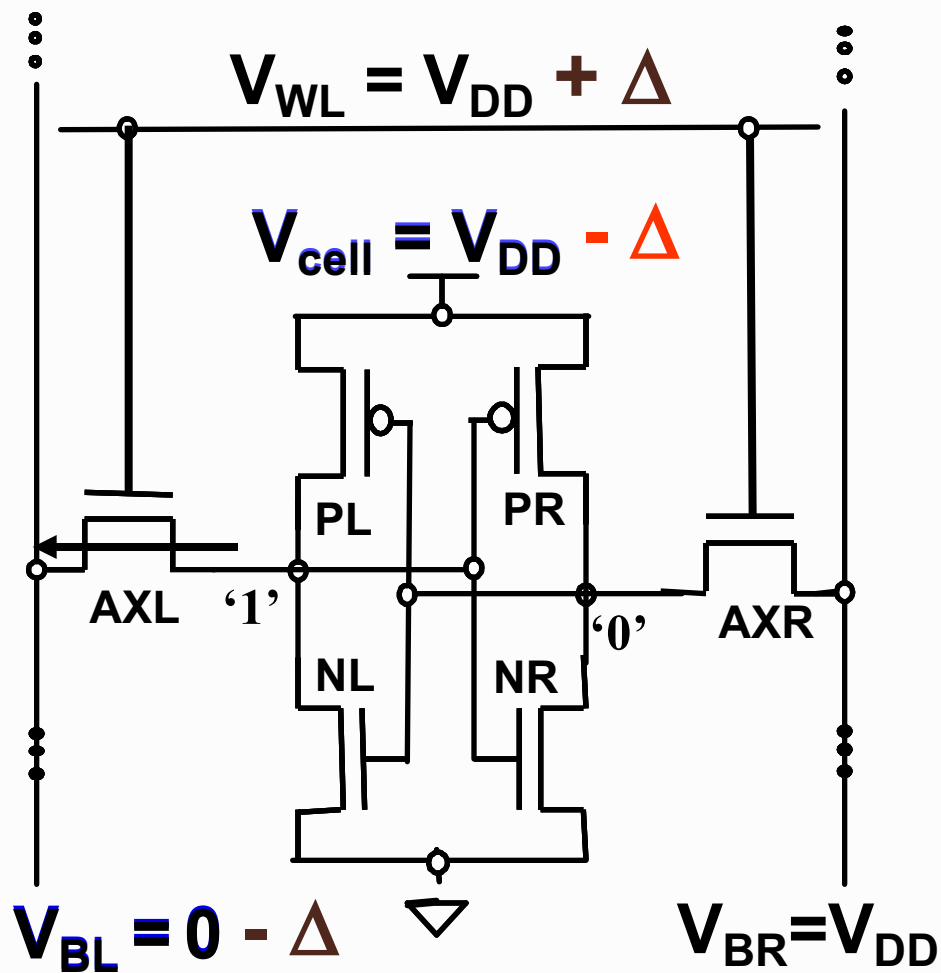Dynamic Circuit Techniques for Variation Tolerant SRAM




	Read	Write
V_{WL}	Lower $V_{WL} \Rightarrow$ lower V_{read} (weak AX)	Higher $V_{WL} \Rightarrow$ Strong AX helps discharge
V_{cs}	Higher $V_{cs} \Rightarrow$ lower V_{read} (strong PD) Higher V_{trip}	Lower $V_{cs} \Rightarrow$ Weak PUP
V_{BL}	Weak impact	Negative V_{BL} for 0 \Rightarrow strong AX helps discharge

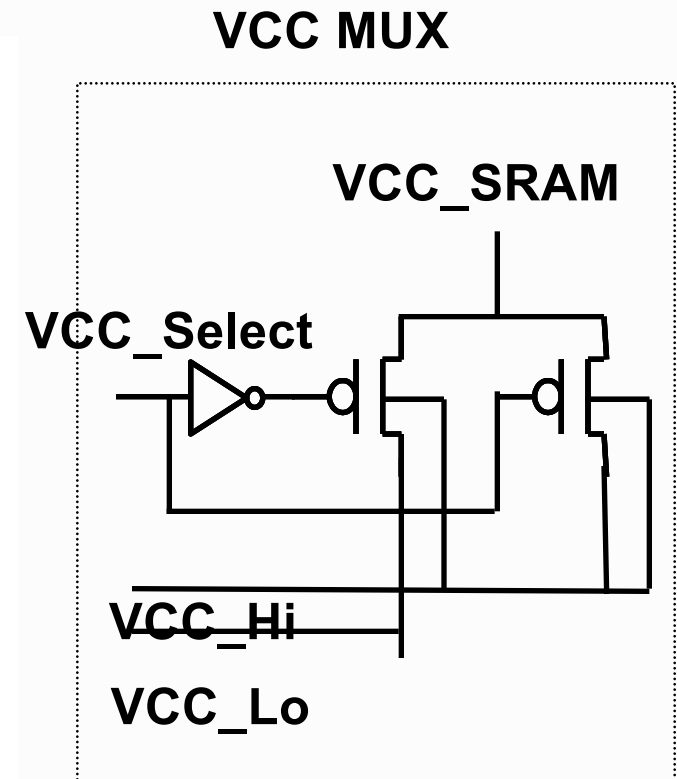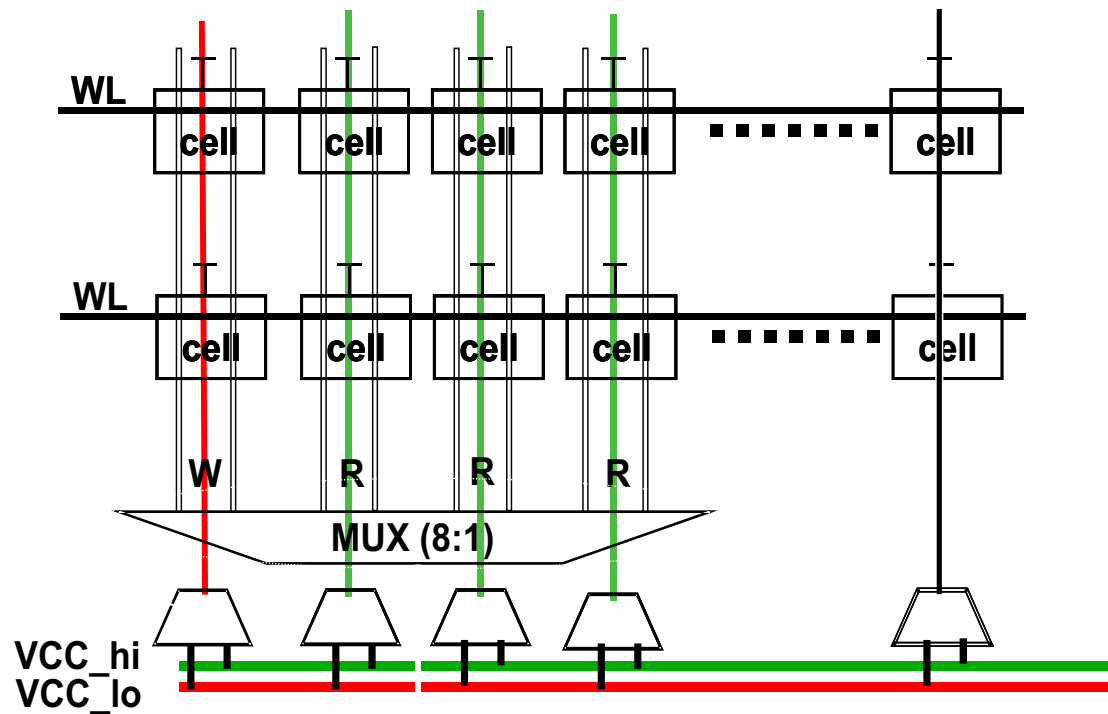Example: Dual-Vcc based Dynamic Circuit Techniques




- Dynamic VCC MUX is integrated into subarray
- VCC selection is along column direction to decouple the Read & Write

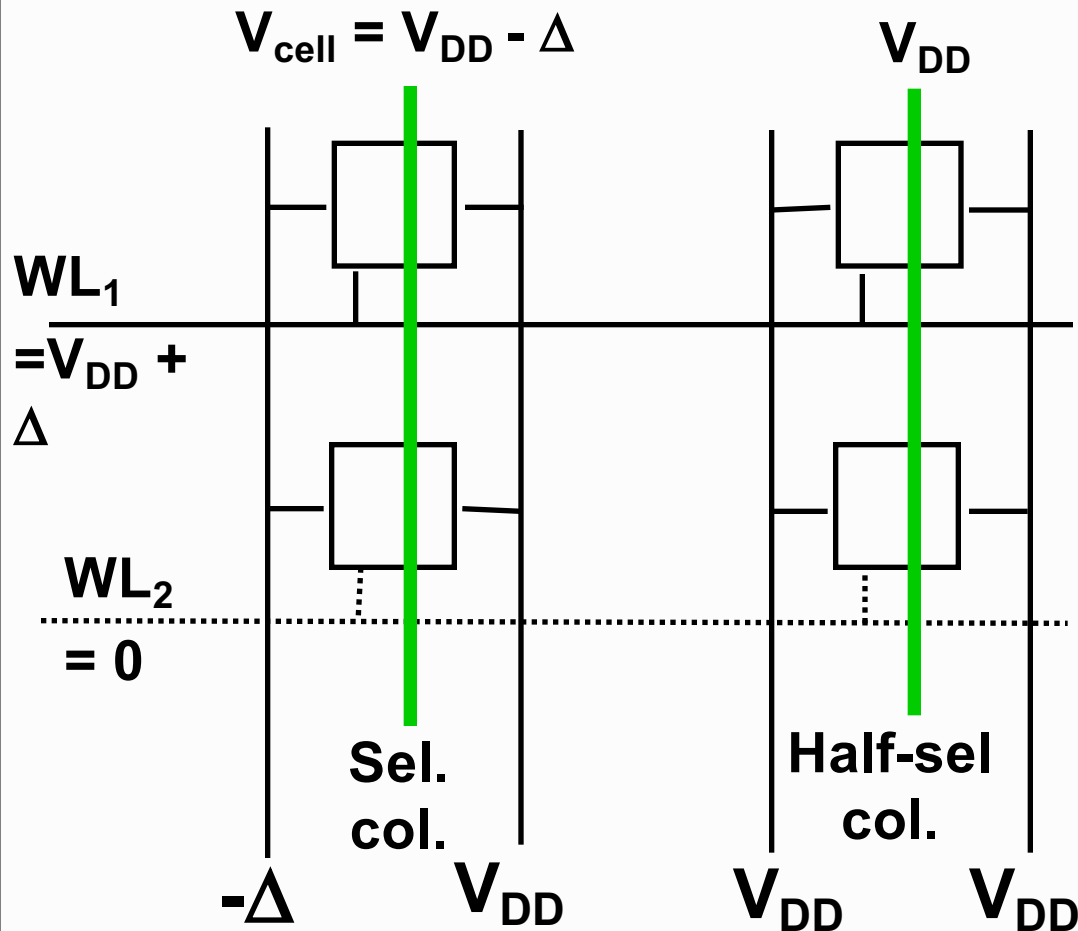Implementation Consideration: Half-Select Stability





- **Higher V_{WL}**
 - Row-based scheme
 - Degrades half-select read stability of the unselected columns
- **Lower V_{cell} or negative bit-line**
 - + Column-based scheme
 - + Half-select read stability remains same

Negative Bit Line Scheme


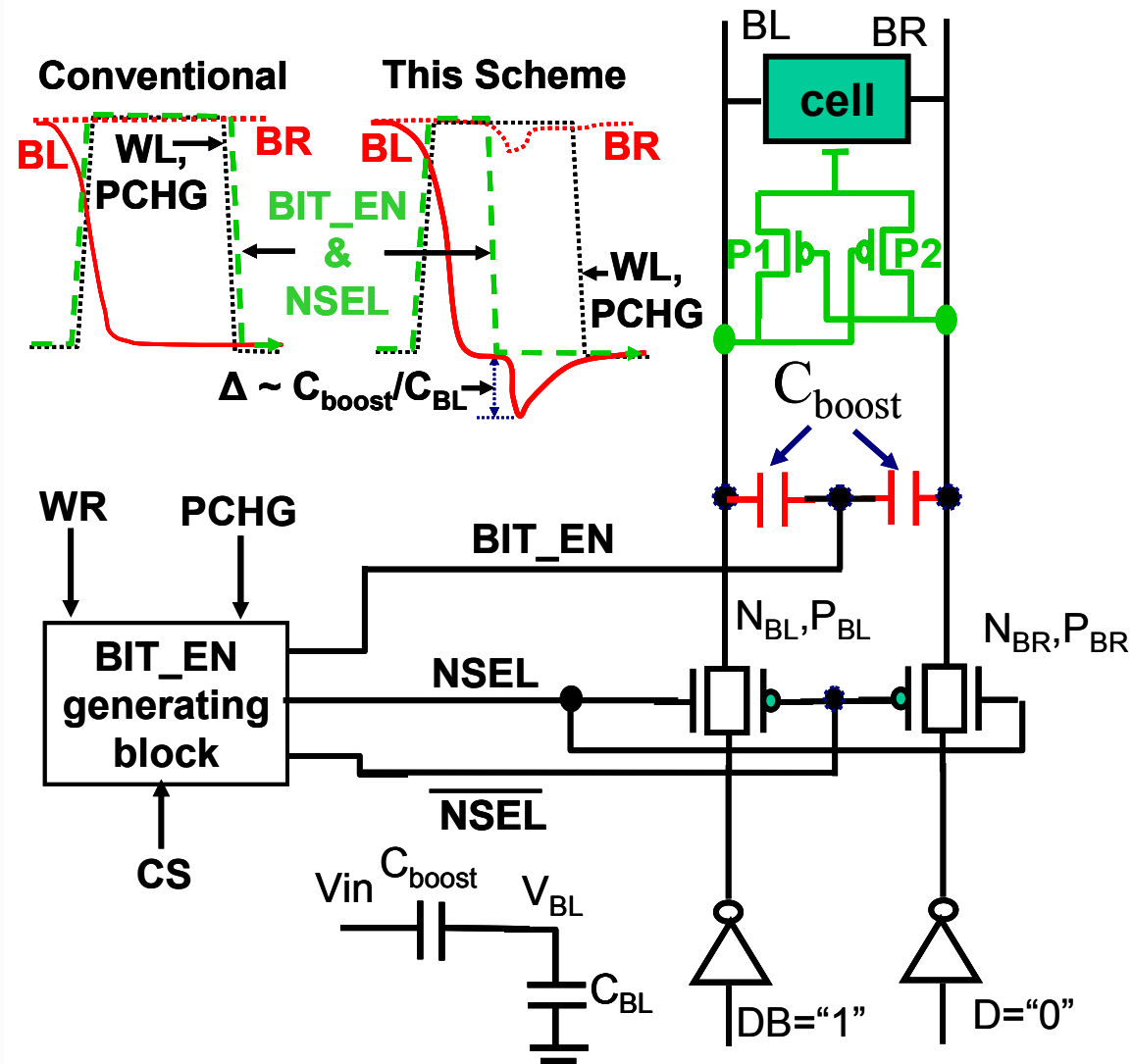


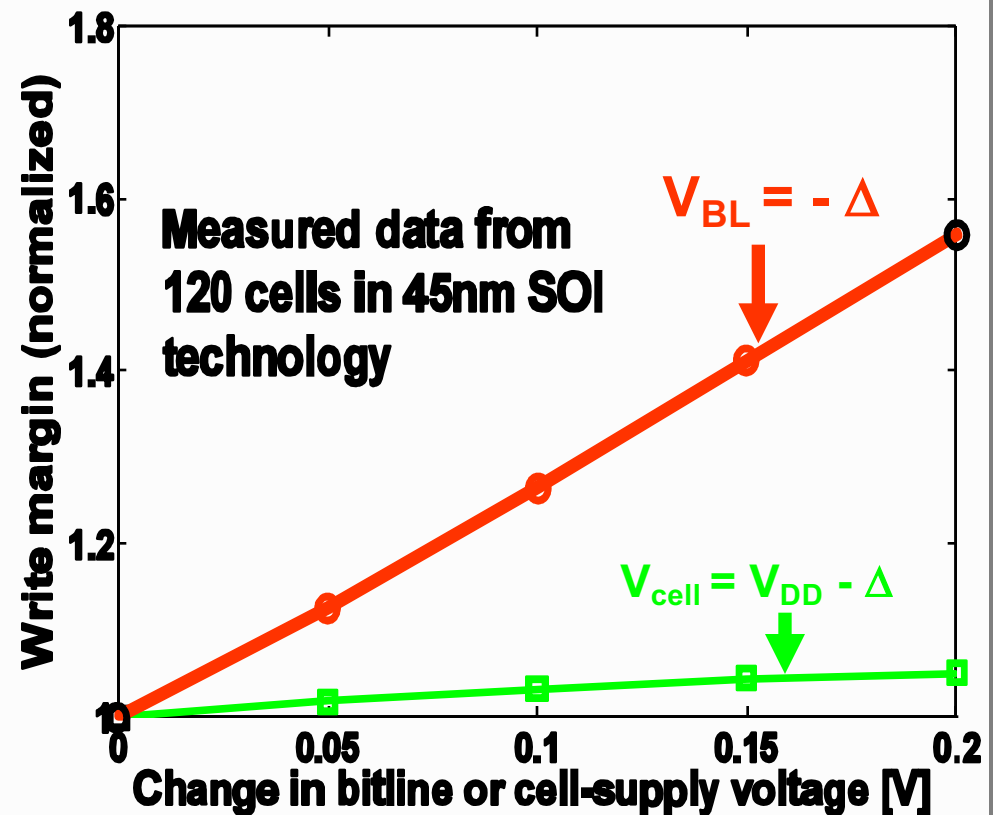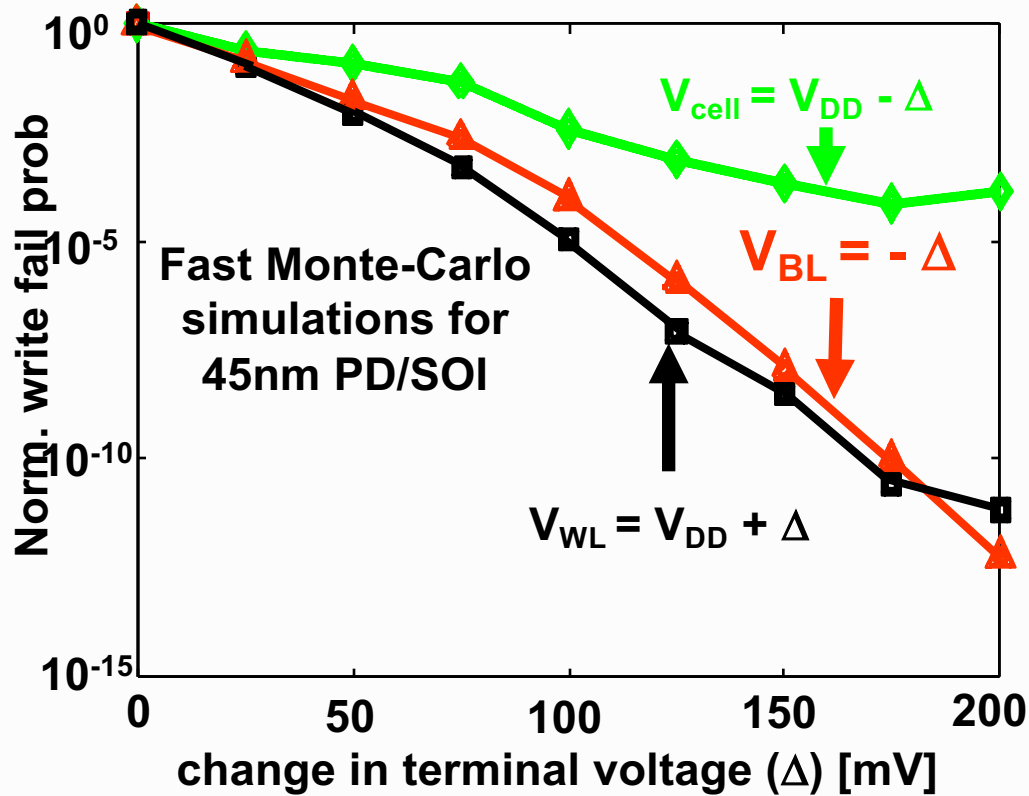Effectiveness Considerations: Writability improvement



- Various dynamic schemes have different effectiveness in improving writability for similar read stability
 - Higher V_{WL} is most effective

Impact on Active Data-Retention

 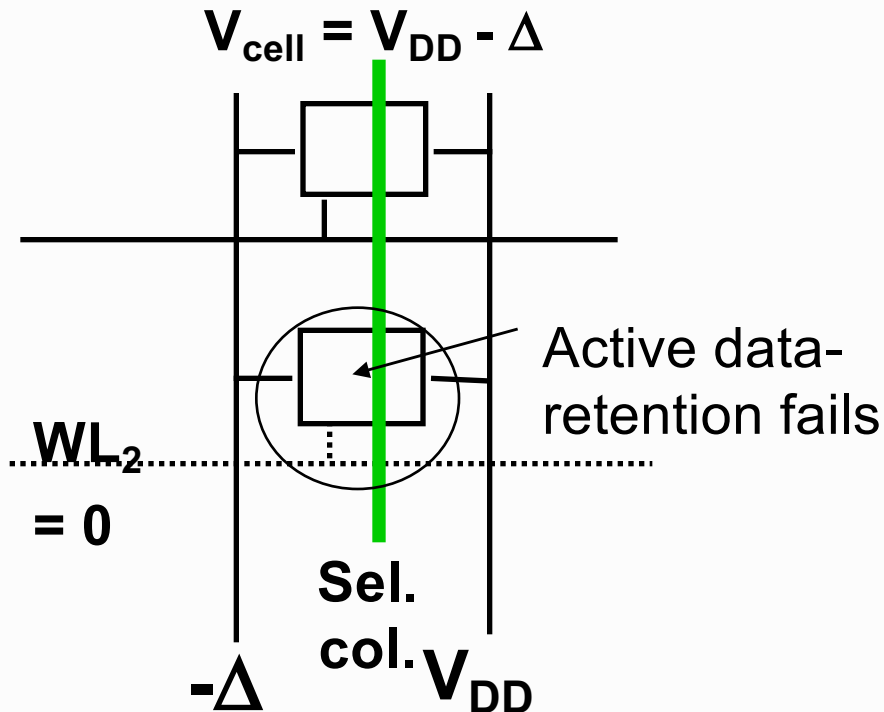


- Column based read-write control adversely impact the active data-retention failures
 - DC negative bitline has higher active data-retention failures
 - Tran-NBL and lower V_{cs} have comparable failure rates

Assist Methods


WLOD (WL Overdrive)

- Strengthen PG

 


VCDL ($V_{DD,CELL}$ Lowering)

Weaken PU

 


NBL (Negative BL)

- Strengthen PG

 


SBL (Suppressed BL)

Weaken BL noise

 


WLUD (WL Underdrive)

- Weaken PG

 


Proposed Dual-Transient WL (DTWL)

 - Dual-Transient WL (DTWL) controls WL transiently
- DTWL provides mix-up assist for read and write
 - Covers different process-corner
 - DTWL mitigate the impact of WLOD (WA)



different
process-corner

 

Question

Of the various assist methods

- a) Negative bit line scheme does not help 8-T sram cell
- b) Word line under drive does not help 8-T sram cell
- c) Word line over drive does not help 7-T conditionally decoupled sram cell
- d) VCDL does not help any kind of assymmetric sram cell

Block Diagram

