

# **Advanced Topics in VLSI**

**EE6361**

**Jan 2018**

# Course Objectives

- ❑ Introduce students to some relevant advanced topics of current interest in academia and industry
- ❑ Give the students a feel for research topics and what research means
- ❑ Make students aware of work happening in India

# Current Topics

- ❑ Embedded Memory Design
  - ❑ Built In Self Test (BIST) – Dr. C. P. Ravikumar, TI
  - ❑ SRAMs (Dr. Rahul Rao, IBM India)
  - ❑ eDRAMs ( Dr. Janakriaman, IITM)

# Learning Objectives for BIST

- ❑ Explain how memories are tested
- ❑ Explain how memory testing is different from digital testing
- ❑ Describe various memory faults
- ❑ Propose solutions to various memory faults
- ❑ Explain the need for ECC in memories
- ❑ Elaborate and explain the concept of BIST



# Learning Objectives for SRAM

- ❑ Articulate memory hierarchy and the value proposition of SRAMs in the memory chain + utilization in current processors
- ❑ Explain SRAM building blocks and peripheral operations and memory architecture (with physical arrangement)
- ❑ Articulate commonly used SRAM cells (6T vs 8T), their advantages and disadvantages
- ❑ Explain the operation of a non-conventional SRAM cells, and their limitations
- ❑ Explain commonly used assist methods
- ❑ Explain how variations impact memory cells

# Learning Objectives for EDRAM

- ❑ Explain the working of a (e)DRAM. What does Embedded mean?
- ❑ Explain the working of a feedback sense amplifier and modify existing designs to improve performance
- ❑ Calculate the voltage levels of operation of various components for an eDRAM
- ❑ Introduce stacked protect devices to reduce voltage stress of the WL driver

# Grading

- ❑ Assignments - 10%
- ❑ Quiz 1- 15%
- ❑ Quiz 2 -15%
- ❑ Project - 20%
- ❑ End Semester - 40%

# Course Schedule

- ❑ Thursday – 2:00 – 3:00 PM and 5:00 – 6:30 PM
  - ❑ Saturday possible for the BIST module?
- ❑ ESB 213B

# Embedded DRAM

**Janakiraman V**

Assistant Professor  
Electrical Department  
IIT Madras

# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example
- ❑ Gated Feedback Sense Amplifier (case study)
- ❑ References

# Acknowledgement


- Raviprasad Kuloor (Course slides were prepared by him)
- John Barth, IBM SRDC for most of the slides content
- Madabusi Govindarajan
- Subramanian S. Iyer
- Many Others

# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example



# Memory Classification revisited

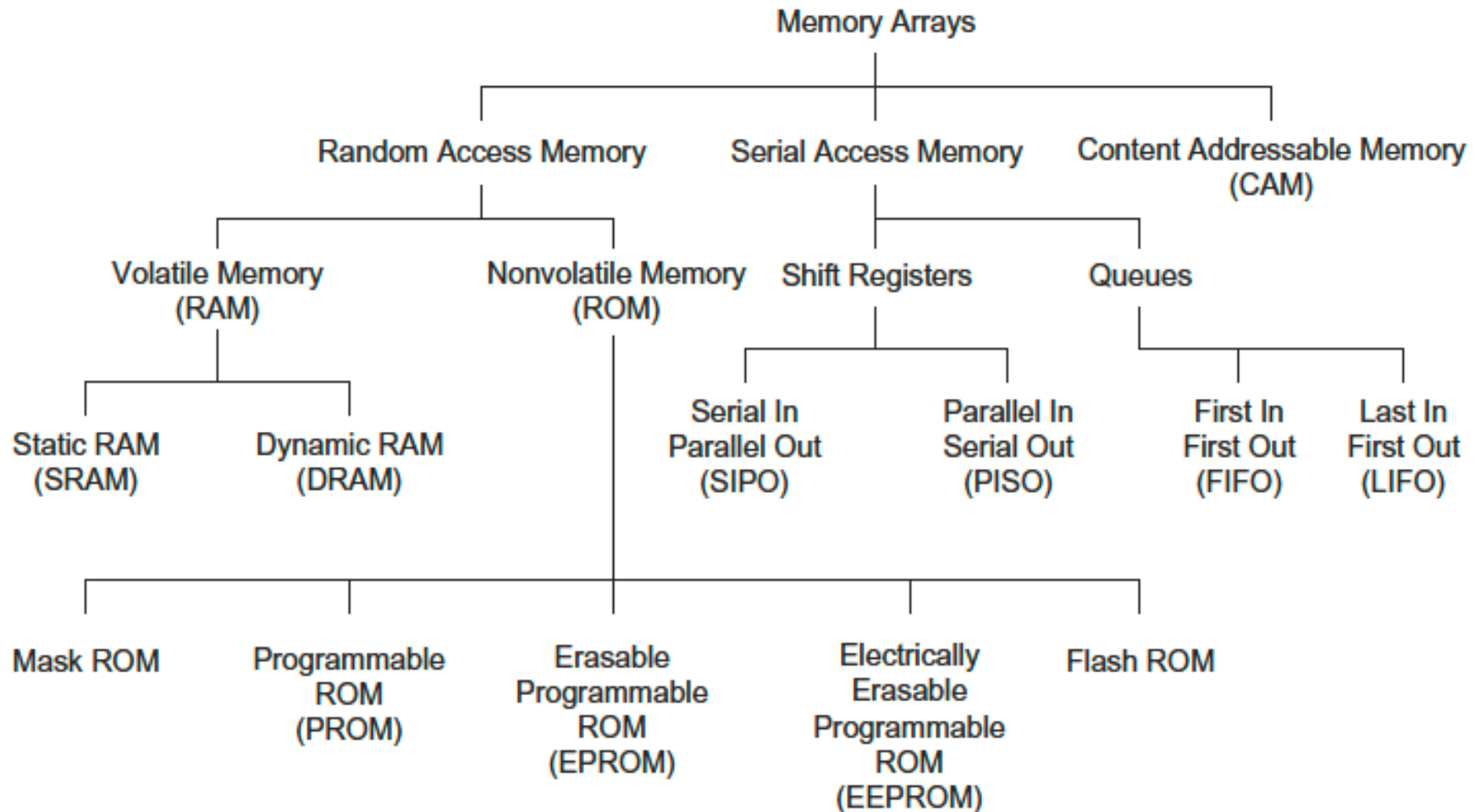

# Motivation for a memory hierarchy - infinite memory



Cycles per Instruction (CPI) = Number of processor clock cycles required per instruction

$CPI[\infty \text{ cache}]$

# Finite memory speed



$$\text{CPI} = \text{CPI}[\infty \text{ cache}] + \text{FCP}$$

Finite cache penalty

# Locality of reference - spatial and temporal

## Temporal

If you access something now you'll need it again soon


*e.g: Loops*

## Spatial

If you accessed something you'll also need its neighbor

*e.g: Arrays*

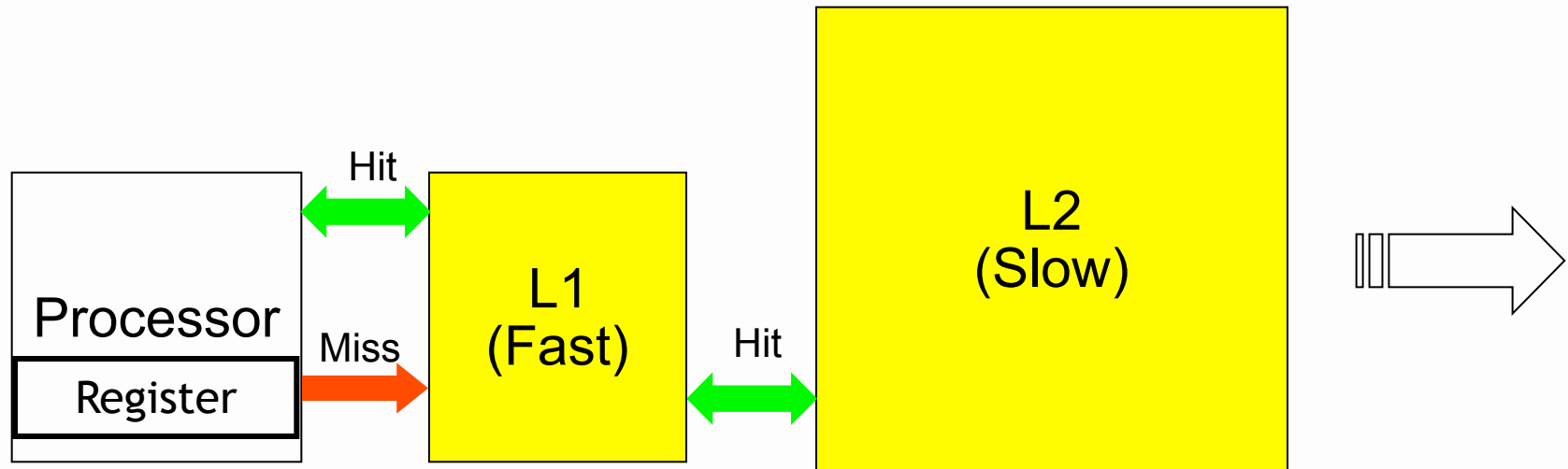*Exploit this to divide memory into hierarchy*




# Cache size impacts cycles-per-instruction

Logic-based  
eDRAM: Origins  
and rationale  
for use


R. E. Matick  
S. E. Schuster

 IBM J. RES. & DEV. VOL. 49 NO. 1 JANUARY 2005



Access rate reduces  $\rightarrow$  Slower memory is sufficient

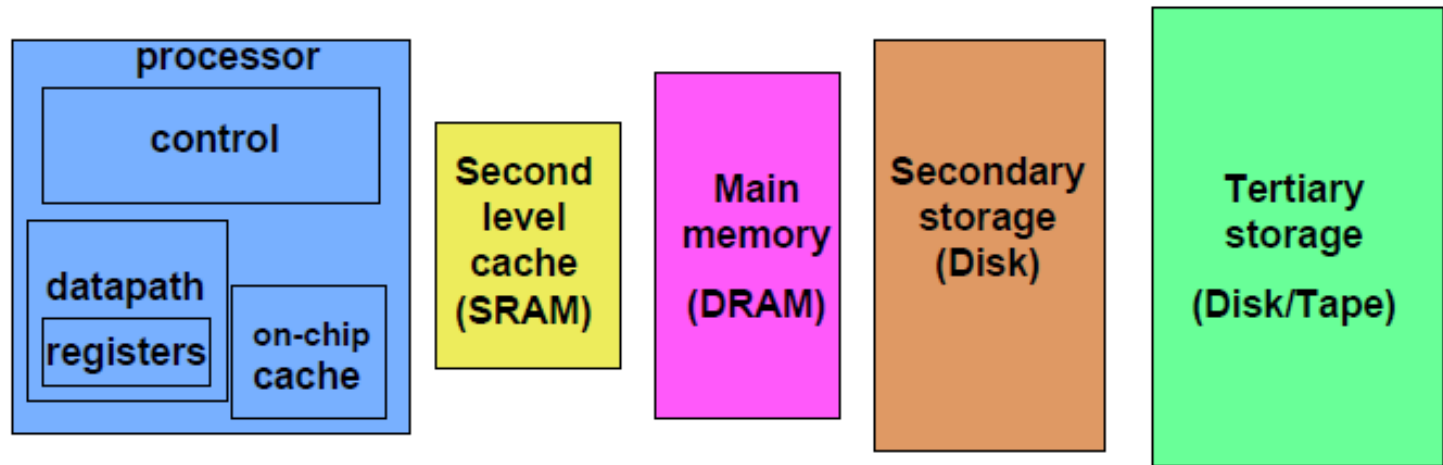
# Cache size impacts cycles-per-instruction



Speed	1ns	10ns	100ns	10ms	10sec
Size	B	KB	MB	GB	TB


For a 5GHz processor, scale the numbers by 5x
 
# Technology choices for memory hierarchy



# eDRAM L3 cache

Power7  
processor

 

Move L2,L3 Cache inside of the data hungry processor

Higher hit rate → Reduced FCP



# Embedded DRAM Advantages



## Memory Advantage

- 2x Cache can provide > 10% Performance
- ~3x Density Advantage over eSRAM
- 1/5x Standby Power Compared to SRAM
- Soft Error Rate 1000x lower than SRAM
- Performance ? DRAM can have lower latency !
- IO Power reduction

## Deep Trench Capacitor


- Low Leakage Decoupling
- 25x more Cap /  $\mu\text{m}^2$  compared to planar
- Noise Reduction = Performance Improvement
- Isolated Plate enables High Density Charge Pump

IBM Power7<sup>tm</sup>  
32MB eDRAM L3

  

# Cache performance - SRAM vs. DRAM


*Chart: Matick & Schuster, op. cit.*

 

# Embedded DRAM Performance

45nm eDRAM vs. SRAM Latency

eDRAM Faster than SRAM

 

Memory Block Size Built With 1Mb Macros

Barth ISSCC 2011

# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example

# Fundamental DRAM Operation


Memory Arrays are composed of Row and Columns

Most DRAMs use 1 Transistor as a switch and  
1 Cap as a storage element (Dennard 1967)



Single Cell Accessed by Decoding One Row / One Column (Matrix)

Row (Word-Line) connects storage Caps to Columns (Bit-Line)

 Storage Cap Transfers Charge to Bit-Line, Altering Bit-Line Voltage



# 1T1C DRAM Cell Terminals

 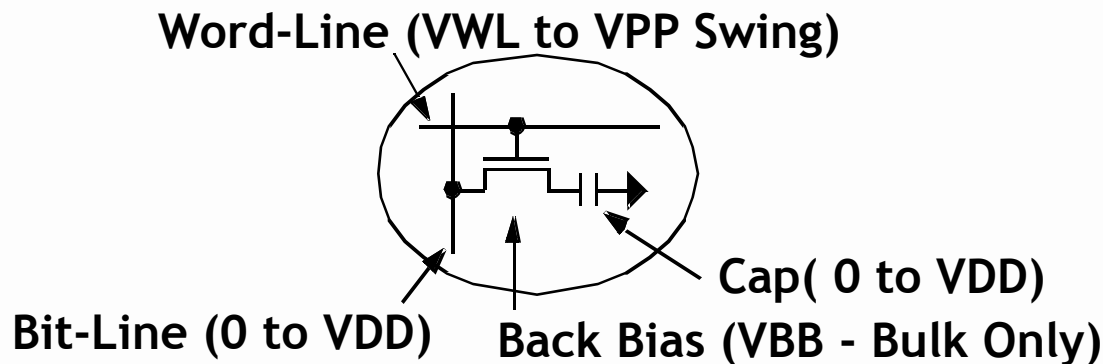


**VWL:** Word-Line Low Supply, GND or Negative for improved leakage

**VPP:** Word-Line High Supply, 1.8V up to 3.5V depending on Technology  
Required to be at least a  $V_t$  above VDD to write full VDD


**VBB:** Back Bias, Typically Negative to improve Leakage  
Not practical on SOI
 
# DRAM cell Cross section



- Store their contents as charge on a capacitor rather than in a feedback loop.
- 1T dynamic RAM cell has a transistor and a capacitor



CMOS VLSI design - PEARSON

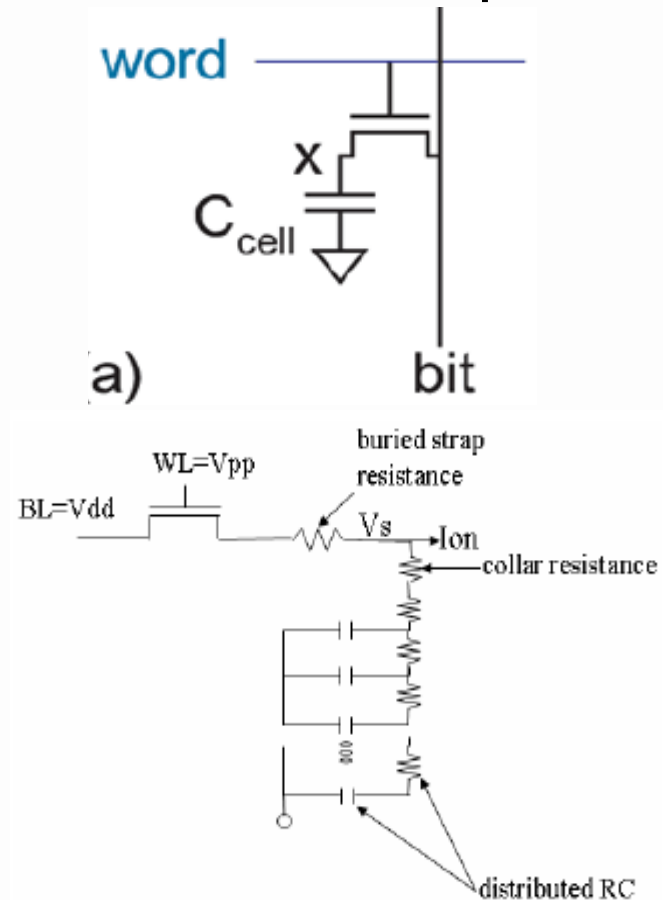

# Storing data '1' in the cell

  


$V_{gs}$  for pass transistor reduces as bitcell voltage rises, increasing  $R_{on}$


Why there is a reduction in cell voltage after WL closes? Experiment



# MIM Cap v/s Trench

 

**MIM eDRAM Process**

 


**Trench eDRAM Process**



- Stack capacitor requires more complex process
- M1 height above gate is increased with stacked capacitor
  - M1 parasitics significantly change when wafer is processed w/o eDRAM
  - Drives unique timings for circuit blocks processed w/ and w/o eDRAM
    - Logic Equivalency is compromised – **Trench is Better Choice**

# Classical DRAM Organization

 

# DRAM Subarray


 


FIGURE 12.43 DRAM subarray

# Trench cell layout and cross-section

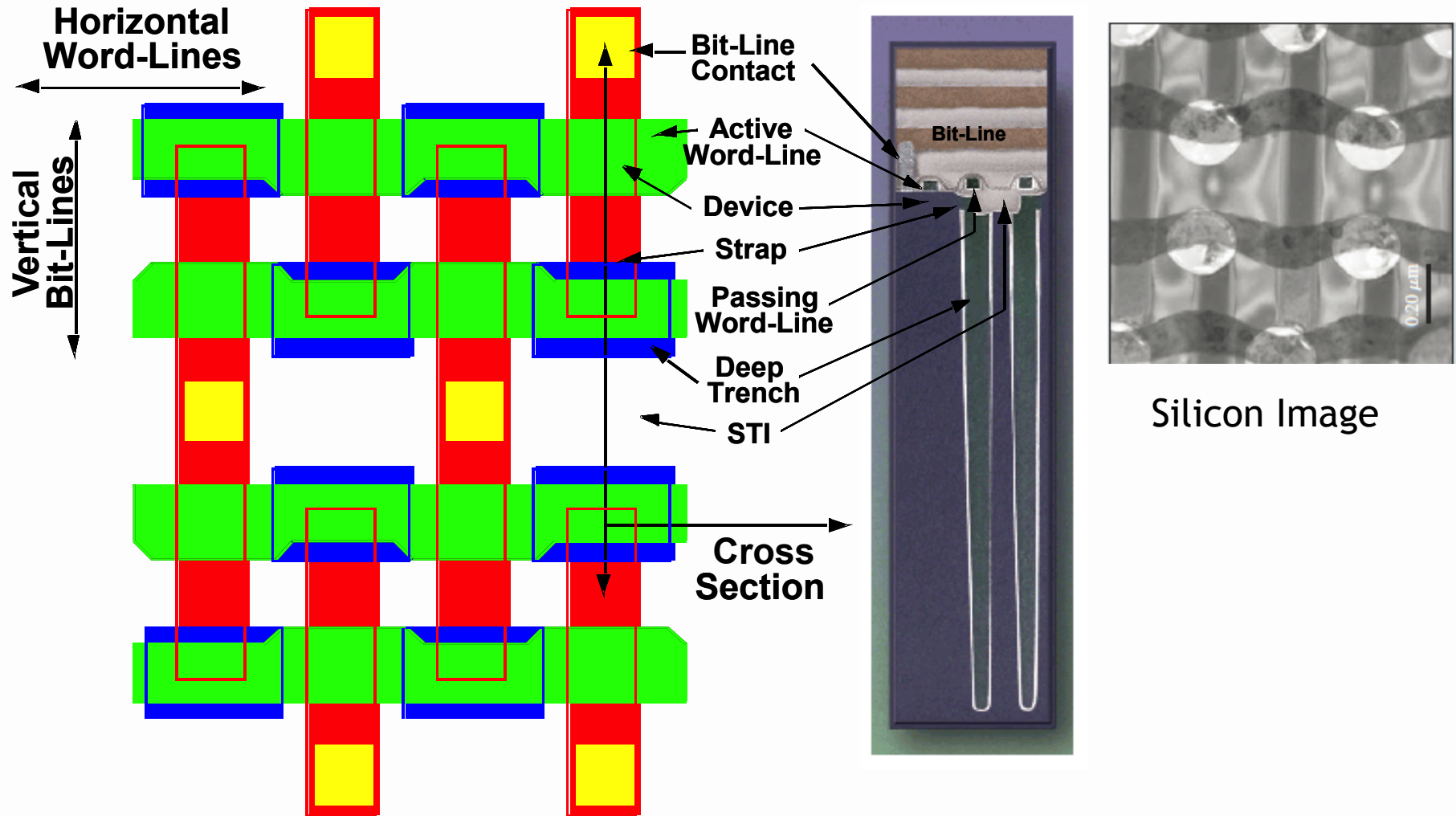

# References so far

Barth, J. et al., “A 300MHz Multi-Banked eDRAM Macro Featuring GND Sense, Bit-line Twisting and Direct Reference Cell Write,” ISSCC Dig. Tech. Papers, pp. 156-157, Feb. 2002.

Barth, J. et. al., “A 500MHz Multi-Banked Compilable DRAM Macro with Direct Write and Programmable Pipeline,” ISSCC Dig. Tech. Papers, pp. 204-205, Feb. 2004.

Barth, J. et al., “A 500MHz Random Cycle 1.5ns-Latency, SOI Embedded DRAM Macro Featuring a 3T Micro Sense Amplifier,” ISSCC Dig. Tech. Papers, pp. 486-487, Feb. 2007.


Barth, J. et al., “A 45nm SOI Embedded DRAM Macro for POWER7™ 32MB On-Chip L3 Cache,” ISSCC Dig. Tech. Papers, pp. 342-3, Feb. 2010.

Butt, N., et al., “A 0.039 $\mu$ m<sup>2</sup> High Performance eDRAM Cell based on 32nm High-K/Metal SOI Technology,” IEDM pp. 27.5.1-2, Dec 2010.



Bright, A. et al., “Creating the BlueGene/L Supercomputer from Low-Power SoC ASICs,” ISSCC Dig. Tech. Papers, pp. 188-189, Feb. 2005.
 
# DRAM Read, Write and Refresh

- Write:
  - 1. Drive bit line
  - 2. Select row
- Read:
  - 1. Precharge bit line
  - 2. Select row
  - 3. Cell and bit line share charges
    - Signal developed on bitline
  - 4. Sense the data
  - 5. Write back: restore the value
- Refresh
  - 1. Just do a dummy read to every cell → auto write-back




# Cell transfer ratio

 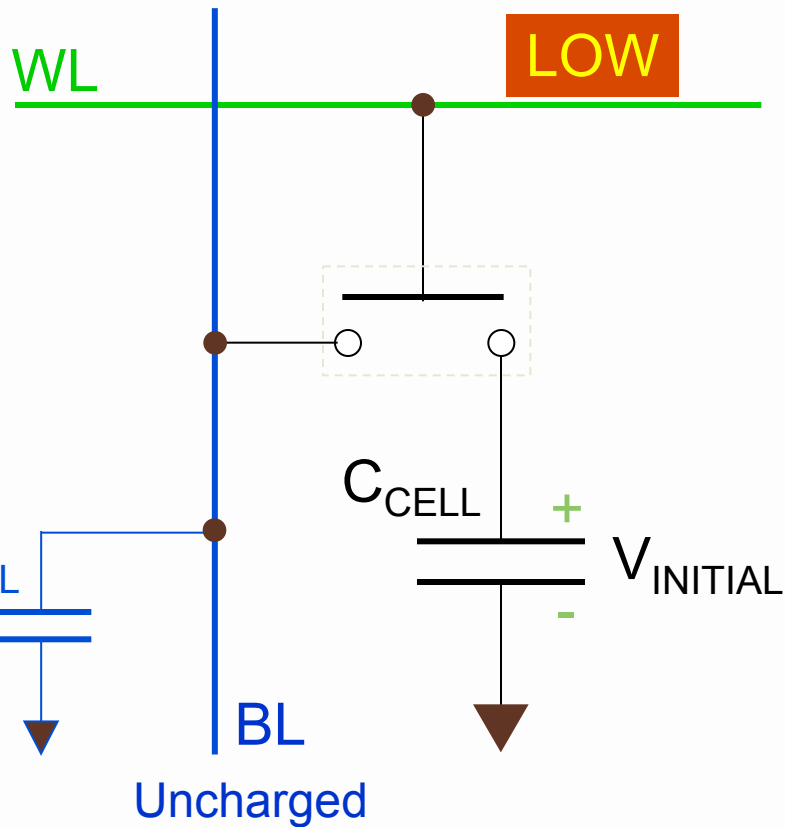

$$C_{CELL} \times V_{INITIAL} = (C_{CELL} + C_{BL}) \times V_{FINAL}$$

$$\text{Transfer ratio} = C_{CELL} / (C_{CELL} + C_{BL})$$

# Cell Charge Transfer

 



# Transfer Ratio and Signal

DBit-Line Voltage Calculated from Initial Conditions and Capacitances:

$$DV = V_{bl} - V_f = V_{bl} - \frac{Q}{C} = V_{bl} - \left[ \frac{C_{bl} * V_{bl} + C_{cell} * V_{cell}}{C_{bl} + C_{cell}} \right]$$

$$DV = (V_{bl} - V_{cell}) \left[ \frac{C_{cell}}{C_{bl} + C_{cell}} \right]$$

↙ Transfer Ratio (typically 0.2)

DBit-Line Voltage is Amplified with Cross Couple “Sense Amp”


Sense Amp Compares Bit-Line Voltage with a Reference

Bit-Line Voltage - Reference = Signal

Pos Signal Amplifies to Logical ‘1’, Neg Signal Amplifies to Logical ‘0’

# Sensing $\rightarrow$ Signal Amplification
 
## Differential Voltage Amplified by Cross Couple Pair




When Set Node  $< (V+DV) - V_{tn1}$ ,  $I+$  will start to flow (On-Side Conduction)

When Set Node  $< (V) - V_{tn0}$ ,  $I$  will start to flow (Off-Side Conduction)

Off-Side Conduction Modulated by Set Speed and Amount of Signal

Complimentary X-Couple Pairs provide Full CMOS Levels on Bit-Line

# Bits per Bit-Line v/s Transfer Ratio

 

# Segmentation

**Array Segmentation Refers to WL / BL Count per Sub-Array**

**Longer Word-Line is Slower but more Area efficient (Less Decode/Drivers)**

**Longer Bit-Line (more Word-Lines per Bit-Line)**

- Less Signal (Higher Bit-Line Capacitance = Lower Transfer Ratio)

- More Power (Bit-Line CV is Significant Component of DRAM Power)

- Slower Performance (Higher Bit-Line Capacitance = Slower Sense Amp)

- More Area Efficient (Fewer Sense Amps)

**Number of Word-Lines Activated determines Refresh Interval and Power**

- All Cells on Active Word-Line are Refreshed

- All Word-Lines must be Refreshed before Cell Retention Expires

- 64ms Cell Retention / 8K Word Lines = 7.8us between refresh cycles

- Activating 2 Word-Lines at a time = 15.6us, 2x Bit-Line CV Power

# Choice of SA

Depending on signal developed SA architecture is chosen

## **Direct sensing**

- Requires large signal development

- An inverter can be used for sensing

- Micro sense amp (uSA) is another option

## **Differential sense amp**

- Can sense low signal developed

This is choice between area, speed/performance

# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example


# DRAM Operation Details (Case Study)

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 43, NO. 1, JANUARY 2008

**A 500 MHz Random Cycle, 1.5 ns Latency, SOI Embedded DRAM Macro Featuring  
a Three-Transistor Micro Sense Amplifier (John Barth/IBM)**

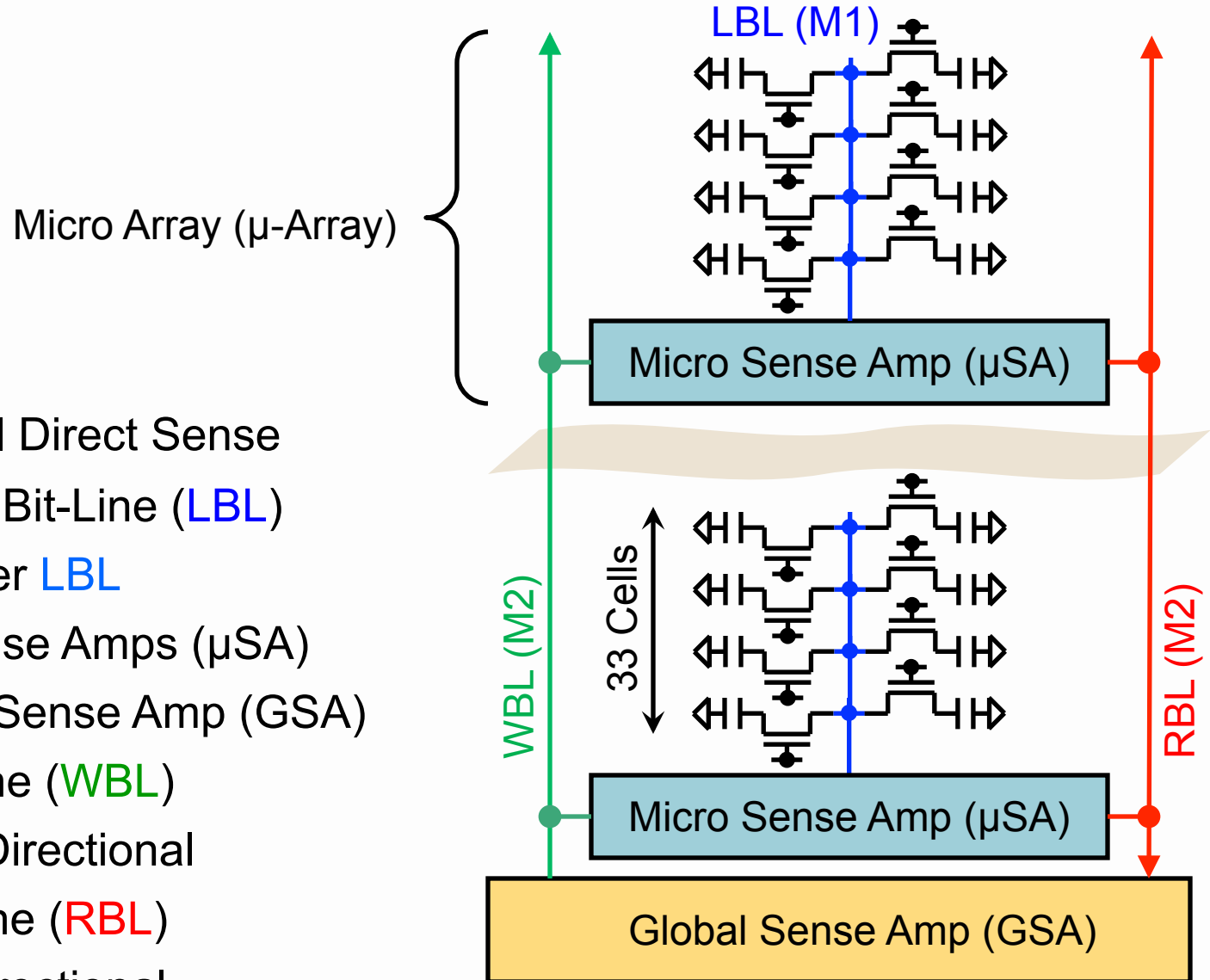
# Micro Sense Architecture

- Hierarchical Direct Sense
- Short Local Bit-Line (**LBL**)
  - 33 Cells per **LBL**
- 8 Micro Sense Amps ( $\mu$ SA) per Global Sense Amp (GSA)
- Write Bit-Line (**WBL**)
  - Uni-Directional
- Read Bit-Line (**RBL**)
  - Bi-Directional






# Micro Sense Hierarchy - Three levels

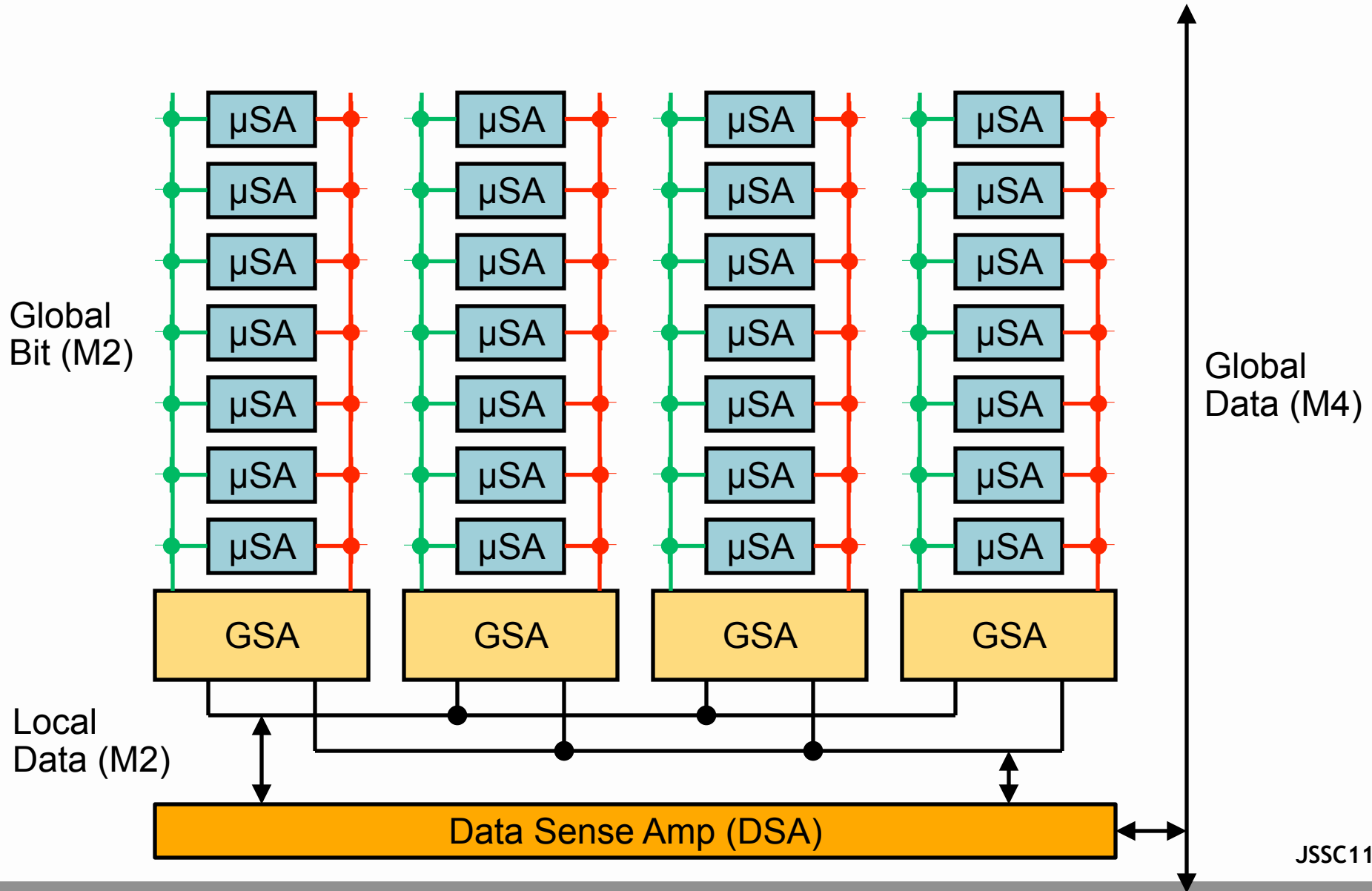

# 3T uSA operation

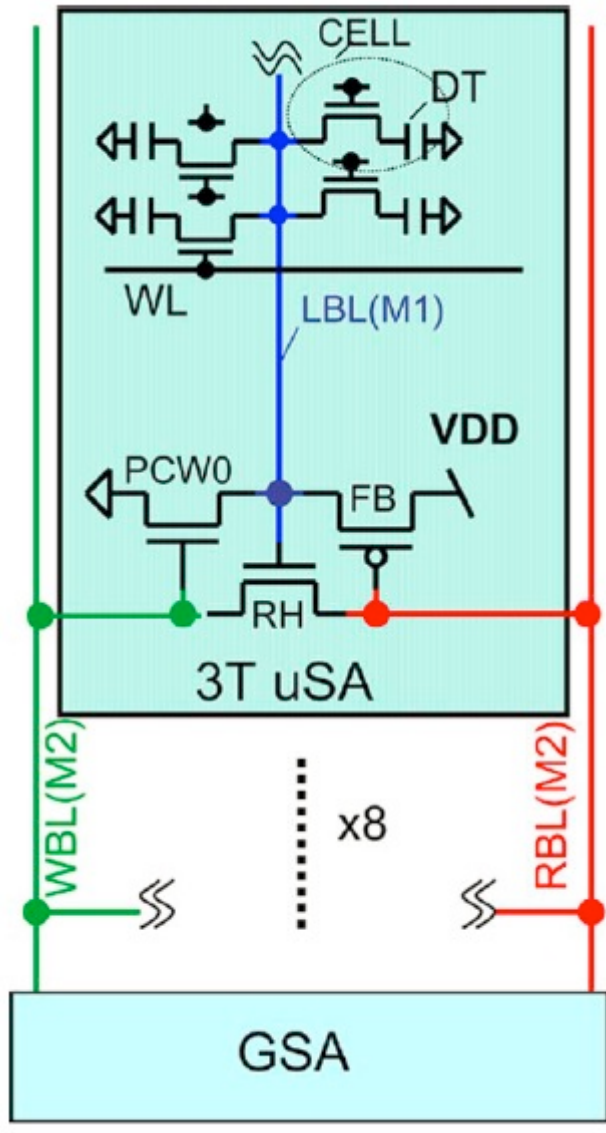

## Pre-charge

WL is low. WBL and RBL both pre-charged to HIGH. Next GSA drives WBL low. LBL floats to GND level

## Read “0”

LBL remains LOW. RBL is HIGH. Sensored as a “0”

## Read “1”

LBL is HIGH. Turns on RH, pulls RBL LOW. + feedback as pFET FB turns ON. Sensored as a “1”



## Write “1”

GSA pulls RBL to GND. FB pFET turns ON. Happens while WL rises (direct write)

## Write “0”

WBL is HIGH, PCW0 ON. Clamps LBL to GND. As WL activates.

# Micro Sense Amp Simulations

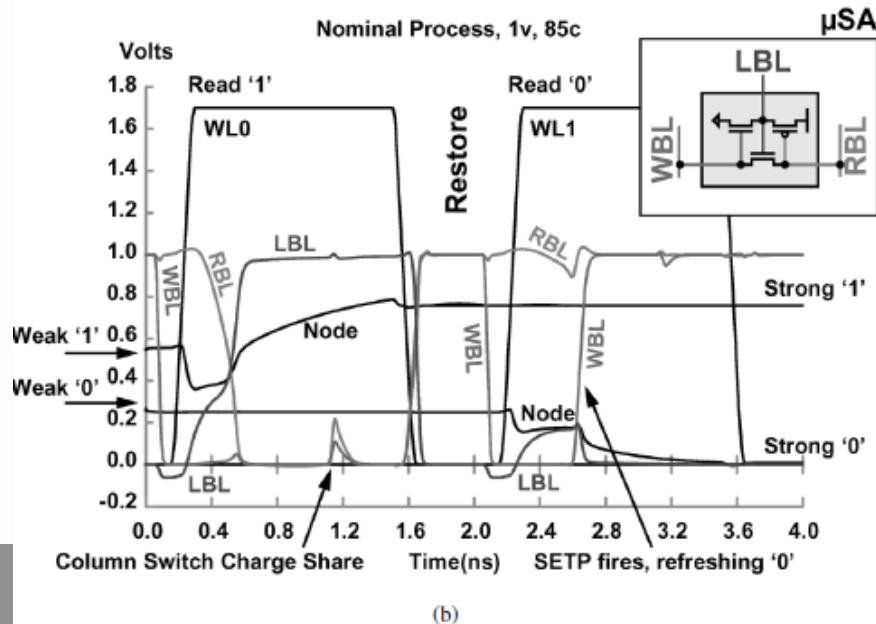 

IEEE JOURNAL OF SOLID-STATE CIRCUITS,  
VOL. 43, NO. 1, JANUARY 2008


A 500 MHz Random Cycle, 1.5 ns  
Latency, SOI Embedded DRAM Macro  
Featuring a Three-Transistor Micro  
Sense Amplifier

JSSC08

 
# Layout Floor plan of Array+SA

GSA Should fit into the bitcell width or  $n \times \text{bitcell width}$

Thus, distributed GSA on two sides of bitcell array




# Column Interleave

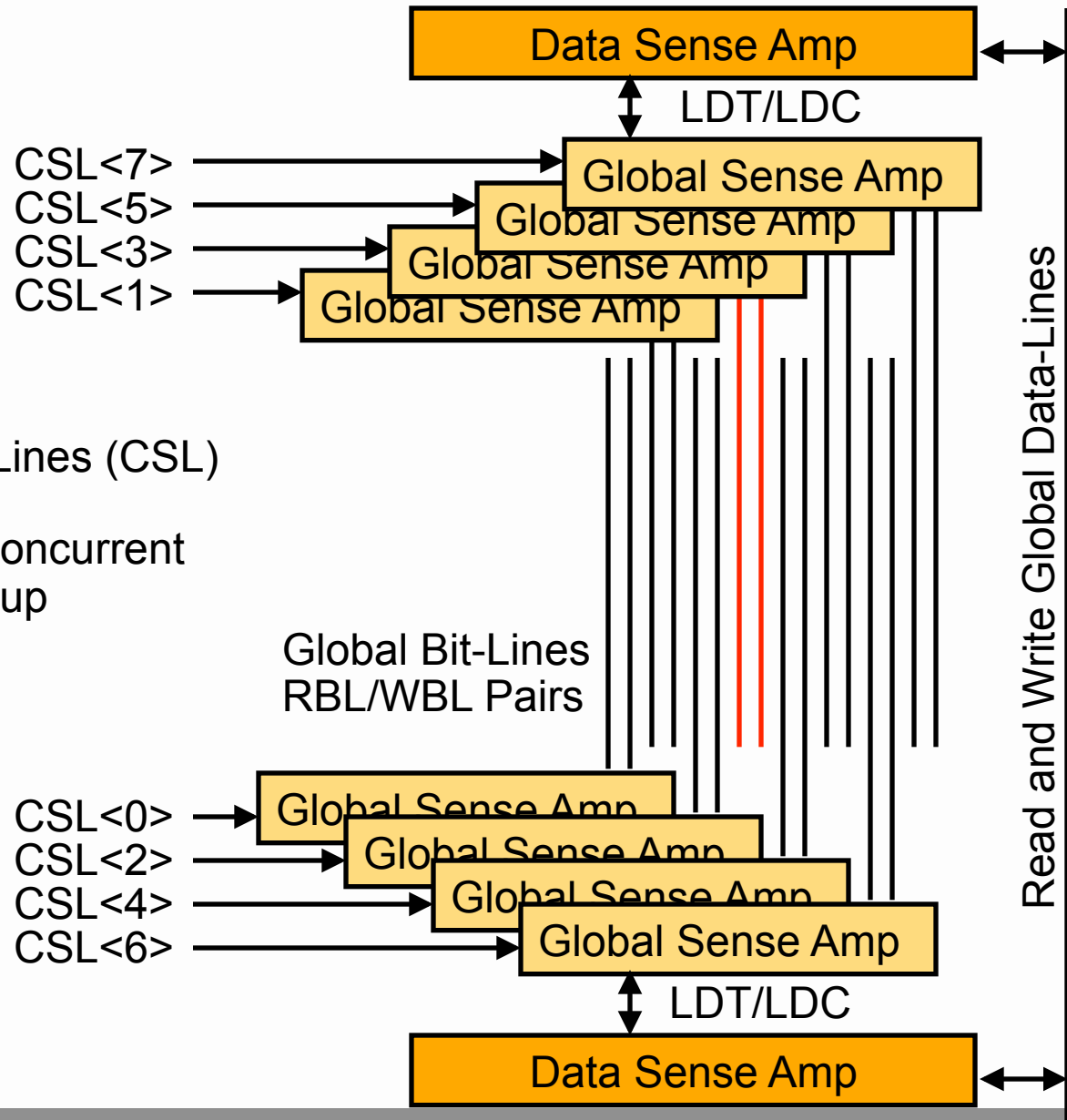


- 1 of 8 Column Select Lines (CSL)
- Fire Early for Write
- Fire Late to Support Concurrent Cache Directory Lookup

# LAYOUT of array

 

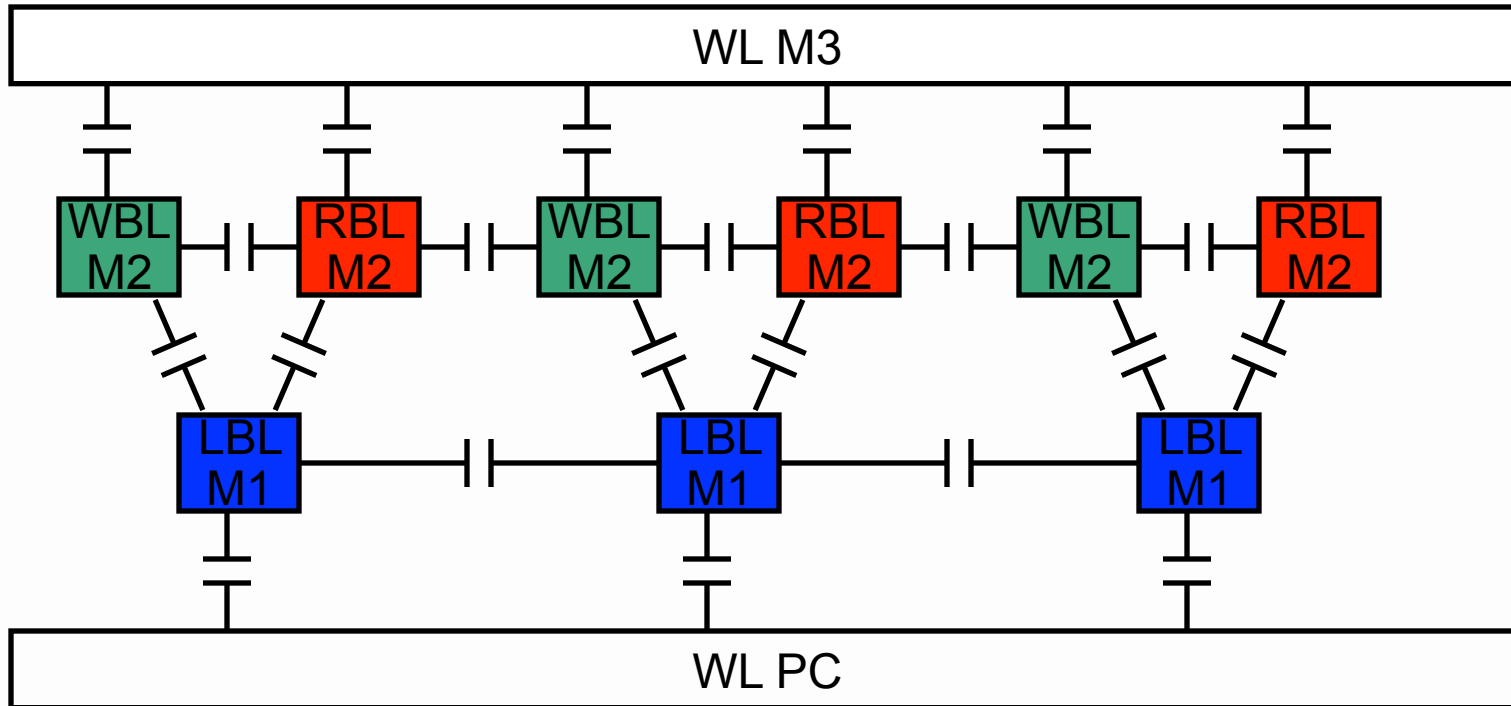
# Micro Sense Local Bit-line Cross Section



Single Ended Sense – Twist not effective  
Line to Line Coupling must be managed


# Micro Sense Coupling Mechanisms

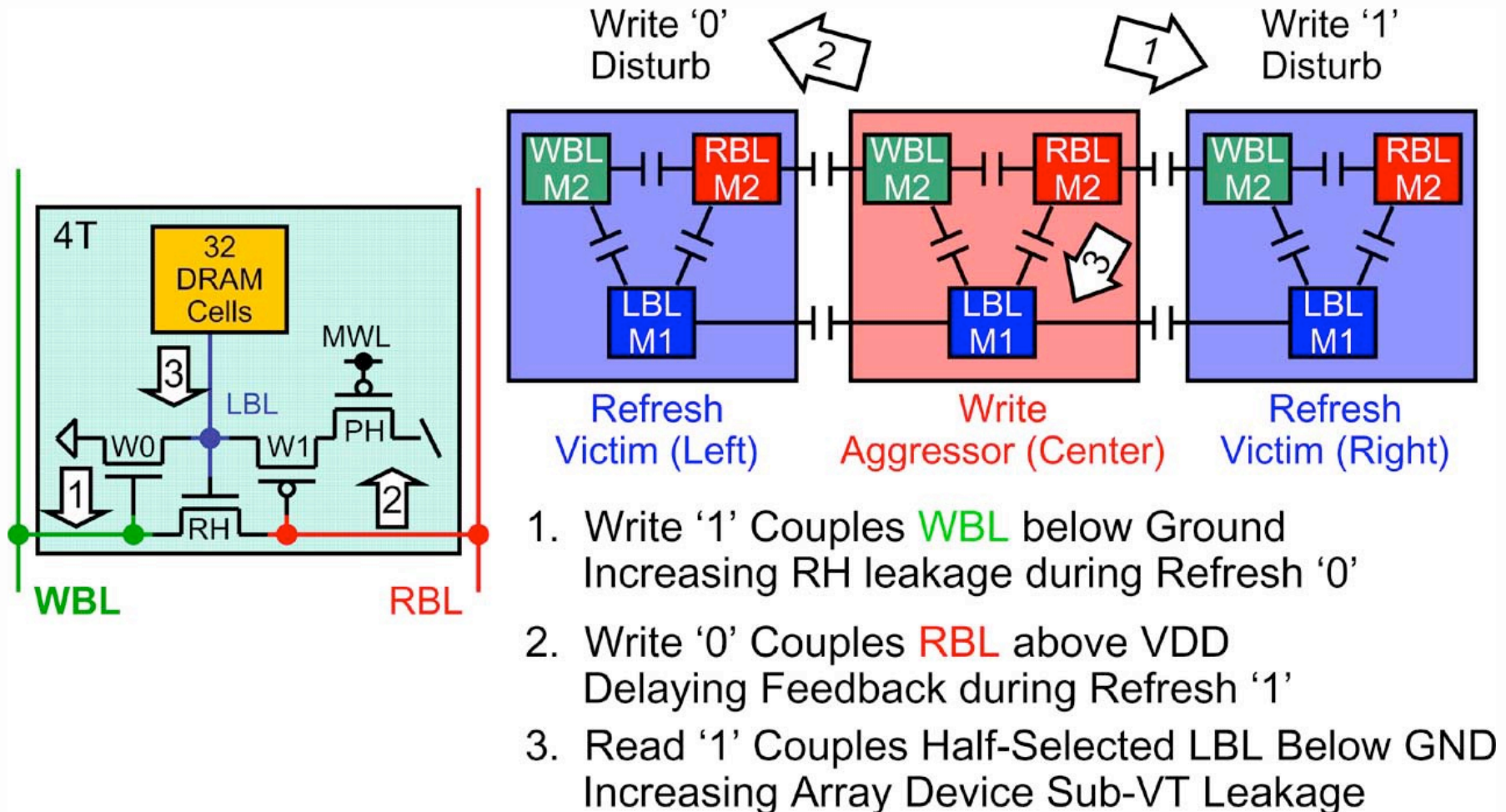




# Micro Sense Evolution

 1. Write Zero (W0)
2. Read Head (RH)
3. Feed-Back (FB)




Barth, ISSCC'07

 4. PFET Header (PH)
  - LBL Power Gate
  - LBL Leakage



Klim, VLSI'07

5. Pre-Charge (PC)
  - WBL Power (Write '0' Only)
6. NFET Footer (NF)
  - RBL Leakage
  - Decompose Pre-Charge and Read Enable (MWL\_RE)

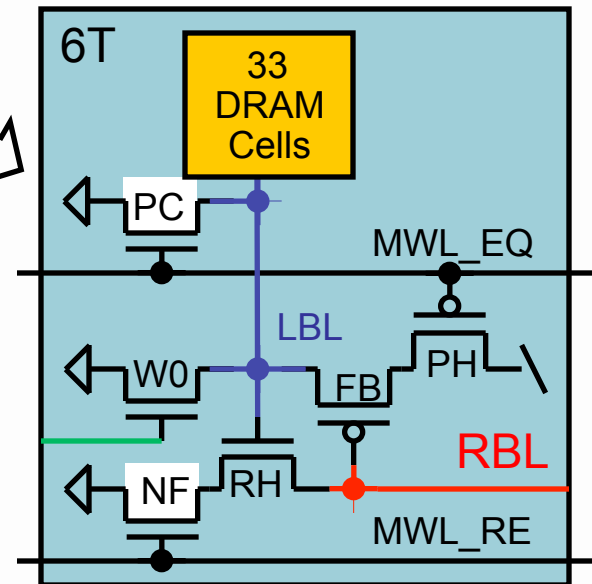


JSSC11

Power Reduction


Power Reduction  
Traded for Transistor Count

Increased Transistor Count

# Micro Sense Architecture ( $\mu$ SA)

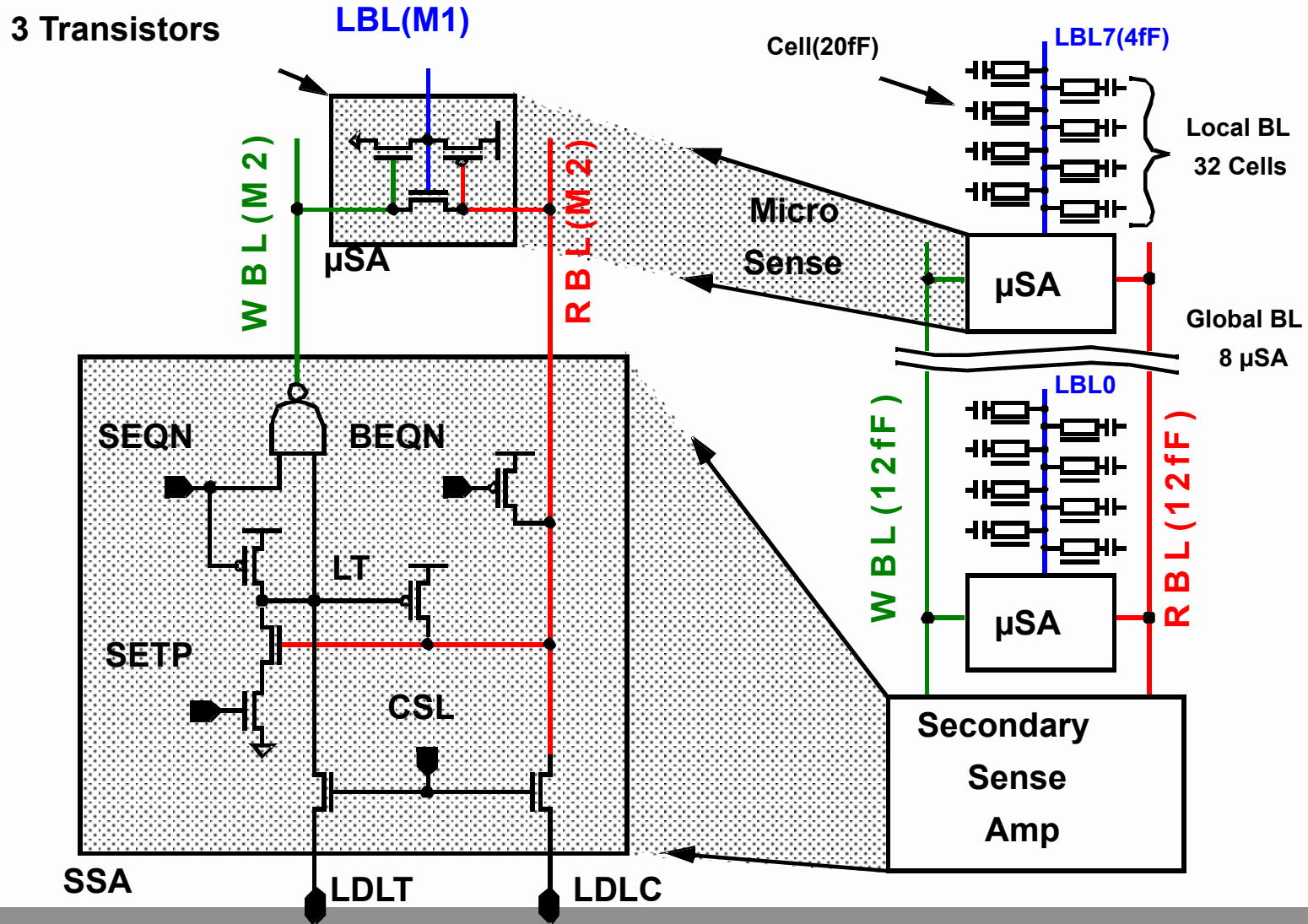

# Data Sense Amp (DSA)

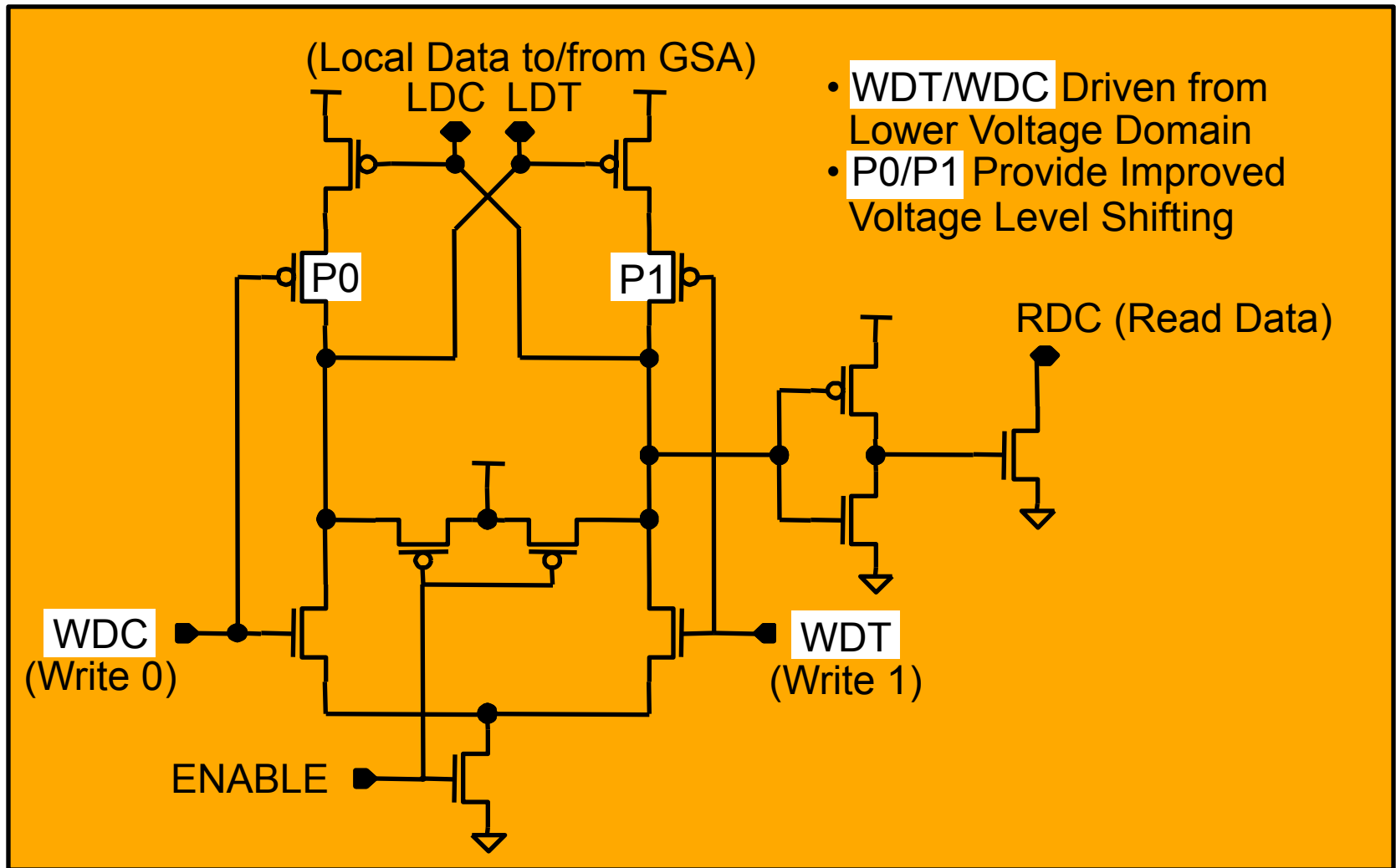


## Micro Sense Advantage

Fast Performance of Short Bit-Line  
Area Overhead of 4x Longer Bit-Line

Bits/BL	256	128	32
Sense Amp	10%	20%	19%
Reference Cells	2.3%	4%	-
Twist Region	2%	2.6%	-
Second Sense Amp	-	-	8%
Total	14.3%	26.6%	27%



Same Overhead

 


# Bit-Line area overhead

Bits/BL	256	128	32
Sense Amp	10%	20%	> 80%
Reference Cells	2.3%	4%	
Twist Region	2%	2.6%	

Unacceptable

 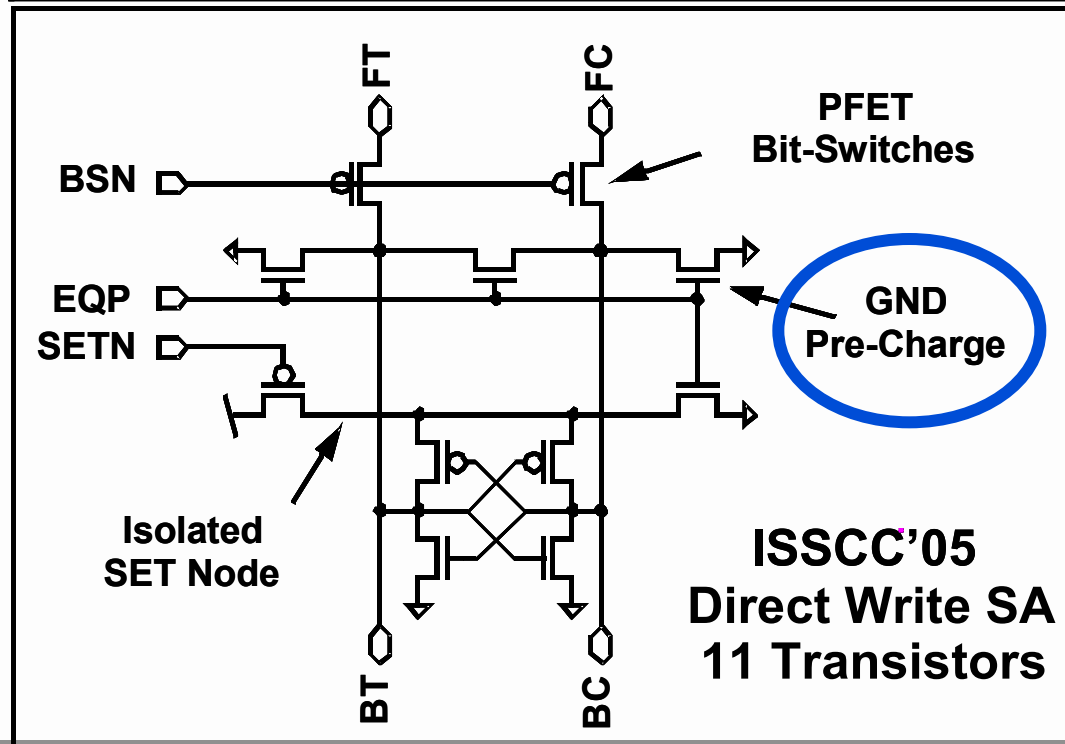


# Array utilization

 

$$\text{Utilization} = \frac{\text{Cell Area}}{\text{IO + Predecode + Redundancy}}$$

Mbits/mm<sup>2</sup>

# Access Shmoo

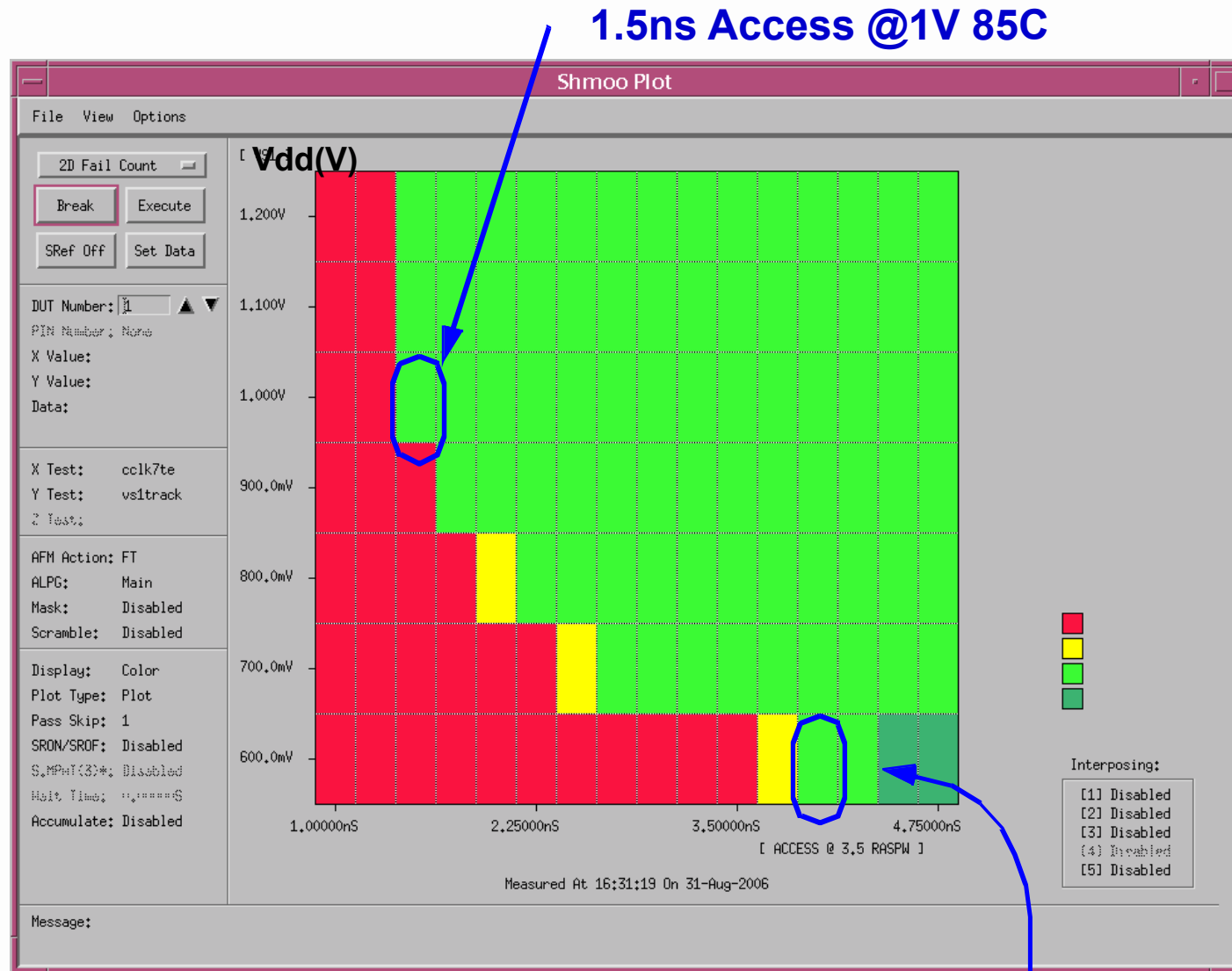


**4ns Access @600mV**

# Redundancy


Notebook



Page 111

 

Extra Page  
R05

 

eFuse based repair table

(see page R05)

<u>INDEX TO BOOK ONE</u>			
<u>PAGE No.</u>	<u>EXPT. No.</u>	<u>Ans</u>	<u>DATE</u>
109	30 APRIL 1999	EXP. 30	
110	1-MAY 1999	EXP 30 CONTD	
111	1-may 1999	EXP 31	
112	1-may 1999	EXP 31 CONTD.	



# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example


# Noise

Coupling and Local Process Variation effectively degrades signal

External Noise (Wire or Sx) Reduced to Common Mode by Folding



 Line to Line Coupling Limited by Bit-Line Twisting




$V_t$  and DL Mis-Match Limited by Longer Channel Length

Overlay Mis-Alignment Limited by Identical Orientation

Capacitive Mis-Match Limited by careful Physical Design (Symmetry)
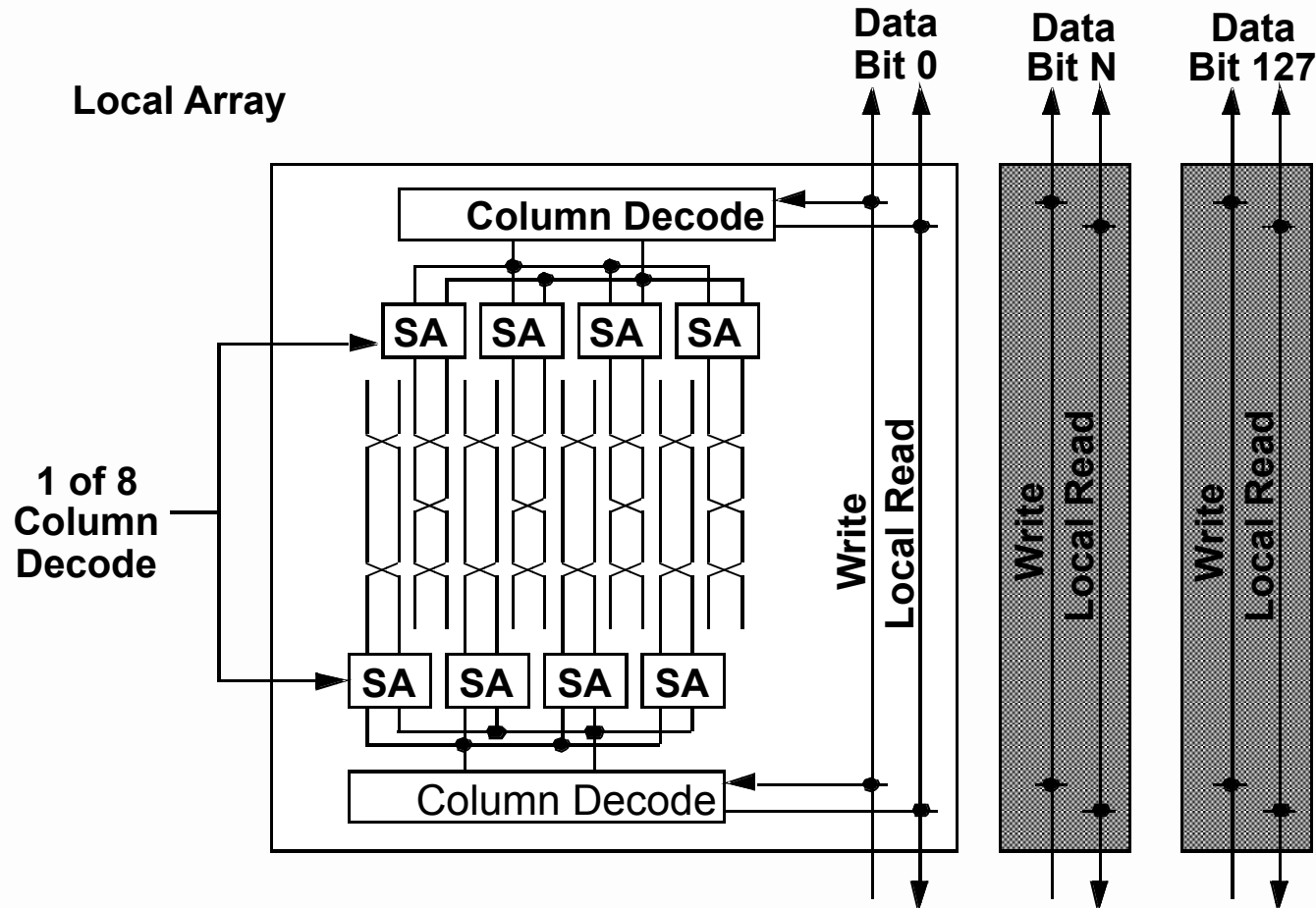
# Interleaved Sense Amp w/ Bit-Line Twist



# Open and Folded Bitline Schematic

 


FIGURE 12.44 Open bitlines

 


FIGURE 12.45 Folded bitlines

# Folded Bitline Layout

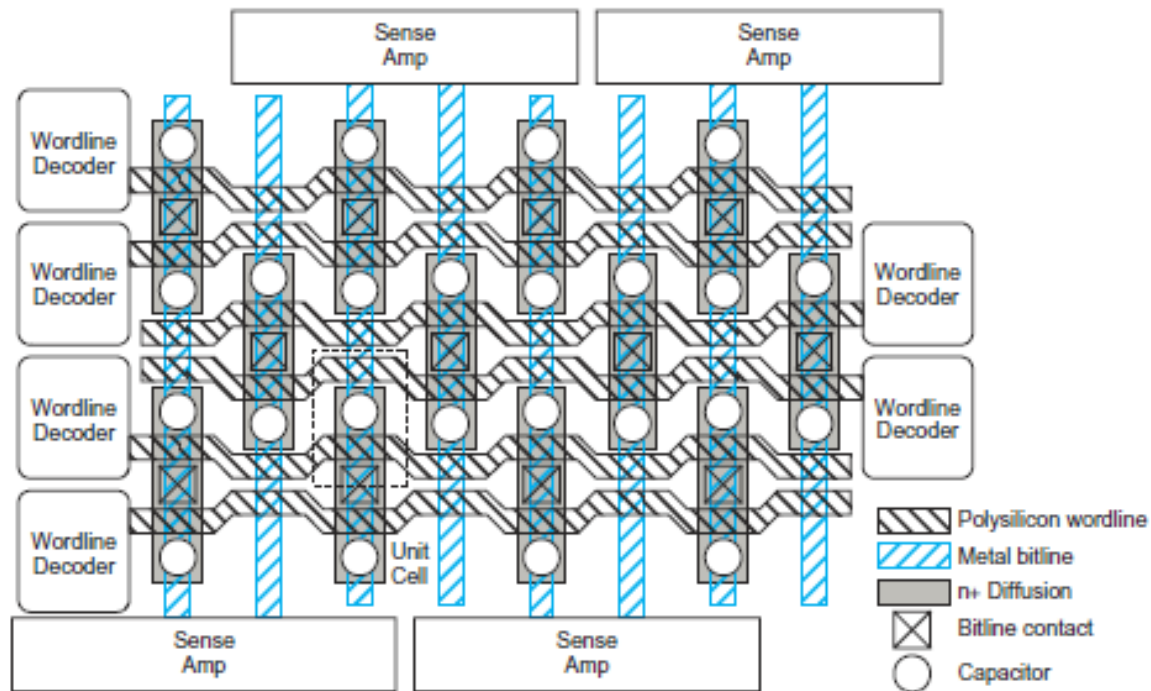


FIGURE 12.46 Layout of folded bitline subarray

# Topics


- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example

# WLDRV

Driver with Low voltage transistors → Logic transistors


No thick gate oxide transistors required!!

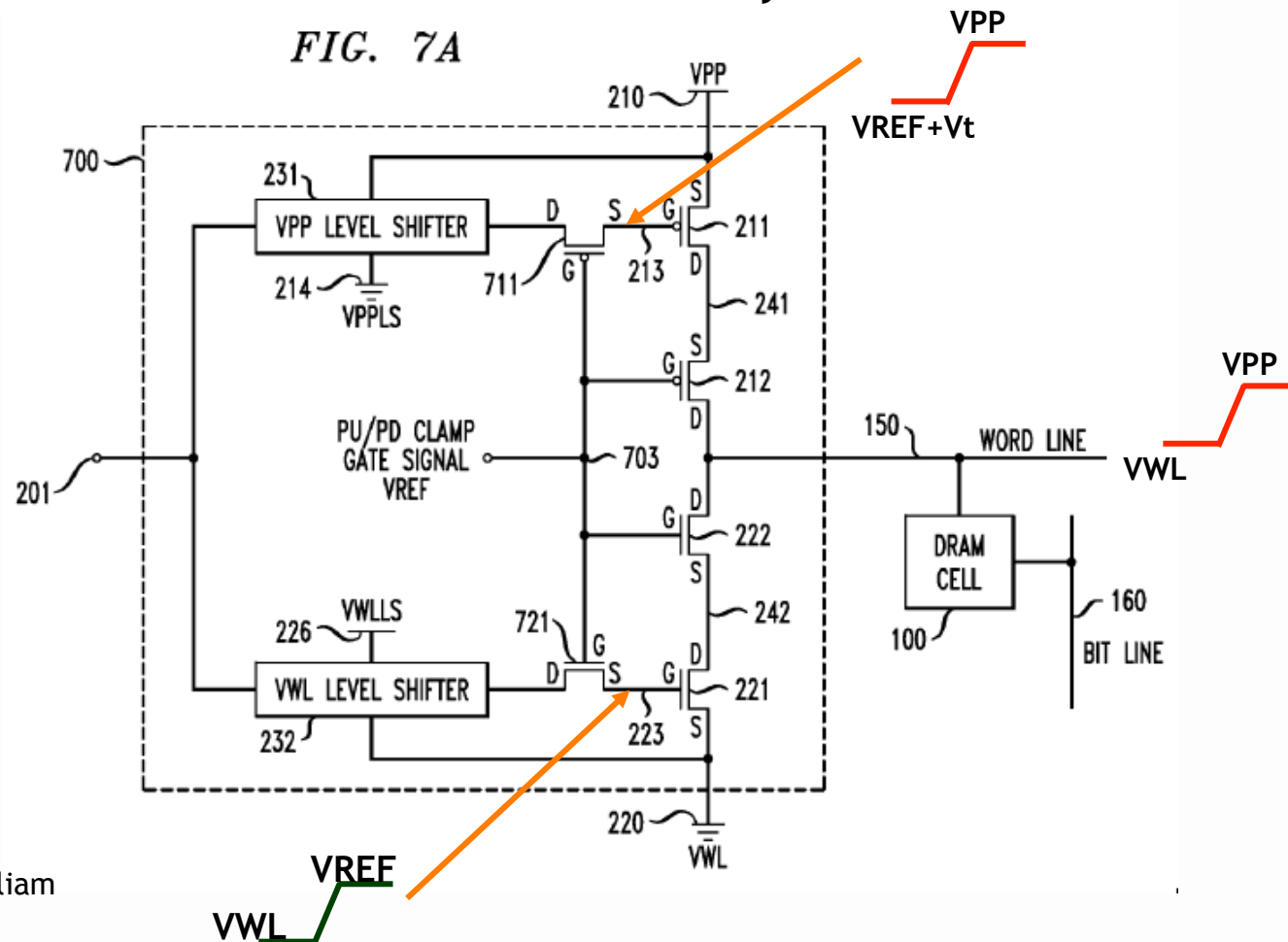Voltage across any two terminals should not exceed reliability limits




1. US patent No: 8,120,968 → William Robert Reohr, John E Barth

# LEVEL Shifter

 

VWL Level shifter


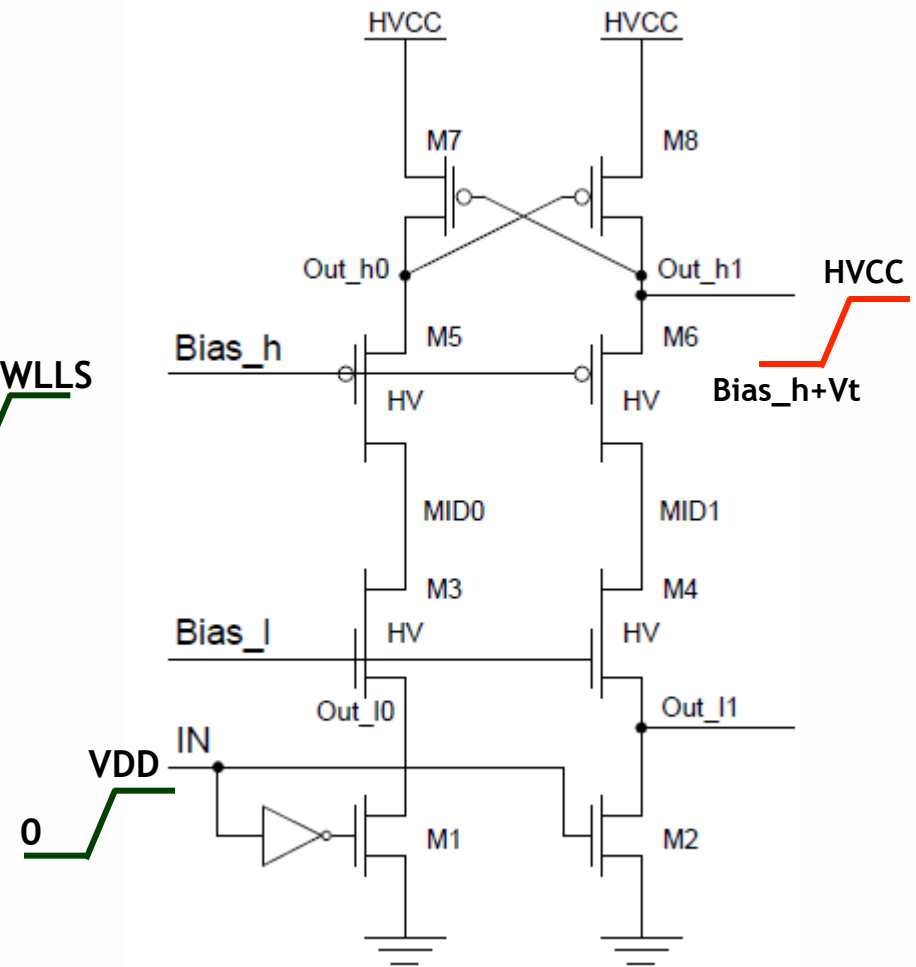


VPP Level shifter

1. US patent No: 8,120,968 → William Robert Reohr, John E Barth
2. A Low Voltage to High Voltage Level Shifter Circuit for MEMS Application → Dong Pan


  
# Orthogonal WLD and pyramid wiring (M3/M4)



# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example

# Retention

Transfer Device and Storage Cap are NOT ideal devices: they LEAK

Leakage Mechanisms include:  $I_{off}$ , Junction Leakage, GIDL,...

Junction Leakage Temperature Dependence =  $2x/10C$

Cell Charge needs to be replenished (Refreshed), Median Retention Time:


$$T = \frac{CDV}{I_{leak}} = \frac{35fF \times 400mV}{2fA} = 7 \text{ seconds}$$

Where DV is acceptable loss  
C is Cell Capacitance  
 $I_{leak}$  is Total Leakage


Retention Distribution has Tails  
created by Defects and Leaky Cells

Weak Cells Tested out (5x Guardband)  
and replaced with Redundancy

Customer issues periodic Refresh Cycle

 

# Pass transistor leakage

 

# Floating Body Effects

Body potential modulated by coupling and leakage


Better source follower vs. bulk during write back (body coupling)

- Improved write '1' cell voltage

Degraded  $I_{off}$  / Retention if body floats high (body leakage)


- GND pre-charge keeps body low

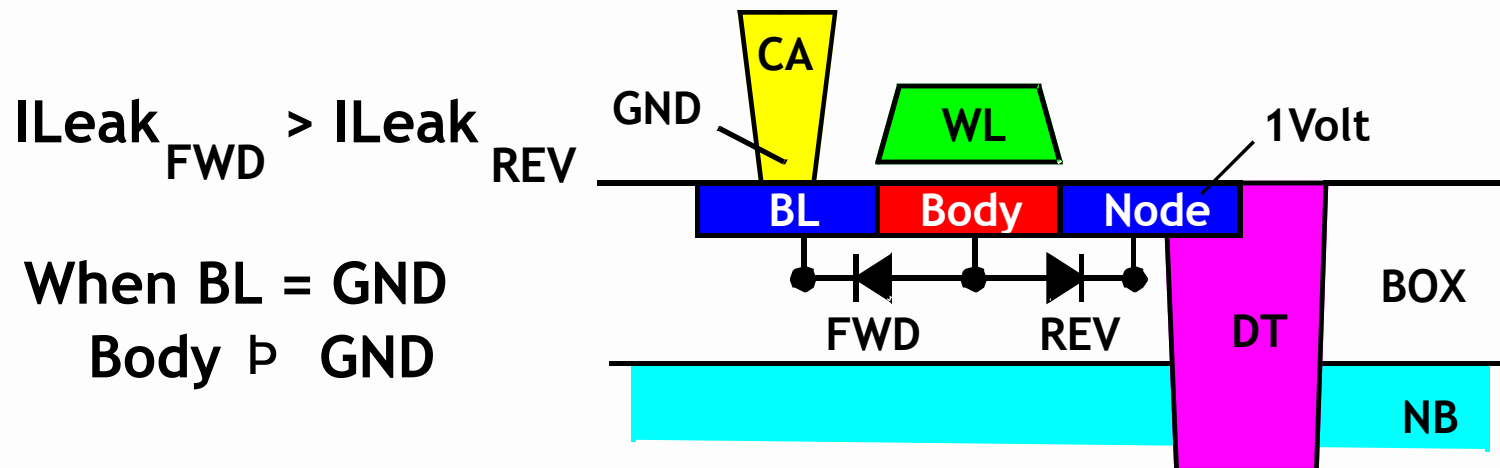- Eliminate long periods with BL high (limit page mode)




# Array Body Charging


## Commodity DRAM (long page mode)

 


## embedded DRAM (limited page mode)

 

# eDRAM vs. SRAM Cycle-Time Comparison

 

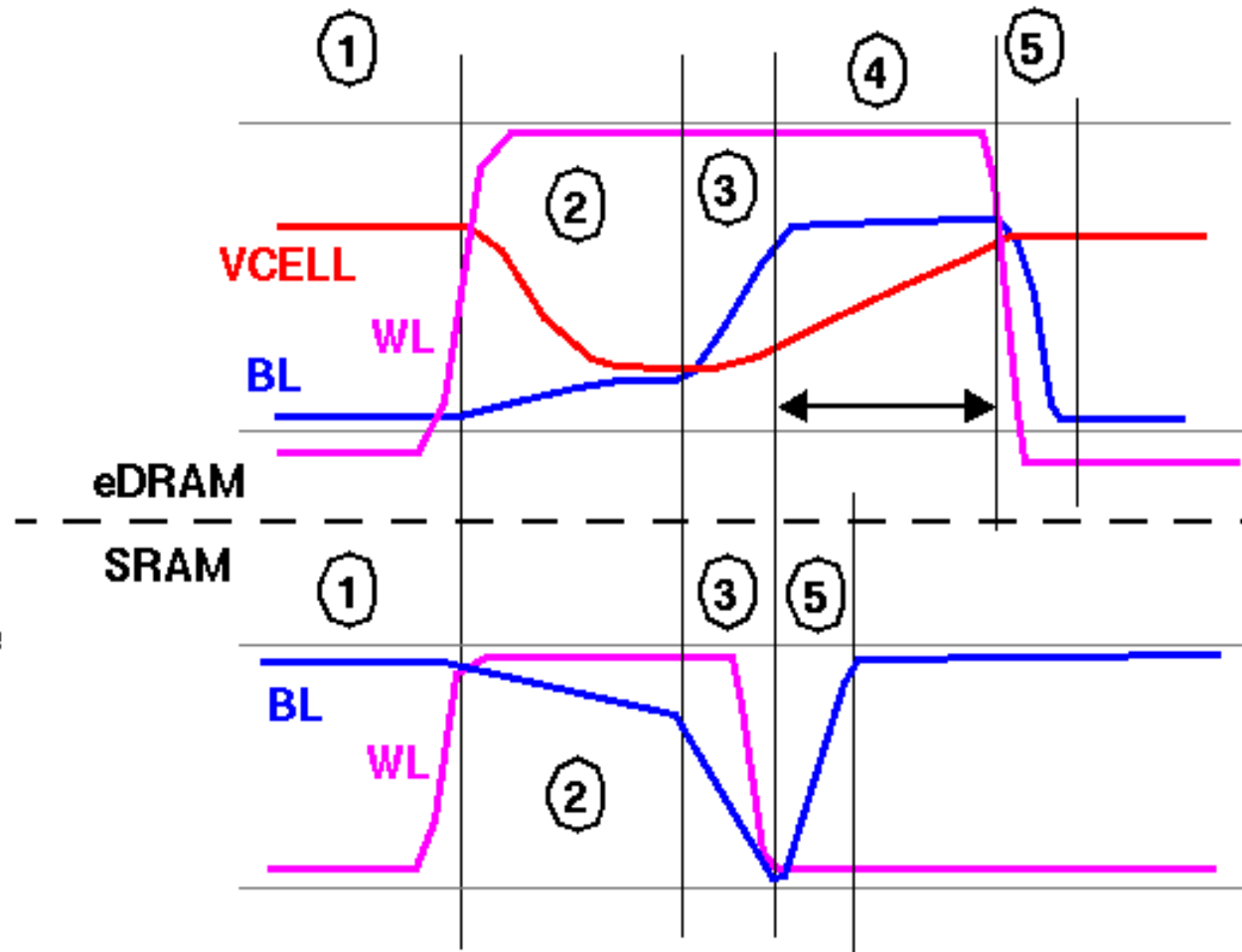1. WL Activation
2. Charge Transfer to Bit-Line  
( $I_{READ}$  Similar to SRAM)
3. Amplification
4. Write-Back
5. Precharge




NET: SRAM Random Cycle will continue to lead!

# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example




# Logic Diagram of a Typical DRAM

 

- Control Signals (RAS\_L, CAS\_L, WE\_L, OE\_L) are all active low
- Din and Dout are combined (D):
  - WE\_L is asserted (Low), OE\_L is disasserted (High)
    - D serves as the data input pin
  - WE\_L is disasserted (High), OE\_L is asserted (Low)
    - D is the data output pin
- Row and column addresses share the same pins (A)
  - RAS\_L goes low: Pins A are latched in as row address
  - CAS\_L goes low: Pins A are latched in as column address
  - RAS/CAS edge-sensitive

# DRAM logical organization (4 Mbit)

 


- Square root of bits per RAS/CAS

Din Dout can be clubbed together with a BiDi buffer
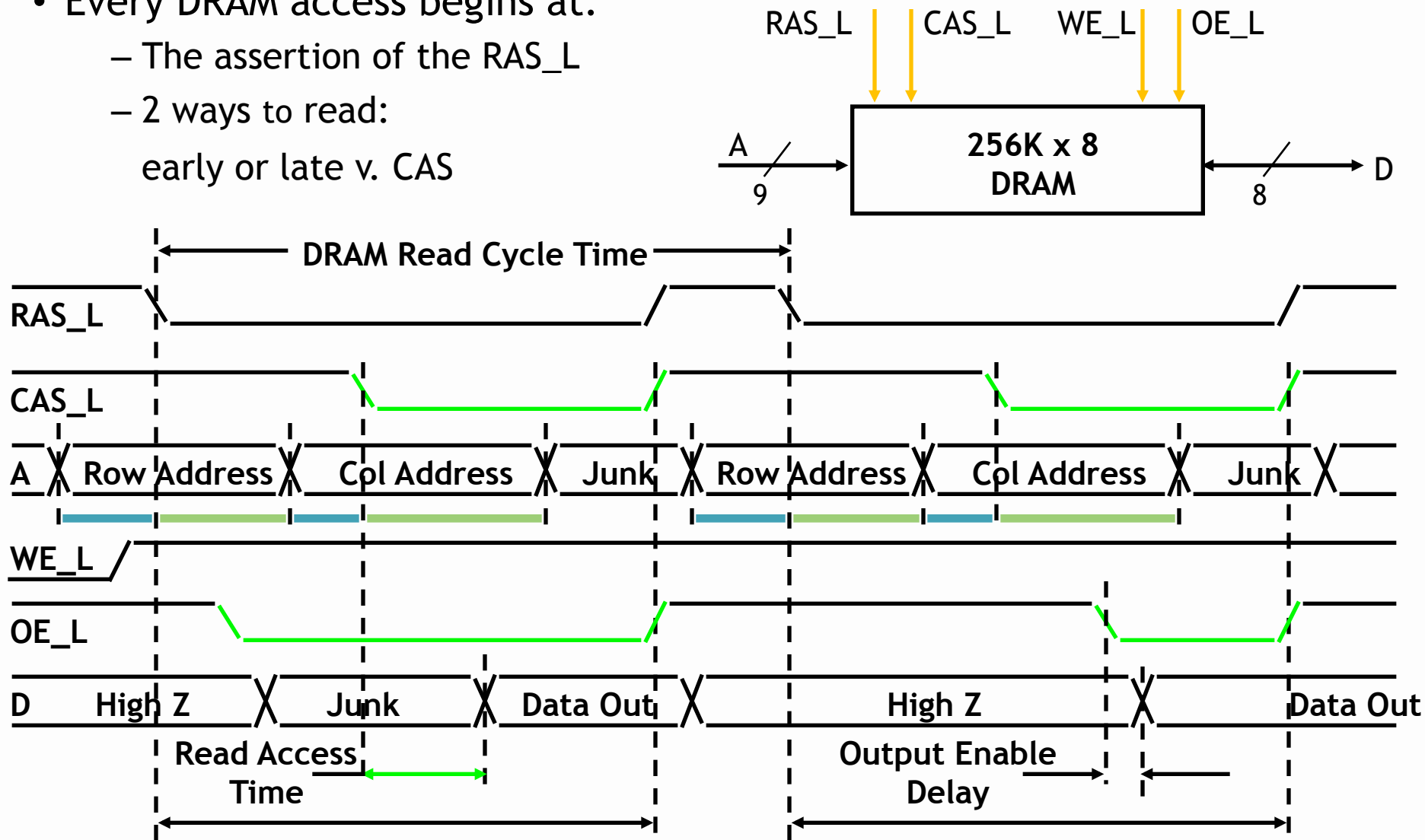
# DRAM Read Timing


- Every DRAM access begins at:
  - The assertion of the RAS\_L
  - 2 ways to read:
    - early or late v. CAS



Early Read Cycle: OE\_L asserted before CAS\_L      Late Read Cycle: OE\_L asserted after CAS\_L
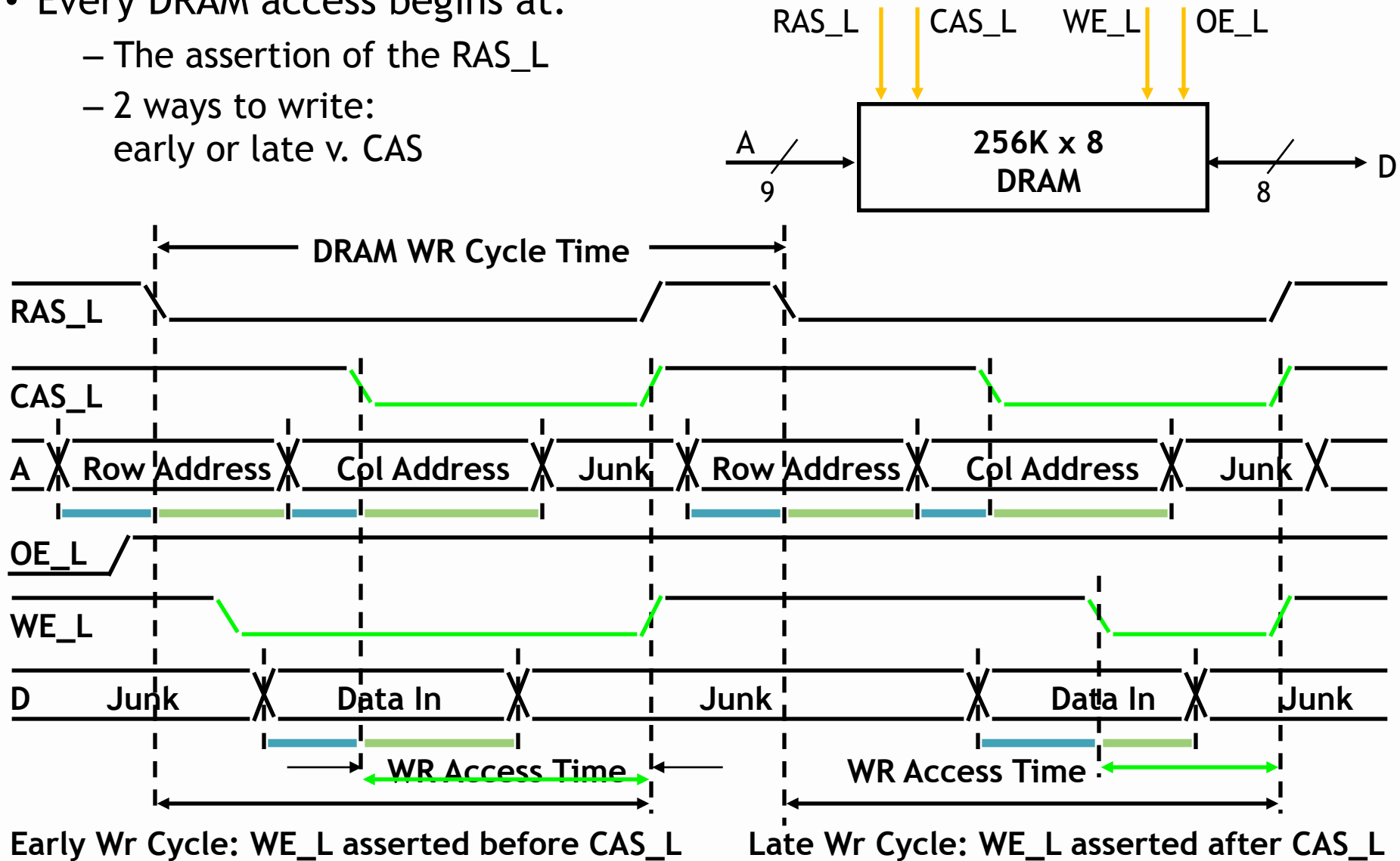
# DRAM Write Timing

- Every DRAM access begins at:
  - The assertion of the RAS\_L
  - 2 ways to write:
    - early or late v. CAS



# A Fast Sense-Amp (Case Study)


G. Fredeman et al., “A 14 nm 1.1 Mb Embedded DRAM Macro With 1 ns Access,”  
in IEEE Journal of Solid-State Circuits, vol. 51, no. 1, pp. 230-239,  
Jan. 2016. doi: 10.1109/JSSC.2015.2456873

# Problems with Micro Sense Amp


- ❑ By default the Sense Amp reads a 0
- ❑ Access transistor has to pull the LBL HIGH to read 1
  - ❑ Asymptotic charge up to High since  $V_{gs}$  keeps reducing
  - ❑ Very slow by nature
  - ❑ Need to minimize the WLs per BL(33) for performance reasons
- ❑ Cannot pre-charge LBL to High
  - ❑ Floating Body Effect affects retention
- ❑ NMOS (Access Device) is very fast when pulling down to zero
  - ❑ Can we make a Sense Amp that reads a one by default?
  - ❑ This will allow more WLs per BL

# Gated Feedback Sense Amp

Sense  
Amp

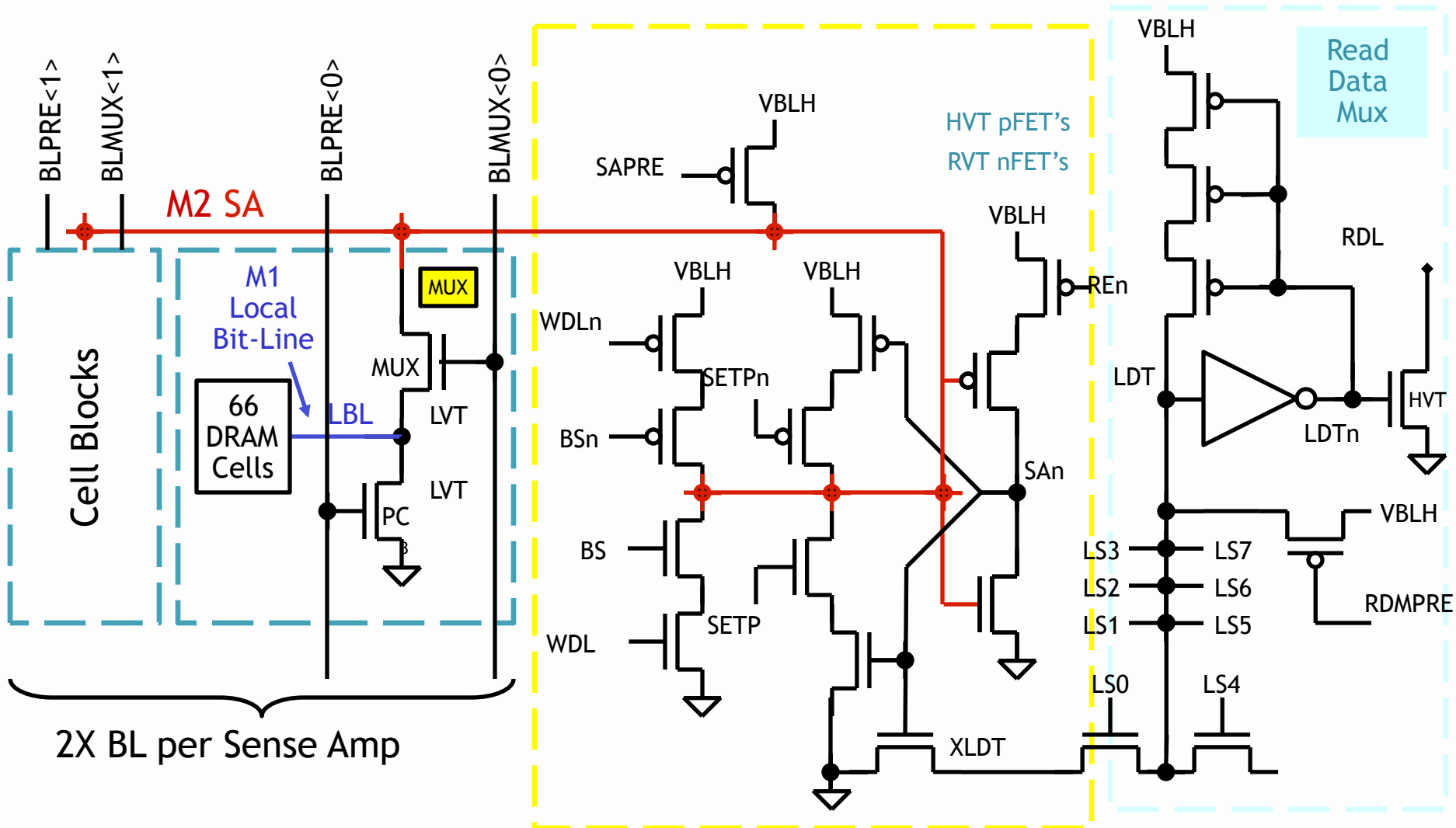


# Read Operation

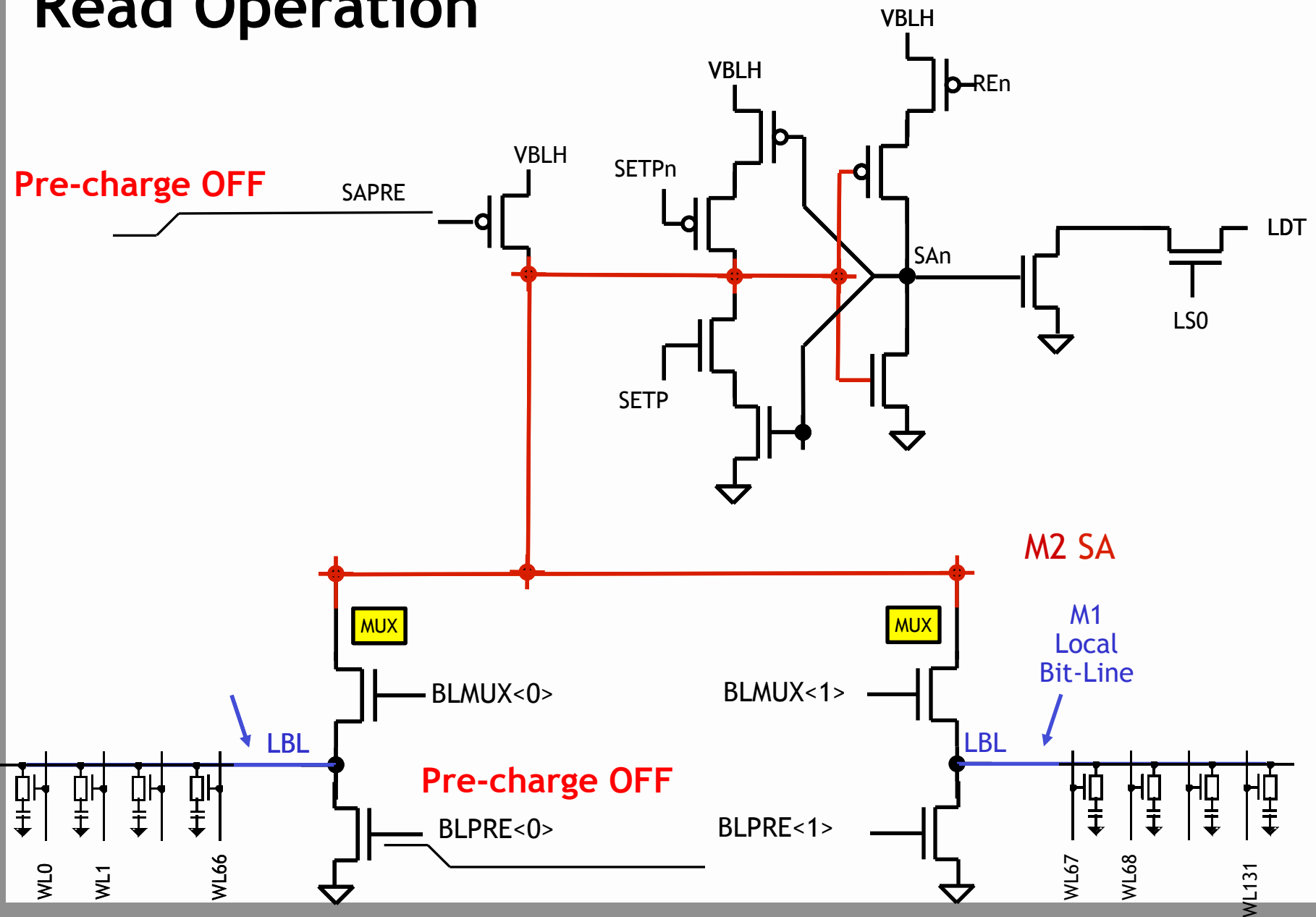





# Read Operation

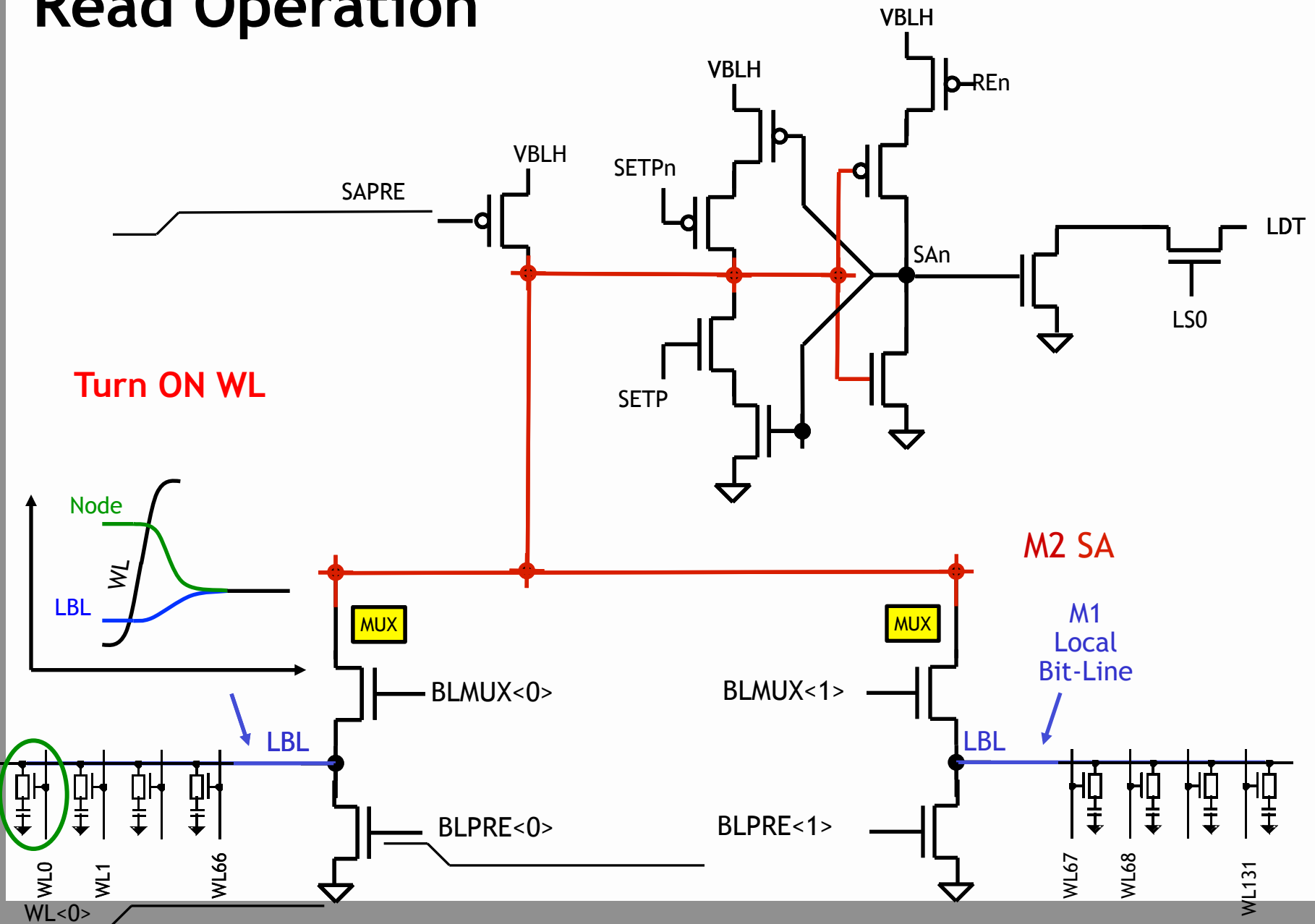

# Read Operation

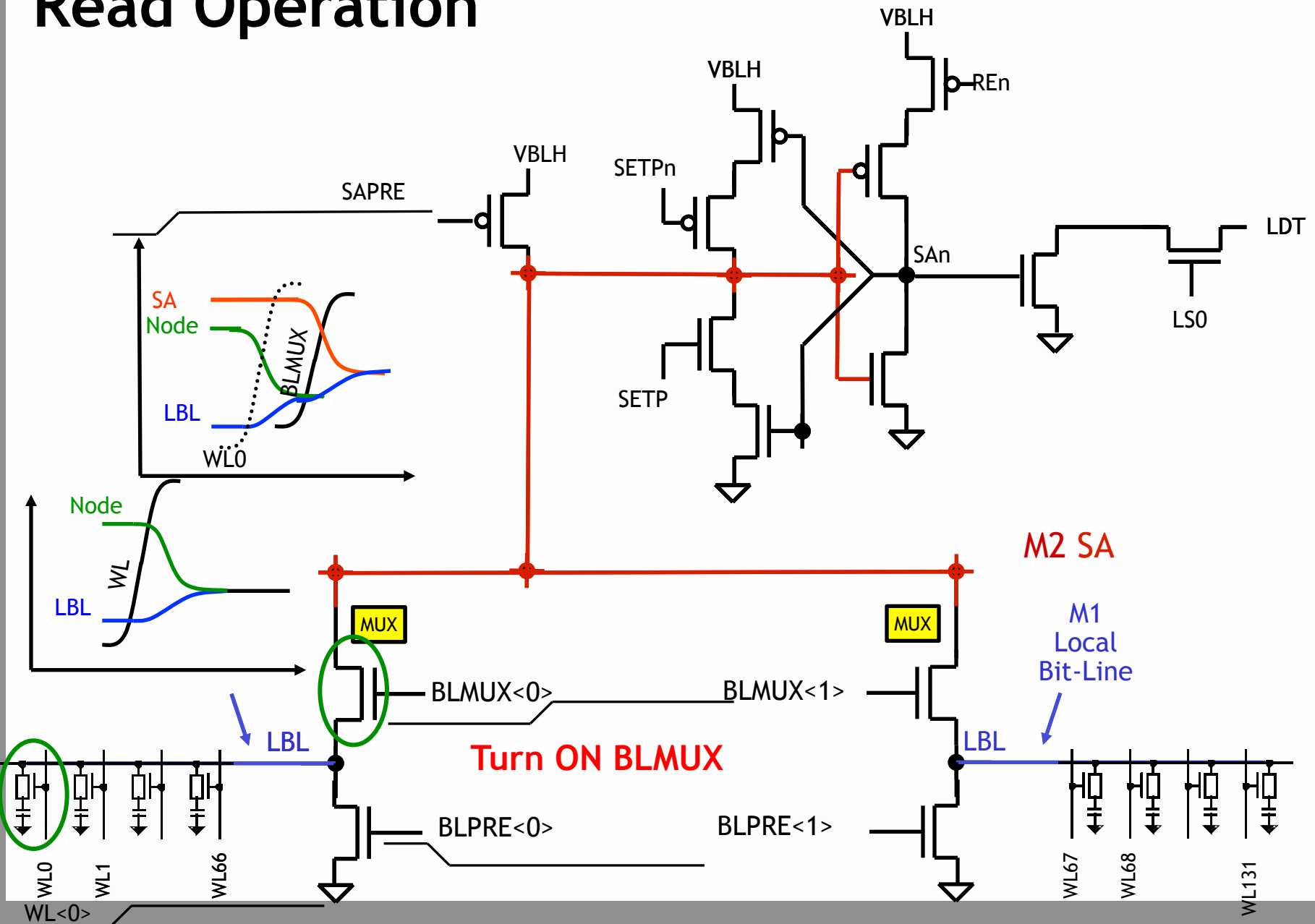


# Read Operation

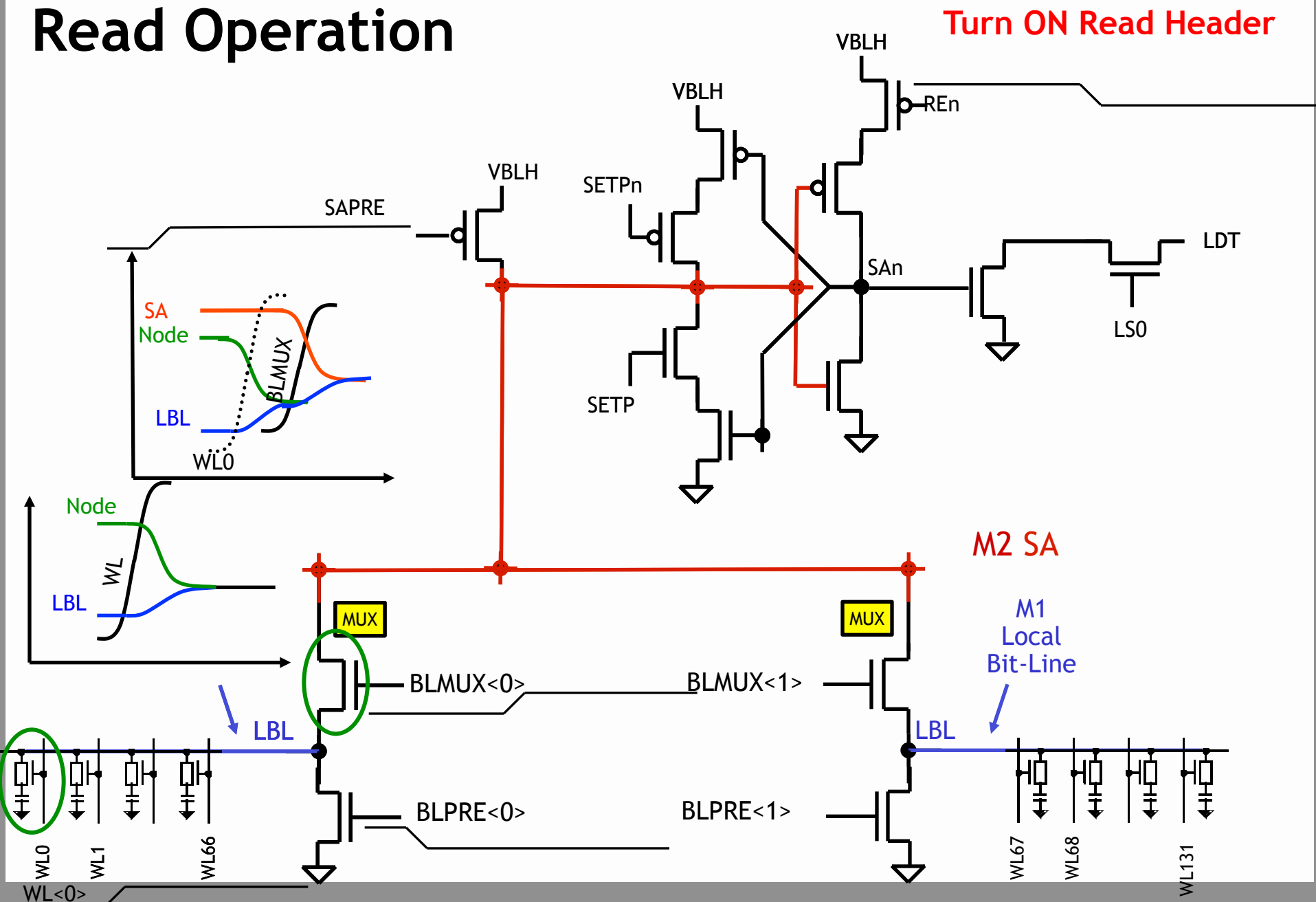


# Read Operation


Turn ON Write-back

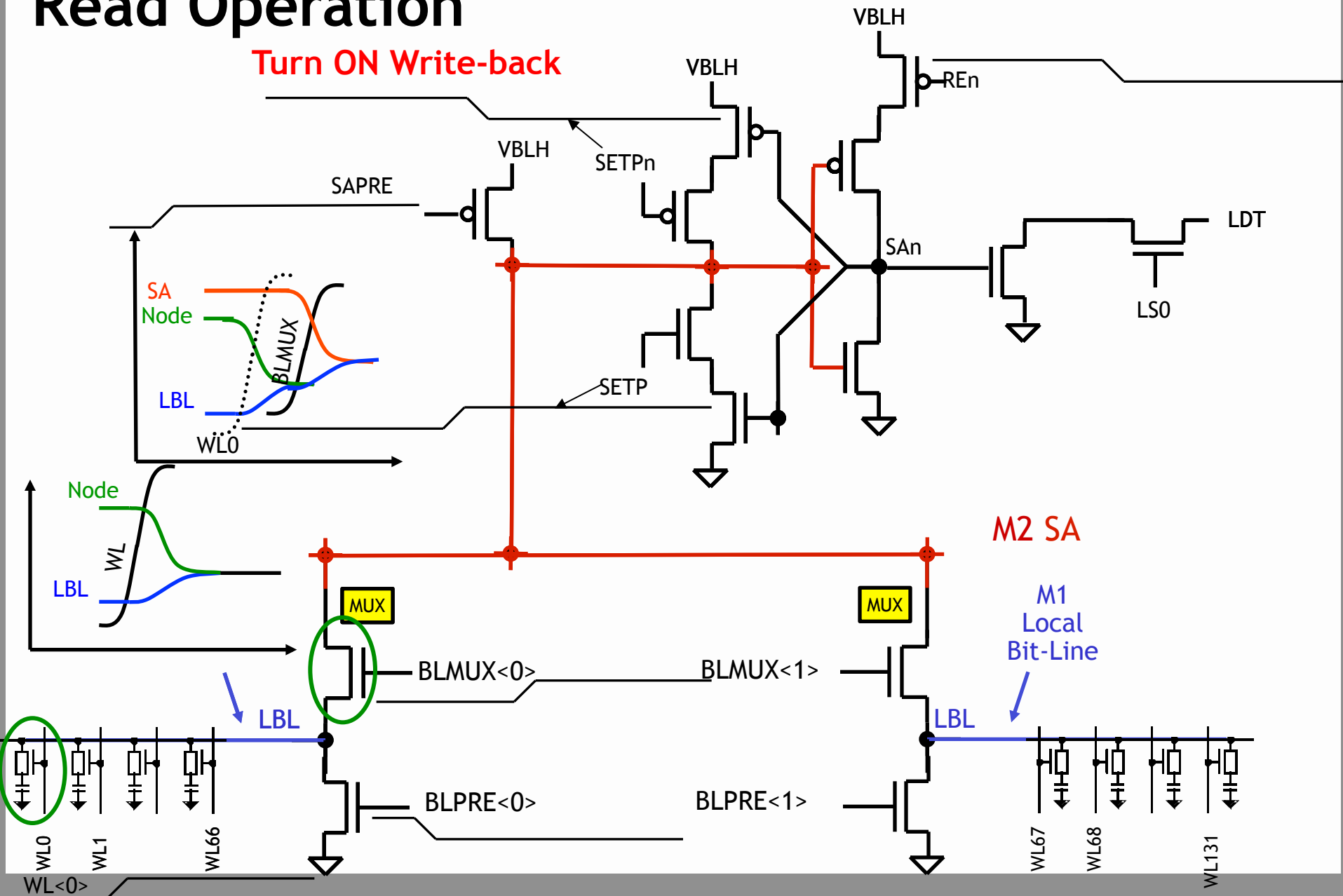


# Read Operation

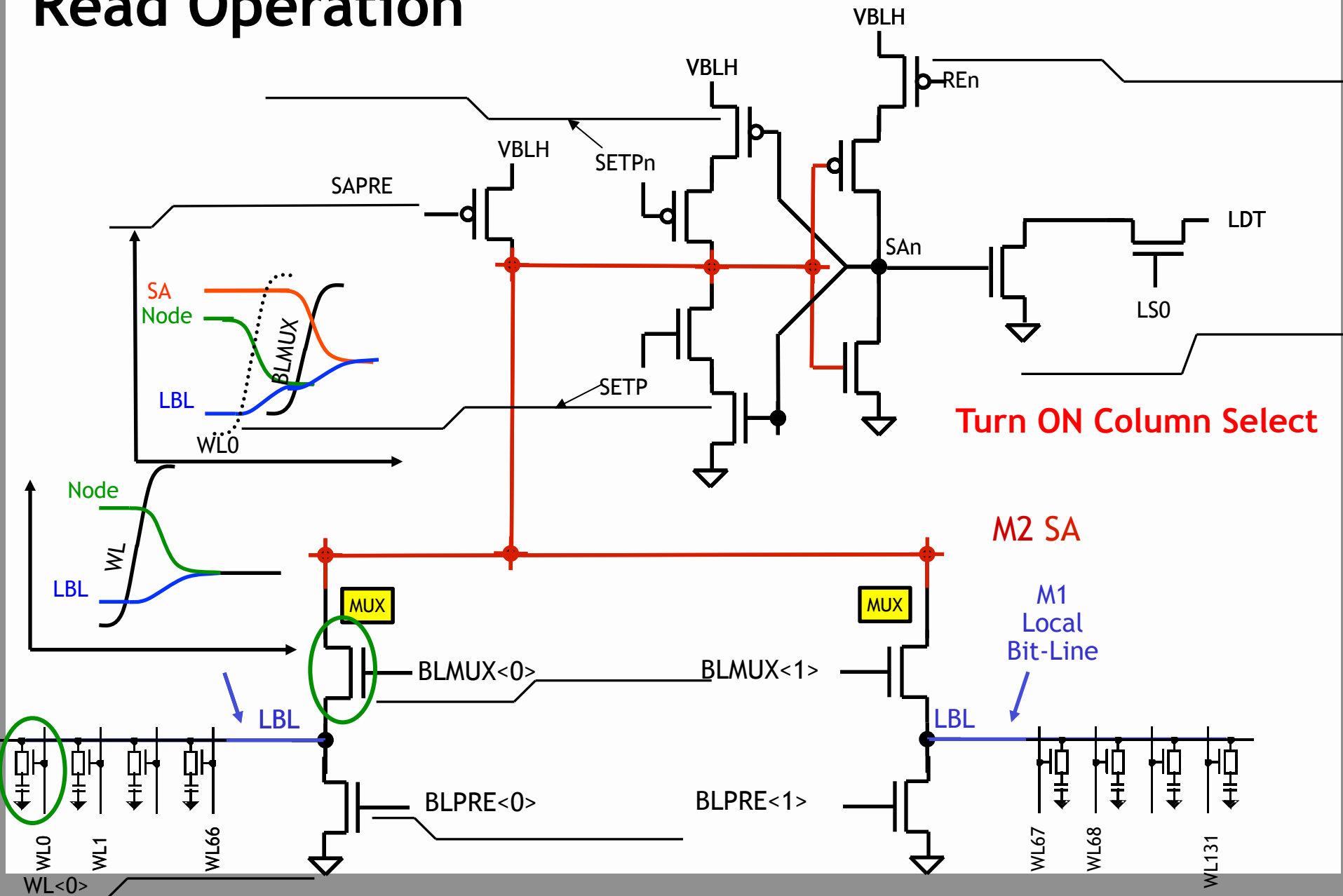


# Column Read Refresh

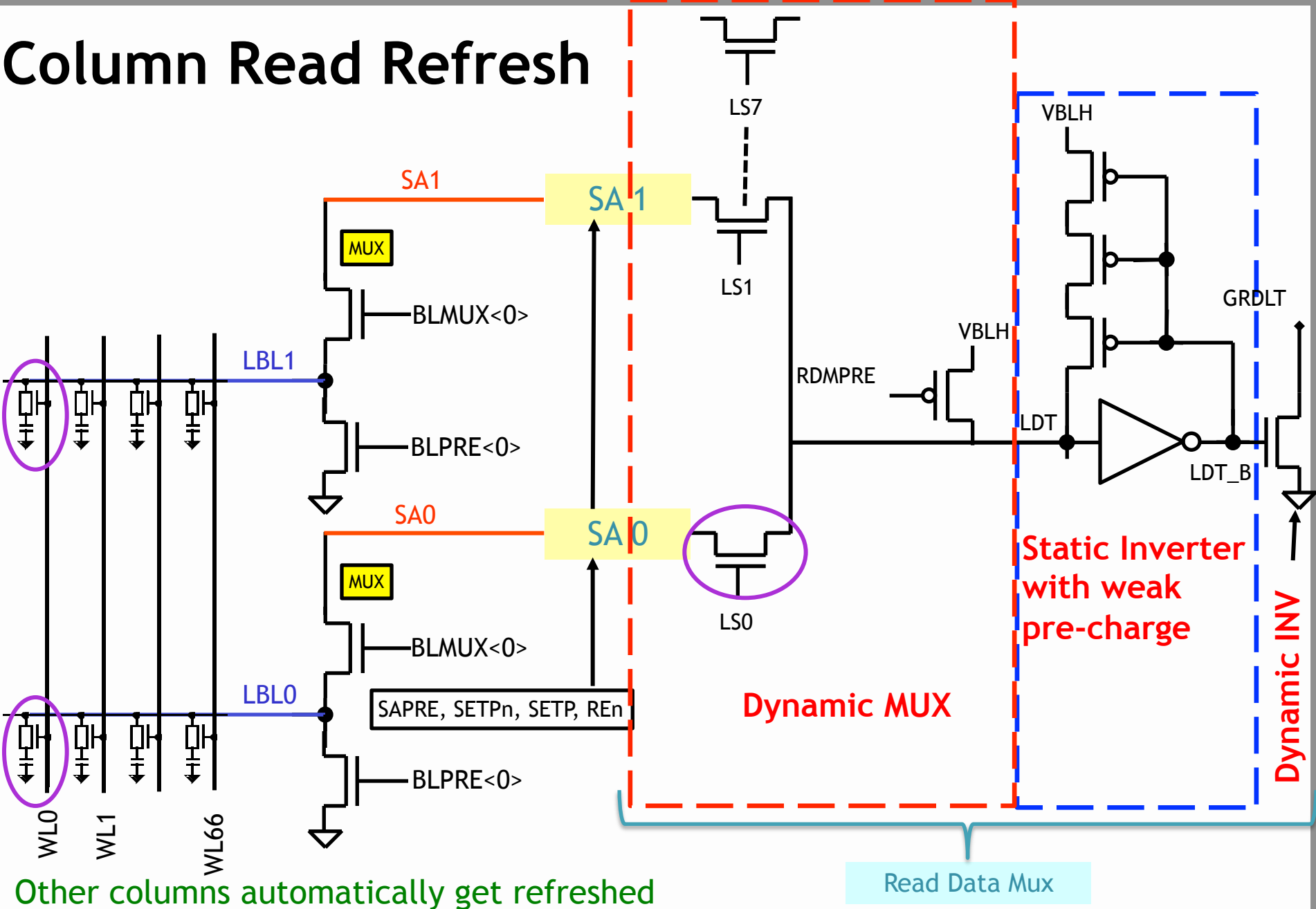

# Write Operation

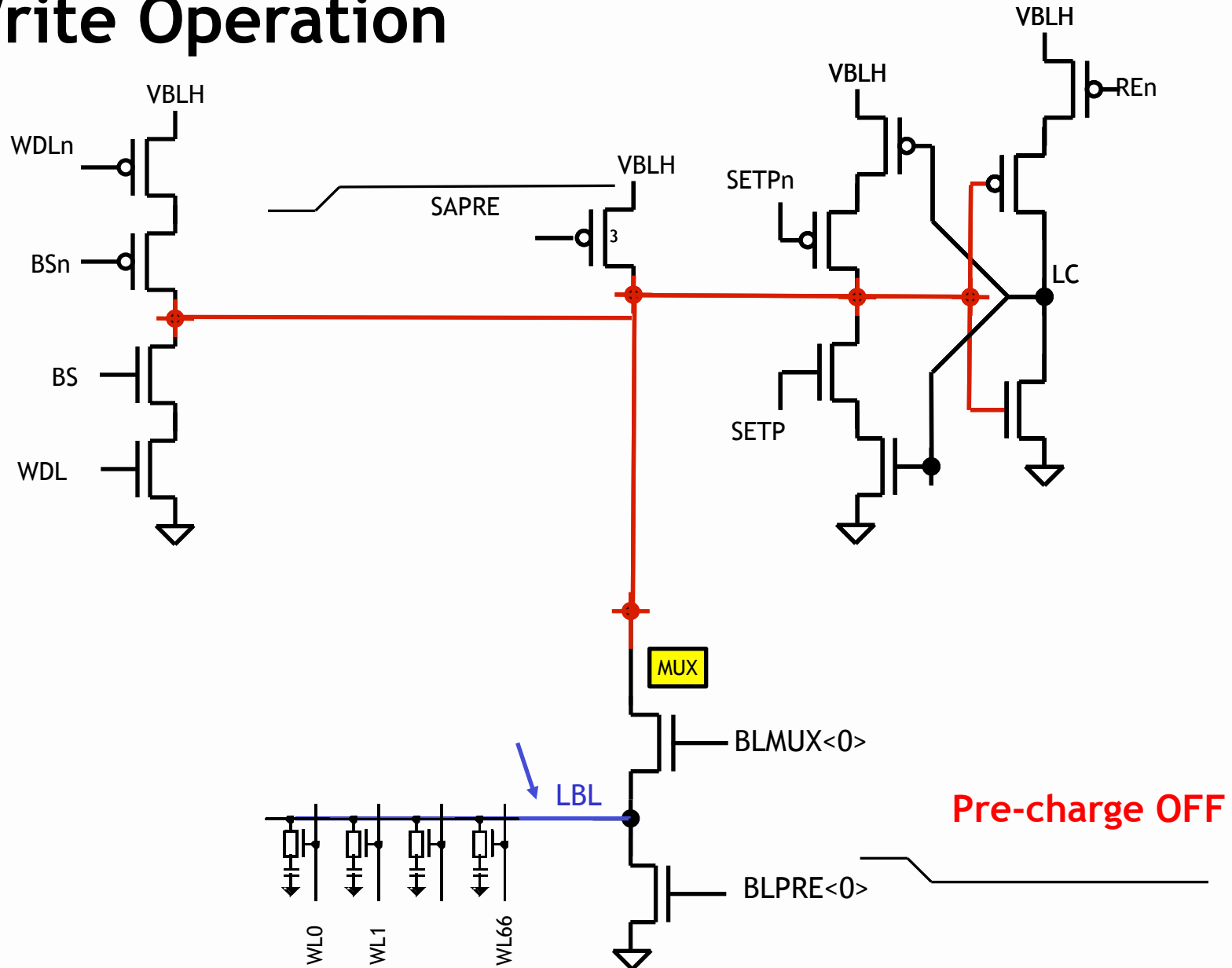


# Write Operation

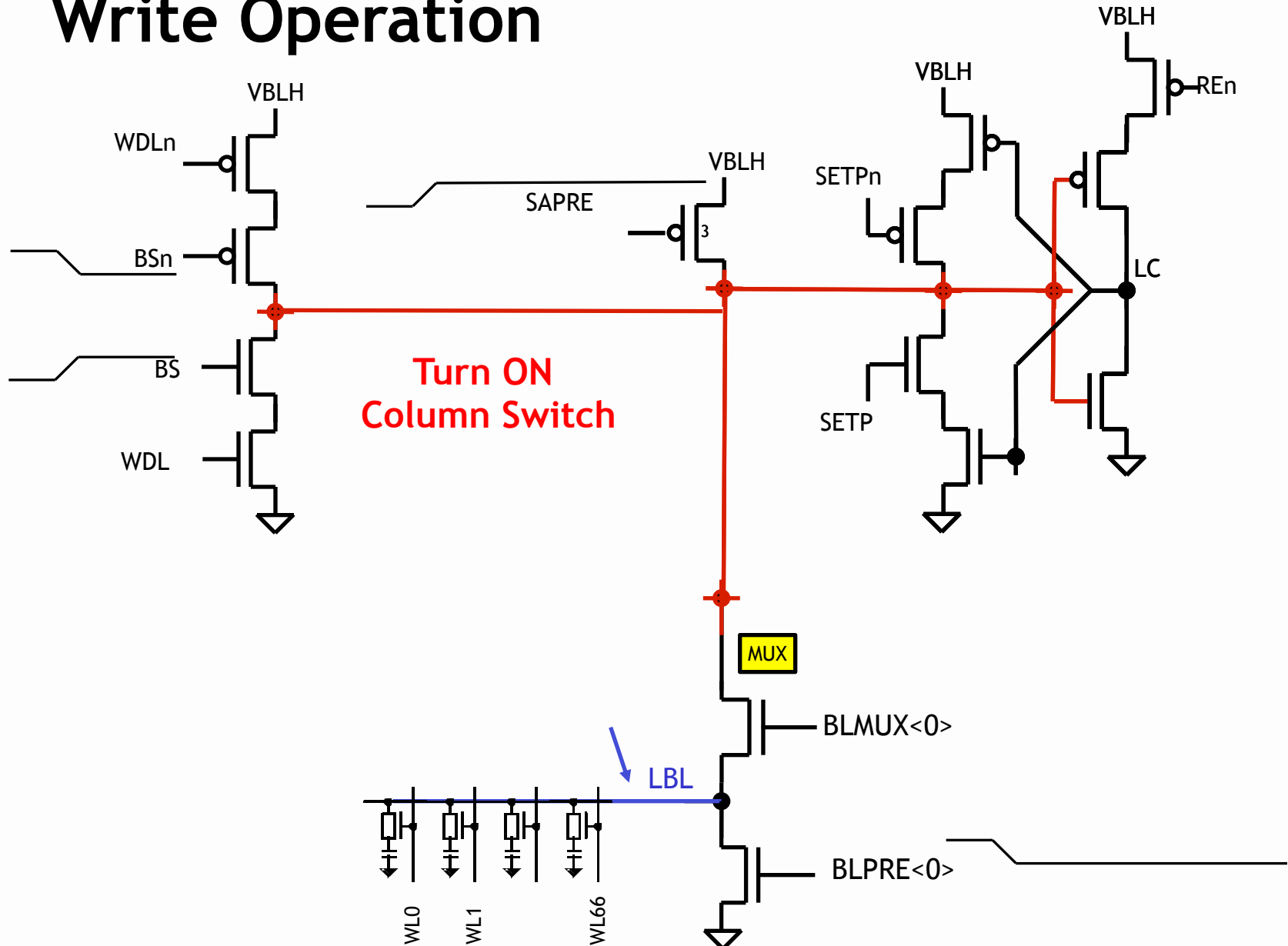





# Write Operation

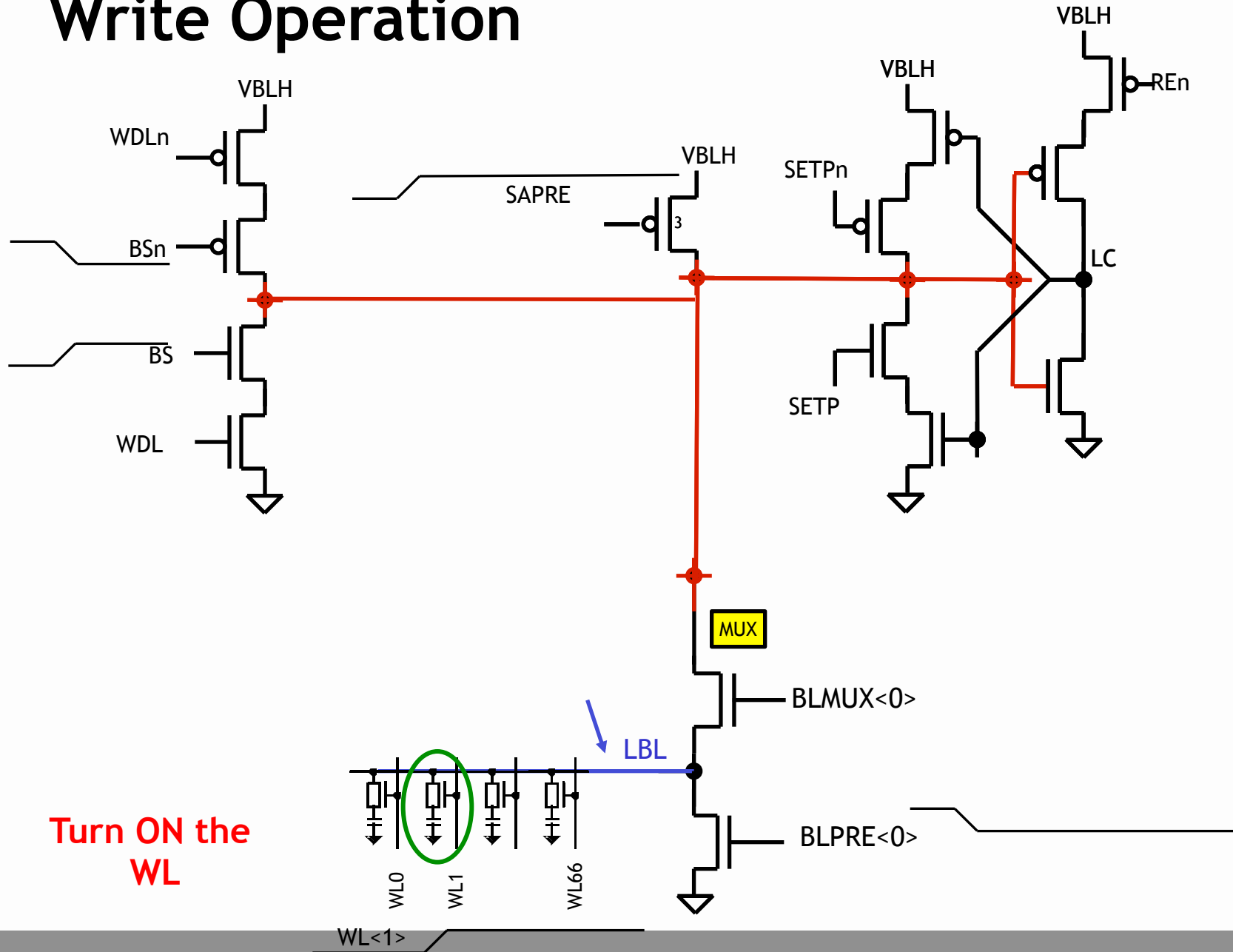

# Write Operation

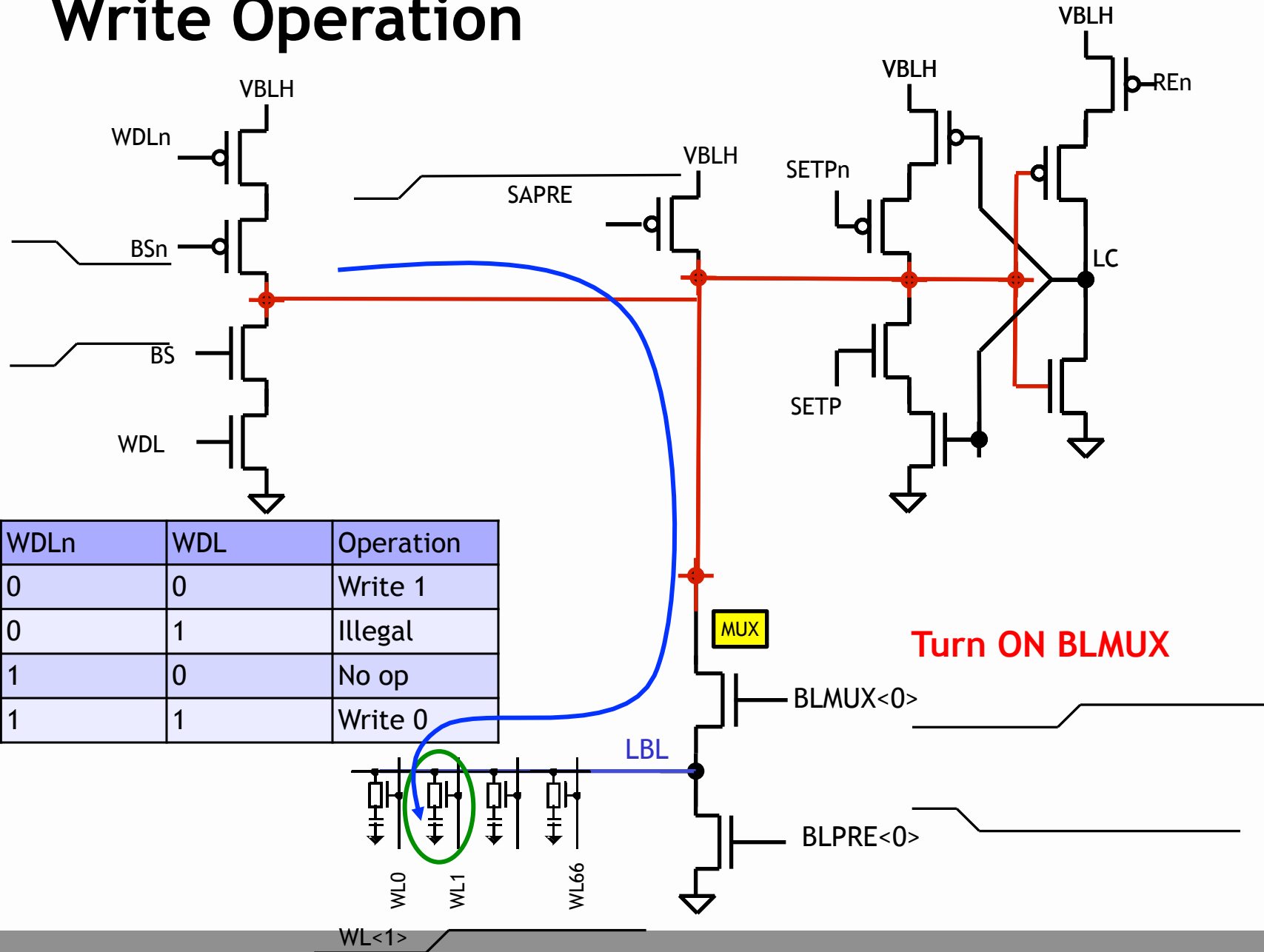


# Write Operation

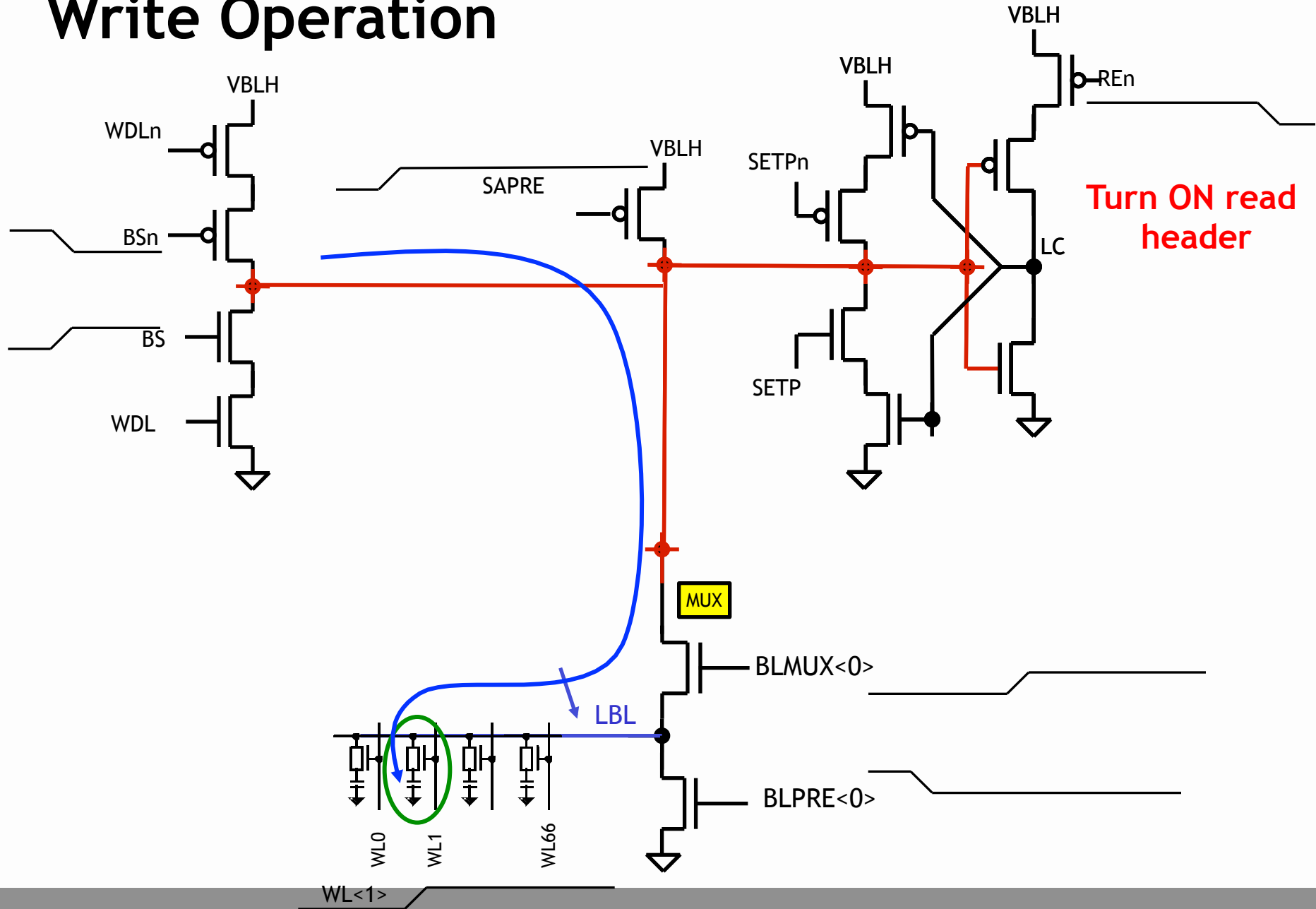


# Write Operation

Turn ON Write-back

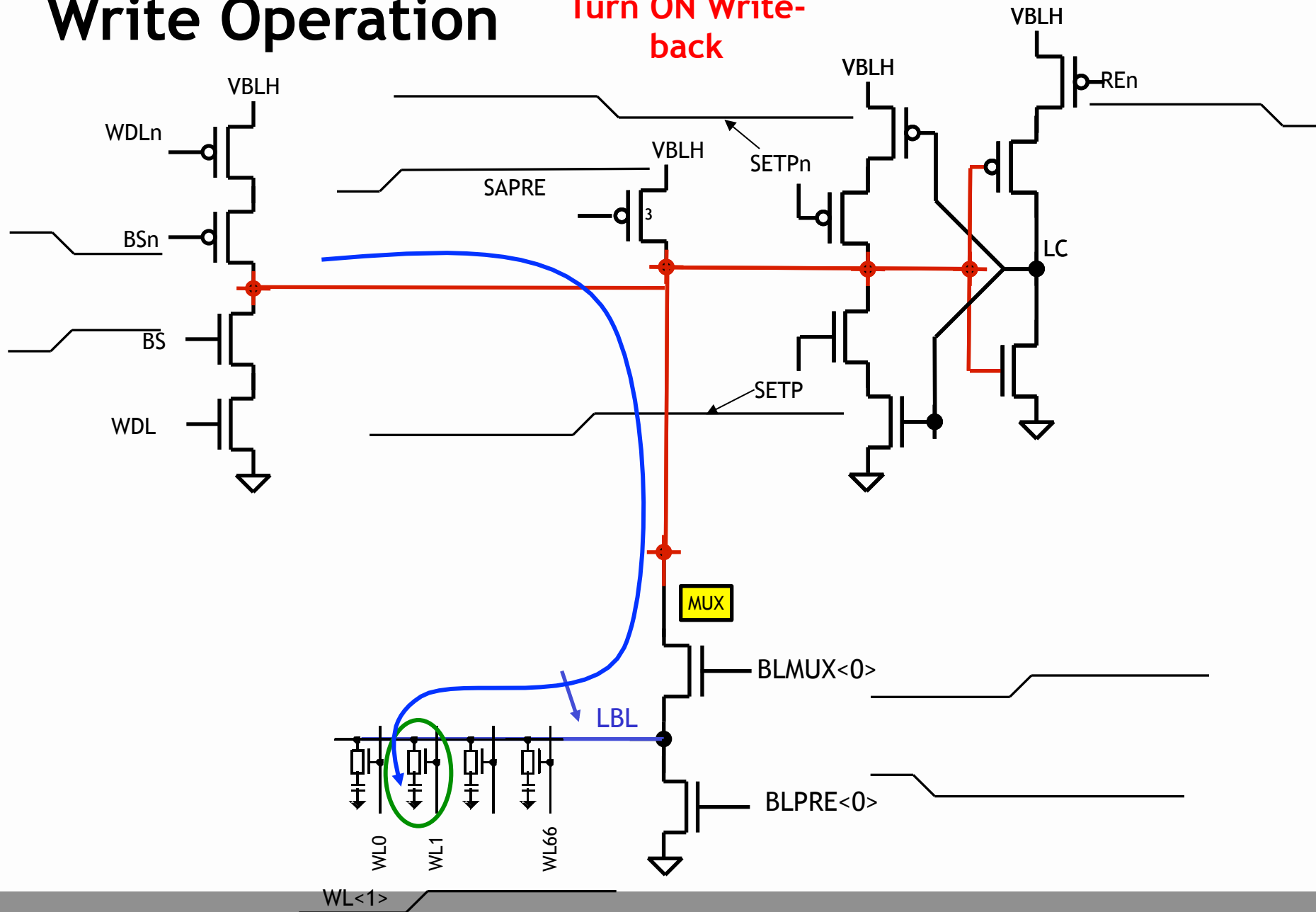


# One Data Line Organization

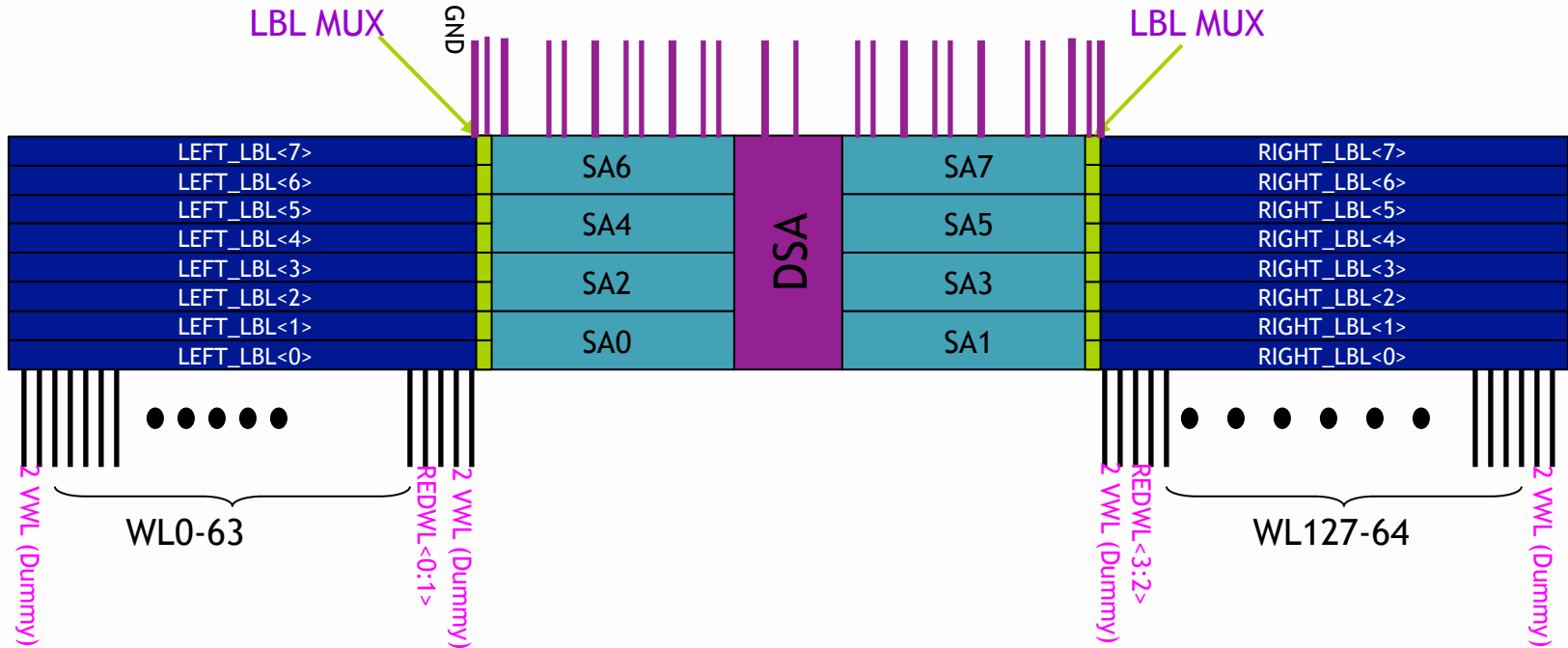

- Single bit can be read out/ written into by selecting one of 128 rows and one of 8 columns
- The components are sized and arranged to make the layout nice and rectangular
- Repeat this structure as many as there are Data-lines

# 14nm FinFET Advantage

 


(b)

14nm Access Device is 2.5X stronger than the 22nm planar device due to

- 50% more effective width
- 42% shorter channel length
- Lower target  $V_{\text{th}}$

Lower  $V_{\text{T}}$  variation due to undoped channel
 
# Lower $V_{th}$ Variation Effect on Retention



- Write a 1 into all the cells
- Read the cells after a pause time
- Ideally (with no local variations) there should be an step jump in the #fail
  - With variations, steeper the slope lesser the variations

# Conclusion

- Pulling more DRAM cache (L2,L3) inside the processor improves overall performance
- eDRAM design using logic process is a challenge
- Case study is done, covering many of the eDRAM design aspects
- Sense amp has to read a 1 by default to provide performance improvement
  - Achieved in the Gated Feedback Sense Amp



# References

- Matick, R. et al., "Logic-based eDRAM: Origins and Rationale for Use," IBM J. Research Dev., vol. 49, no. 1, pp. 145-165, Jan. 2005.
- Barth, J. et al., "A 500MHz Random Cycle 1.5ns-Latency, SOI Embedded DRAM Macro Featuring a 3T Micro Sense Amplifier," ISSCC Dig. Tech. Papers, pp. 486-487, Feb. 2007.
- Barth, J. et al., "A 500 MHz Random Cycle, 1.5 ns Latency, SOI Embedded DRAM Macro Featuring a Three-Transistor Micro Sense Amplifier," IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 43, NO. 1, JANUARY 2008.
- Barth, J. et al., "A 45nm SOI Embedded DRAM Macro for POWER7™ 32MB On-Chip L3 Cache," ISSCC Dig. Tech. Papers, pp. 342-3, Feb. 2010.
- Barth, J. et al., "A 45 nm SOI Embedded DRAM Macro for the POWER™ Processor 32 MByte On-Chip L3 Cache," IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 46, NO. 1, JANUARY 2011.
- S. Iyer et al., "Embedded DRAM: Technology Platform for BlueGene/L Chip," IBM J. Res. & Dev., Vol. 49, No. 2/3, MARCH/MAY 2005, pp.333-50.
- Barth, J. et al., "A 300MHz Multi-Banked eDRAM Macro Featuring GND Sense, Bit-line Twisting and Direct Reference Cell Write," ISSCC Dig. Tech. Papers, pp. 156-157, Feb. 2002.
- Barth, J. et al., "A 500-MHz Multi-Banked Compilable DRAM Macro With Direct Write and Programmable Pipelining," IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 40, NO. 1, JANUARY 2005.
- Butt, N., et al., "A 0.039um<sup>2</sup> High Performance eDRAM Cell based on 32nm High-K/Metal SOI Technology," IEDM pp. 27.5.1-2, Dec 2010.
- Bright, A. et al., "Creating the BlueGene/L Supercomputer from Low-Power SoC ASICs," ISSCC Dig. Tech. Papers, pp. 188-189, Feb. 2005.
- Blagojevic, M. et al., "SOI Capacitor-Less 1-Transistor DRAM Sensing Scheme with Automatic Reference Generation," Symposium on VLSI Circuits Dig. Tech. Papers, pp. 182-183, Jun. 2004.

# References

- Karp, J. et al., "A 4096-bit Dynamic MOS RAM" ISSCC Dig. Tech. Papers, pp. 10-11, Feb. 1972.
- Kirihata, T. et al., "An 800-MHz Embedded DRAM with a Concurrent Refresh Mode," IEEE Journal of Solid State Circuits, pp. 1377-1387, Vol. 40, Jun. 2003.
- Luk, W. et al., "2T1D Memory Cell with Voltage Gain," Symposium on VLSI Circuits Dig. Tech. Papers, pp. 184-187, Jun. 2004.
- Luk, W. et al., "A 3-Transistor DRAM Cell with Gated Diode for Enhanced Speed and Retention Time," Symposium on VLSI Circuits Dig. Tech. Papers, pp. 228-229, Jun. 2006.
- NEC eDRAM Cell Structure (MIM Capacitor): <http://www.necel.com/process/en/edramstructure.html>
- Ohsawa, T. et al., "Memory Design using One-Transistor Gain Cell on SOI," ISSCC Dig. Tech. Papers, pp. 152-153, Feb. 2002.
- Pilo, H. et al., "A 5.6ns Random Cycle 144Mb DRAM with 1.4Gb/s/pin and DDR3-SRAM Interface," ISSCC Dig. Tech. Papers, pp. 308-309, Feb. 2003.
- Taito, Y. et al., "A High Density Memory for SoC with a 143MHz SRAM Interface Using Sense-Synchronized-Read/Write," ISSCC Dig. Tech. Papers, pp. 306-307, Feb. 2003.
- Wang, G. et al., "A 0.127 mm<sup>2</sup> High Performance 65nm SOI Based embedded DRAM for on-Processor Applications," International Electron Devices Meeting, Dec. 2006.
- G. Fredeman et al., "A 14 nm 1.1 Mb Embedded DRAM Macro With 1 ns Access," in IEEE Journal of Solid-State Circuits, vol. 51, no. 1, pp. 230-239, Jan. 2016. doi: 10.1109/JSSC.2015.2456873