

# High-Performance Design

**Rahul Rao**

IBM Systems and Technology Group

# Content & Learning Objectives

## □ SRAMs

- Memory hierarchy and organization, SRAM building blocks and peripherals, modes of operation, common and uncommonly used cell types with their merits / demerits, Assists circuitry
- Introduction to next generation memory (circuits)

## □ Reliability and Variation

- Source of variation, Variation detection circuits, impact on SRAMs
- Bias Temperature Instability
- Variation tolerant circuits / methods

## □ Other topics?

# References

## ❑ CMOS VLSI Design: Circuits and Systems Perspective


- ❑ Chapter 12 'Array Subsystem'
- ❑ Authors: Neil Weste and David Harris

## ❑ Design of High performance Microprocessor Circuits

- ❑ Part V: Memory System Design
- ❑ Authors: A Chandrakasan, W Bowhill, F Fox

## ❑ Conference / Journal papers (as we go)




# Memory Classification revisited

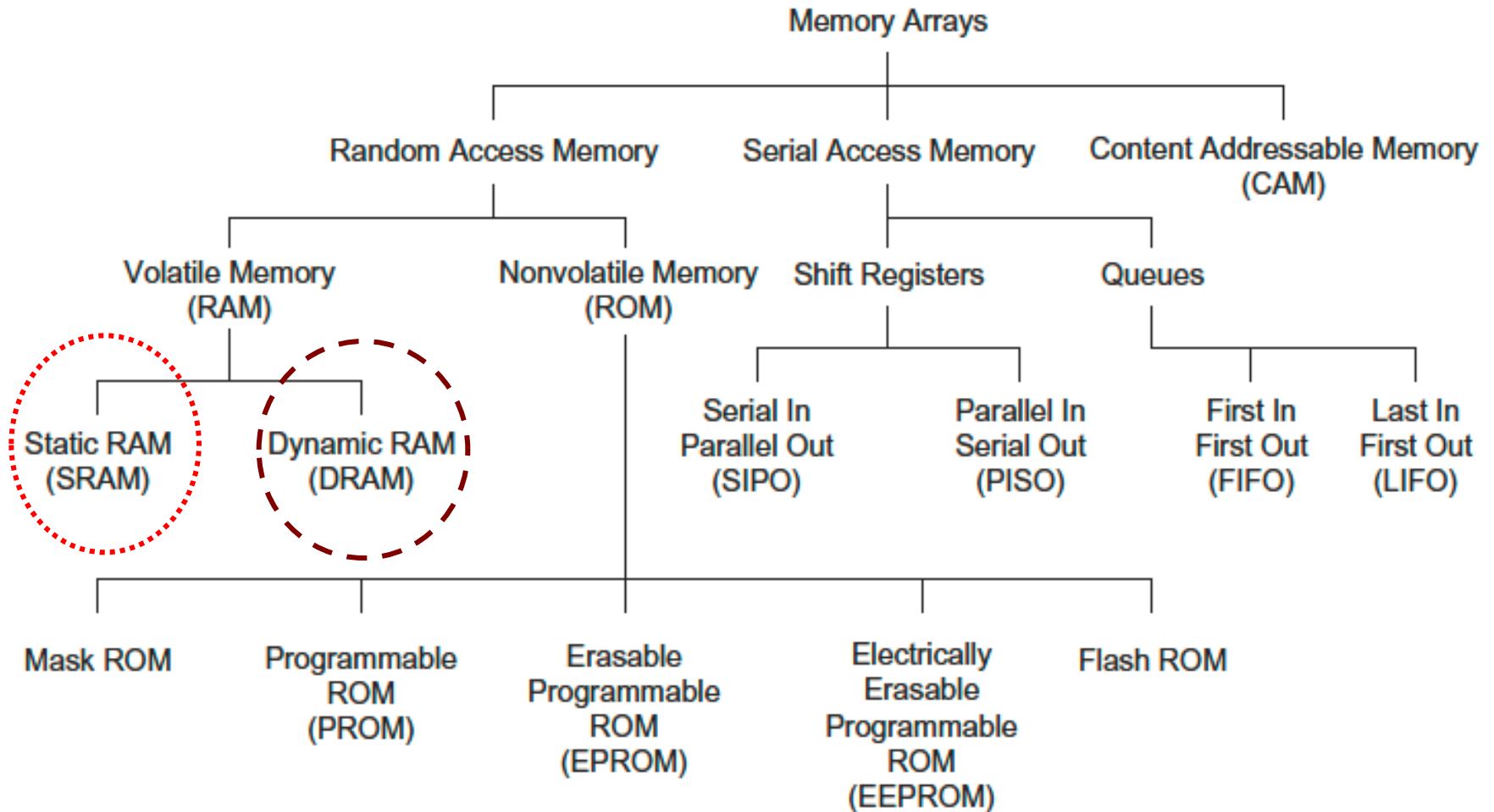


# Topics

- ❑ SRAM : Basic memory element
- ❑ Operations and modes of failure
- ❑ Cell optimization
- ❑ SRAM peripherals
- ❑ Memory architecture and folding


# Back to Back Inverters

   

# Butterfly Curve

 


# SRAM Cell

 

5T-SRAM Cell


WLO

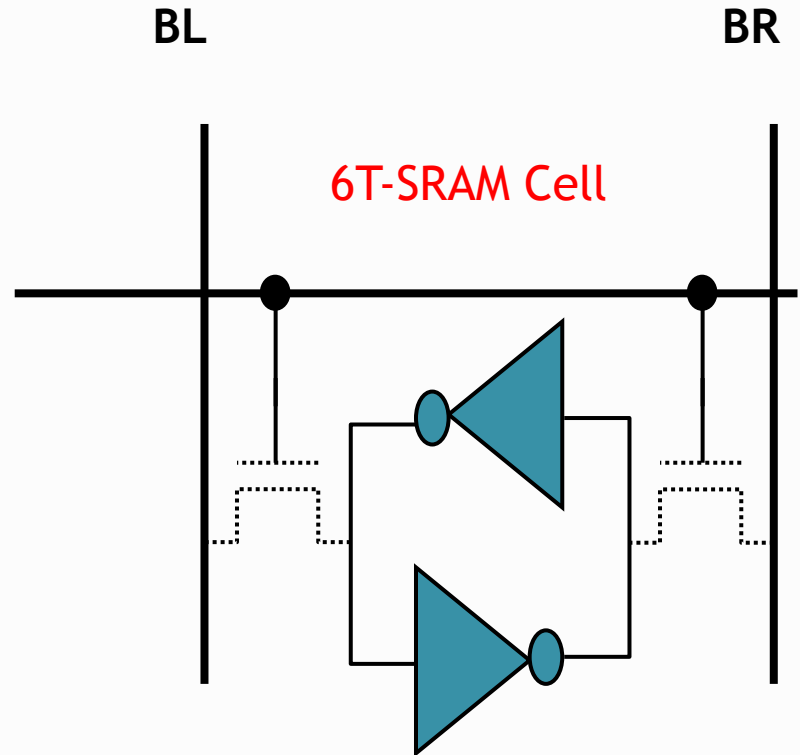



6T-SRAM Cell




# No Operation (Hold)

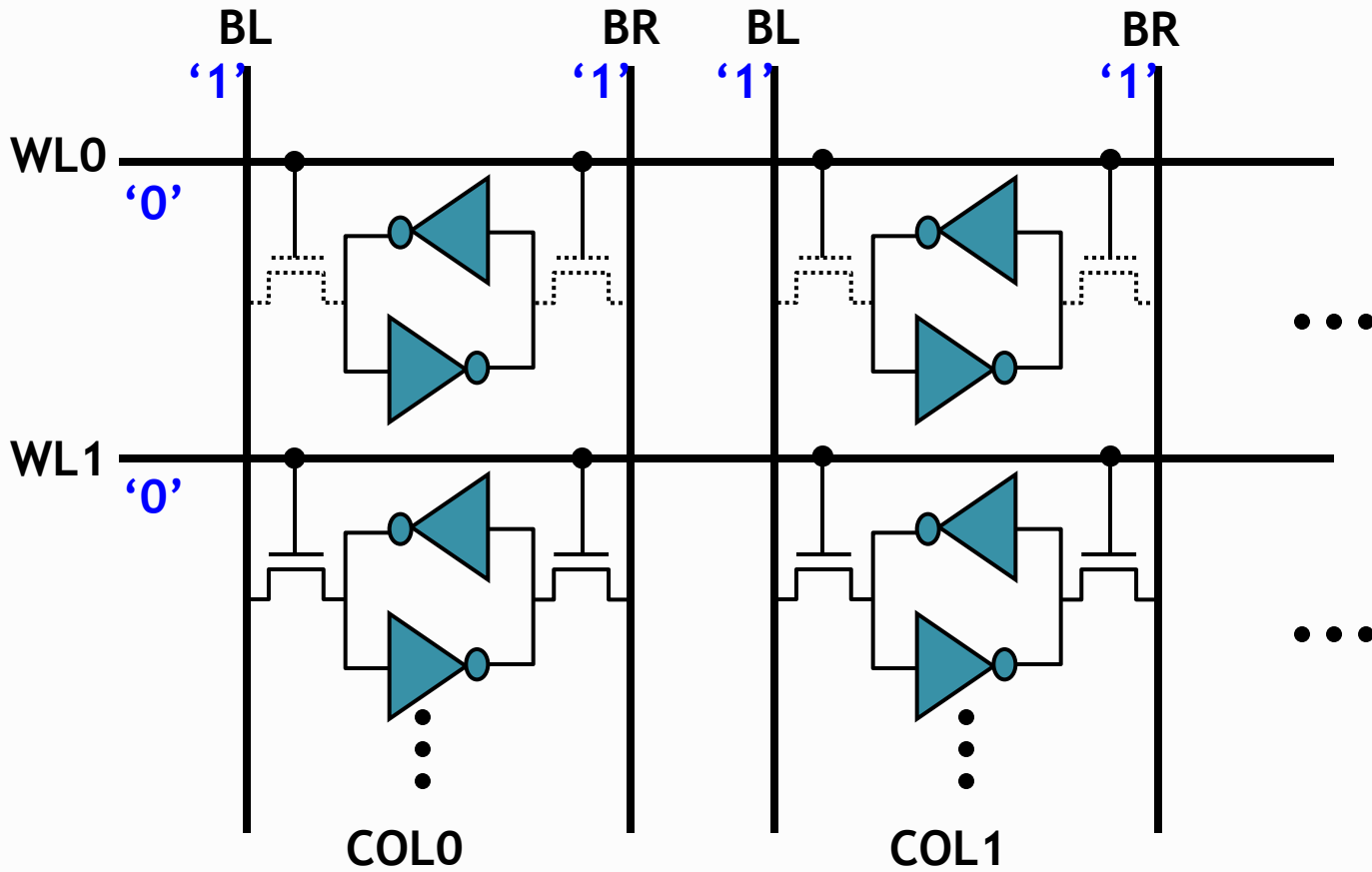
  
# Differences between latch and memory cell?




# Margin Measurement


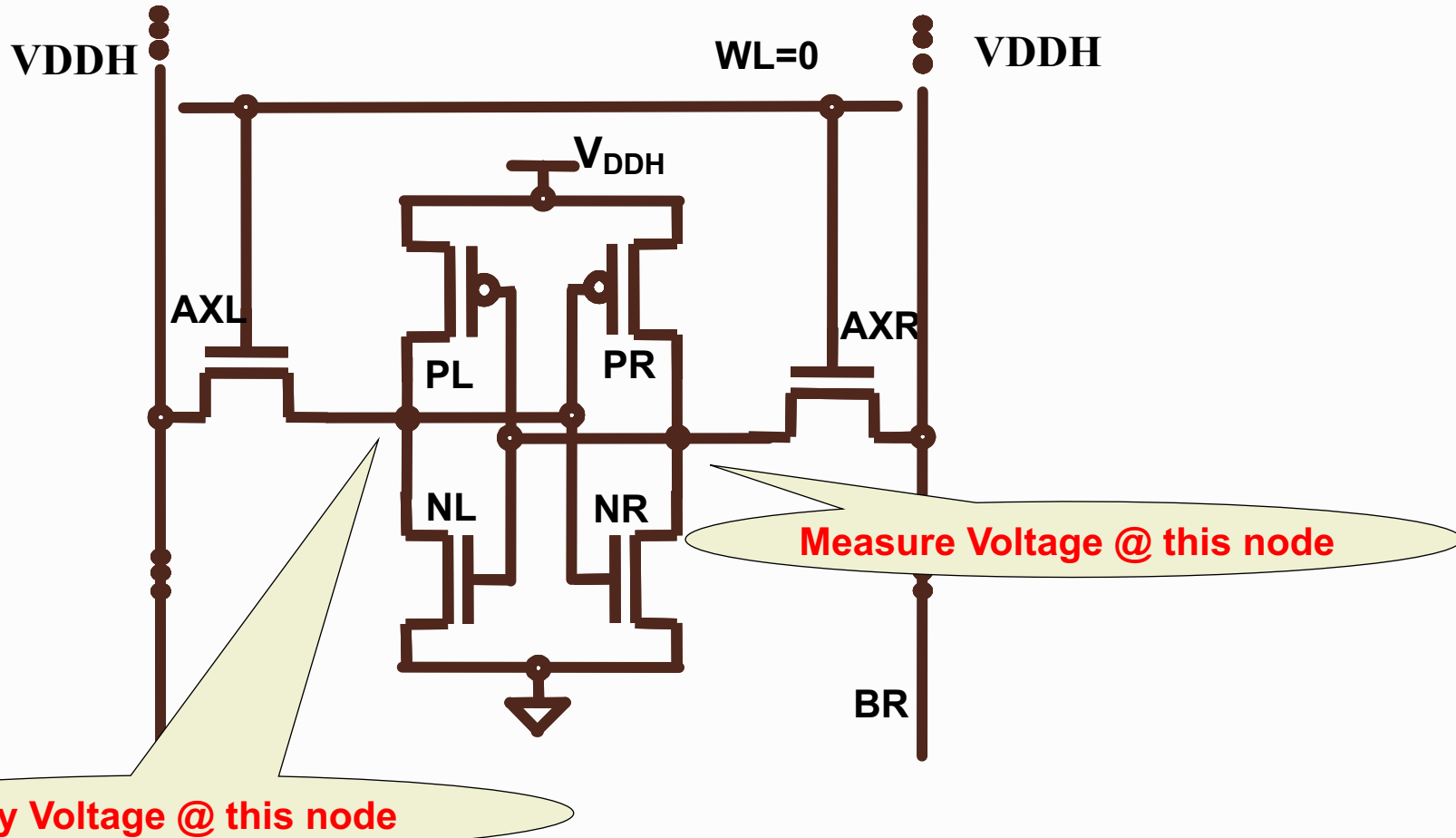


Then flip the application and measurement sides (use half cells).  
Plot the Transfer curves on the same graph

# Hold Failure

 


$$P_{HF} = P(V_{DDHmin} > V_{HOLD})$$

  


**Hold Failure => Flipping of cell data in the Hold mode with the application of a lower supply voltage.**


# Hold Margin

 


# Hold Margin

 

# Hold Margin



 


# Read Operation

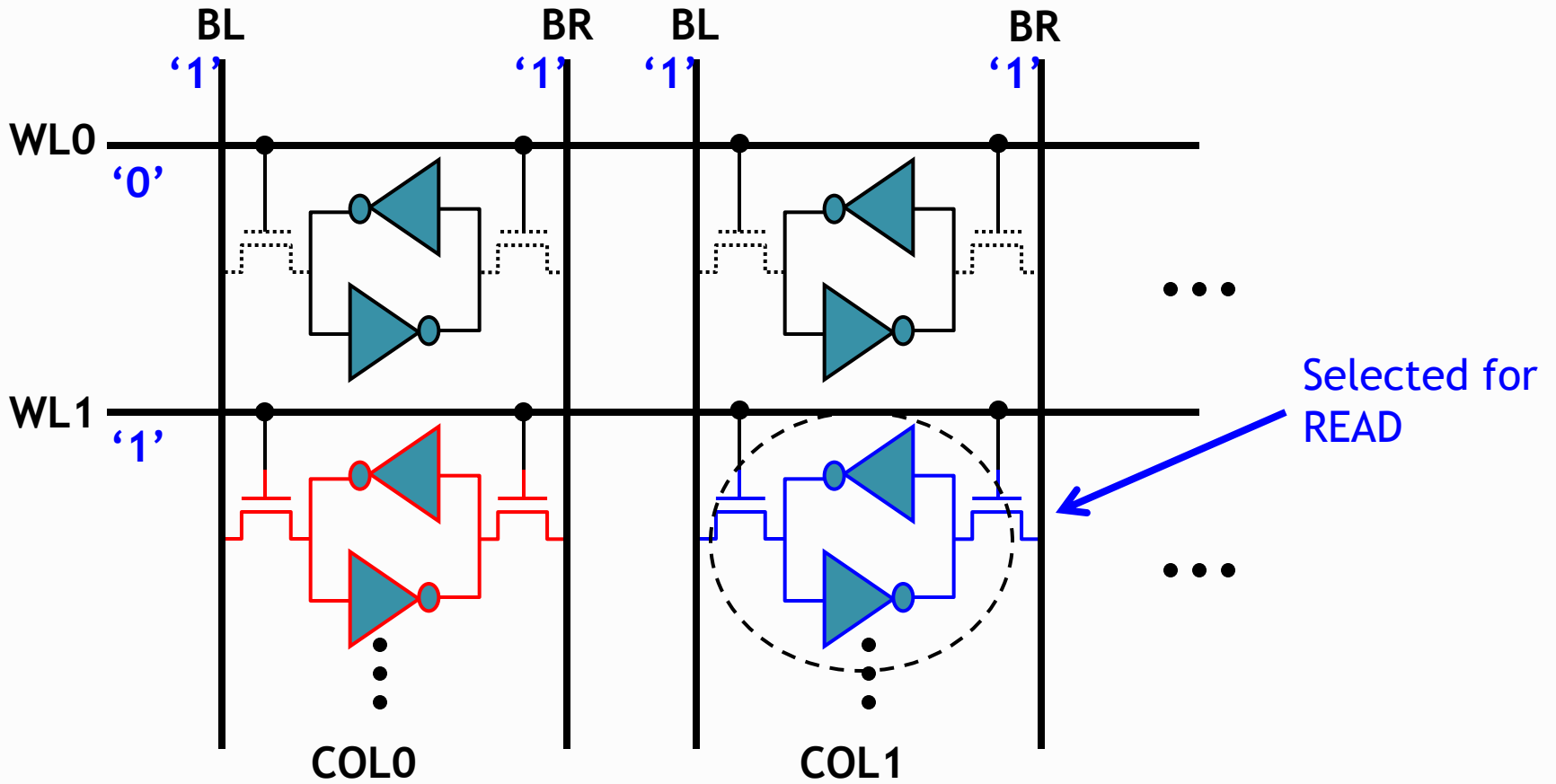



# Flip During Read: Read Failure

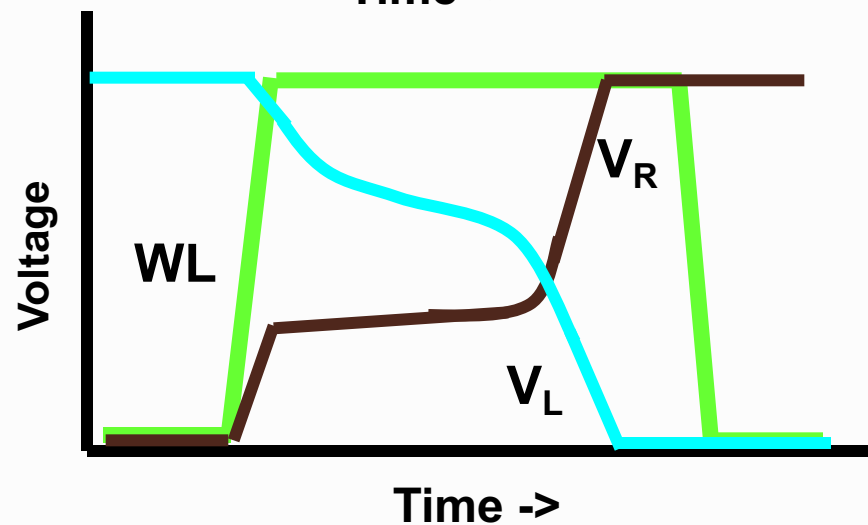 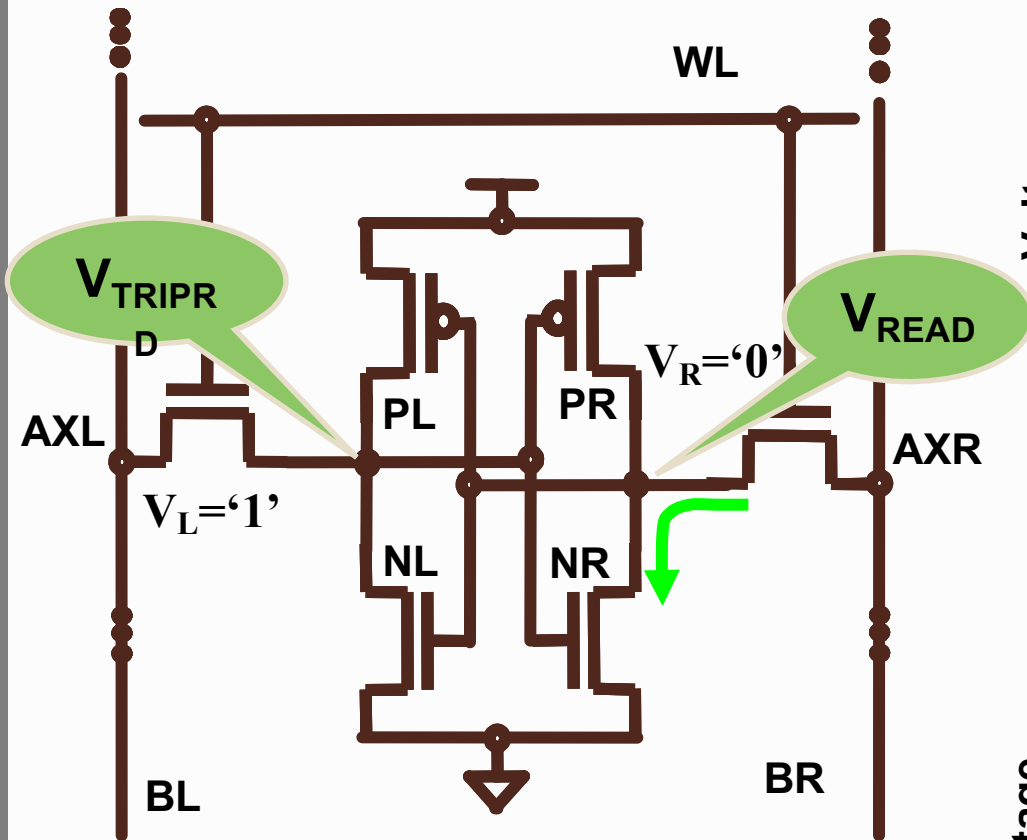

$$P_{RF} = P(V_{READ} > V_{TRIPRD})$$


Read failure => Flipping of Cell Data while Reading

# Question 1


## Hold Margin for an SRAM cell

- a) Is always greater than read margin
- b) Can be improved by making the access transistor bigger
- c) Defines the minimum supply voltage required to perform a read operation
- d) Depends on the number of cells on the bit line




# Hold vs Read Margin

 

# Write Operation

 


# Write Failure

  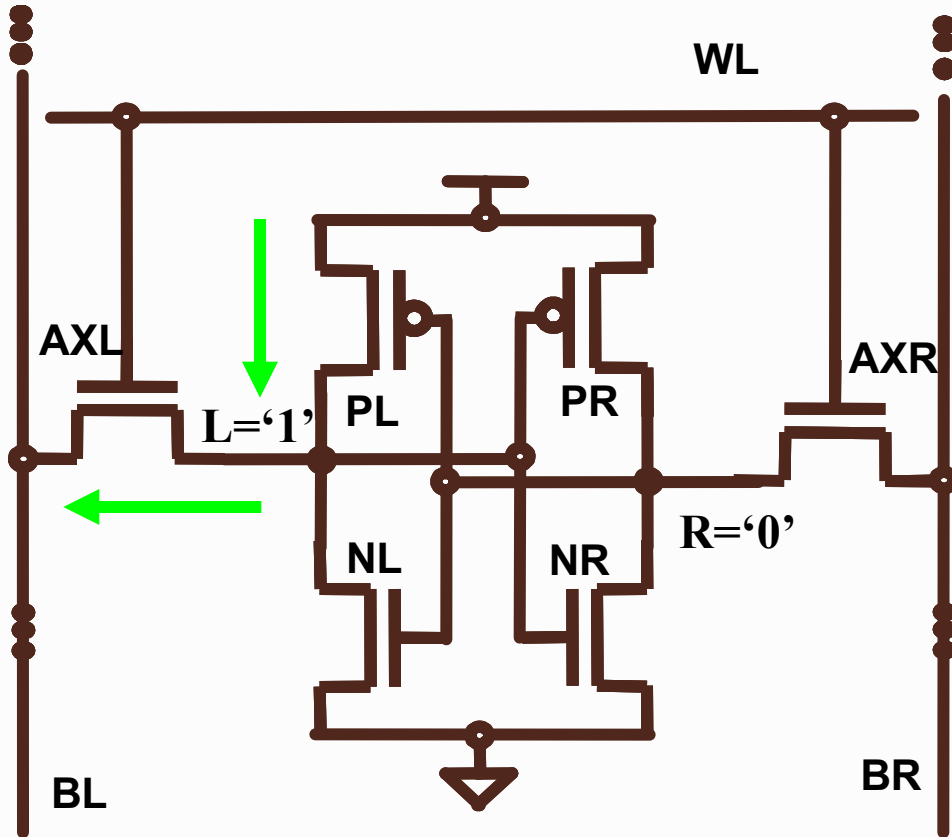



$$P_{WF} = P(T_{WRITE} > T_{WL})$$

Write Failure => Unsuccessful write to the cell.

# Write Margin

 

# Access Failure

  

$$P_{AF} = P(T_{ACCESS} > T_{MAX})$$

**Access Failure :** Time required to produce a pre-specified bit-differential is higher than a maximum allowed time.


## Question 2

### Write Margin for an SRAM cell

- a) Is always greater than read margin
- b) Can be improved by making the access transistor bigger
- c) Defines the minimum supply voltage required to perform a read operation
- d) Depends on the number of cells on the bit line



# The Balancing Act

 


**Large N:** Better READ performance. If too large, trip voltage of inverter becomes so low that cell becomes unstable.

**Large A:** Better Performance. If too large, storage node voltage goes high during READ, causing cell flip


**Large P:** Increase stability. If too large, hard to WRITE.

Need to balance all : **NR:XR:PR** ~ 2:1:1


# Workhorse 6T-Cell

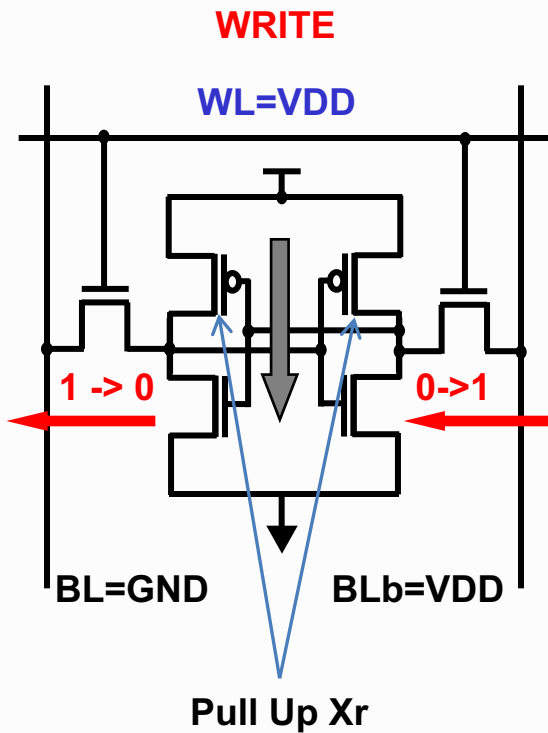

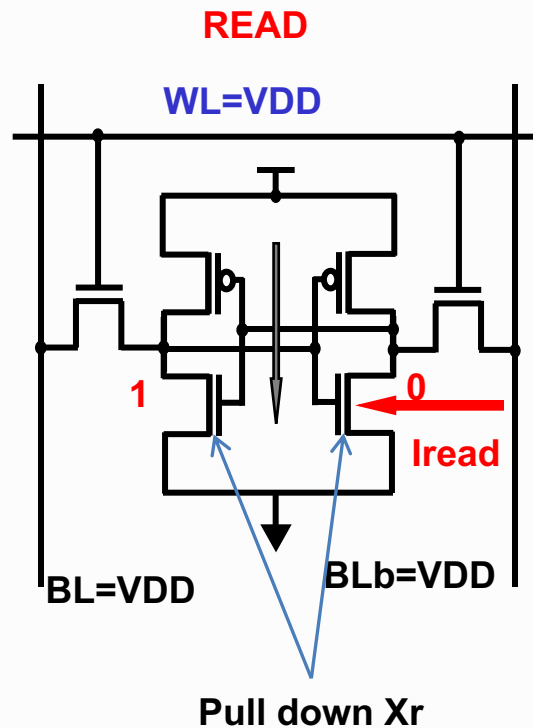Access  $X_r$ : On  
 Data driven on bit - lines  
 Data Flipped by over-  
 coming pull-up / pull -  
 down  $X_r$ s




 
Access  $X_r$ : On  
 BL, Blb pre-conditioned,  
 and then floated, one  
 line discharges thru the  
 cell ( $I_{read}$ ), voltage  
 sensed, Data Retained



Access  $X_r$  : Off  
 Data Retained, due  
 to back-to-back  
 inverters

# Thin Cell (Litho-Friendly)

Cell area vital for density

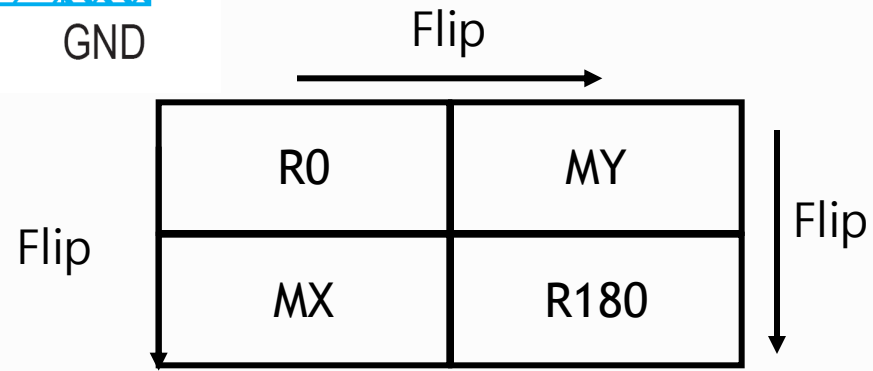 

## Question 2c

Decreasing the size of only one side of NFET transistors will improve the cell

- a) Cell density
- b) Read margin
- c) Write margin
- d) Hold margin

# Topics

- ❑ Introduction to memory
- ❑ SRAM : Basic memory element
- ❑ Operations and modes of failure
- ❑ Cell optimization
- ❑ SRAM peripherals
- ❑ Memory architecture and folding


# Decoders and Drivers

WL driver	cell	cell	cell	cell
WL driver	cell	cell	cell	cell


•  
Word line driver layout needs to be pitch  
matched to SRAM cell  
•

WL driver	cell	cell	cell	cell
WL driver	cell	cell	cell	cell
Decoder and Control	Column Circuitry			


# Column Circuitry for Read and Write

 

**READ**

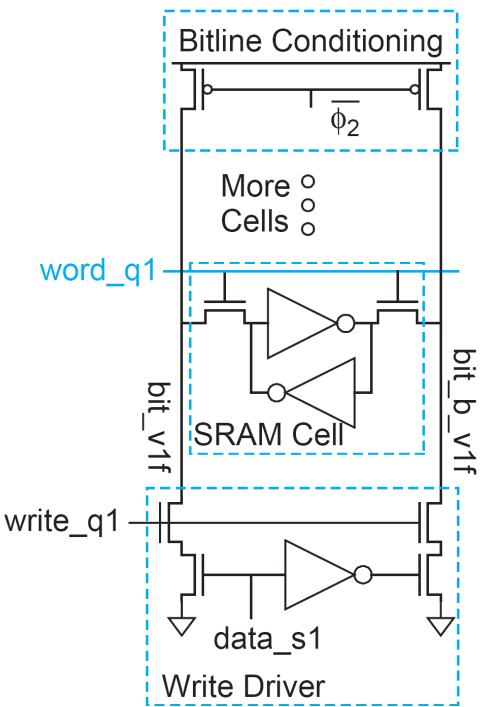


(a)

 

(b)

**WRITE**

# Sense Amplifiers

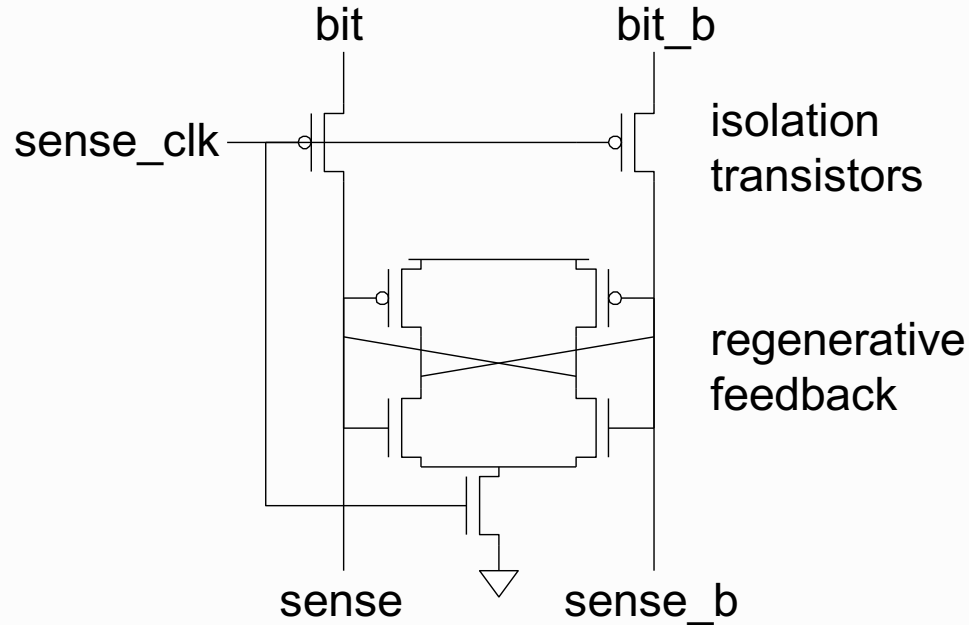


Sense-amp provide necessary gain (small input  $\rightarrow$  large output) for read  
If sense\_clk arrives too early  $\rightarrow$  False read may happen due to too small difference  
If sense\_clk arrives too late  $\rightarrow$  Too slow

Isolation transistors: Disconnects sense amp to cutoff large bit line capacitance once sensing starts




# Hierarchical Bit-lines

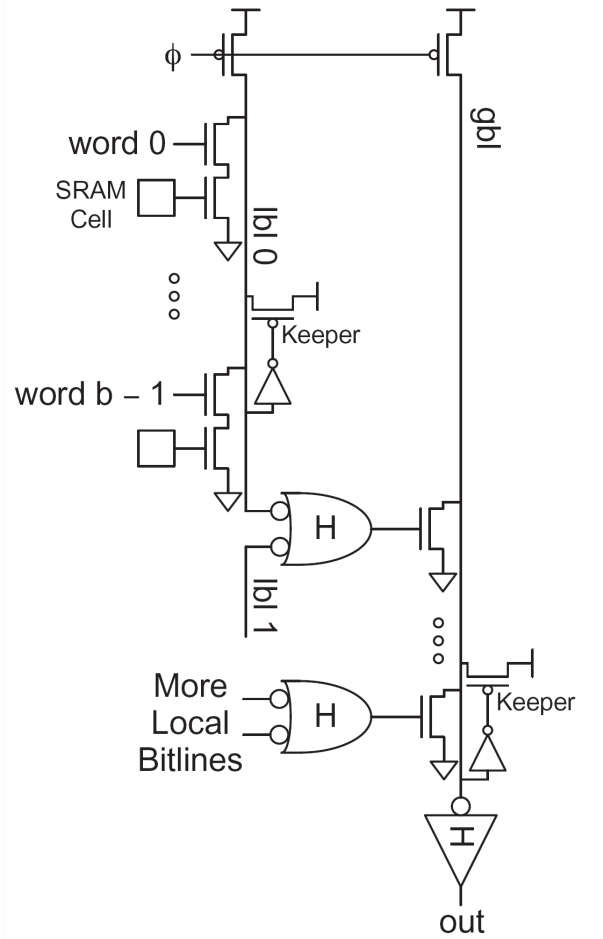


Hierarchical Bit-lines

# Pre-Conditioning

Precharge

 

Equalizer

 

Pre-Conditioning

## Question 3

### Equalizer is required

- a) Both the bitlines are pre-charged at the same time
- b) To ensure that the bit-lines are conditioned suitably for write operation
- c) To minimize offset between the bitlines prior to read operation
- d) To improve the hold and read margin of the memory cells