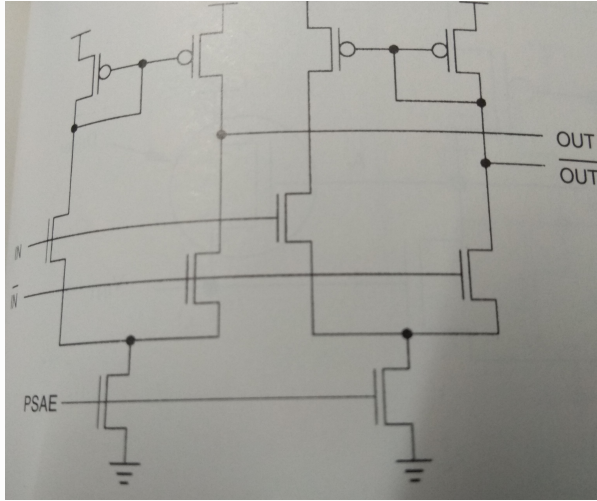


Advanced Topics in VLSI


Rahul Rao

IBM Systems and Technology Group


Sense Amplifiers (Alternate)



Current Mirror Based

 



Half Latch Based

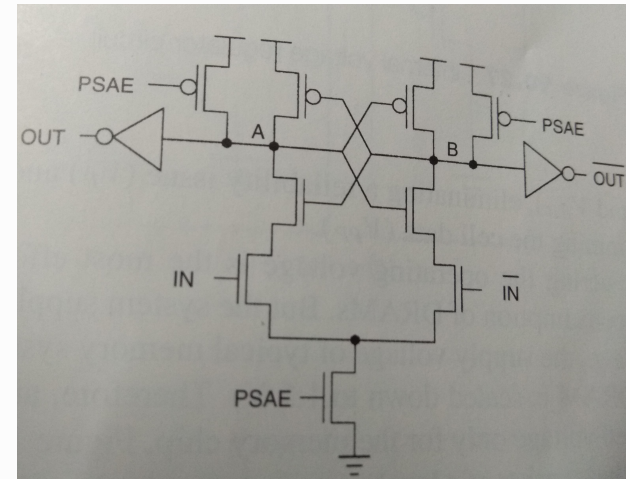

Full Differential



Discuss in class next week

Conditionally decoupling regeneration

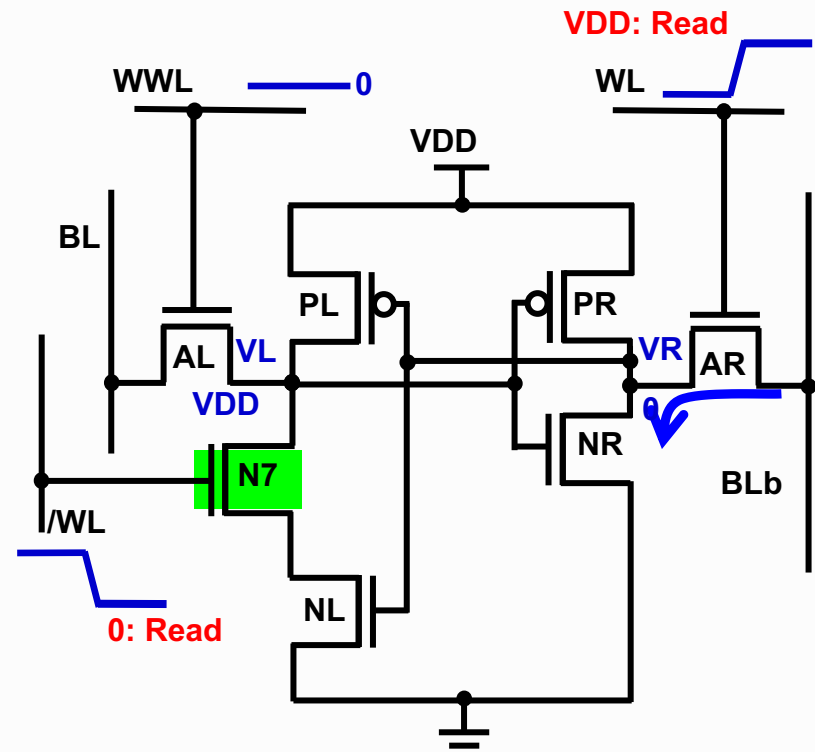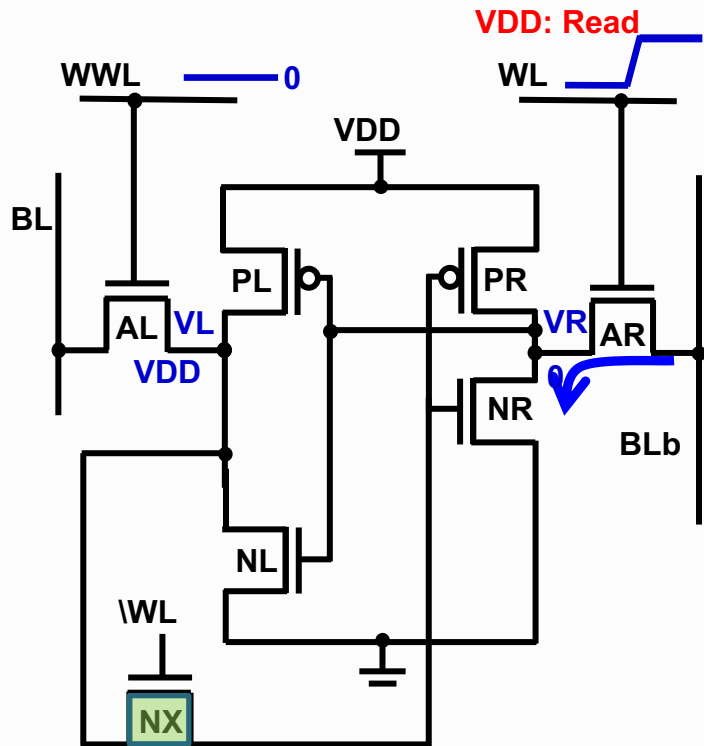


Why use /WL ...?

Thought exercise

  


Implement logic function via 8T merge

 - Concept: Use the 8-T portion of the cell for implementing logic functions
 - Possible due to decoupling of read and write paths
- RBL discharges when either C0 or C1 is high
 - Read stack remains 2-high
- And function: switch definition of WBL and WBLB
- An OR2 embodiment is shown on right
 - Can be complex OR4, OR8, etc.




A More Practical Implementation

 - + Share RWL between adjacent cells
 - => 3 word-lines in 4 metal tracks
 - Reduces coupling capacitance (+ performance and power)
- + All FEOL features identical to conventional 8T cell
 - OR
 - upper device in stack can be made smaller, reducing cell size




Low leakage SRAM

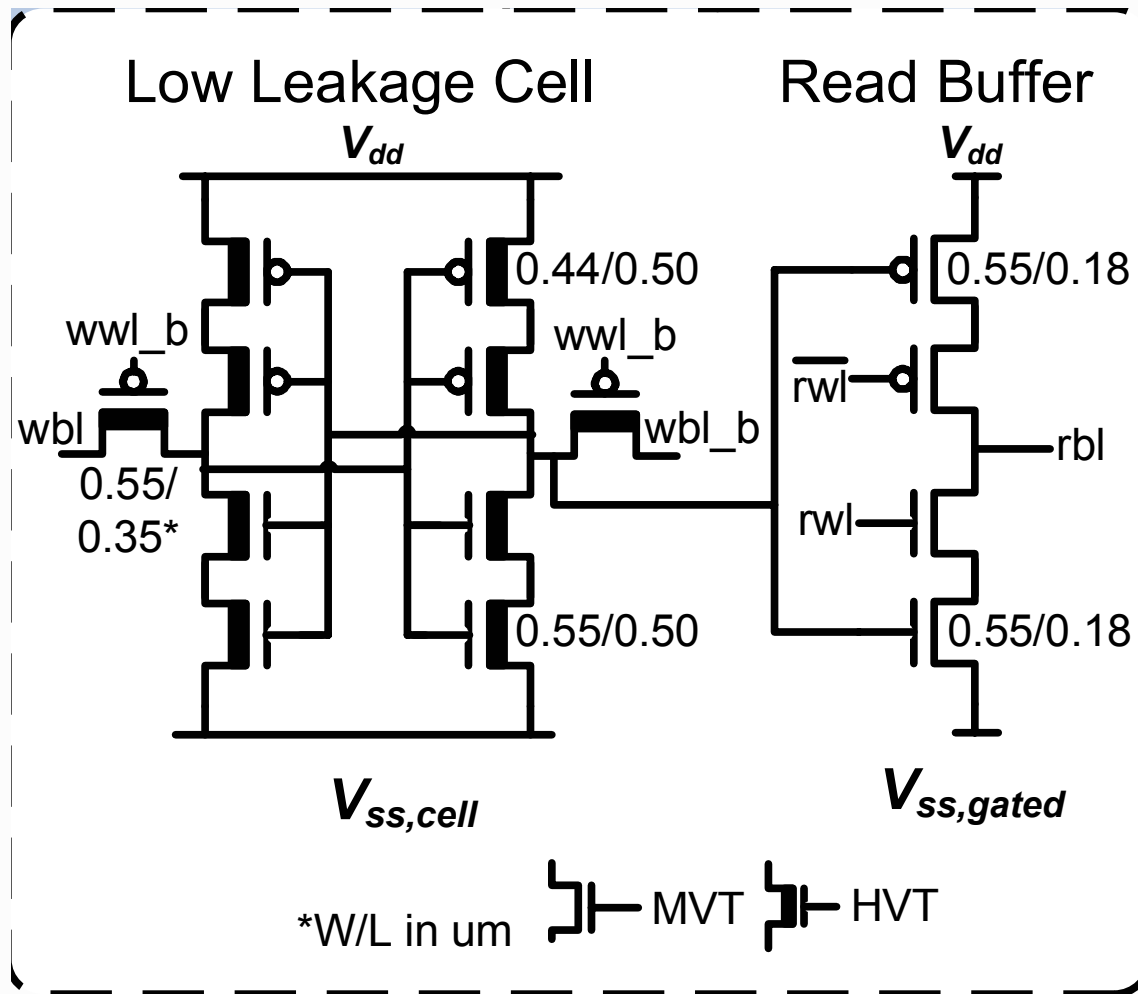


The Phoenix Processor: A 30pW Platform for Sensor Applications

(S. Hanson , VLSI Symp '08)


Multi-porting SRAM Cell

 


Multi read ports

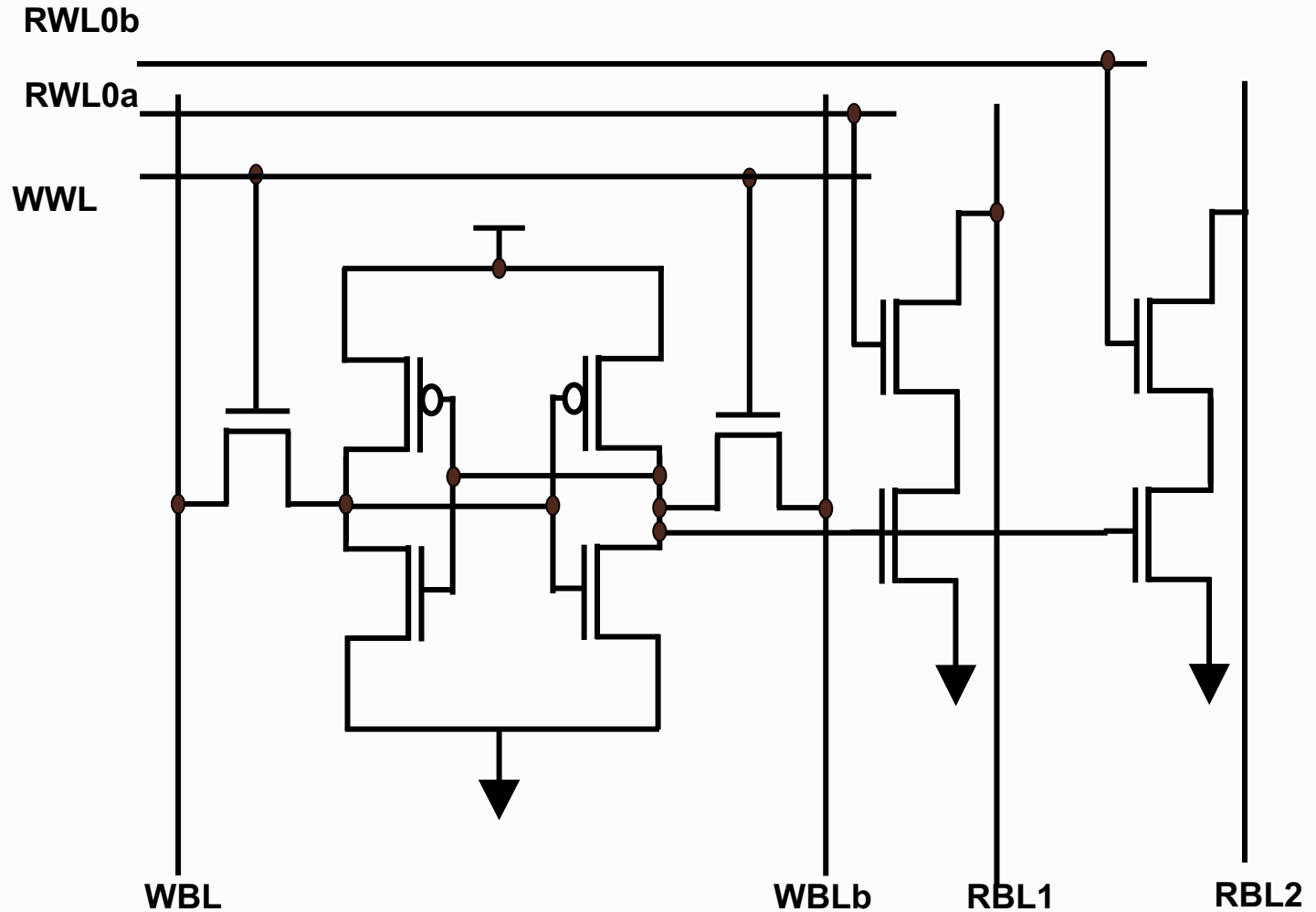

Multi read ports

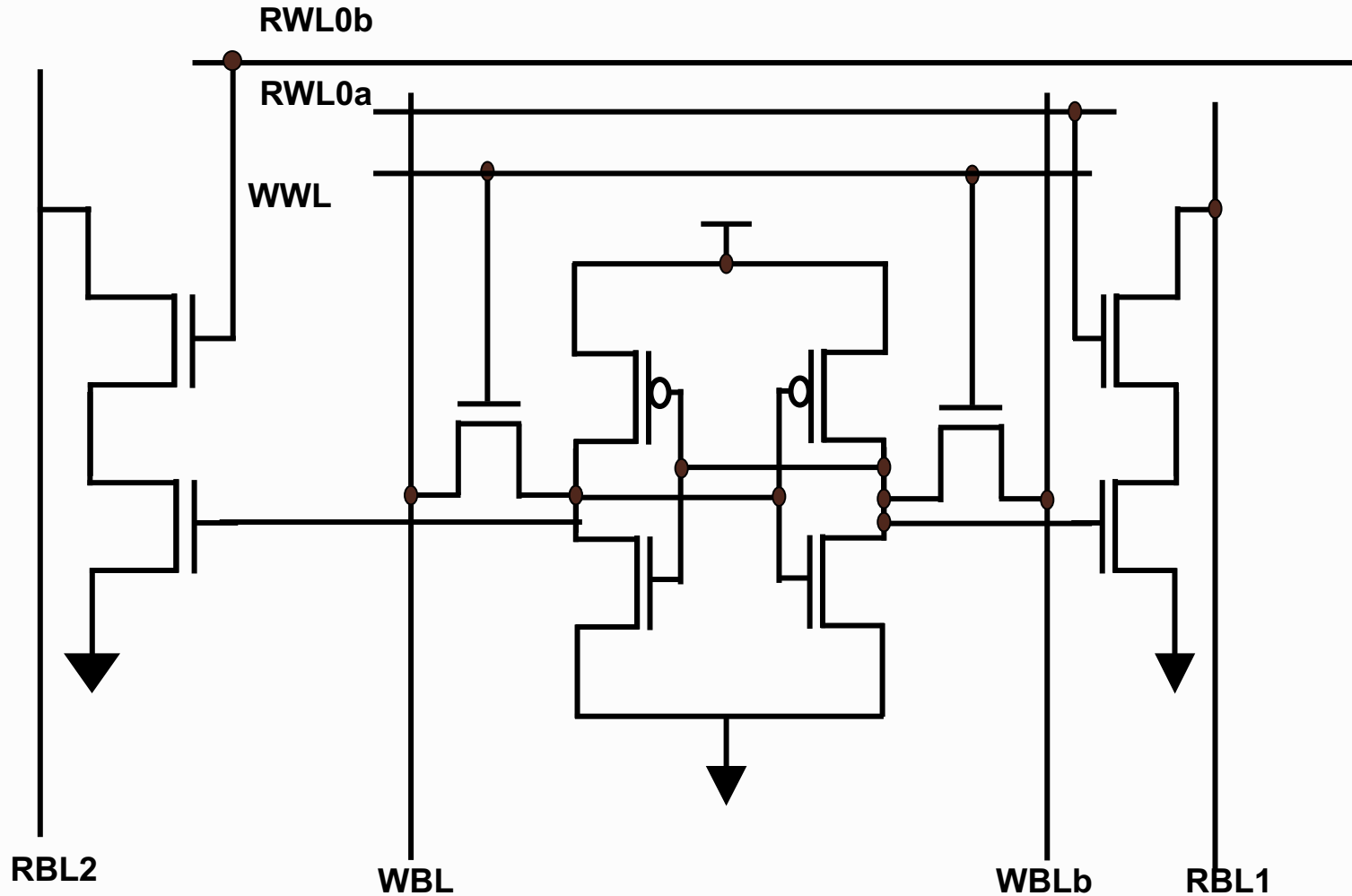


Block Diagram

 


Bank and
Bank Conflicts

Global and Local Variations





Random Dopant Fluctuation

 




intra-die

 




inter-die

    




Hold Failure

   



Read Failure

 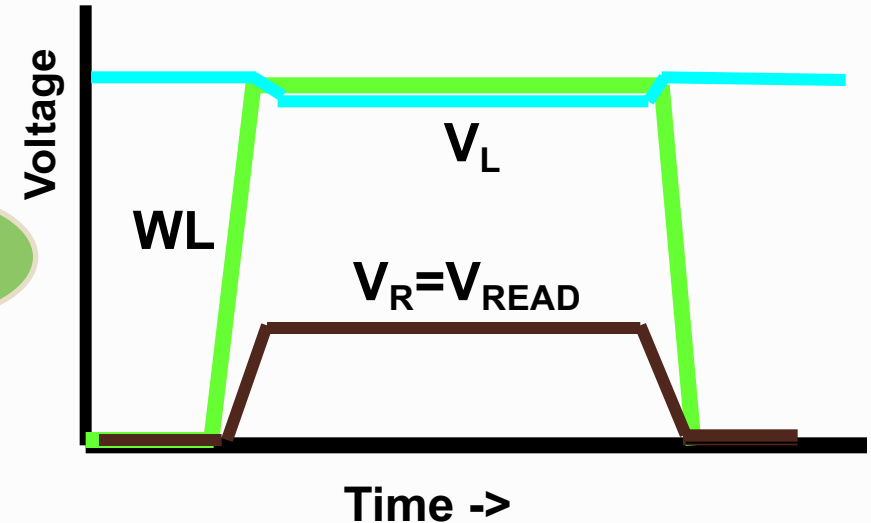 


Write Failure

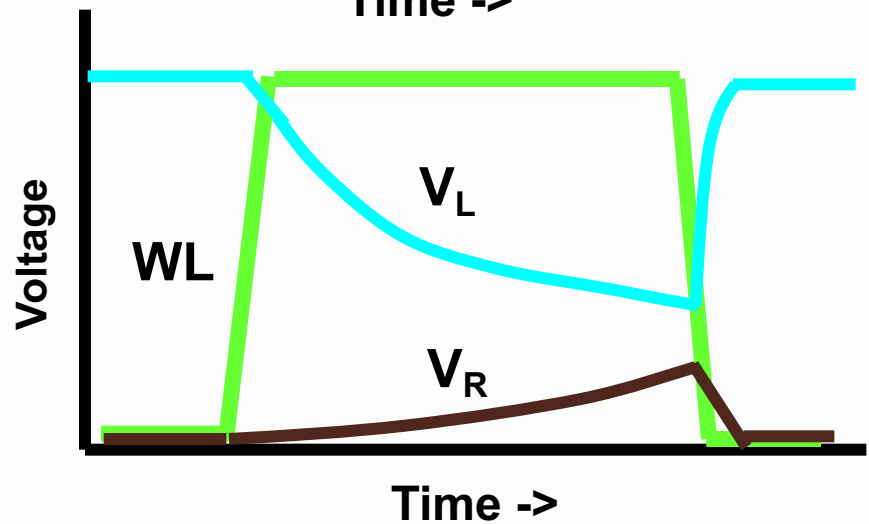  

Access Failure

  



Inter-die Variation & Cell Failures

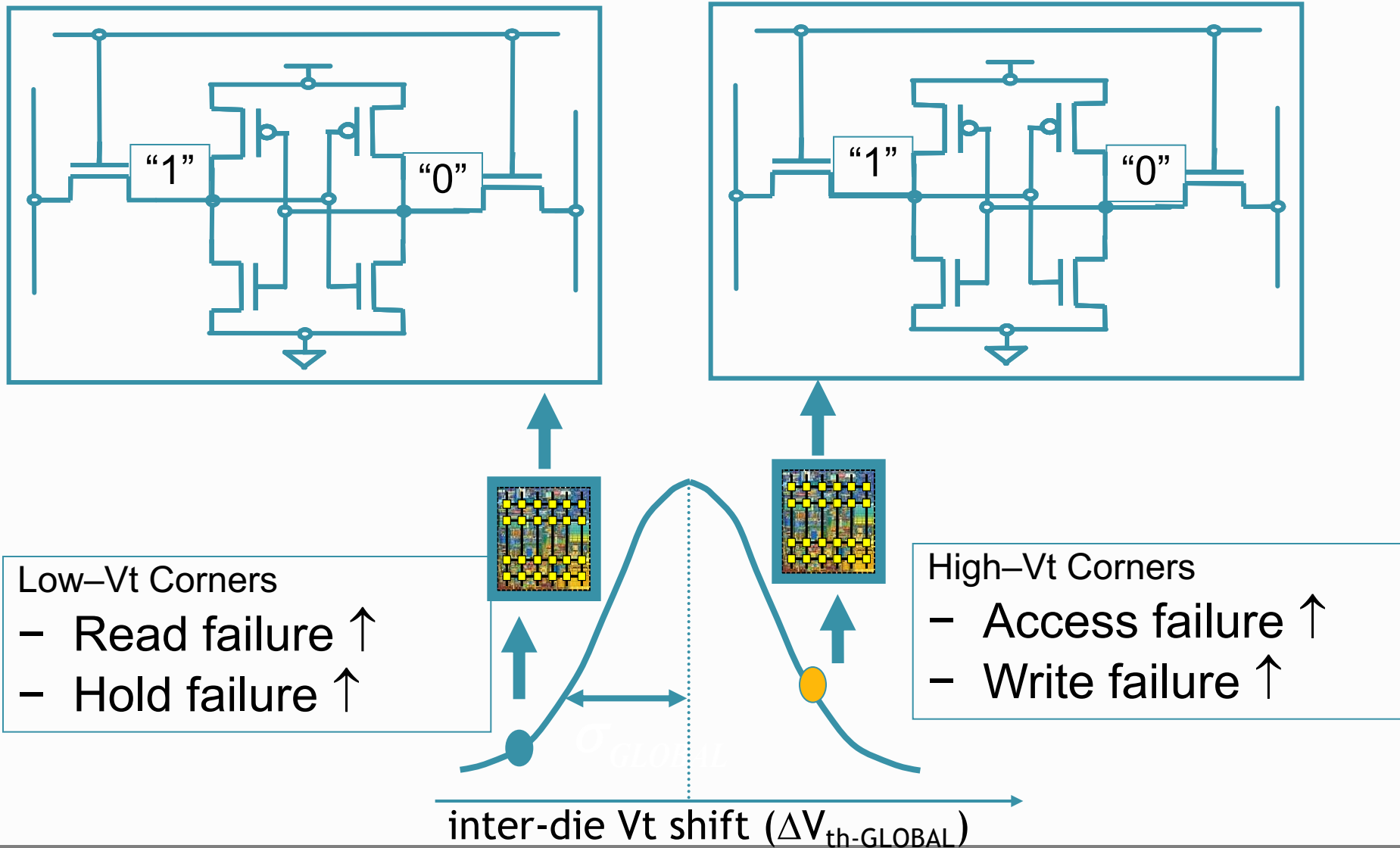

Failures in SRAM Array

Overall Cell Failure:

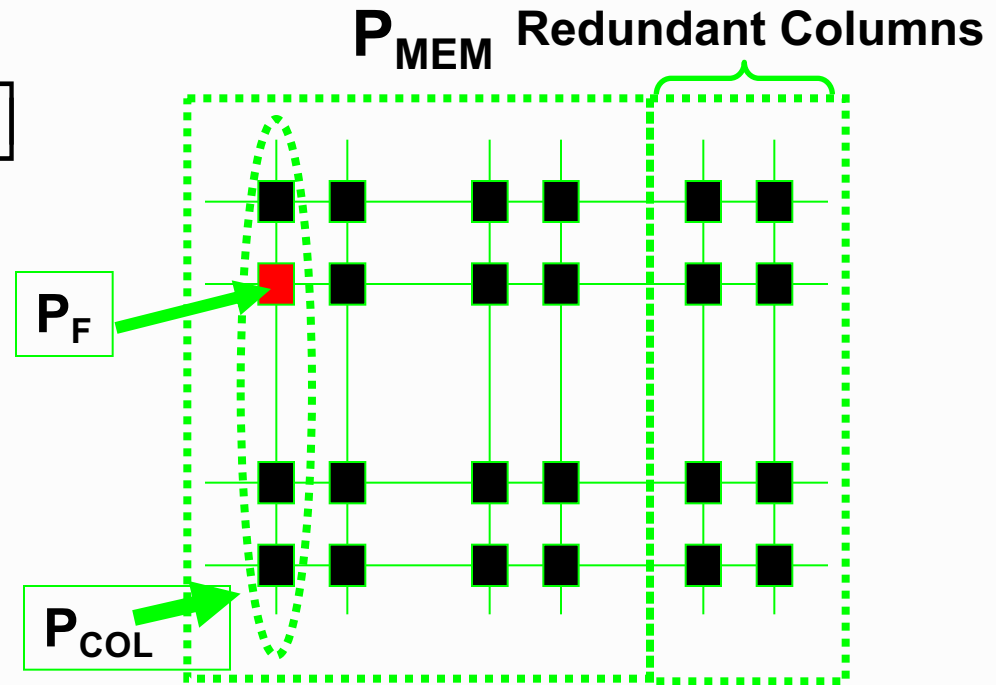 
$$P_F = P[Fail] = P[A_F \cup R_F \cup W_F \cup H_F]$$





- P_{COL} : Probability that any of the cells in a column fail

$$P_{COL} = 1 - (1 - P_F)^{N_{ROW}}$$

Transistor Sizing

 

Impact of Redundancy on Memory Failure

  

Larger redundancy



- (1) more column to replace (less memory failure).
- (2) smaller cell area (larger cell failure).

Question

☐ Array redundancy

- a) Improves cell stability
- b) Degrades cell performance (i.e increases read and write times)
- c) Does not require any change to cell peripheral circuits
- d) Row redundancy is better than column redundancy

Example: Multi-VCC for SRAM Cell

  

- Create differential voltage between WL and Cell to decouple the Read & Write
 - Write: $V_{WL} > V_{Cell}$
 - Read: $V_{WL} < V_{Cell}$