

# Variation Characterization


**Rahul Rao**

IBM Systems and Technology Group

# Characterization Circuits


	Local Variation	Global Variation
Process	Early	Mature
What is characterized	Devices (Several)	Circuits
Output Feeds	Models, Technology Tweaks, Design Trade-Offs & Margins	Adaptive Mechanisms (Static / Dynamic), Field Failure Debug
Area Constraint	Ports (PI, Pos, Clk Infrastructure)	
Power Constraint	Test Infrastructure Max Current Capacity (Test time vs Power)	If Always On. Else, Power Noise to neighboring Ckts
Timing Constraint	Test Time	Sense and React Time
Measurement	Analog or DAC based	Mostly digital
S/N Ratio	Cancel Global effects	Cancel local effects
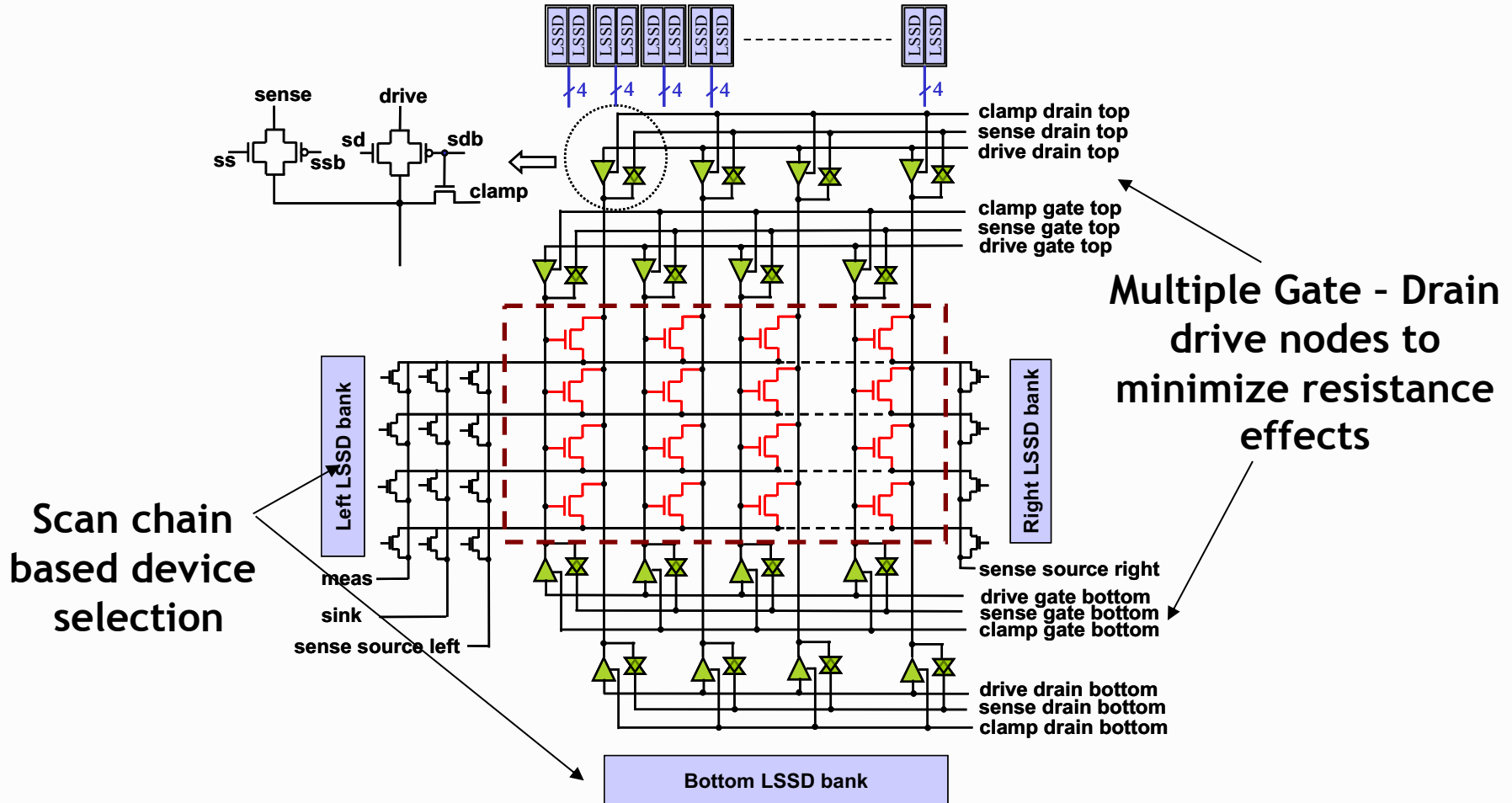
# Array Based I-V Characterization Circuits





- Measure I-V of devices in an array
- Extract  $V_t$  mismatch from “current difference” between identical transistors
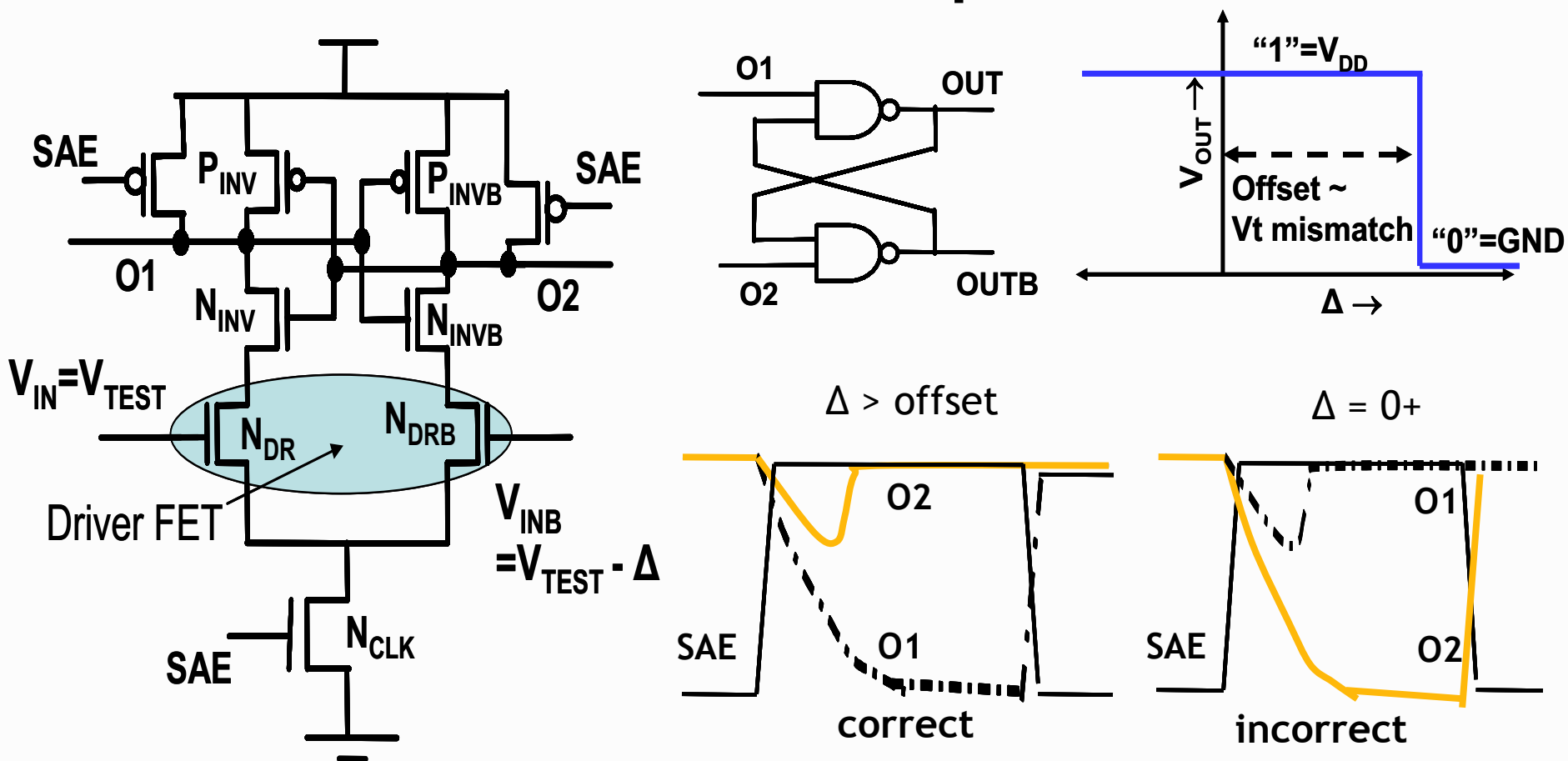
# Digital Characterization with Current Latch based Sense Amplifier




Minimum input voltage difference required for correct sensing (offset) indicates local random mismatch

# Measured Values of Local Mismatch

 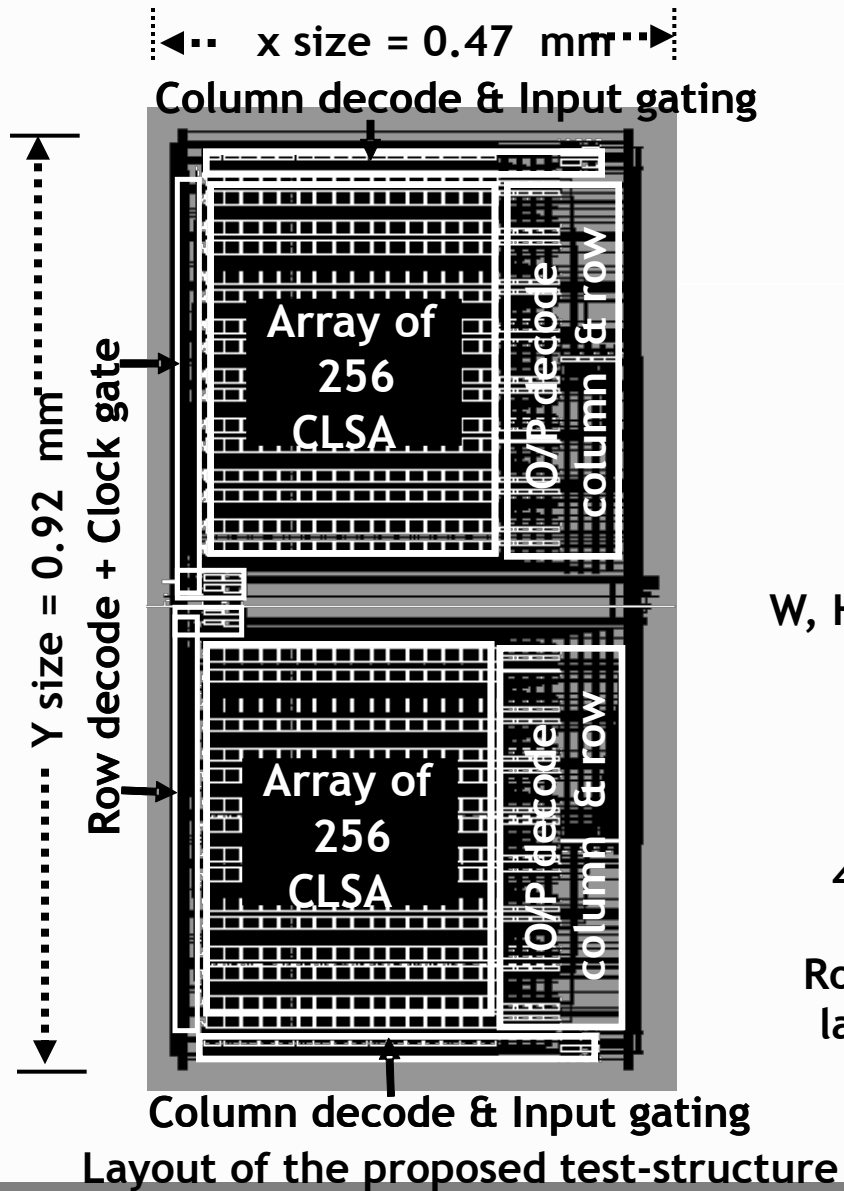

 
# Statistical Characterization of Local Variations of Individual Device



Array of identical devices

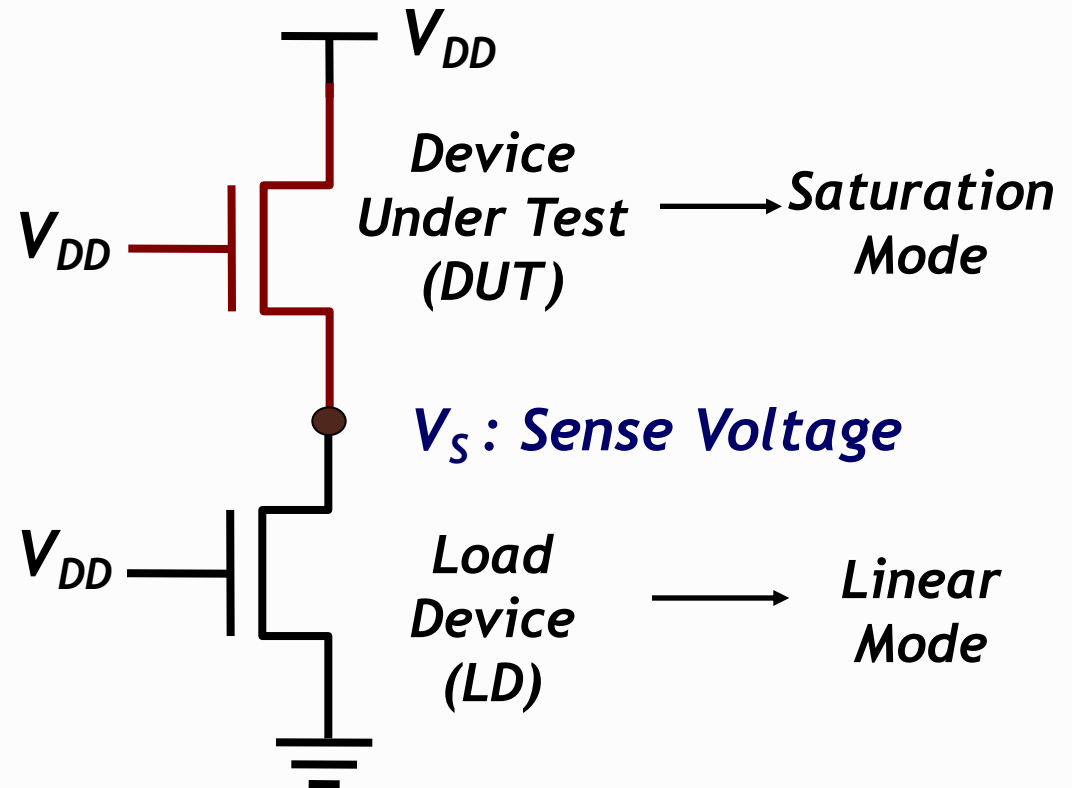
Test structure consisting of array of devices arranged in a stacked configuration with a common load device for local variability characterization



$$V_{S1} = f(V_{TH}(DUT1), V_{TH}(LD))$$


$$V_{S2} = f(V_{TH}(DUT2), V_{TH}(LD))$$

# Sensor Block

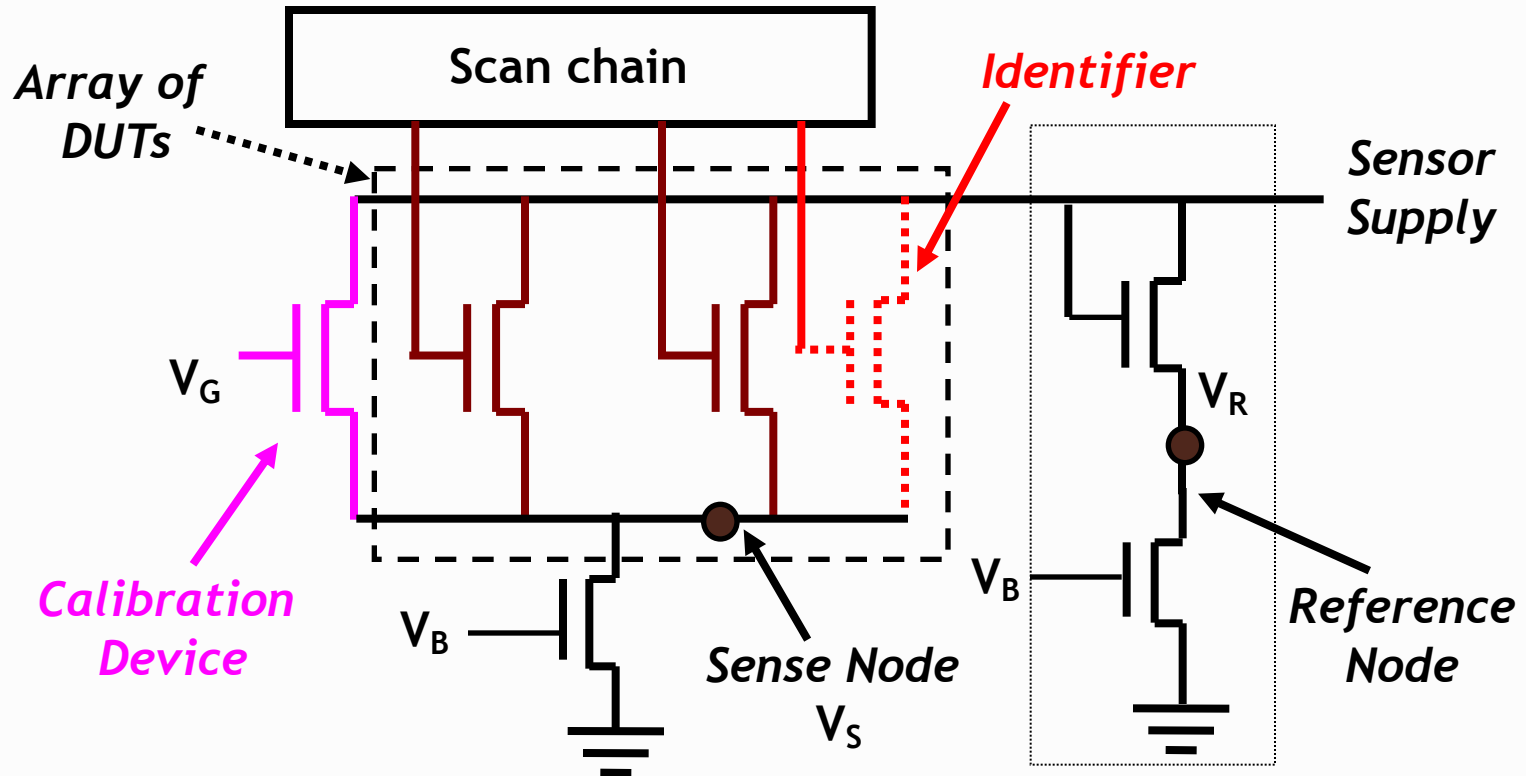

- Select each DUT individually to form stacked configuration with load device
- Determine Sense Node Voltage ( $V_S$ )
- Difference in  $V_S$  represents current mismatch between the DUTs


# Sensor Block

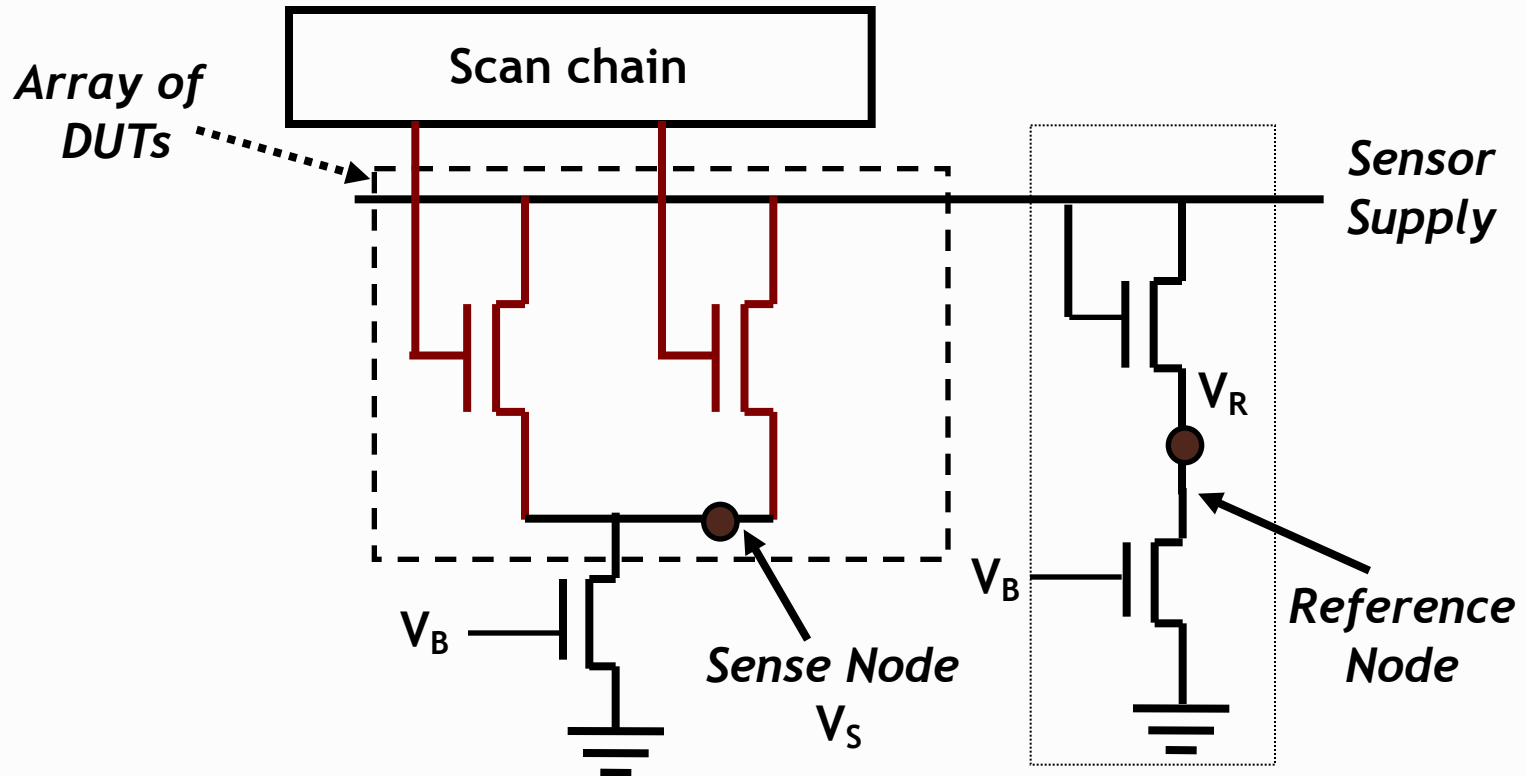


- Select each DUT individually to form stacked configuration with load device
- Determine Sense Node Voltage ( $V_S$ )
- Difference in  $V_S$  represents current mismatch between the DUTs



# Sensor Block

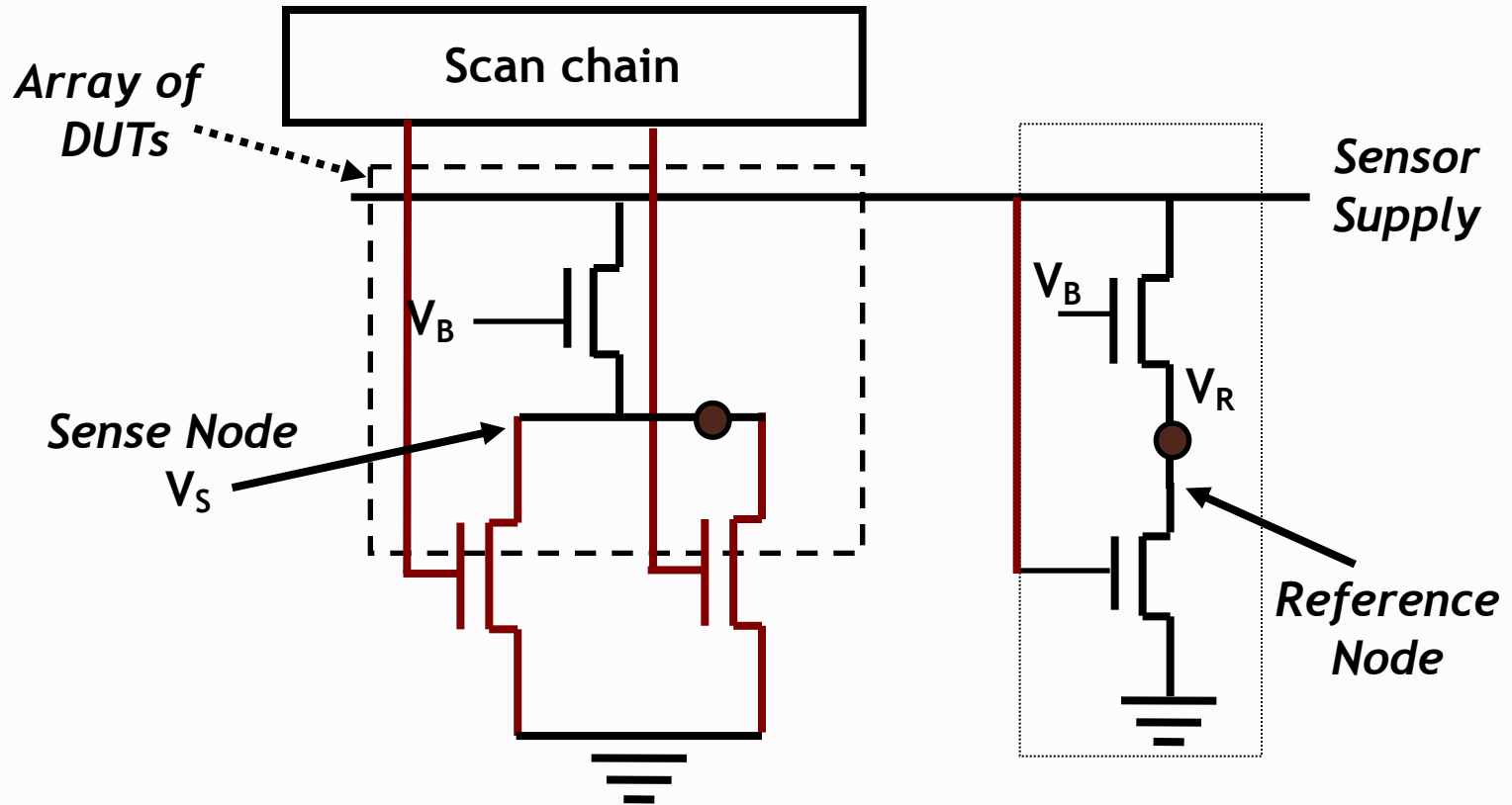


# Block Diagram

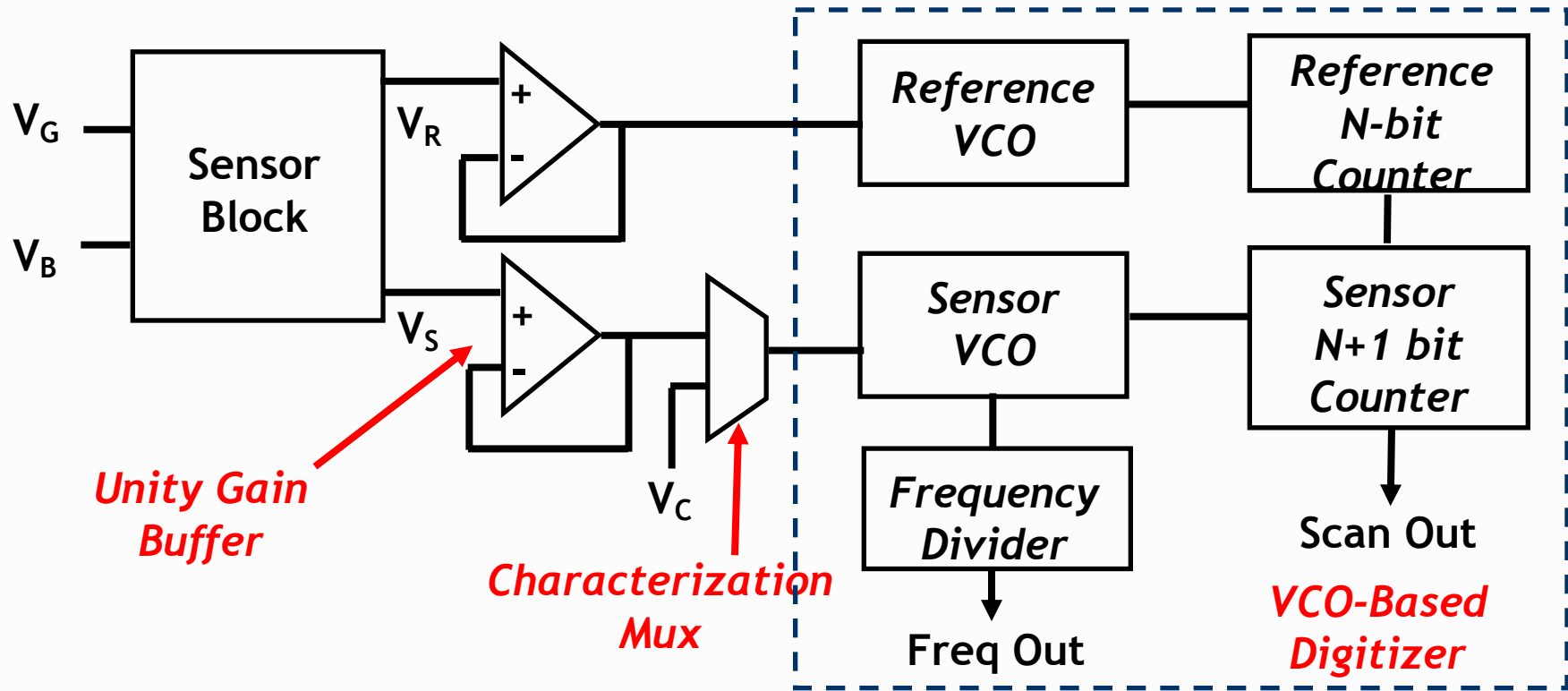

- Unity Gain Buffer protects sense node from mux / VCO noise
- Reference VCO sets up time - base for Sensor Counter
- Output of Sensor counter is digital indication of sensor VCO frequency and hence a representation of threshold voltage of DUT


# High Sensivity Variation Sensor

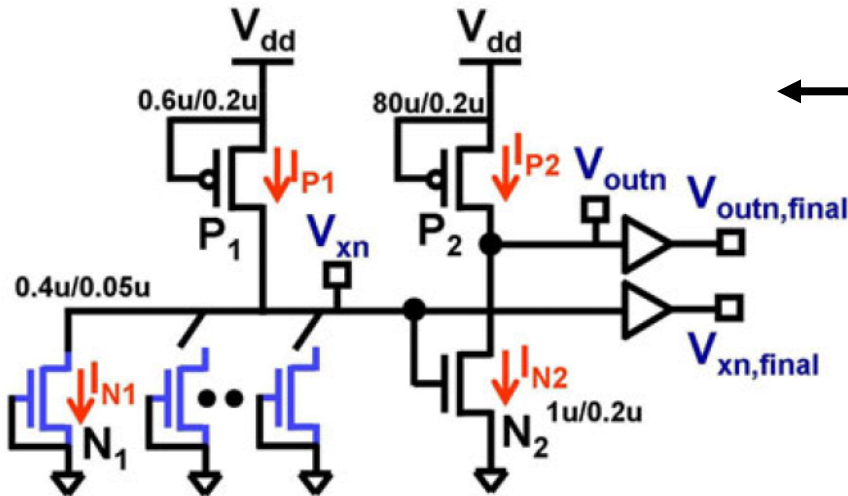


← Biasing DUTs in sub-threshold mode to enhance sensitivity

2<sup>nd</sup> stage is for amplification

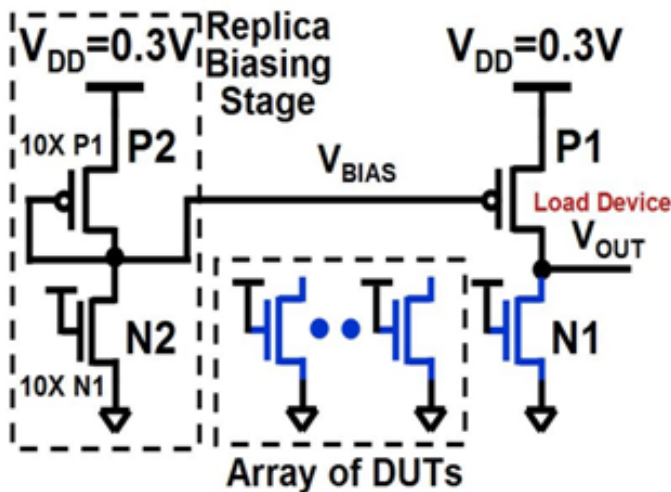
Hierarchical Switch Network to minimize leakage noise from unselected DUTs




On-chip generation of V<sub>Bias</sub>

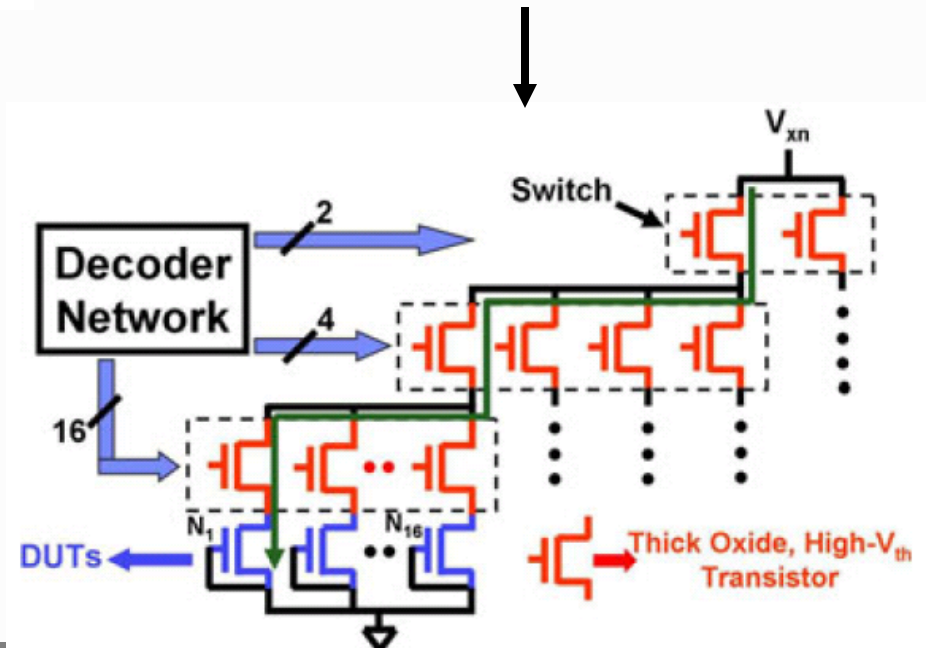

# High Sensivity Variation Sensor

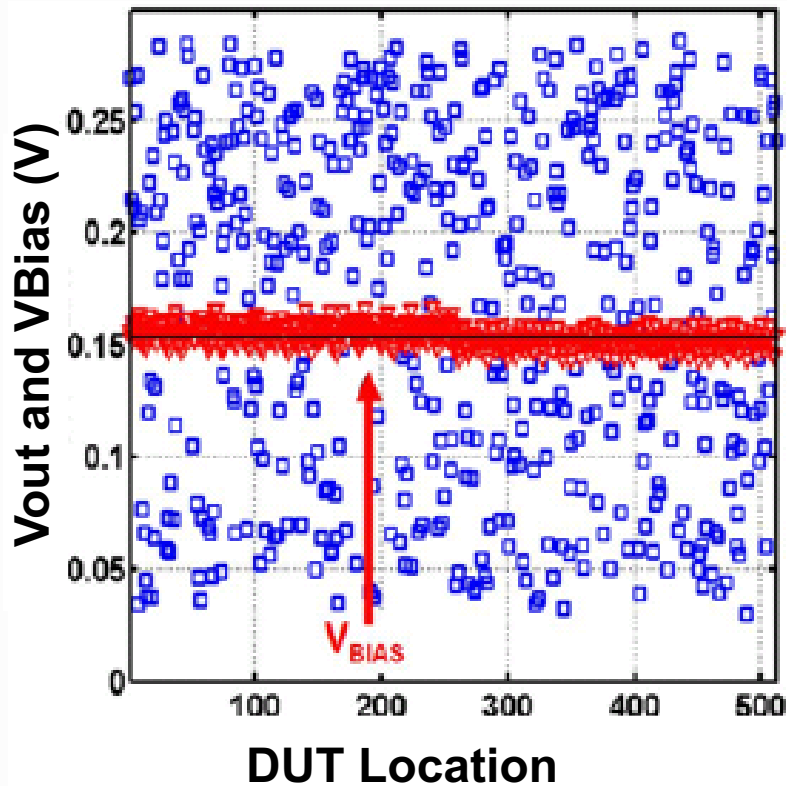

Measurement for 512 minimum sized DUTs

 


Extracted  $V_{TH}$  from measurement

# Improving Signal to Noise Ratio

□ Approaches used to improve signal to noise during measurement include


- a) Clamp gates of unselected DUTs to a negative voltage
- b) Raise the voltage applied to the selection devices
- c) Use voltage measurement instead of current measurement
- d) Use forced stacking on the selection devices

# Gate Oxide Monitor

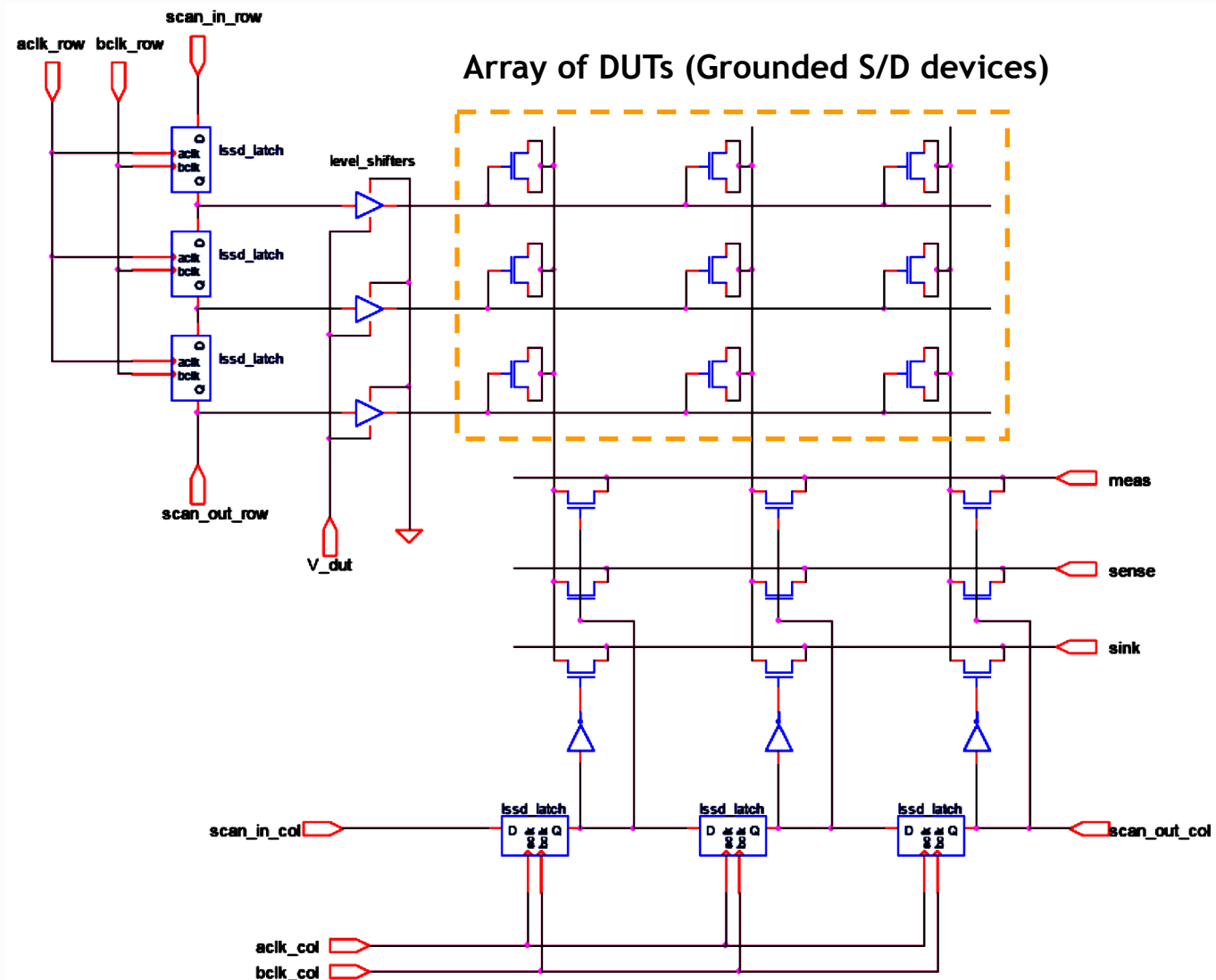


# Gate Oxide Monitor

Gate leakage variation

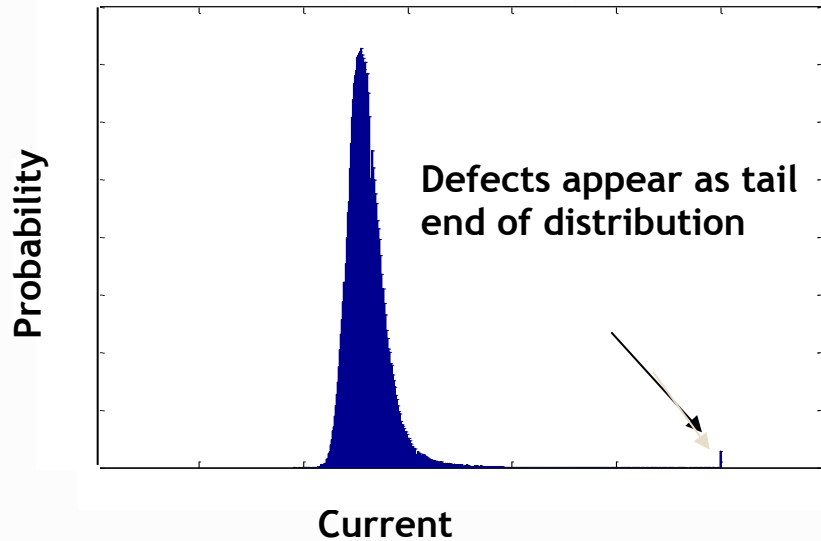


- Characterizes Gate Oxide Defects
- Millions of SRAM devices in an individually addressable array
- Measure gate leakage currents to identify defects

Rows

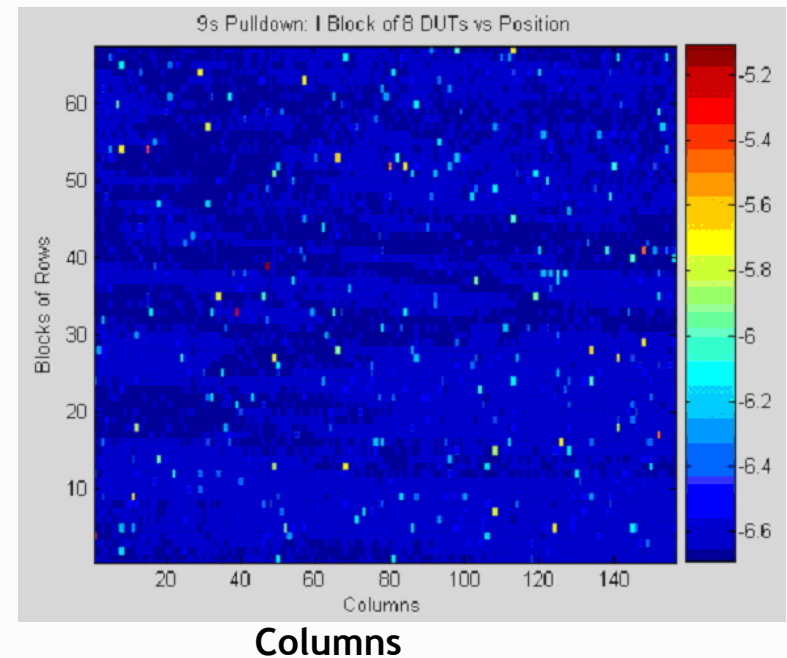

# Contact Resistance Sensor

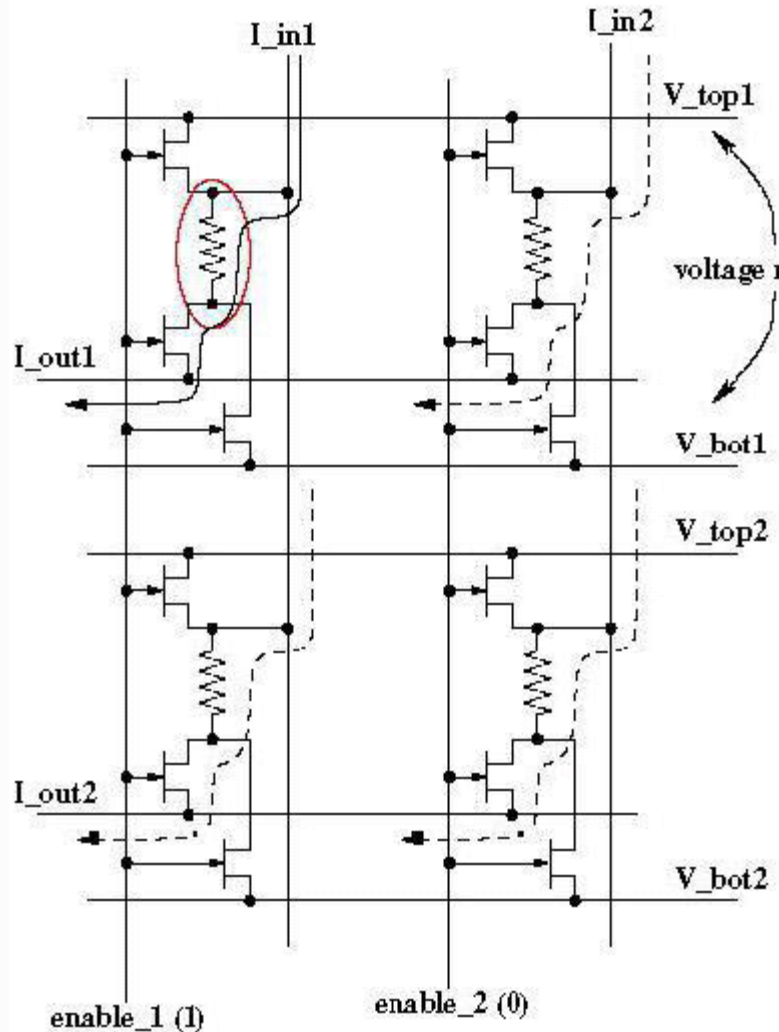



- Array of Contact cells
- Each Row has  $V_{top}(i)$ ,  $V_{bot}(i)$  and  $I_{out}(i)$
- Each column has  $I_{in}(j)$  and  $enable(j)$
- For selected DUT,  $enable(j)$  ensures that  $I_{in}(j)$  is steered to  $I_{out}(i)$
- $V_{top}(i)$  and  $V_{bot}(i)$  are sensed to estimate CA resistance
- For unselected columns, Enable is kept below 0 to reduce leakage noise



# How to characterize global or systematic variations in process ?

- Challenge
  - Sense and characterize observable circuit parameters that depend on process parameters
- Methods
  - Delay based sensing
  - Slew based sensing
  - Leakage based sensing

# Ring Oscillator Structures

 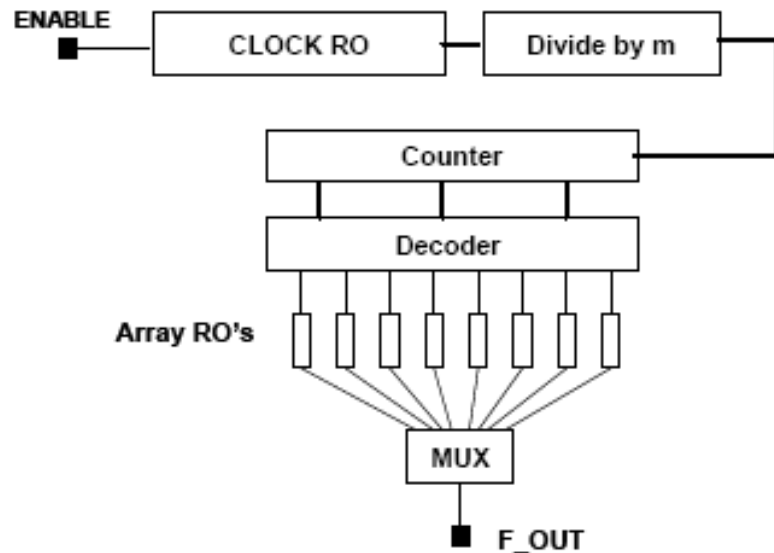


## Modified Ring Oscillator


Oscillators of different gate lengths by tapping multiple nodes
 
## Ring Oscillator (RO)

- FET to FET variation averaged out with large number of stages
- Multiple ROs selected through a finite state machine (or counter)
- Frequency is independent of downstream delay of the multiplexer




# Delay Variation of a Ring Oscillator

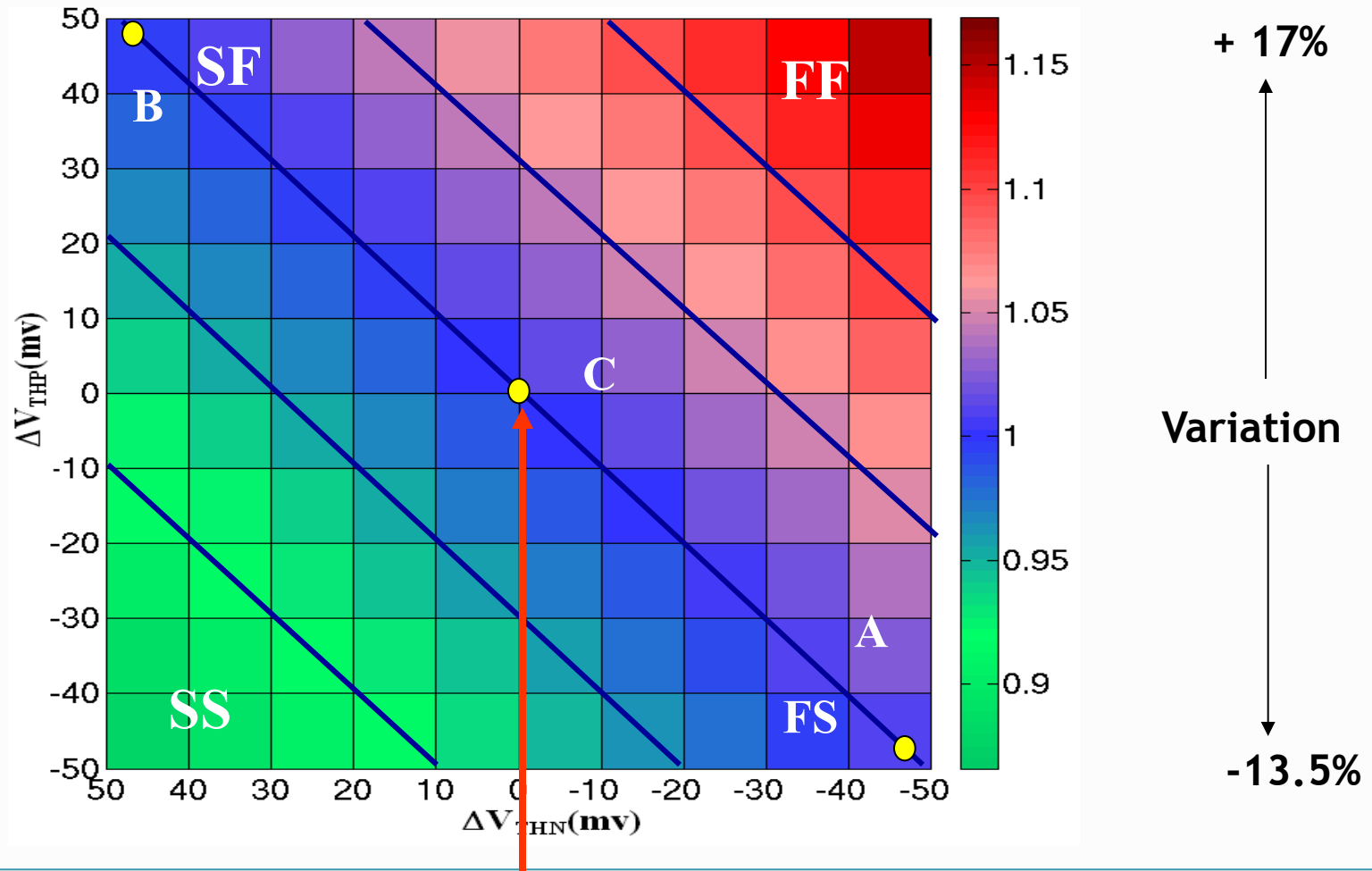

Nominal operating point of the circuit with no threshold voltage variation

Delay is good for detection of Slow-Slow and Slow-Fast Corners


# Normalized Slew

 

Slew is more sensitive to mismatch in device strengths  
 Good for detection of Slow-Fast and Fast-Slow Corners

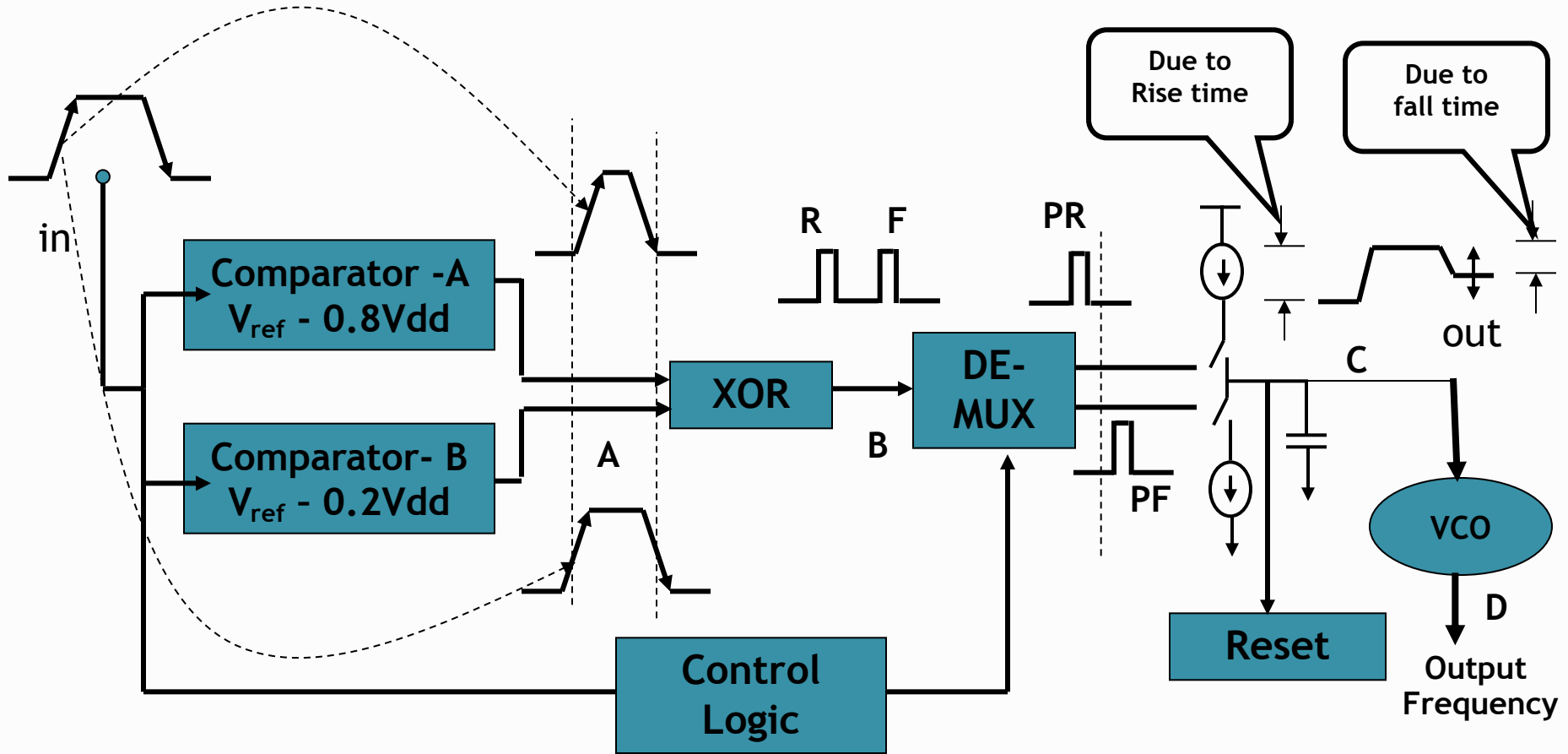
# Slew Monitor

$\Delta_{\text{rise-fall}}$  - the relative mismatch between the strength of the NMOS and PMOS devices





Can be used to drive body bias compensation for NMOS and PMOS devices for leakage control
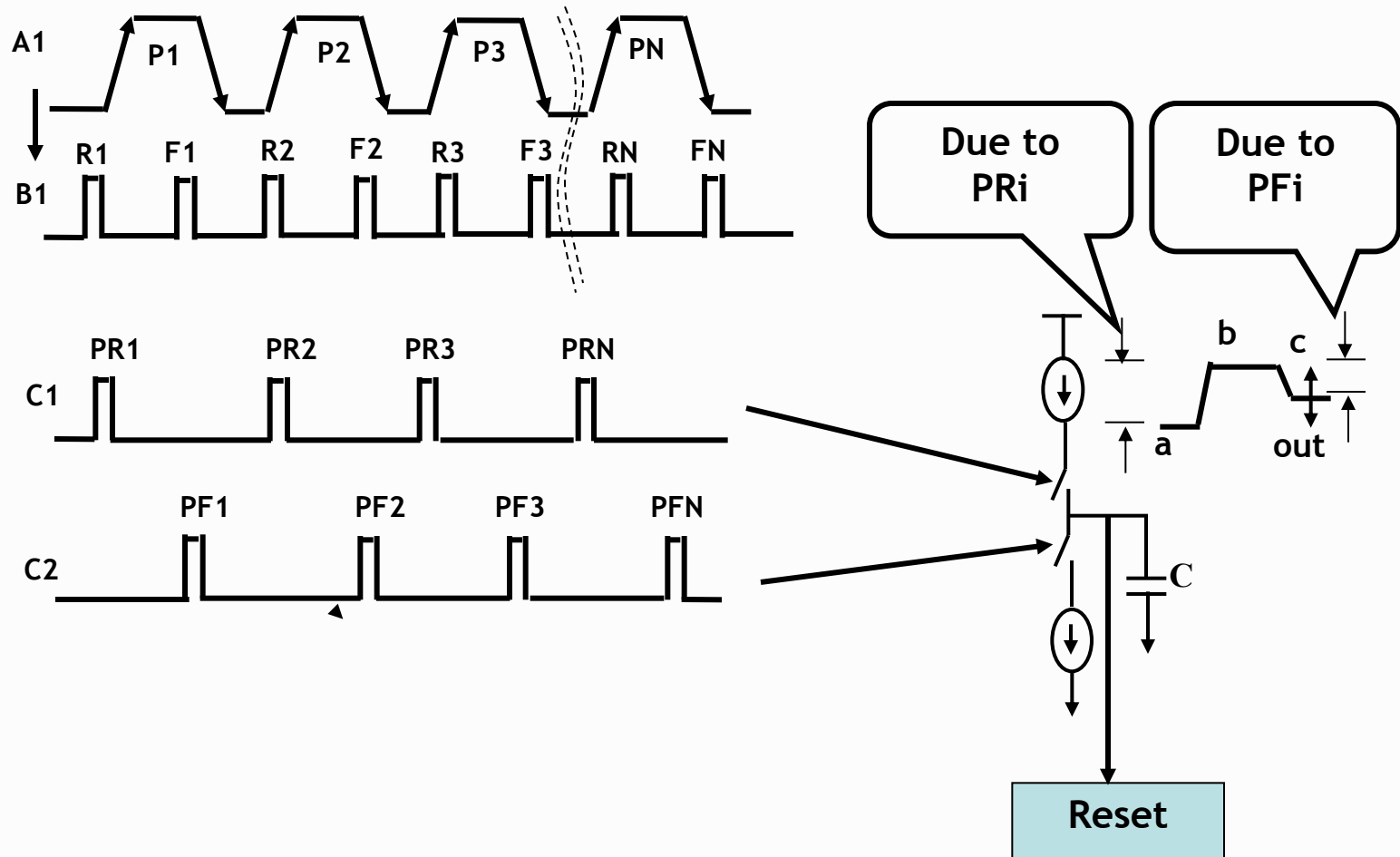
# Using Multiple Pulses to Improve Sensitivity




# Leakage Detection Circuit

 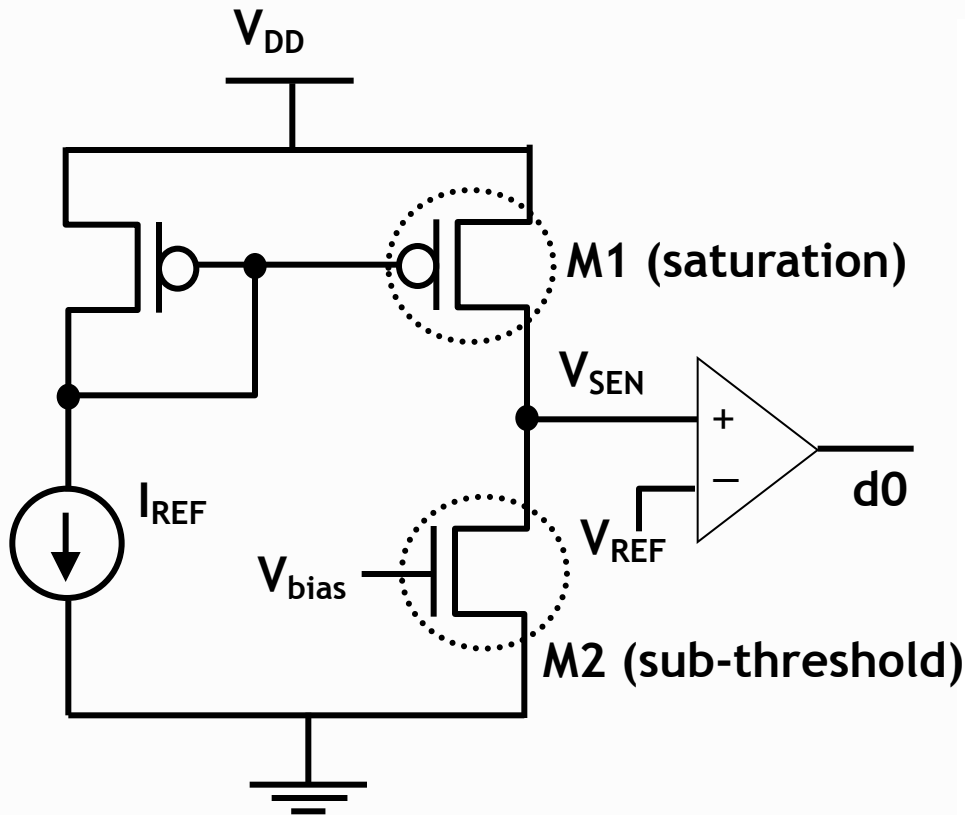

- **Sense the current of a transistor in sub-threshold**
  - Intersection of the two curves represents the voltage output
  - **Generate PVT tolerant  $I_{REF}$  and  $V_{bias}$**

# Multi-Channel Leakage Sensor

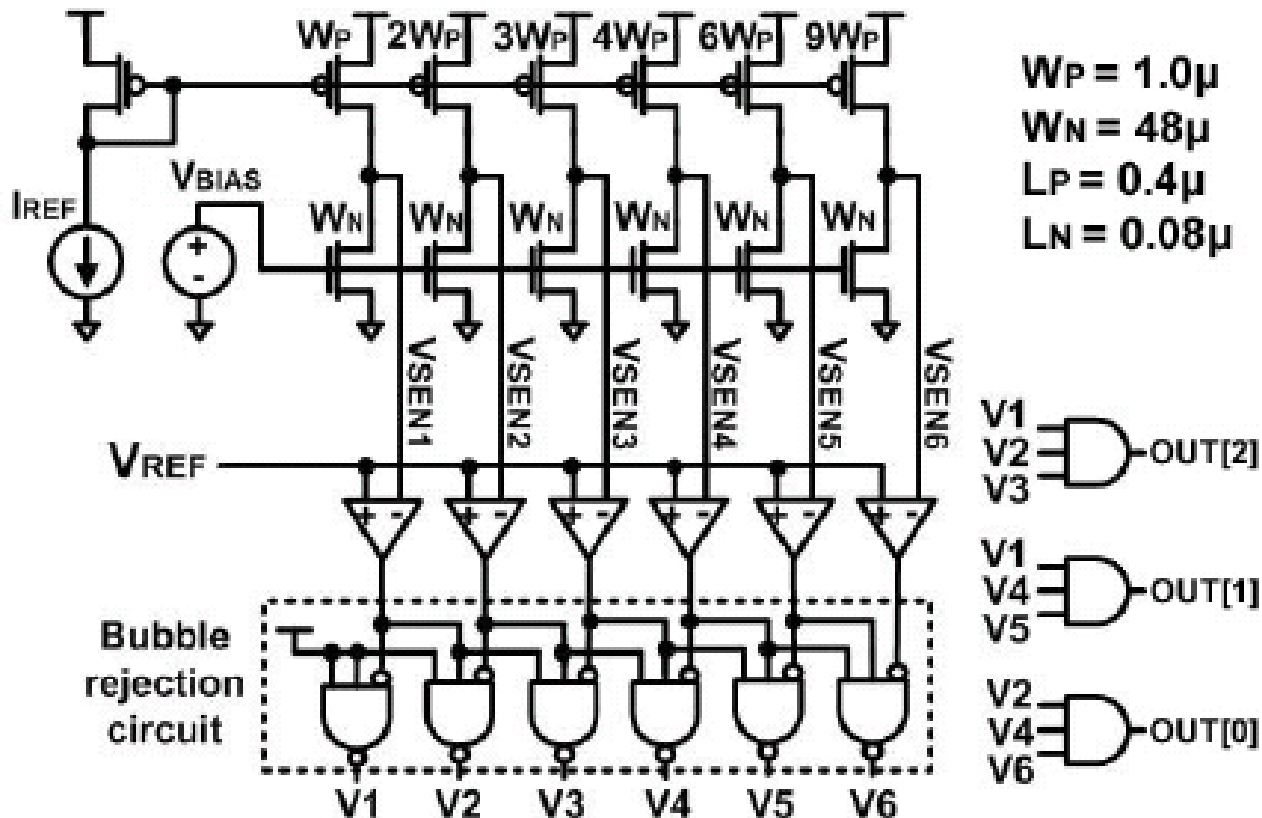


- Use PMOS devices of different widths to obtain multiple channel leakage sensor
  - Digital signature of analog leakage variation



# Improving Signal to Noise Ratio

- An oscillator with large number of stages
  - a) Helps differentiate variation by device type
  - b) Averages out the effect of local variation
  - c) Requires fewer division stages before readout
  - d) Shouldn't be used for a VCO operation

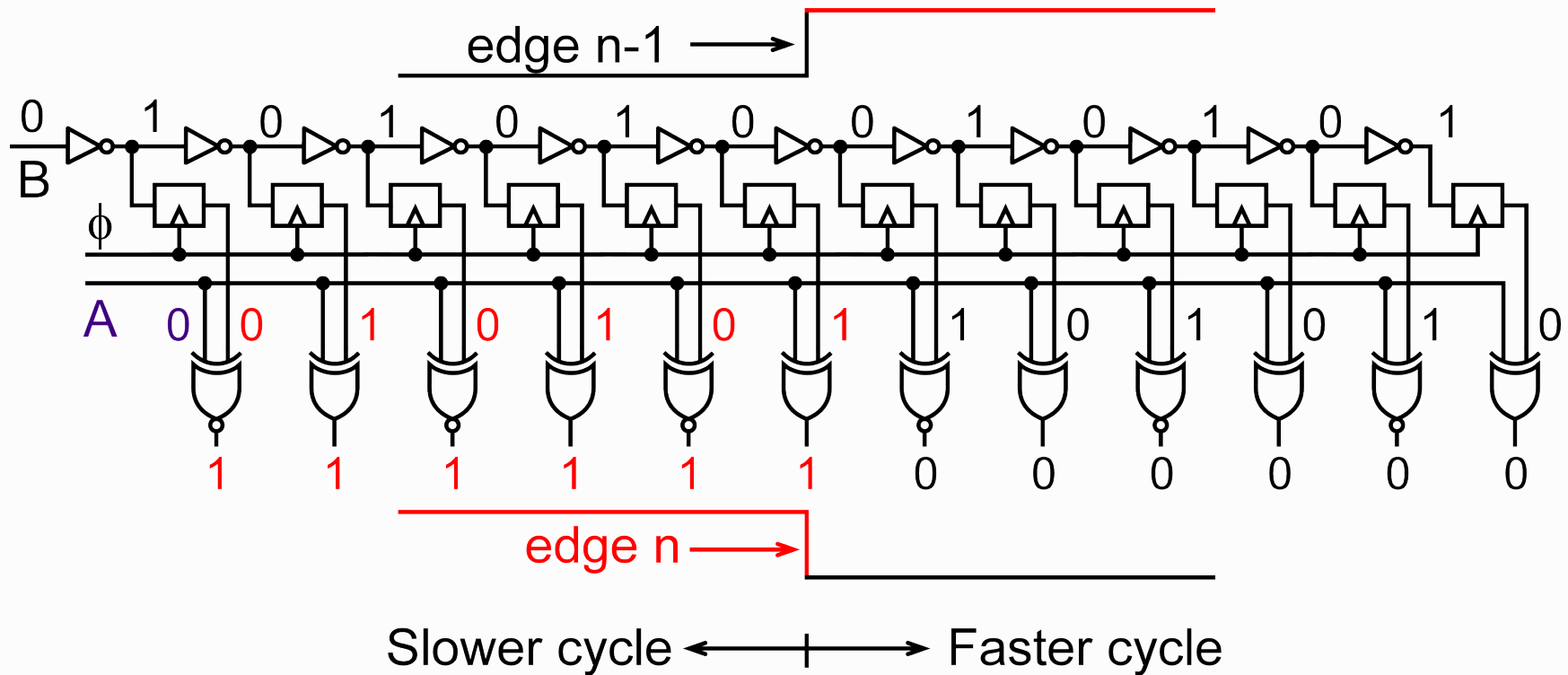
# Time-to-Digital Conversion Using an Edge Detector



- Edge movement due to
  - Changes in clock cycle
  - Changes in path delay
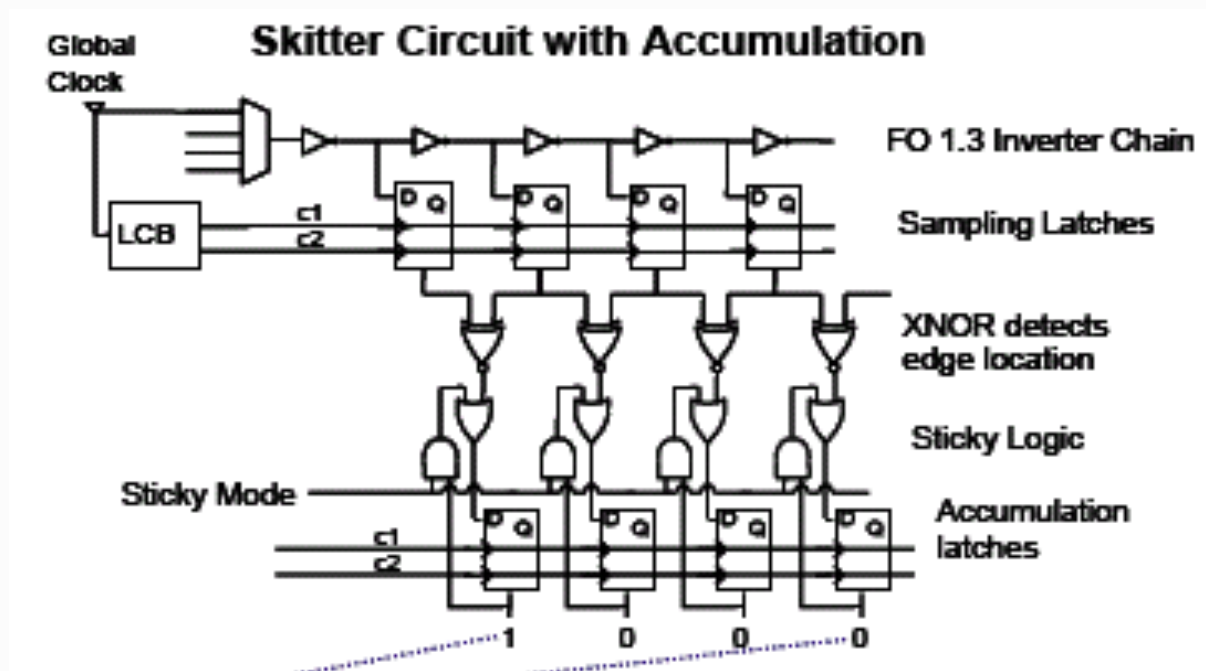
# Skitter (Skew + Jitter) Circuit

- Measure timing uncertainties from all sources
- Track skew between different regions (also environmental effects)
- During debug, detect supply voltage droops, detect failure mechanism
- Complete digital readout through scan-chains
- Cycle-Cycle variation, Best-Worst case detection



# Skitter (Skew + jITTER) Circuit

