

# Course Objectives

- ❑ Introduce students to some relevant advanced topics of current interest in academia and industry
- ❑ Give the students a feel for research topics and what research means
- ❑ **Make students aware of work happening in India**

# Current Topics

- ❑ Embedded Memory Design
  - ❑ SRAMs (Dr. Rahul Rao, IBM India)
  - ❑ eDRAMs ( Dr. Janakriaman, IITM)
  - ❑ Advanced Memories

# Learning Objectives for SRAM

- ❑ Articulate memory hierarchy and the value proposition of SRAMs in the memory chain + utilization in current processors
- ❑ Explain SRAM building blocks and peripheral operations and memory architecture (with physical arrangement)
- ❑ Articulate commonly used SRAM cells (6T vs 8T), their advantages and disadvantages
- ❑ Explain the operation of a non-conventional SRAM cells, and their limitations
- ❑ Explain commonly used assist methods
- ❑ Explain how variations impact memory cells

# Learning Objectives for EDRAM

- ❑ Explain the working of a (e)DRAM. What does Embedded mean?
- ❑ Explain the working of a feedback sense amplifier and modify existing designs to improve performance
- ❑ Calculate the voltage levels of operation of various components for an eDRAM
- ❑ Introduce stacked protect devices to reduce voltage stress of the WL driver



# Grading

- ❑ Assignments - 10%
- ❑ Midsem – 30%
- ❑ Project - 20%
- ❑ End Semester - 40%

# Course Schedule

☐ Friday – 2:00 –5:00

☐ ESB 207A

# Embedded DRAM

**Janakiraman V**

Assistant Professor  
Electrical Department  
IIT Madras

# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example
- ❑ Gated Feedback Sense Amplifier (case study)
- ❑ References


# Acknowledgement

- Raviprasad Kuloor (Course slides were prepared by him)
- John Barth, IBM SRDC for most of the slides content
- Madabusi Govindarajan
- Subramanian S. Iyer
- Many Others

# Topics

- Introduction to memory
- DRAM basics and bitcell array
- eDRAM operational details (case study)
- Noise concerns
- Wordline driver (WLDRV) and level translators (LT)
- Challenges in eDRAM
- Understanding Timing diagram - An example

# Memory Classification revisited

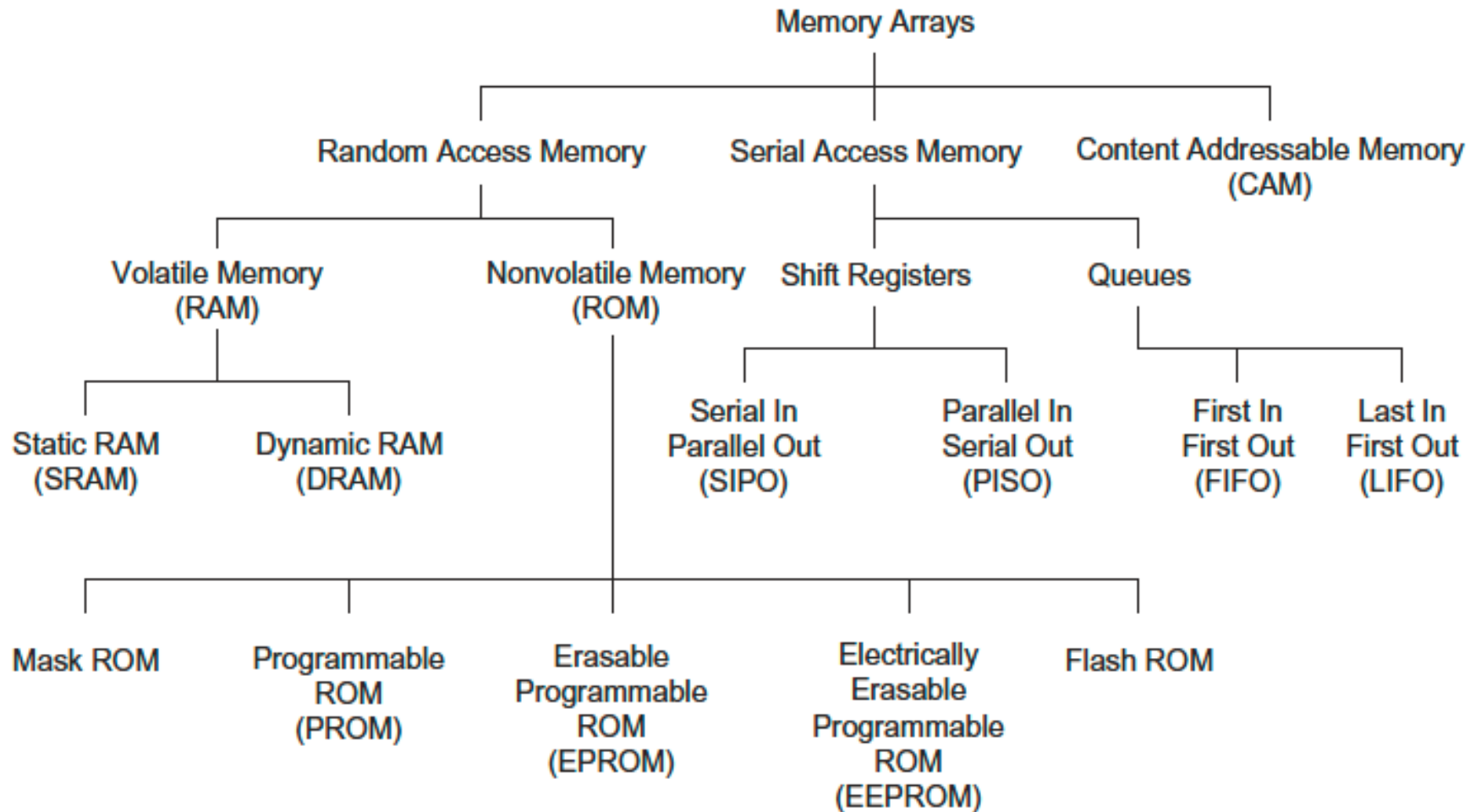

# Motivation for a memory hierarchy - infinite memory



Cycles per Instruction  
(CPI)

=

Number of processor clock cycles  
required per instruction

$CPI[\infty \text{ cache}]$



# Finite memory speed



$$\text{CPI} = \text{CPI}[\infty \text{ cache}] + \text{FCP}$$

Finite cache penalty

# Locality of reference - spatial and temporal

## Temporal

If you access something now you'll need it again soon


*e.g: Loops*

## Spatial

If you accessed something you'll also need its neighbor

*e.g: Arrays*

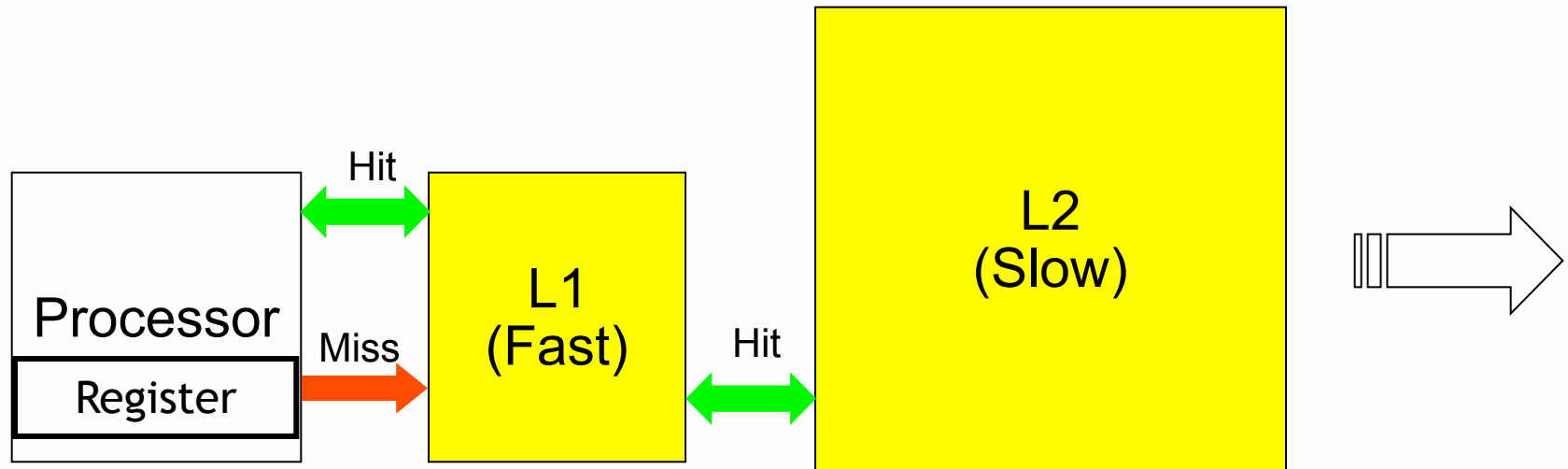*Exploit this to divide memory into hierarchy*




# Cache size impacts cycles-per-instruction

Logic-based  
eDRAM: Origins  
and rationale  
for use

R. E. Matick  
S. E. Schuster

 IBM J. RES. & DEV. VOL. 49 NO. 1 JANUARY 2005



No. of L2 hits per instruction  
 $mr_1 - mr_2$


No. of L3 hits per instruction  
 $mr_2 - mr_3$

No. of L4 hits per instruction  
 $mr_3 - mr_4$

Finite cache penalty	=	Delay / I for L2 hits	+	Delay / I for L3 hits	+	Delay / I for L4 hits ...
FCP	=	$(mr_1 - mr_2) T_2$	+	$(mr_2 - mr_3) T_3$	+	$(mr_3 - mr_4) T_4 + \dots$
Cycles per instruction	=	Hits per instruction × cycles per hit				

—————→ Access rate reduces → Slower memory is sufficient

 
# Cache size impacts cycles-per-instruction



Speed	1ns	10ns	100ns	10ms	10sec
Size	B	KB	MB	GB	TB


For a 5GHz processor, scale the numbers by 5x
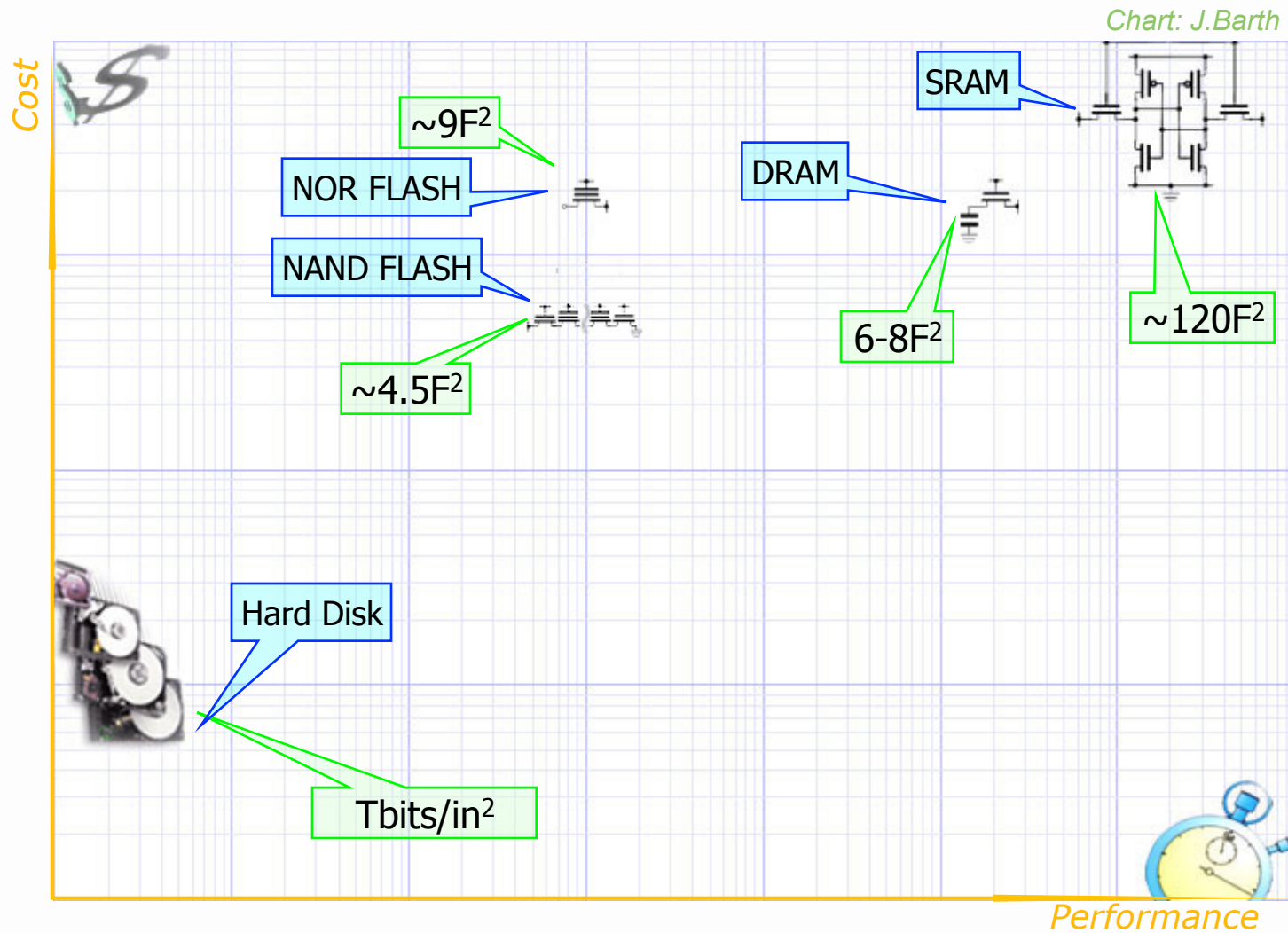
# Technology choices for memory hierarchy



# eDRAM L3 cache

Power7  
processor

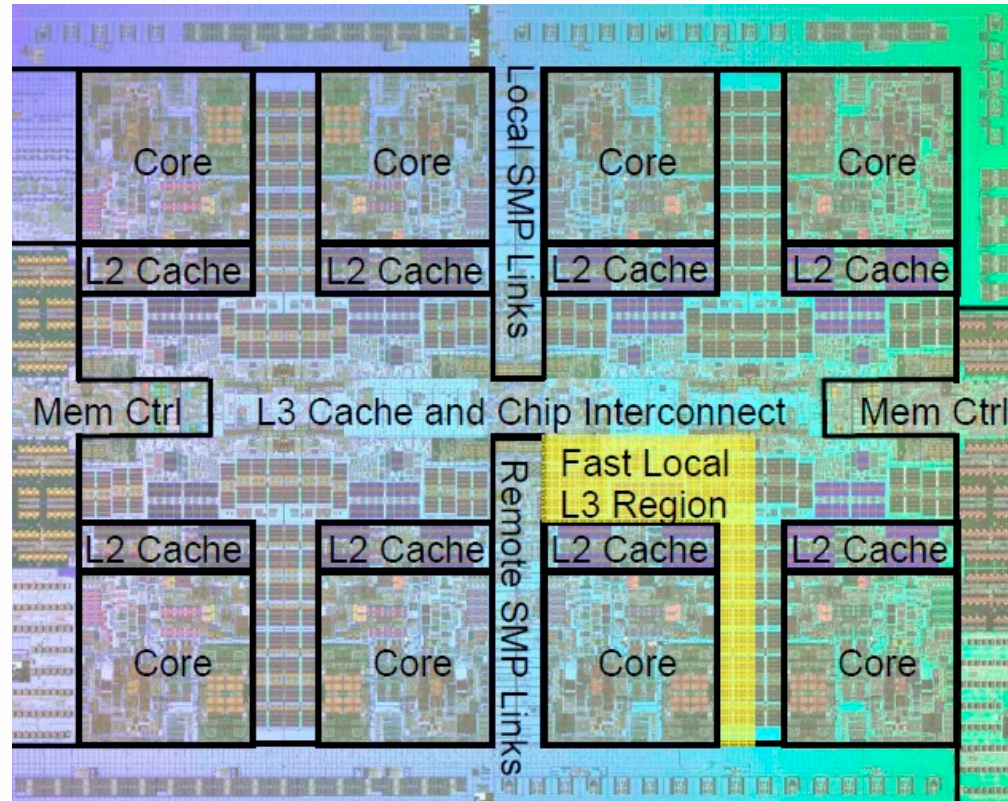

Move L2,L3 Cache inside of the data hungry processor

Higher hit rate → Reduced FCP

# Embedded DRAM Advantages



## Memory Advantage

- 2x Cache can provide > 10% Performance
- ~3x Density Advantage over eSRAM
- 1/5x Standby Power Compared to SRAM
- Soft Error Rate 1000x lower than SRAM
- Performance ? DRAM can have lower latency !
- IO Power reduction


## Deep Trench Capacitor

- Low Leakage Decoupling
- 25x more Cap /  $\mu\text{m}^2$  compared to planar
- Noise Reduction = Performance Improvement
- Isolated Plate enables High Density Charge Pump

IBM Power7<sup>tm</sup>  
32MB eDRAM L3

 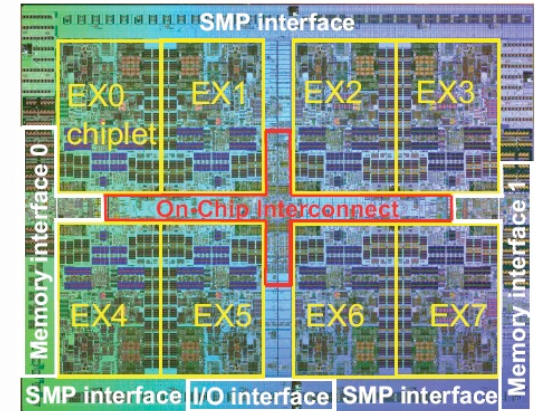


# eDRAM Advantages – Stand By Leakage

 




# eDRAM Advantages – Stand By Leakage

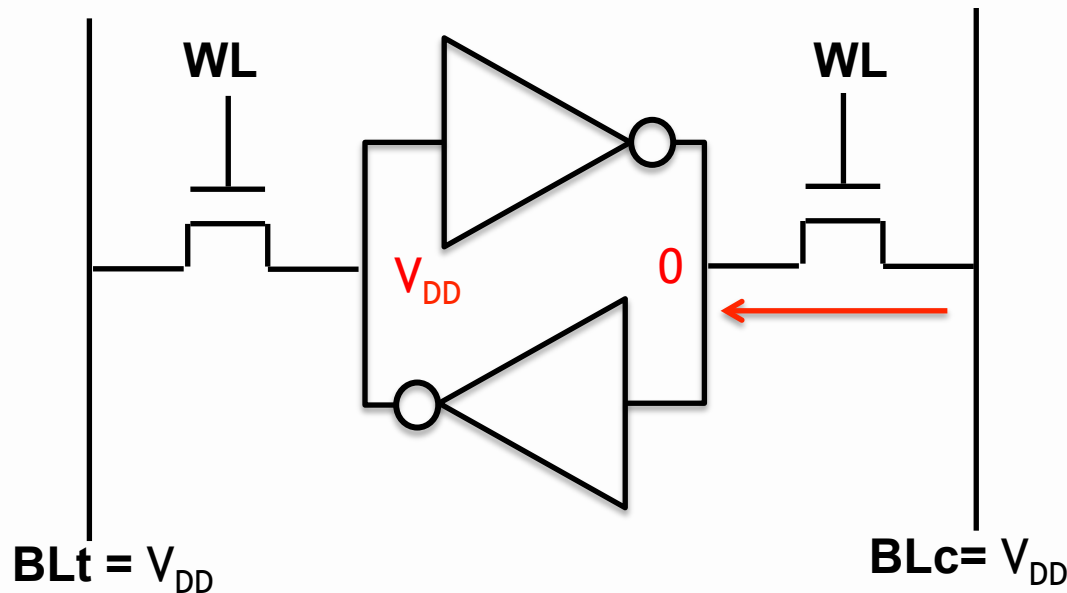


 Both inverters leak  
Complement Pass transistor leaks




Leakage exists

# eDRAM Advantages – Stand By Leakage

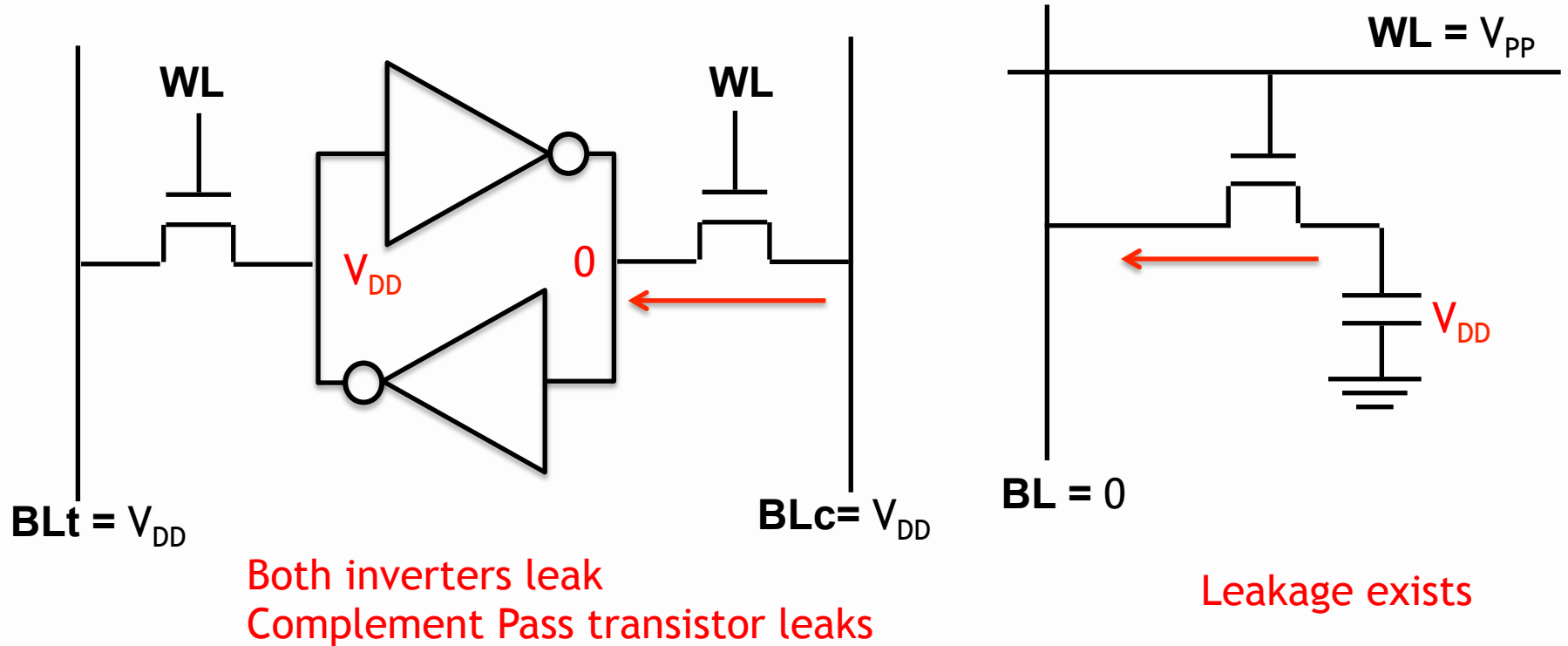


On average: eDRAMs have 1/5x Standby Power Compared to SRAM

# eDRAM Advantages – Performance

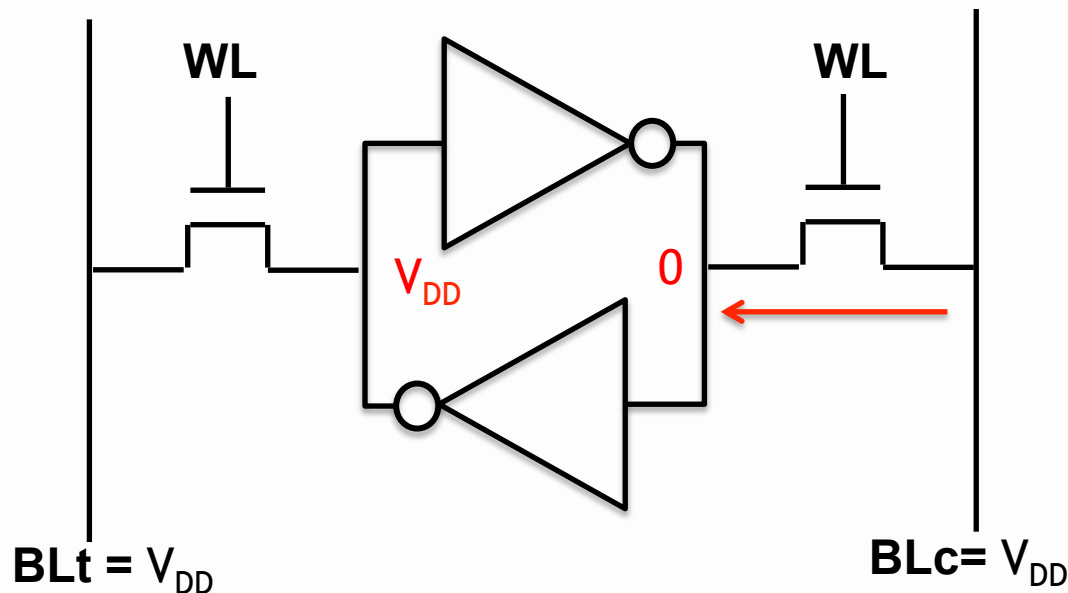


 Both inverters leak  
Complement Pass transistor leaks



Leakage exists

# eDRAM Advantages – Soft Error Rate

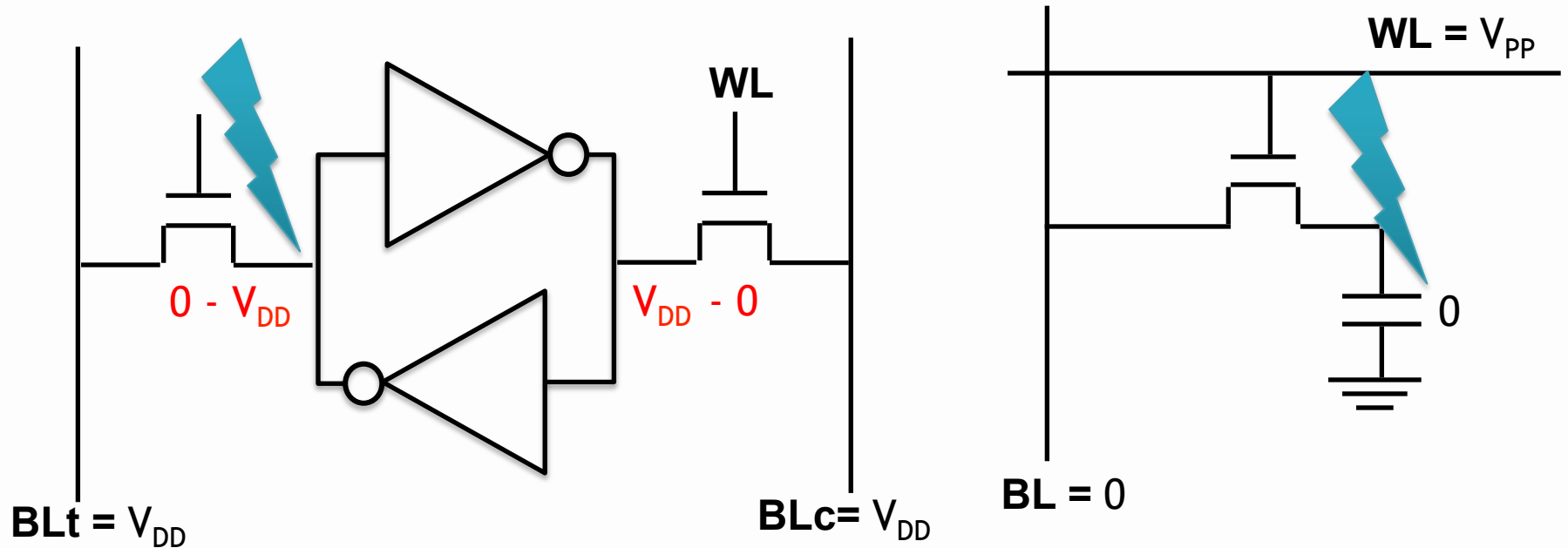



- Cosmic particles can bombard the cell and cause a bump in the cell voltage
- If voltage bump is large enough SRAM can permanently flip
  - Static cross couple inverters
- Voltage on DRAM capacitor node can also bump
- But will leak away with time –
  - Only those cells which get refreshed in a certain period will flip
- **Soft Error Rate 1000x lower than SRAM**

# Embedded DRAM Advantages

## Deep Trench Capacitor

- Low Leakage Decoupling
- 25x more Cap /  $\mu\text{m}^2$  compared to planar
- Noise Reduction = Performance Improvement
- Isolated Plate enables High Density Charge Pump

IBM Power7<sup>tm</sup>  
32MB eDRAM L3

  

# Embedded DRAM Advantages



## Memory Advantage

- 2x Cache can provide > 10% Performance
- ~3x Density Advantage over eSRAM
- 1/5x Standby Power Compared to SRAM
- Soft Error Rate 1000x lower than SRAM
- Performance ? DRAM can have lower latency !
- IO Power reduction

## Deep Trench Capacitor


- Low Leakage Decoupling
- 25x more Cap /  $\mu\text{m}^2$  compared to planar
- Noise Reduction = Performance Improvement
- Isolated Plate enables High Density Charge Pump

IBM Power7<sup>tm</sup>  
32MB eDRAM L3

 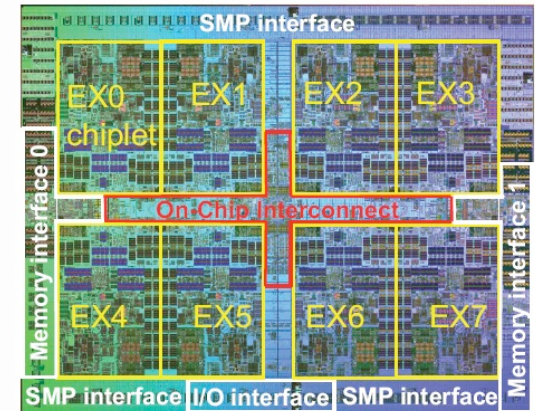


# Cache performance - SRAM vs. DRAM

*Chart: Matick & Schuster, op. cit.*

 

# Cache performance - SRAM vs. DRAM

 


Time to access the farthest word-line determines performance  
Access time = Cell access time + time of flight interconnect delay



# Embedded DRAM Performance

45nm eDRAM vs. SRAM Latency

eDRAM Faster than SRAM

 

Memory Block Size Built With 1Mb Macros

Barth ISSCC 2011

# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM Write Analysis
- ❑ eDRAM Sense-Amplifier Specification
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example

# Fundamental DRAM Operation


Memory Arrays are composed of Row and Columns

Most DRAMs use 1 Transistor as a switch and  
1 Cap as a storage element (Dennard 1967)



Single Cell Accessed by Decoding One Row / One Column (Matrix)

Row (Word-Line) connects storage Caps to Columns (Bit-Line)

 Storage Cap Transfers Charge to Bit-Line, Altering Bit-Line Voltage



# 1T1C DRAM Cell Terminals

  


**VWL:** Word-Line Low Supply, GND or Negative for improved leakage

**VPP:** Word-Line High Supply, 1.8V up to 3.5V depending on Technology  
Required to be at least a  $V_t$  above VDD to write full VDD


**VBB:** Back Bias, Typically Negative to improve Leakage  
Not practical on SOI
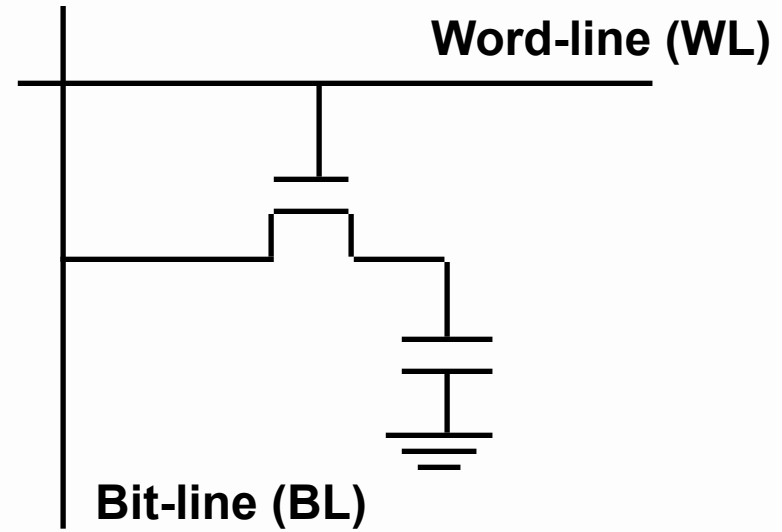
# Choice of Access Transistor


- DRAMs are limited by sub-threshold leakage
  - $I_{\text{off}} \propto 1/t_{\text{ox}}$
  - Use thick oxide transistor
    - $t_{\text{ox}} \approx 3\text{nm}$  in 14nm Technology
    - Thin oxide transistors ( $t_{\text{ox}} \approx 1\text{nm}$ )
  - What should be the width of the device?
    - Density constraints => Unit size
  - Unit size transistor also provides least leakage



# MIM Cap v/s Trench

 

**MIM eDRAM Process**

 


**Trench eDRAM Process**



- Stack capacitor requires more complex process
- M1 height above gate is increased with stacked capacitor
  - M1 parasitics significantly change when wafer is processed w/o eDRAM
  - Drives unique timings for circuit blocks processed w/ and w/o eDRAM
    - Logic Equivalency is compromised – **Trench is Better Choice**

 
# Word-line Swing - High

- WL High Voltage – ON State
  - Technology maximum high voltage?
    - Access device is thick oxide
    - Can handle a swing of more than  $V_{DD}$ .
  - How high?
    - We wish to write a logic-1 completely
    - Logic-1 =  $V_{DD}$
    - Access device is an NMOS transistor
      - Cannot pass  $V_{DD}$  fully if  $WL = V_{DD}$
    - WL high =  $V_{PP} \geq V_{DD} + V_{Tn}$
    - What about  $V_{Tn}$  variability
    - $V_{PP} \geq V_{DD} + V_{Tn} + \Delta V_{Tn}$
- Typical value of  $V_{PP} = 0.9 + 0.4 + 0.2 = 1.5V$


 
# Word-line Swing - Low


- WL Low Voltage ( $V_{WL}$ ) – OFF State
- BL will be pre-charged to either 0 or  $V_{DD}$ 
  - BL pre-charged to 0
    - Cell storing a 1 causes leakage
  - BL pre-charged to 1
    - Cell storing a 0 causes leakage
- Need to minimize leakage current either way
- $V_{GS}$  of access device needs to be as low as possible
  - IOFF decreases exponentially with  $V_{GS}$
  - Can we lower the WL down to  $-V_{DD}$ ?
  - What is the limit?
  - Lower the WL voltage down to the point where GIDL – Gate Induced Drain Leakage sets in
  - Typical value of  $V_{WL} = -300$  mV





 
# DRAM cell Cross section



- Store their contents as charge on a capacitor rather than in a feedback loop.
- 1T dynamic RAM cell has a transistor and a capacitor



CMOS VLSI design - PEARSON

 


# Storing data '1' in the cell

  

$V_{gs}$  for pass transistor reduces as bitcell voltage rises, increasing  $R_{on}$

Why there is a reduction in cell voltage after WL closes? Experiment

# Classical DRAM Organization

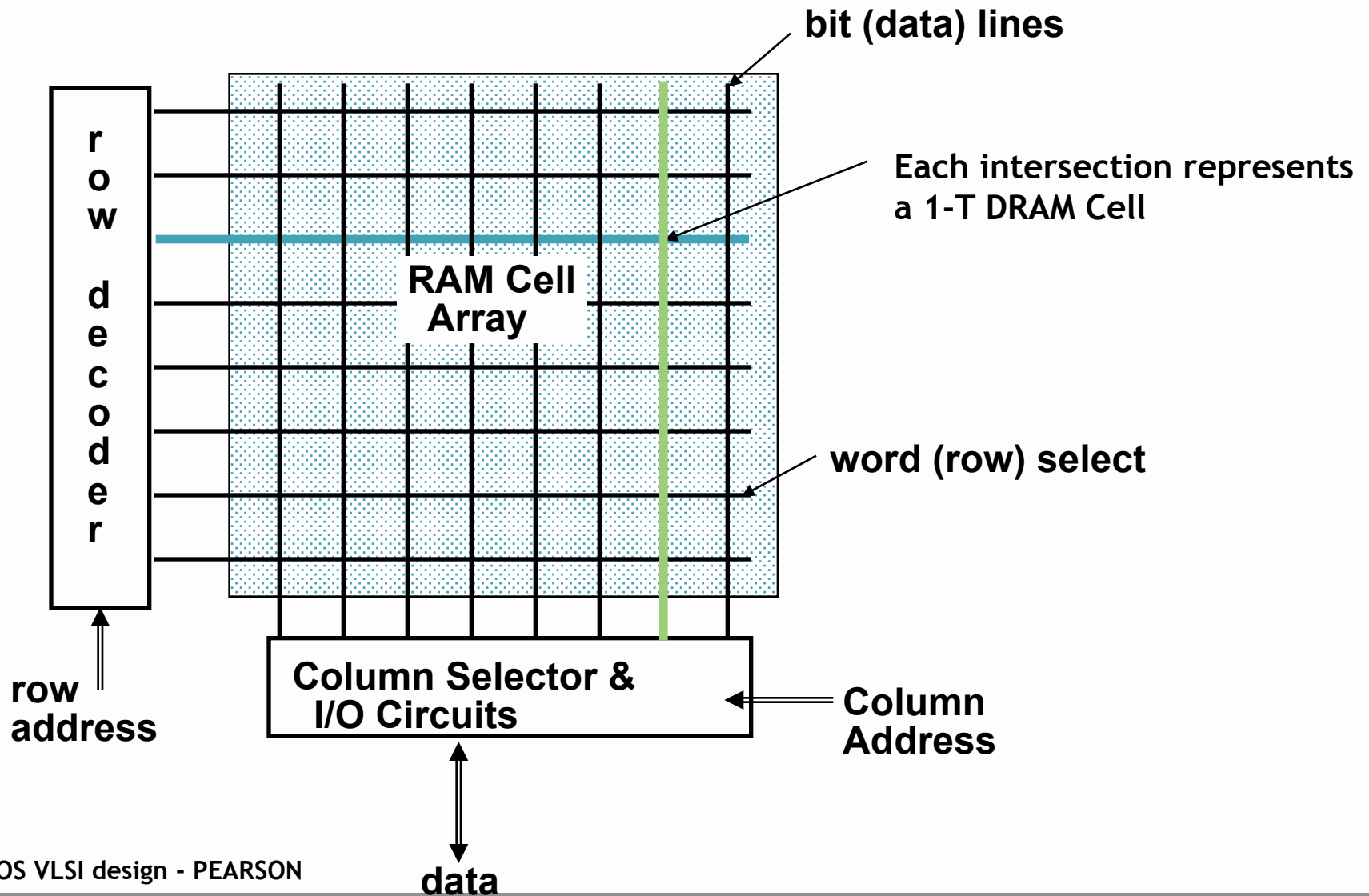

# DRAM Subarray


 


FIGURE 12.43 DRAM subarray

# Trench cell layout and cross-section

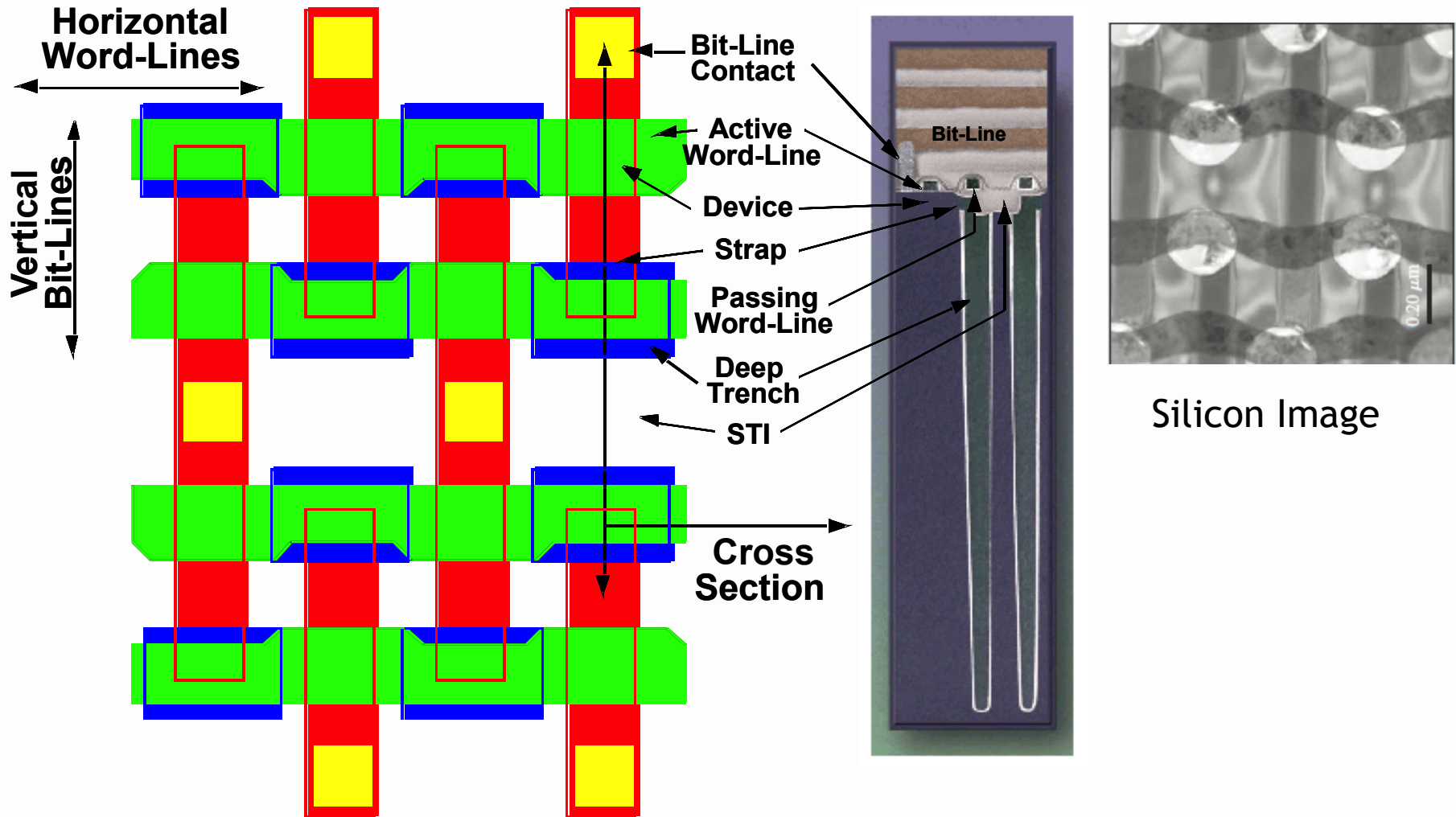

# References so far

Barth, J. et al., “A 300MHz Multi-Banked eDRAM Macro Featuring GND Sense, Bit-line Twisting and Direct Reference Cell Write,” ISSCC Dig. Tech. Papers, pp. 156-157, Feb. 2002.

Barth, J. et. al., “A 500MHz Multi-Banked Compilable DRAM Macro with Direct Write and Programmable Pipeline,” ISSCC Dig. Tech. Papers, pp. 204-205, Feb. 2004.

Barth, J. et al., “A 500MHz Random Cycle 1.5ns-Latency, SOI Embedded DRAM Macro Featuring a 3T Micro Sense Amplifier,” ISSCC Dig. Tech. Papers, pp. 486-487, Feb. 2007.


Barth, J. et al., “A 45nm SOI Embedded DRAM Macro for POWER7™ 32MB On-Chip L3 Cache,” ISSCC Dig. Tech. Papers, pp. 342-3, Feb. 2010.

Butt, N., et al., “A 0.039 $\mu$ m<sup>2</sup> High Performance eDRAM Cell based on 32nm High-K/Metal SOI Technology,” IEDM pp. 27.5.1-2, Dec 2010.

Bright, A. et al., “Creating the BlueGene/L Supercomputer from Low-Power SoC ASICs,” ISSCC Dig. Tech. Papers, pp. 188-189, Feb. 2005.


# DRAM Operations

- Write
- Read
- Refresh

 
 
# DRAM Read, Write and Refresh


- Write:
  - 1. Drive bit line
  - 2. Select row





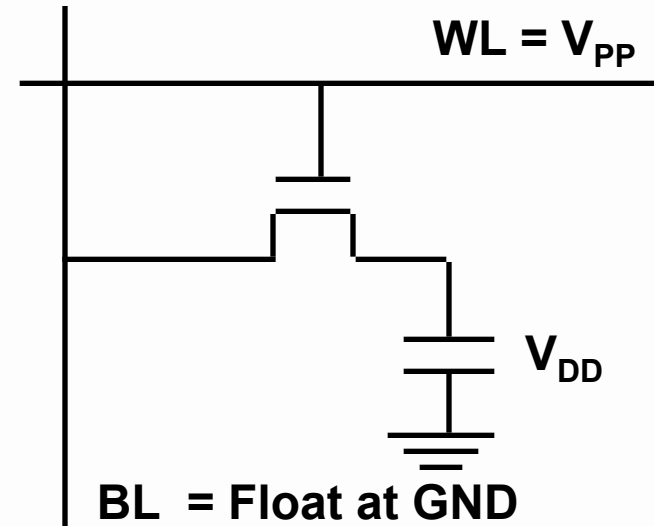
# DRAM Read, Write and Refresh

- Read:
  - 1. Pre-charge bit line
  - 2. Select row – Turn ON WL
  - 3. Cell and bit line share charges
    - Signal developed on bitline
  - 4. Sense the data
  - 5. **Write back: restore the value**





# DRAM Read, Write and Refresh

 

- Refresh
  - 1. Just do a dummy read to every cell → auto write-back


# Read - Cell transfer ratio

 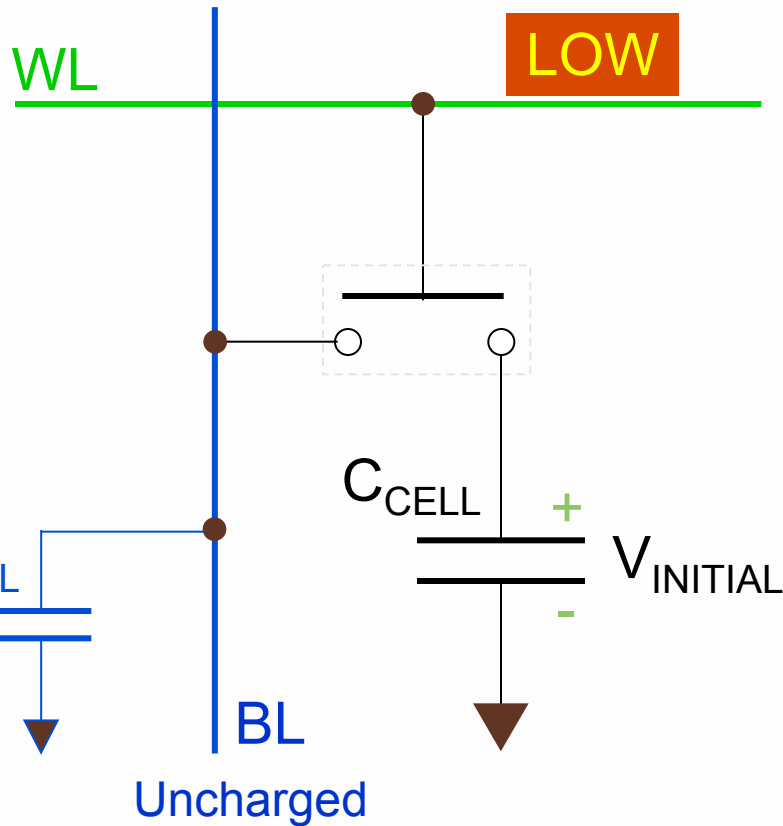


$$C_{CELL} \times V_{INITIAL} = (C_{CELL} + C_{BL}) \times V_{FINAL}$$

$$\text{Transfer ratio} = C_{CELL} / (C_{CELL} + C_{BL})$$


# Cell Charge Transfer

 

# Sensing

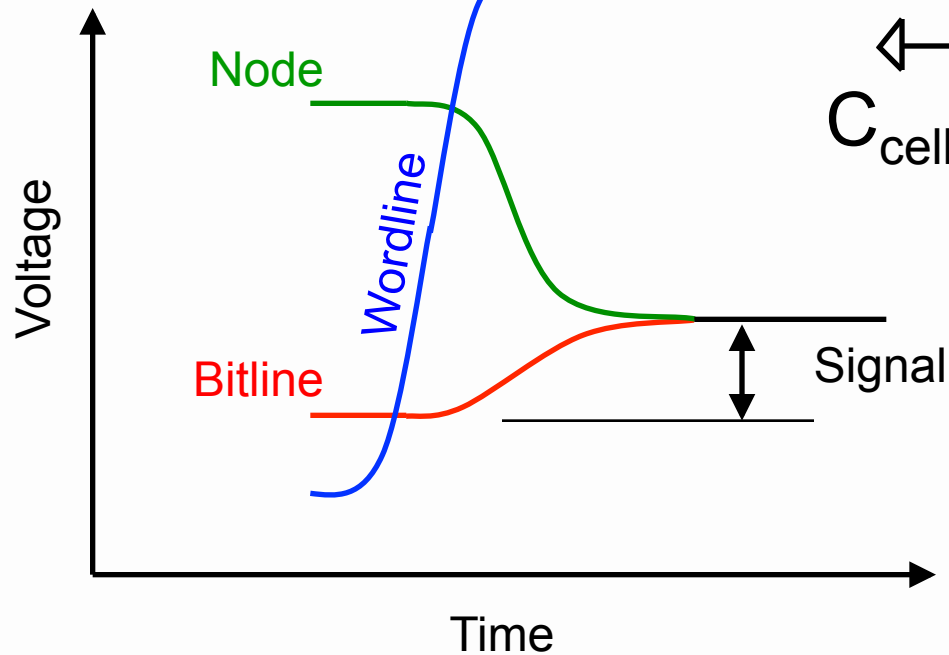

Signal  $\Delta V > V_M$  (Trip Point)


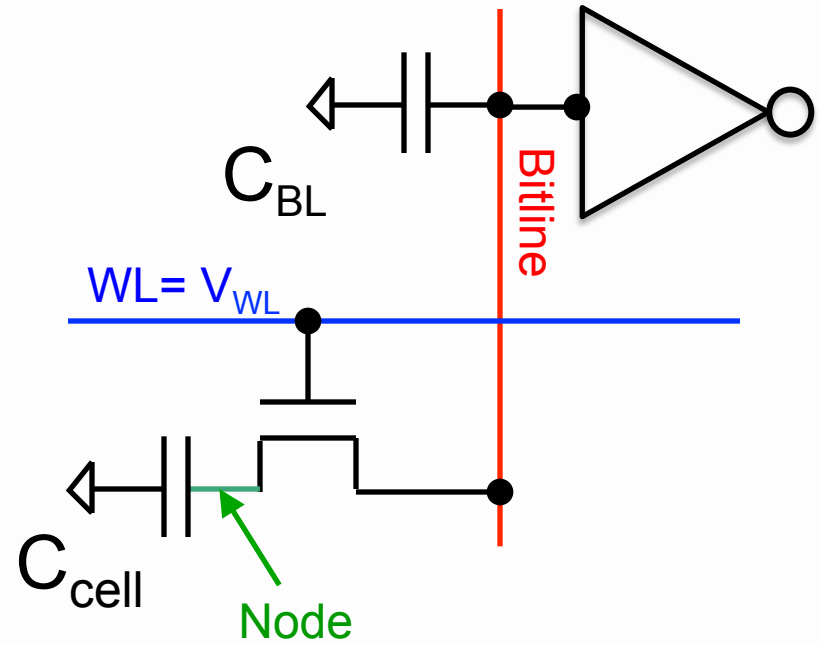


$$\Delta V = (V_{bl} - V_{cell}) \left[ \frac{C_{cell}}{C_{bl} + C_{cell}} \right]$$

Transfer ratio

# Retention

Signal  $\Delta V > V_M$  (Trip Point)

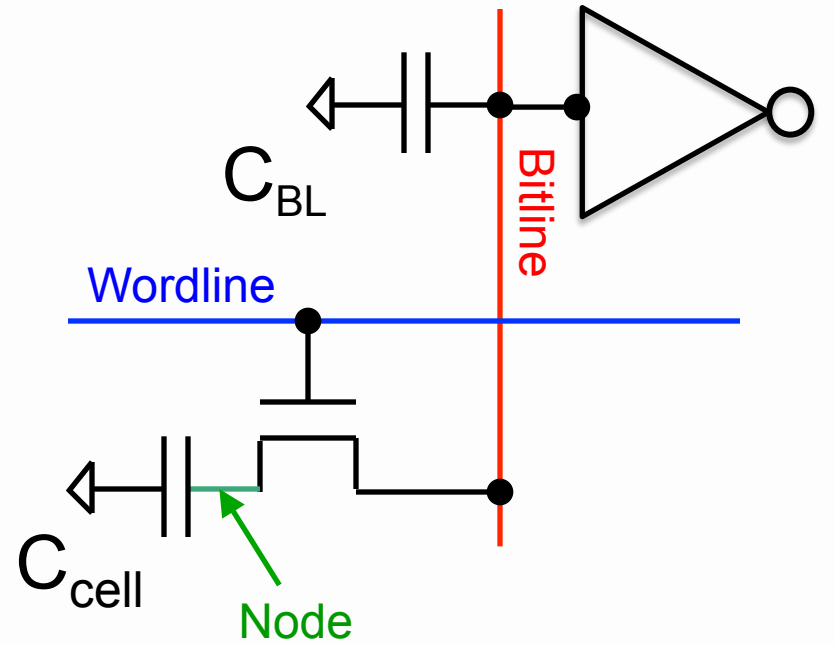 

$$\Delta V = (V_{bl} - V_{cell}) \left[ \frac{C_{cell}}{C_{bl} + C_{cell}} \right]$$

Transfer ratio

# Transfer Ratio and Signal

**ΔBit-Line Voltage Calculated from Initial Conditions and Capacitances:**

$$\Delta V = V_{bl} - V_f = V_{bl} - \frac{Q}{C} = V_{bl} - \left[ \frac{C_{bl} * V_{bl} + C_{cell} * V_{cell}}{C_{bl} + C_{cell}} \right]$$

$$\Delta V = (V_{bl} - V_{cell}) \left[ \frac{C_{cell}}{C_{bl} + C_{cell}} \right]$$

↙ Transfer Ratio (typically 0.2)

**ΔBit-Line Voltage is Amplified with Cross Couple “Sense Amp”**

**Sense Amp Compares Bit-Line Voltage with a Reference**


**Bit-Line Voltage - Reference = Signal**

**Pos Signal Amplifies to Logical ‘1’, Neg Signal Amplifies to Logical ‘0’**


# Signal: # WLs on a BL

$$C_{BL} = N C_{DIFF} + N C_{M1}$$

$$TR = C_{Cell} / (C_{BL} + C_{Cell})$$

 


BL Float  
at GND

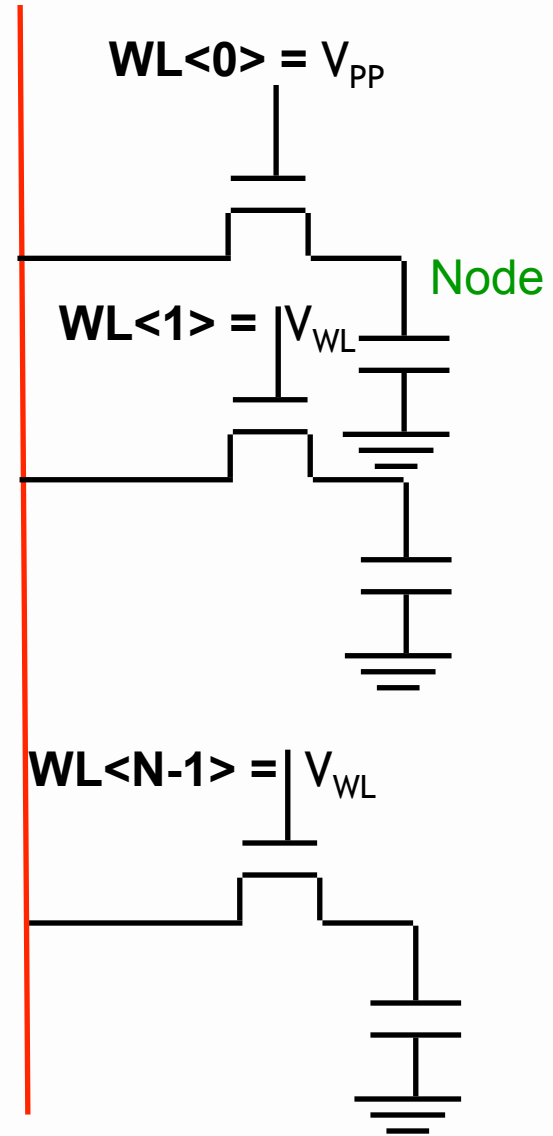




# Bits per Bit-Line v/s Transfer Ratio

 


# Signal: # WLs on a BL

Short BLs are Mandatory in DRAMs

 

BL Float at GND

 

# Segmentation

**Array Segmentation Refers to WL / BL Count per Sub-Array**

**Longer Word-Line is Slower but more Area efficient (Less Decode/Drivers)**

**Longer Bit-Line (more Word-Lines per Bit-Line)**

Less Signal (Higher Bit-Line Capacitance = Lower Transfer Ratio)

More Power (Bit-Line CV is Significant Component of DRAM Power)

Slower Performance (Higher Bit-Line Capacitance = Slower Sense Amp)

More Area Efficient (Fewer Sense Amps)

**Number of Word-Lines Activated determines Refresh Interval and Power**

All Cells on Active Word-Line are Refreshed

All Word-Lines must be Refreshed before Cell Retention Expires

64ms Cell Retention / 8K Word Lines = 7.8us between refresh cycles

Activating 2 Word-Lines at a time = 15.6us, 2x Bit-Line CV Power

# Choice of SA

Depending on signal developed SA architecture is chosen

## **Direct sensing**

- Requires large signal development

- An inverter can be used for sensing

- Micro sense amp ( $\mu$ SA) is another option


## **Differential sense amp**

- Can sense low signal developed

This is choice between area, speed/performance

# Sensing $\rightarrow$ Signal Amplification
 
## Differential Voltage Amplified by Cross Couple Pair



When Set Node  $< (V + \Delta V) - V_{tn1}$ ,  $I^+$  will start to flow (On-Side Conduction)

When Set Node  $< (V) - V_{tn0}$ ,  $I^-$  will start to flow (Off-Side Conduction)

Off-Side Conduction Modulated by Set Speed and Amount of Signal



Complimentary X-Couple Pairs provide Full CMOS Levels on Bit-Line

# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM Write Analysis
- ❑ eDRAM Sense-Amplifier Specification
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example
  
# Write-Margin

How much signal can we write into the cell?



# Write-Margin


How much signal can we write into the cell?

Assume:

- Bit-line is charged to  $V_{DD}$
- Word-line rises instantly to  $V_{PP}$

$$V_{GS} = V_{PP} - V(t)$$

$$V_{DS} = V_{DD} - V(t)$$

 



# Write-Margin

How much signal can we write into the cell?

Assume:

- Bit-line is charged to  $V_{DD}$
- Word-line rises instantly to  $V_{PP}$

$$V_{GS} = V_{PP} - V(t)$$


$$V_{DS} = V_{DD} - V(t)$$

Access transistor is a thick oxide device  $\Rightarrow V_{DSAT} \gg V_{PP}$

$$V_{DS} = V_{DD} - V(t) < V_{GS} - V_{Tn} = V_{PP} - V(t) - V_{Tn}$$

$$V_{PP} \geq V_{DD} + V_{Tn} + \Delta V_{Tn}$$

 *Access device is in the linear region throughout*



# Write-Margin

$$I_{DS} = \mu_n C_{OX} (W/L) V_{DS} (V_{GS} - V_{Tn} - V_{DS}/2) = C_{Cell} dV/dt$$

$$V_{GS} = V_{PP} - V(t)$$

$$V_{DS} = V_{DD} - V(t)$$

Assume you wish to write a voltage  $V_f$  into the cell in a time  $T_{WRITE}$


Solving you will get:

$$T_{WRITE} = 2 T_0 \ln[(1 - V_f/2\Delta)/(1 - V_f/V_{DD})]$$

Where

$$T_0 = \{C_{cell} / [\mu_n C_{OX} (W/L) (2\Delta - V_{DD})]\}$$

$$\Delta = V_{PP} - V_{Tn} - V_{DD}/2$$

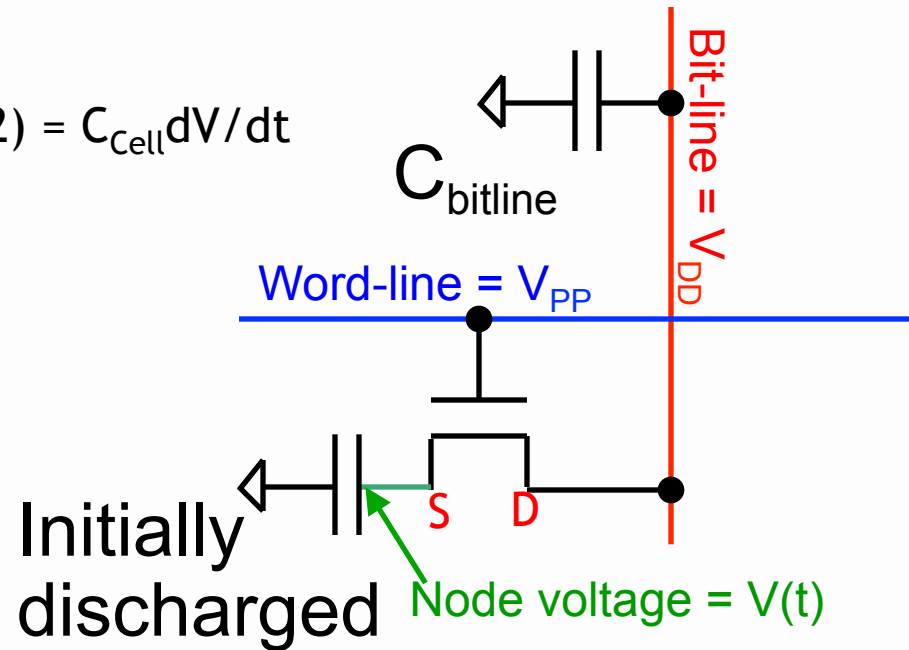

$$I_{DS} = \mu_n C_{ox} \left( \frac{W}{L} \right) \cdot V_{DS} \left( V_{GS} - V_{Tn} - \frac{V_{DS}}{2} \right)$$

$$I_{DS} = C \frac{dV}{dt} \quad (C = C_{cell})$$

$$\Rightarrow K V_{DS} \left( V_{GS} - V_{Tn} - \frac{V_{DS}}{2} \right) = C \frac{dV}{dt}$$

$$K = \mu_n C_{ox} \left( \frac{W}{L} \right)$$

$$\Rightarrow \left( \frac{K}{C} \right) \cdot (V_{DD} - V) \left( V_{PP} - V - V_{Tn} - \frac{V_{DD} - V}{2} \right) = \frac{dV}{dt}$$

$$\Rightarrow \left( \frac{K}{C} \right) (V_{DD} - V) \left( V_{PP} - V_{Tn} - \frac{V_{DD}}{2} - \frac{V}{2} \right) = \frac{dV}{dt}$$

$$\Rightarrow \frac{K}{C} dt = \frac{dV}{(V_{DD} - V) \left( \Delta - \frac{V}{2} \right)}$$

$$\text{Where } \Delta = \left( V_{PP} - V_{Tn} - \frac{V_{DD}}{2} \right)$$

$$\Rightarrow \frac{K}{C} dt = \frac{2 dV}{(2\Delta - V_{DD})} \times \left[ \frac{1}{V_{DD} - V} - \frac{1}{2\Delta - V} \right]$$

$$\Rightarrow \frac{K}{C} \tau_{WRITE} = \frac{2}{2\Delta - V_{DD}} \cdot \ln \left[ \frac{2\Delta - V}{V_{DD} - V} \right] \Bigg|_0^{V_f}$$



$$\Rightarrow \tau_{WRITE} = \frac{2C}{K(2\Delta - V_{DD})} \left[ \ln \left[ \left( \frac{2\Delta - V_f}{V_{DD} - V_f} \right) \left( \frac{V_{DD}}{2\Delta} \right) \right] \right]$$

$$\tau_{WRITE} = \frac{2C}{K(2\Delta - V_{DD})} \ln \left[ \frac{1 - V_f/2\Delta}{1 - V_f/V_{DD}} \right]$$


# Write-Margin – Analysis

$$T_{\text{WRITE}} = 2 T_0 \ln[(1 - V_f / 2\Delta) / (1 - V_f / V_{\text{DD}})]$$

Where

$$T_0 = \{C_{\text{cell}} / [\mu_n C_{\text{OX}} (W/L)(2\Delta - V_{\text{DD}})]\}$$
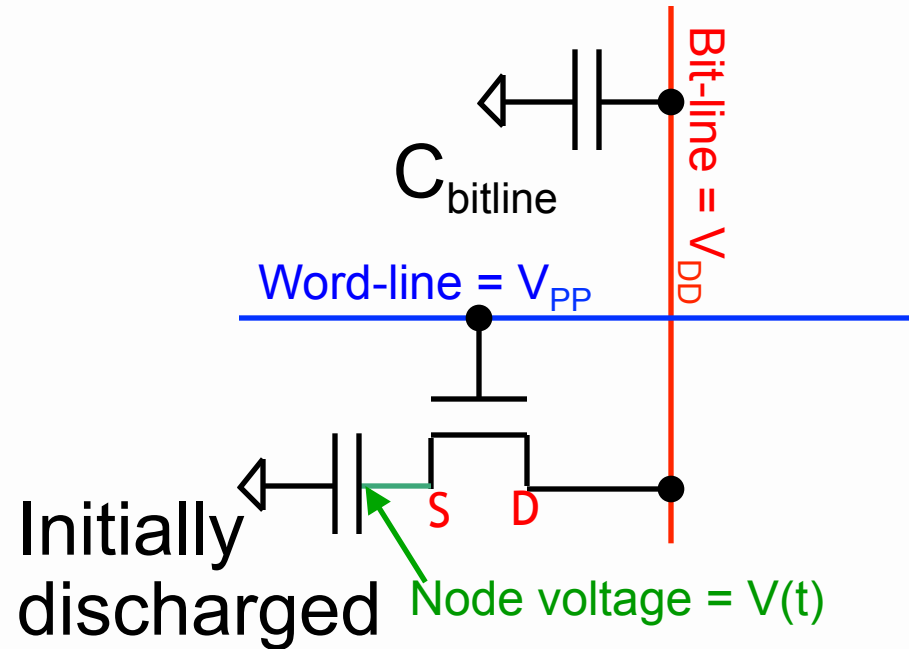
$$\Delta = V_{\text{PP}} - V_{\text{Tn}} - V_{\text{DS}}/2$$



1. What happens when  $V_{\text{PP}}$  is increased?
2. What happens when  $V_f \rightarrow V_{\text{DD}}$


# Write-Margin – Analysis

$$T_{\text{WRITE}} = 2 T_0 \ln[(1-V_f/2\Delta)/(1-V_f/V_{\text{DD}})]$$

Where

$$T_0 = \{C_{\text{cell}} / [\mu_n C_{\text{OX}} (W/L)(2\Delta - V_{\text{DD}})]\}$$
 
$$\Delta = V_{\text{PP}} - V_{\text{Tn}} - V_{\text{DD}}/2$$



1. What happens when  $V_{\text{PP}}$  is increased?

- $\Delta$  increases and  $T_0$  decreases
- $\ln[(1-V_f/2\Delta)/(1-V_f/V_{\text{DD}})]$  increases logarithmically
- $T_{\text{WRITE}}$  effectively decreases.
- However WL power goes up as  $(V_{\text{PP}} - V_{\text{WL}})^2$

# Write-Margin – Analysis

$$T_{\text{WRITE}} = 2 T_0 \ln[(1-V_f/2\Delta)/(1-V_f/V_{\text{DD}})]$$


Where

$$T_0 = \{C_{\text{cell}} / [\mu_n C_{\text{OX}} (W/L)(2\Delta - V_{\text{DD}})]\}$$

$$\Delta = V_{\text{PP}} - V_{\text{Tn}} - V_{\text{DS}}/2$$


 
1. What happens when  $V_f \rightarrow V_{\text{DD}}$

- $(1-V_f/V_{\text{DD}})$  approaches 0
- $\ln[(1-V_f/2\Delta)/(1-V_f/V_{\text{DD}})]$  shoots to  $\infty$



**You cannot write a FULL  $V_{\text{DD}}$  into the cell in finite time**



# Storing data '1' in the cell

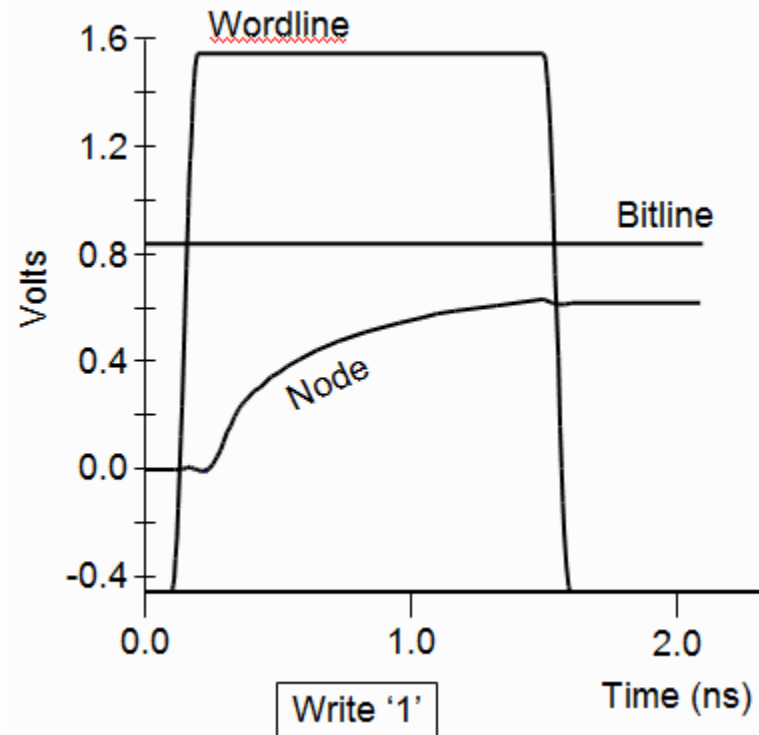 

$V_{gs}$  for pass transistor reduces as bitcell voltage rises, increasing  $R_{on}$

Why there is a reduction in cell voltage after WL closes? Experiment

# Reality

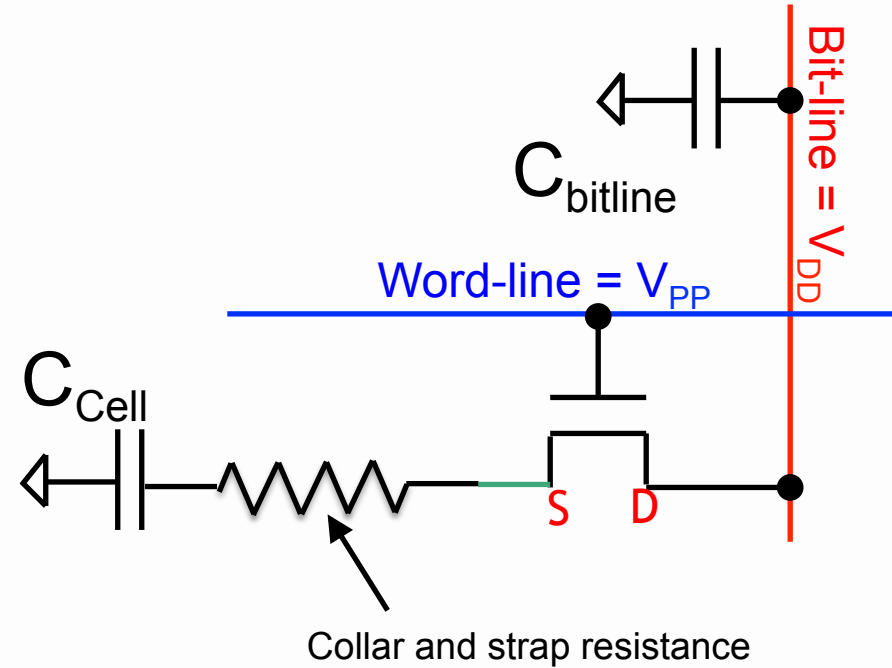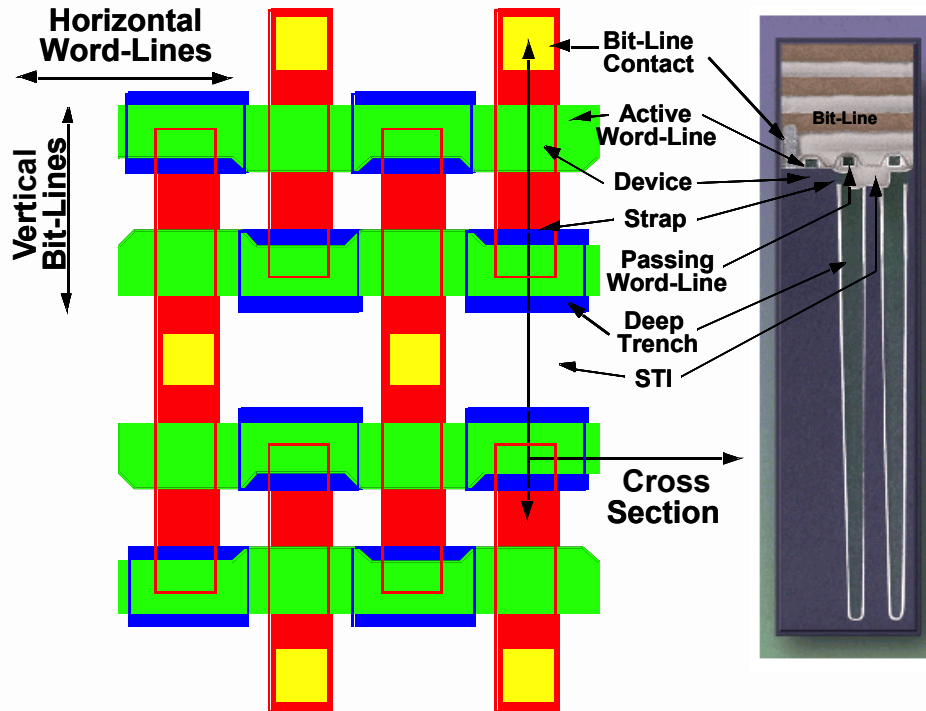

The node takes longer to charge than what we calculated analytically  
Conclusions do not change:

- Increasing  $V_{PP}$  decreases the write time
- Cannot write a full  $V_{DD}$  in finite time




# Topics


- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM Write Analysis
- ❑ eDRAM Sense-Amplifier Specification
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example

# Signal: # WLs on a BL

Short BLs are Mandatory in DRAMs

 

BL Float at GND

 

# SRAM vs DRAM



Assume a 1Mb memory with 512 WLs and 2048 BLs and 8 Columns. i.e. 256 DLs

	SRAM	DRAM
#WLs per BL	512	32
# BLs per DL	8	8
Sharing Sense Amps across columns	Yes	Possible?
Effective number of cells connected to a SA	4096	?
# Sense Amps	256	?



# Half Select Condition - SRAM

**BLt0 = Float @  $V_{DD}$**



**BLc0 = Float @  $V_{DD}$**

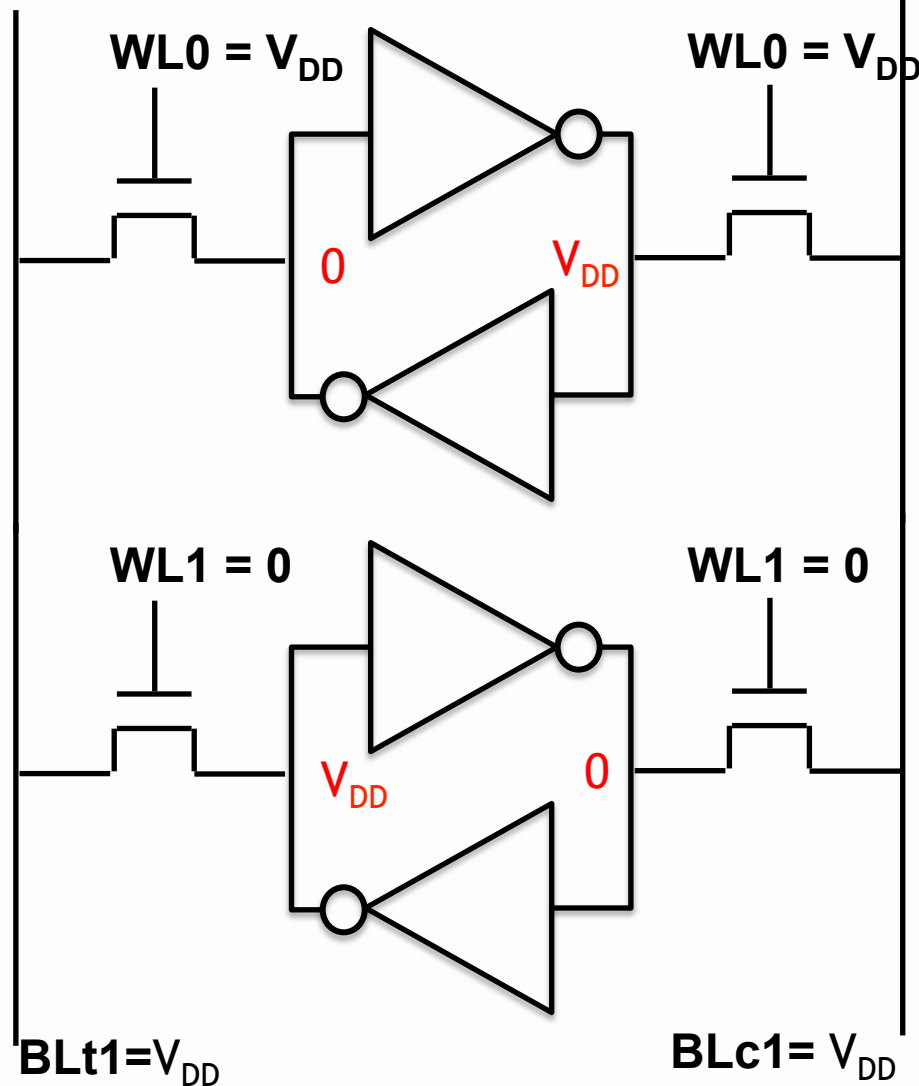 

# Half Select Condition - eDRAM

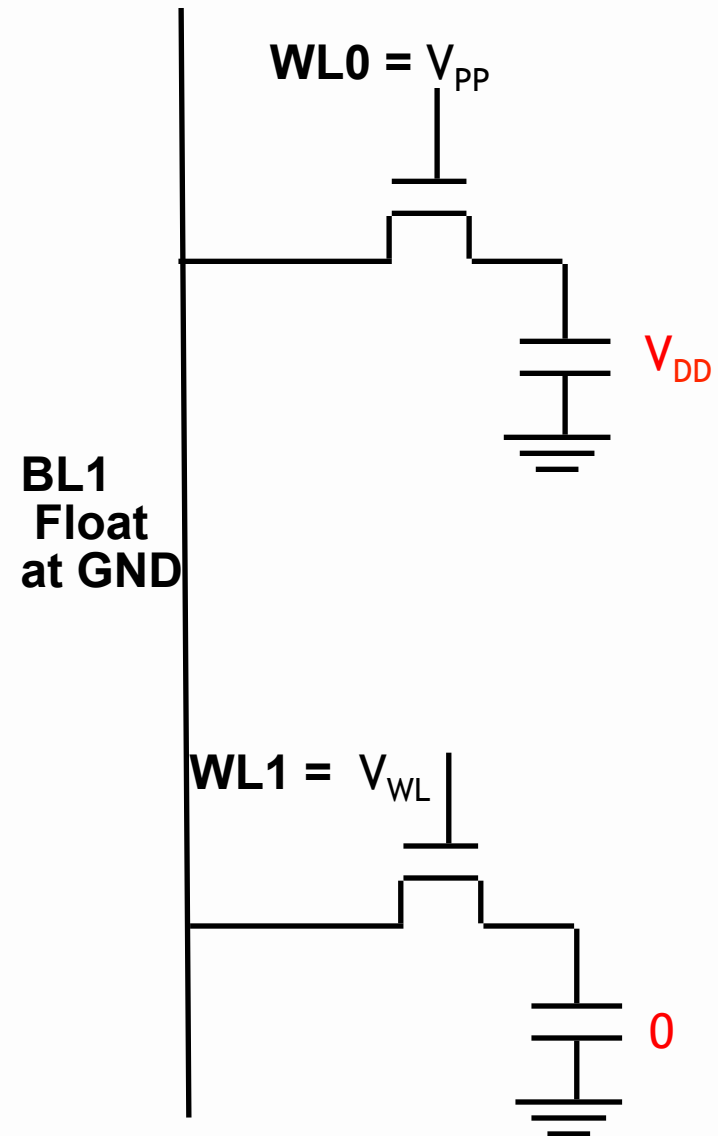 

# Half Select Condition - eDRAM

  

# SRAM vs DRAM

Assume a 1Mb memory with 512 WLs and 2048 BLs and 8 Columns. i.e. 256 DLs

	SRAM	DRAM
#WLs per BL	512	32
# BLs per DL	8	8
Sharing Sense Amps across columns	Yes	No
Effective number of cells connected to a SA	4096	32
# Sense Amps	256	

## Extremely small SA

- Number of transistors
- Sizes of transistors

# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM Write Analysis
- ❑ eDRAM Sense-Amplifier Specification
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example




# DRAM Operation Details (Case Study)

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 43, NO. 1, JANUARY 2008


**A 500 MHz Random Cycle, 1.5 ns Latency, SOI Embedded DRAM Macro Featuring a Three-Transistor Micro Sense Amplifier (John Barth/IBM)**
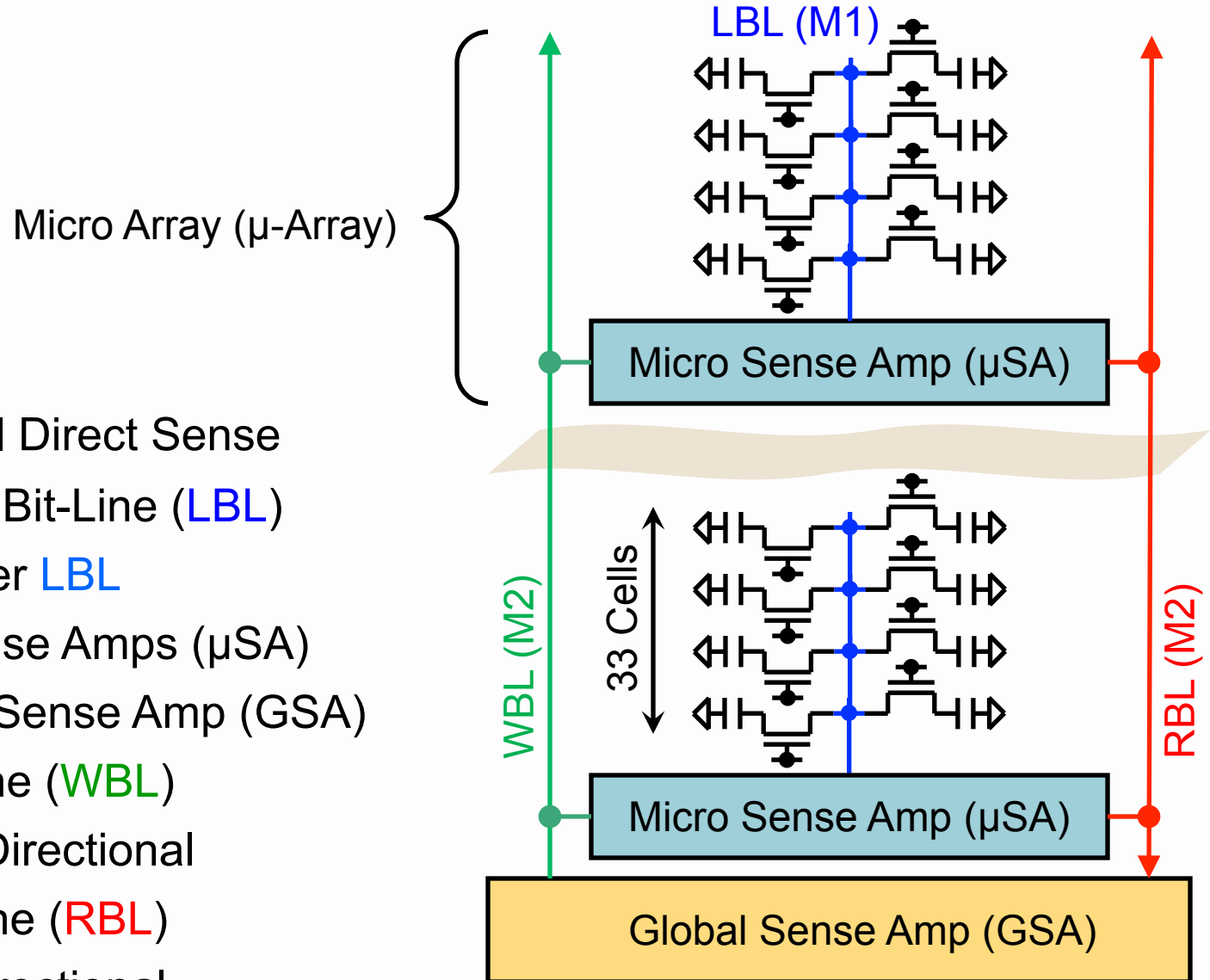
# Micro Sense Architecture


- Hierarchical Direct Sense
- Short Local Bit-Line (LBL)
  - 33 Cells per LBL
- 8 Micro Sense Amps ( $\mu$ SA) per Global Sense Amp (GSA)
- Write Bit-Line (WBL)
  - Uni-Directional
- Read Bit-Line (RBL)
  - Bi-Directional




# Sense Hierarchy - Motivation

 

# Micro Sense Hierarchy - Three levels

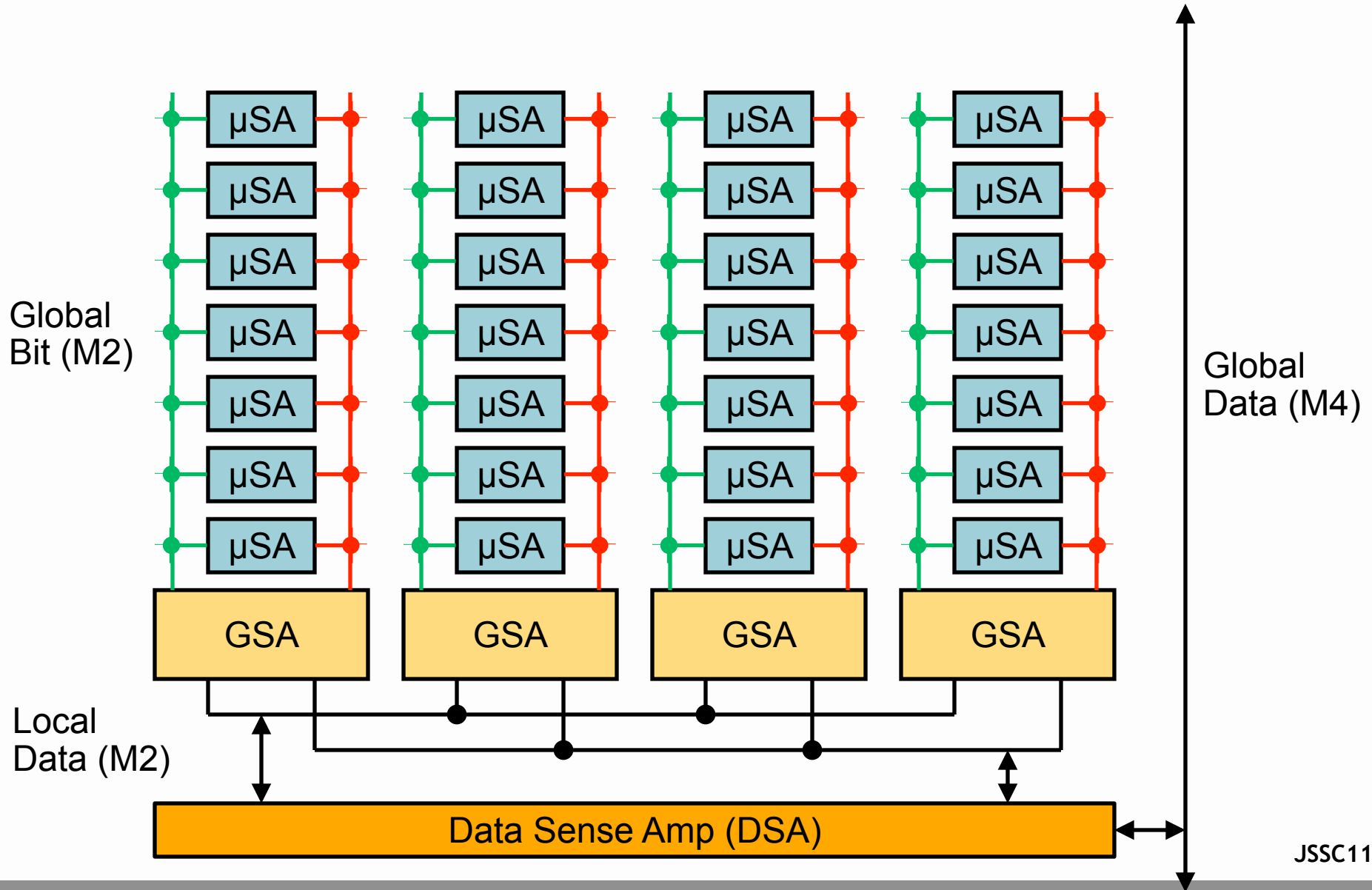

# 3T uSA operation

 

## Pre-charge

WL is low. WBL and RBL both pre-charged to HIGH. Next GSA drives WBL low. LBL floats to GND level

## Read "0"

LBL remains LOW. RBL is HIGH. Sensed as a "0"

## Read "1"

LBL is HIGH. Turns on RH, pulls RBL LOW. + feedback as pFET FB turns ON. Sensed as a "1"


## Write "1"

GSA pulls RBL to GND. FB pFET turns ON. Happens while WL rises (direct write)


## Write "0"

WBL is HIGH, PCW0 ON. Clamps LBL to GND. As WL activates.

# Simulations - Write

 


# Simulations - Read

 

(b)

JSSC08

# Micro Sense Hierarchy - Three levels

 





 
# Layout Floor plan of Array+SA

GSA Should fit into the bitcell width or  $n \cdot \text{bitcell width}$


Thus, distributed GSA on two sides of bitcell array



# Layout Floor plan of Array+SA

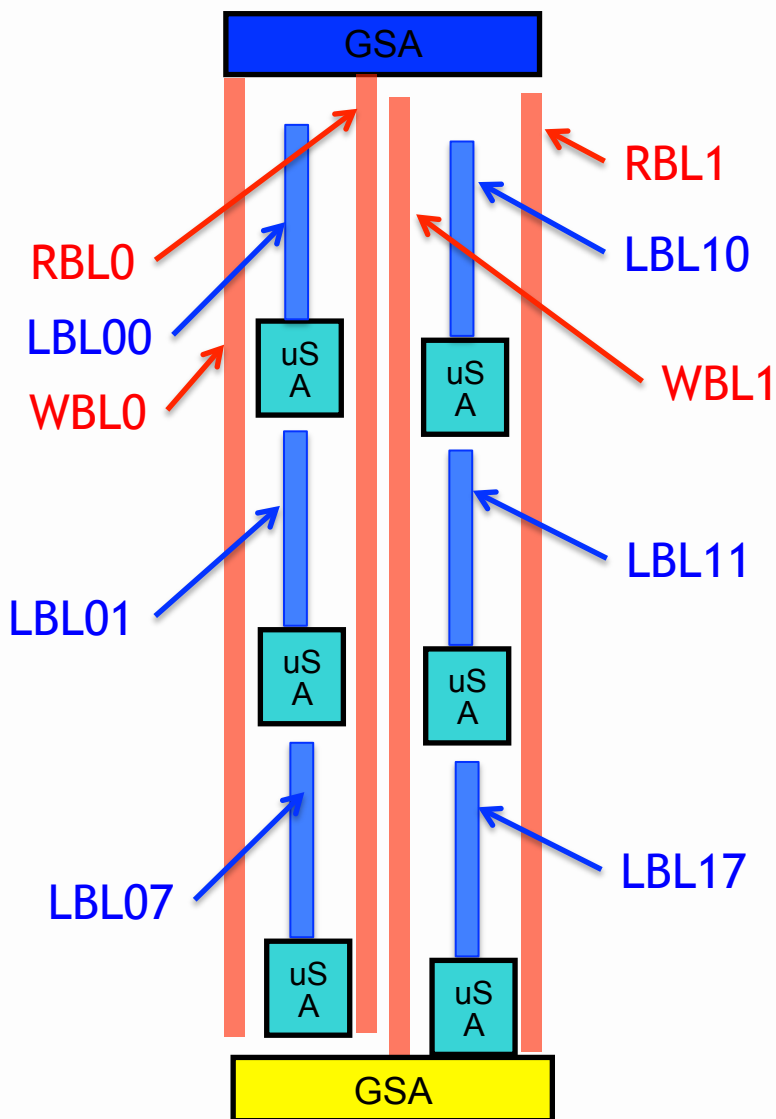 


# Column Interleave

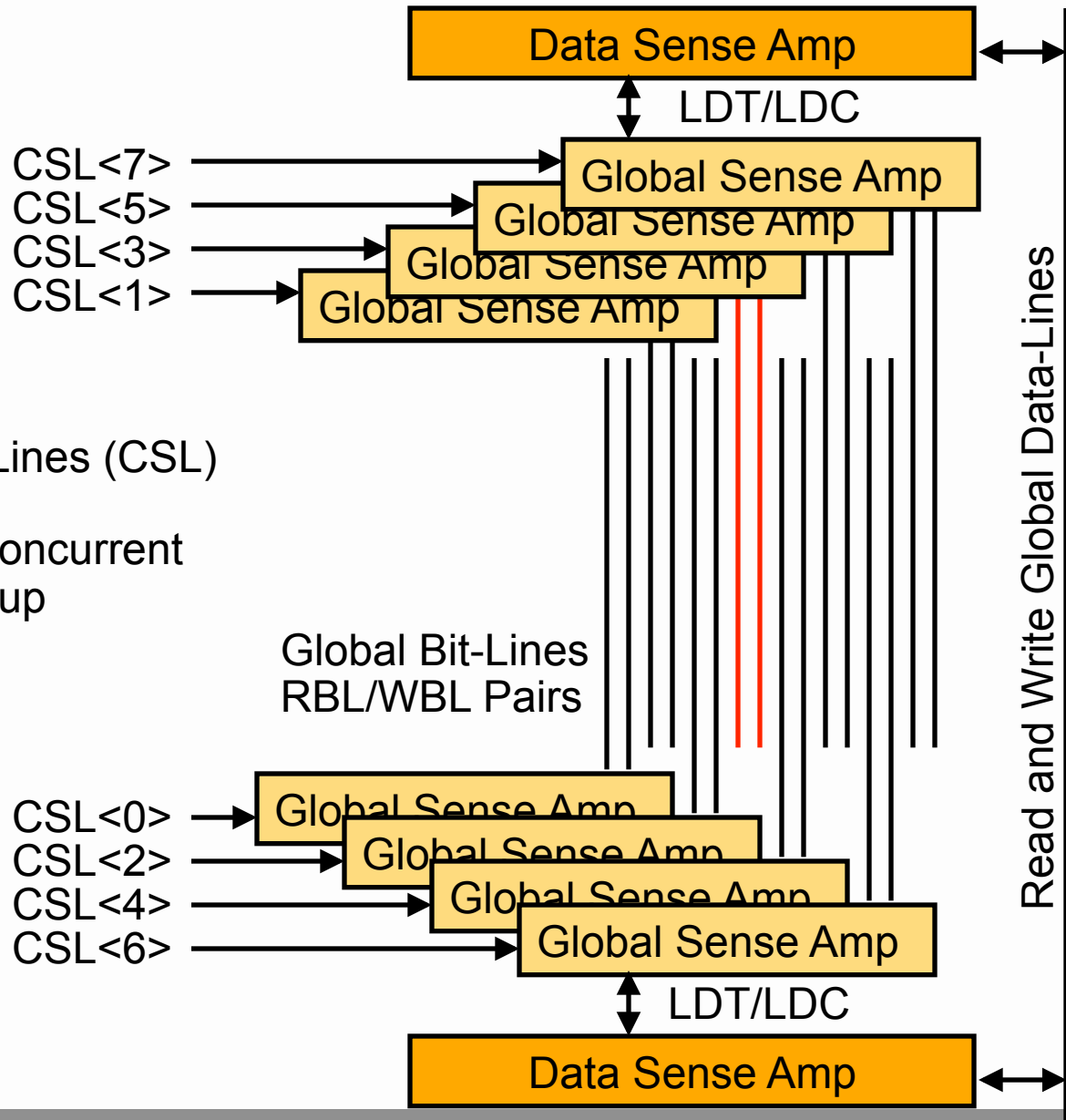


- 1 of 8 Column Select Lines (CSL)
- Fire Early for Write
- Fire Late to Support Concurrent Cache Directory Lookup

# LAYOUT of array


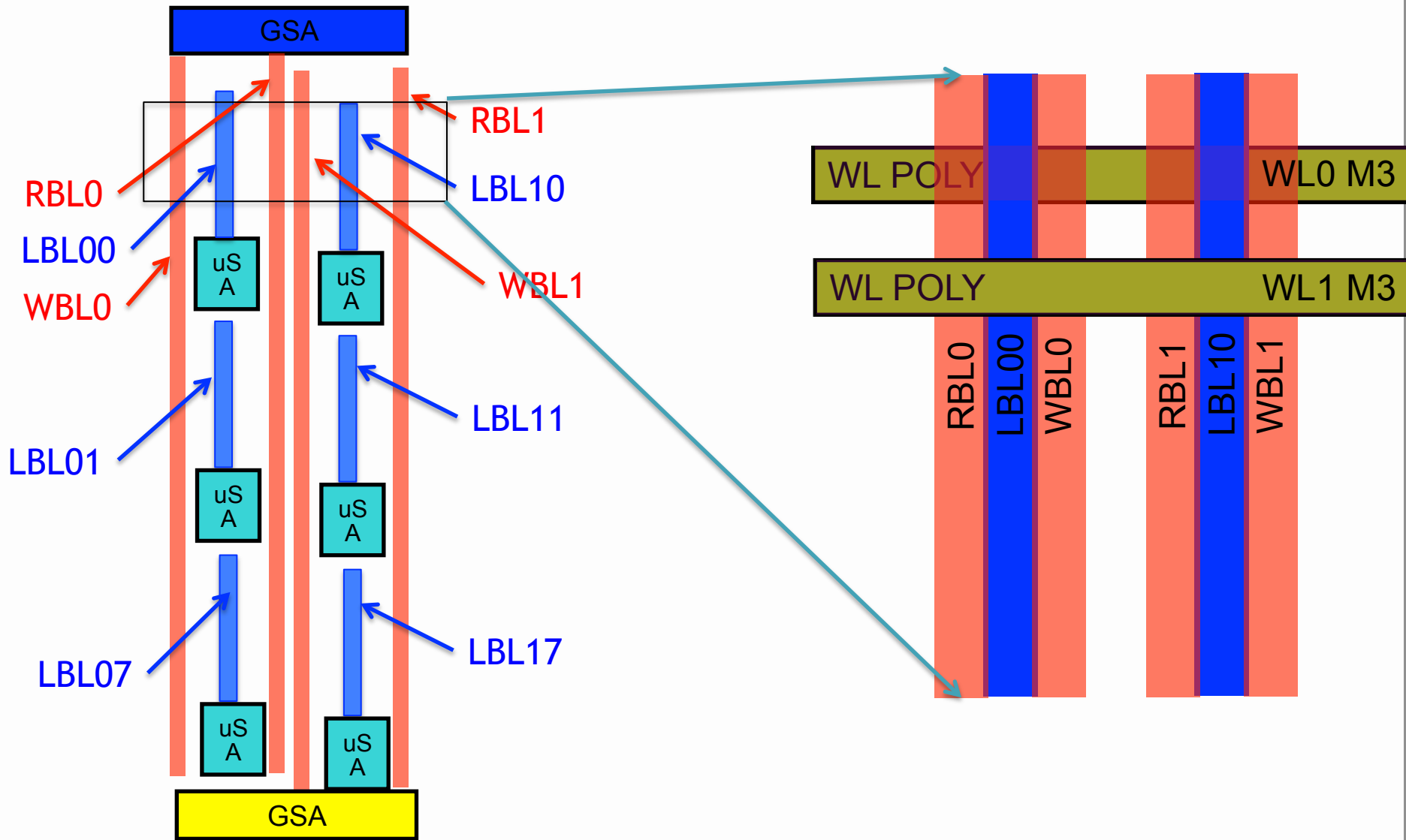

 
# Micro Sense Local Bit-line Cross Section




Single Ended Sense – Twist not effective  
Line to Line Coupling must be managed

# Micro Sense Coupling Mechanisms

  

1. Write '1' Couples **WBL** below Ground Increasing RH leakage during Refresh '0'
2. Write '0' Couples **RBL** above VDD Delaying Feedback during Refresh '1'
3. Read '1' Couples Half-Selected LBL Below GND Increasing Array Device Sub-VT Leakage


# Half Selected LBL

 

- Accessing one of WL0-32
- Cell connected is on LBL00
- LBL01-07 – Half Selected LBLs


# Micro Sense Evolution

 1. Write Zero (W0)
2. Read Head (RH)
3. Feed-Back (FB)




Barth, ISSCC'07

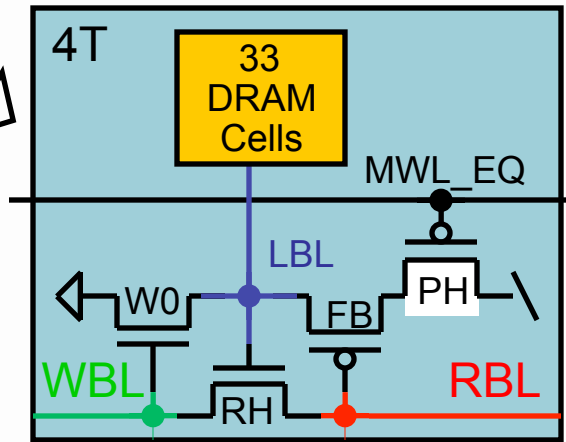4. PFET Header (PH)
  - LBL Power Gate
  - LBL Leakage



Klim, VLSI'07

5. Pre-Charge (PC)
  - WBL Power (Write '0' Only)
6. NFET Footer (NF)
  - RBL Leakage
  - Decompose Pre-Charge and Read Enable (MWL\_RE)

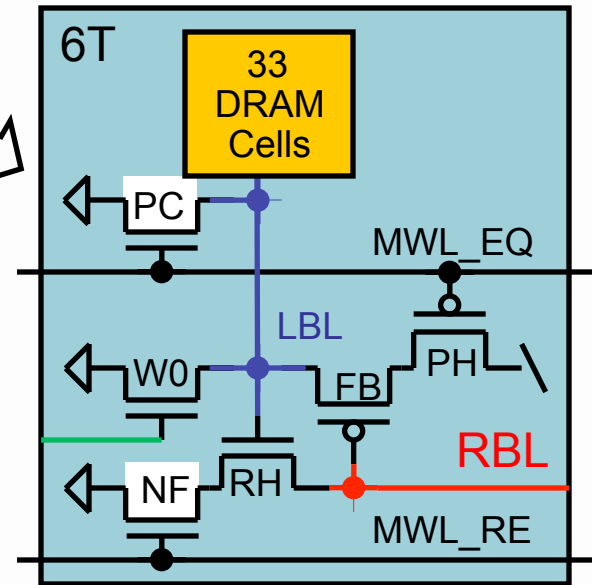

JSSC11


Power Reduction

Power Reduction  
Traded for Transistor Count

Increased Transistor Count




# Micro Sense Hierarchy - Three levels

 


# Micro Sense Architecture ( $\mu$ SA)

3 Transistors

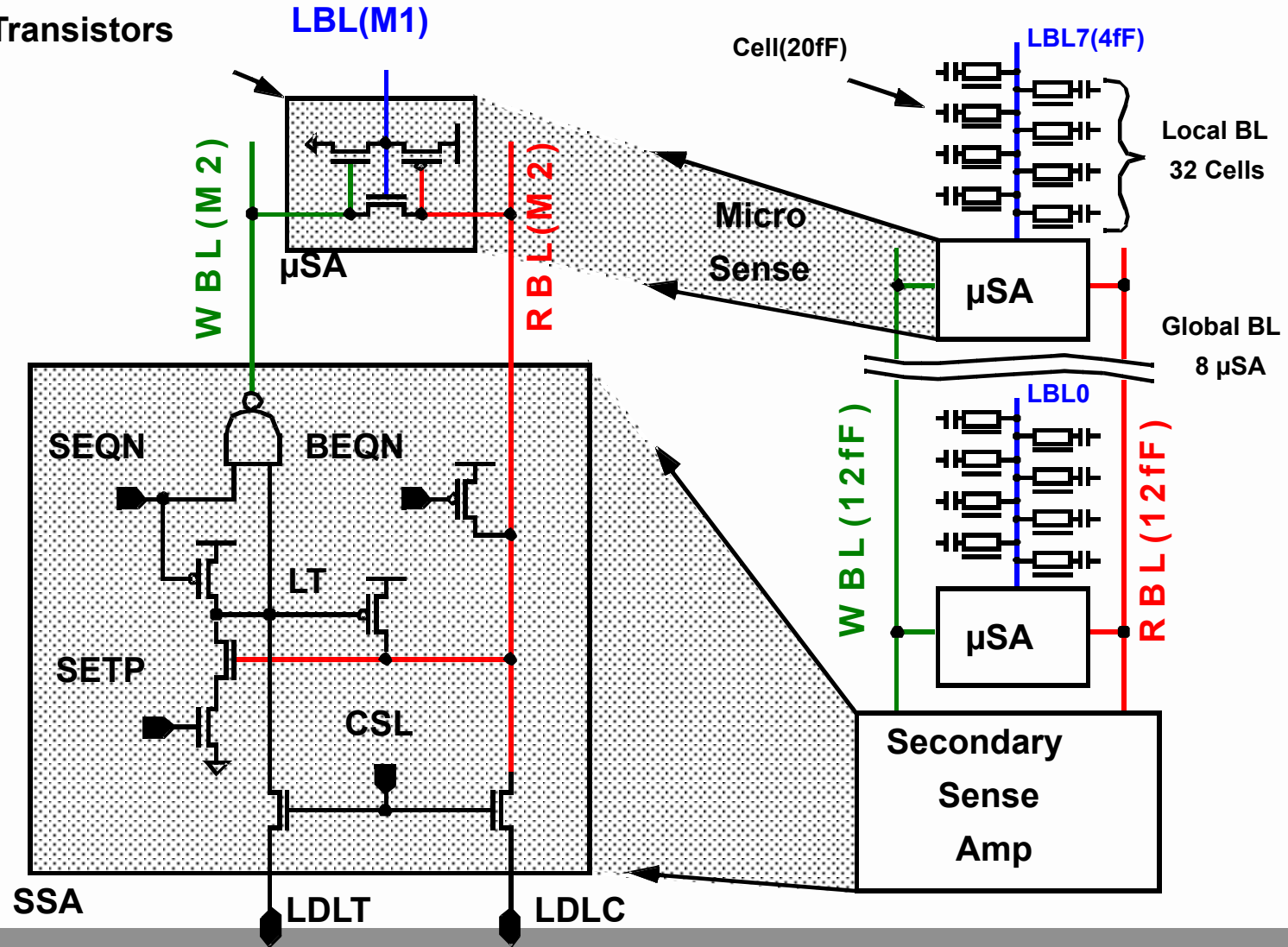


# Micro Sense Architecture ( $\mu$ SA)

 


(b)


3 Transistors

 


# Micro Sense Hierarchy - Three levels

 


# Data Sense Amp (DSA)

 


# Data Sense Amp (DSA) – Write

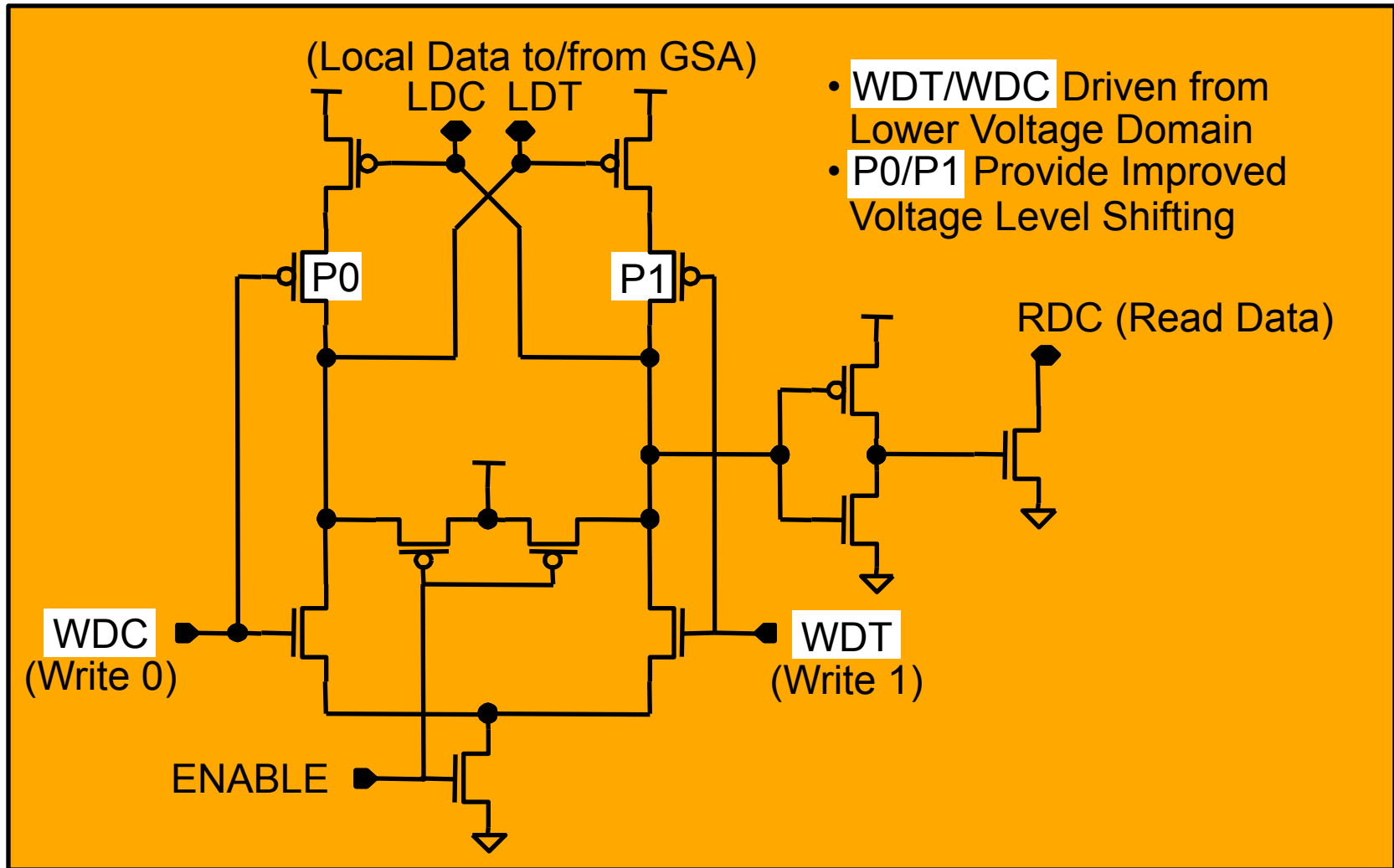

# Data Sense Amp (DSA) – Read

 

# Combining DSA's- Dynamic NOR Gate

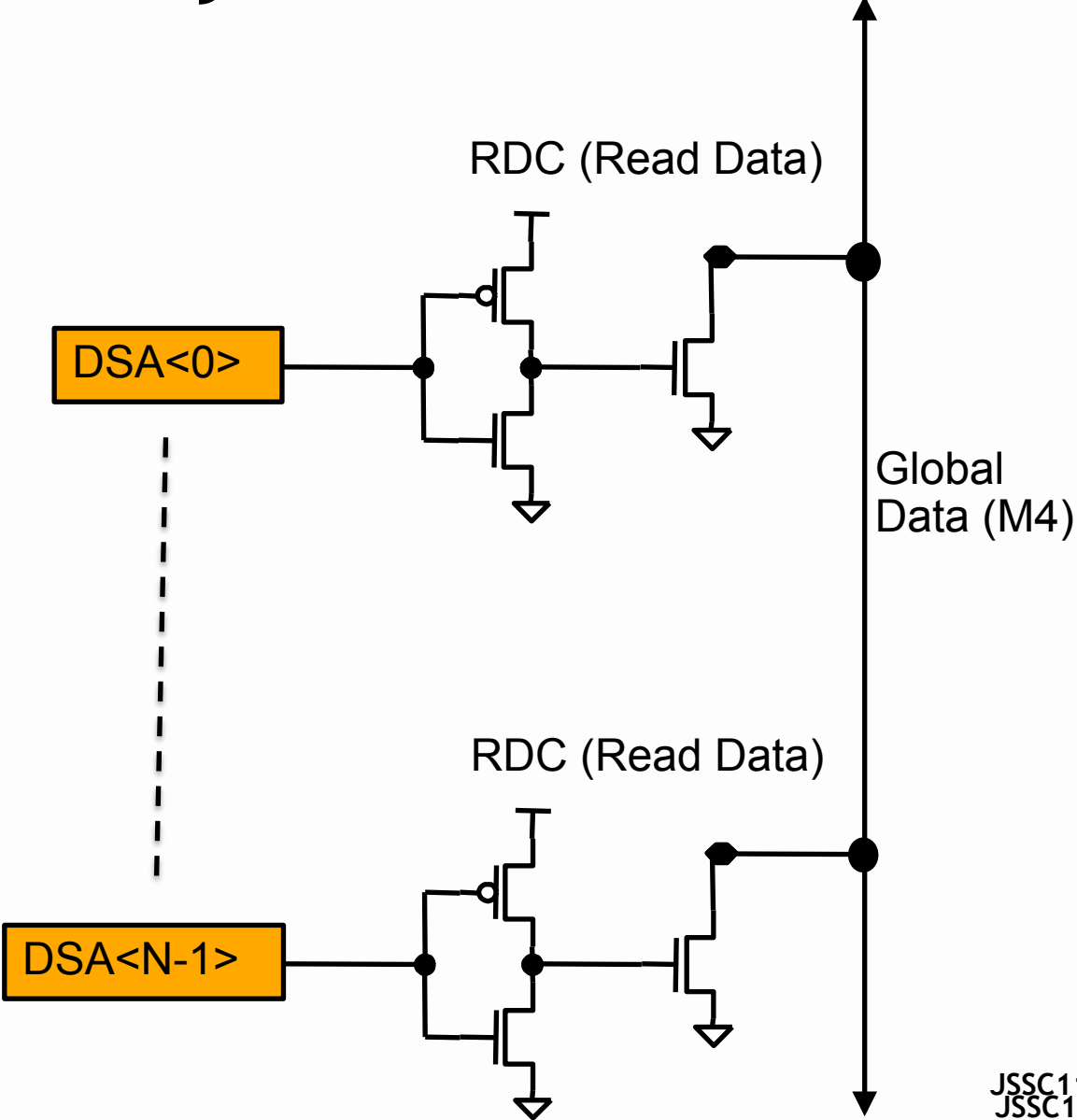




# Micro Sense Advantage

Fast Performance of Short Bit-Line

Area Overhead of 4x Longer Bit-Line

Bits/BL	256	128	32
Sense Amp	10%	20%	19%
Reference Cells	2.3%	4%	-
Twist Region	2%	2.6%	-
Second Sense Amp	-	-	8%
Total	14.3%	26.6%	27%



Same Overhead

 


# Bit-Line area overhead

<b>Bits/BL</b>	<b>256</b>	<b>128</b>	<b>32</b>
<b>Sense Amp</b>	<b>10%</b>	<b>20%</b>	<b>&gt; 80%</b>
<b>Reference Cells</b>	<b>2.3%</b>	<b>4%</b>	
<b>Twist Region</b>	<b>2%</b>	<b>2.6%</b>	

**Unacceptable**

  

# Array utilization

 

$$\text{Utilization} = \frac{\text{Cell Area}}{\text{IO + Predecode + Redundancy}}$$

Mbits/mm<sup>2</sup>

# Access Shmoo

1.5ns Access @1V 85C




4ns Access @600mV


# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM Write Analysis
- ❑ eDRAM Sense-Amplifier Specification
- ❑ eDRAM operational details (case study)
- ❑ eDRAM Read Analysis
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM

# Read Time Calculation

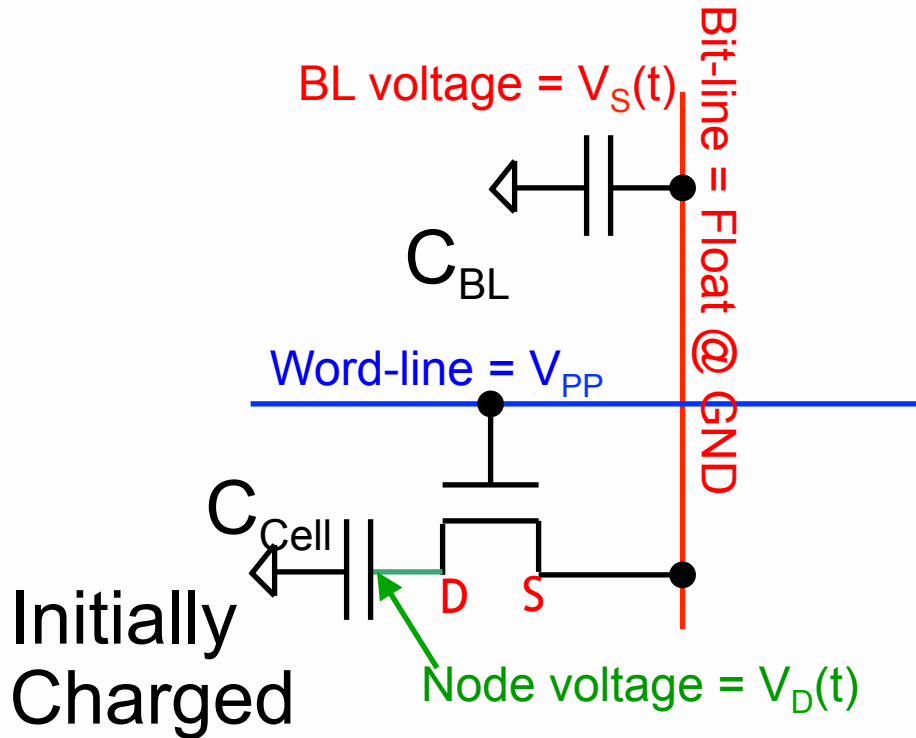

BL – Pre-discharged  
Read-1

 

BL – Pre-charged  
Read-0

Read time : Let us define it as time required for BL to reach  $V_{DD}/2$

# Read Time





	BL pre-discharged	BL pre-charged
Source	BL	Node
Drain	Node	BL
Initial Charge	$C_{Cell} V_{DD}$	$C_{BL} V_{DD}$
Charge	$C_{Cell} V_D + C_{BL} V_S = C_{Cell} V_{DD}$	$C_{Cell} V_S + C_{BL} V_D = C_{BL} V_{DD}$
Charging Equation	$I_{DS} \left[ \frac{1}{C_{Cell}} + \frac{1}{C_{BL}} \right] = - \frac{dV_{DS}}{dt}$	
Current	$I_{DS} = \mu_n C_{OX} \frac{W}{L} V_{DS} (V_{PP} - V_{Tn} - V_S - V_{DS}/2)$	
$V_S$	$\alpha (V_{DD} - V_{DS})$	$(1 - \alpha) (V_{DD} - V_{DS})$
$\alpha$	$\frac{C_{Cell}}{C_{Cell} + C_{BL}}$	
$I_{DS}$	$K V_{DS} (\Delta_1 + (\alpha - 0.5) V_{DS})$	$K V_{DS} (\Delta_2 - (\alpha - 0.5) V_{DS})$
$K$	$\frac{C_{EFF}}{\mu_n C_{OX} (W/L)}; C_{EFF} = \frac{C_{Cell} C_{BL}}{C_{Cell} + C_{BL}}$	
$\Delta$	$\Delta_1 = V_{PP} - V_{Tn} - \alpha V_{DD}$	$\Delta_2 = V_{PP} - V_{Tn} - (1 - \alpha) V_{DD}$

	BL pre-discharged	BL pre-charged
Read Threshold	$V_S = V_{DD}/2$	$V_D = V_{DD}/2$
$V_{DS-TH} (V_{FINAL})$	$\frac{V_{DD}}{2} \left(1 - \frac{C_{BL}}{C_{Cell}}\right)$	
$T_{WRITE}$	$-K \int_{V_{DD}}^{V_{FINAL}} \frac{dV_{DS}}{V_{DS}(\Delta_1 + (\alpha - 0.5)V_{DS})}$	$-K \int_{V_{DD}}^{V_{FINAL}} \frac{dV_{DS}}{V_{DS}(\Delta_2 - (\alpha - 0.5)V_{DS})}$
$T_{WRITE}$	$\frac{K}{\Delta_1} \ln\left(\frac{V_{DD}(\Delta_1 + (\alpha - 0.5)V_{FINAL})}{V_{FINAL}(\Delta_1 + (\alpha - 0.5)V_{DD})}\right)$	$\frac{K}{\Delta_2} \ln\left(\frac{V_{DD}(\Delta_2 + (0.5 - \alpha)V_{FINAL})}{V_{FINAL}(\Delta_2 + (0.5 - \alpha)V_{DD})}\right)$



# Read Time



# Intuition

  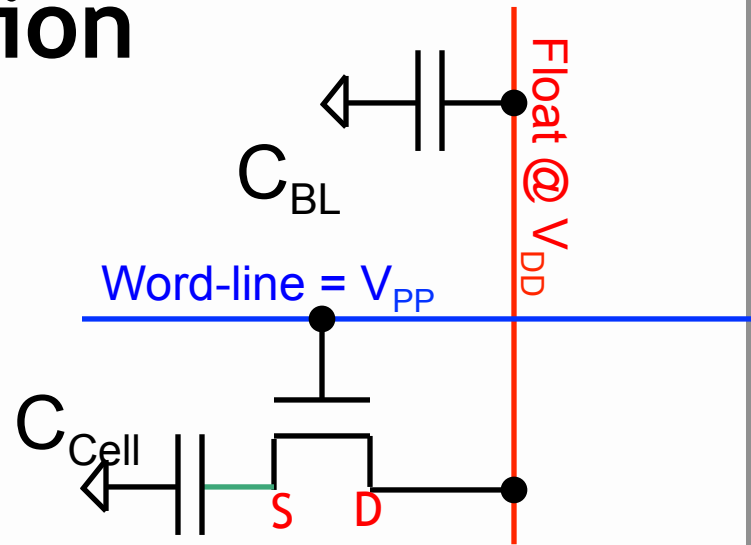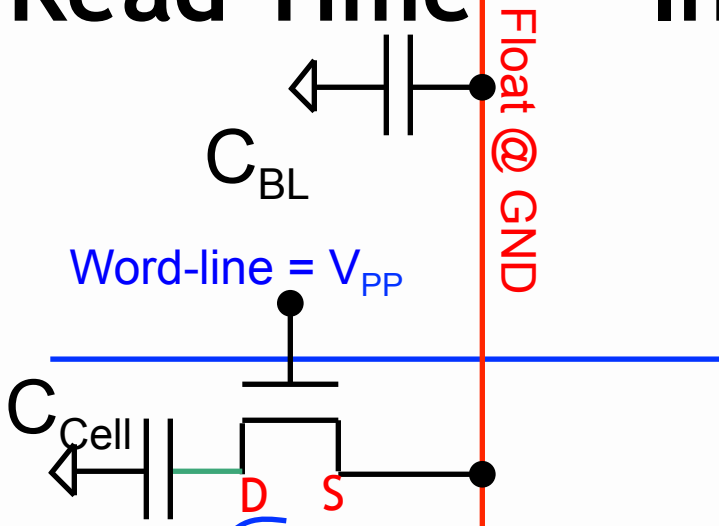

# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM Write Analysis
- ❑ eDRAM Sense-Amplifier Specification
- ❑ eDRAM operational details (case study)
- ❑ eDRAM Read Analysis
- ❑ SOI Technology
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM

# Bulk vs SOI Technology

  

Body contact can be used to fix the body potential in bulk technology  
SOI Technology

- Floating body is a problem
- History effect
- SOI provides better sub-threshold slope
- Higher performance with lower leakage

# Floating Body Effects

Body potential modulated by coupling and leakage

Better source follower vs. bulk during write back (body coupling)

Improved write '1' cell voltage


Degraded  $I_{off}$  / Retention if body floats high (body leakage)

GND pre-charge keeps body low

Eliminate long periods with BL high (limit page mode)

$I_{Leak_{FWD}} > I_{Leak_{REV}}$

When BL = GND  
Body ~ GND

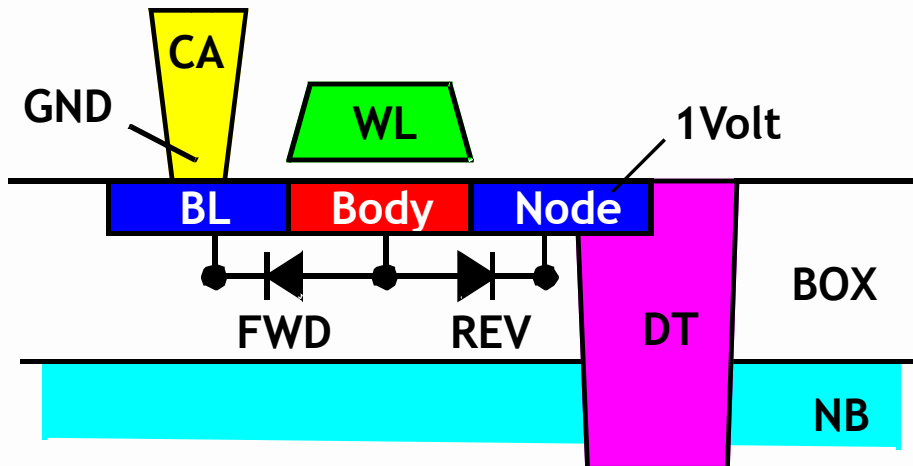

# Floating Body Effects

Body potential modulated by coupling and leakage

Better source follower vs. bulk during write back (body coupling)

Improved write '1' cell voltage


Degraded  $I_{off}$  / Retention if body floats high (body leakage)

GND pre-charge keeps body low

Eliminate long periods with BL high (limit page mode)


$I_{Leak_{FWD}} > I_{Leak_{REV}}$

When BL = GND  
Body ~ GND

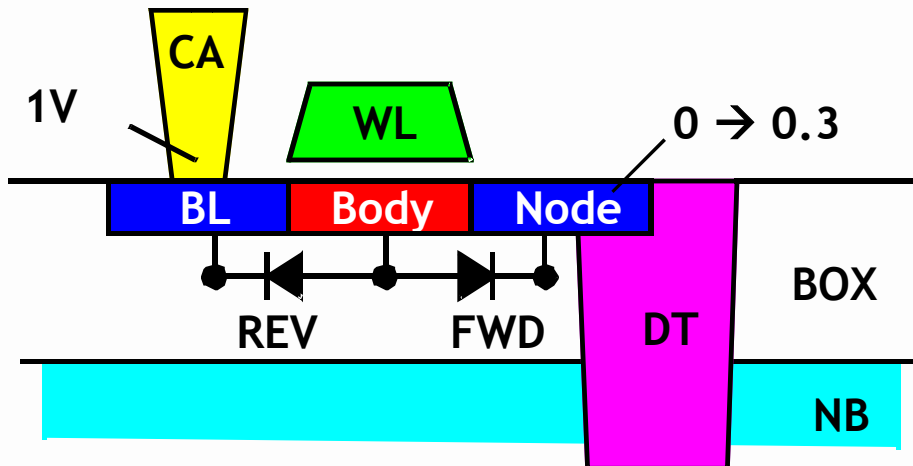


# Array Body Charging

## Commodity DRAM (long page mode)

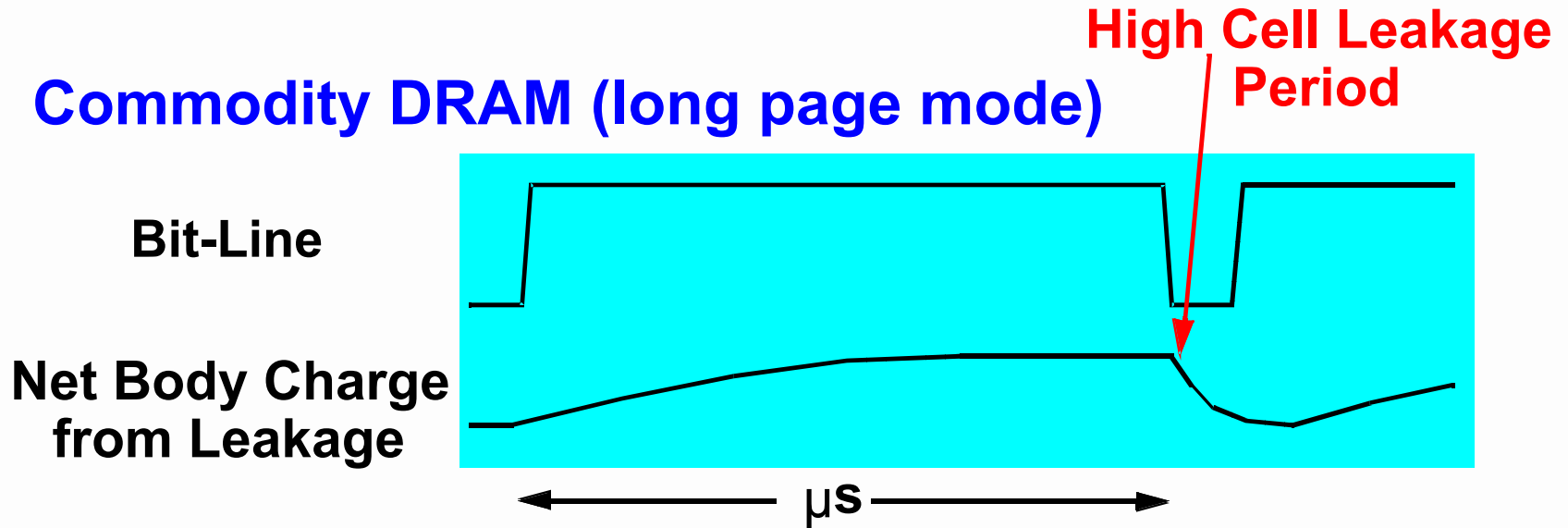

## embedded DRAM (limited page mode)

 


# Noise

Coupling and Local Process Variation effectively degrades signal

External Noise (Wire or Sx) Reduced to Common Mode by Folding



 Line to Line Coupling Limited by Bit-Line Twisting




$V_t$  and DL Mis-Match Limited by Longer Channel Length

Overlay Mis-Alignment Limited by Identical Orientation

Capacitive Mis-Match Limited by careful Physical Design (Symmetry)
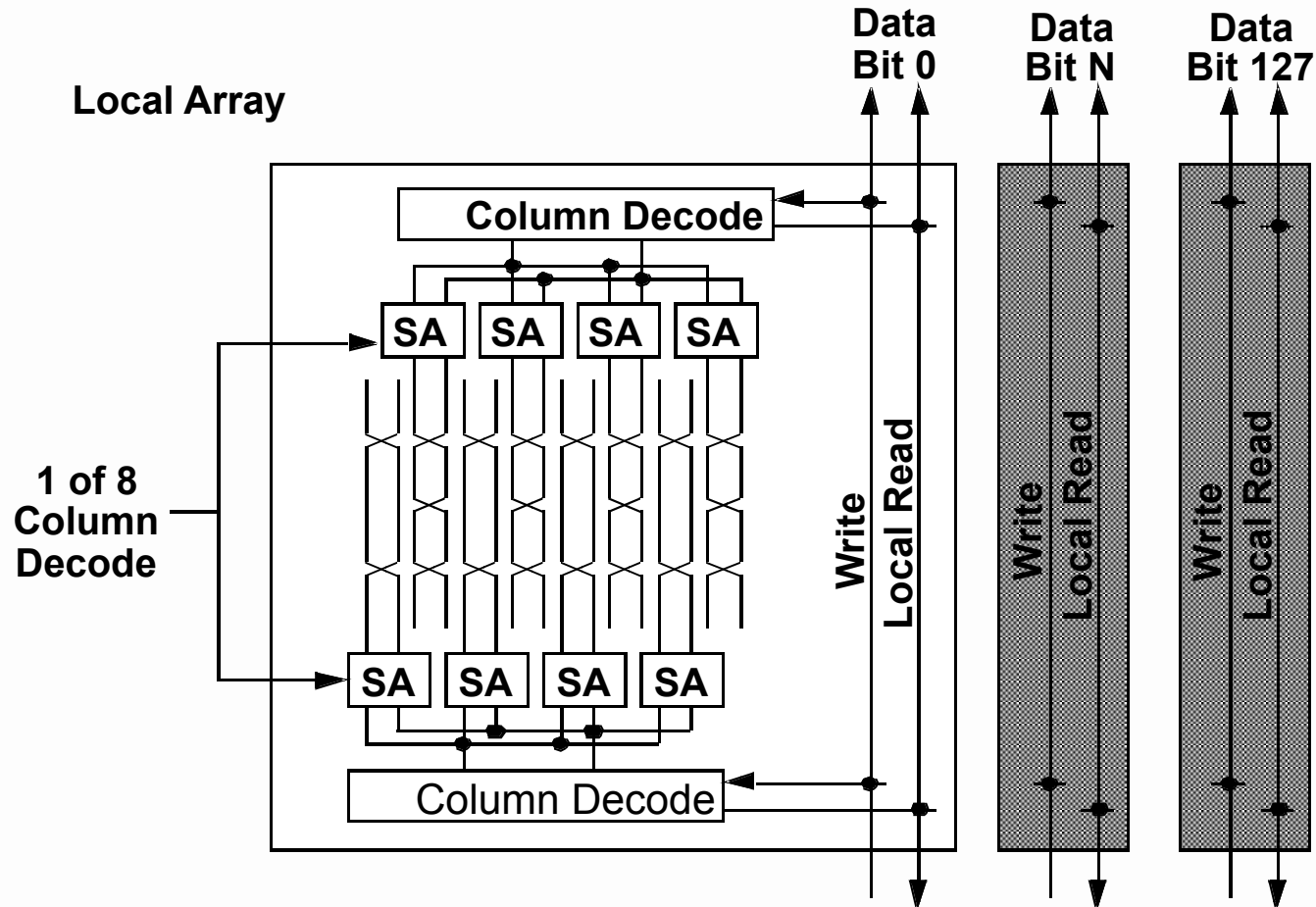
# Interleaved Sense Amp w/ Bit-Line Twist





# Open and Folded Bitline Schematic

 


FIGURE 12.44 Open bitlines

 


FIGURE 12.45 Folded bitlines

# Folded Bitline Layout


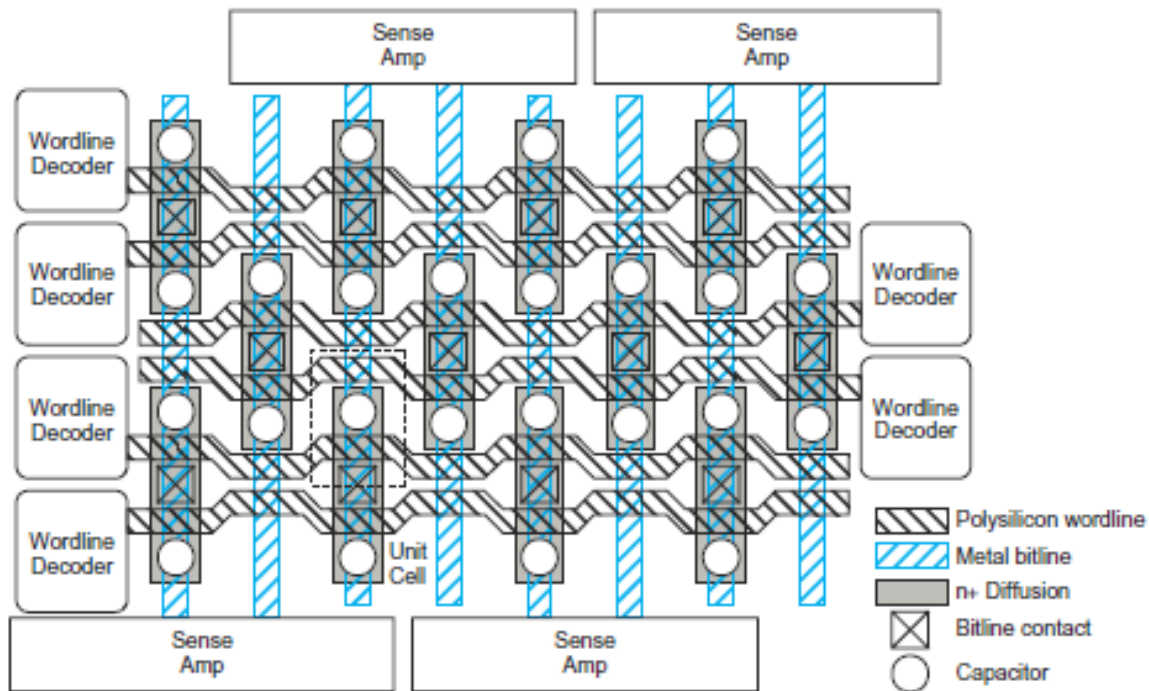


FIGURE 12.46 Layout of folded bitline subarray


# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example

# SRAM – Word-line Driver

 


# WL Capacitance Load

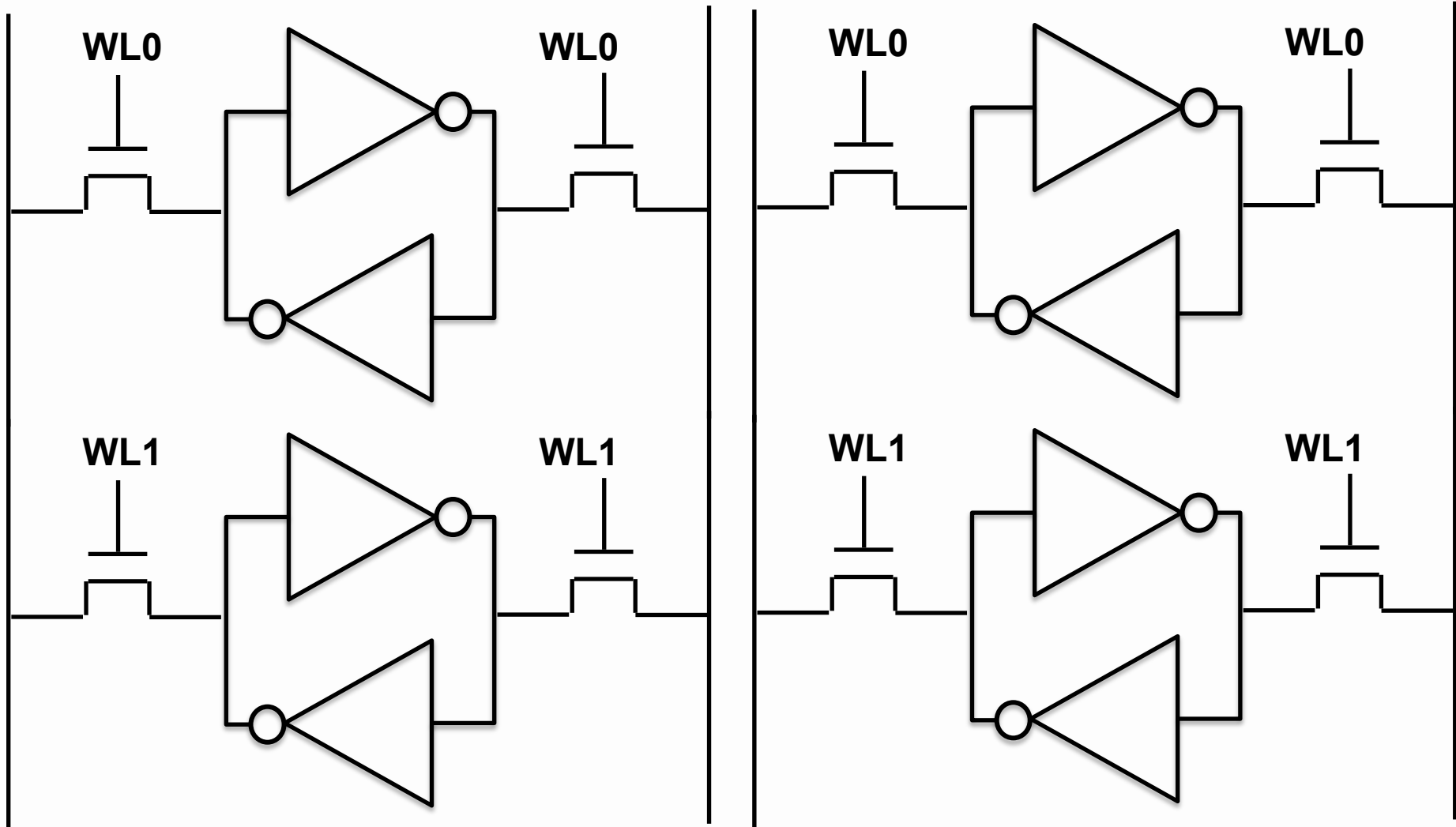

Large load capacitance = #DL x #Columns x Access Transistor Capacitance


# WL – Metal Capacitance Load

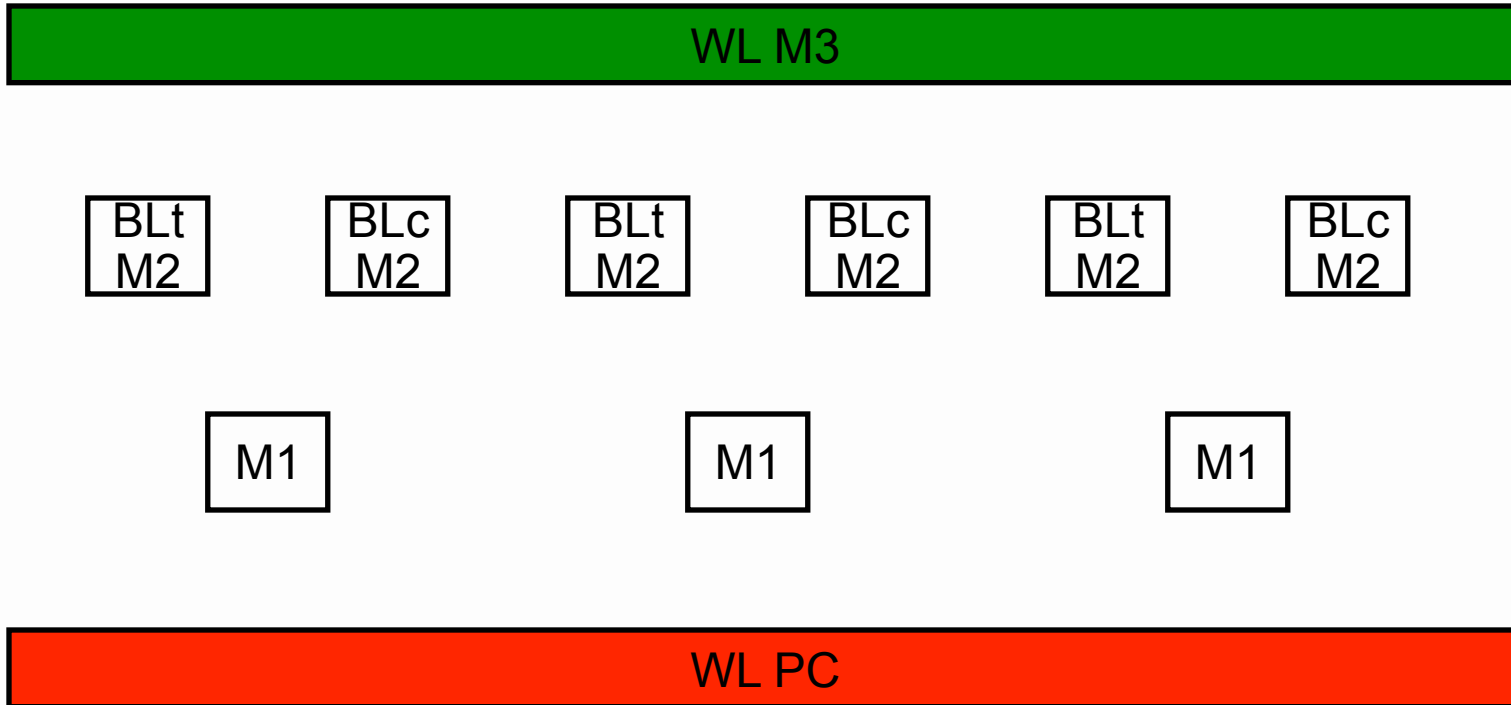

RC delay due to Metal 3 + Poly

Length = #DL x #Columns x width of each cell?


# WL – Metal Capacitance Load

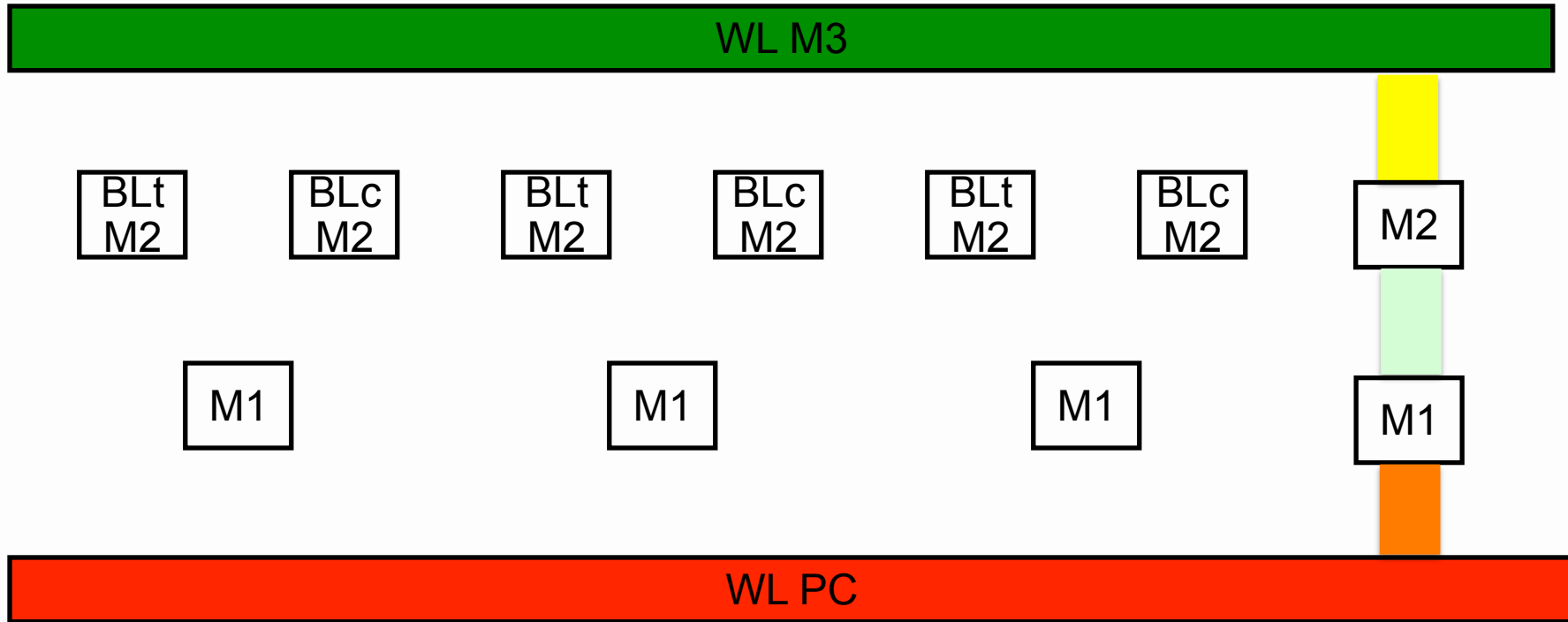

Stitch cell – Connect M3 to PC

Length > #DL x #Columns x width of each cell?


# Word Line Driver

 


- Need to drive a large load capacitance
- For SRAMs – It is nothing but a buffer
- Need to accommodate within y direction of a cell




# SRAM - WLDRV

 


# SRAM – Word-line Driver

 


# SRAM – Word-line Driver

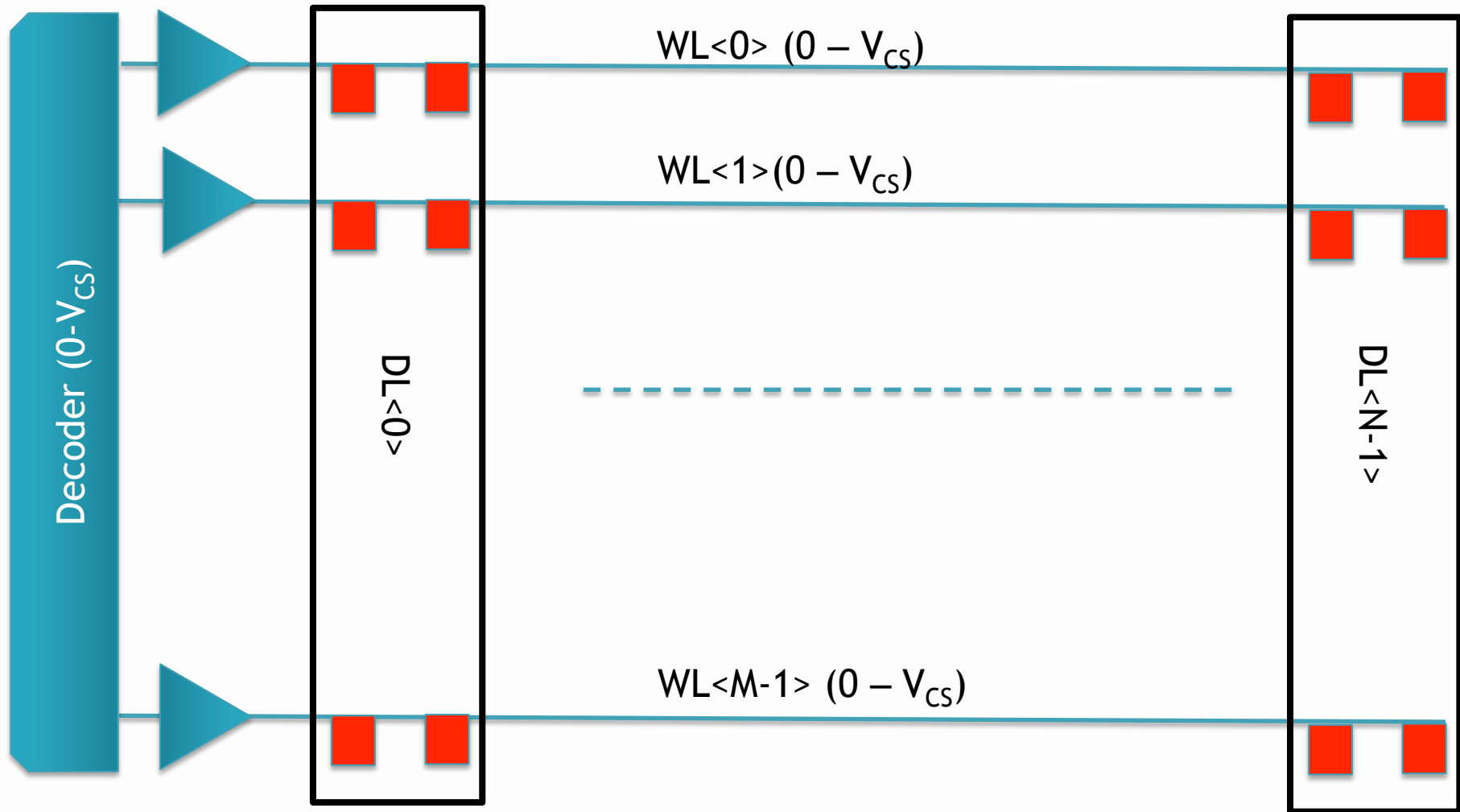

# eDRAM – Word-line Driver


 


# eDRAM - Word Line Driver

 


- Need to drive a large load capacitance
- Need to accommodate within  $y$  direction of a cell
- Need to level translate to  $V_{WL} - V_{PP}$  domain.


# Level Translator

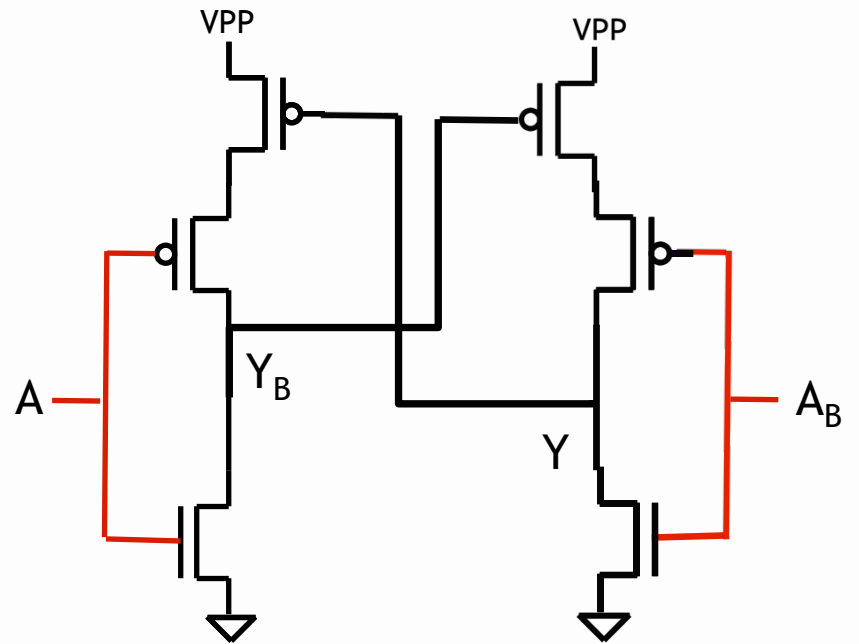 

# Level Translator

 


# Level Translator - Stress

 


- Need thick oxide transistors
  - Large Area
  - Does not track the logic transistor process
  - Hard to integrate with the array
- Need thin oxide WL drivers




# Level Translator - Stress

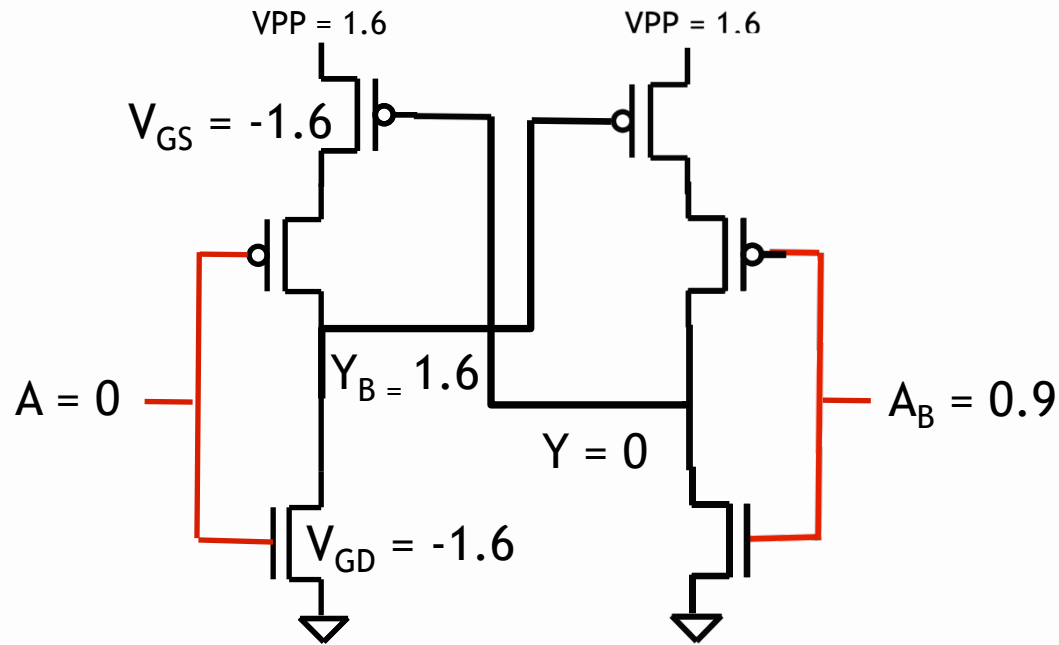


# Level Translator - Stress

 


# Protect Transistor

 


# Protect Transistor

 

# Protect Transistor

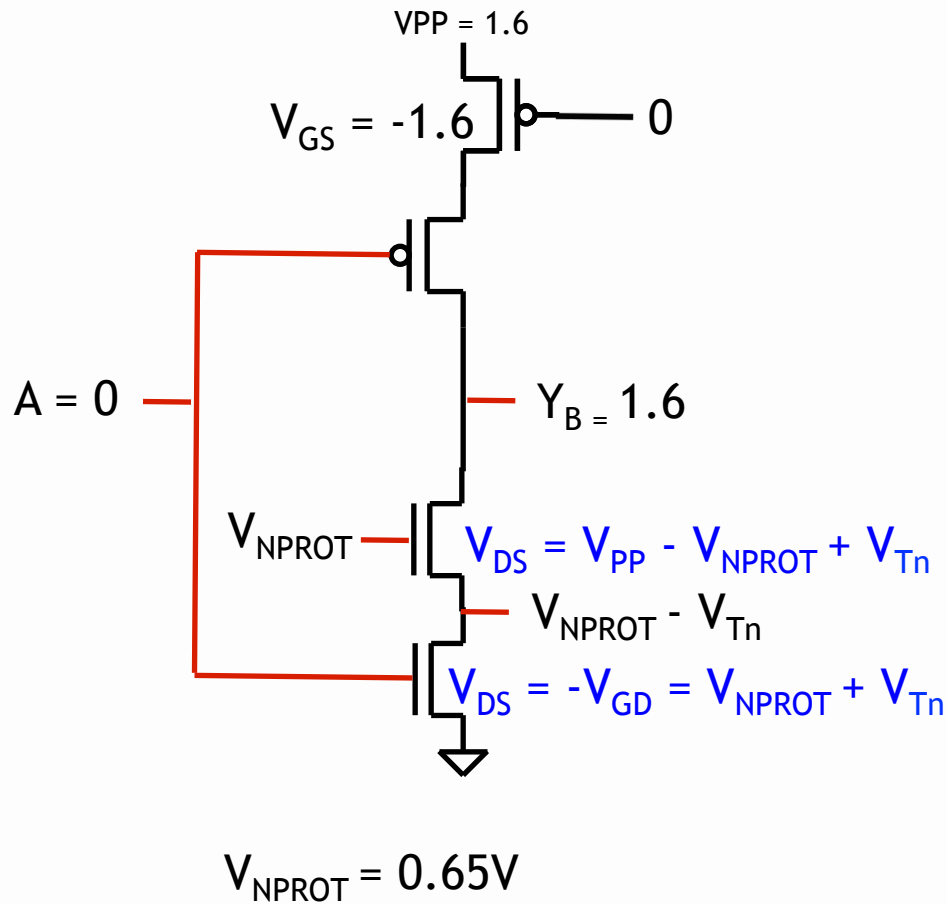


# eDRAM - Word Line Driver

 


- Start with the Final Stage
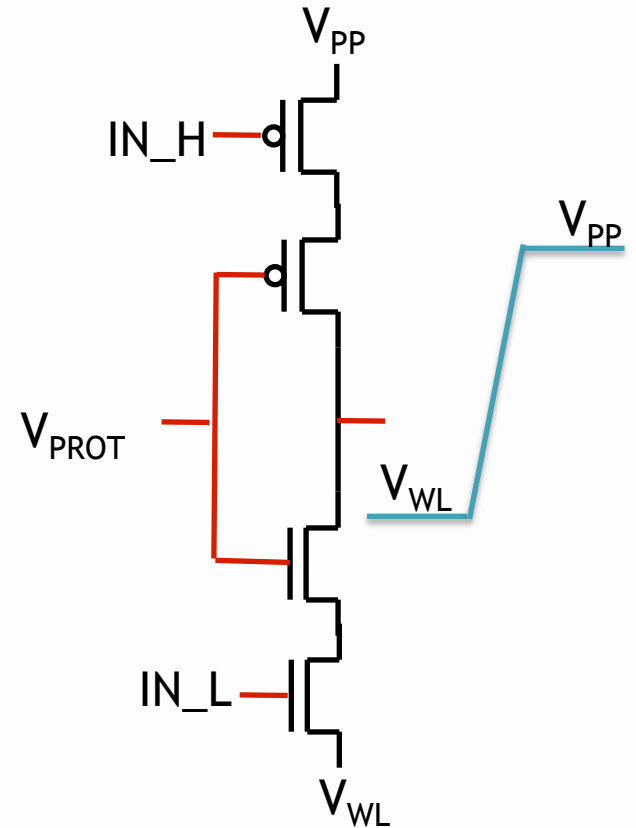
# WLD – Final Stage

$$V_{\text{PROT}} = (V_{\text{PP}} + V_{\text{WL}}) / 2$$




# WLD - Rise

 





# WLD - Fall

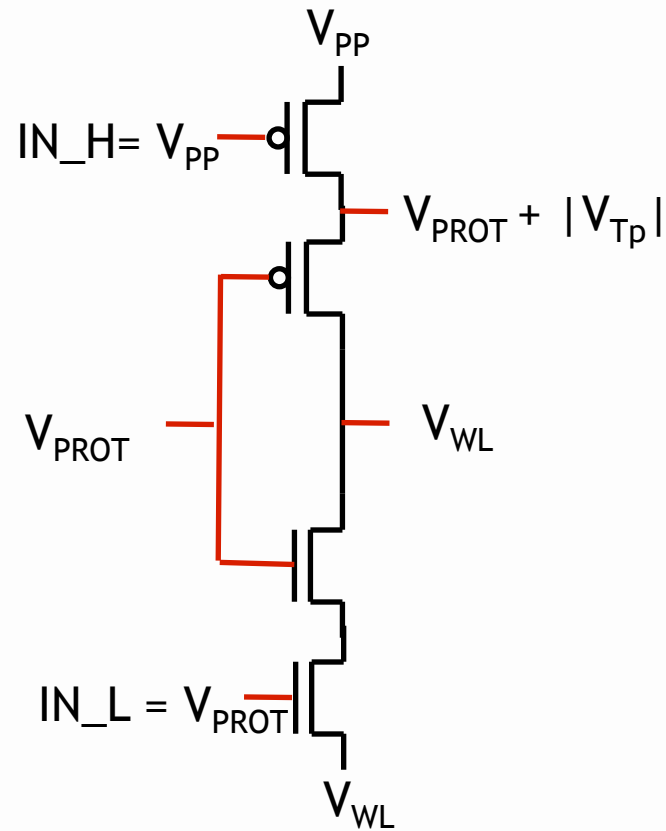


# Word-line Driver

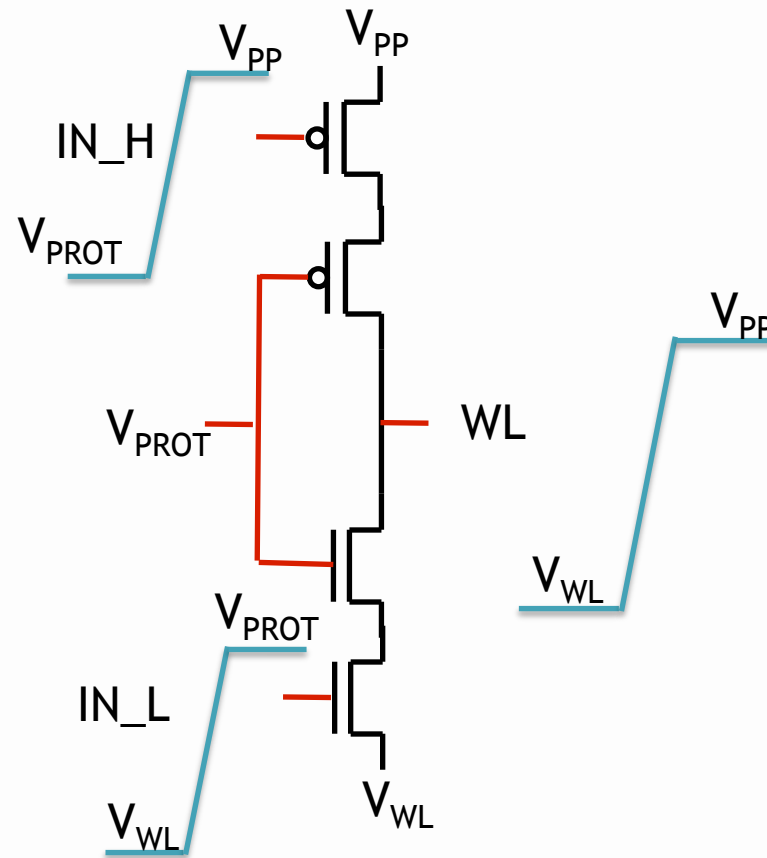


# Word-line System

 


# VWL - Level Translator

 



# VWL - Level Translator

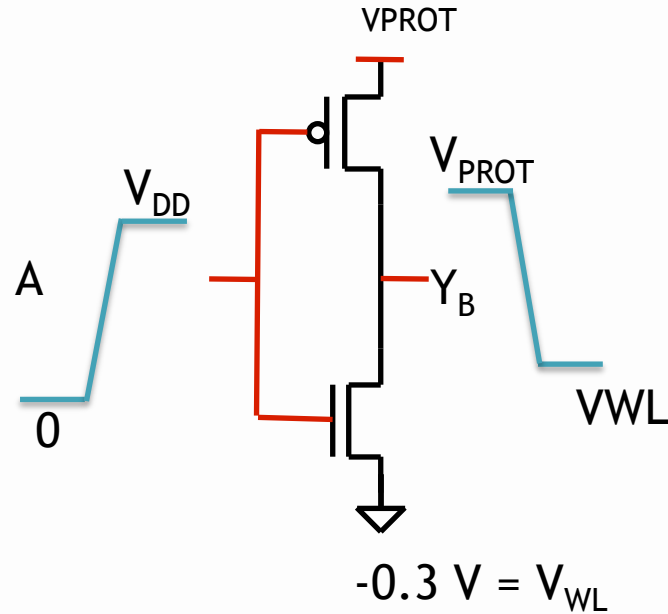


# VWL - Level Translator

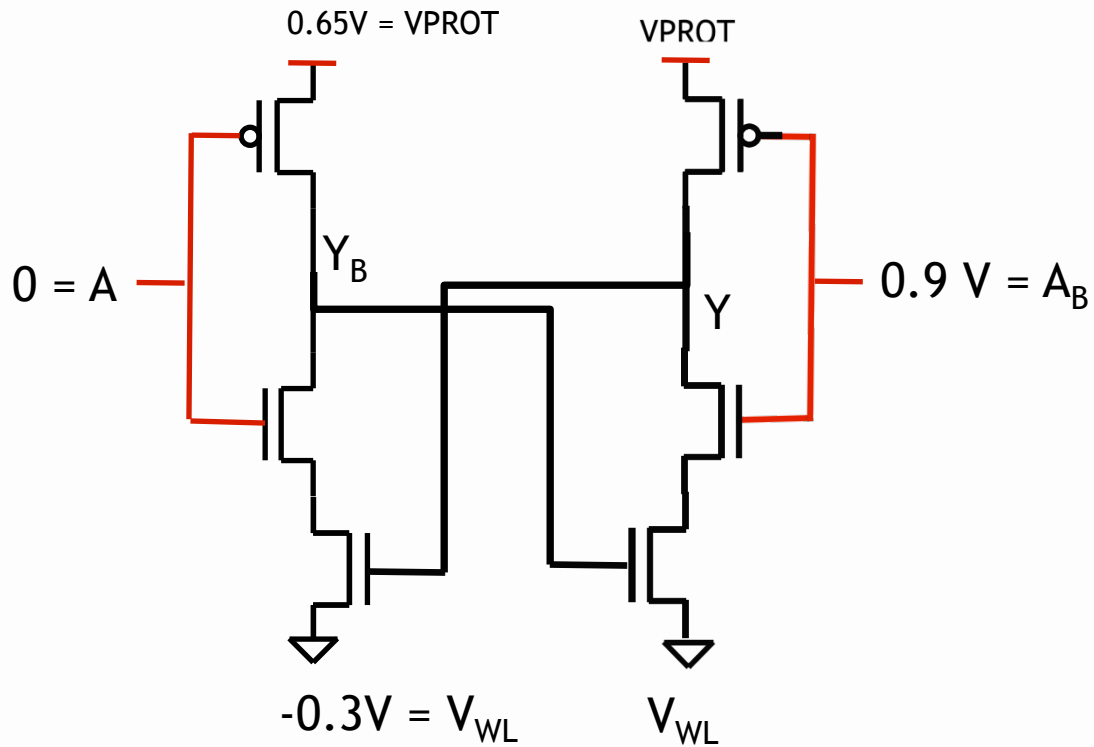

# VPP - Level Translator

 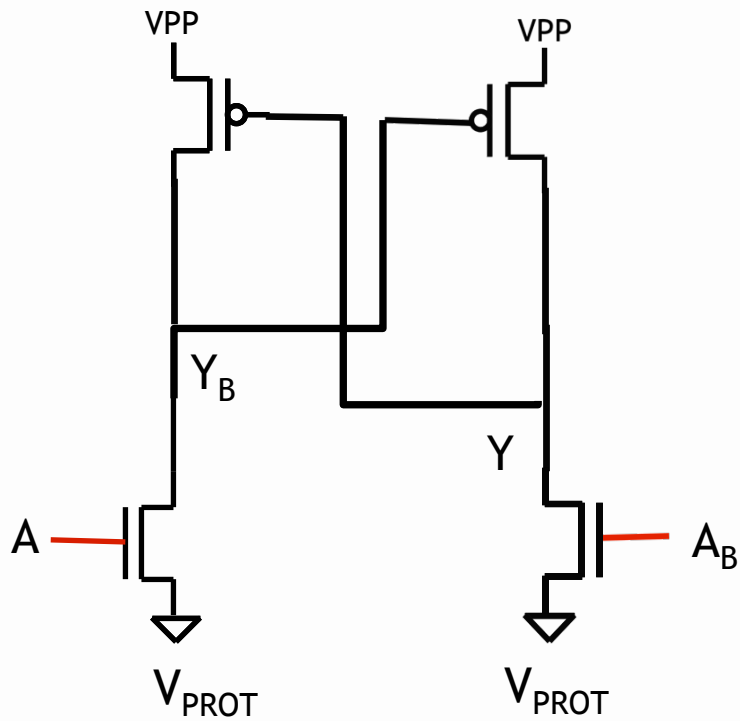


# VPP - Level Translator

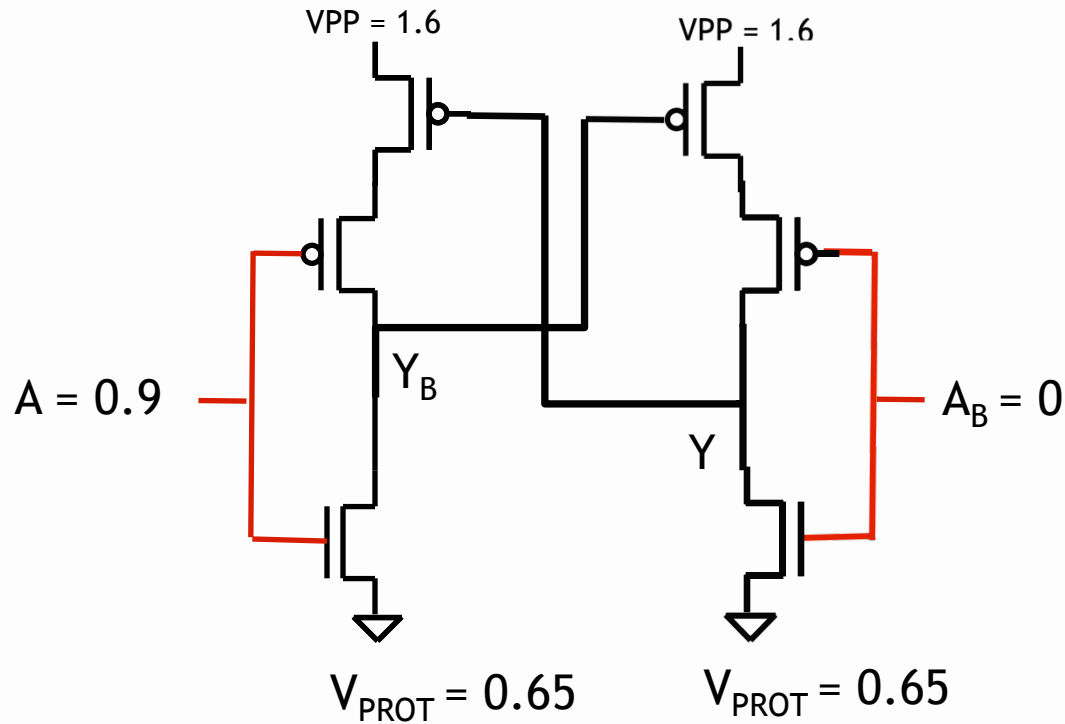





# VPP - Level Translator

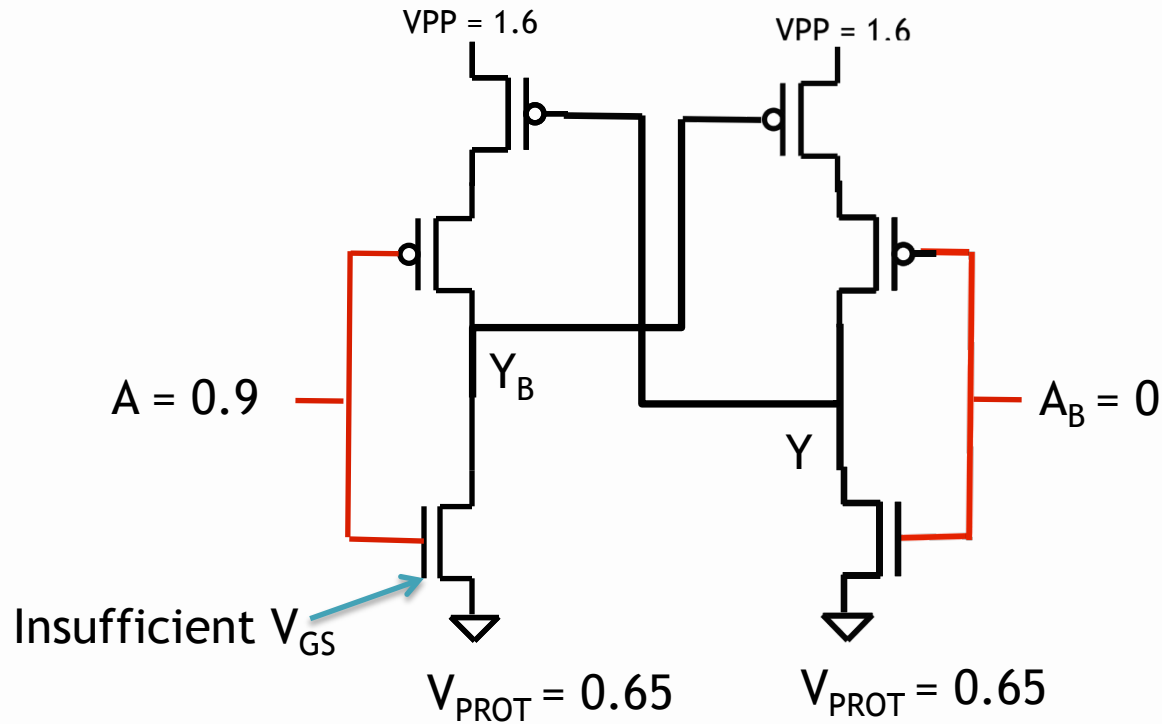


# VPP - Level Translator

 


# VPP - Level Translator

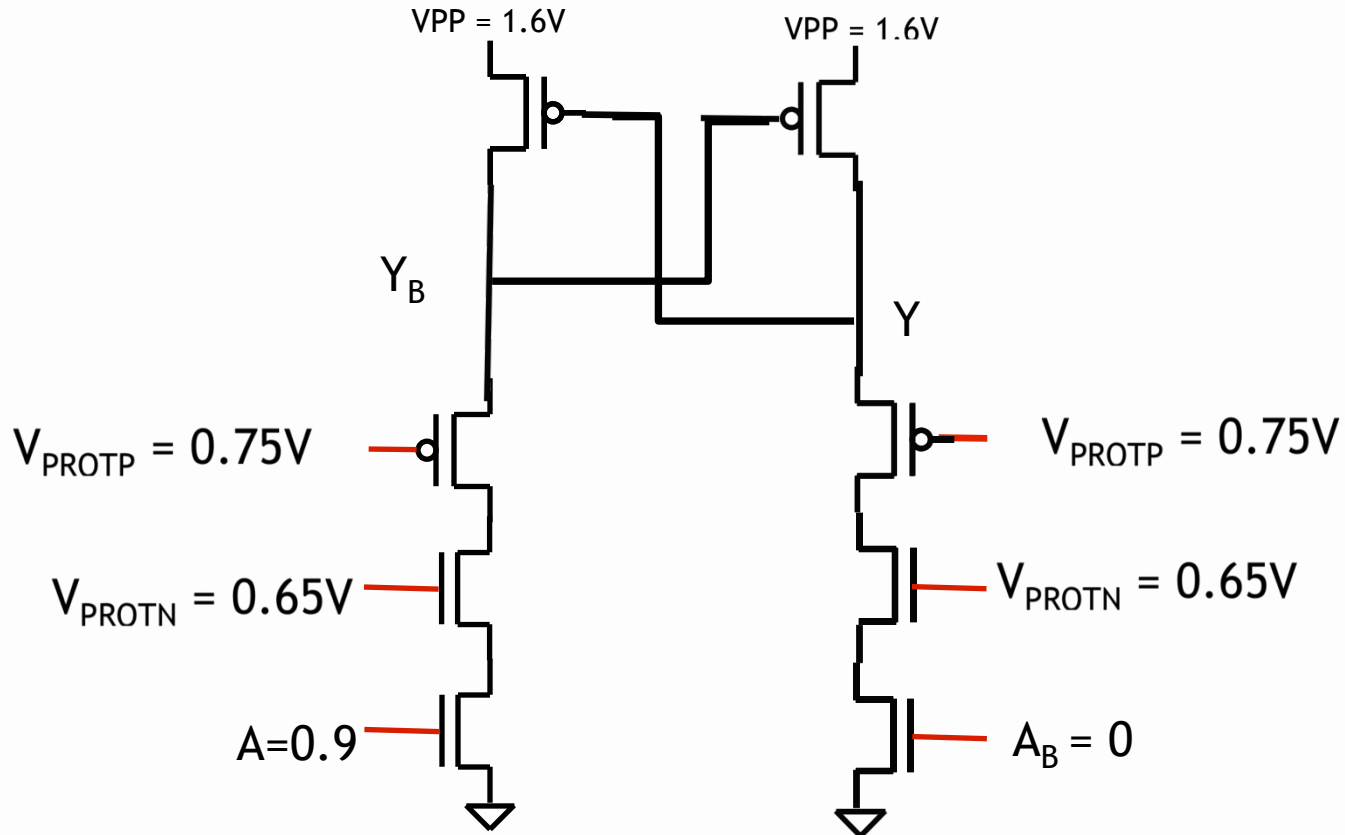


# VPP - Level Translator

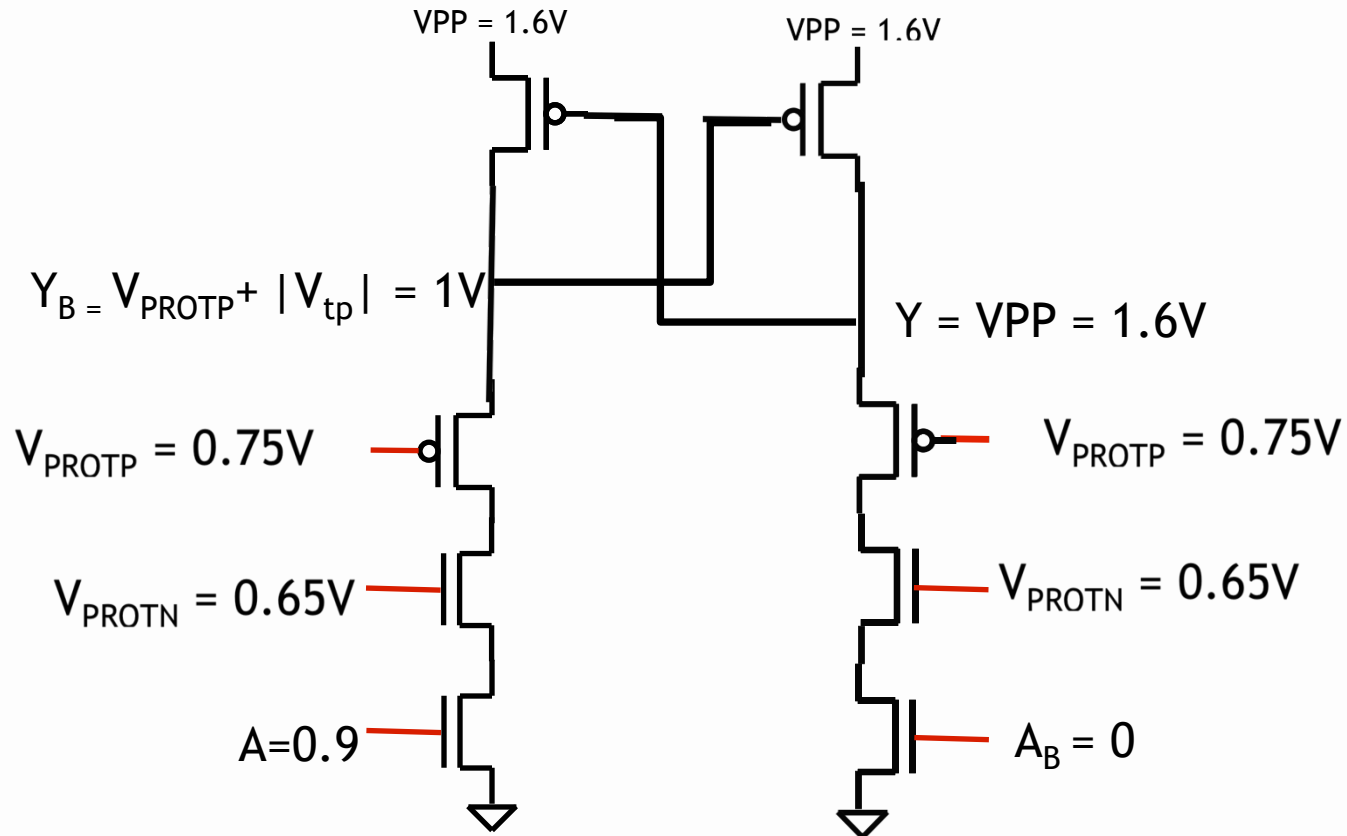

# VPP - Level Translator

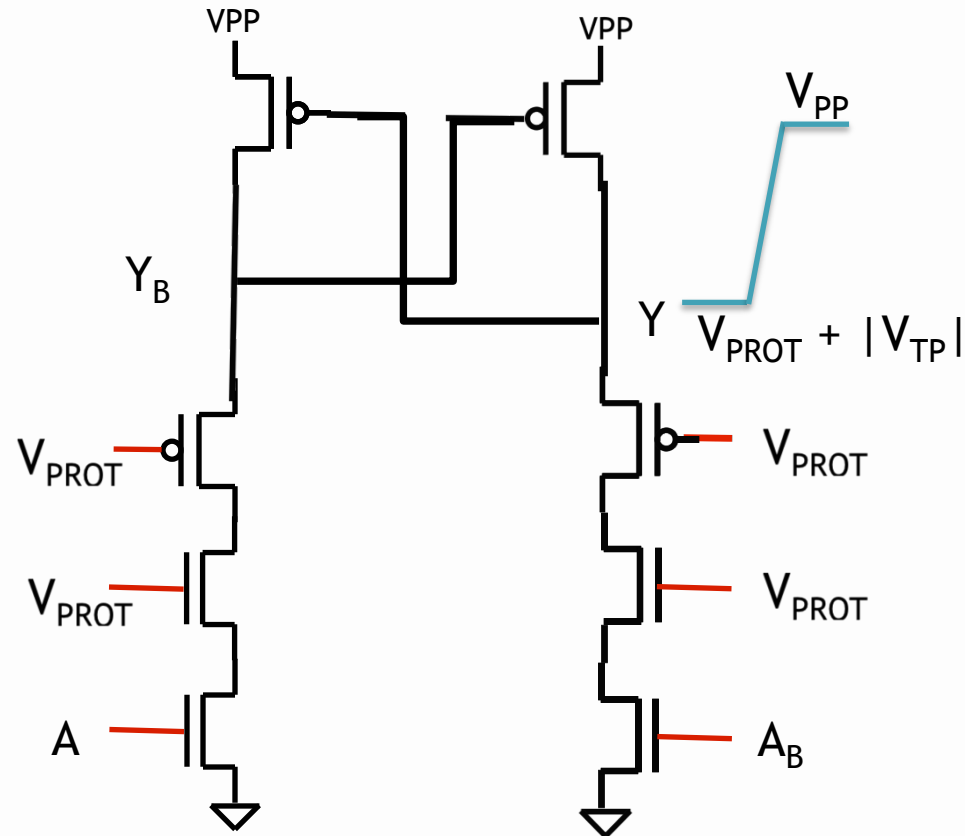

# Word-line System

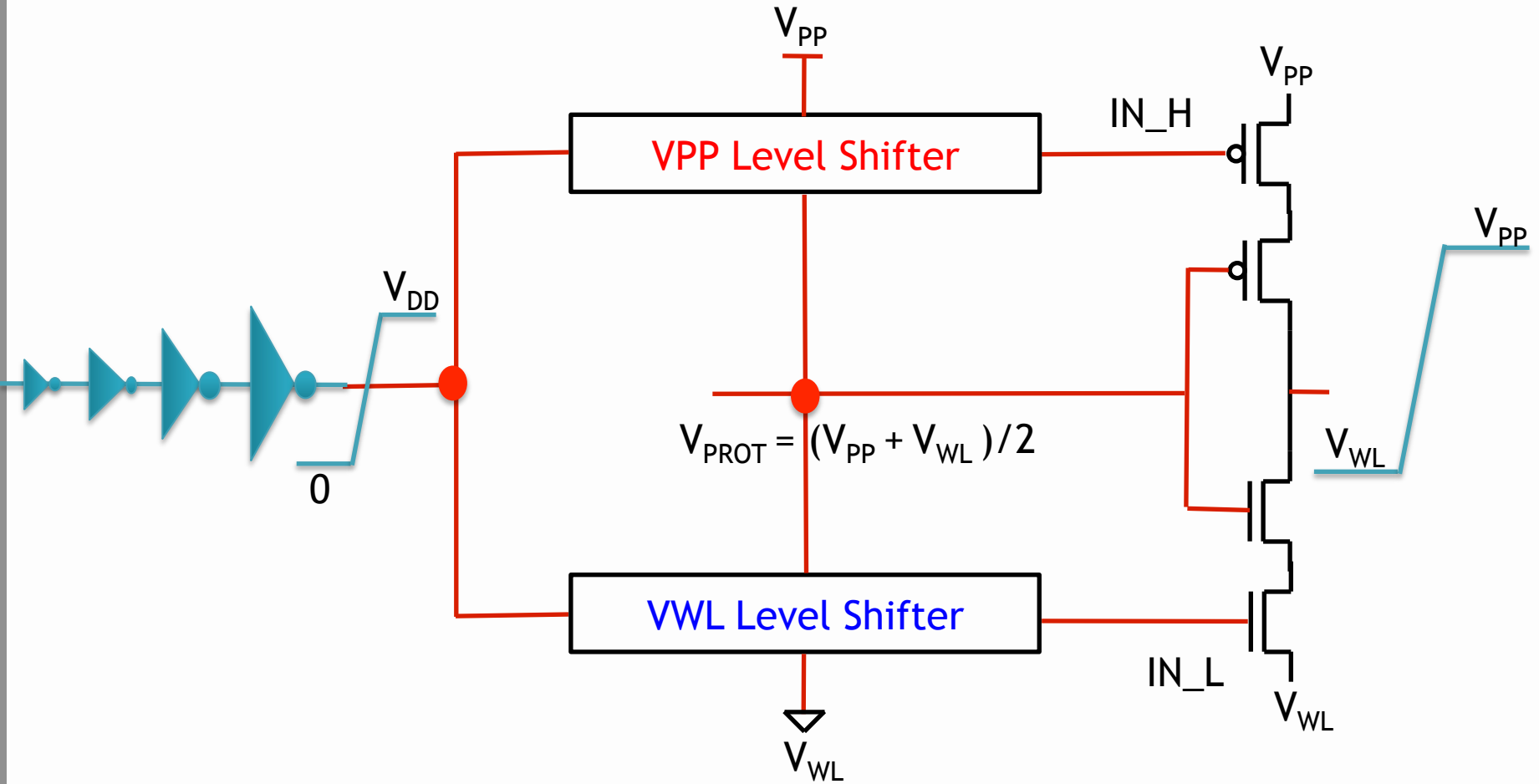


# WLDRV

Driver with Low voltage transistors → Logic transistors



No thick gate oxide transistors required!!

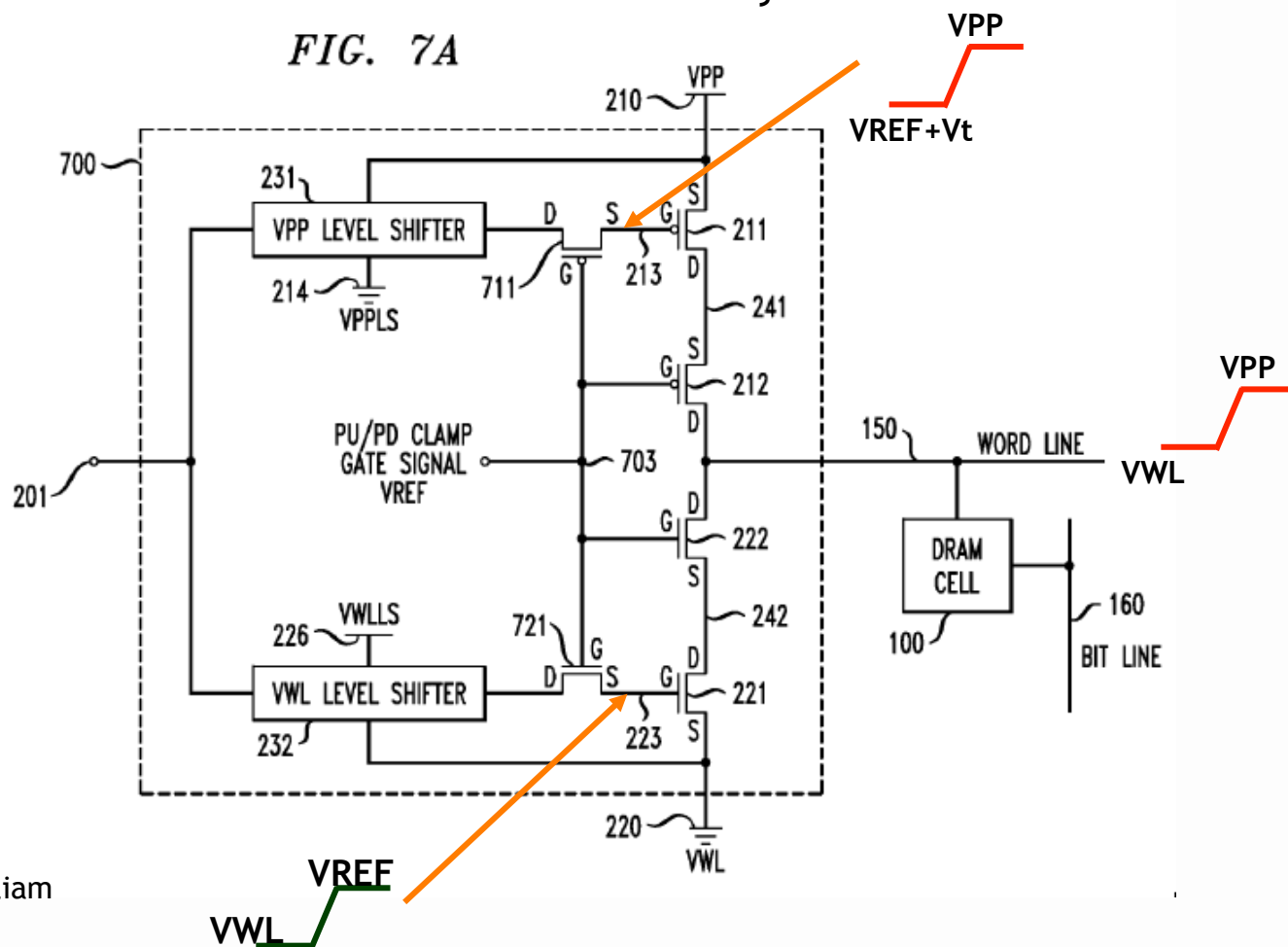Voltage across any two terminals should not exceed reliability limits



1. US patent No: 8,120,968 → William Robert Reohr, John E Barth
  
# Orthogonal WLD and pyramid wiring (M3/M4)





# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example

# Retention

Transfer Device and Storage Cap are NOT ideal devices: they LEAK

Leakage Mechanisms include:  $I_{off}$ , Junction Leakage, GIDL,...

Junction Leakage Temperature Dependence =  $2x/10C$

Cell Charge needs to be replenished (Refreshed), Median Retention Time:


$$T = \frac{CDV}{I_{leak}} = \frac{35fF \times 400mV}{2fA} = 7 \text{ seconds}$$

Where DV is acceptable loss  
C is Cell Capacitance  
 $I_{leak}$  is Total Leakage


Retention Distribution has Tails  
created by Defects and Leaky Cells

Weak Cells Tested out (5x Guardband)  
and replaced with Redundancy


Customer issues periodic Refresh Cycle

 


# Pass transistor leakage

 

# eDRAM vs. SRAM Cycle-Time Comparison

 

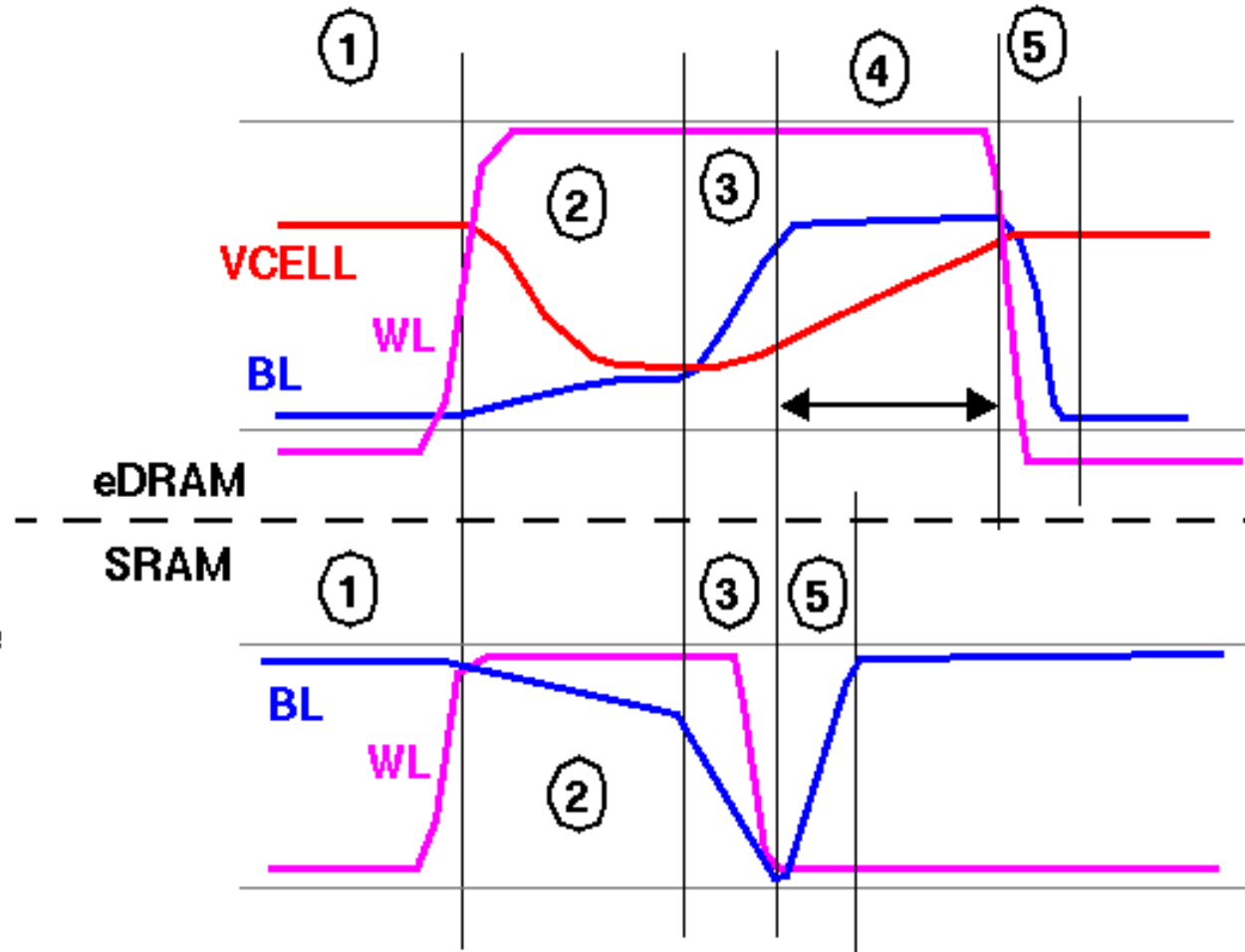1. WL Activation
2. Charge Transfer to Bit-Line  
( $I_{\text{READ}}$  Similar to SRAM)
3. Amplification
4. Write-Back
5. Precharge




**NET: SRAM Random Cycle will continue to lead!**

# Topics


- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example

# Logic Diagram of a Typical DRAM

 

- Control Signals (RAS\_L, CAS\_L, WE\_L, OE\_L) are all active low
- Din and Dout are combined (D):
  - WE\_L is asserted (Low), OE\_L is disasserted (High)
    - D serves as the data input pin
  - WE\_L is disasserted (High), OE\_L is asserted (Low)
    - D is the data output pin
- Row and column addresses share the same pins (A)
  - RAS\_L goes low: Pins A are latched in as row address
  - CAS\_L goes low: Pins A are latched in as column address
  - RAS/CAS edge-sensitive

# DRAM logical organization (4 Mbit)


 


◦ Square root of bits per RAS/CAS

Din Dout can be clubbed together with a BiDi buffer
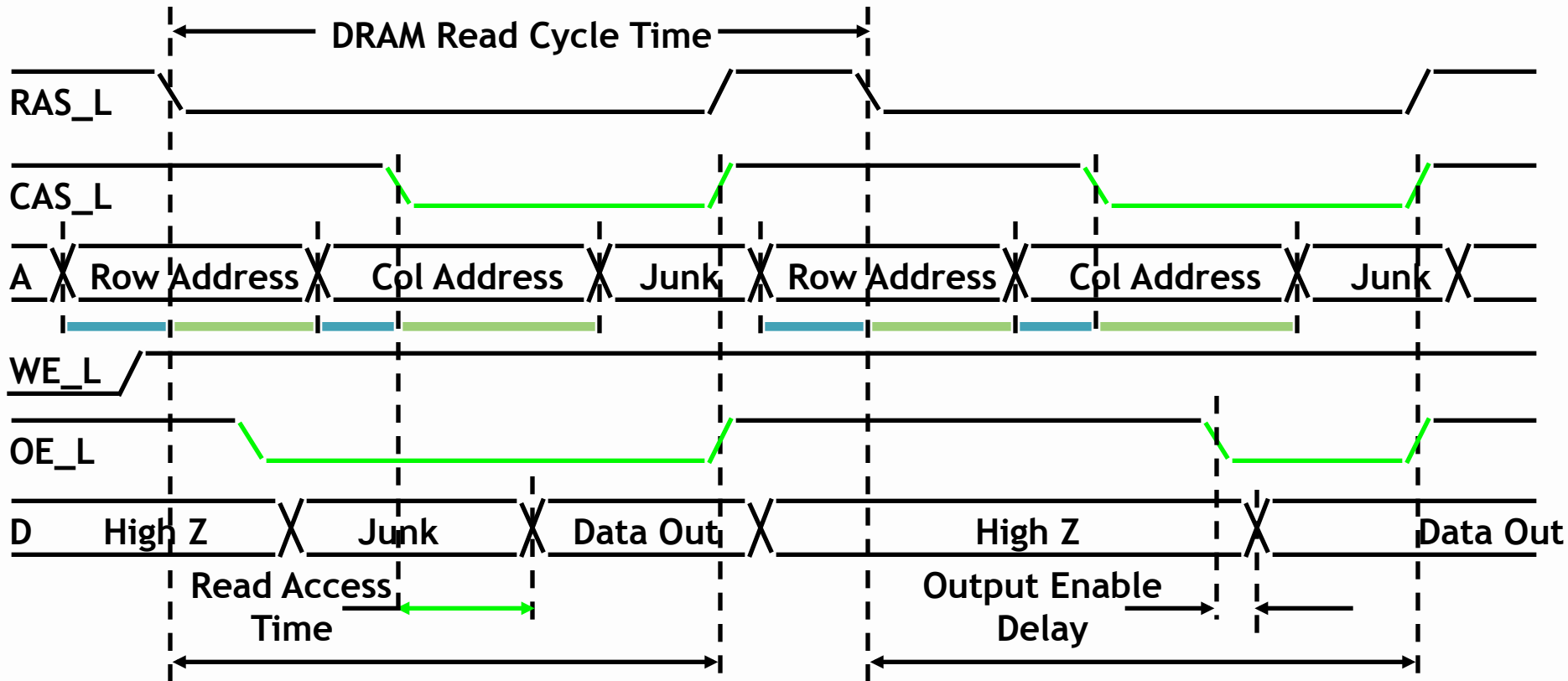 
# DRAM Read Timing

- Every DRAM access begins at:
  - The assertion of the RAS\_L
  - 2 ways to read:
    - early or late v. CAS




Early Read Cycle: OE\_L asserted before CAS\_L    Late Read Cycle: OE\_L asserted after CAS\_L


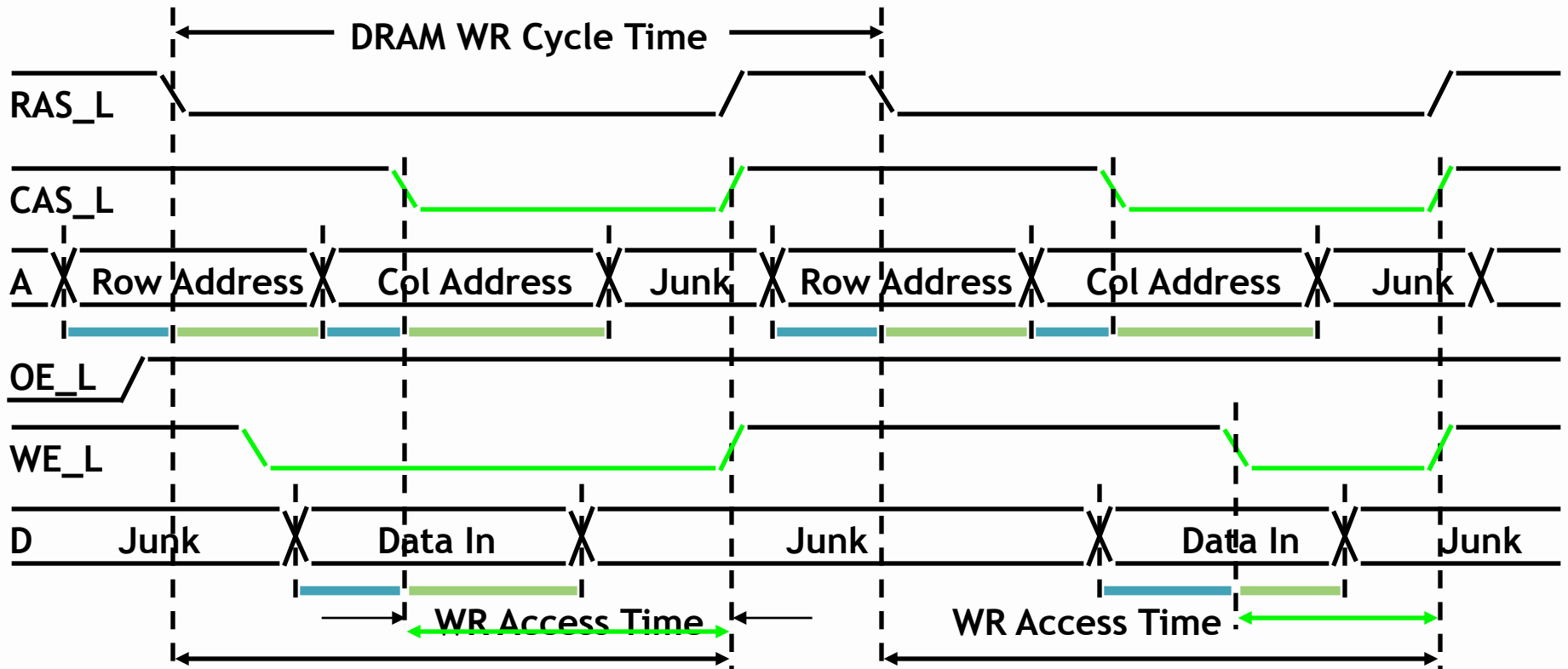
# DRAM Write Timing

- Every DRAM access begins at:
  - The assertion of the RAS\_L
  - 2 ways to write:
    - early or late v. CAS



Early Wr Cycle: WE\_L asserted before CAS\_L

Late Wr Cycle: WE\_L asserted after CAS\_L


# A Fast Area Efficient Sense-Amp (Case Study)

G. Fredeman et al., “A 14 nm 1.1 Mb Embedded DRAM Macro With 1 ns Access,”  
in IEEE Journal of Solid-State Circuits, vol. 51, no. 1, pp. 230-239,  
Jan. 2016. doi: 10.1109/JSSC.2015.2456873


# Problems with Micro Sense Amp

- ❑ By default the Sense Amp reads a 0
- ❑ Access transistor has to pull the LBL HIGH to read 1
  - ❑ Asymptotic charge up to High since  $V_{gs}$  keeps reducing
  - ❑ Very slow by nature
  - ❑ Need to minimize the WLS per BL(33) for performance reasons
- ❑ Cannot pre-charge LBL to High
  - ❑ Floating Body Effect affects retention
- ❑ NMOS (Access Device) is very fast when pulling down to zero
  - ❑ Can we make a Sense Amp that reads a one by default?
  - ❑ This will allow more WLS per BL

# LBL Pre-charge vs Pre-discharge

 


# Basic Structure

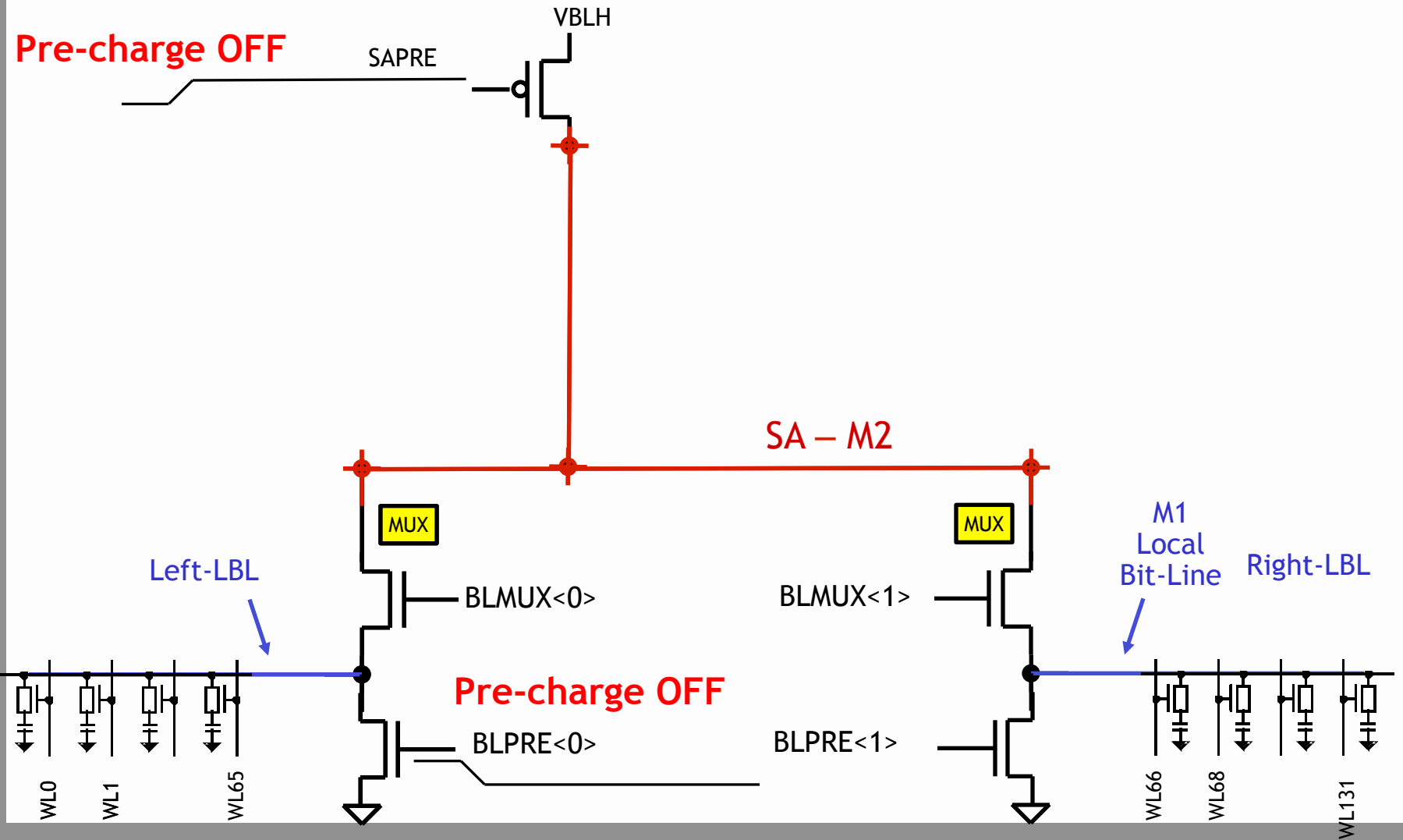


# Gated Feedback Sense Amp

Sense Amp

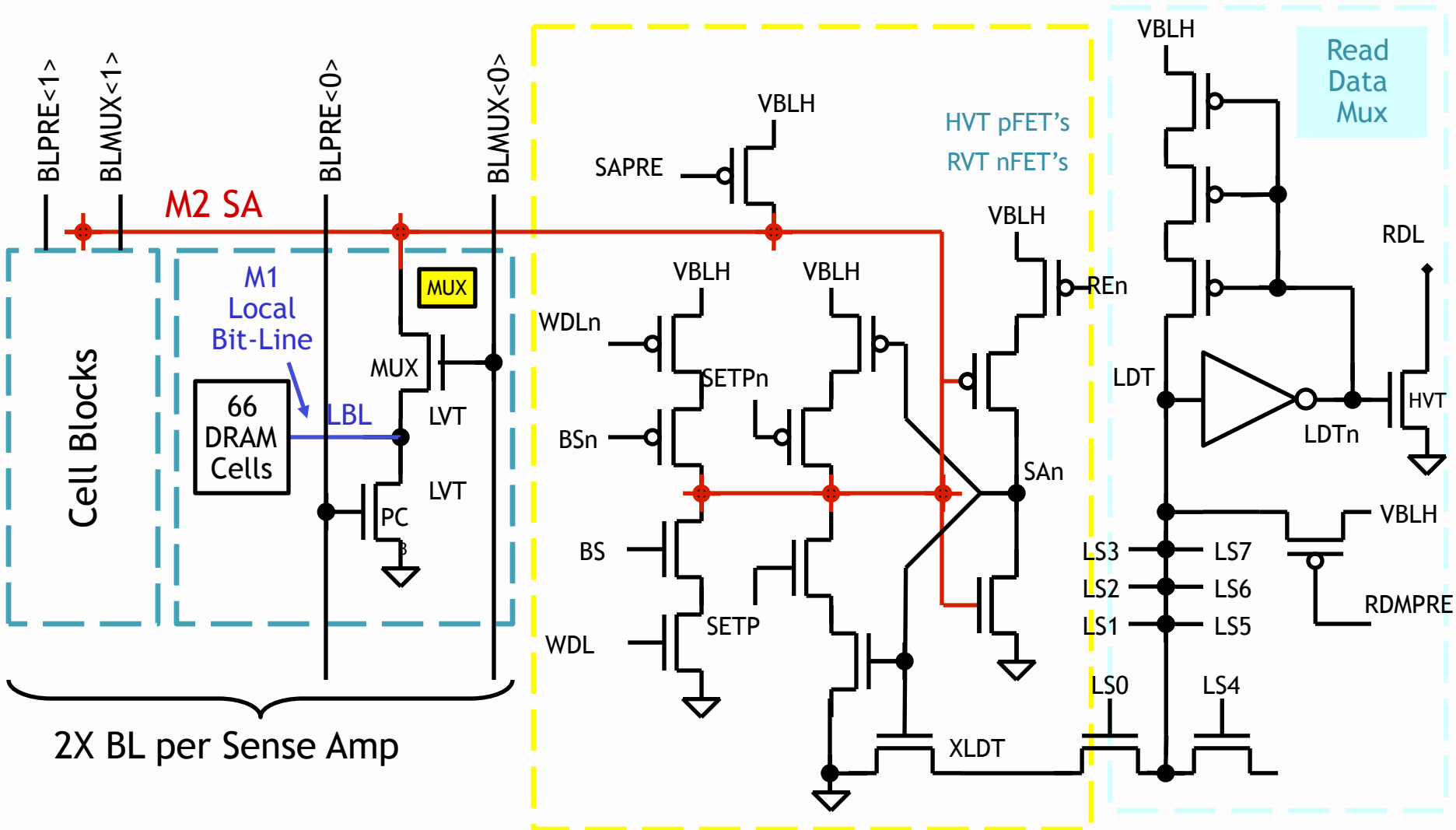


# Gated Feedback Sense Amp - Construction

READ-1

 


READ-0

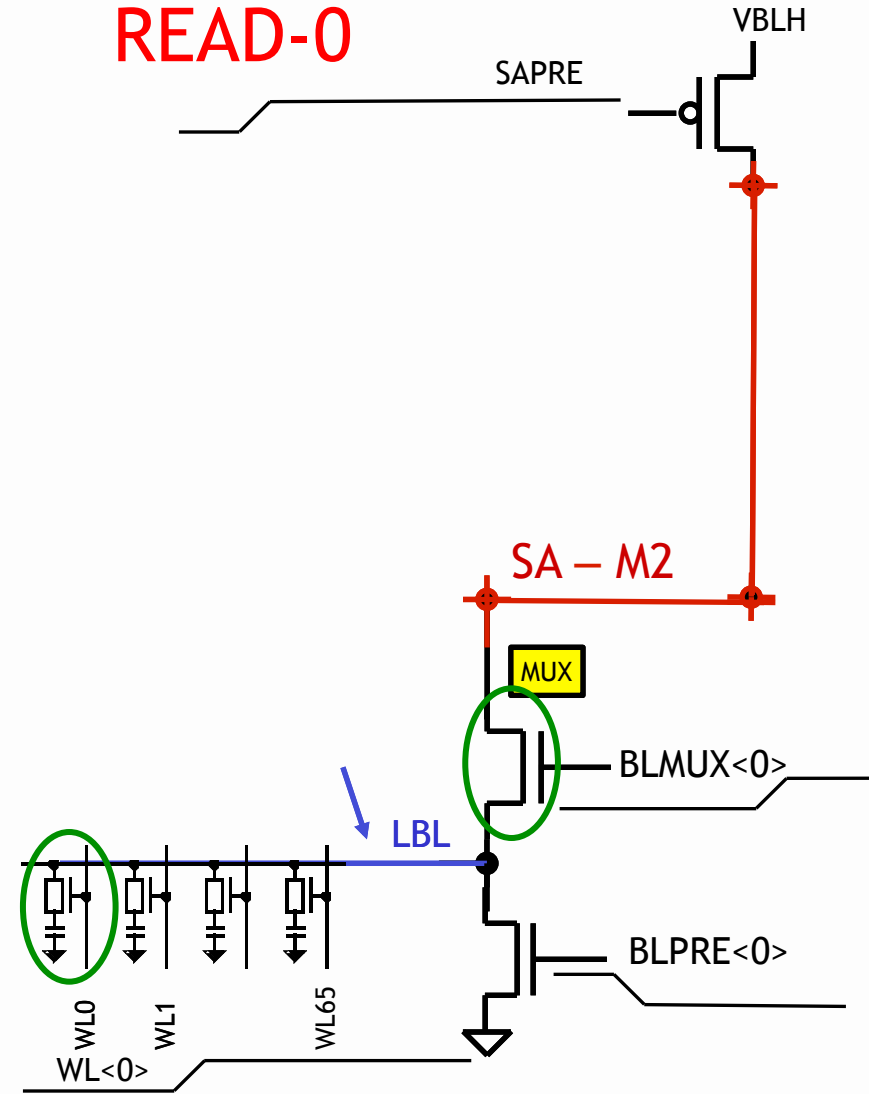


Animation

# Gated Feedback Sense Amp - Construction

READ-1

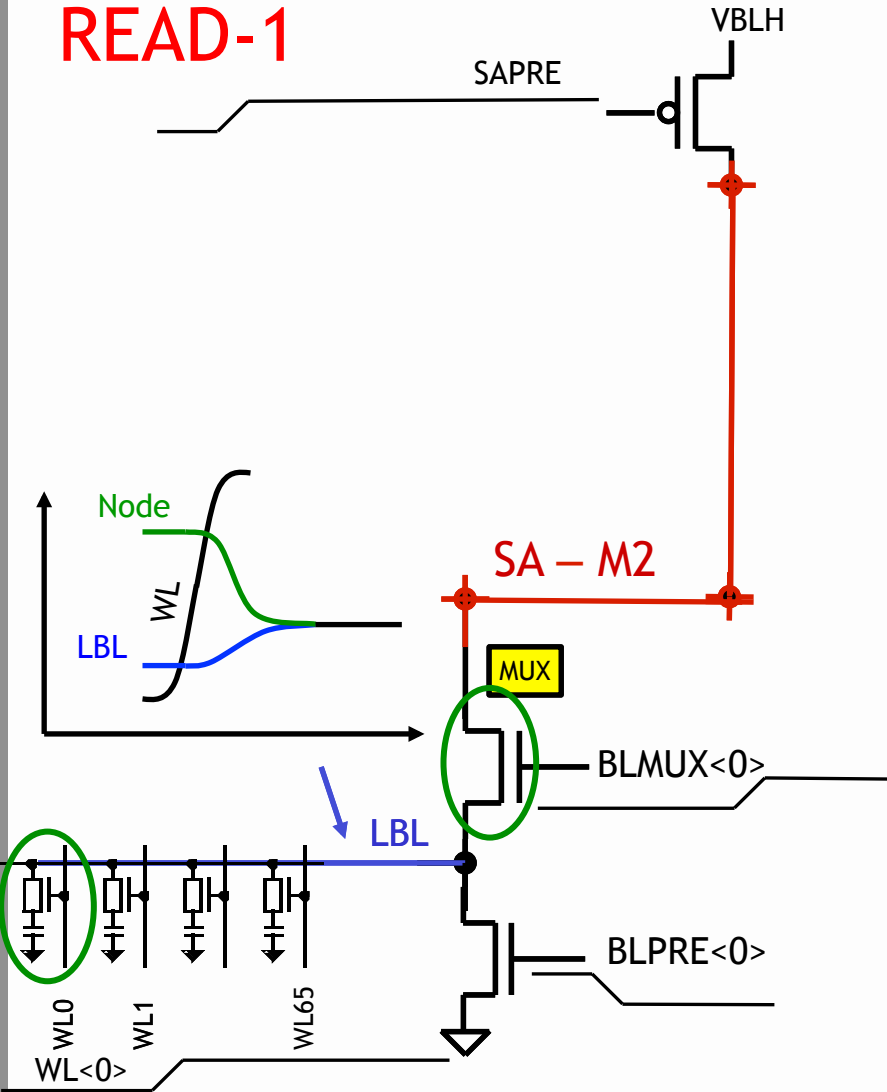

READ-0

 


Animation




# Gated Feedback Sense Amp - Construction

**READ-1**

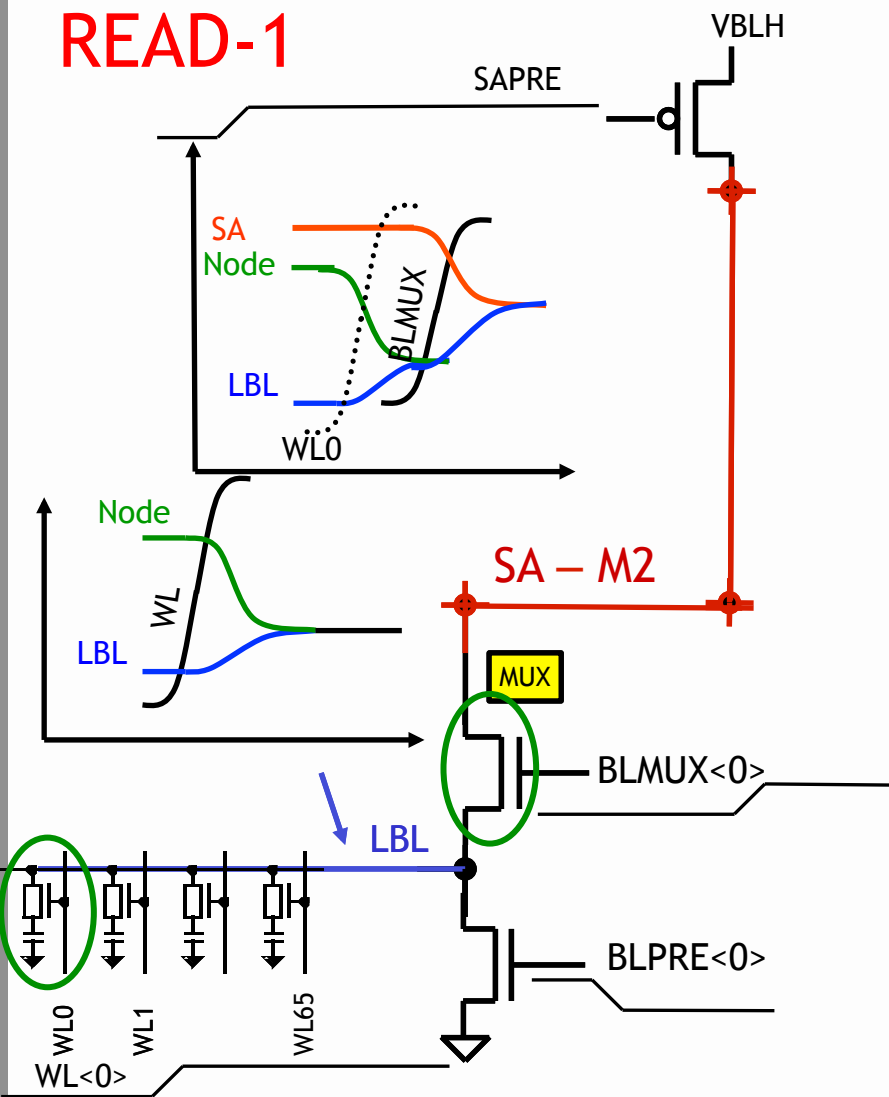


**READ-0**

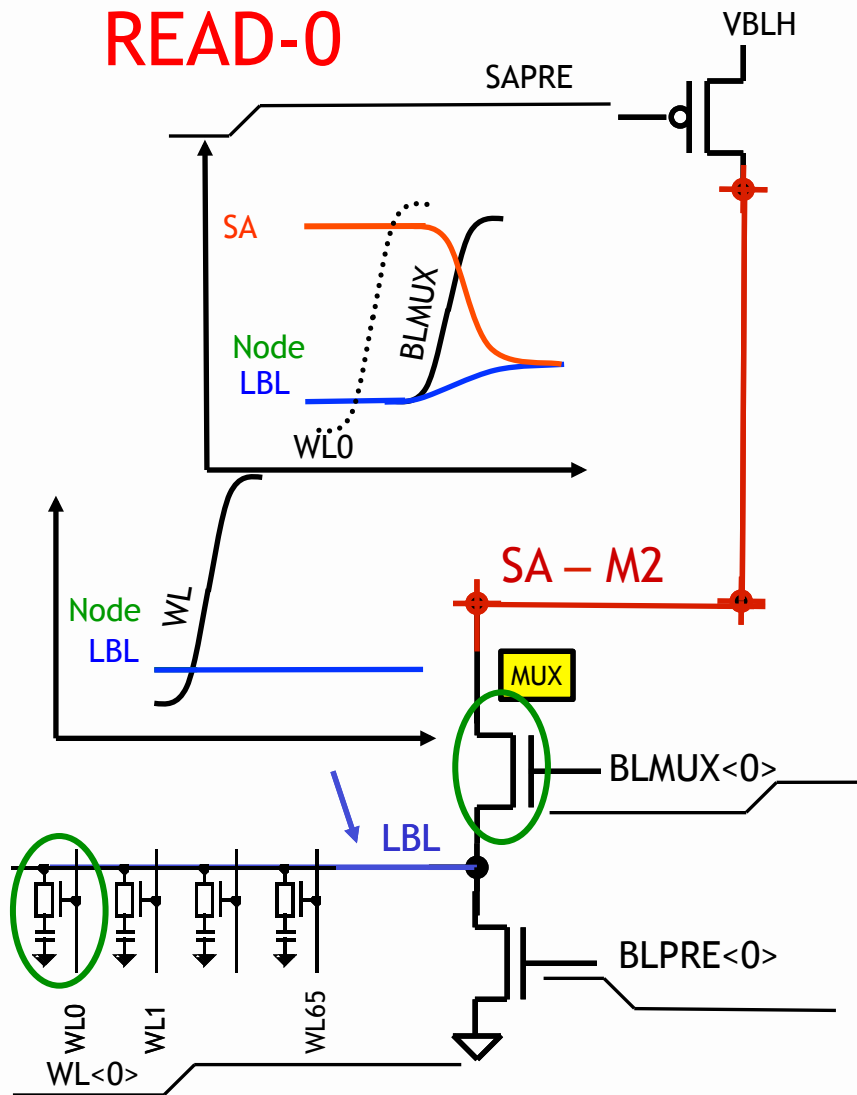


Animation

# Gated Feedback Sense Amp - Construction

**READ-1**

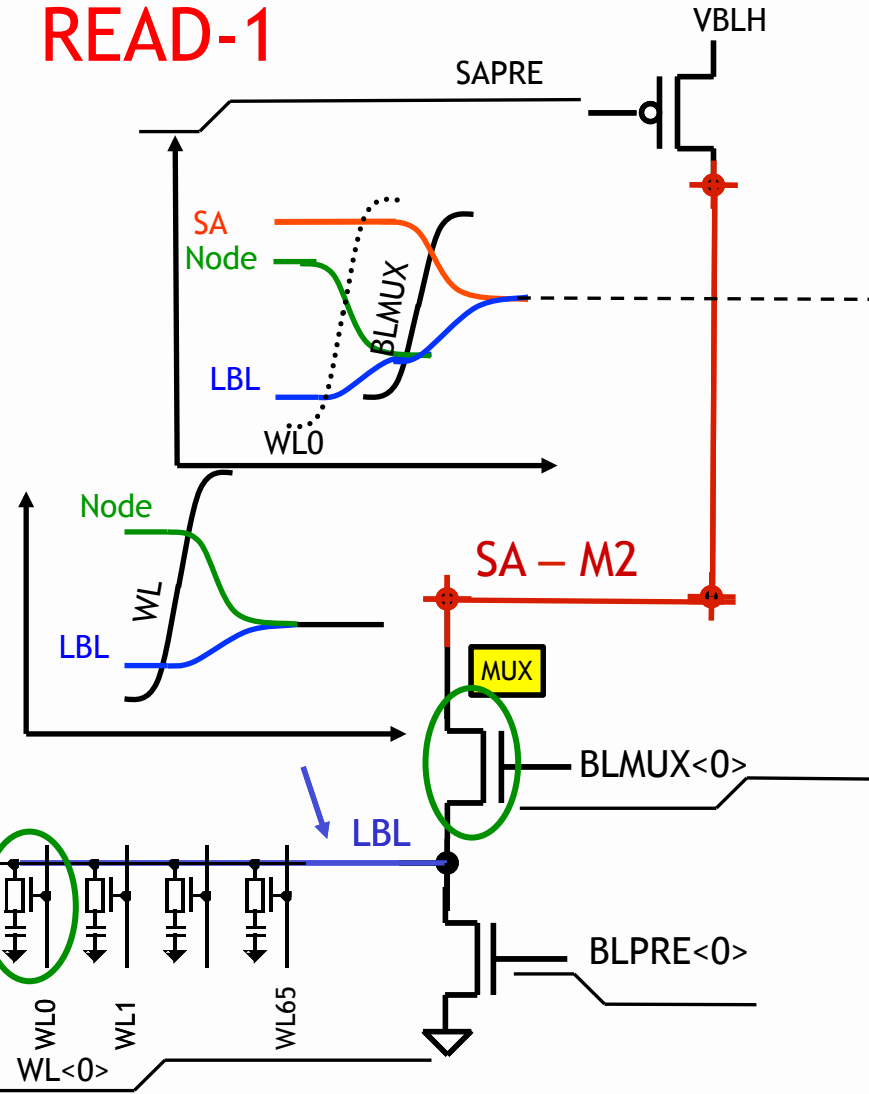


**READ-0**

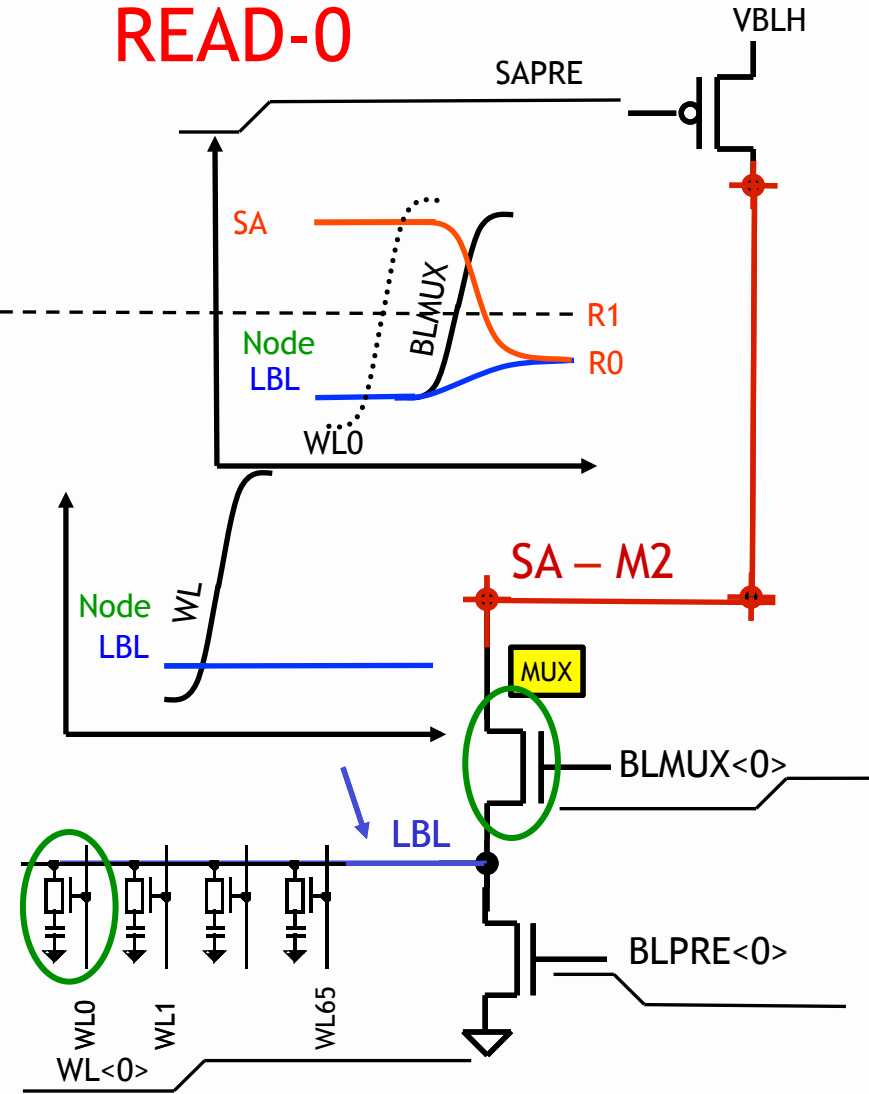


Animation
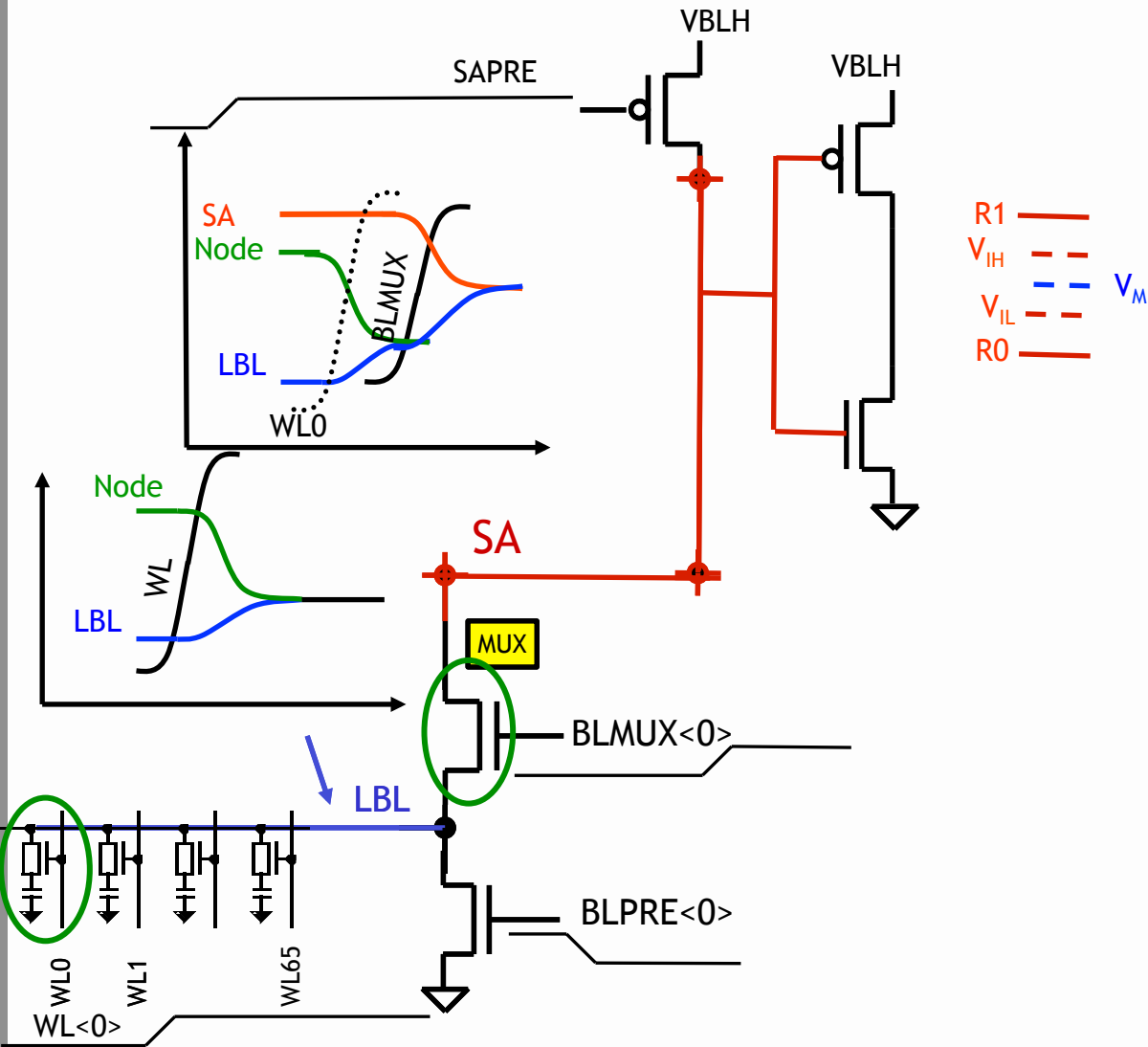
# Gated Feedback Sense Amp - Construction




Animation
 
# Gated Feedback Sense Amp - Construction




Animation
 
# Gated Feedback Sense Amp - Construction




Animation
 
# Gated Feedback Sense Amp - Construction




Animation
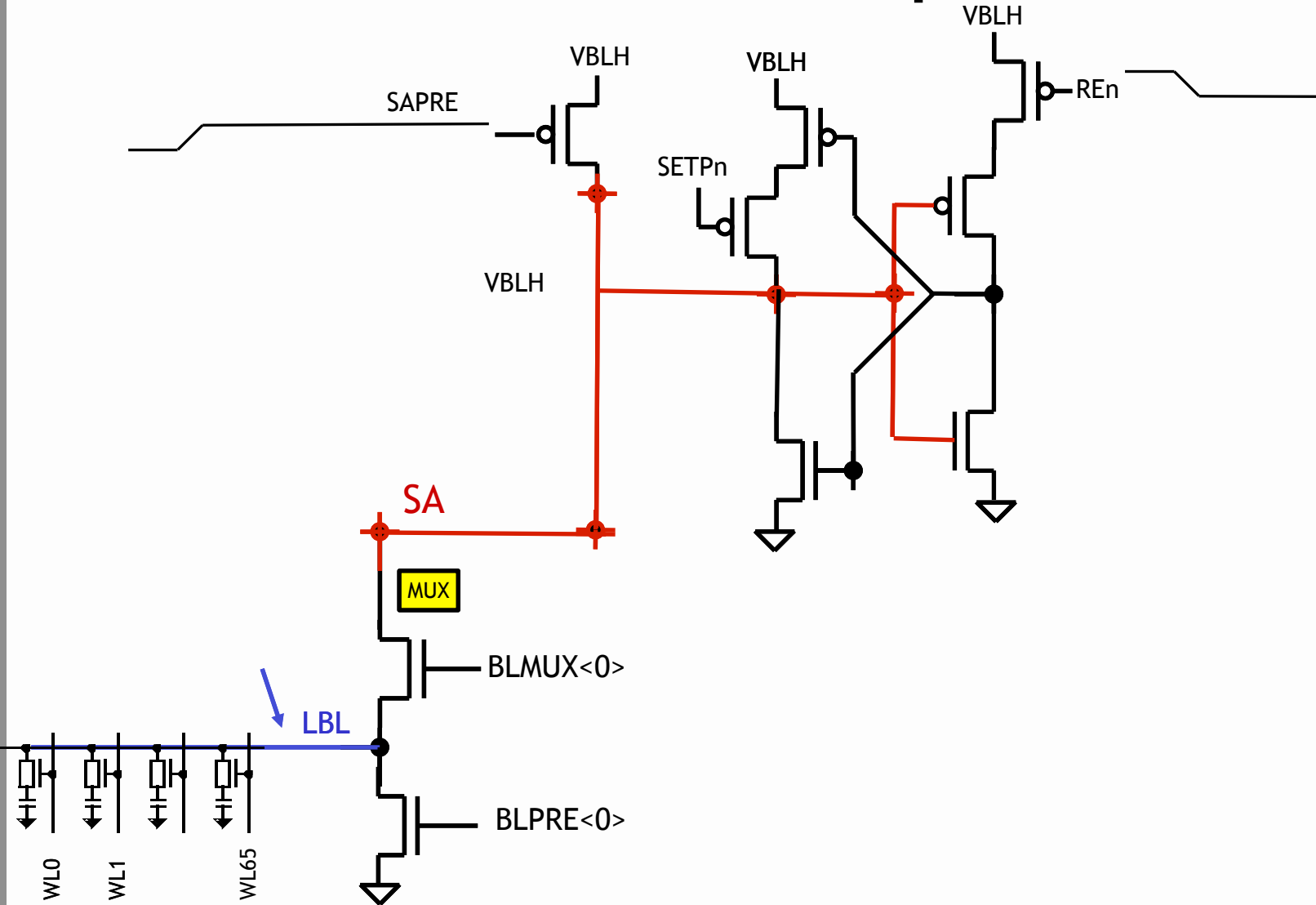
# Gated Feedback Sense Amp - Construction



Animation

 
# Gated Feedback Sense Amp - Construction



Timing of  $SETPn$  is critical



 
# Gated Feedback Sense Amp - Construction




Animation
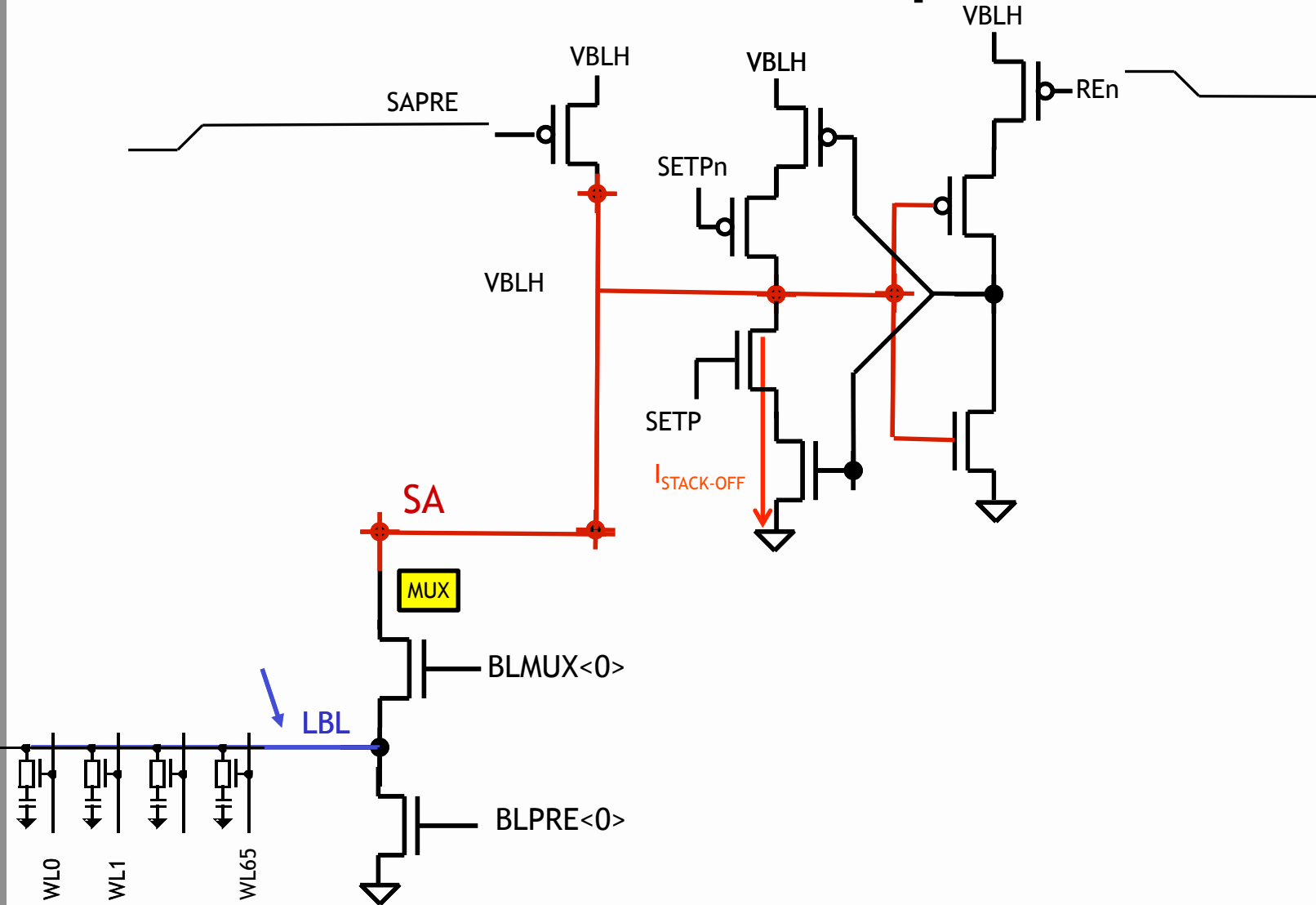
# Gated Feedback Sense Amp - Construction




Animation
 
# Gated Feedback Sense Amp - Construction



Cannot combine SA's to connect to the next hierarchy of SA – Need a wired OR output

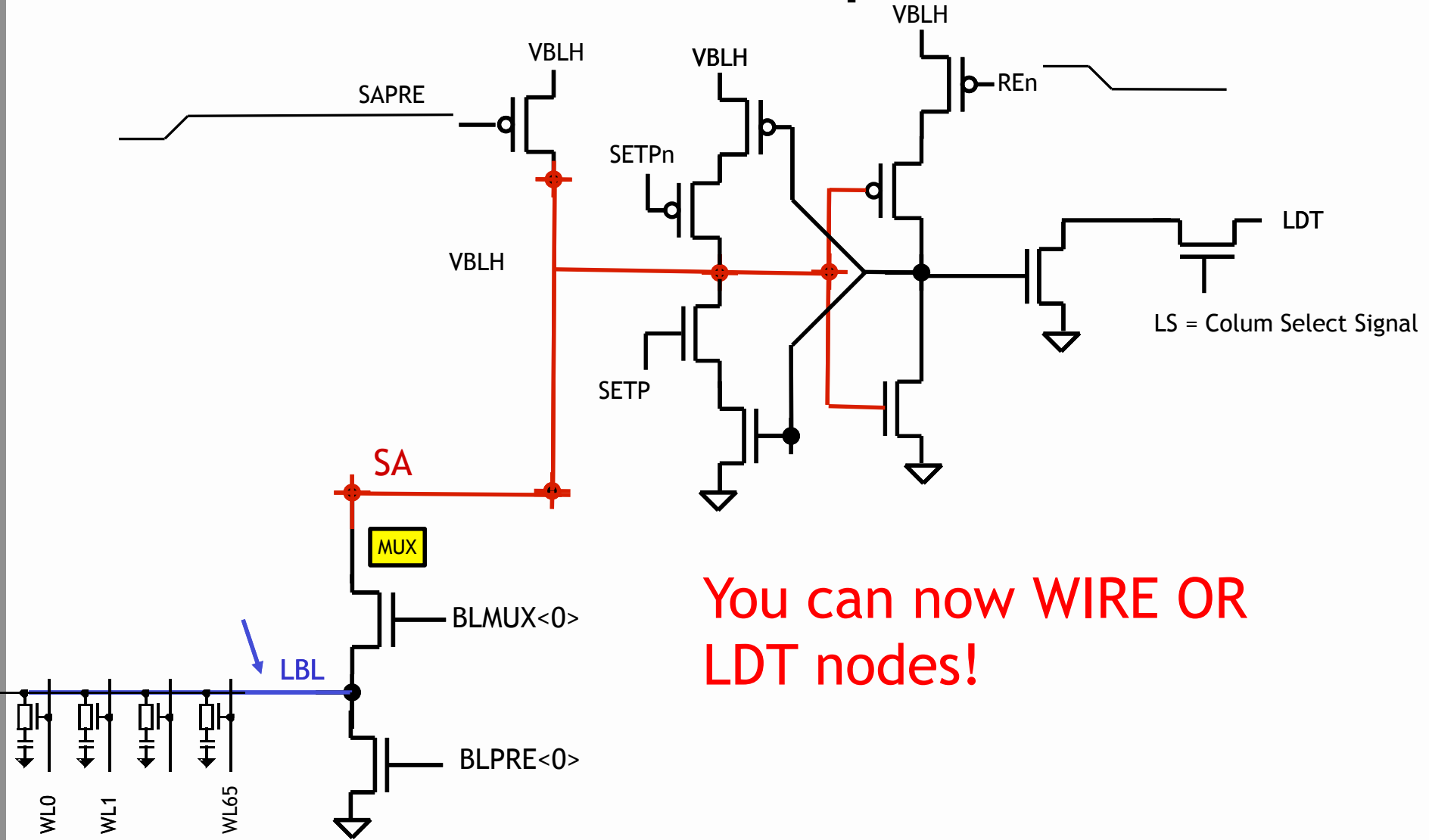
# Gated Feedback Sense Amp - Construction




You can now WIRE OR LDT nodes!

# Read Operation


Pre-charge OFF

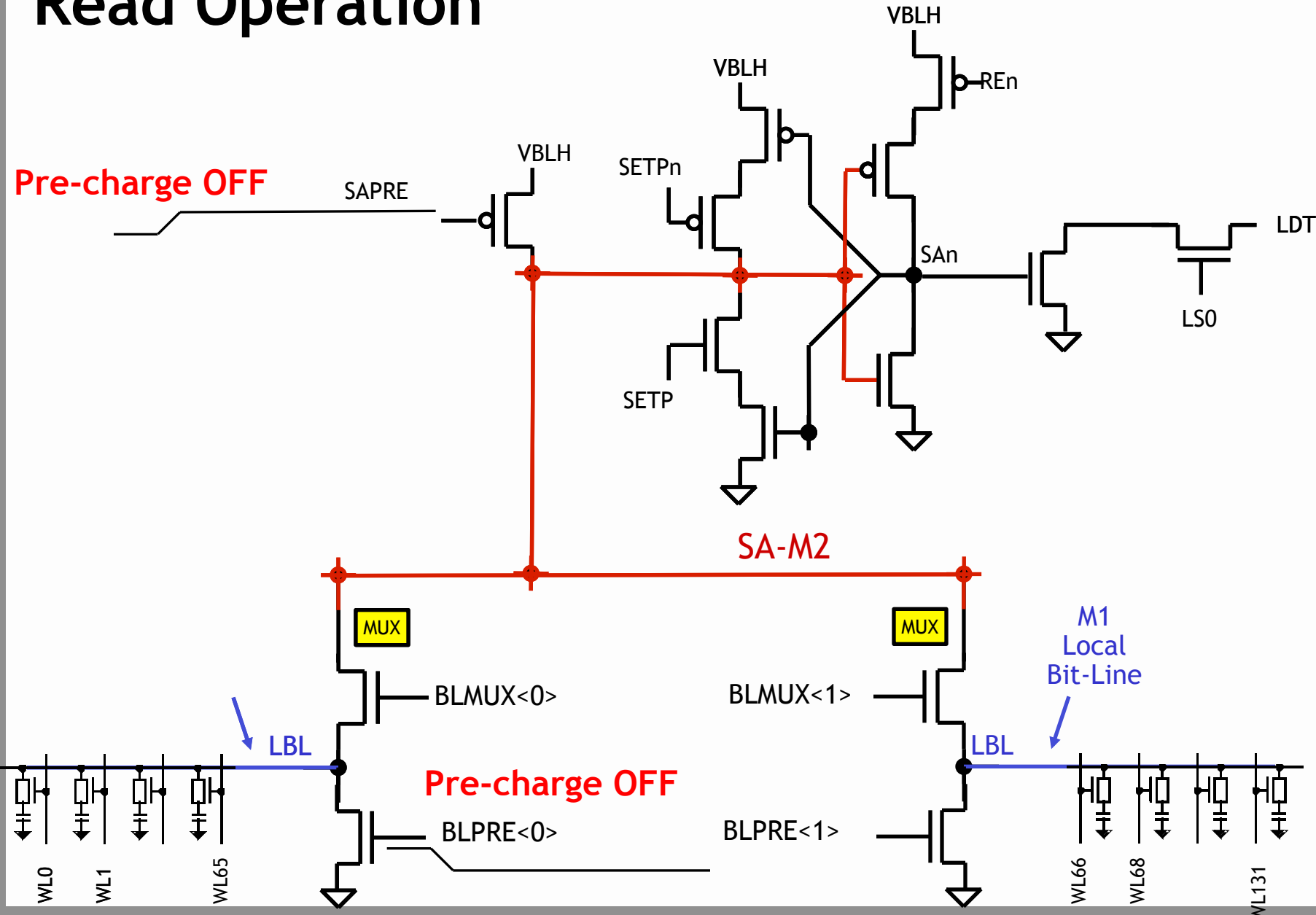

# Read Operation

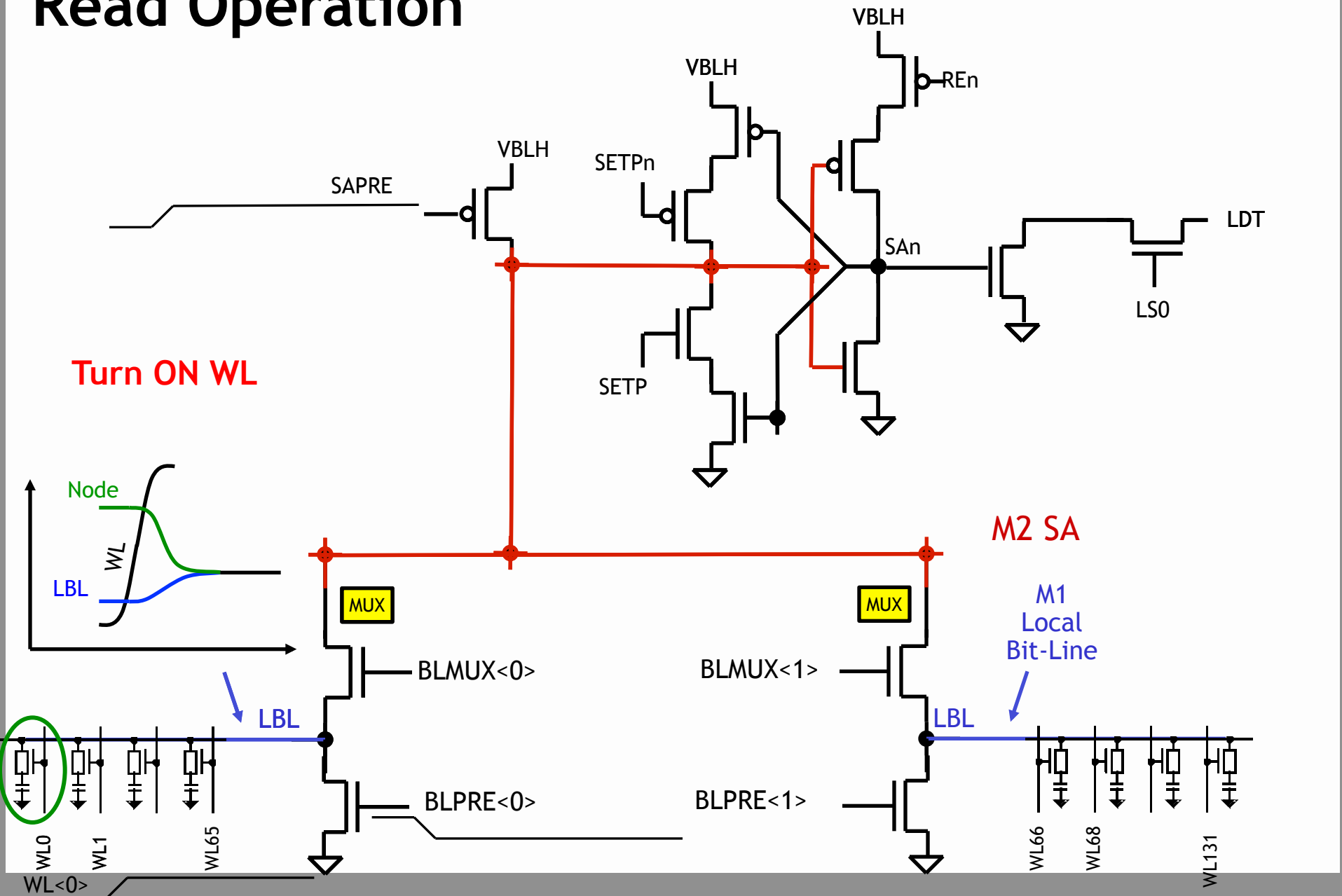


# Read Operation

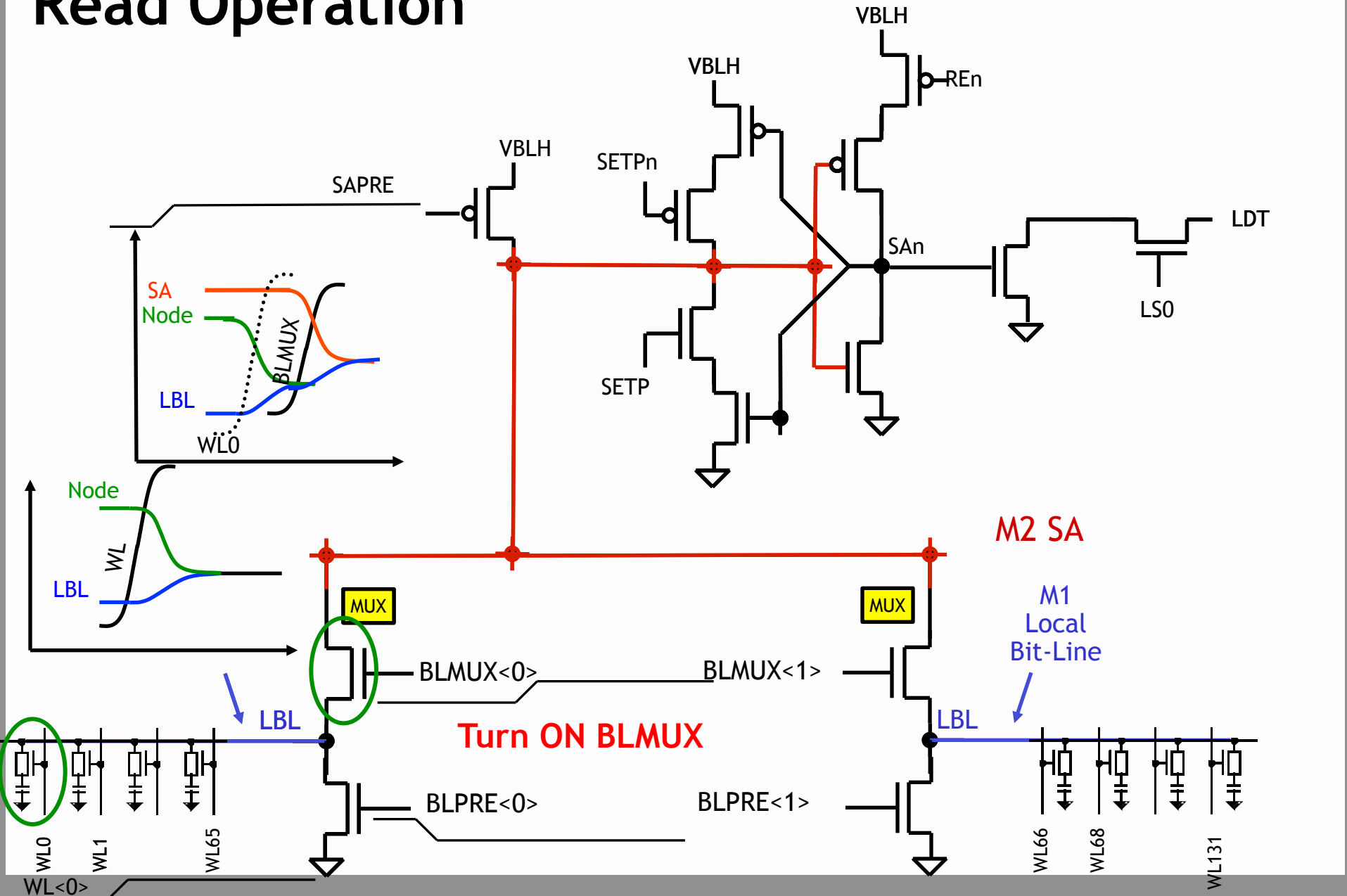

# Read Operation


Turn ON Read Header

 




# Read Operation


Turn ON Write-back

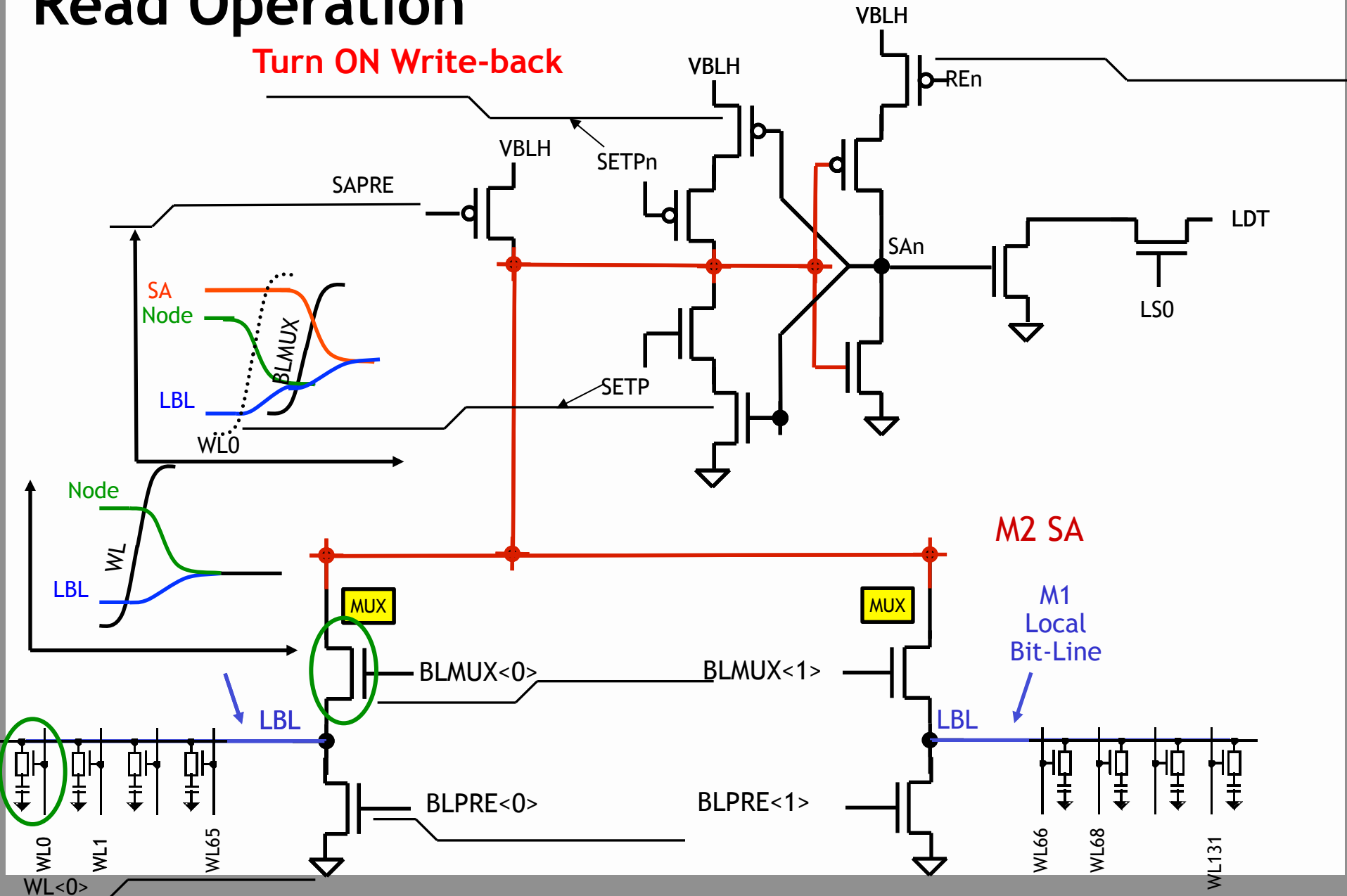

# Read Operation

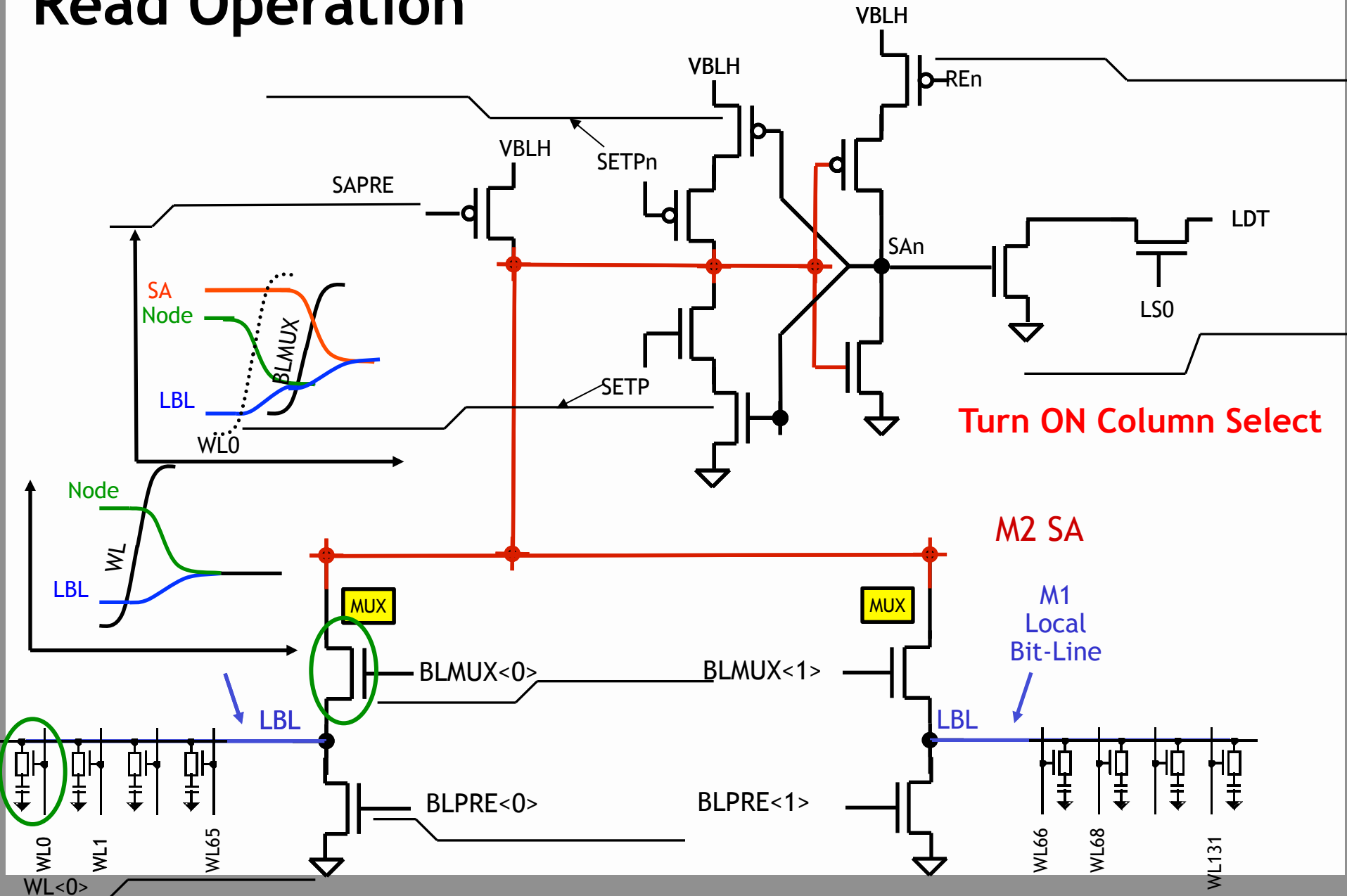


# Column Read Refresh

 

Other columns automatically get refreshed


Read Data Mux

# Read Data Mux

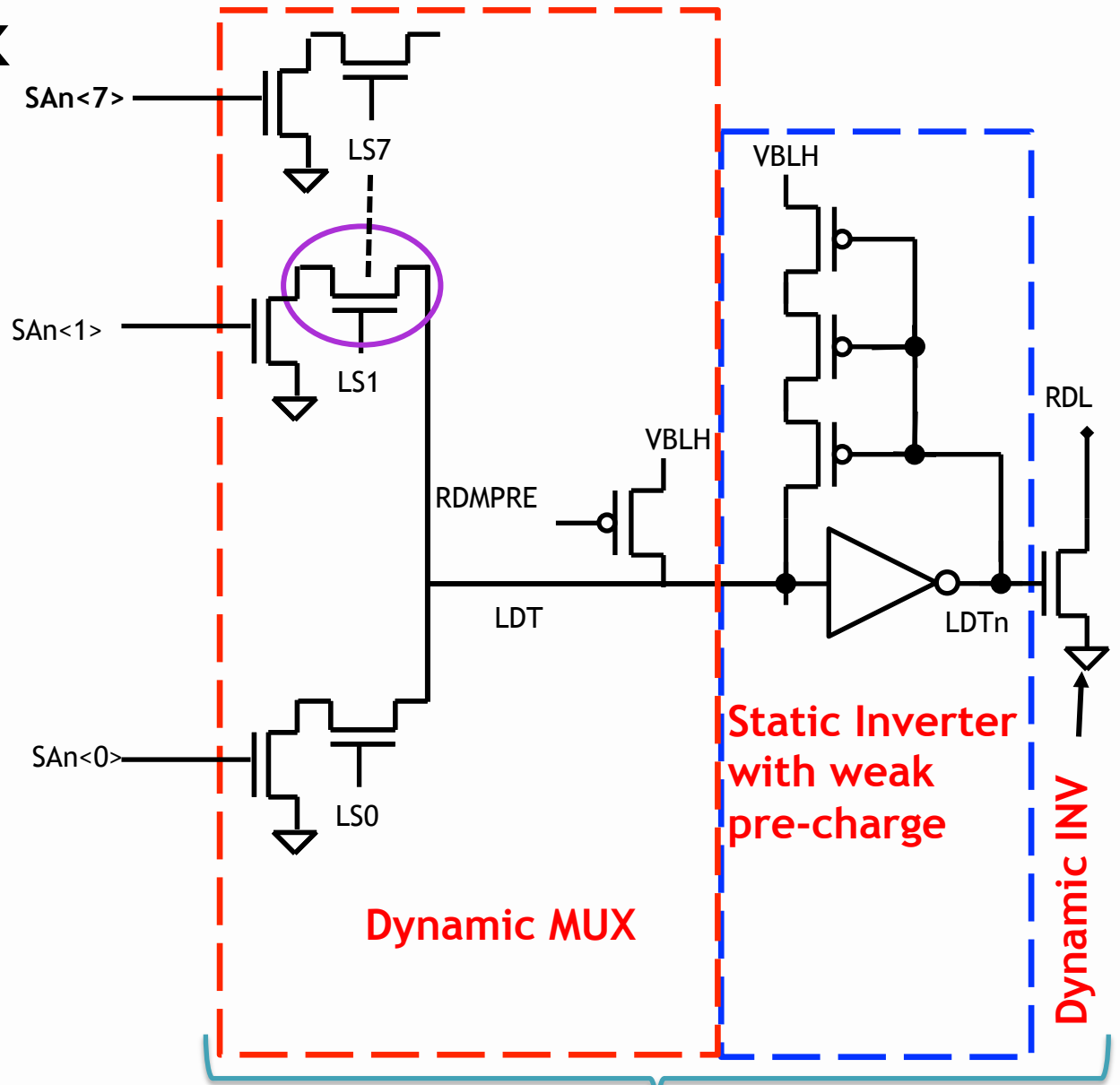


Read Data Mux


# Combining RDM's- Dynamic NOR Gate

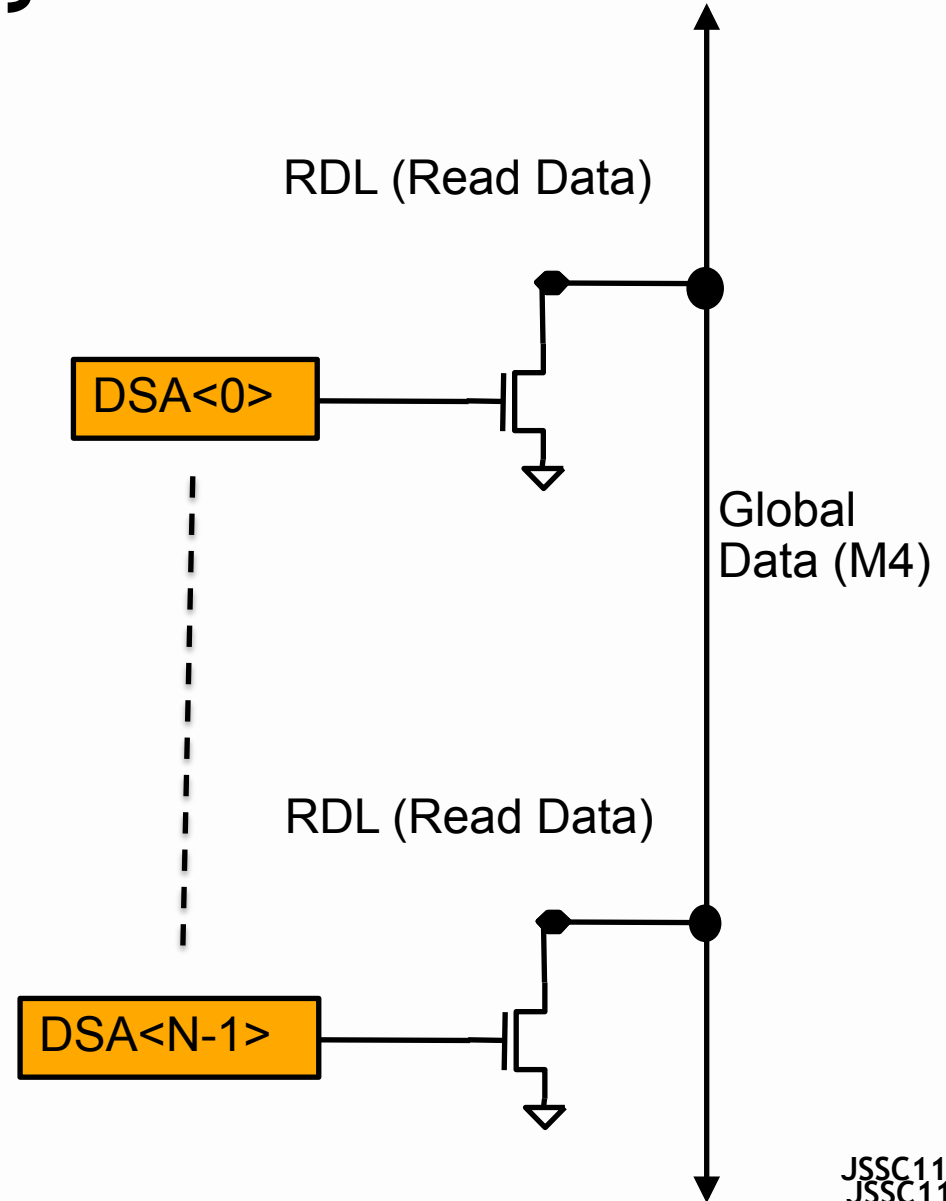

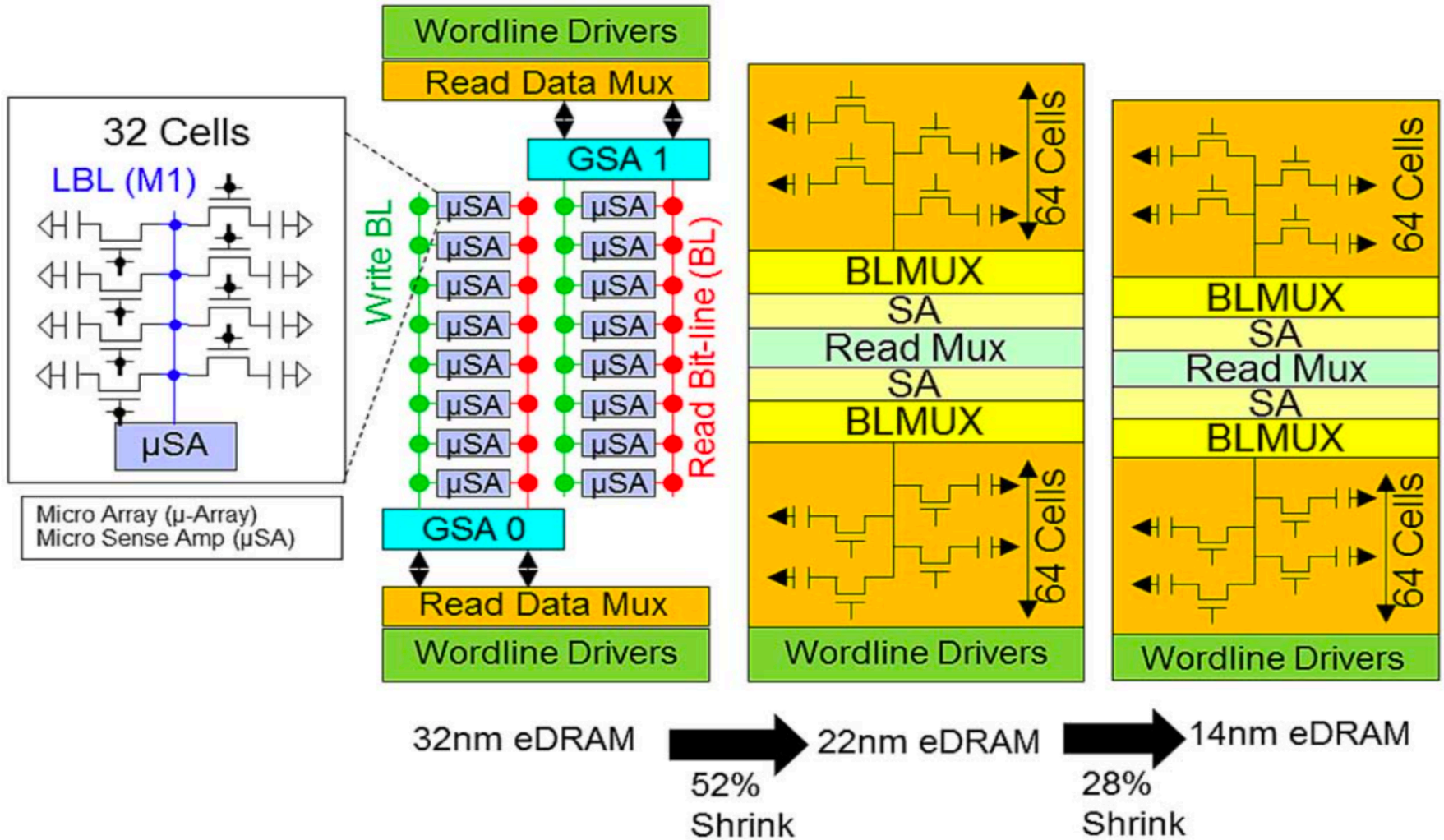
# Area Savings and Comparison with 3T uSA



# Write Operation

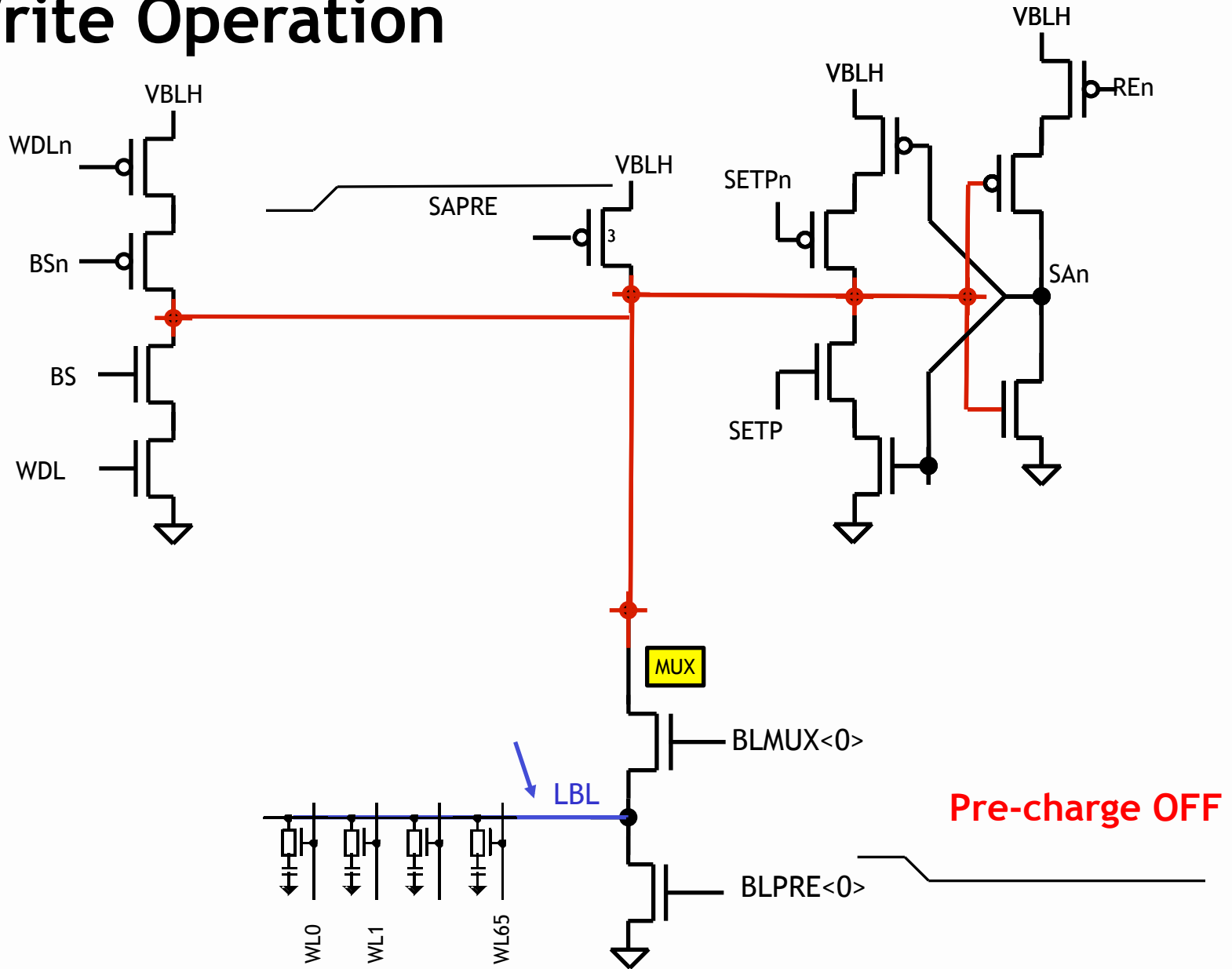


# Write Operation

 




# Write Operation

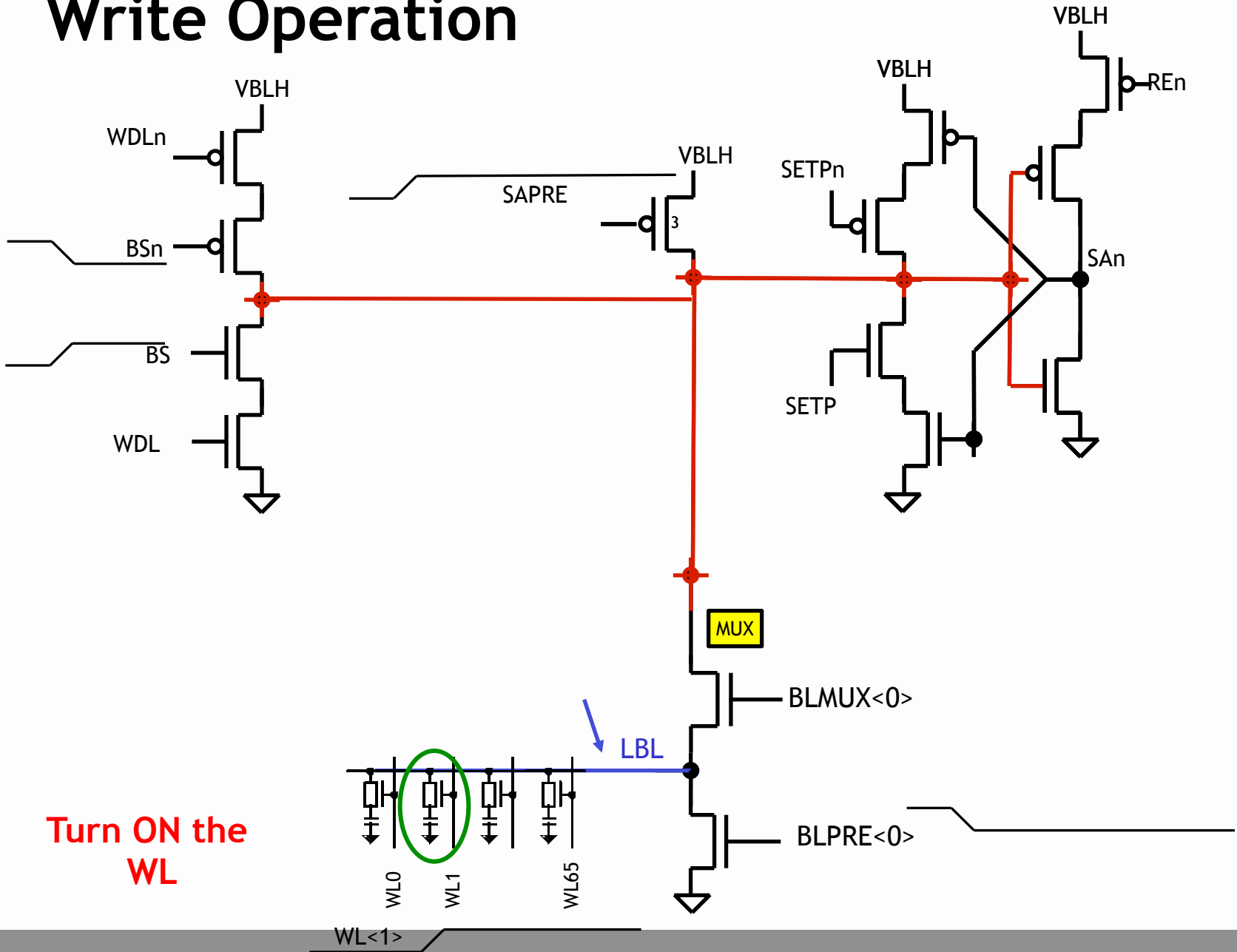


Turn ON the  
WL

# Write Operation

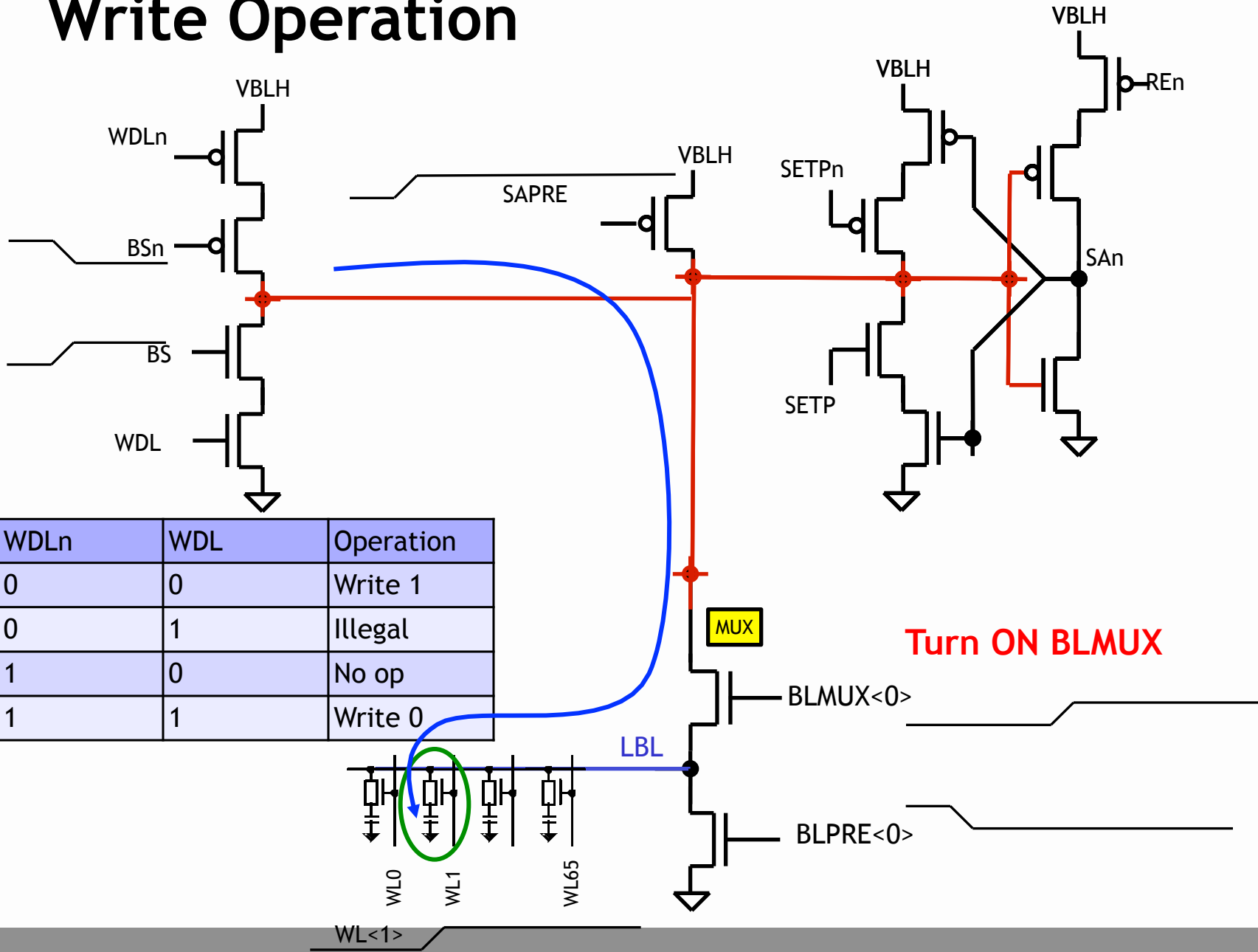


# Write Operation

 


# Write Operation

Turn ON Write-back

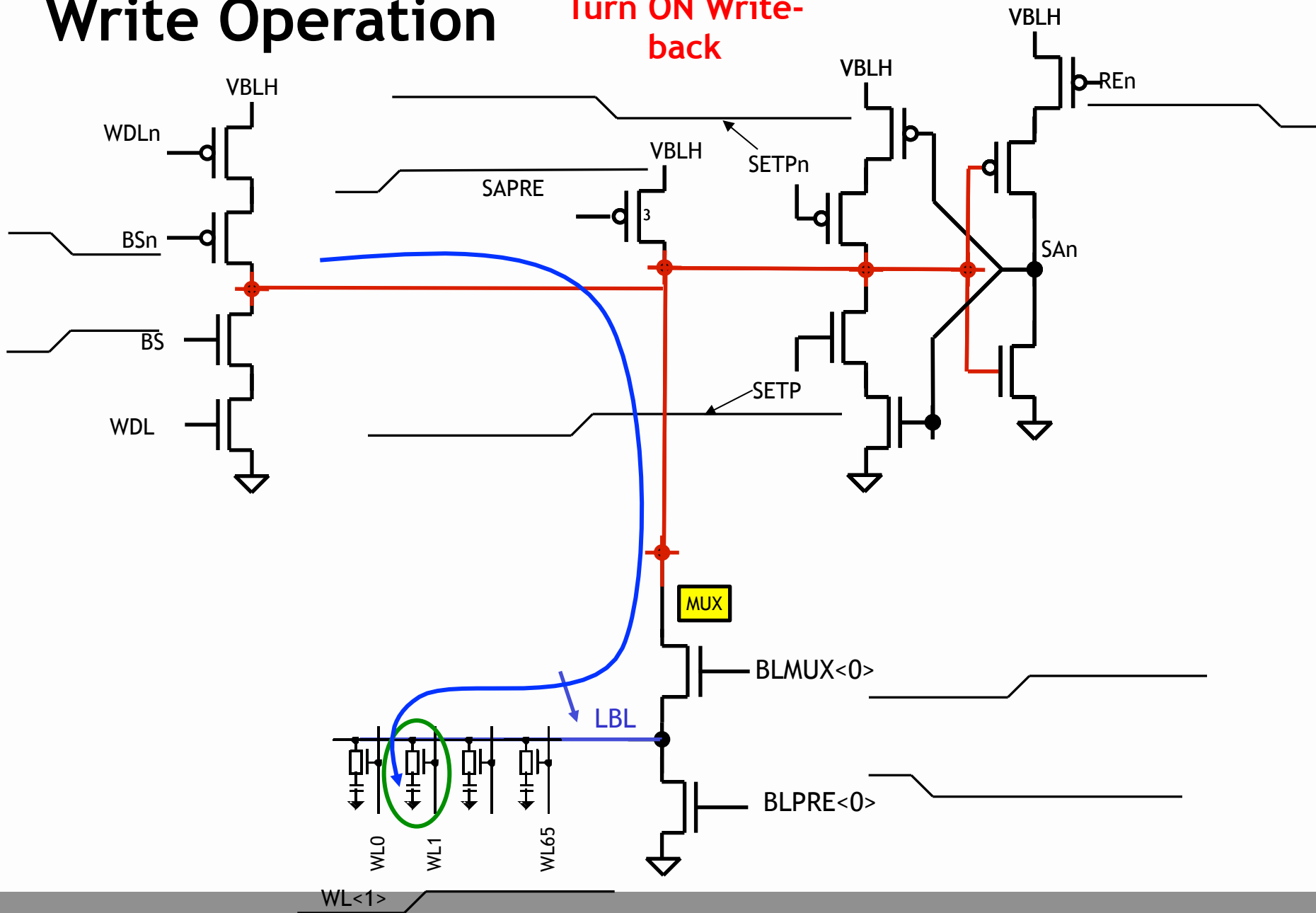


# One Data Line Organization

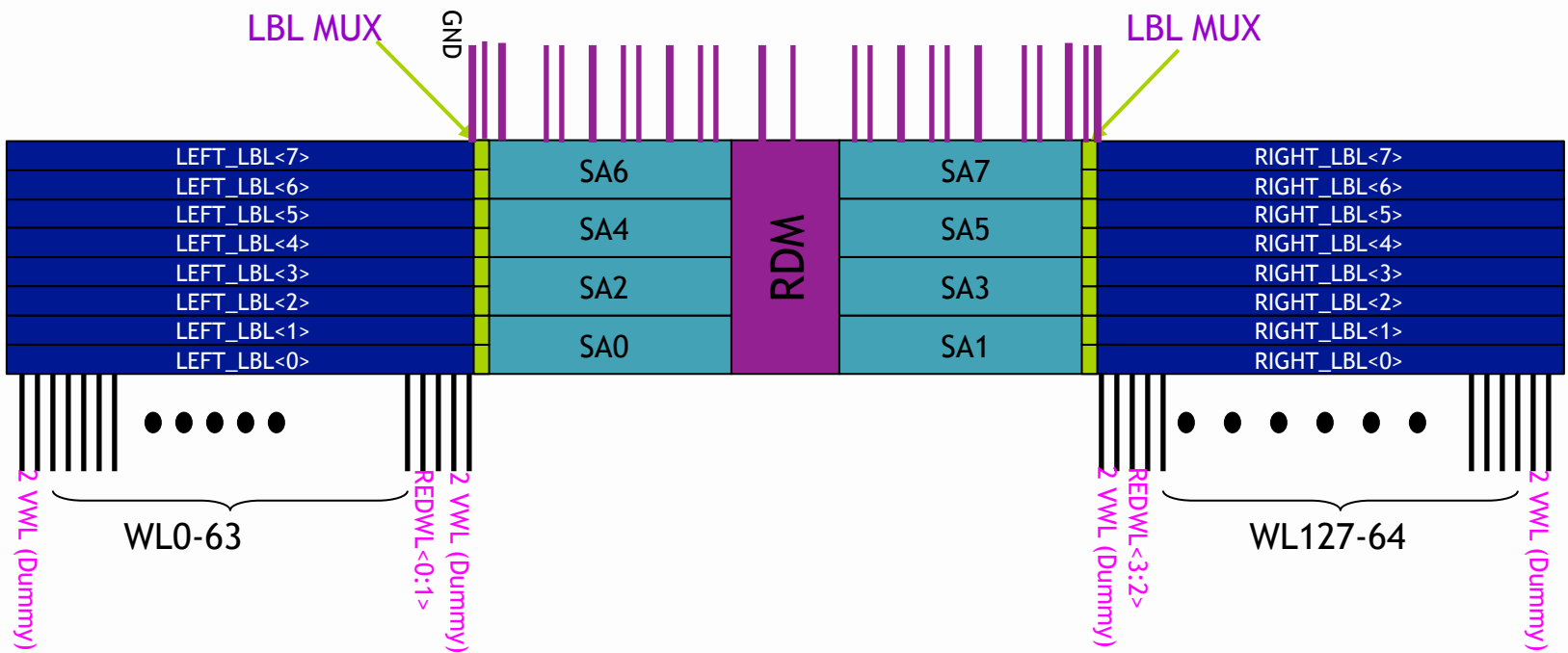

- Single bit can be read out/ written into by selecting one of 128 rows and one of 8 columns
- The components are sized and arranged to make the layout nice and rectangular
- Repeat this structure as many as there are Data-lines

# 14nm FinFET Advantage

 


(b)

14nm Access Device is 2.5X stronger than the 22nm planar device due to

- 50% more effective width
- 42% shorter channel length
- Lower target  $V_{\text{th}}$


Lower  $V_{\text{T}}$  variation due to undoped channel
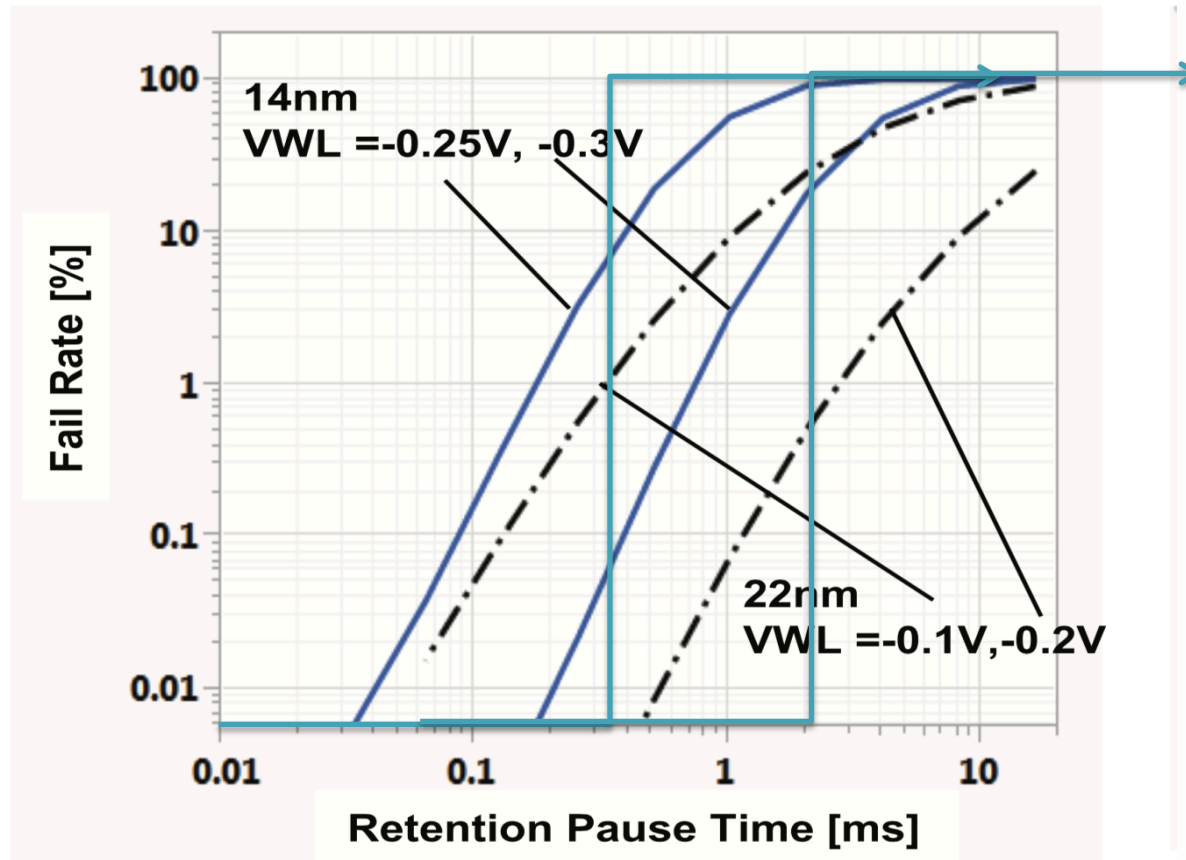
# Lower $V_{th}$ Variation Effect on Retention



- Write a 1 into all the cells
- Read the cells after a pause time
- Ideally (with no local variations) there should be an step jump in the #fail
  - With variations, steeper the slope lesser the variations

# Memory Testing

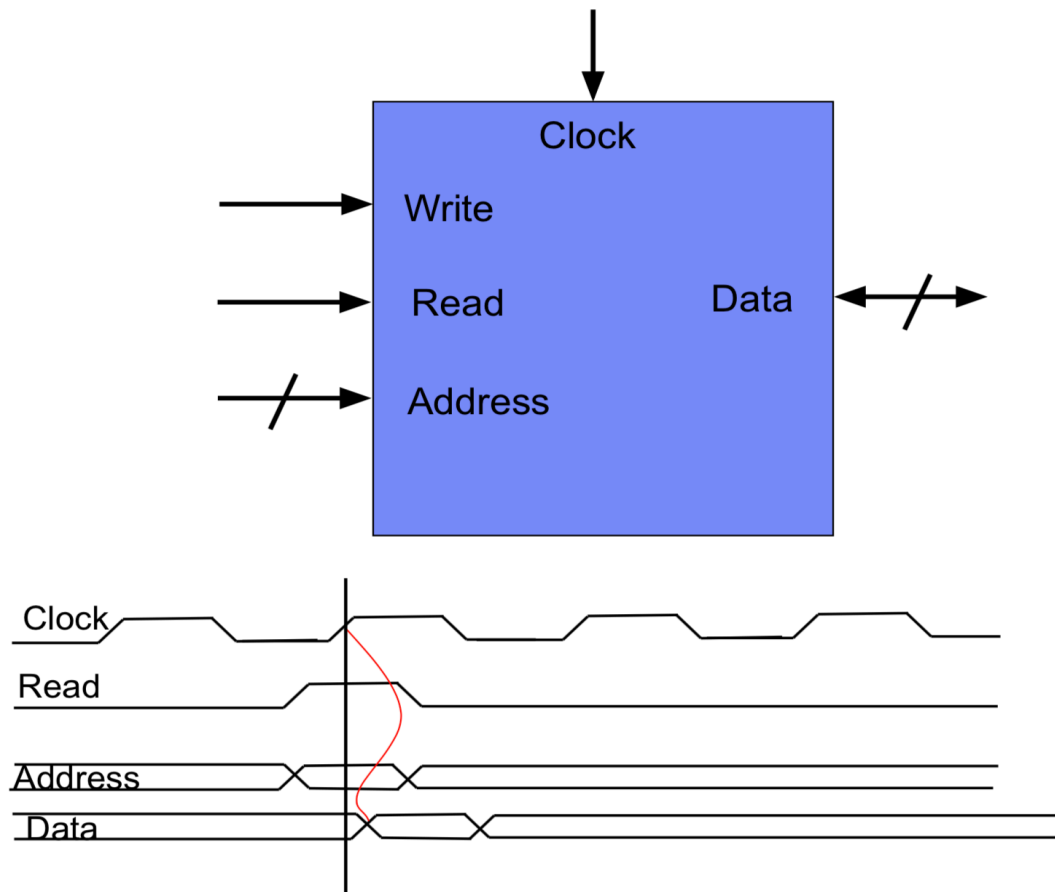

- No access to internal signals
- Need to detect and fix faults from outside



# Memory Faults


- Data faults – Pattern dependent
- Address faults
- Technology Specific faults
- Need to come up with test patterns to detect various faults.

# Address Faults

- Write zero to all addresses in increasing order:  $\uparrow\{W0\}$
  - Read zero from all addresses in increasing order:  $\uparrow\{R0\}$
  - Write one to all addresses in decreasing order:  $\downarrow\{W1\}$
  - Read one from all addresses in decreasing order:  $\downarrow\{R1\}$
- 
- Decoder error
    - Multiple WLs might fire at the same time.
    - No WL might fire
 
# Address Faults


- Test pattern:
  - $\uparrow\{W0\}$
  - $\uparrow\{R0\}$
  - $\uparrow\{W1\}$
  - $\uparrow\{R1\}$



- Decoder error
  - Not sufficient to just read OR write in a single operation
 
# Decoder Address Fault


- Test pattern:
  - $\uparrow\{W0\}$
  - $\uparrow\{R0\ W1\}$
  - $\uparrow\{R1\}$



- Decoder error
  - Not sufficient to just read OR write in a single operation
 
# Decoder Address Fault

- Test pattern:
  - $\uparrow\{W0\}$
  - $\uparrow\{R0\ W1\}$
  - $\uparrow\{R1\}$




- Decoder error
  - Not sufficient to just read OR write in a single operation
 
# Decoder Address Fault

- MARCH Pattern

- $\uparrow\{W0\}$
- $\uparrow\{R0\ W1\}$
- $\uparrow\{R1\}$




- Decoder error

- Fault: Row-0 and row-2 fire together
- Not sufficient to just read OR write in a single operation
 
# Decoder Address Fault

- MARCH Pattern
  - $\uparrow\{W0\}$
  - $\uparrow\{R0\ W1\}$
  - $\uparrow\{R1\}$




- Decoder error
  - MARCH Patterns

# Redundancy


Notebook



Page 111

 

Extra Page  
R05

 

eFuse based repair table

(see page R05)

<u>INDEX TO BOOK ONE</u>			
<u>PAGE No.</u>	<u>EXPT. No.</u>	<u>AND</u>	<u>DATE</u>
109	30 APRIL 1999	-	EXP. 30
110	1-MAY 1999		EXP 30 CONTD
111	1-MAY 1999		EXP 31
112	1-MAY 1999		EXP 31 CONTD.



# Fault Detection and Correction

- Run various patterns and detect failed rows and columns
- Mark the addresses as failed ones
- Map them to redundant rows/ columns
- Compare incoming address with failed rows and columns
  - If match found – Change address to redundant row/ column
  - Else let the address through
- Errors on the field are fixed using error correcting codes

# Conclusion

- Pulling more DRAM cache (L2,L3) inside the processor improves overall performance
- eDRAM design using logic process is a challenge
- Case study is done, covering many of the eDRAM design aspects
- Sense amp has to read a 1 by default to provide performance improvement
  - Achieved in the Gated Feedback Sense Amp

# Learning Objectives for EDRAM

- ❑ Explain the working of a (e)DRAM. What does Embedded mean?
- ❑ Explain the working of a feedback sense amplifier and modify existing designs to improve performance
- ❑ Calculate the voltage levels of operation of various components for an eDRAM
- ❑ Introduce stacked protect devices to reduce voltage stress of the WL driver

# References

- Matick, R. et al., "Logic-based eDRAM: Origins and Rationale for Use," IBM J. Research Dev., vol. 49, no. 1, pp. 145-165, Jan. 2005.
- Barth, J. et al., "A 500MHz Random Cycle 1.5ns-Latency, SOI Embedded DRAM Macro Featuring a 3T Micro Sense Amplifier," ISSCC Dig. Tech. Papers, pp. 486-487, Feb. 2007.
- Barth, J. et al., "A 500 MHz Random Cycle, 1.5 ns Latency, SOI Embedded DRAM Macro Featuring a Three-Transistor Micro Sense Amplifier," IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 43, NO. 1, JANUARY 2008.
- Barth, J. et al., "A 45nm SOI Embedded DRAM Macro for POWER7™ 32MB On-Chip L3 Cache," ISSCC Dig. Tech. Papers, pp. 342-3, Feb. 2010.
- Barth, J. et al., "A 45 nm SOI Embedded DRAM Macro for the POWER™ Processor 32 MByte On-Chip L3 Cache," IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 46, NO. 1, JANUARY 2011.
- S. Iyer et al., "Embedded DRAM: Technology Platform for BlueGene/L Chip," IBM J. Res. & Dev., Vol. 49, No. 2/3, MARCH/MAY 2005, pp.333-50.
- Barth, J. et al., "A 300MHz Multi-Banked eDRAM Macro Featuring GND Sense, Bit-line Twisting and Direct Reference Cell Write," ISSCC Dig. Tech. Papers, pp. 156-157, Feb. 2002.
- Barth, J. et al., "A 500-MHz Multi-Banked Compilable DRAM Macro With Direct Write and Programmable Pipelining," IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 40, NO. 1, JANUARY 2005.
- Butt, N., et al., "A 0.039 $\mu$ m<sup>2</sup> High Performance eDRAM Cell based on 32nm High-K/Metal SOI Technology," IEDM pp. 27.5.1-2, Dec 2010.
- Bright, A. et al., "Creating the BlueGene/L Supercomputer from Low-Power SoC ASICs," ISSCC Dig. Tech. Papers, pp. 188-189, Feb. 2005.
- Blagojevic, M. et al., "SOI Capacitor-Less 1-Transistor DRAM Sensing Scheme with Automatic Reference Generation," Symposium on VLSI Circuits Dig. Tech. Papers, pp. 182-183, Jun. 2004.

# References

Karp, J. et al., “A 4096-bit Dynamic MOS RAM” ISSCC Dig. Tech. Papers, pp. 10-11, Feb. 1972.

Kirihata, T. et al., “An 800-MHz Embedded DRAM with a Concurrent Refresh Mode,” IEEE Journal of Solid State Circuits, pp. 1377-1387, Vol. 40, Jun. 2003.

Luk, W. et al., “2T1D Memory Cell with Voltage Gain,” Symposium on VLSI Circuits Dig. Tech. Papers, pp. 184-187, Jun. 2004.

Luk, W. et al., “A 3-Transistor DRAM Cell with Gated Diode for Enhanced Speed and Retention Time,” Symposium on VLSI Circuits Dig. Tech. Papers, pp. 228-229, Jun. 2006.

NEC eDRAM Cell Structure (MIM Capacitor): <http://www.necel.com/process/en/edramstructure.html>

Ohsawa, T. et al., “Memory Design using One-Transistor Gain Cell on SOI,” ISSCC Dig. Tech. Papers, pp. 152-153, Feb. 2002.

Pilo, H. et al., “A 5.6ns Random Cycle 144Mb DRAM with 1.4Gb/s/pin and DDR3-SRAM Interface,” ISSCC Dig. Tech. Papers, pp. 308-309, Feb. 2003.

Taito, Y. et al., “A High Density Memory for SoC with a 143MHz SRAM Interface Using Sense-Synchronized-Read/Write,” ISSCC Dig. Tech. Papers, pp. 306-307, Feb. 2003.

Wang, G. et al., “A 0.127 mm<sup>2</sup> High Performance 65nm SOI Based embedded DRAM for on-Processor Applications,” International Electron Devices Meeting, Dec. 2006.

G. Fredeman et al., “A 14 nm 1.1 Mb Embedded DRAM Macro With 1 ns Access,” in IEEE Journal of Solid-State Circuits, vol. 51, no. 1, pp. 230-239, Jan. 2016. doi: 10.1109/JSSC.2015.2456873