

Course Objectives

- ❑ Introduce students to some relevant advanced topics of current interest in academia and industry
- ❑ Give the students a feel for research topics and what research means
- ❑ **Make students aware of work happening in India**

Current Topics

- ❑ Embedded Memory Design
 - ❑ SRAMs (Dr. Rahul Rao, IBM India)
 - ❑ eDRAMs (Dr. Janakriaman, IITM)
 - ❑ Advanced Memories

Learning Objectives for SRAM

- ❑ Articulate memory hierarchy and the value proposition of SRAMs in the memory chain + utilization in current processors
- ❑ Explain SRAM building blocks and peripheral operations and memory architecture (with physical arrangement)
- ❑ Articulate commonly used SRAM cells (6T vs 8T), their advantages and disadvantages
- ❑ Explain the operation of a non-conventional SRAM cells, and their limitations
- ❑ Explain commonly used assist methods
- ❑ Explain how variations impact memory cells

Learning Objectives for EDRAM

- ❑ Explain the working of a (e)DRAM. What does Embedded mean?
- ❑ Explain the working of a feedback sense amplifier and modify existing designs to improve performance
- ❑ Calculate the voltage levels of operation of various components for an eDRAM
- ❑ Introduce stacked protect devices to reduce voltage stress of the WL driver

Grading

- ❑ Assignments - 10%
- ❑ Midsem – 30%
- ❑ Project - 20%
- ❑ End Semester - 40%

Course Schedule

☐ Friday – 2:00 –5:00

☐ ESB 207A

Embedded DRAM

Janakiraman V

Assistant Professor
Electrical Department
IIT Madras

Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example
- ❑ Gated Feedback Sense Amplifier (case study)
- ❑ References


Acknowledgement

- Raviprasad Kuloor (Course slides were prepared by him)
- John Barth, IBM SRDC for most of the slides content
- Madabusi Govindarajan
- Subramanian S. Iyer
- Many Others

Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example

Memory Classification revisited

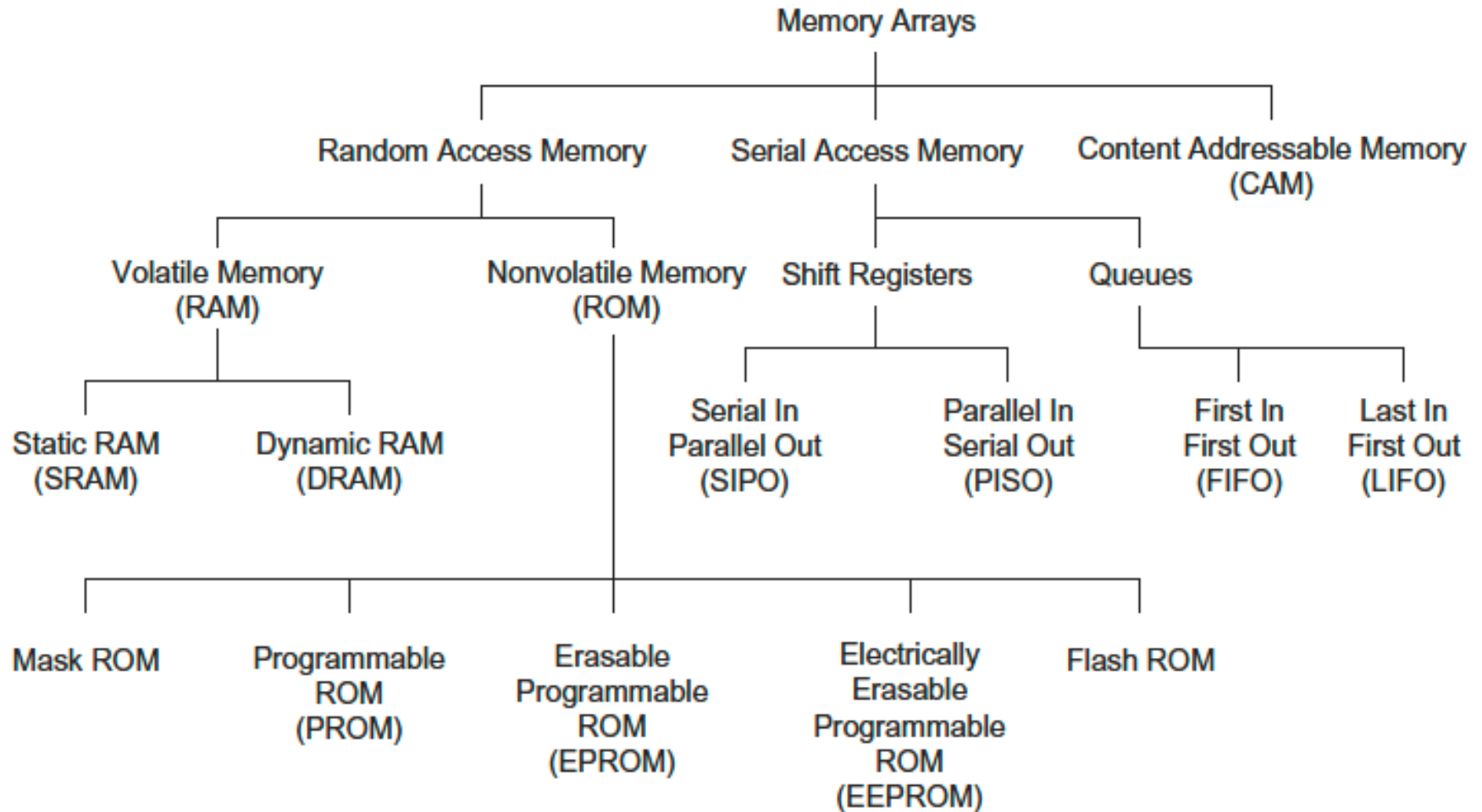

Motivation for a memory hierarchy - infinite memory



Cycles per Instruction
(CPI)

=

Number of processor clock cycles
required per instruction

$CPI[\infty \text{ cache}]$

Finite memory speed



$$\text{CPI} = \text{CPI}[\infty \text{ cache}] + \text{FCP}$$

Finite cache penalty

Locality of reference - spatial and temporal

Temporal

If you access something now you'll need it again soon


e.g: Loops

Spatial

If you accessed something you'll also need its neighbor

e.g: Arrays

 Exploit this to divide memory into hierarchy




Cache size impacts cycles-per-instruction

Logic-based
eDRAM: Origins
and rationale
for use

R. E. Matick
S. E. Schuster

 IBM J. RES. & DEV. VOL. 49 NO. 1 JANUARY 2005



No. of L2 hits per instruction
 $mr_1 - mr_2$


No. of L3 hits per instruction
 $mr_2 - mr_3$

No. of L4 hits per instruction
 $mr_3 - mr_4$

Finite cache penalty	=	Delay / I for L2 hits	+	Delay / I for L3 hits	+	Delay / I for L4 hits ...
FCP	=	$(mr_1 - mr_2) T_2$	+	$(mr_2 - mr_3) T_3$	+	$(mr_3 - mr_4) T_4 + \dots$
Cycles per instruction	=	Hits per instruction × cycles per hit				

—————→ Access rate reduces → Slower memory is sufficient

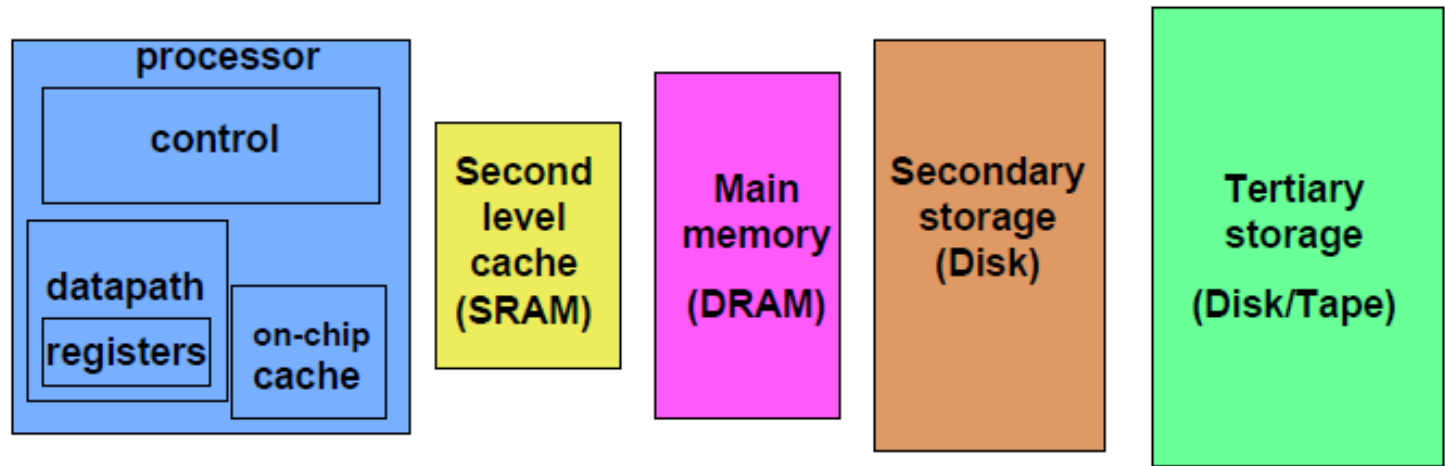
Cache size impacts cycles-per-instruction



Speed	1ns	10ns	100ns	10ms	10sec
Size	B	KB	MB	GB	TB


For a 5GHz processor, scale the numbers by 5x

Technology choices for memory hierarchy

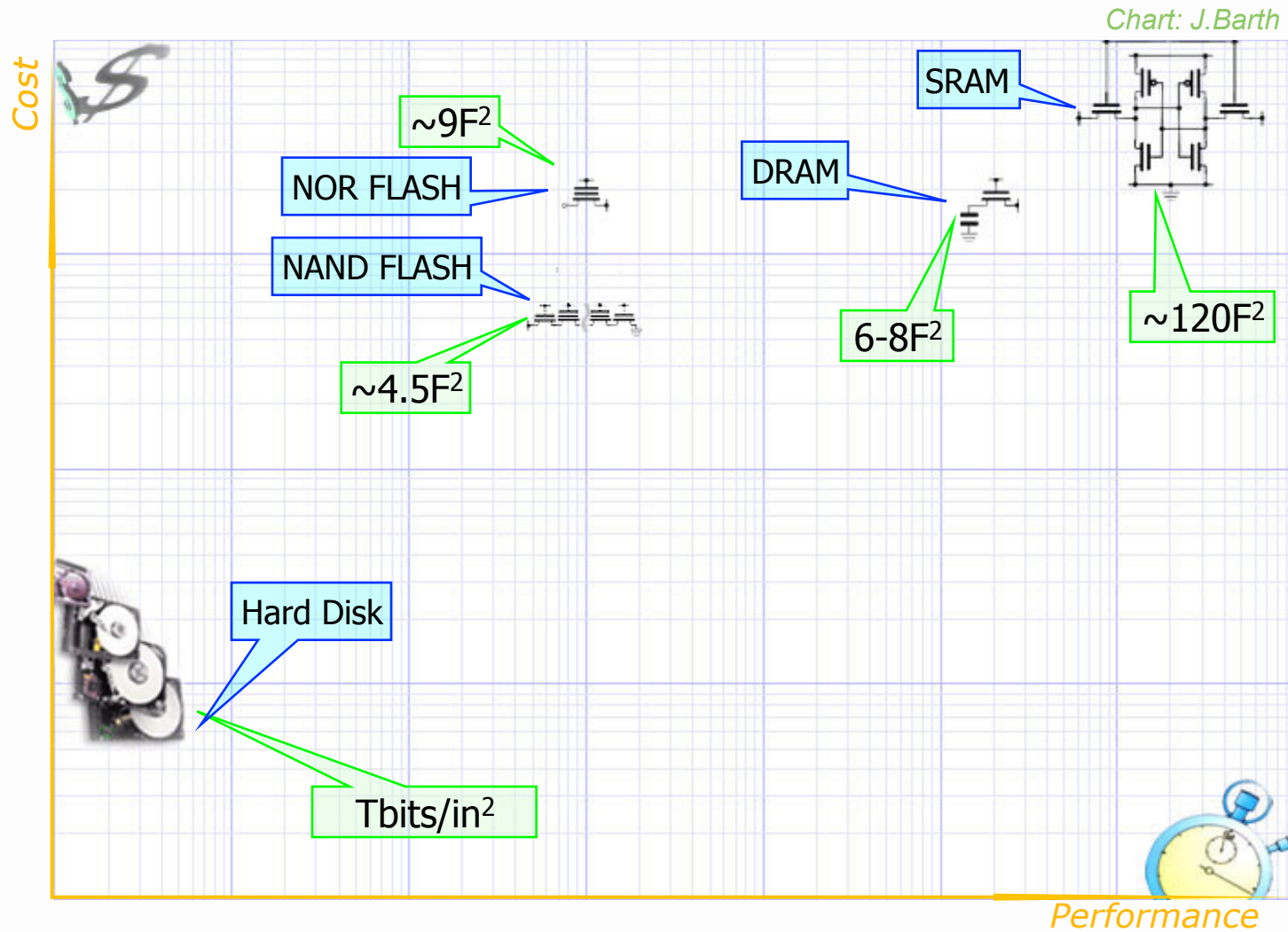

eDRAM L3 cache

Power7
processor

 

Move L2,L3 Cache inside of the data hungry processor

Higher hit rate → Reduced FCP

Embedded DRAM Advantages



Memory Advantage

- 2x Cache can provide > 10% Performance
- ~3x Density Advantage over eSRAM
- 1/5x Standby Power Compared to SRAM
- Soft Error Rate 1000x lower than SRAM
- Performance ? DRAM can have lower latency !
- IO Power reduction


Deep Trench Capacitor

- Low Leakage Decoupling
- 25x more Cap / μm^2 compared to planar
- Noise Reduction = Performance Improvement
- Isolated Plate enables High Density Charge Pump


IBM Power7tm
32MB eDRAM L3

  


eDRAM Advantages – Stand By Leakage

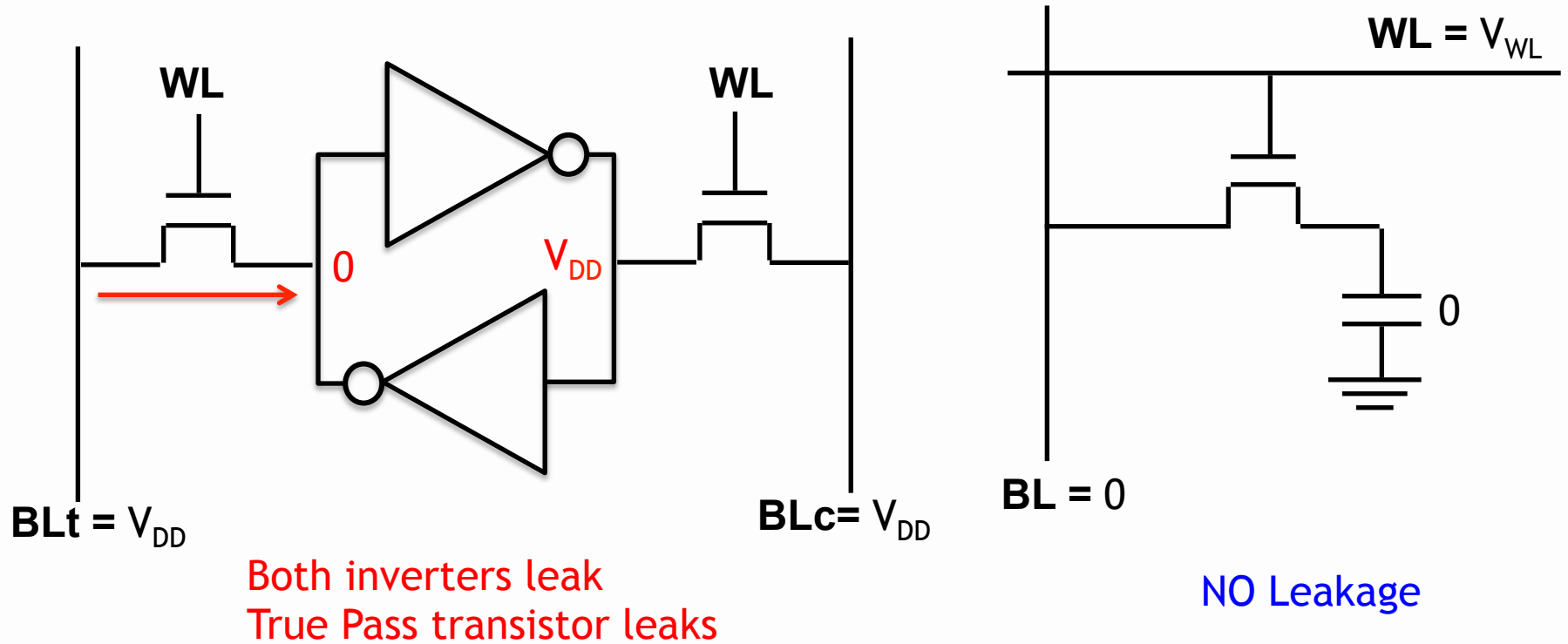

eDRAM Advantages – Stand By Leakage

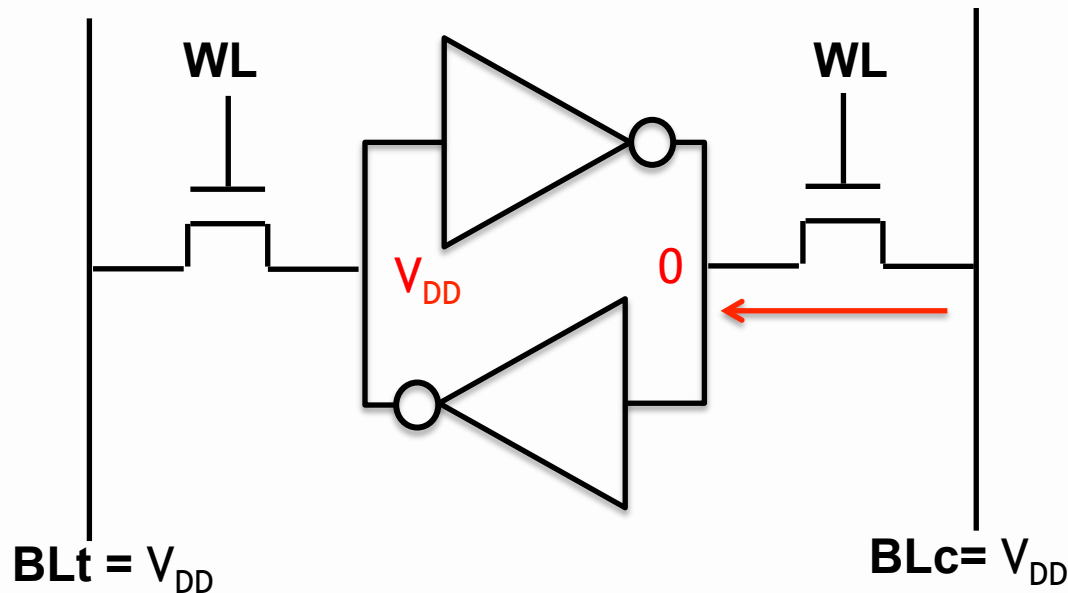


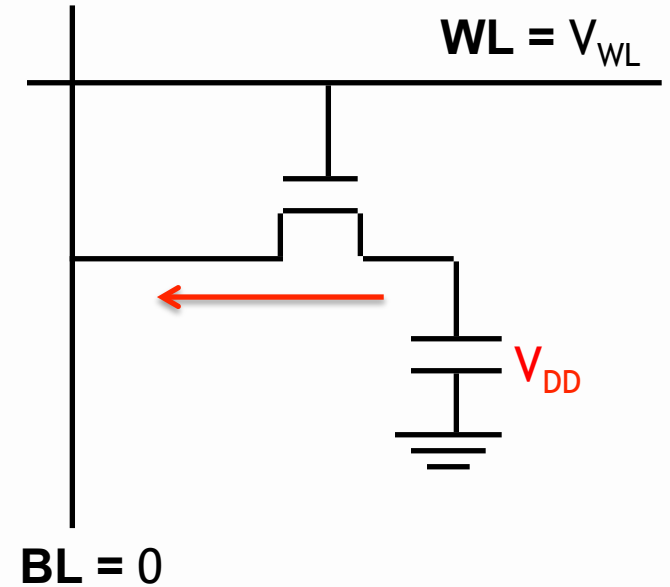Both inverters leak
Complement Pass transistor leaks




Leakage exists

eDRAM Advantages – Stand By Leakage

 


On average: eDRAMs have 1/5x Standby Power Compared to SRAM

eDRAM Advantages – Performance

 


 Both inverters leak
Complement Pass transistor leaks



Leakage exists

eDRAM Advantages – Soft Error Rate

 



- Cosmic particles can bombard the cell and cause a bump in the cell voltage
- If voltage bump is large enough SRAM can permanently flip
 - Static cross couple inverters
- Voltage on DRAM capacitor node can also bump
- But will leak away with time –
 - Only those cells which get refreshed in a certain period will flip
- **Soft Error Rate 1000x lower than SRAM**

Embedded DRAM Advantages

Deep Trench Capacitor

- Low Leakage Decoupling
- 25x more Cap / μm^2 compared to planar
- Noise Reduction = Performance Improvement
- Isolated Plate enables High Density Charge Pump

IBM Power7tm
32MB eDRAM L3

 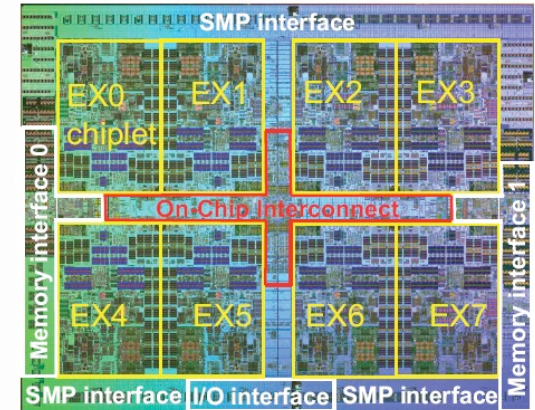

Embedded DRAM Advantages



Memory Advantage

- 2x Cache can provide > 10% Performance
- ~3x Density Advantage over eSRAM
- 1/5x Standby Power Compared to SRAM
- Soft Error Rate 1000x lower than SRAM
- Performance ? DRAM can have lower latency !
- IO Power reduction

Deep Trench Capacitor


- Low Leakage Decoupling
- 25x more Cap / μm^2 compared to planar
- Noise Reduction = Performance Improvement
- Isolated Plate enables High Density Charge Pump

IBM Power7tm
32MB eDRAM L3

  


Cache performance - SRAM vs. DRAM

Chart: Matick & Schuster, op. cit.

 

Cache performance - SRAM vs. DRAM

 


Time to access the farthest word-line determines performance
Access time = Cell access time + time of flight interconnect delay

Embedded DRAM Performance

45nm eDRAM vs. SRAM Latency

eDRAM Faster than SRAM

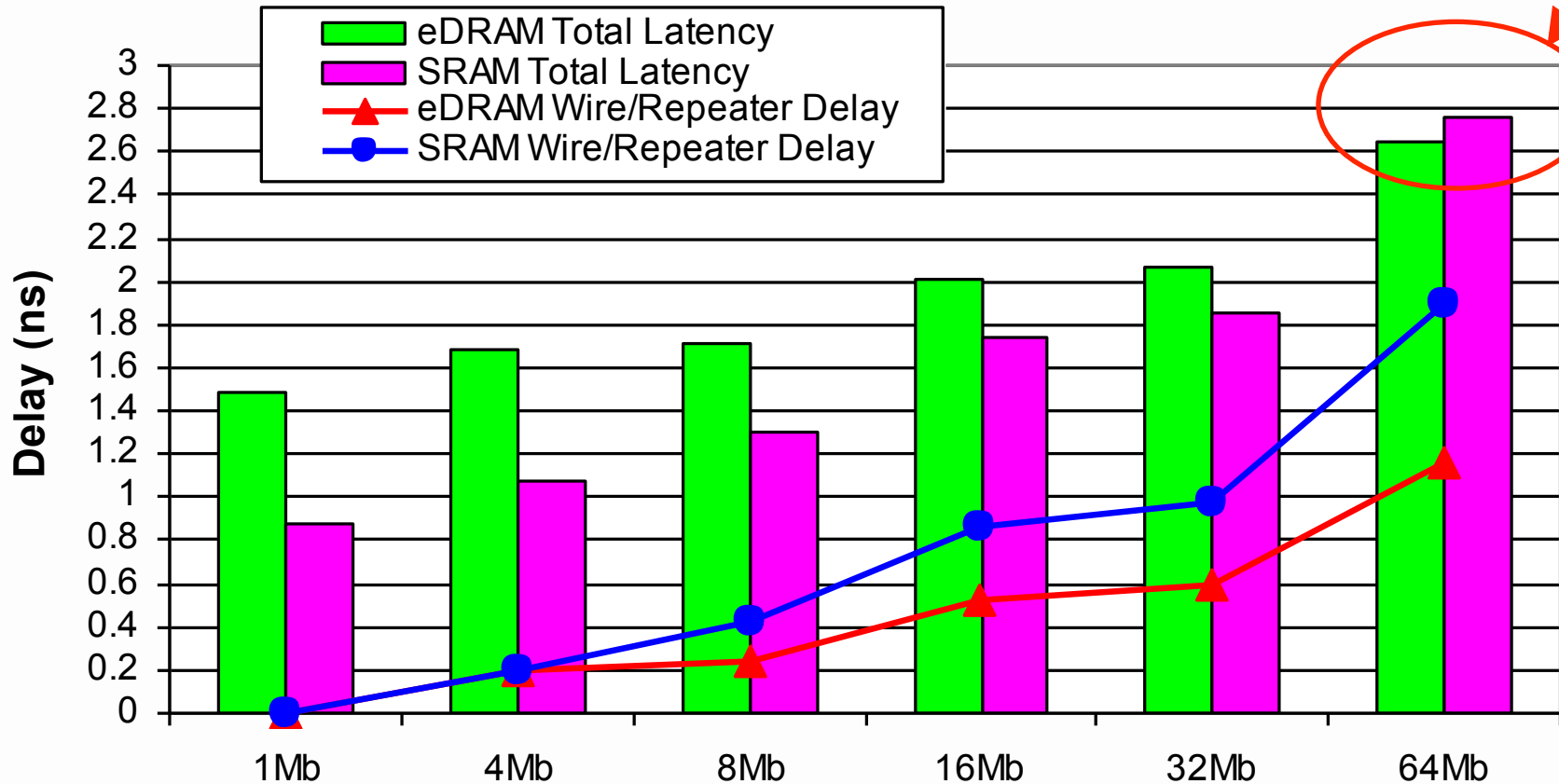

Memory Block Size Built With 1Mb Macros

Barth ISSCC 2011

Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example

Fundamental DRAM Operation


Memory Arrays are composed of Row and Columns

Most DRAMs use 1 Transistor as a switch and
1 Cap as a storage element (Dennard 1967)



Single Cell Accessed by Decoding One Row / One Column (Matrix)

Row (Word-Line) connects storage Caps to Columns (Bit-Line)

 Storage Cap Transfers Charge to Bit-Line, Altering Bit-Line Voltage



1T1C DRAM Cell Terminals

 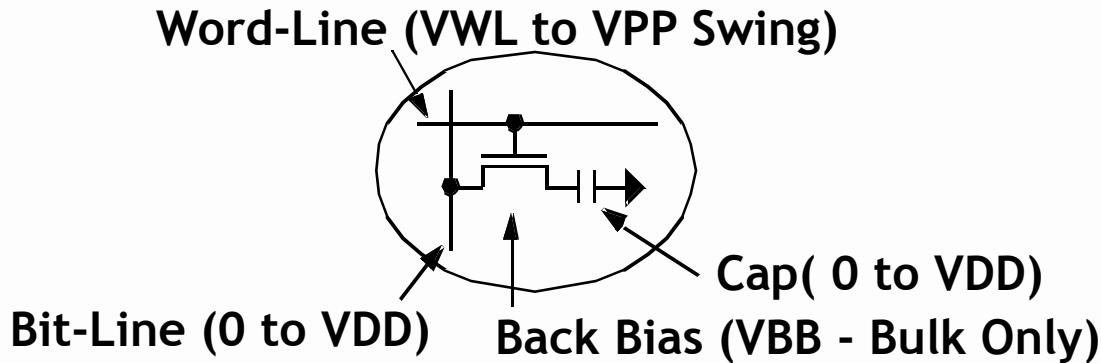


VWL: Word-Line Low Supply, GND or Negative for improved leakage

VPP: Word-Line High Supply, 1.8V up to 3.5V depending on Technology
Required to be at least a V_t above VDD to write full VDD


VBB: Back Bias, Typically Negative to improve Leakage
Not practical on SOI

Choice of Access Transistor

 
- DRAMs are limited by sub-threshold leakage
 - $I_{\text{off}} \propto 1/t_{\text{ox}}$
 - Use thick oxide transistor
 - $t_{\text{ox}} \approx 3\text{nm}$ in 14nm Technology
 - Thin oxide transistors ($t_{\text{ox}} \approx 1\text{nm}$)
 - What should be the width of the device?
 - Density constraints => Unit size
 - Unit size transistor also provides least leakage



MIM Cap v/s Trench

 

MIM eDRAM Process

 


Trench eDRAM Process



- Stack capacitor requires more complex process
- M1 height above gate is increased with stacked capacitor
 - M1 parasitics significantly change when wafer is processed w/o eDRAM
 - Drives unique timings for circuit blocks processed w/ and w/o eDRAM
 - Logic Equivalency is compromised – **Trench is Better Choice**


Word-line Swing - High

- WL High Voltage – ON State
 - Technology maximum high voltage?
 - Access device is thick oxide
 - Can handle a swing of more than V_{DD} .
 - How high?
 - We wish to write a logic-1 completely
 - Logic-1 = V_{DD}
 - Access device is an NMOS transistor
 - Cannot pass V_{DD} fully if $WL = V_{DD}$
 - $WL \text{ high} = V_{PP} \geq V_{DD} + V_{Tn}$
 - What about V_{Tn} variability
 - $V_{PP} \geq V_{DD} + V_{Tn} + \Delta V_{Tn}$
- Typical value of $V_{PP} = 0.9 + 0.4 + 0.2 = 1.5V$

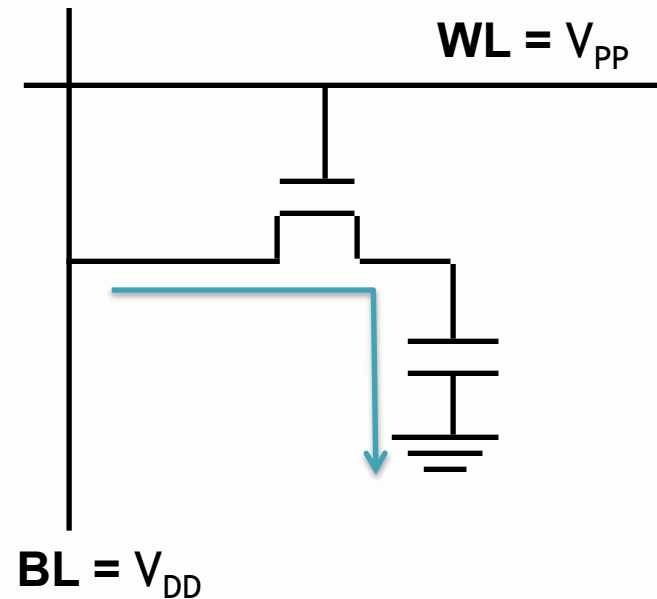


Word-line Swing - Low

- WL Low Voltage (V_{WL}) – OFF State
- BL will be pre-charged to either 0 or V_{DD}
 - BL pre-charged to 0
 - Cell storing a 1 causes leakage
 - BL pre-charged to 1
 - Cell storing a 0 causes leakage
- Need to minimize leakage current either way
- V_{GS} of access device needs to be as low as possible
 - IOFF decreases exponentially with V_{GS}
 - Can we lower the WL down to $-V_{DD}$?
 - What is the limit?
 - Lower the WL voltage down to the point where GIDL – Gate Induced Drain Leakage sets in
 - Typical value of $V_{WL} = -300$ mV

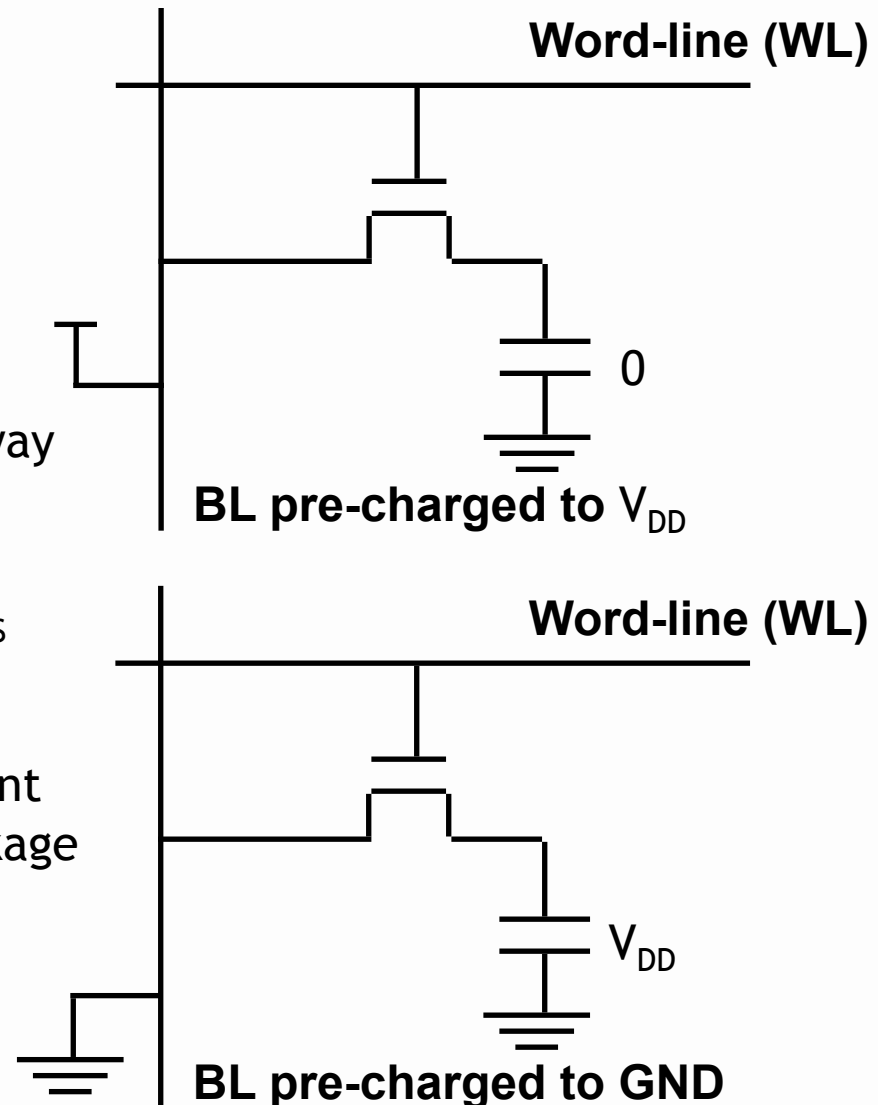


DRAM cell Cross section


 
- Store their contents as charge on a capacitor rather than in a feedback loop.
- 1T1 dynamic RAM cell has a transistor and a capacitor



CMOS VLSI design - PEARSON

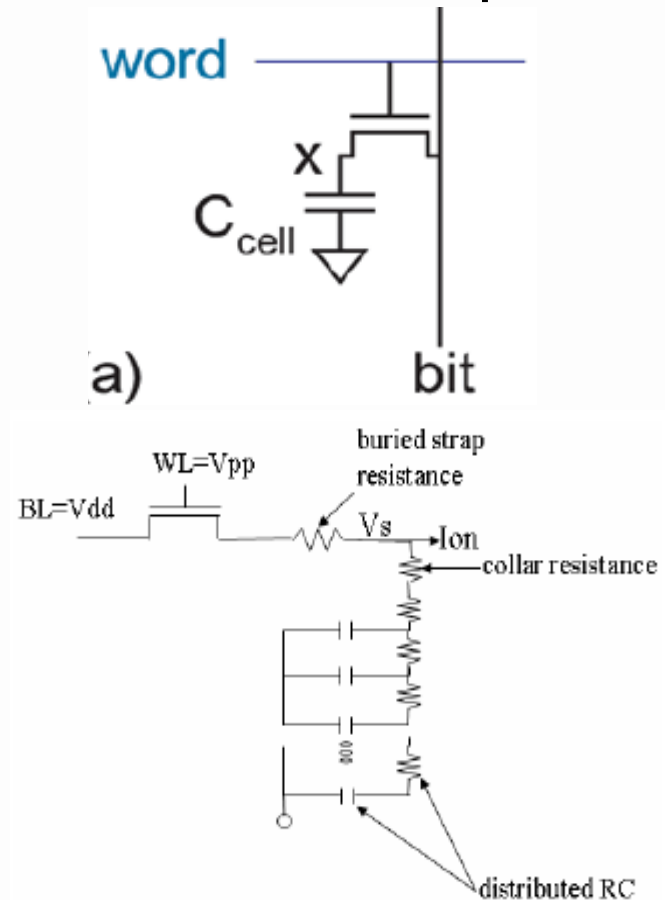


Storing data '1' in the cell

  

V_{gs} for pass transistor reduces as bitcell voltage rises, increasing R_{on}

Why there is a reduction in cell voltage after WL closes? Experiment

Classical DRAM Organization

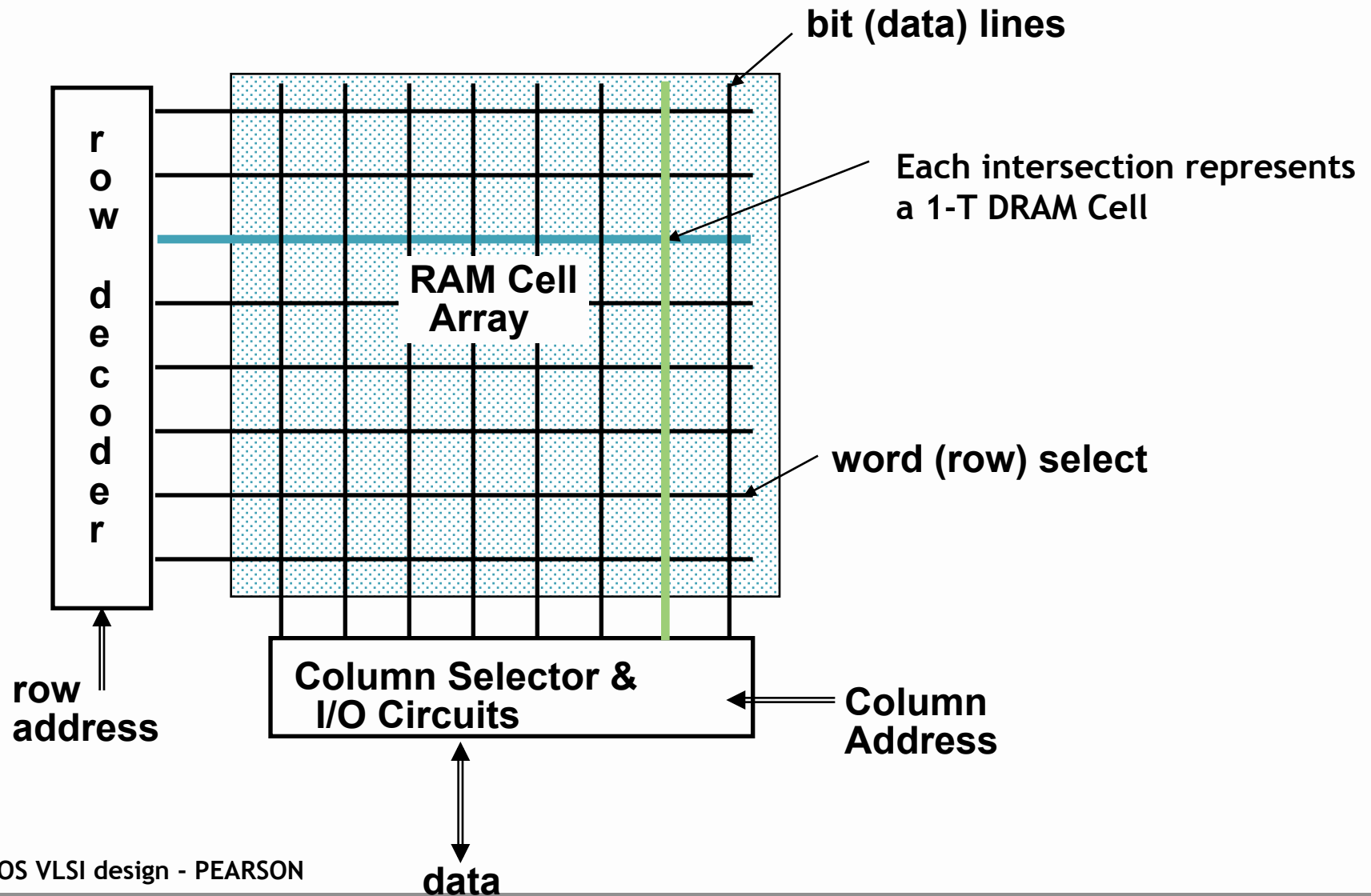

DRAM Subarray


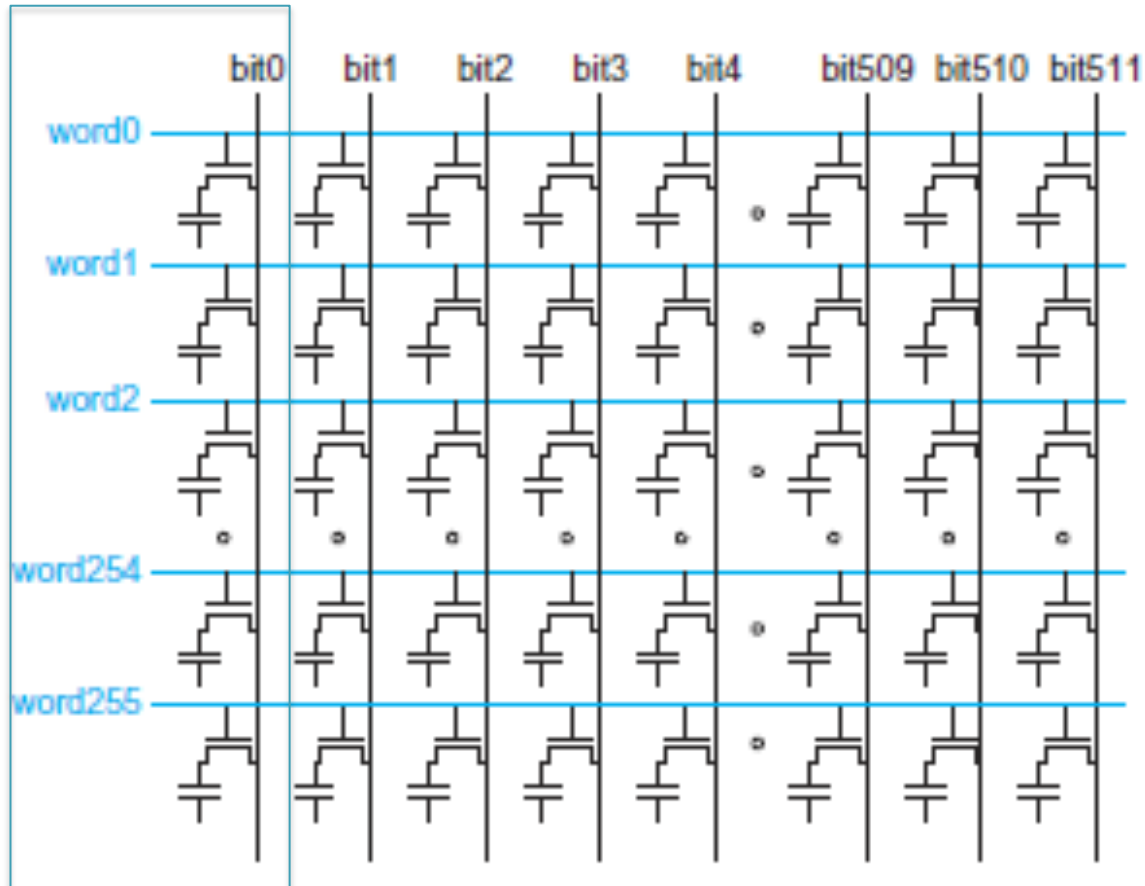


FIGURE 12.43 DRAM subarray

Trench cell layout and cross-section

 

References so far

Barth, J. et al., “A 300MHz Multi-Banked eDRAM Macro Featuring GND Sense, Bit-line Twisting and Direct Reference Cell Write,” ISSCC Dig. Tech. Papers, pp. 156-157, Feb. 2002.

Barth, J. et. al., “A 500MHz Multi-Banked Compilable DRAM Macro with Direct Write and Programmable Pipeline,” ISSCC Dig. Tech. Papers, pp. 204-205, Feb. 2004.

Barth, J. et al., “A 500MHz Random Cycle 1.5ns-Latency, SOI Embedded DRAM Macro Featuring a 3T Micro Sense Amplifier,” ISSCC Dig. Tech. Papers, pp. 486-487, Feb. 2007.


Barth, J. et al., “A 45nm SOI Embedded DRAM Macro for POWER7™ 32MB On-Chip L3 Cache,” ISSCC Dig. Tech. Papers, pp. 342-3, Feb. 2010.

Butt, N., et al., “A 0.039 μ m² High Performance eDRAM Cell based on 32nm High-K/Metal SOI Technology,” IEDM pp. 27.5.1-2, Dec 2010.

Bright, A. et al., “Creating the BlueGene/L Supercomputer from Low-Power SoC ASICs,” ISSCC Dig. Tech. Papers, pp. 188-189, Feb. 2005.


DRAM Operations

- Write
- Read
- Refresh

 


DRAM Read, Write and Refresh

 - Write:
 - 1. Drive bit line
 - 2. Select row




DRAM Read, Write and Refresh

 - Read:
 - 1. Pre-charge bit line
 - 2. Select row – Turn ON WL
 - 3. Cell and bit line share charges
 - Signal developed on bitline
 - 4. Sense the data
 - 5. **Write back: restore the value**





DRAM Read, Write and Refresh

 

- Refresh
 - 1. Just do a dummy read to every cell → auto write-back



Read - Cell transfer ratio

 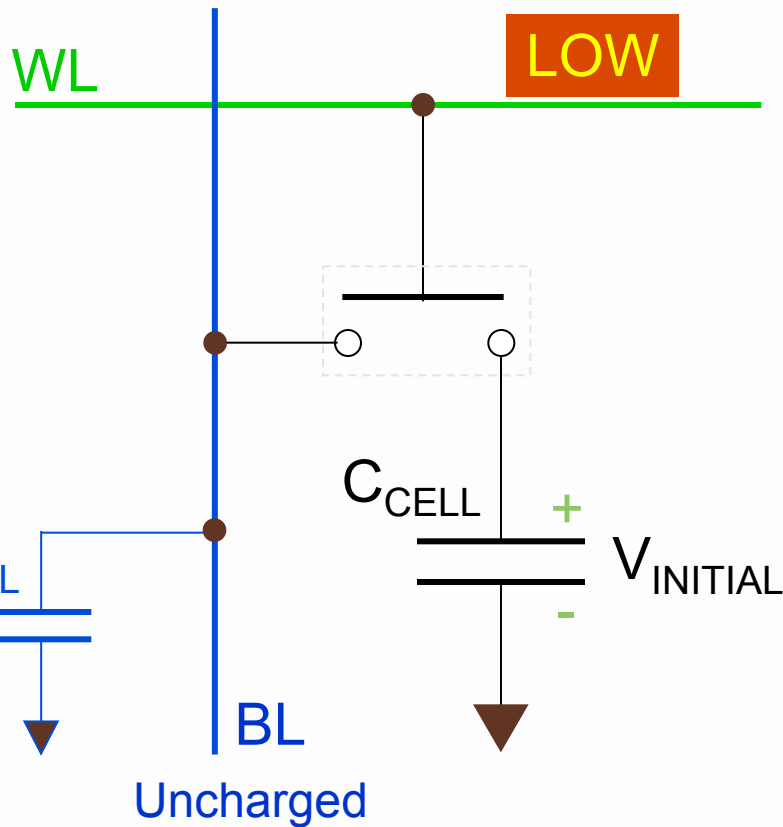

$$C_{CELL} \times V_{INITIAL} = (C_{CELL} + C_{BL}) \times V_{FINAL}$$

$$\text{Transfer ratio} = C_{CELL} / (C_{CELL} + C_{BL})$$


Cell Charge Transfer

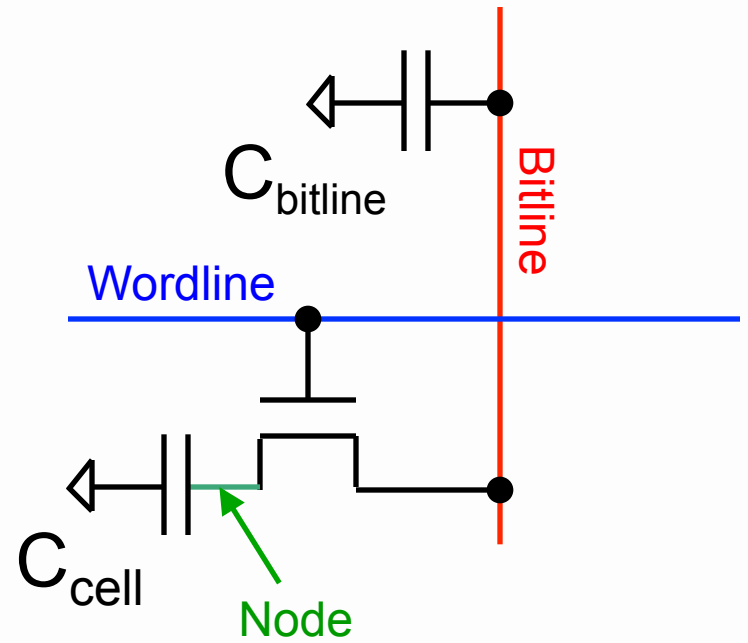 


$$\Delta V = (V_{\text{bl}} - V_{\text{cell}}) \left[\frac{C_{\text{cell}}}{C_{\text{bl}} + C_{\text{cell}}} \right]$$

Transfer ratio

Sensing

 

Signal $\Delta V > V_M$ (Trip Point)


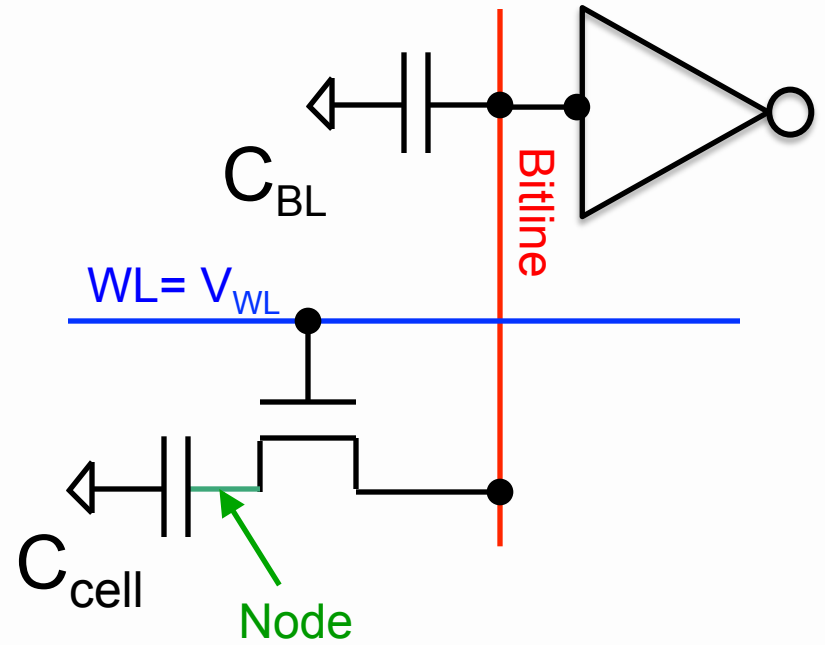


$$\Delta V = (V_{bl} - V_{cell}) \left[\frac{C_{cell}}{C_{bl} + C_{cell}} \right]$$

Transfer ratio

Retention

Signal $\Delta V > V_M$ (Trip Point)

  

$$\Delta V = (V_{bl} - V_{cell}) \left[\frac{C_{cell}}{C_{bl} + C_{cell}} \right]$$

Transfer ratio

Transfer Ratio and Signal

ΔBit-Line Voltage Calculated from Initial Conditions and Capacitances:

$$\Delta V = V_{bl} - V_f = V_{bl} - \frac{Q}{C} = V_{bl} - \left[\frac{C_{bl} * V_{bl} + C_{cell} * V_{cell}}{C_{bl} + C_{cell}} \right]$$

$$\Delta V = (V_{bl} - V_{cell}) \left[\frac{C_{cell}}{C_{bl} + C_{cell}} \right]$$

↙ Transfer Ratio (typically 0.2)

ΔBit-Line Voltage is Amplified with Cross Couple “Sense Amp”

Sense Amp Compares Bit-Line Voltage with a Reference


Bit-Line Voltage - Reference = Signal

Pos Signal Amplifies to Logical ‘1’, Neg Signal Amplifies to Logical ‘0’


Signal: # WLs on a BL

$$C_{BL} = N C_{DIFF} + N C_{M1}$$


$$TR = C_{Cell} / (C_{BL} + C_{Cell})$$

 

BL Float
at GND

 


Bits per Bit-Line v/s Transfer Ratio

 


Signal: # WLs on a BL

Short BLs are Mandatory in DRAMs

 

BL Float at GND

 

Segmentation

Array Segmentation Refers to WL / BL Count per Sub-Array

Longer Word-Line is Slower but more Area efficient (Less Decode/Drivers)

Longer Bit-Line (more Word-Lines per Bit-Line)

Less Signal (Higher Bit-Line Capacitance = Lower Transfer Ratio)

More Power (Bit-Line CV is Significant Component of DRAM Power)

Slower Performance (Higher Bit-Line Capacitance = Slower Sense Amp)

More Area Efficient (Fewer Sense Amps)

Number of Word-Lines Activated determines Refresh Interval and Power

All Cells on Active Word-Line are Refreshed

All Word-Lines must be Refreshed before Cell Retention Expires

64ms Cell Retention / 8K Word Lines = 7.8us between refresh cycles

Activating 2 Word-Lines at a time = 15.6us, 2x Bit-Line CV Power

Choice of SA

Depending on signal developed SA architecture is chosen

Direct sensing

- Requires large signal development

- An inverter can be used for sensing

- Micro sense amp (uSA) is another option


Differential sense amp

- Can sense low signal developed

This is choice between area, speed/performance

Sensing \rightarrow Signal Amplification

 Differential Voltage Amplified by Cross Couple Pair



When Set Node $< (V + \Delta V) - V_{tn1}$, $I+$ will start to flow (On-Side Conduction)

When Set Node $< (V) - V_{tn0}$, I will start to flow (Off-Side Conduction)

Off-Side Conduction Modulated by Set Speed and Amount of Signal

Complimentary X-Couple Pairs provide Full CMOS Levels on Bit-Line