
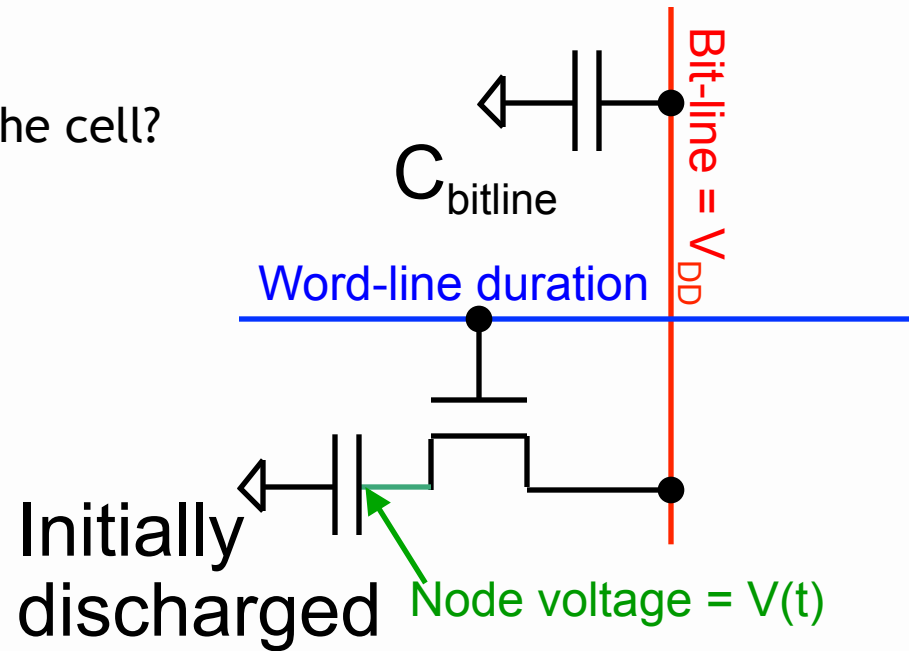


# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM Write Analysis
- ❑ eDRAM Sense-Amplifier Specification
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example
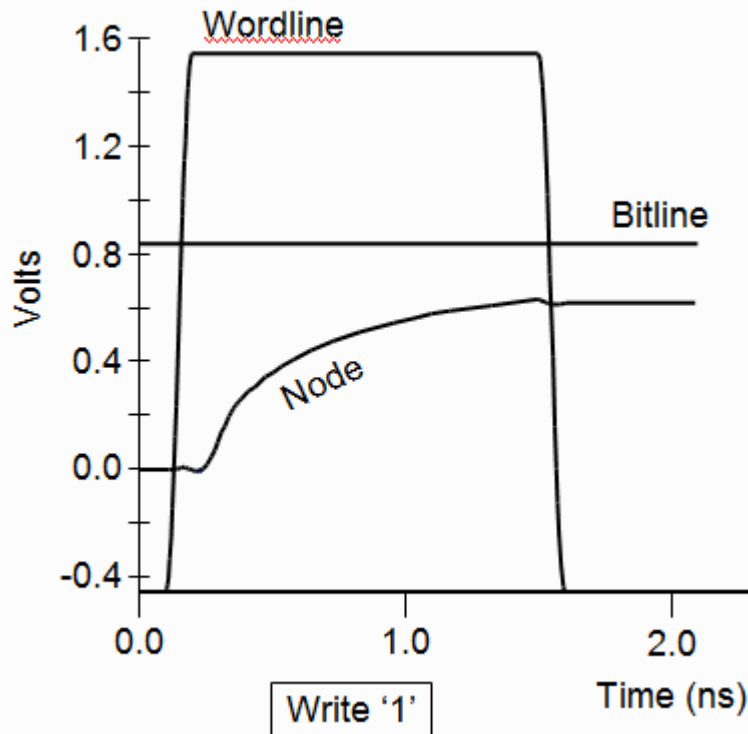
# Write-Margin

How much signal can we write into the cell?



# Write-Margin


How much signal can we write into the cell?

Assume:

- Bit-line is charged to  $V_{DD}$
- Word-line rises instantly to  $V_{PP}$

$$V_{GS} = V_{PP} - V(t)$$

$$V_{DS} = V_{DD} - V(t)$$

 

# Write-Margin

How much signal can we write into the cell?

Assume:

- Bit-line is charged to  $V_{DD}$
- Word-line rises instantly to  $V_{PP}$

$$V_{GS} = V_{PP} - V(t)$$


$$V_{DS} = V_{DD} - V(t)$$

Access transistor is a thick oxide device  $\Rightarrow V_{DSAT} \gg V_{PP}$

$$V_{DS} = V_{DD} - V(t) < V_{GS} - V_{Tn} = V_{PP} - V(t) - V_{Tn}$$

$$V_{PP} \geq V_{DD} + V_{Tn} + \Delta V_{Tn}$$

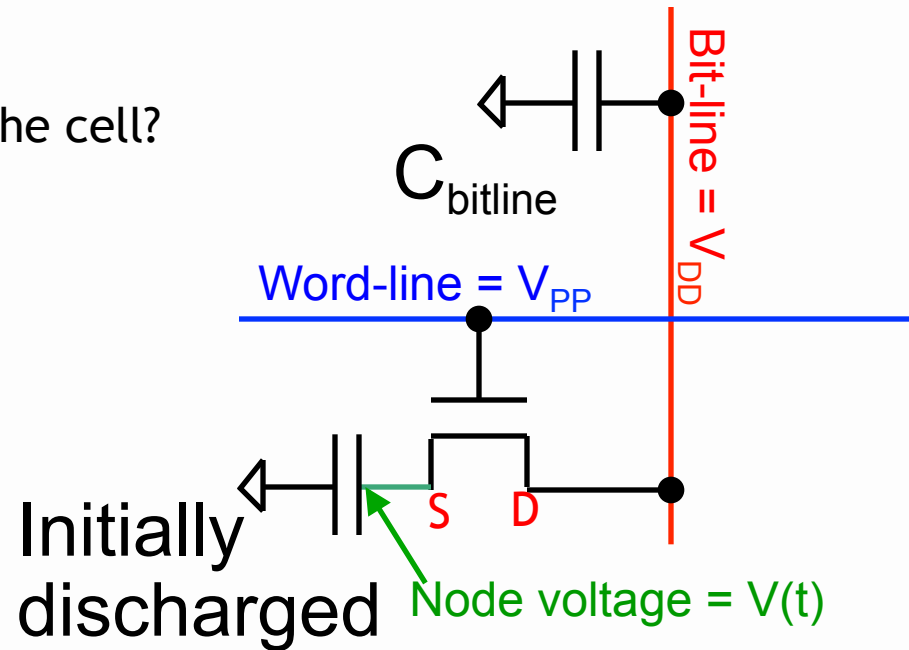*Access device is in the linear region throughout*



# Write-Margin

$$I_{DS} = \mu_n C_{OX} (W/L) V_{DS} (V_{GS} - V_{Tn} - V_{DS}/2) = C_{Cell} dV/dt$$

$$V_{GS} = V_{PP} - V(t)$$

$$V_{DS} = V_{DD} - V(t)$$

Assume you wish to write a voltage  $V_f$  into the cell in a time  $T_{WRITE}$


Solving you will get:

$$T_{WRITE} = 2 T_0 \ln[(1 - V_f/2\Delta)/(1 - V_f/V_{DD})]$$

Where

$$T_0 = \{C_{cell} / [\mu_n C_{OX} (W/L) (2\Delta - V_{DD})]\}$$

$$\Delta = V_{PP} - V_{Tn} - V_{DD}/2$$

 

$$I_{DS} = \mu_n C_{ox} \left( \frac{W}{L} \right) \cdot V_{DS} \left( V_{GS} - V_{Tn} - \frac{V_{DS}}{2} \right)$$

$$I_{DS} = C \frac{dV}{dt} \quad (C = C_{cell})$$

$$\Rightarrow K V_{DS} \left( V_{GS} - V_{Tn} - \frac{V_{DS}}{2} \right) = C \frac{dV}{dt}$$

$$K = \mu_n C_{ox} \left( \frac{W}{L} \right)$$

$$\Rightarrow \left( \frac{K}{C} \right) \cdot (V_{DD} - V) \left( V_{PP} - V - V_{Tn} - \frac{V_{DD} - V}{2} \right) = \frac{dV}{dt}$$

$$\Rightarrow \left( \frac{K}{C} \right) (V_{DD} - V) \left( V_{PP} - V_{Tn} - \frac{V_{DD}}{2} - \frac{V}{2} \right) = \frac{dV}{dt}$$

$$\Rightarrow \frac{K}{C} dt = \frac{dV}{(V_{DD} - V) \left( \Delta - \frac{V}{2} \right)}$$

$$\text{Where } \Delta = \left( V_{PP} - V_{Tn} - \frac{V_{DD}}{2} \right)$$

$$\Rightarrow \frac{K}{C} dt = \frac{2 dV}{(2\Delta - V_{DD})} \times \left[ \frac{1}{V_{DD} - V} - \frac{1}{2\Delta - V} \right]$$

$$\Rightarrow \frac{K}{C} \tau_{WRITE} = \frac{2}{2\Delta - V_{DD}} \cdot \ln \left[ \frac{2\Delta - V}{V_{DD} - V} \right] \Bigg|_0^{V_f}$$



$$\Rightarrow \tau_{WRITE} = \frac{2C}{K(2\Delta - V_{DD})} \left[ \ln \left[ \left( \frac{2\Delta - V_f}{V_{DD} - V_f} \right) \left( \frac{V_{DD}}{2\Delta} \right) \right] \right]$$

$$\tau_{WRITE} = \frac{2C}{K(2\Delta - V_{DD})} \ln \left[ \frac{1 - V_f/2\Delta}{1 - V_f/V_{DD}} \right]$$


# Write-Margin – Analysis

$$T_{\text{WRITE}} = 2 T_0 \ln[(1-V_f/2\Delta)/(1-V_f/V_{\text{DD}})]$$

Where

$$T_0 = \{C_{\text{cell}} / [\mu_n C_{\text{OX}} (W/L)(2\Delta - V_{\text{DD}})]\}$$
 
$$\Delta = V_{\text{PP}} - V_{\text{Tn}} - V_{\text{DS}}/2$$



1. What happens when  $V_{\text{PP}}$  is increased?
2. What happens when  $V_f \rightarrow V_{\text{DD}}$


# Write-Margin – Analysis

$$T_{\text{WRITE}} = 2 T_0 \ln[(1-V_f/2\Delta)/(1-V_f/V_{\text{DD}})]$$

Where

$$T_0 = \{C_{\text{cell}} / [\mu_n C_{\text{OX}} (W/L)(2\Delta - V_{\text{DD}})]\}$$
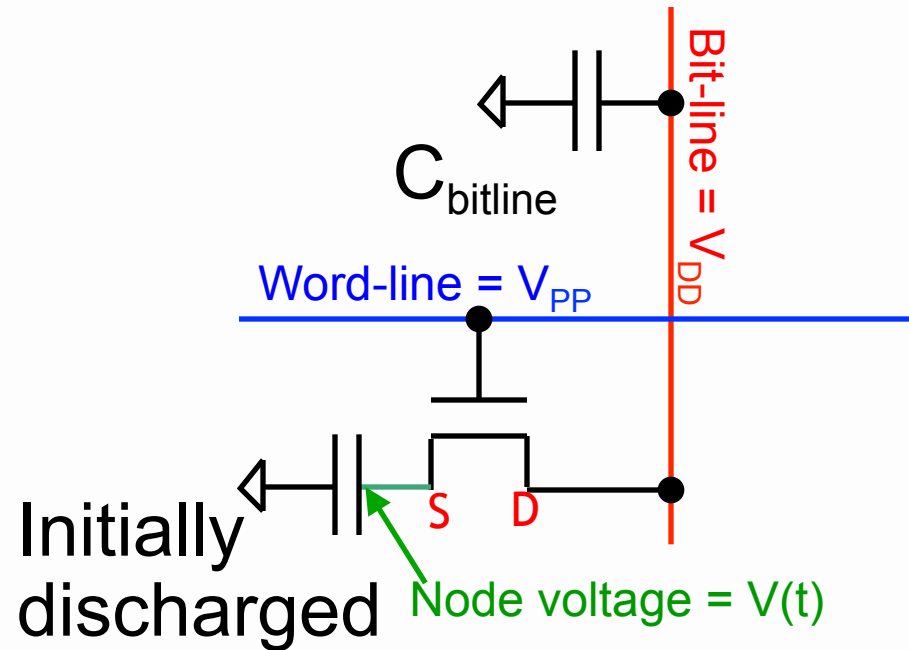
$$\Delta = V_{\text{PP}} - V_{\text{Tn}} - V_{\text{DD}}/2$$



1. What happens when  $V_{\text{PP}}$  is increased?

- $\Delta$  increases and  $T_0$  decreases
- $\ln[(1-V_f/2\Delta)/(1-V_f/V_{\text{DD}})]$  increases logarithmically
- $T_{\text{WRITE}}$  effectively decreases.
- However WL power goes up as  $(V_{\text{PP}} - V_{\text{WL}})^2$



# Write-Margin – Analysis

$$T_{\text{WRITE}} = 2 T_0 \ln[(1-V_f/2\Delta)/(1-V_f/V_{\text{DD}})]$$

Where


$$T_0 = \{C_{\text{cell}} / [\mu_n C_{\text{OX}} (W/L)(2\Delta - V_{\text{DD}})]\}$$

$$\Delta = V_{\text{PP}} - V_{\text{Tn}} - V_{\text{DS}}/2$$



1. What happens when  $V_f \rightarrow V_{\text{DD}}$

- $(1-V_f/V_{\text{DD}})$  approaches 0
- $\ln[(1-V_f/2\Delta)/(1-V_f/V_{\text{DD}})]$  shoots to  $\infty$

 **You cannot write a FULL  $V_{\text{DD}}$  into the cell in finite time**





# Storing data '1' in the cell

  

$V_{gs}$  for pass transistor reduces as bitcell voltage rises, increasing  $R_{on}$

Why there is a reduction in cell voltage after WL closes? Experiment

# Reality

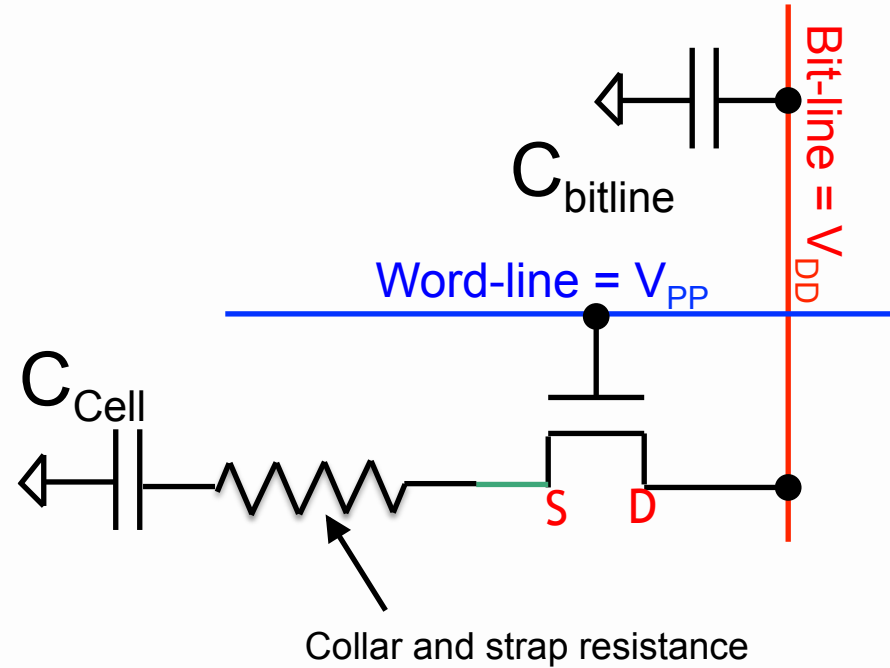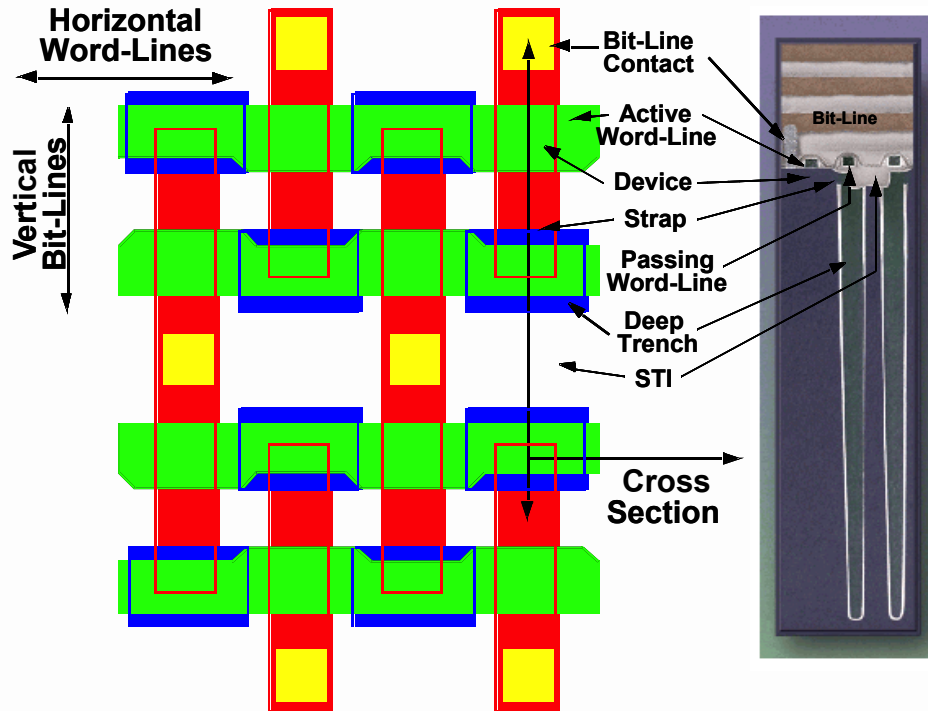

The node takes longer to charge than what we calculated analytically  
Conclusions do not change:


- Increasing  $V_{PP}$  decreases the write time
- Cannot write a full  $V_{DD}$  in finite time

# Topics


- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM Write Analysis
- ❑ eDRAM Sense-Amplifier Specification
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example

# Signal: # WLs on a BL

Short BLs are Mandatory in DRAMs

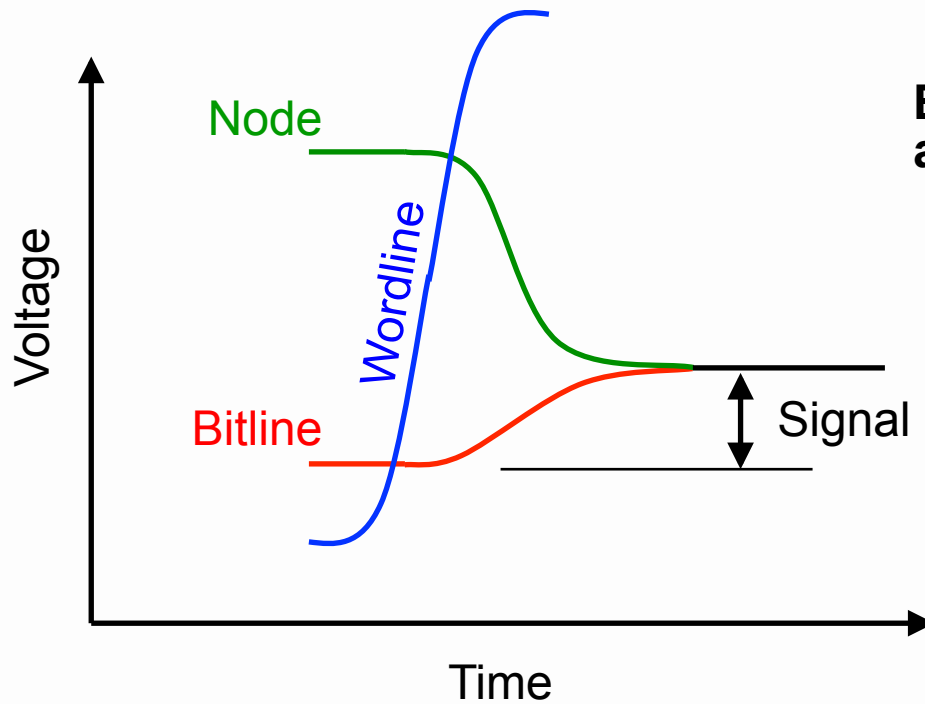

BL Float at GND

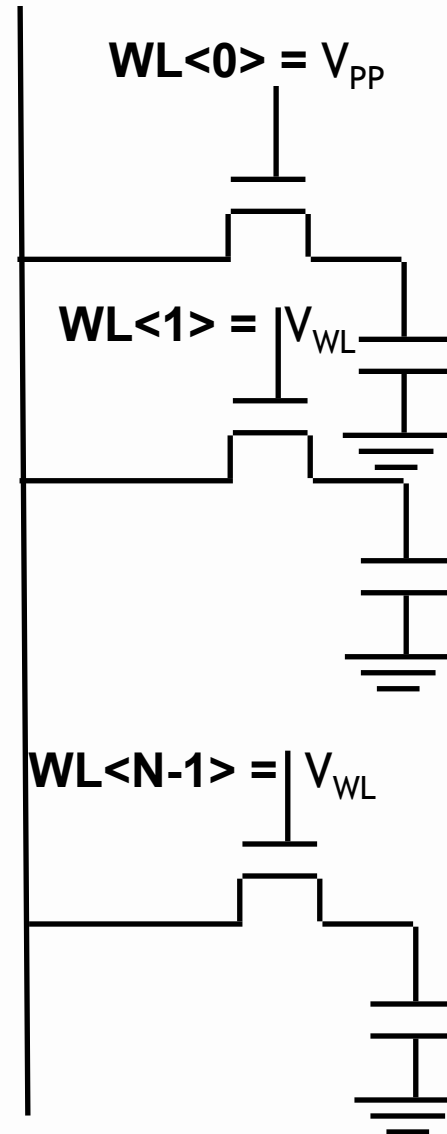

# SRAM vs DRAM



Assume a 1Mb memory with 512 WLs and 2048 BLs and 8 Columns. i.e. 256 DLs

	SRAM	DRAM
#WLs per BL	512	32
# BLs per DL	8	8
Sharing Sense Amps across columns	Yes	Possible?
Effective number of cells connected to a SA	4096	?
# Sense Amps	256	?

# Half Select Condition - SRAM

**BLt0 = Float @  $V_{DD}$**



**BLc0 = Float @  $V_{DD}$**

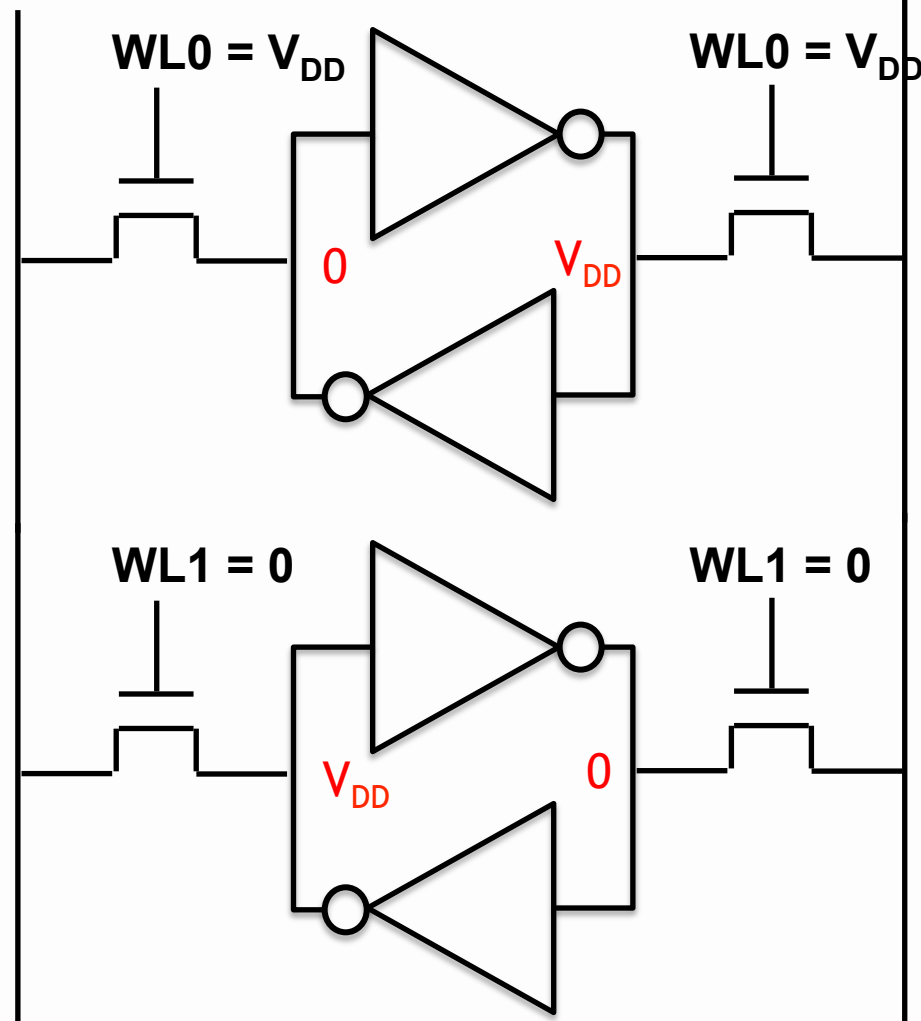 

**BLt1 =  $V_{DD}$**



**BLc1 =  $V_{DD}$**

# Half Select Condition - eDRAM

 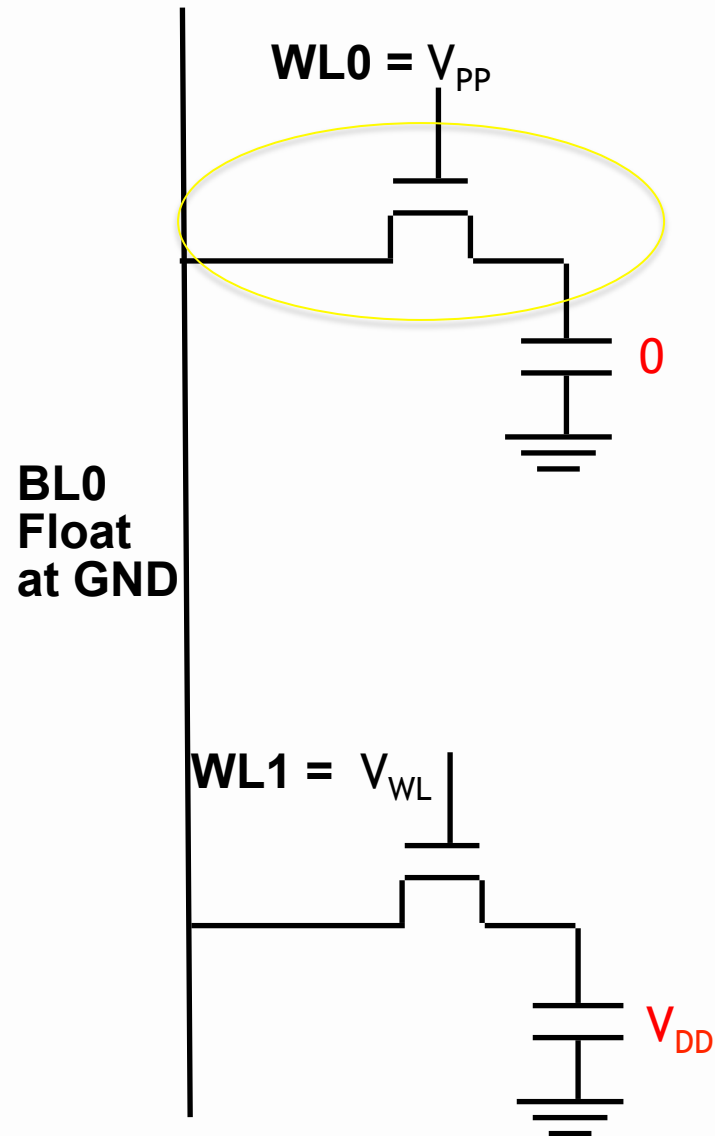



# Half Select Condition - eDRAM

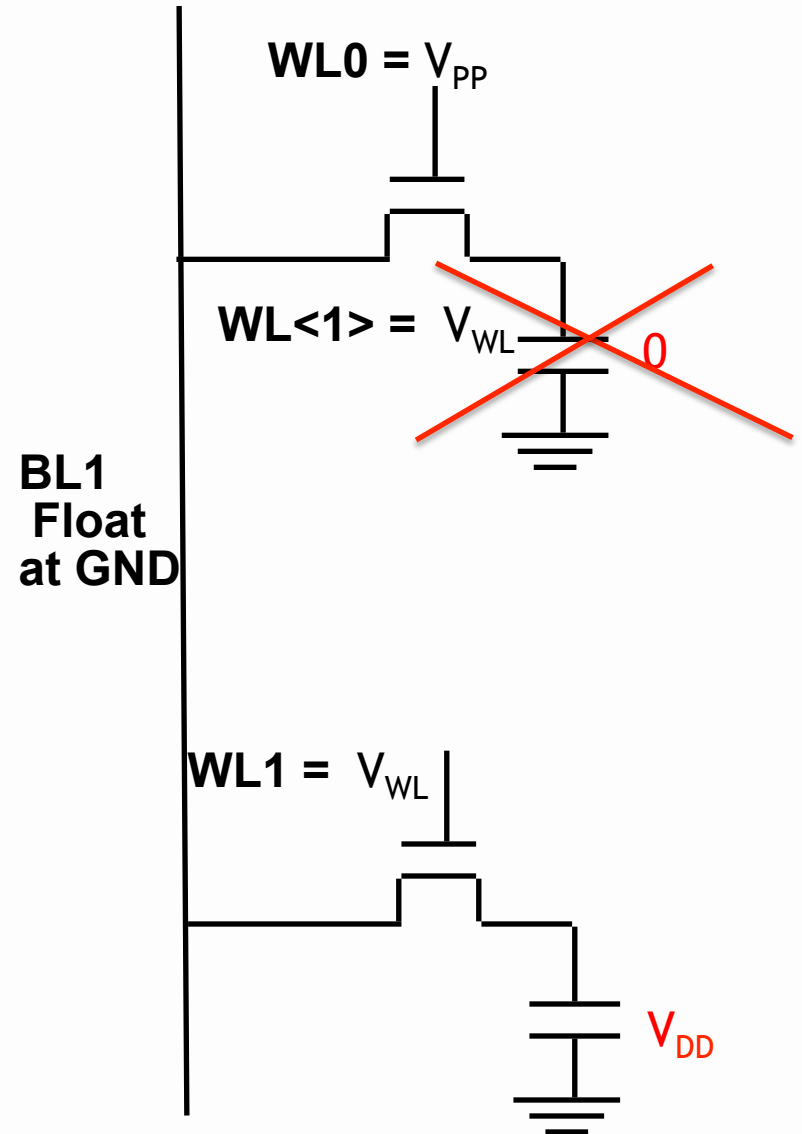 

# SRAM vs DRAM

Assume a 1Mb memory with 512 WLs and 2048 BLs and 8 Columns. i.e. 256 DLs

	SRAM	DRAM
#WLs per BL	512	32
# BLs per DL	8	8
Sharing Sense Amps across columns	Yes	No
Effective number of cells connected to a SA	4096	32
# Sense Amps	256	

## Extremely small SA

- Number of transistors
- Sizes of transistors

# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM Write Analysis
- ❑ eDRAM Sense-Amplifier Specification
- ❑ eDRAM operational details (case study)
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM
- ❑ Understanding Timing diagram - An example


# DRAM Operation Details (Case Study)

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 43, NO. 1, JANUARY 2008


**A 500 MHz Random Cycle, 1.5 ns Latency, SOI Embedded DRAM Macro Featuring a Three-Transistor Micro Sense Amplifier (John Barth/IBM)**
 
# Micro Sense Architecture


- Hierarchical Direct Sense
- Short Local Bit-Line (LBL)
  - 33 Cells per LBL
- 8 Micro Sense Amps ( $\mu$ SA) per Global Sense Amp (GSA)
- Write Bit-Line (WBL)
  - Uni-Directional
- Read Bit-Line (RBL)
  - Bi-Directional




# Sense Hierarchy - Motivation

 

# Micro Sense Hierarchy - Three levels

 

# 3T uSA operation

 

## Pre-charge

WL is low. WBL and RBL both pre-charged to HIGH. Next GSA drives WBL low. LBL floats to GND level

## Read "0"

LBL remains LOW. RBL is HIGH. Sensed as a "0"

## Read "1"

LBL is HIGH. Turns on RH, pulls RBL LOW. + feedback as pFET FB turns ON. Sensed as a "1"

## Write "1"


GSA pulls RBL to GND. FB pFET turns ON. Happens while WL rises (direct write)

## Write "0"


WBL is HIGH, PCW0 ON. Clamps LBL to GND. As WL activates.



# Simulations - Write

 


# Simulations - Read

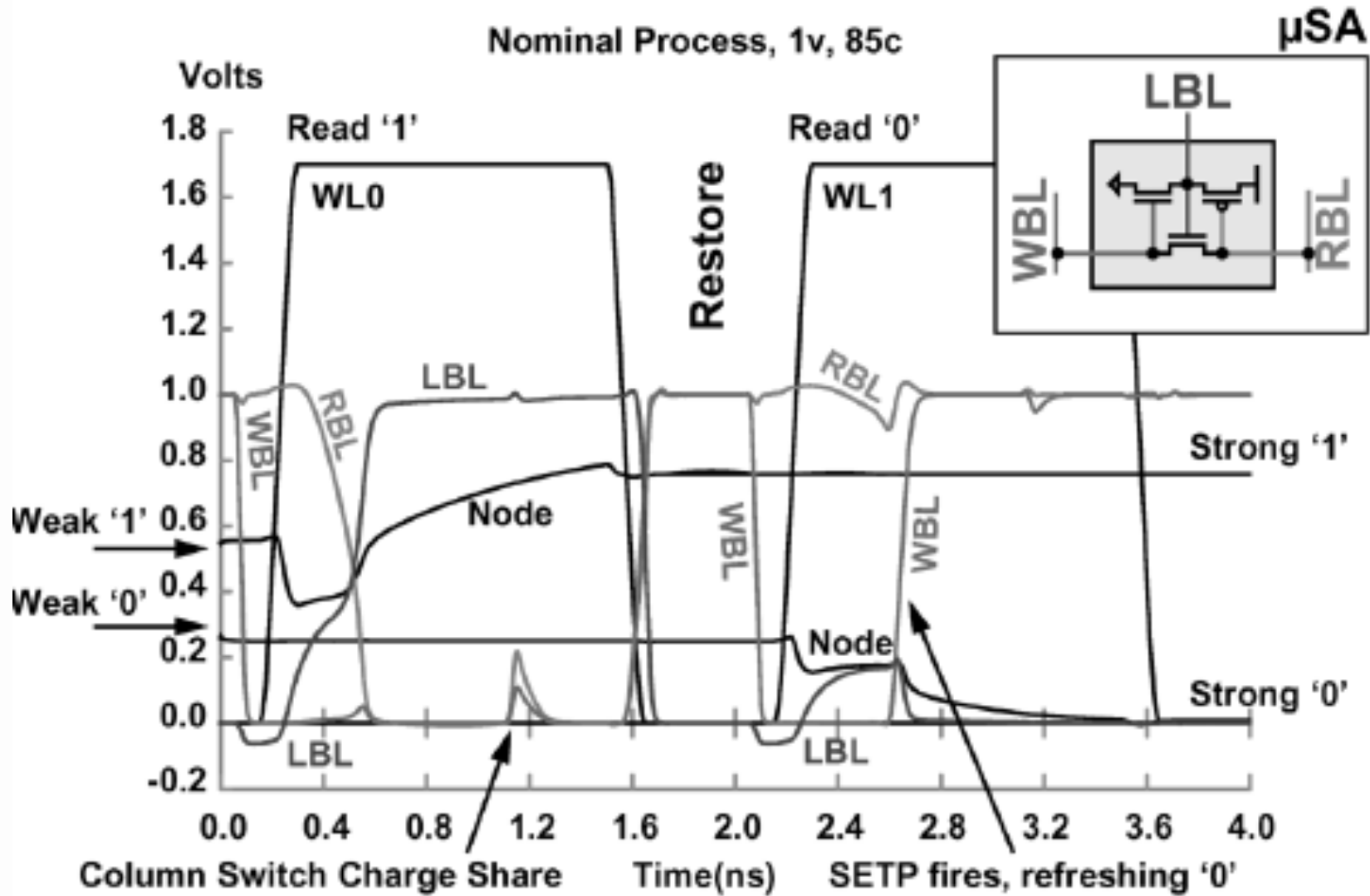

(b)


# Micro Sense Hierarchy - Three levels

 


 
# Layout Floor plan of Array+SA

GSA Should fit into the bitcell width or  $n \cdot \text{bitcell width}$


Thus, distributed GSA on two sides of bitcell array



# Layout Floor plan of Array+SA

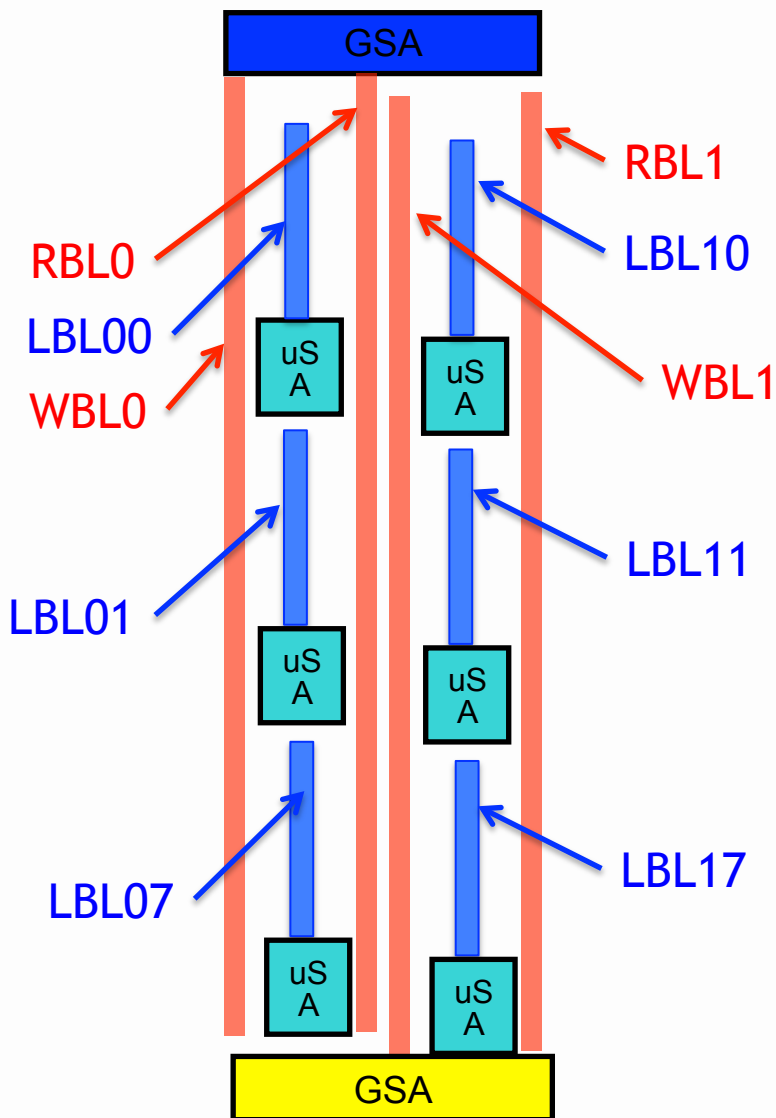 


# Column Interleave

 


- 1 of 8 Column Select Lines (CSL)
- Fire Early for Write
- Fire Late to Support Concurrent Cache Directory Lookup

# LAYOUT of array

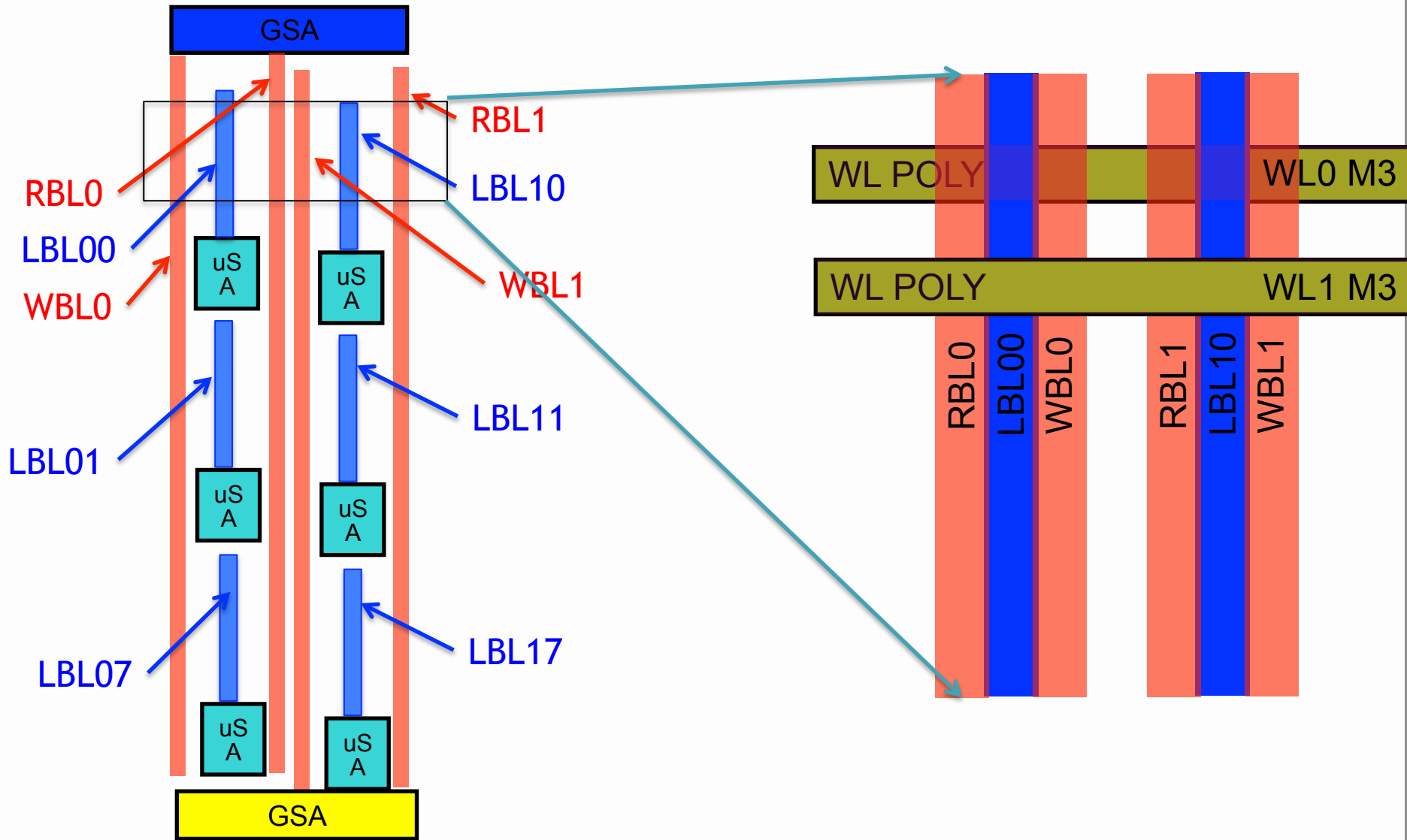


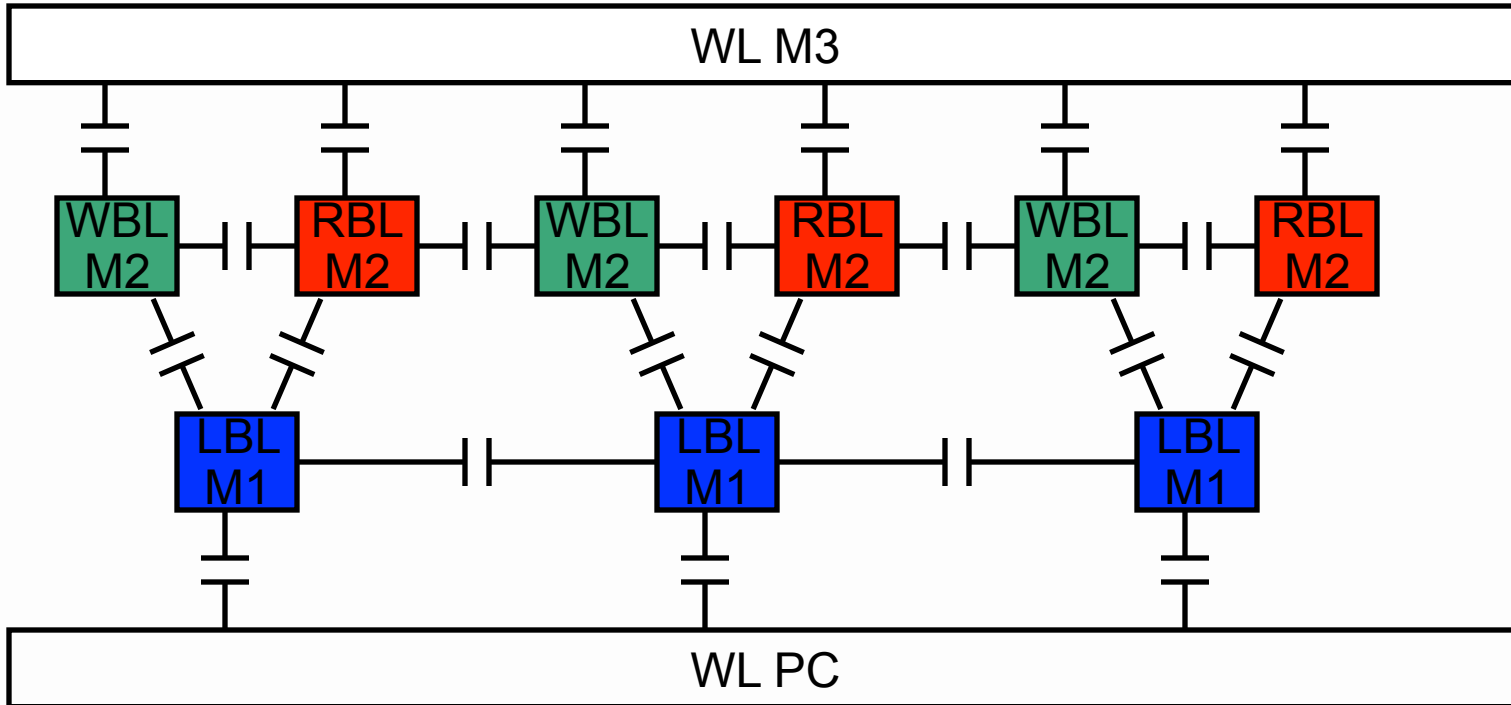
# Micro Sense Local Bit-line Cross Section



Single Ended Sense – Twist not effective  
Line to Line Coupling must be managed




# Micro Sense Coupling Mechanisms

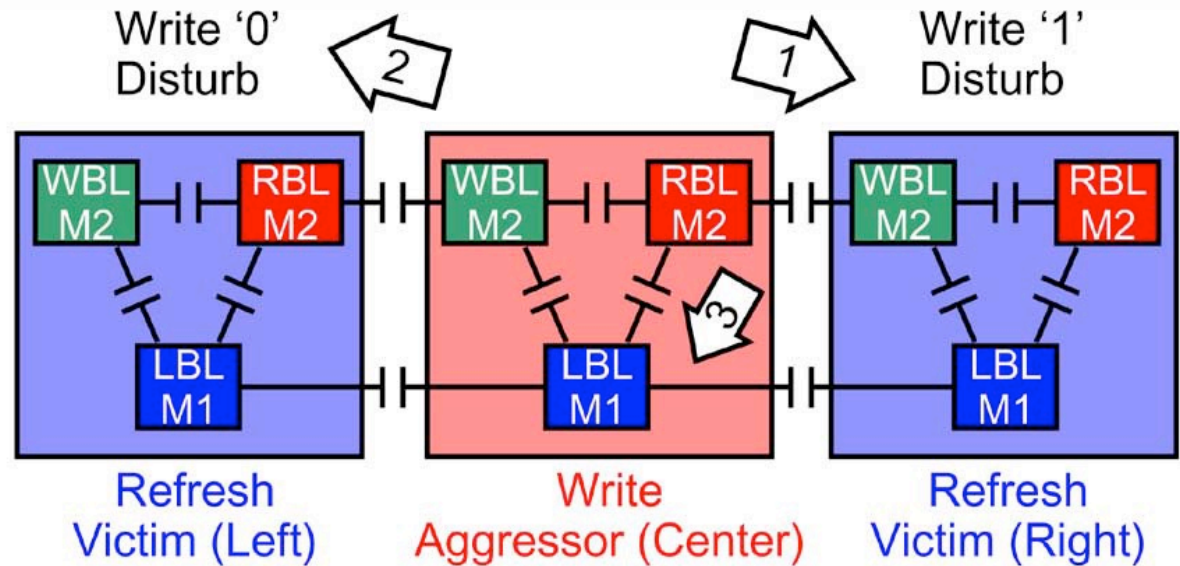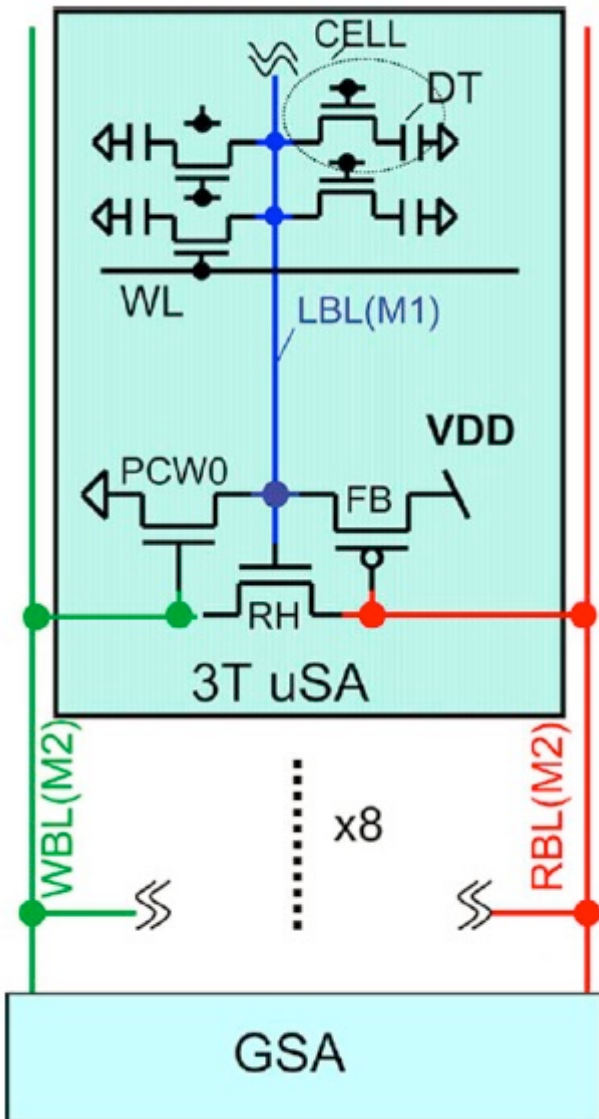

1. Write '1' Couples **WBL** below Ground Increasing RH leakage during Refresh '0'
2. Write '0' Couples **RBL** above VDD Delaying Feedback during Refresh '1'
3. Read '1' Couples Half-Selected LBL Below GND Increasing Array Device Sub-VT Leakage

# Half Selected LBL

 

- Accessing one of WL0-32
- Cell connected is on LBL00
- LBL01-07 – Half Selected LBLs