


# DRAM Operation Details (Case Study)

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 43, NO. 1, JANUARY 2008


**A 500 MHz Random Cycle, 1.5 ns Latency, SOI Embedded DRAM Macro Featuring a Three-Transistor Micro Sense Amplifier (John Barth/IBM)**
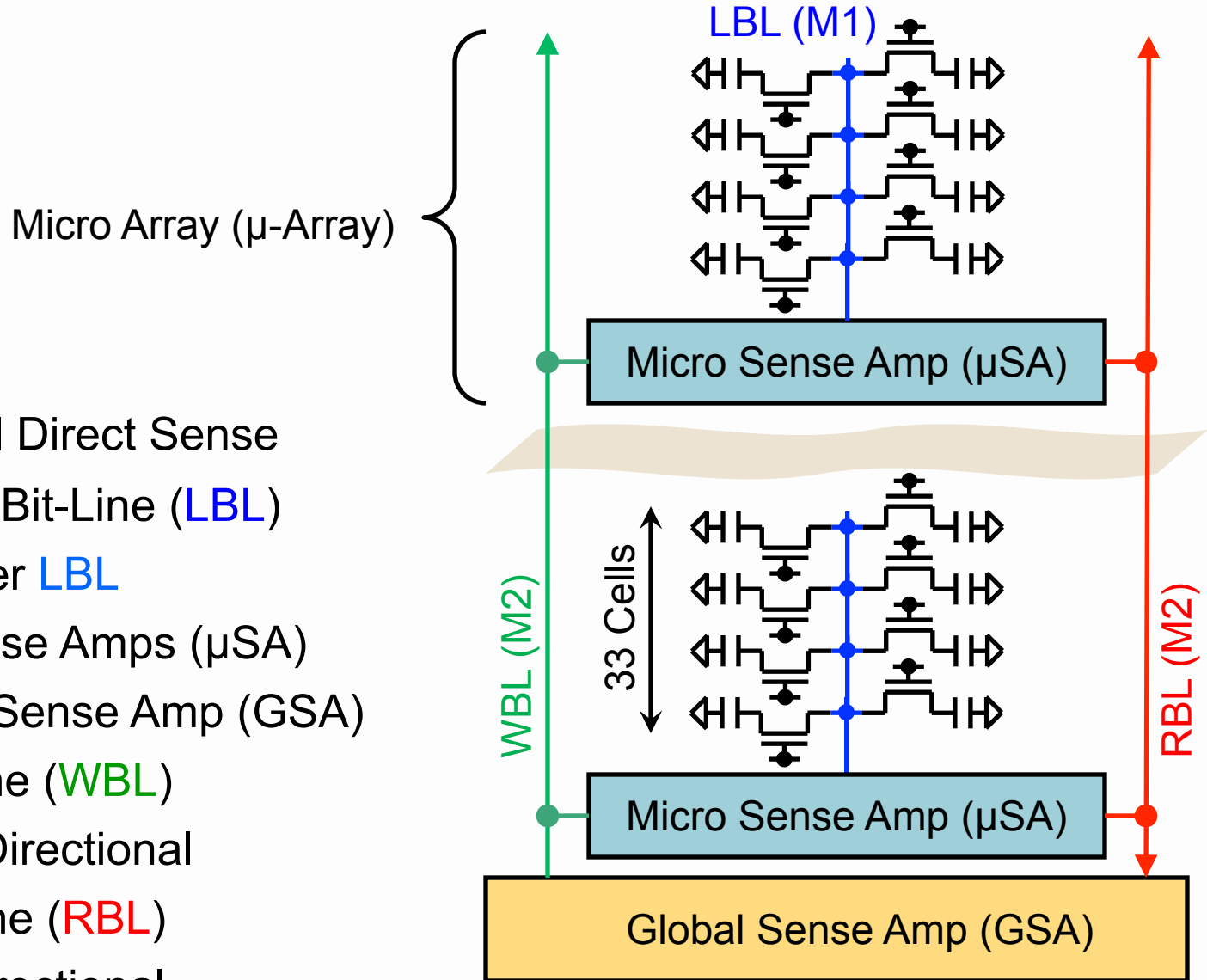
# Micro Sense Architecture


- Hierarchical Direct Sense
- Short Local Bit-Line (LBL)
  - 33 Cells per LBL
- 8 Micro Sense Amps ( $\mu$ SA) per Global Sense Amp (GSA)
- Write Bit-Line (WBL)
  - Uni-Directional
- Read Bit-Line (RBL)
  - Bi-Directional




# Sense Hierarchy - Motivation

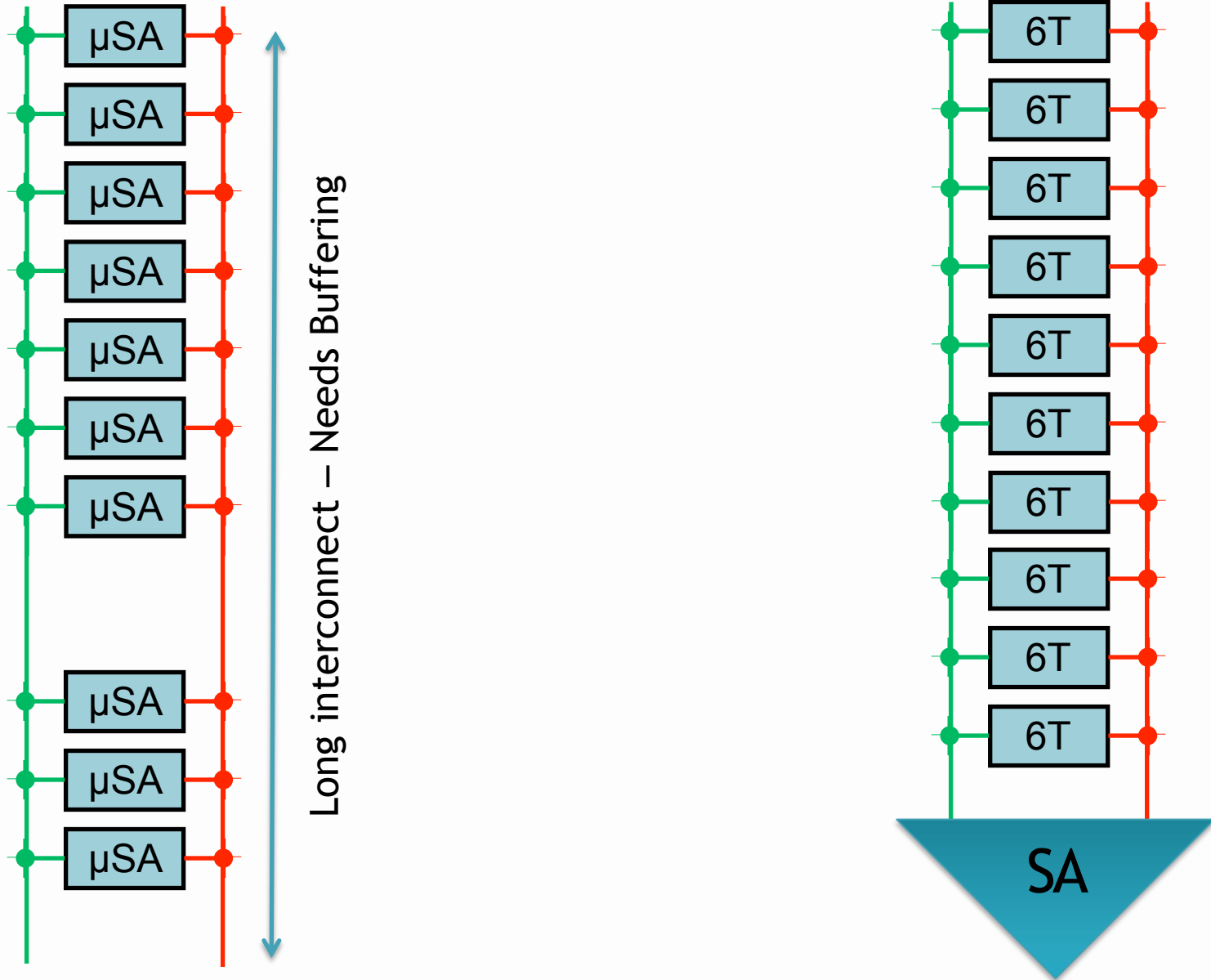

# Micro Sense Hierarchy - Three levels

 

# 3T uSA operation

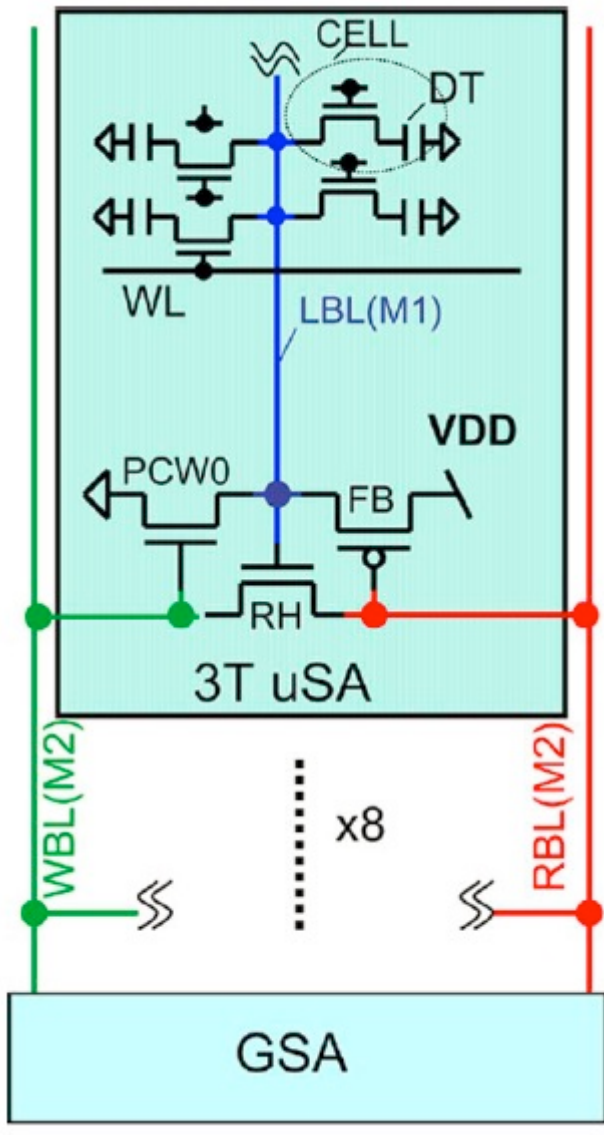

## Pre-charge

WL is low. WBL and RBL both pre-charged to HIGH. Next GSA drives WBL low. LBL floats to GND level

## Read "0"

LBL remains LOW. RBL is HIGH. Sensored as a "0"

## Read "1"

LBL is HIGH. Turns on RH, pulls RBL LOW. + feedback as pFET FB turns ON. Sensored as a "1"


## Write "1"

GSA pulls RBL to GND. FB pFET turns ON. Happens while WL rises (direct write)


## Write "0"

WBL is HIGH, PCW0 ON. Clamps LBL to GND. As WL activates.

# Simulations - Write

 


# Simulations - Read

 

(b)

JSSC08

# Micro Sense Hierarchy - Three levels

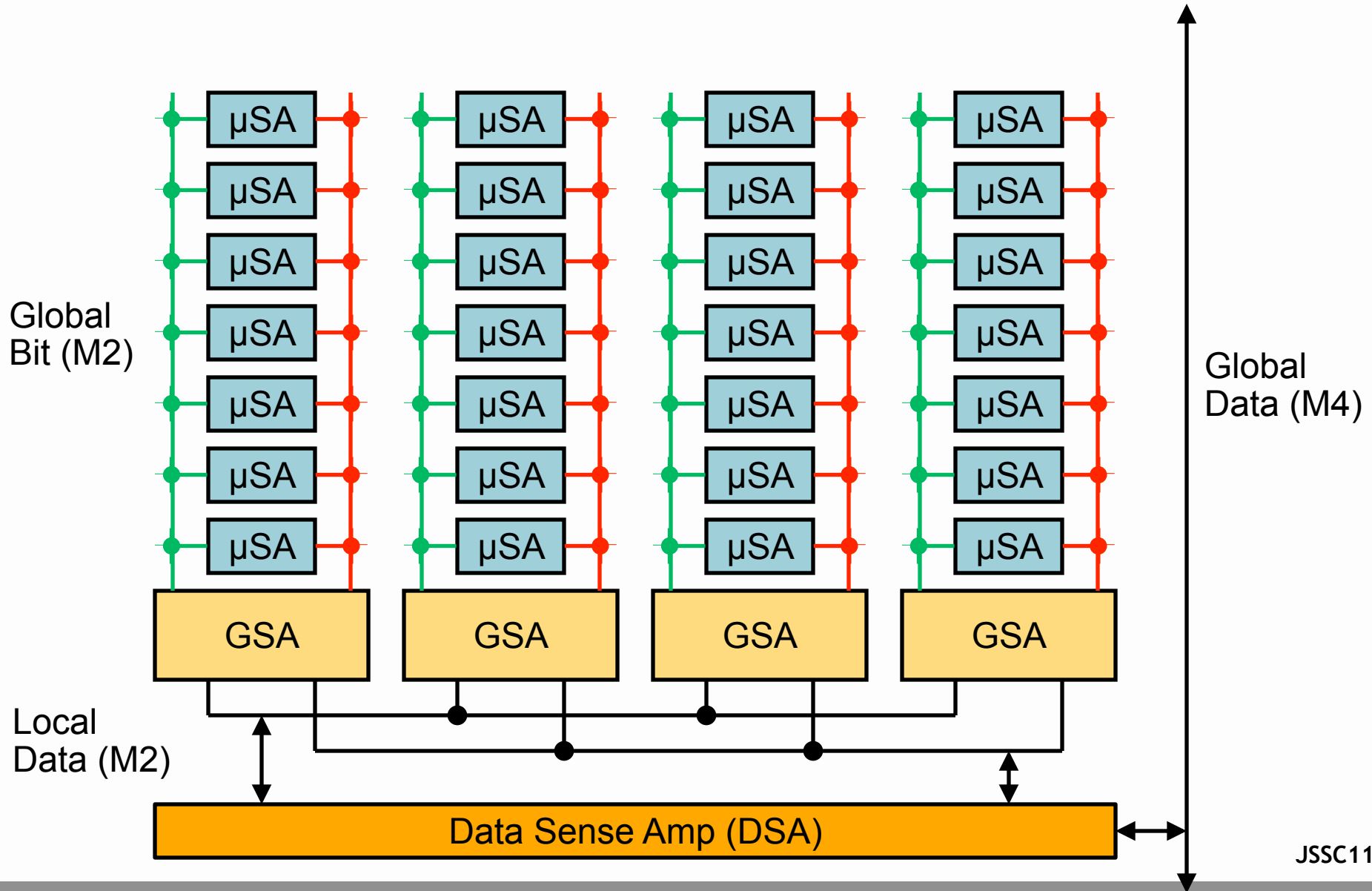





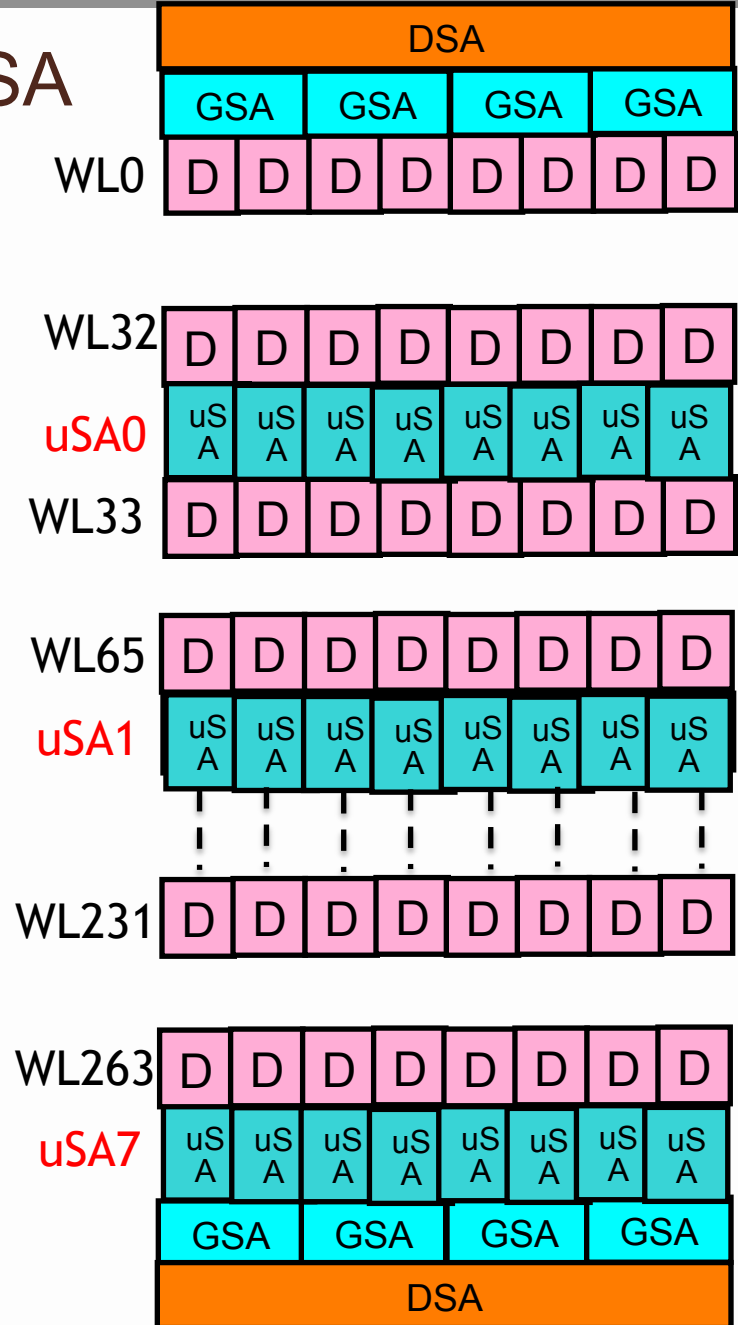
# Layout Floor plan of Array+SA

GSA Should fit into the bitcell width or  $n \cdot \text{bitcell width}$


Thus, distributed GSA on two sides of bitcell array



# Layout Floor plan of Array+SA

  


# Column Interleave

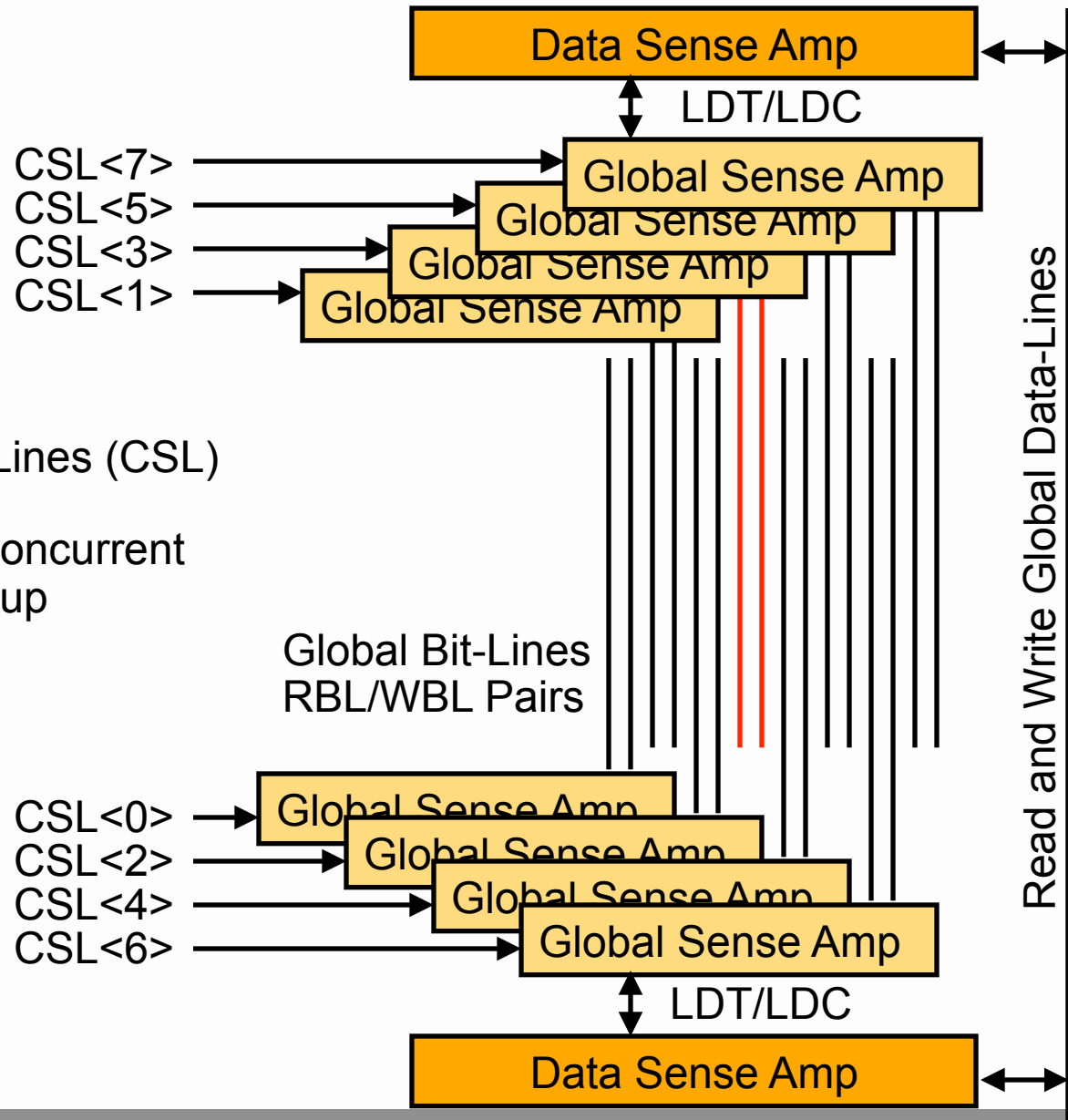


- 1 of 8 Column Select Lines (CSL)
- Fire Early for Write
- Fire Late to Support Concurrent Cache Directory Lookup

# LAYOUT of array


 

 
# Micro Sense Local Bit-line Cross Section




Single Ended Sense – Twist not effective  
Line to Line Coupling must be managed

# Micro Sense Coupling Mechanisms

  

1. Write '1' Couples **WBL** below Ground Increasing RH leakage during Refresh '0'
2. Write '0' Couples **RBL** above VDD Delaying Feedback during Refresh '1'
3. Read '1' Couples Half-Selected LBL Below GND Increasing Array Device Sub-VT Leakage


# Half Selected LBL

 

- Accessing one of WL0-32
- Cell connected is on LBL00
- LBL01-07 – Half Selected LBLs


# Micro Sense Evolution

 1. Write Zero (W0)
2. Read Head (RH)
3. Feed-Back (FB)




Barth, ISSCC'07

 4. PFET Header (PH)
  - LBL Power Gate
  - LBL Leakage



Klim, VLSI'07

5. Pre-Charge (PC)
  - WBL Power (Write '0' Only)
6. NFET Footer (NF)
  - RBL Leakage
  - Decompose Pre-Charge and Read Enable (MWL\_RE)

 

JSSC11


Power Reduction

Power Reduction  
Traded for Transistor Count

Increased Transistor Count




# Micro Sense Hierarchy - Three levels

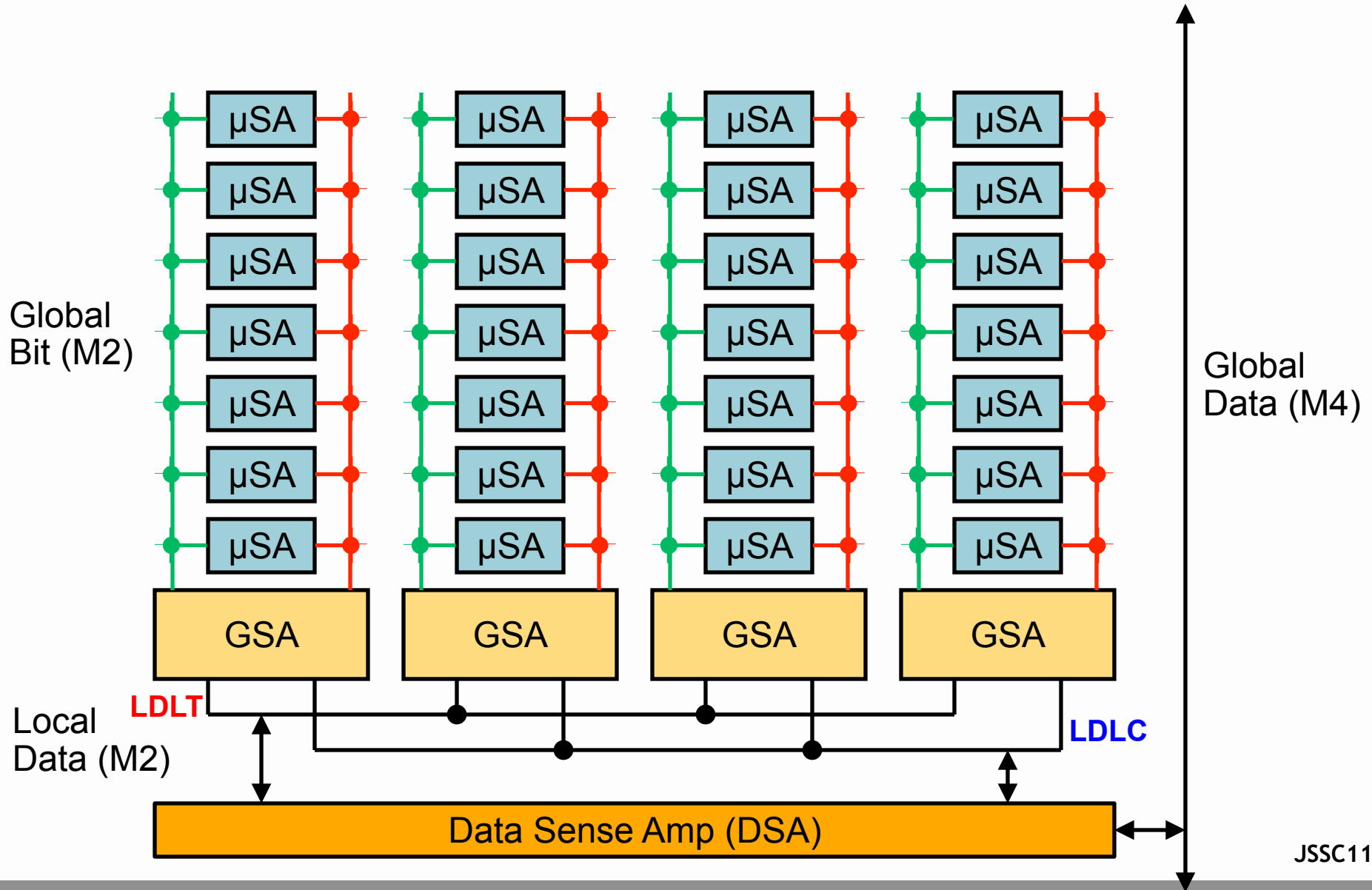


# Micro Sense Architecture ( $\mu$ SA)

3 Transistors

 


# Micro Sense Architecture ( $\mu$ SA)

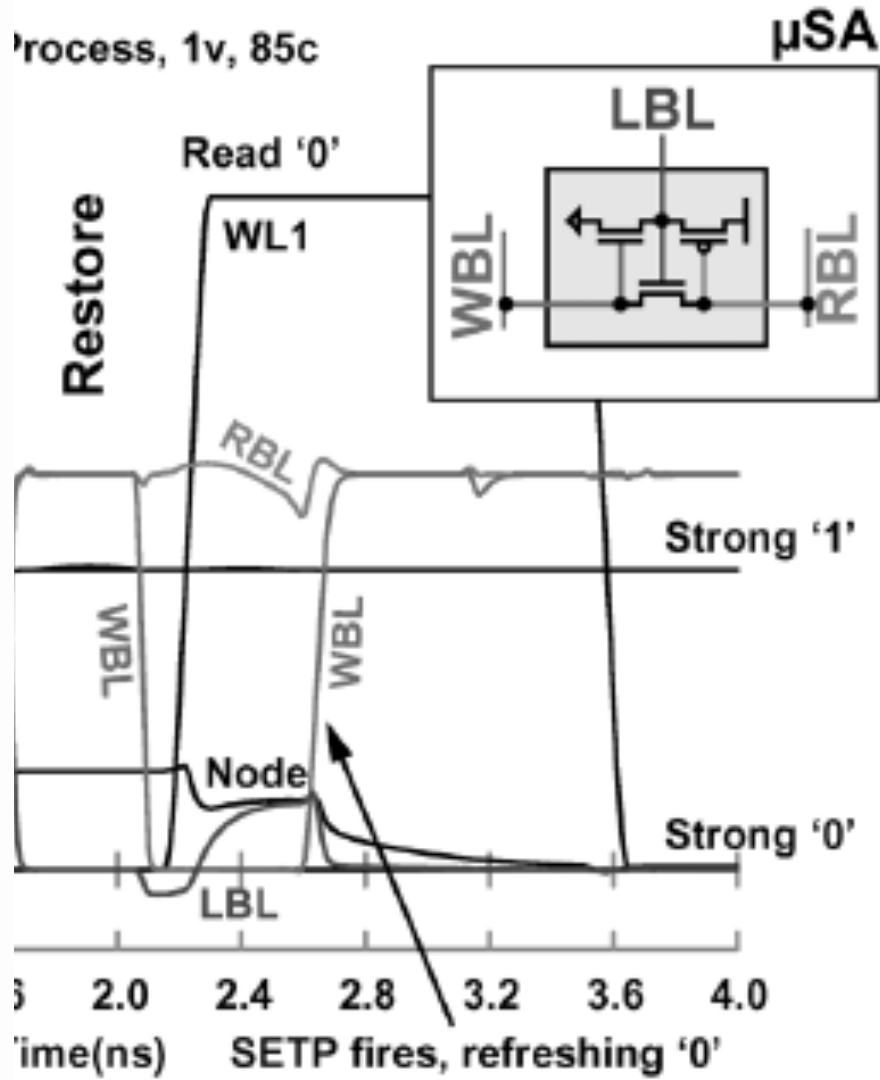


(b)


3 Transistors

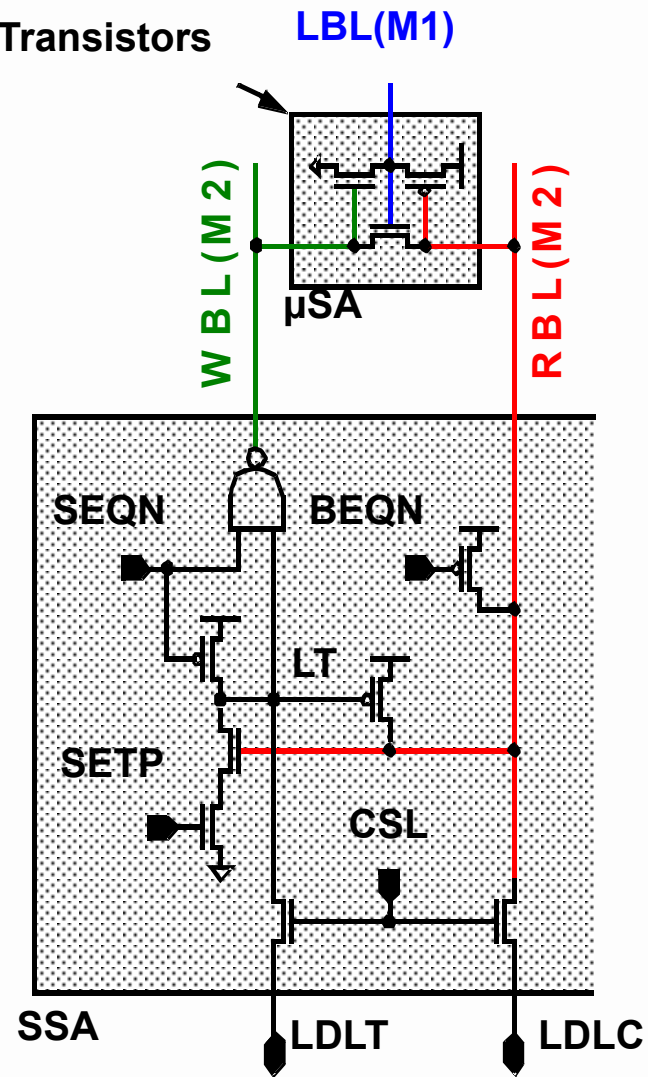


# Micro Sense Hierarchy - Three levels

 


# Data Sense Amp (DSA)

 


# Data Sense Amp (DSA) – Write

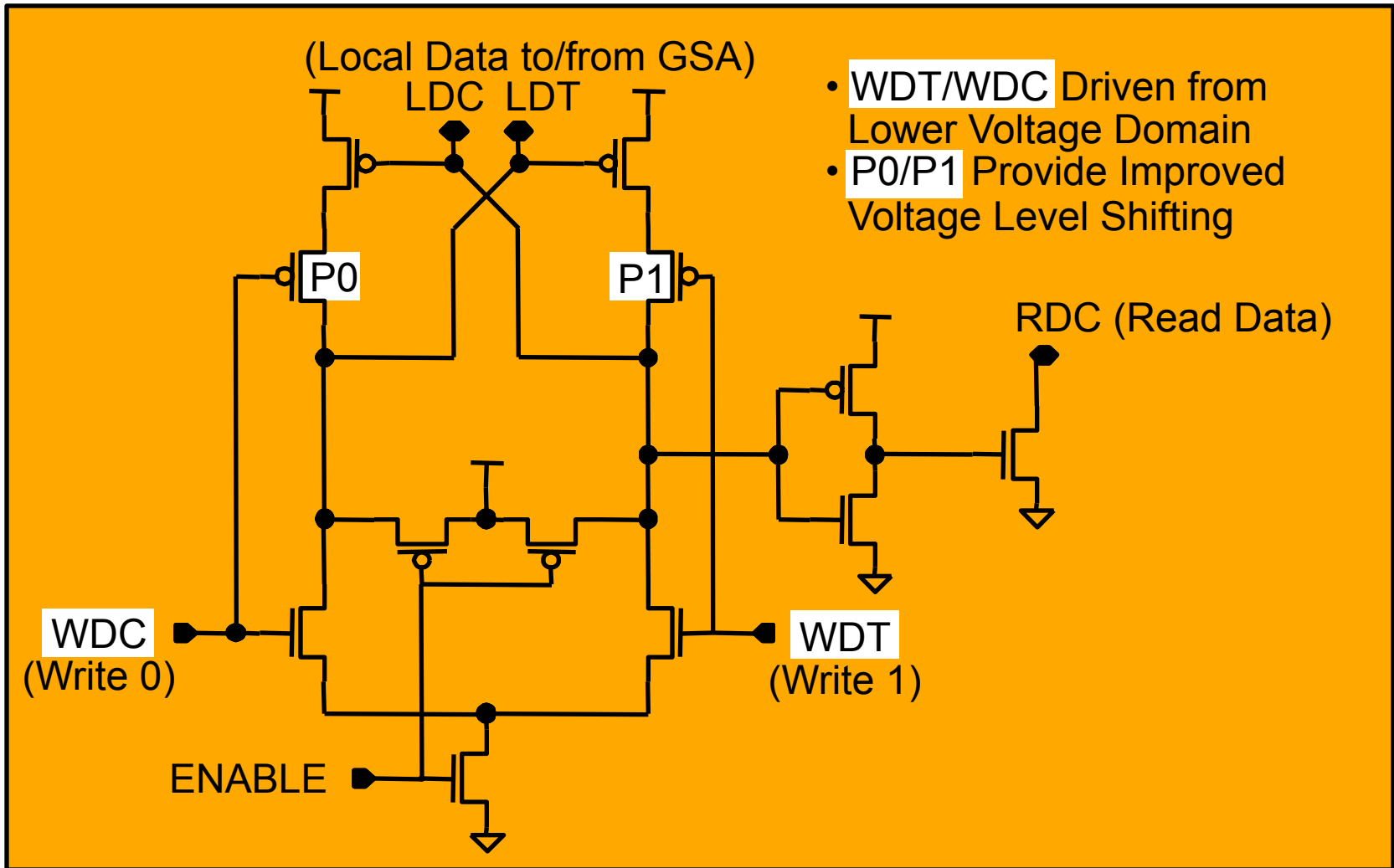

# Data Sense Amp (DSA) – Read

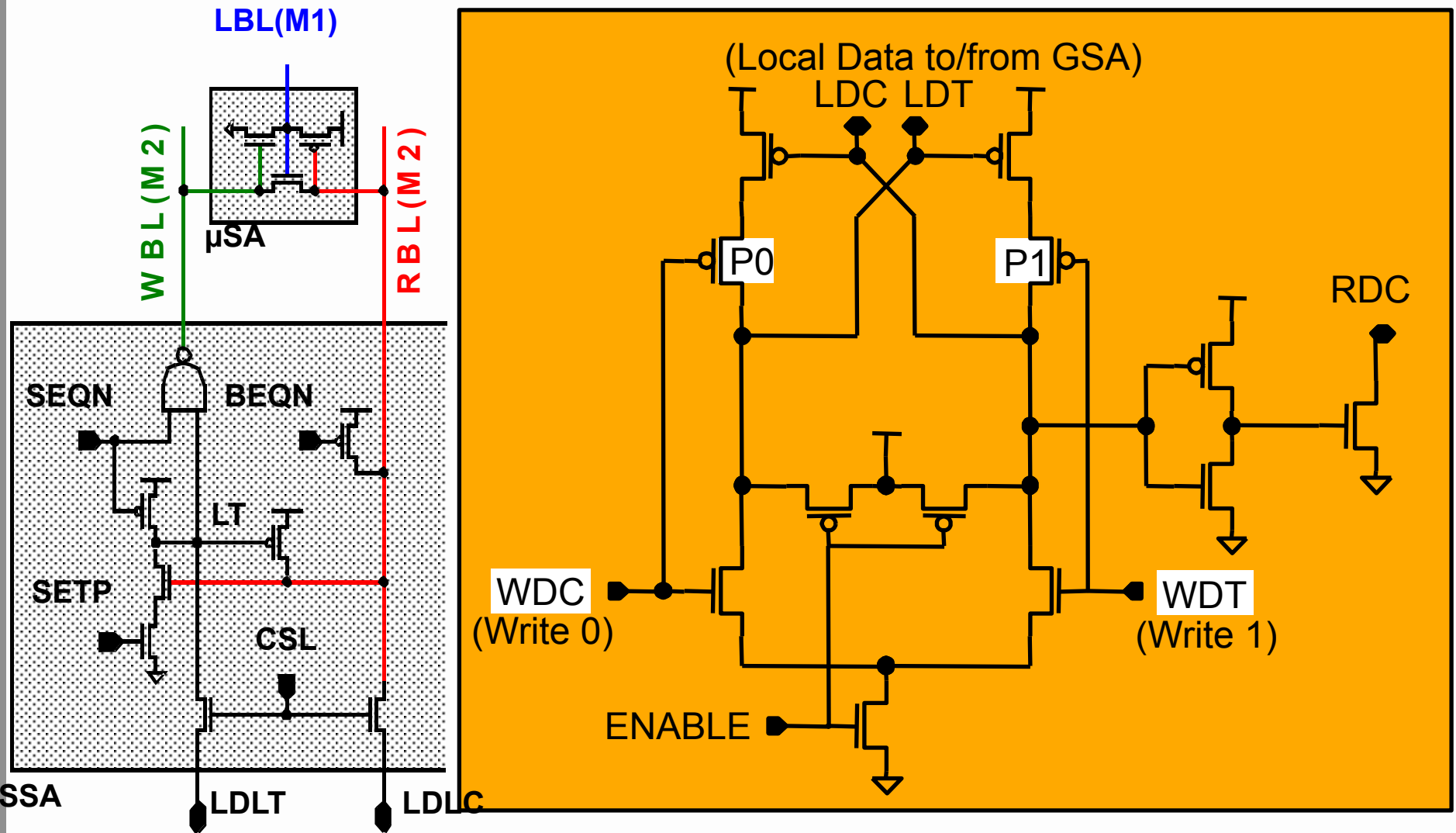

# Combining DSA's- Dynamic NOR Gate

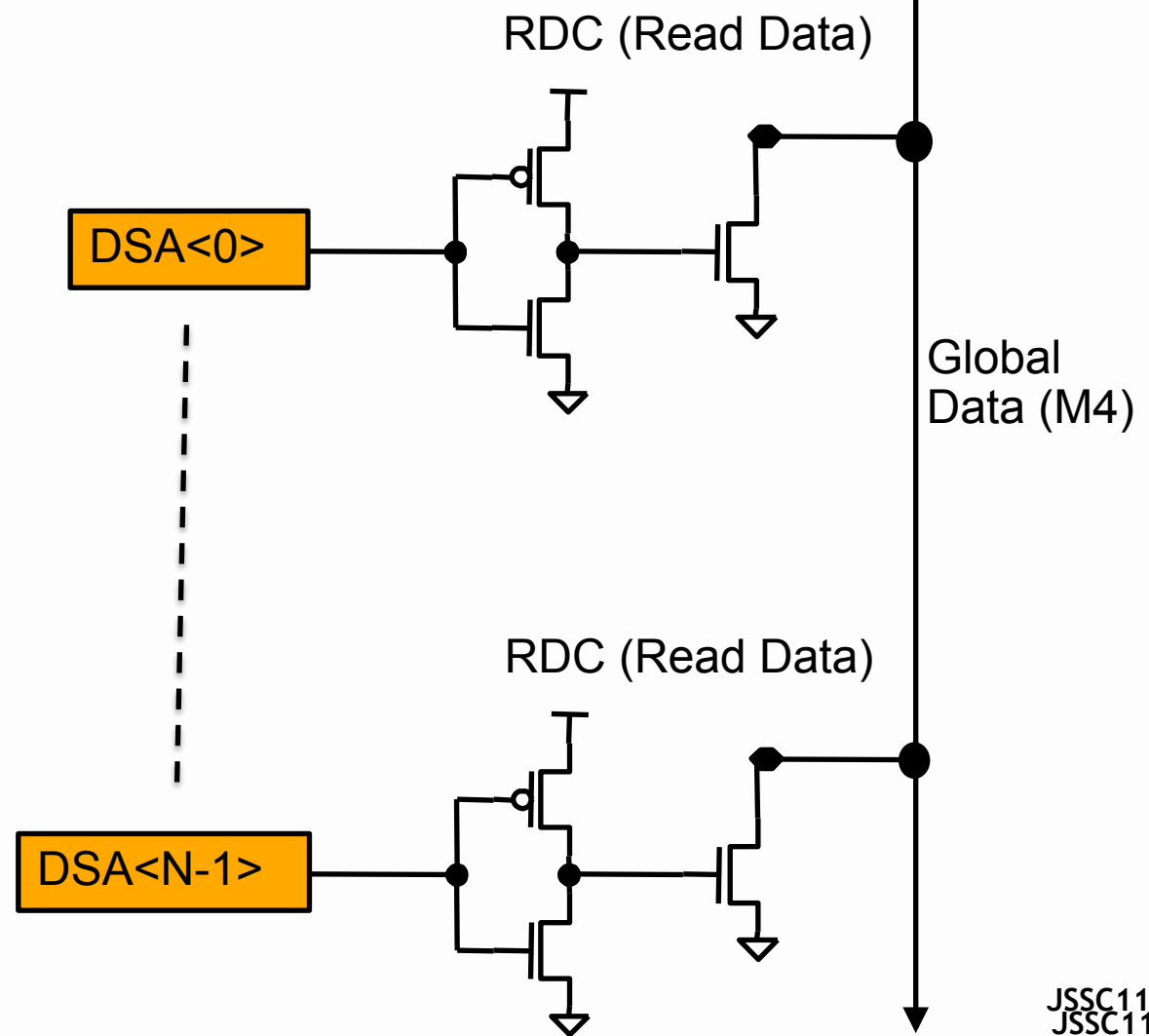




# Micro Sense Advantage

Fast Performance of Short Bit-Line

Area Overhead of 4x Longer Bit-Line

Bits/BL	256	128	32
Sense Amp	10%	20%	19%
Reference Cells	2.3%	4%	-
Twist Region	2%	2.6%	-
Second Sense Amp	-	-	8%
Total	14.3%	26.6%	27%



Same Overhead

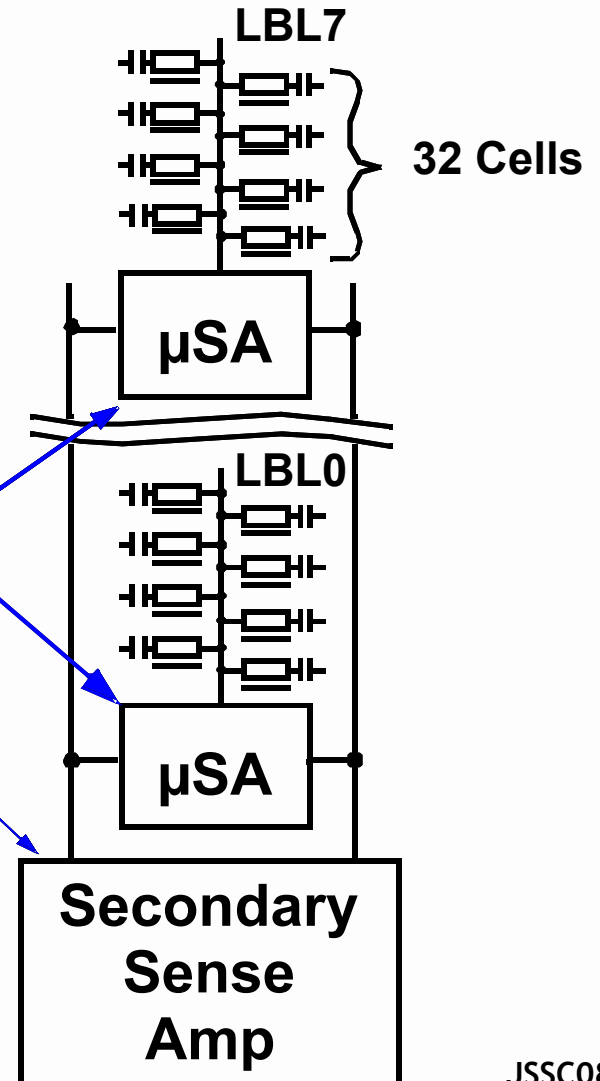


# Bit-Line area overhead

Bits/BL	256	128	32
Sense Amp	10%	20%	> 80%
Reference Cells	2.3%	4%	
Twist Region	2%	2.6%	

Unacceptable

 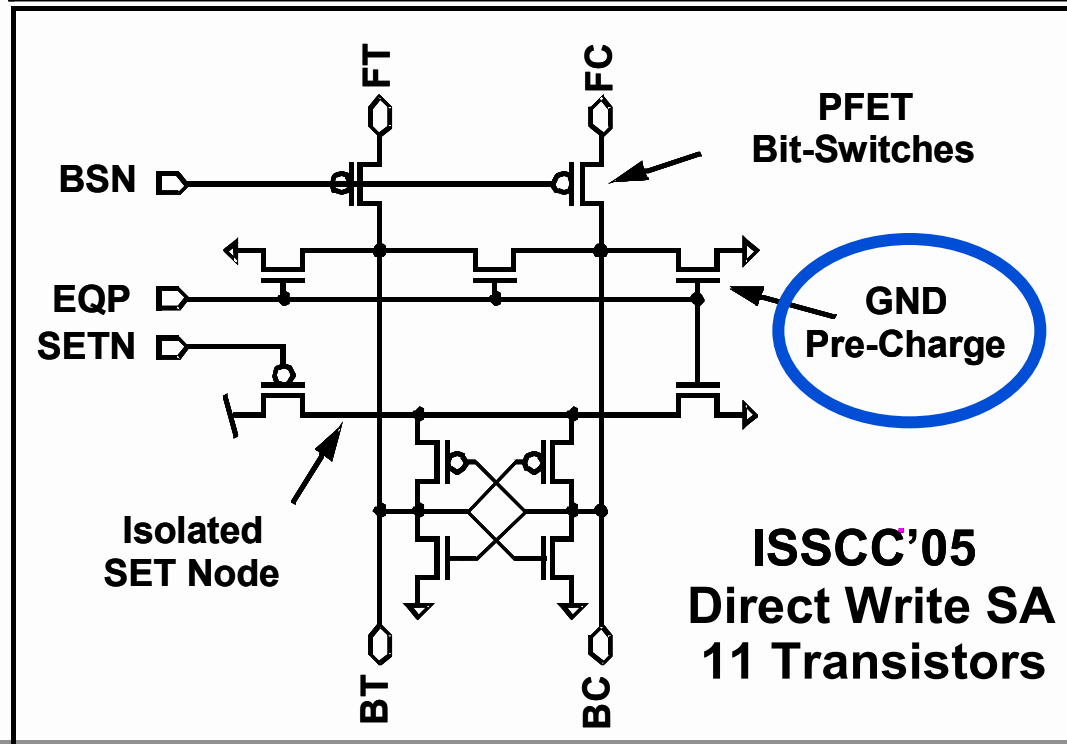

# Array utilization

 


$$\text{Utilization} = \frac{\text{Cell Area}}{\text{IO + Predecode + Redundancy}}$$

Mbits/mm<sup>2</sup>

# Access Shmoo


1.5ns Access @1V 85C

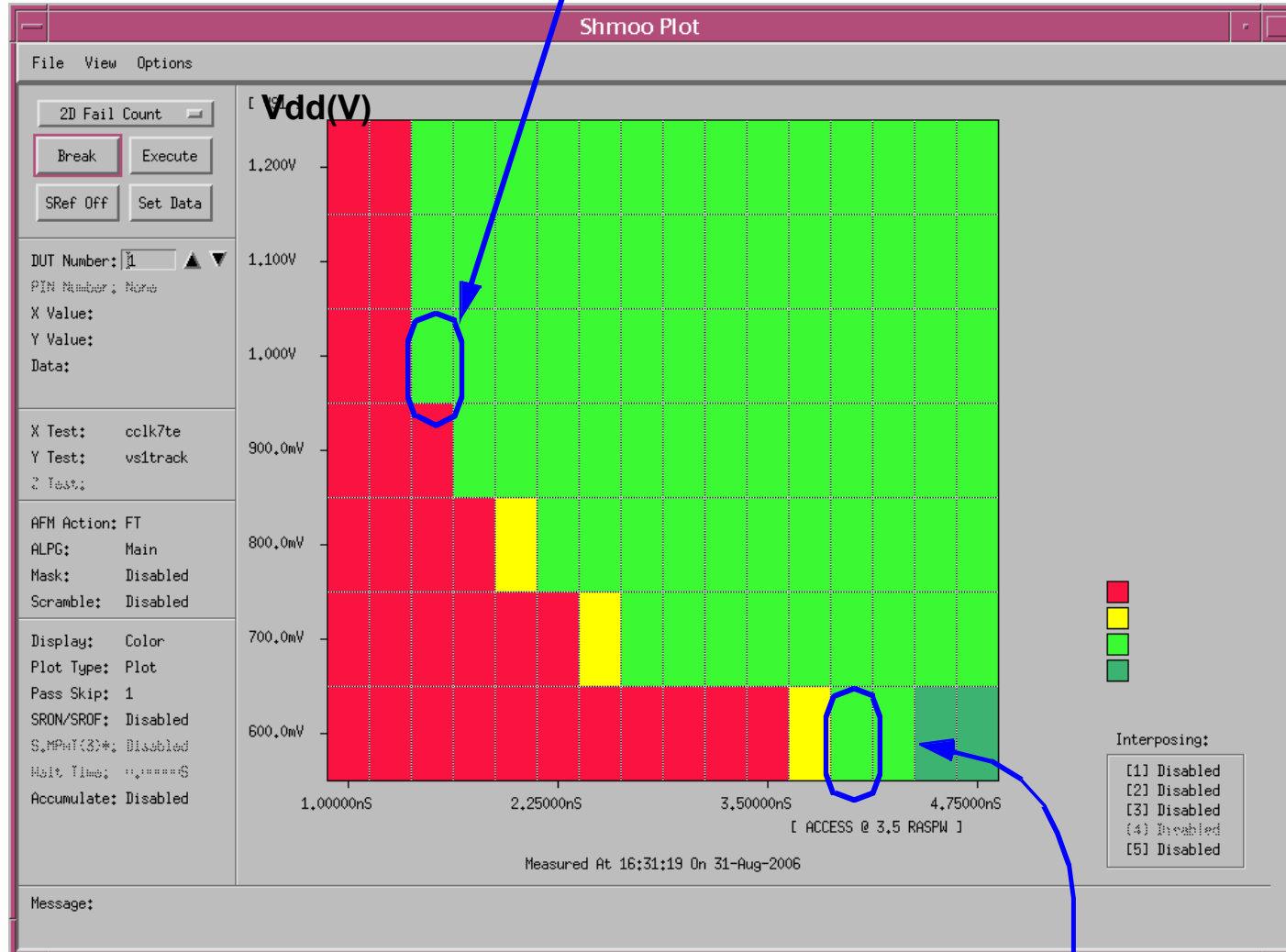


4ns Access @600mV

# Redundancy

Notebook

 

Page 111

 

Extra Page  
R05



eFuse based repair table


(see page R05)

<u>INDEX TO BOOK ONE</u>			
<u>PAGE No</u>	<u>EXPT. No.</u>	<u>AND</u>	<u>DATE</u>
109	30 APRIL 1999	-	EXP. 30
110	1-MAY 1999		EXP 30 CONTD
111	1-may 1999		EXP 31
112	1-may 1999		EXP 31 CONTD.


# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM Write Analysis
- ❑ eDRAM Sense-Amplifier Specification
- ❑ eDRAM operational details (case study)
- ❑ eDRAM Read Analysis
- ❑ Noise concerns
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM

# Read Time Calculation

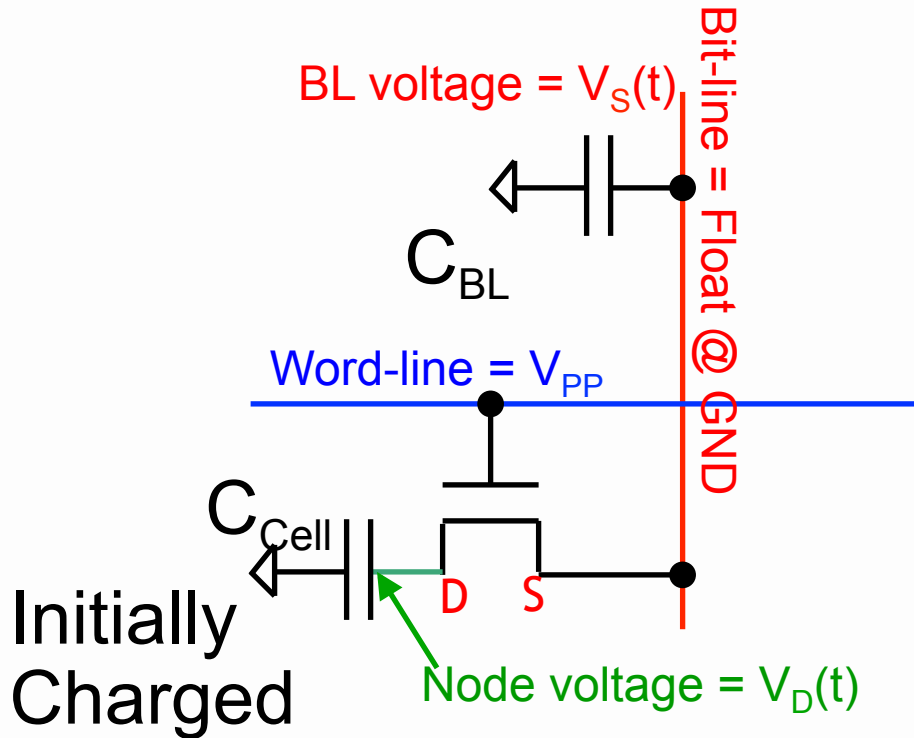

BL – Pre-discharged  
Read-1

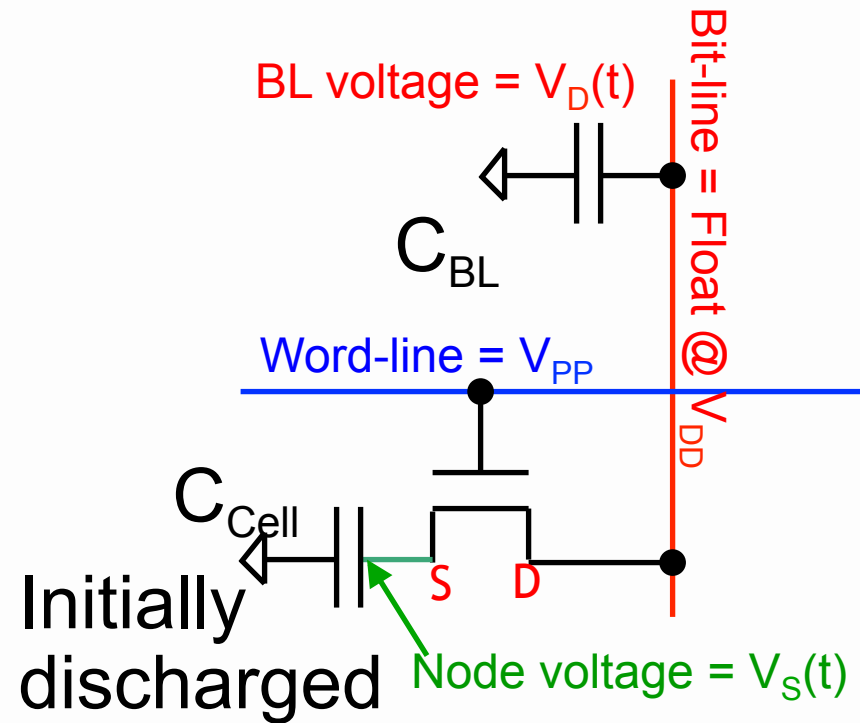

BL – Pre-charged  
Read-0

Read time : Let us define it as time required for BL to reach  $V_{DD}/2$

# Read Time





	BL pre-discharged	BL pre-charged
Source	BL	Node
Drain	Node	BL
Initial Charge	$C_{Cell} V_{DD}$	$C_{BL} V_{DD}$
Charge	$C_{Cell} V_D + C_{BL} V_S = C_{Cell} V_{DD}$	$C_{Cell} V_S + C_{BL} V_D = C_{BL} V_{DD}$
Charging Equation	$I_{DS} \left[ \frac{1}{C_{Cell}} + \frac{1}{C_{BL}} \right] = - \frac{dV_{DS}}{dt}$	
Current	$I_{DS} = \mu_n C_{OX} \frac{W}{L} V_{DS} (V_{PP} - V_{Tn} - V_S - V_{DS}/2)$	
$V_S$	$\alpha (V_{DD} - V_{DS})$	$(1 - \alpha) (V_{DD} - V_{DS})$
$\alpha$	$\frac{C_{Cell}}{C_{Cell} + C_{BL}}$	
$I_{DS}$	$K V_{DS} (\Delta_1 + (\alpha - 0.5) V_{DS})$	$K V_{DS} (\Delta_2 - (\alpha - 0.5) V_{DS})$
$K$	$\frac{C_{EFF}}{\mu_n C_{OX} (W/L)}; C_{EFF} = \frac{C_{Cell} C_{BL}}{C_{Cell} + C_{BL}}$	
$\Delta$	$\Delta_1 = V_{PP} - V_{Tn} - \alpha V_{DD}$	$\Delta_2 = V_{PP} - V_{Tn} - (1 - \alpha) V_{DD}$



	BL pre-discharged	BL pre-charged
Read Threshold	$V_S = V_{DD}/2$	$V_D = V_{DD}/2$
$V_{DS-TH} (V_{FINAL})$	$\frac{V_{DD}}{2} \left(1 - \frac{C_{BL}}{C_{Cell}}\right)$	
$T_{WRITE}$	$-K \int_{V_{DD}}^{V_{FINAL}} \frac{dV_{DS}}{V_{DS}(\Delta_1 + (\alpha - 0.5)V_{DS})}$	$-K \int_{V_{DD}}^{V_{FINAL}} \frac{dV_{DS}}{V_{DS}(\Delta_2 - (\alpha - 0.5)V_{DS})}$
$T_{WRITE}$	$\frac{K}{\Delta_1} \ln\left(\frac{V_{DD}(\Delta_1 + (\alpha - 0.5)V_{FINAL})}{V_{FINAL}(\Delta_1 + (\alpha - 0.5)V_{DD})}\right)$	$\frac{K}{\Delta_2} \ln\left(\frac{V_{DD}(\Delta_2 + (0.5 - \alpha)V_{FINAL})}{V_{FINAL}(\Delta_2 + (0.5 - \alpha)V_{DD})}\right)$

# Read Time



# Intuition

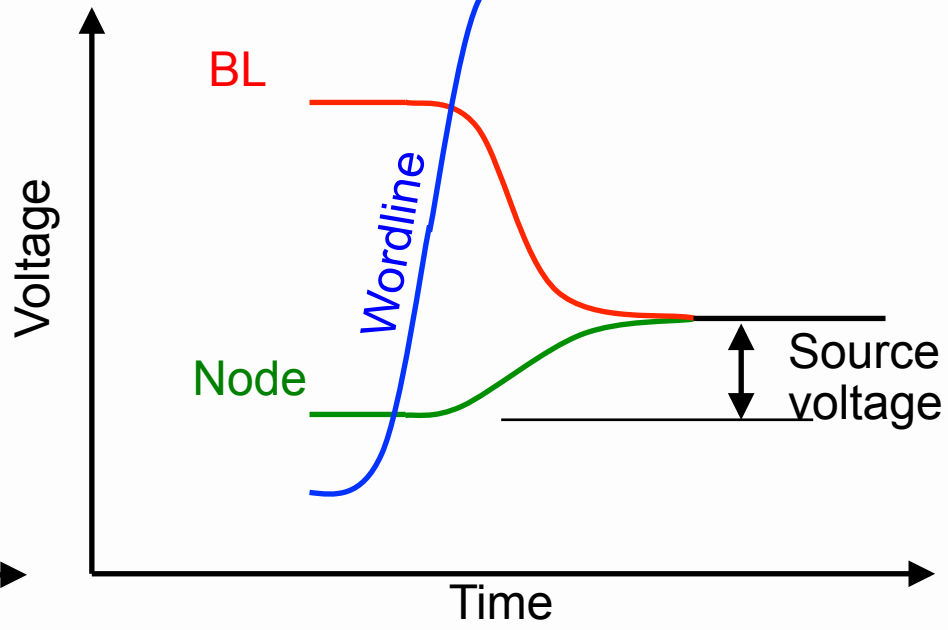 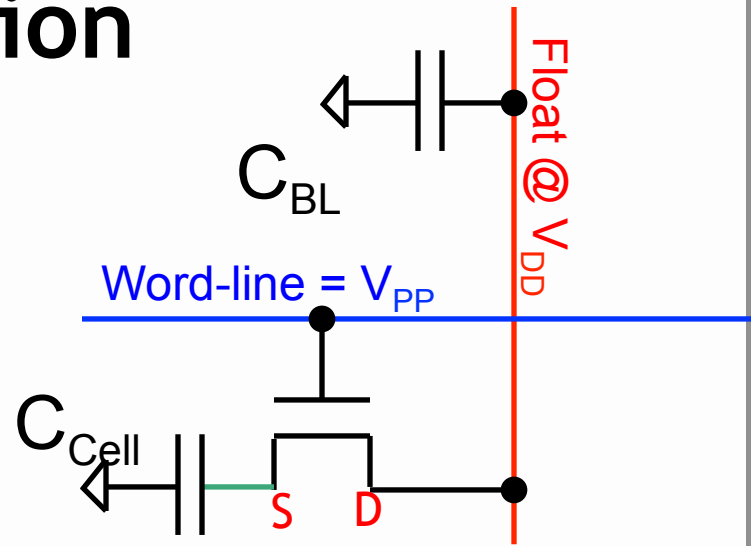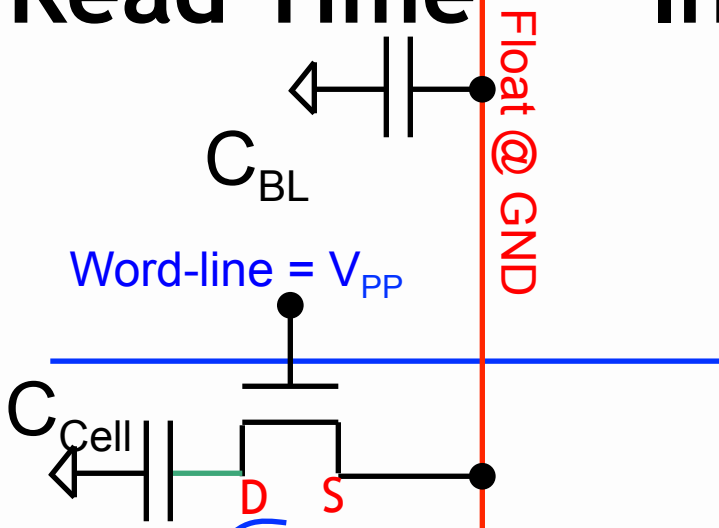

# Topics

- ❑ Introduction to memory
- ❑ DRAM basics and bitcell array
- ❑ eDRAM Write Analysis
- ❑ eDRAM Sense-Amplifier Specification
- ❑ eDRAM operational details (case study)
- ❑ eDRAM Read Analysis
- ❑ SOI Technology
- ❑ Wordline driver (WLDRV) and level translators (LT)
- ❑ Challenges in eDRAM

# Bulk vs SOI Technology

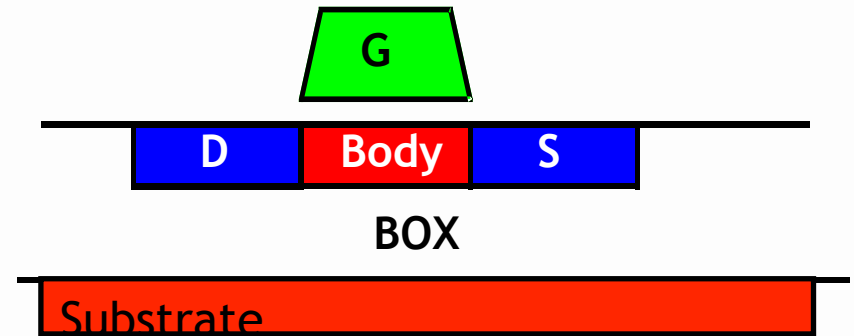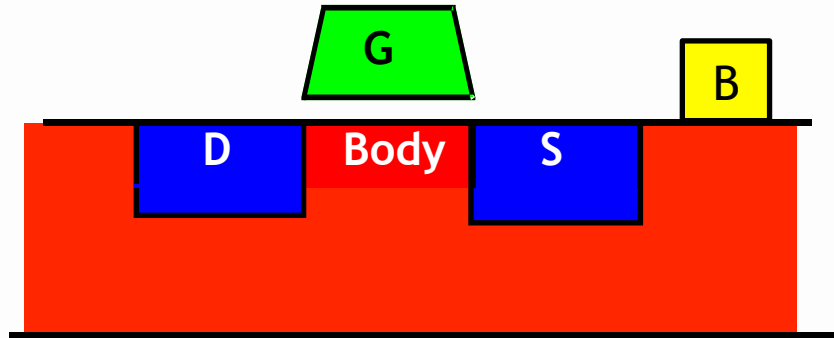

Body contact can be used to fix the body potential in bulk technology  
SOI Technology

- Floating body is a problem
- History effect
- SOI provides better sub-threshold slope
- Higher performance with lower leakage

# Floating Body Effects

Body potential modulated by coupling and leakage

Better source follower vs. bulk during write back (body coupling)

Improved write '1' cell voltage


Degraded  $I_{off}$  / Retention if body floats high (body leakage)

GND pre-charge keeps body low

Eliminate long periods with BL high (limit page mode)

$I_{Leak_{FWD}} > I_{Leak_{REV}}$

When BL = GND  
Body ~ GND

 

# Floating Body Effects

Body potential modulated by coupling and leakage


Better source follower vs. bulk during write back (body coupling)

Improved write '1' cell voltage

Degraded  $I_{off}$  / Retention if body floats high (body leakage)


GND pre-charge keeps body low

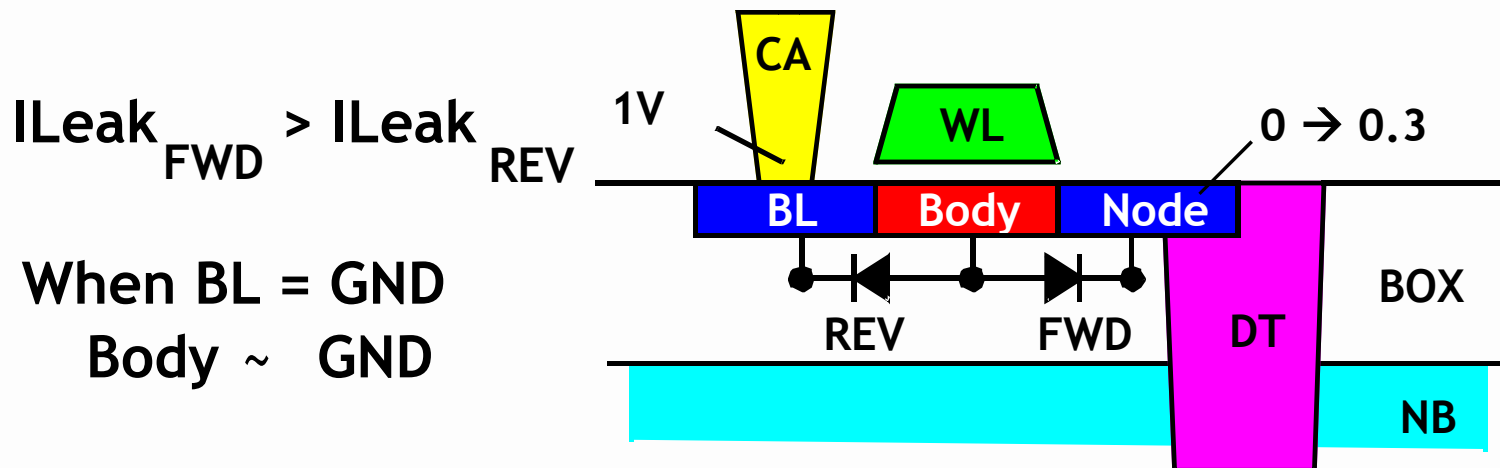Eliminate long periods with BL high (limit page mode)



# Array Body Charging

## Commodity DRAM (long page mode)

 

## embedded DRAM (limited page mode)

