

Spring 2005; E4332: VLSI Design Laboratory; HW1

Nagendra Krishnapura (nkrishna@vitesse.com)

due on 1 Feb. 2005

 


Figure 1:

1. Design a CMOS inverter with minimum length p- and n-channel devices with equal widths.
 - (a) Simulate the DC characteristics with a 5 V supply. What V_{IH} , V_{IL} , assuming that the output low and high voltages away from their ideal values by 10% of the supply voltage.
 - (b) Design a 7 stage ring oscillator using the inverters designed above. What is the oscillation frequency? Repeat the simulations with supply voltages from 2.5 V to 4.5 V in increments of 0.5 V and determine the oscillation frequency in each case.
2. Design an inverter with p- and n-channel MOS device widths such that the transition in the inverter's characteristics is in the middle of the 5 V supply rail. Repeat the DC and transient simulations specified in the previous problem with this inverter.
3. Determine "textbook" I_D vs. V_{DS} ($0 \leq V_{DS} \leq 5$ V) curves (Fig. 2(a)) for V_{GS} from 1 V to 5 V in increments of 0.5 V. Do this for transistors of lengths $0.5 \mu\text{m}$, $1 \mu\text{m}$, and $2 \mu\text{m}$ (three sets of curves for p- and n- channel transistors). Use $W/L = 10$ in each case. In each of the curves, determine the slope in the saturation region, and the corresponding output resistance of the transistor.
4. Determine "textbook" I_D vs. V_{GS} ($0 \leq V_{GS} \leq 5$ V) curves (Fig. 2(b)) with $V_{DS} = 3$ V. Do this for transistors of lengths $0.5 \mu\text{m}$, $1 \mu\text{m}$, and $2 \mu\text{m}$ (three sets of curves each for p- and n- channel transistors). Use $W/L = 10$ in each case. From the curves, determine the current factors $K_{n,p}$ and the threshold voltages V_{THN} , V_{THP} .

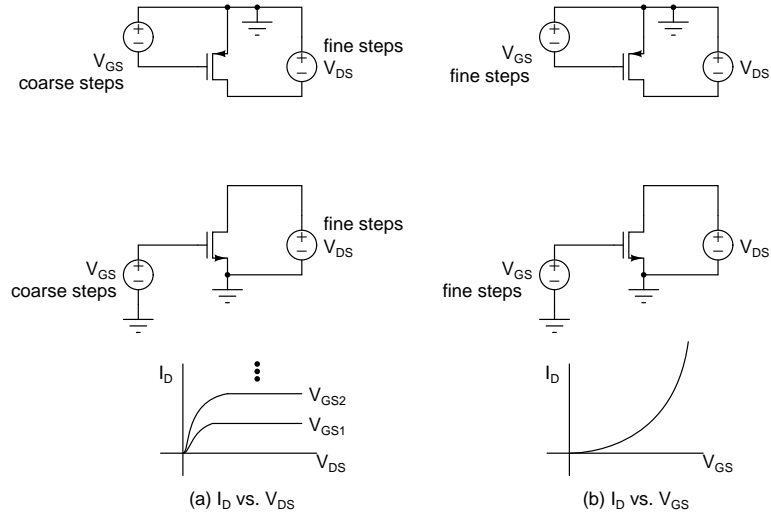


Figure 2:

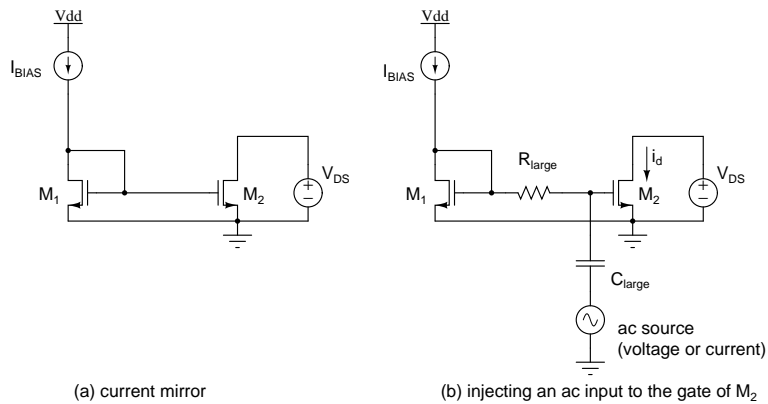


Figure 3:

5. For the circuit in Fig. 3, carry out a parametric simulation as I_{in} from $1 \mu A$ to $100 \mu A$ in 7 logarithmically spaced steps. Plot a) the DC value of V_{GS} , b) the inherent dc gain of the transistor g_m/g_{ds} , and c) the unity gain frequency of the transistor gain. For c), you need to do a parametric ac analysis. Do this for n- and p-channel transistors of $0.5 \mu m$ and $2 \mu m$ channel lengths. Use $W/L = 10$ in each case.