### E4332: VLSI Design Laboratory

Nagendra Krishnapura Columbia University Spring 2005: Lectures nkrishna@vitesse.com

# AM radio receiver

- AM radio signals: Audio signals on a carrier
- Intercept the signal
- Amplify the signal
- Demodulate the signal-recover the audio
- Amplify the audio to drive a speaker

# AM signal basics: time domain



• Envelope(peak) of the carrier is the message

# AM signal basics: frequency domain



Sidebands around the carrier

# AM signals



Sidebands around the carrier

# **Broadcast AM signals**



 Broadcast AM channels 10kHz from each other

#### Receiver bandwidth



Receiver bandwidth must be constant

### Receiver bandwidth

- $f_c/f_{bw}$ =53 at the lowest end
- $f_c/f_{bw}$ =161 at the highest end
- High Q (~ quality factor)
- Maintain constant bandwidth

# Receiver sensitivity and selectivity

- Sensitivity: ability to detect small signals
  - AM radio sensitivity: ~50uV signals with 30% modulation
- Selectivity: ability to reject adjacent signals
  - Dictated by the choice of architecture in our case

# Tuned Radio Frequency(TRF) receiver



- Input tuned circuit is the only filter providing selectivity
- Coil on a ferrite rod

### TRF receiver: input tuning



# 2<sup>nd</sup> order filter basics

• Resonant frequency(radians per second)  $\omega_{o}$ 

 $= 1/sqrt(LC_{tune})$ 

- 3dB bandwidth  $\omega_{h}$
- Quality factor  $Q = \omega_0 / \omega_b$
- Series loss:  $Q_s = 1/R_s sqrt(L/C)$ 
  - Bandwidth =  $R_s/L$
- Parallel loss:  $Q_{D} = R_{D} sqrt(C/L)$ 
  - Bandwidth  $= 1/CR_{p}$

# TRF receiver: input tuning

- Resonant frequency(1/sqrt(LC<sub>tune</sub>)) varies
  from 530 to 1610kHz, approx 3x
- Fixed L,  $\Rightarrow C_{tune}$  varies by 9x
- Series  $loss(R_s)$  only
  - Bandwidth =  $R_s/L$
  - No change with C<sub>tune</sub>
- Parallel loss(R<sub>D</sub>) only
  - Bandwidth =  $1/C_{tune}R_{s}$
  - varies by 9x with change in  $C_{tun}$

# TRF receiver: input tuning

- Some bandwidth variation with tuning
  - Bandwidth < 10kHz at low end</li>
  - Bandwidth > 10kHz at high end
- 2<sup>nd</sup> order filter. Limited out of band attenuation
- ⇒ Poor selectivity in a TRF receiver
- Suggestion: Use a very large on chip R<sub>p</sub> to maintain as high a Q as possible

# TRF receiver: Input amplifier



- High impedance input necessary
  - Source follower buffer
  - Differential amplifier

### TRF receiver: Input amplifier



#### Use large resistors for input biasing



#### **TRF receiver: Detector**



- No diodes in CMOS process
- Input amplitude > diode drop
- Use of an amplifier in feedback to improve sensitivity

# AM radio: specifications

Signal levels:

- Input from  $50\mu V$  to 5mV
- RF amplifier with AGC
- Output of RF amplifier with AGC from 50mV to 200mV
  - Max. gain =  $50 \text{mV}/50 \mu \text{V} = 1000$  (60dB)
  - Min. gain = 200 mV/5 mV = 40 (32 dB)
  - Total gain variability = 1:25 (28dB)
- Detector must work with 50mV-200mV inputs
- Audio output max. ~  $1V_{pk}$  into  $8\Omega$  speaker

# AM radio: specifications

<u>Misc.:</u>

- Supply voltage: 4.2-4.5V
  - Operation with 3x 1.5V batteries
  - Try to design for 4.2V

# AM radio: input signal generation



- Use A from  $50\mu V$  to 5mV
- Parameterized subcircuit(using pPar("m"), pPar("A") etc.) to make an AM source in Cadence

#### **Amplifier basics**



### **Amplifier basics**

- Gain =  $g_m(R_L + 1/g_{ds}) \sim g_m R_L$
- Gm = sqrt( $\mu C_{ox}/2^*W/L^*I_0$ ) =  $I_0/V_{GS}-V_T$
- Gain =  $g_m R_L = I_0 R_L / V_{GS} V_T$ 
  - To change gain,  $I_0^{R_L}$  (the dc voltage drop across  $R_L$ ) or  $V_{gs}^{-}-V_{\tau}$  (related to transistor current density) has to be changed
- Linearity improves with increasing  $V_{GS}$ - $V_{T}$ 
  - Amplifier: larger  $V_{gs}$ - $V_{T}$
  - Switch: smaller  $V_{gs}$ - $V_{T}$

# **RF** amplifier I



# **RF** amplifier I

- AC coupled to remove offsets
- Single ended input/output-simple
- Gain =  $g_m R_L/2$ (Analyze this!)
- Ac coupling resistors: pMOS transistors
- Ac coupling corner frequency: ~ 1dB attenuation at lower end of AM band
- Capacitor values: 5pF or less
   Linear capacitor density ~ 0.9fF/μm<sup>2</sup>
- Resistor values: upto  $10k\Omega$ 
  - Resistivity ~  $800\Omega/sq$ .

# **RF** amplifier II



# RF amplifier II

- AC coupled to remove offsets
- Single ended input/output-simple
- Gain =  $g_m R_L$  (Analyze this!)
- Ac coupling resistors: pMOS transistors
- Ac coupling corner frequency: ~ 1dB attenuation at lower end of AM band
- Capacitor values: 5pF or less
   Linear capacitor density ~ 0.9fF/µm<sup>2</sup>
- Resistor values: upto  $10k\Omega$ 
  - Resistivity ~  $800\Omega/sq$ .

# **RF** amplifier III



# RF amplifier III

- AC coupled to remove offsets
- Differential stages
  - 2x ac coupling capacitors
- Gain =  $g_m R_L$ (Analyze this!)
- Ac coupling resistors: pMOS transistors
- Ac coupling corner frequency: ~ 1dB attenuation at lower end of AM band
- Capacitor values: 5pF or less
  - Linear capacitor density ~ 0.9fF/ $\mu$ m<sup>2</sup>
- Resistor values: upto  $10k\Omega$

- Resistivity ~  $800\Omega/sq$ .



### Detector I

- Implement  $v_i(t)$ \*sgn( $v_i(t)$ ) and filter the result
  - Full wave rectification and filtering
- Filtering capacitor C
  - retain audio, remove RF
  - External, if too large
- Upper pair should act as a switch: sgn(v<sub>i</sub>(t))
- Lower pair should act as a linear amplifier (over the entire range of input signals)

### **Detector II**



# Detector II

- Full wave rectifier with differential inputs
- Half wave rectifier with single ended inputs
- Followed by amplifier and filter
- Filtering capacitor C
  - retain audio, remove RF
  - External, if too large

#### Peak detector









### **Detector III**



### Detector III



• Single stage "op amp"

# Detector III

- Peak detector
- Discharge time constant slower than charging time constant
  - Negligible discharge between RF cycles
  - Full discharge between audio cycles



- Feedback for linearity
- Output current ~  $1V/8\Omega = 125$ mA

# Class A opamp



• Need to bias with I0 = 125 mA!



V<sub>b1</sub> and V<sub>b2</sub> adjusted so that output branch
 Current is I<sub>0</sub>
 Nagendra Krishnapura: VLSI Design Laboratory, Spring 2005



 Output pMOS gate pulled down to drive out a large current ( > bias)



 Output nMOS gate pulled up to pull in a large current (> bias)

# Class AB opamp: bias generation



# Class AB opamp: full schematic



### **Bias current generation**



common bias line; potential coupling between stages

 One external resistor to fix bias currents
 Bias line coupling can lead to problems in high gain multistage circuits

#### **Bias current generation**



- Separate mirroring branch for each stage
  + Reduced interstage coupling
- Increased current in bias branches

#### **Bias current generation**



RC filter to each biasing MOS transistor
 + Reduced interference and noise
 + No increase in bias currents

#### **Passive components**



### Passive components: Resistors

- Passive resistor
  - Min. width=; few kOhms
- MOS resistors
  - Need bias
  - Greater range of values
  - Voltage tunability

### Passive components: capacitors

- Passive (poly1-poly2)
  - Few pF
  - Bottom plate to ground parasitic
- MOS capacitors
  - Higher capacitor density
  - Need to be biased in strong inversion