

①

Fall 2004

EE316: Analog systems in VLSI: Midterm solutions

Nagendra Krishapura

1. Residue ( $= V_{LSB} = \frac{V_{ref}}{2^4}$ ) should be amplified to the range ( $= V_{ref}$ ) of the second A/D converter.

$$G = 2^4 = 16$$

$$(a) \cdot |\Delta V_{amp}| \leq V_{LSB}/2 \cdot G = \frac{V_{ref}}{2^5} = 31.25 \text{ mV}$$

( $V_{LSB}$ : LSB of the overall converter)

$$(b) \cdot |\Delta V_{amp}| = |V_{in,amp,max}| \cdot \Delta G_{max} \leq \frac{V_{LSB}}{2} \cdot G \quad [\text{from (a)}]$$

$$= \frac{V_{ref}}{2^4} \cdot \Delta G_{max} \leq \frac{V_{ref}}{2^9} \cdot G$$

$$\therefore \Delta G_{max} = \frac{1}{2}$$

Amplifier gain with an opamp whose gain is  $A_0$

$$\text{is: } G' = \frac{G_0}{1 + \frac{G_0 + 1}{A_0}}$$

$$\Delta G = G' - G_0 = - \frac{G_0 (G_0 + 1) / A_0}{1 + G_0 + 1/A_0}$$

$$\therefore A_0 \geq 2G_0 (G_0 + 1) - (G_0 + 1) = 527 \quad (= 54.4 \text{ dB})$$

c) 
$$\Delta V_{amp} = V_{os} \cdot (1+G) \leq \frac{V_{LSB}}{2} \cdot G \quad (\text{from (a)})$$

$$V_{os} \leq \frac{V_{LSB}}{2} \cdot \frac{G}{1+G} = \frac{V_{ref}}{2^9} \cdot \frac{G}{1+G} = \underline{1.84 \text{ mV}}$$

d) Transfer function of the amplifier

$$= \frac{G_0}{1 + \frac{s}{\omega_n}(G_0+1)}$$

Ideal ~~input~~ <sup>output</sup> =  $V_{in,amp} \cdot G_0$

Actual =  $V_{in,amp} \cdot G_0 \left( 1 - e^{-\frac{\omega_n \cdot t}{G_0+1}} \right)$

$$|\text{Error}| = V_{in,amp} \cdot G_0 \cdot e^{-\frac{\omega_n \cdot t}{G_0+1}} \leq \frac{V_{ref}}{2^5} \quad (\text{From (a)})$$

$$V_{in,amp, max} = V_{LSB1} = \frac{V_{ref}}{2^4}$$

$$\therefore e^{-\frac{\omega_n t}{G_0+1}} \leq \frac{1}{2^5}, \quad t = \frac{T_s}{2} = 2.5 \text{ ns}$$

$$\therefore \omega_n \geq \frac{G_0+1}{(T_s/2)} \cdot 5 \ln(2) = 23.6 \text{ Grad/s}$$

Unity gain frequency of the opamp = 3.75 GHz!

2. Accuracy of the D/A used in the 2 step converter is 8 bits. i.e error in the op voltage can be at most  $\frac{V_{ref}}{2^9} \cdot \left(\frac{V_{LSB}}{2}\right)$

$$\text{Ideal output: } V_{o, ideal} = -V_{ref} \left[ \frac{b_3}{2R} + \frac{b_2}{4R} + \frac{b_1}{8R} + \frac{b_0}{16R} \right] \cdot R$$

Actual output:

$$V_{o, actual} = -V_{ref} \left[ \frac{b_3}{2R(1+\alpha_3)} + \frac{b_2}{4R(1+\alpha_2)} + \frac{b_1}{8R(1+\alpha_1)} + \frac{b_0}{16R(1+\alpha_0)} \right] \cdot R$$

$$|\text{Error}| \approx V_{ref} \left[ \frac{b_3}{2} \cdot \alpha_3 + \frac{b_2}{4} \cdot \alpha_2 + \frac{b_1}{8} \cdot \alpha_1 + \frac{b_0}{16} \cdot \alpha_0 \right]$$

Note that, in a D/A converter used in a 2 step converter, the absolute error matters. i.e

$V_o$  is of importance. In a stand alone

D/A Converter, this merely influences the gain

Assume  $\alpha_3 = \alpha_2 = \alpha_1 = \alpha_0$ .

$$\text{Worst error case} = V_{ref} \cdot \frac{15}{16} \cdot \alpha \leq \frac{V_{LSB}}{2} = \frac{V_{ref}}{2^9}$$

$$(b_3 b_2 b_1 b_0 = 1111)$$

$$\therefore \alpha \leq \frac{1}{15 \cdot 2^5} = \approx 0.21\%$$

Worst case error due to offset at  $b_3 b_2 b_1 b_0 = 1111$

$$\Delta V_{\text{out}} = V_{\text{os}} \cdot \left(1 + \frac{15}{16}\right) \leq \frac{V_{\text{ref}}}{2^9}$$

$$\therefore V_{\text{os}} \leq \frac{V_{\text{ref}}}{2^5 \cdot 31} = 1 \text{ mV}$$

$$(3) (a) \quad V_{\text{LSB}} = \frac{V_{\text{ref}}}{2^6} = 15.6 \text{ mV}$$

Minimum input to preamplifiers =  $\frac{V_{\text{LSB}}}{2}$ , which must be amplified to 50mV

$$\therefore \text{Gain} = 6.4$$

(b) For an input @  $f_s/2$ , error due to jitter

$$\Delta V = 2\pi \cdot V_{\text{in,peak}} \cdot \frac{f_s}{2} \cdot \Delta t_{\text{jitter}} \leq \frac{V_{\text{LSB}}}{2}$$


$$V_{\text{in,peak,max}} = \frac{V_{\text{ref}}}{2}$$

$$\Delta t_{\text{jitter}} = \frac{V_{\text{ref}}/2^7}{2\pi \cdot \frac{V_{\text{ref}}}{2} \cdot \frac{f_s}{2}} = \frac{1}{f_s} \cdot \frac{1}{\pi \cdot 2^6}$$
$$= \underline{2.5 \text{ ps}}$$

(c) The logic looks for a '011' pattern in the output of the comparators to eliminate single bubbles in the ~~say~~ thermometer code.

	Ideal differential input to preamplifiers	Ideal Comparator o/p	Non ideal Comparator o/p
m+3	$-5 \cdot V_{LSB}/2$	0	0
m+2	$-3 \cdot V_{LSB}/2$	0	0
m+1	$-V_{LSB}/2$ (A)	0	1
m	$+V_{LSB}/2$	1	1
m-1	$+3 \cdot V_{LSB}/2$ (B)	1	0
m-2	$+5 \cdot V_{LSB}/2$	1	1
m-3	$+7 \cdot V_{LSB}/2$	1	1

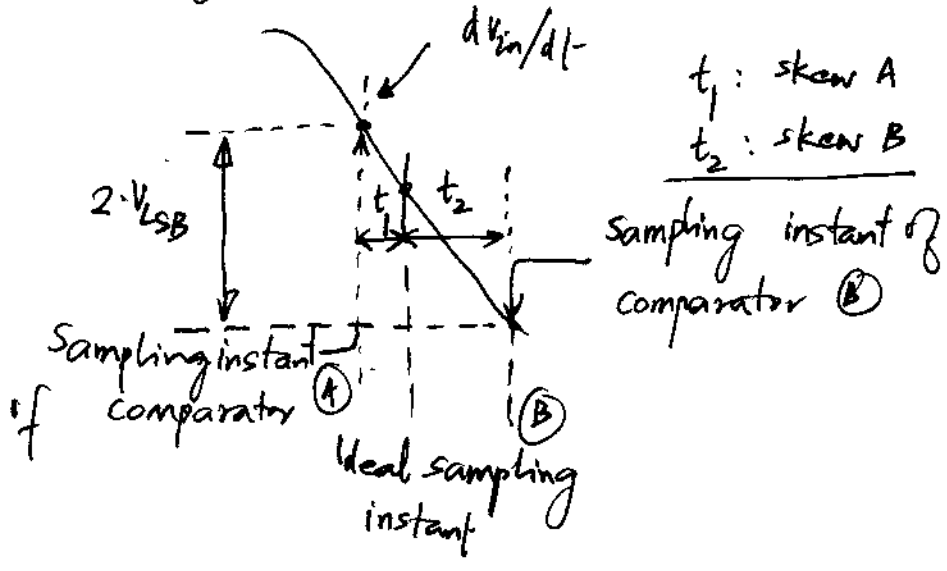If the skews are such that comparator (A) sees an input  $V_{LSB}/2$  more than what it should be and (B) sees an input  $\frac{3V_{LSB}}{2}$  less than what it should be, a ... 011 011 ... pattern is seen at the o/p of the comparators, i.e. an uncorrectable bubble.



A net skew  $t_1 + t_2 = \frac{2V_{LSB}}{dv_{in}/dt}$  results in

an uncorrectable bubble.

$$\left. \frac{dv_{in}}{dt} \right|_{max} = 2\pi \cdot \frac{f_s}{2} \cdot \frac{V_{ref}}{2}$$

$\therefore$  A skew of  $\frac{1}{f_s} \cdot \frac{1}{\pi \cdot 2^4} = 10ps$  can

result in a bubble.

[Maximum slope above holds if the skew is in the comparators near the middle of the ladder have a skew].

(d) Input to the 3 comparators in the 2 circuits in Fig. 3(b)

No Interpolation	with 2x Interpolation
top: $(V_{in} - (m+1)V_{LSB}) G$	top: $(V_{in} - (m+1)V_{LSB}) G$
mid: $(V_{in} - m \cdot V_{LSB}) G$	mid: $\left\{ (V_{in} - (m+1)V_{LSB}) G + (V_{in} - (m-1)V_{LSB}) G \right\} \frac{1}{2}$
bot: $(V_{in} - (m-1)V_{LSB}) G$	$= (V_{in} - m \cdot V_{LSB}) G$
	bot: $(V_{in} - (m-1)V_{LSB}) G$

The required gains are identical.  $G = 6.4$