
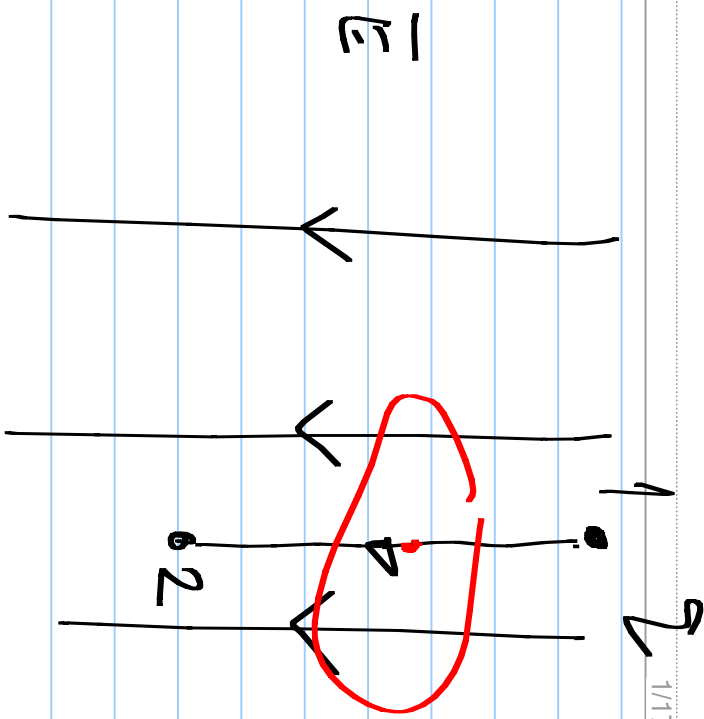


Lecture #2

Note Title

1/17/2013

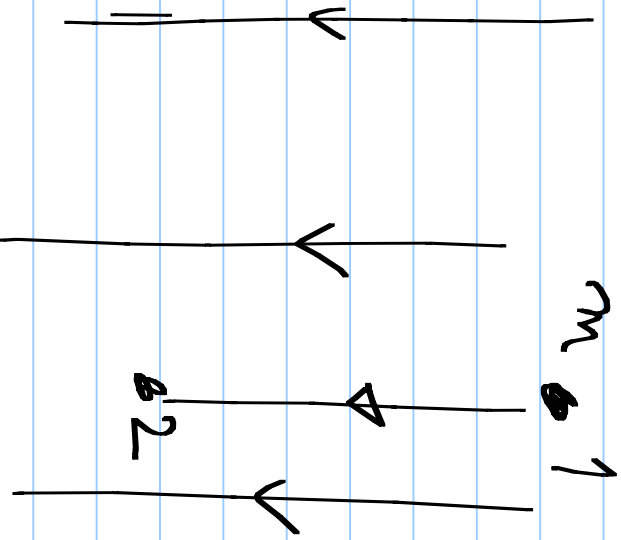

EARTH


$$\rho_m g (h_1 - h_2)$$

$$\rho g (V_1 - V_2)$$

Potential diff. / Voltage

Current: Rate of flow of charge across a


Surface

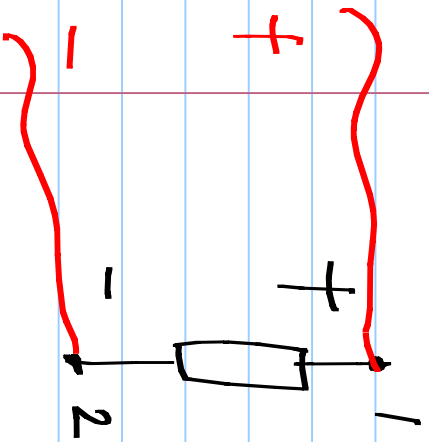




elements:

- At least two terminals

Elements:

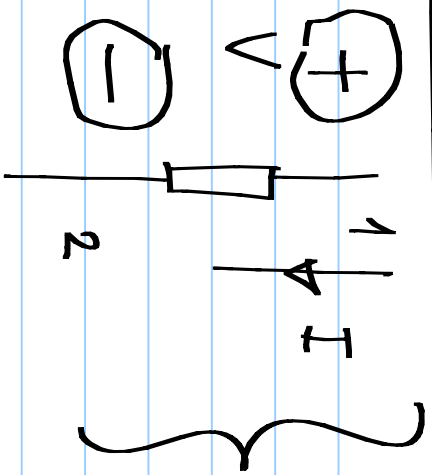

Defining the element characteristics

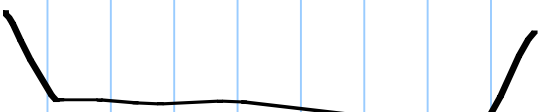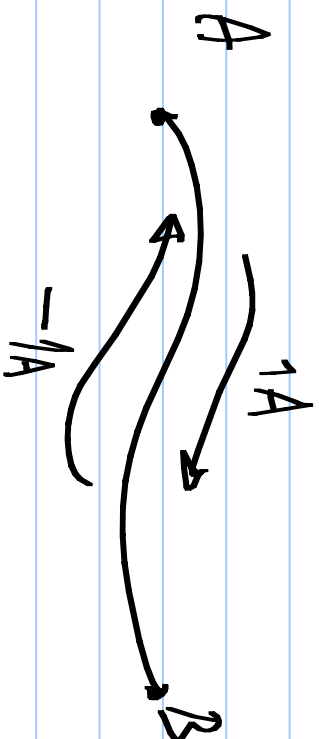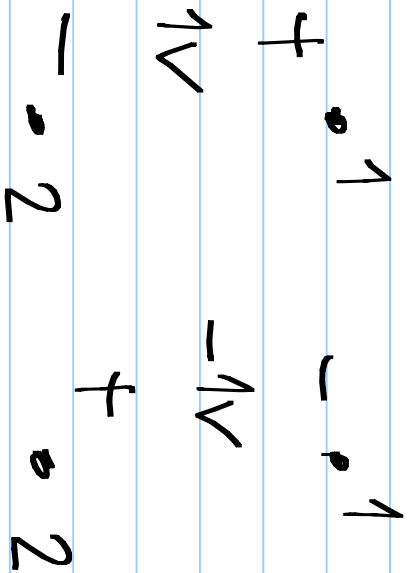

Resistor:

$$V = I \cdot R \quad R: \text{ohms } (\Omega)$$



$$I = G \cdot V$$


$$\text{Conductance } G = \frac{1}{R}$$

Siemens (S)



$$\text{slope} = \frac{1}{R} = G$$

"Linear"

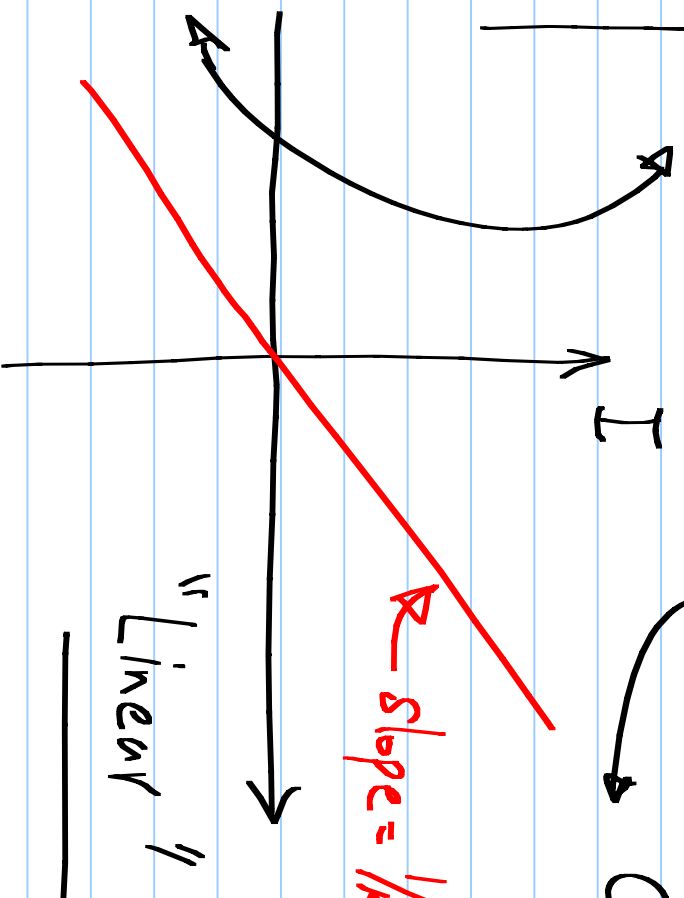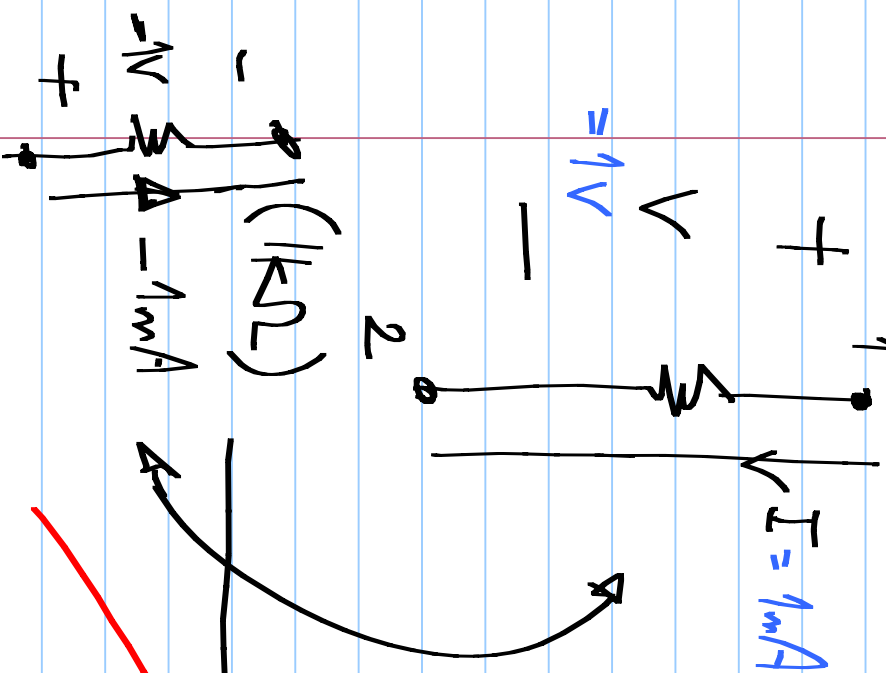

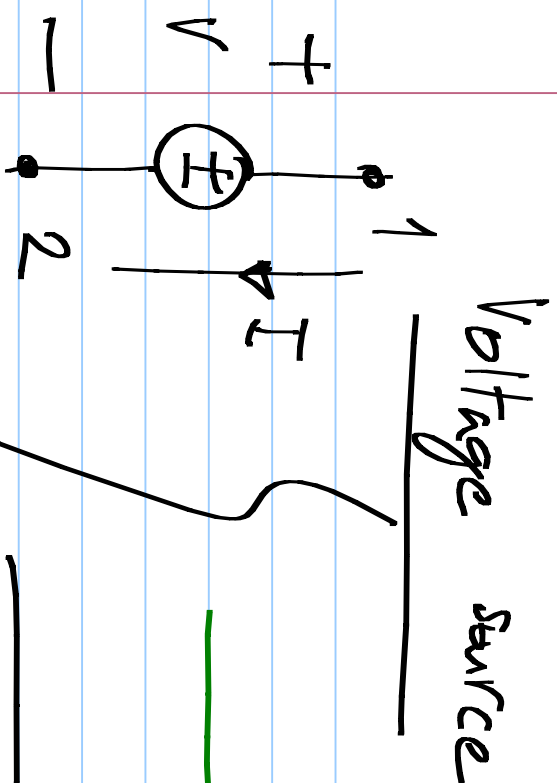

Voltage source

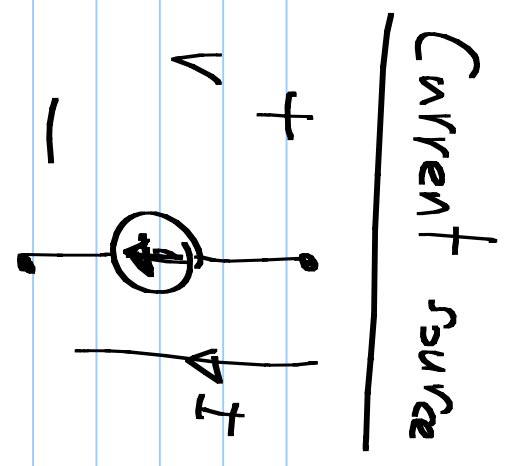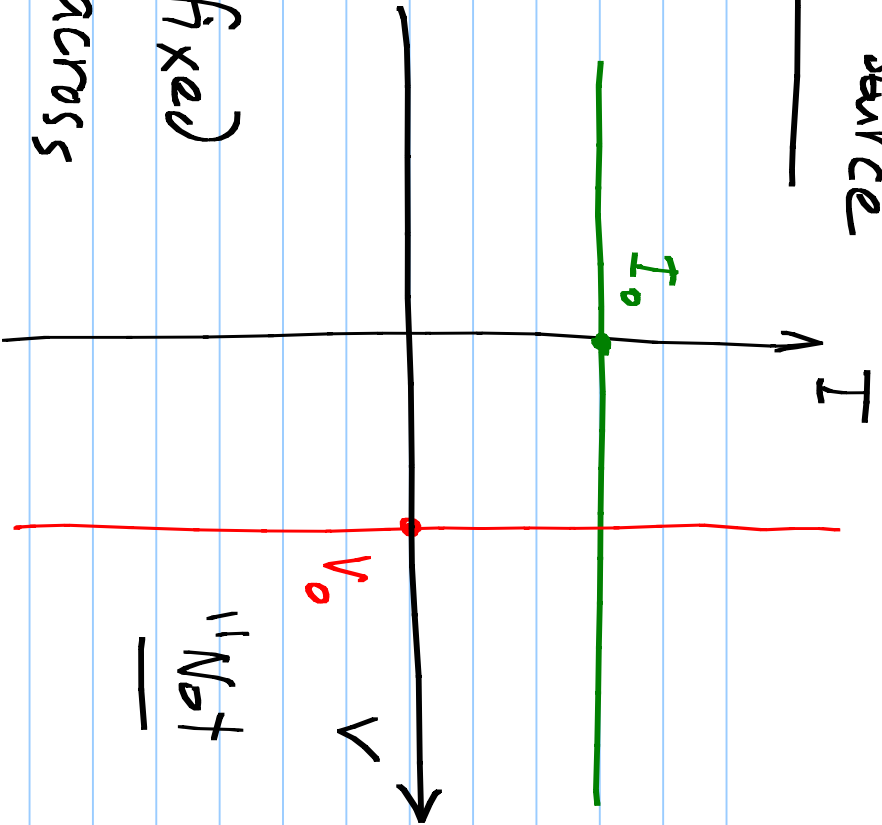

Current source

$I = I_0$

"Not linear"

Establishes a fixed
p. difference across

1-2

$V = V_0$

Linearity:

response \propto stimulus
output \propto input

output₁ \leftarrow input₁


output₂ \leftarrow input₂

output₁ + output₂ \leftarrow input₁ + input₂

$\alpha \cdot$ output₁ + β output₂

\leftarrow

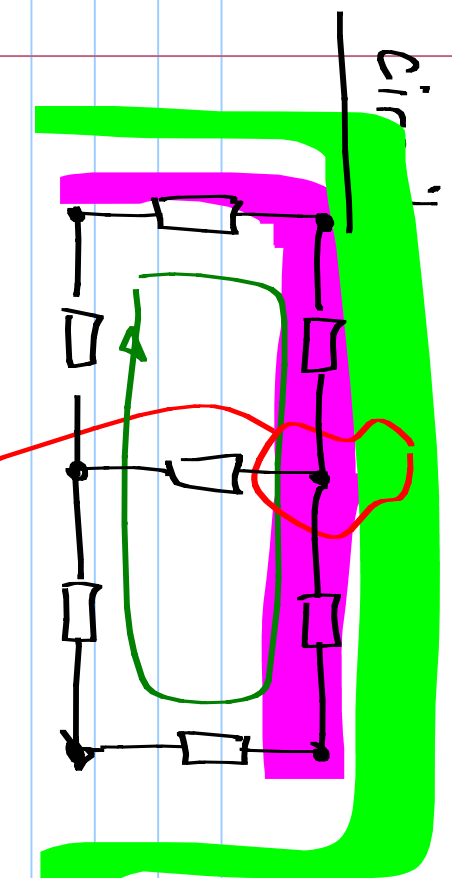$\alpha \cdot$ input₁ + $\beta \cdot$ input₂



Circuit: Interconnection
of elements w/ at least
1 closed loop.


Path: Elements + nodes (contiguous)

Loop: Closed path

Branch: Element connects between two nodes

②


Node :

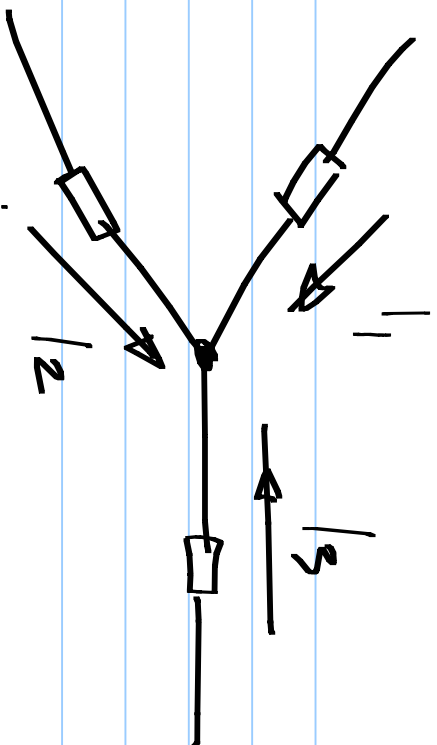

Kirchhoff's
Current
Law (KCL)

$$I_1 + I_2 + I_3 = 0$$

Σ currents flowing into a node = 0

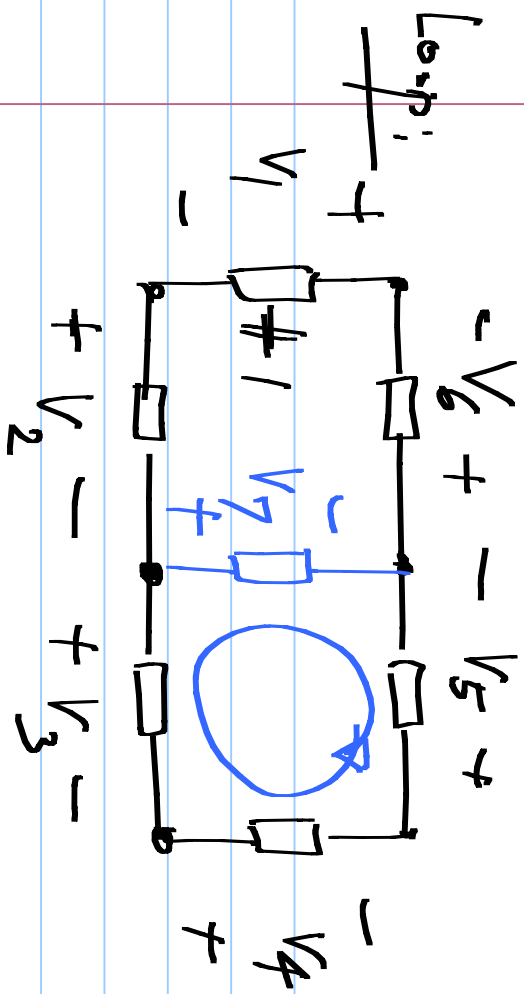


$$\sum_{k=1}^6 V_k = 0$$

Kirchhoff's voltage law (KVL)


$$V_1 + V_2 + V_7 + V_6 = 0$$

$$V_5 + V_4 + V_3 - V_7 = 0$$

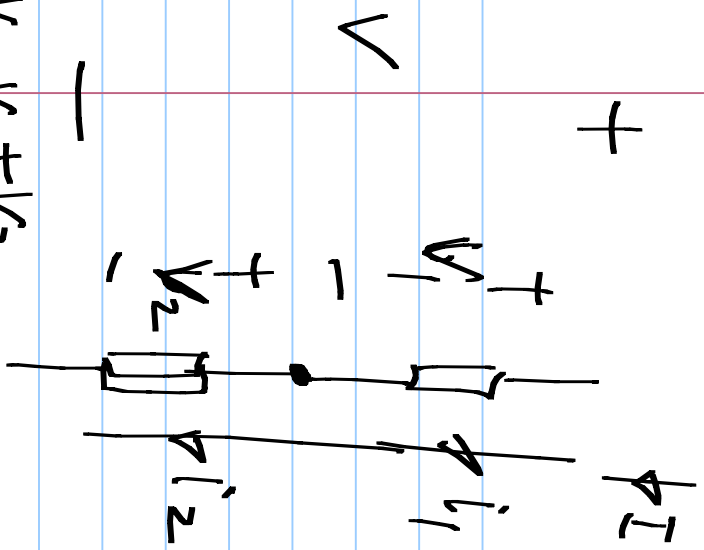


$V = V_1 + V_2$
 $I = I_1 = I_2$ Series Connection

(Identical currents)


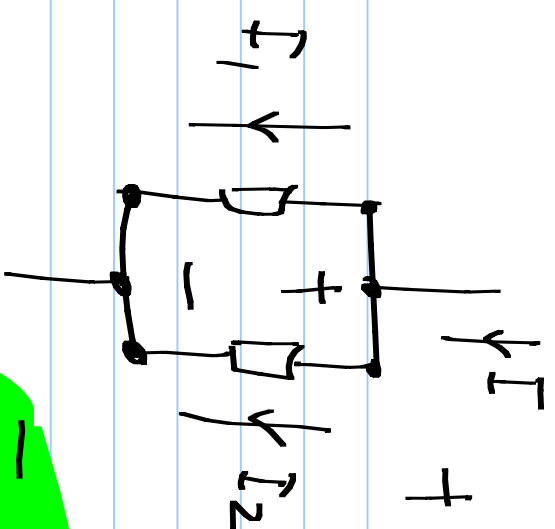


Parallel Connection
 $V = V_1 = V_2$
 $I = I_1 + I_2$

(Identical Voltages)

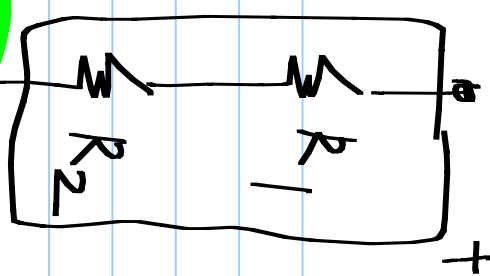

$V = (R_1 + R_2) I$

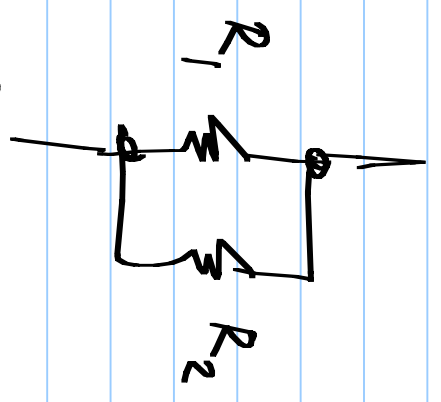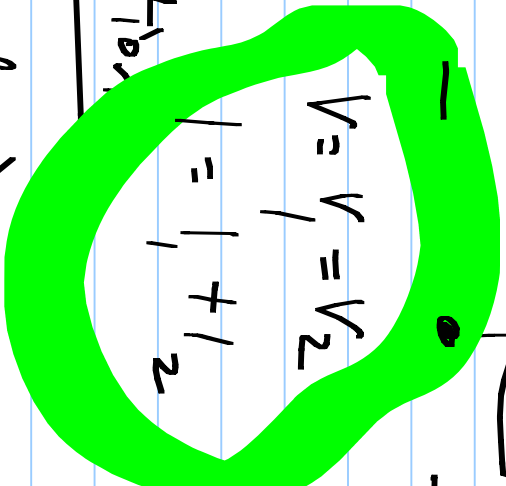

$V = \frac{R_1 R_2}{R_1 + R_2} \cdot I$

