

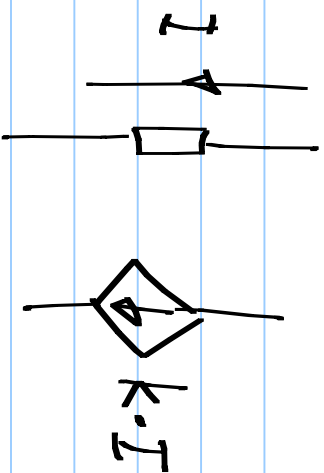
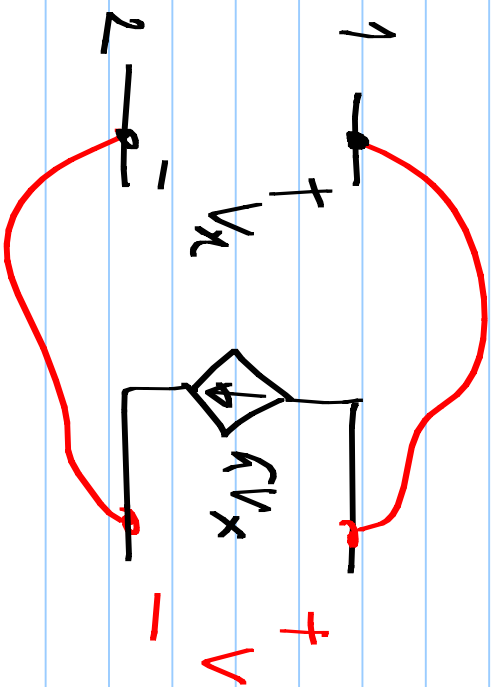
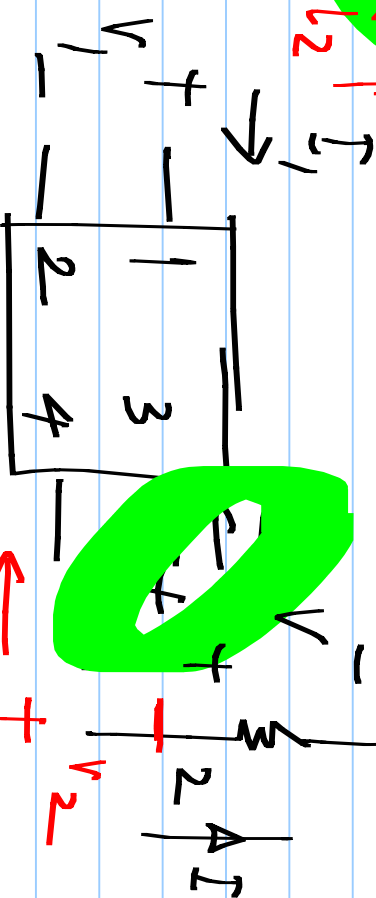
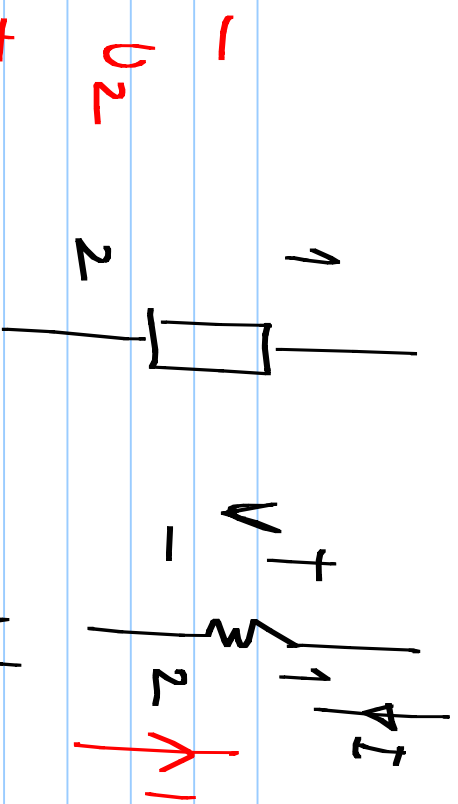



Lecture #4 Voltage dependent source


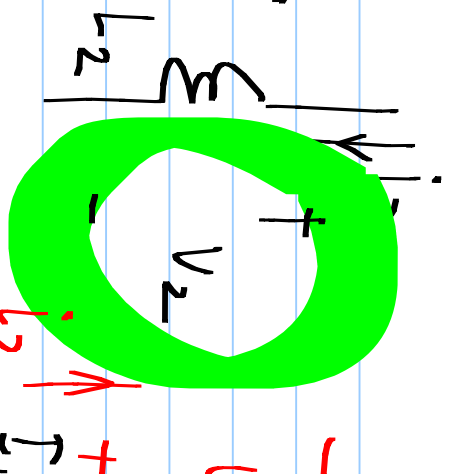


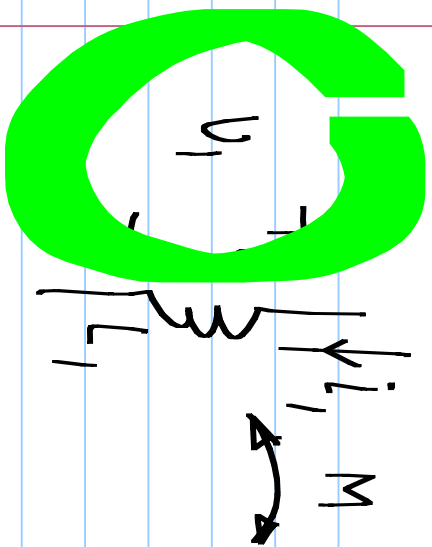

$$V_1 = L_1 \cdot \frac{di_1}{dt} + M \cdot \frac{di_2}{dt}$$

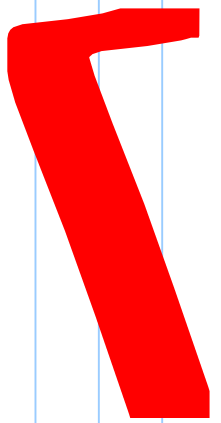
$$V_2 = M \cdot \frac{di_1}{dt} + L_2 \cdot \frac{di_2}{dt}$$



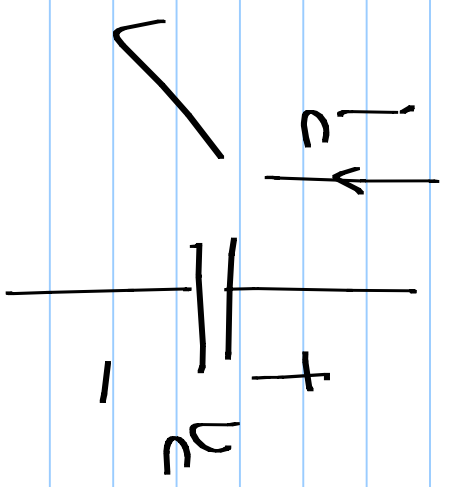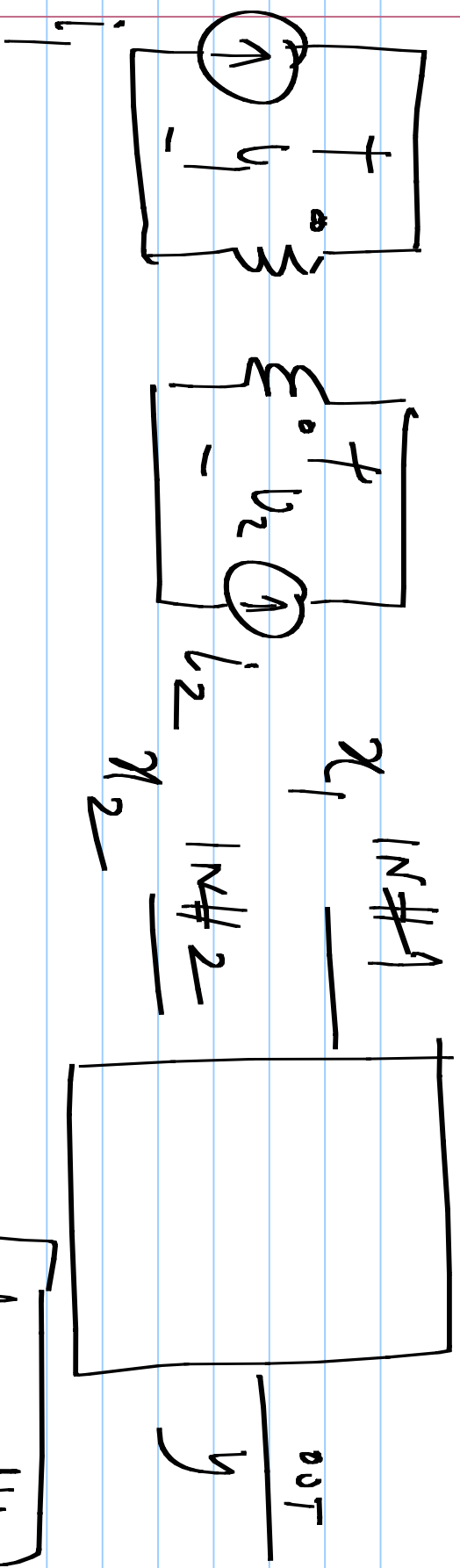


$$i_C = C \cdot \frac{dv_C}{dt}$$

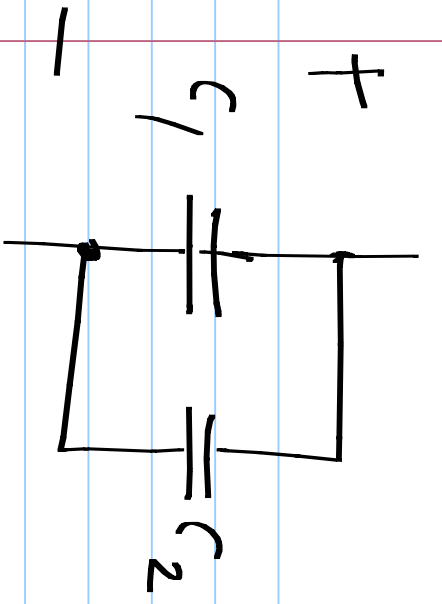
$$\frac{dv_C}{dt} = \frac{1}{C} \frac{d(v_1 + v_2)}{dt}$$




$$\equiv C_1 + C_2$$

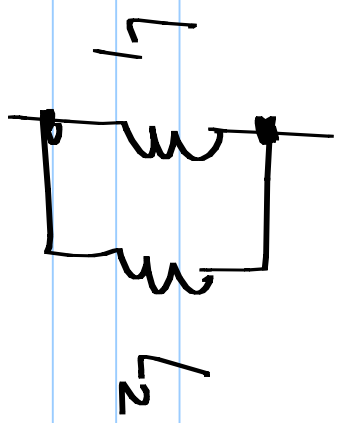


$$\equiv \frac{L_1 L_2}{L_1 + L_2}$$

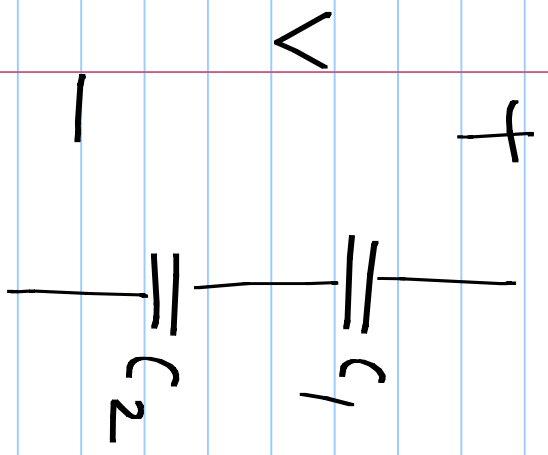

$$\equiv \frac{C_1 C_2}{C_1 + C_2}$$

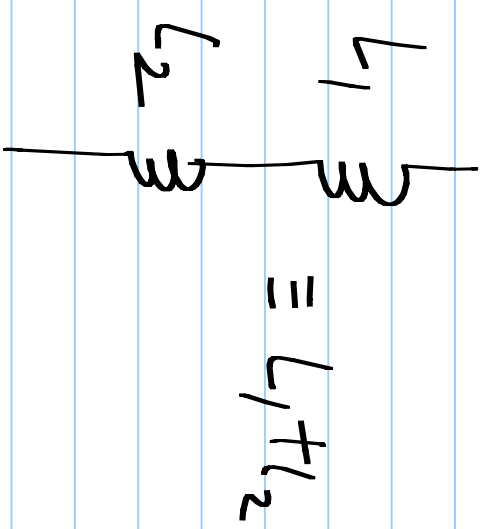

$$\equiv L_1 + L_2$$

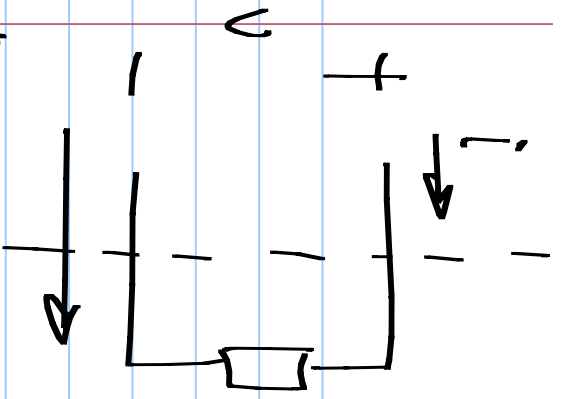


Power going into

$$P(t) = v \cdot i$$

this part = $v \cdot i$

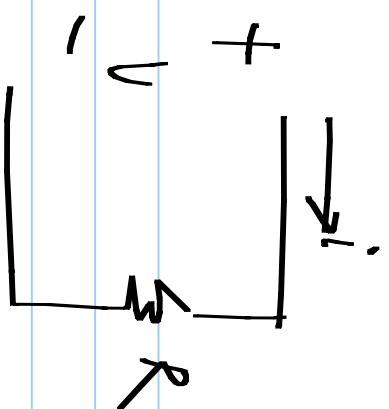
$$E = \int_0^{t^-} v(t) \cdot i(t) \cdot dt$$



$$v = iR$$

$$P = v^2 / R = i^2 \cdot R$$

Always dissipates power

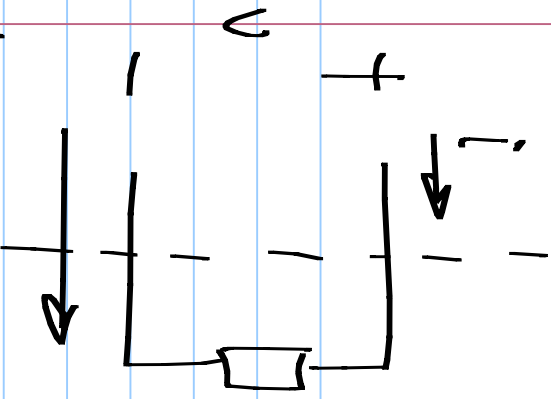


Power going into

$$P(t) = v \cdot i$$

this part = $v \cdot i$

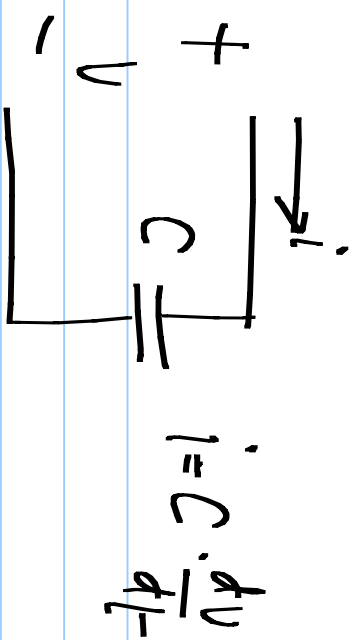
$$E = \int_0^{t^-} v(t) \cdot i(t) \cdot dt$$




$$P = C v \cdot \frac{dv}{dt} = \frac{d}{dt} \left(\frac{Cv^2}{2} \right)$$


$$E = \frac{Cv^2}{2} \quad \text{(Stored in the)}$$

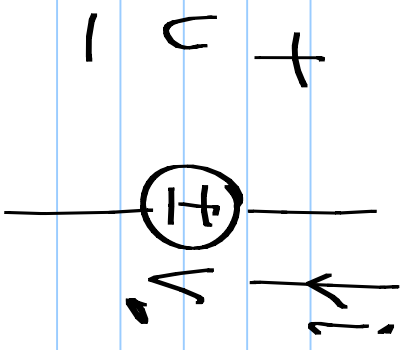
$$P = \frac{L i \frac{di}{dt}}{\text{(capacitor)}} = \frac{d}{dt} \left(\frac{Li^2}{2} \right)$$



$V_0 \cdot i_i$

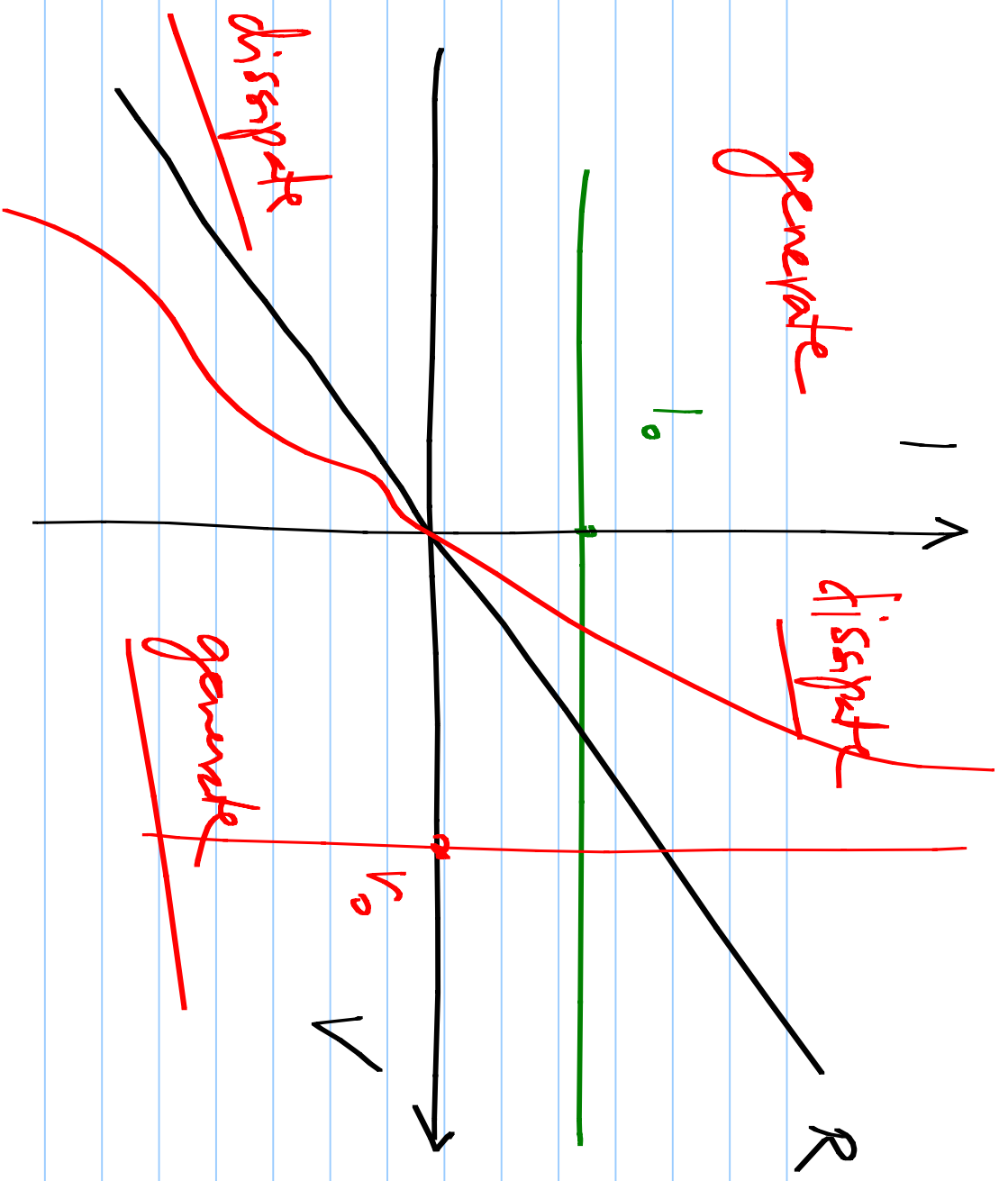

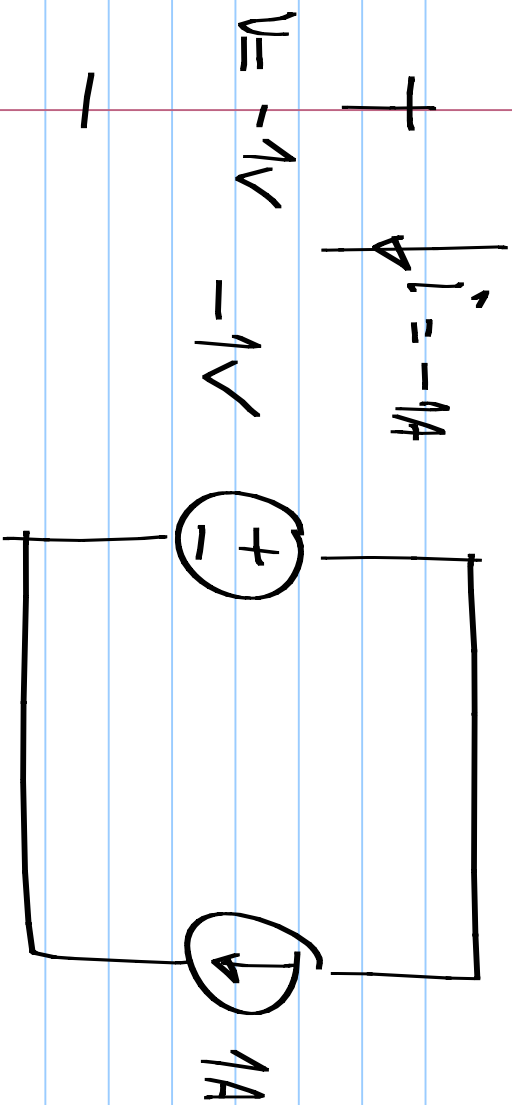

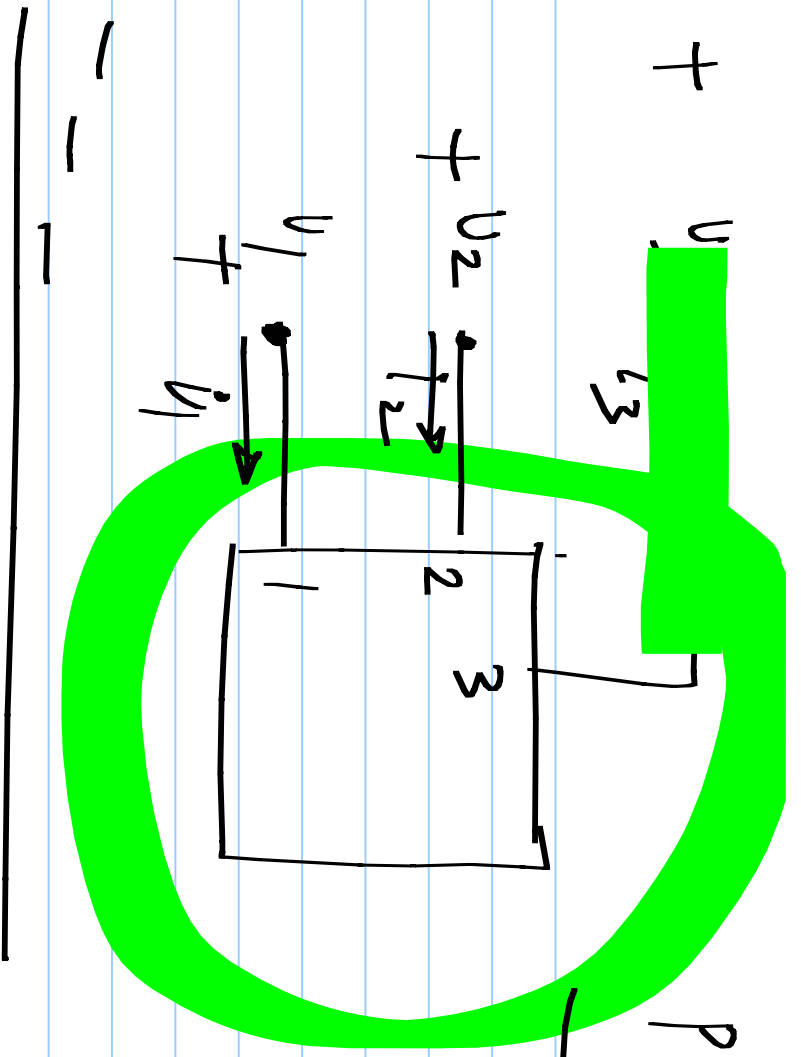


$$+ v_3 i_3 \quad P = v_1 i_1 + v_2 i_2 + v_3 i_3$$

$$i_1 + i_2 + i_3 = 0$$

$$i_3 = -i_1 - i_2$$

$$P = v_1 i_1 + v_2 i_2 + v_3 (-i_1 - i_2)$$


$$= (v_1 - v_3) i_1 + (v_2 - v_3) i_2$$

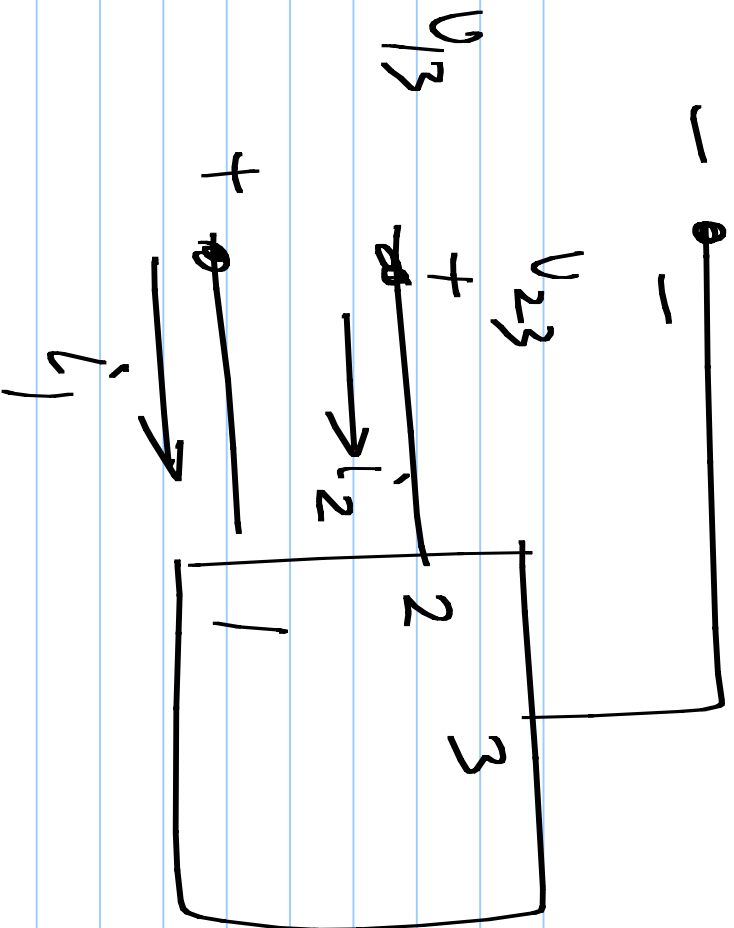

$$p = V_{13} i_1 + V_{23} i_2$$

Total power input to the 3 terminal

Circuit-

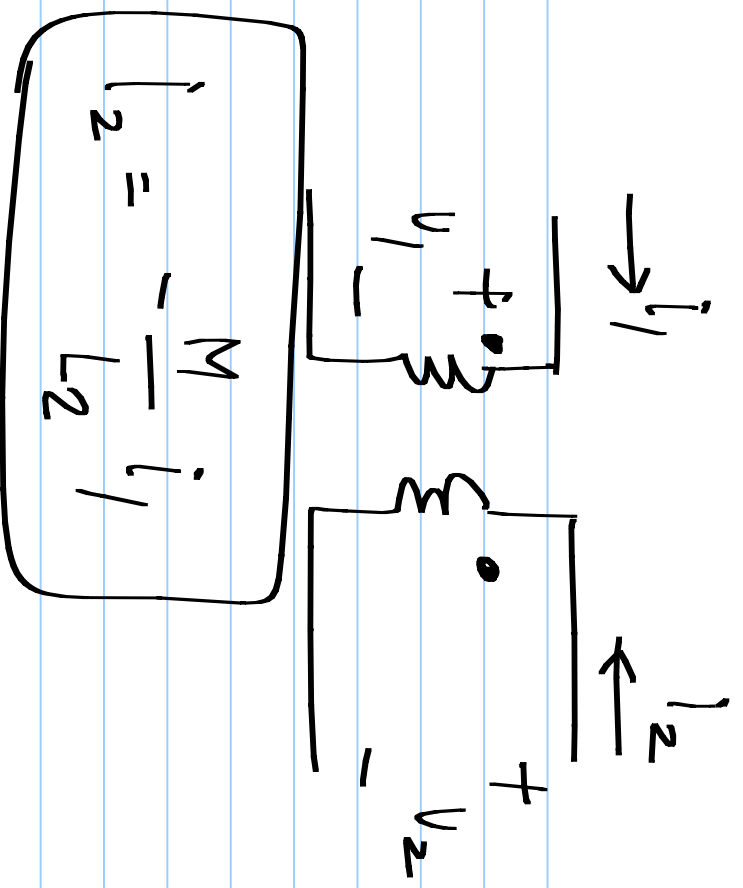

$$P = v_1 i_1 + v_2 i_2$$

$$= L_1 i_1 \frac{di_1}{dt} + M i_1 \frac{di_2}{dt}$$

$$+ M i_2 \frac{di_1}{dt} + L_2 i_2 \frac{di_2}{dt}$$

$$= \frac{d}{dt} \left(\frac{L_1 i_1^2}{2} + \frac{L_2 i_2^2}{2} + M i_1 i_2 \right)$$

Energy

$$E | = \left(L_1 - \frac{M_2^2}{L_2} \right) \cdot \frac{L_1^2}{2}$$

$$L_2' = -\frac{M_2}{L_2}$$