

Lecture 5


Energy in a
mutual inductor: $\frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M \cdot i_1 i_2$

$$\text{For } i_2 = -\frac{M}{L_2} \cdot i_1$$

$$\left(L_1 - \frac{M^2}{L_2} \right) \frac{1}{2} i_1^2 = \left(\frac{L_1 L_2 - M^2}{L_2} \right) \frac{1}{2} i_1^2$$

$$L_1 L_2 \geq M^2 \quad M \leq \sqrt{L_1 L_2}$$

$$k = \frac{M}{\sqrt{L_1 L_2}} \leq 1$$

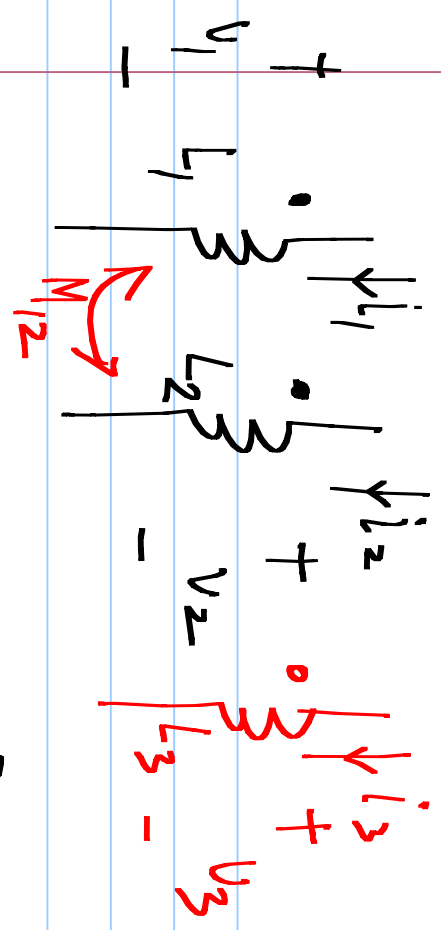

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} L_1 & M_{12} \\ M_{12} & L_2 \end{bmatrix} \begin{bmatrix} \frac{dx_1^i}{dt} \\ \frac{dx_2^i}{dt} \end{bmatrix}$$


$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} L_1 & M_{12} & M_{13} \\ M_{12} & L_2 & M_{23} \\ M_{13} & M_{23} & L_3 \end{bmatrix} \begin{bmatrix} \frac{dx_1^i}{dt} \\ \frac{dx_2^i}{dt} \\ \frac{dx_3^i}{dt} \end{bmatrix}$$

Linear elements: R, L, C, M, Controlled sources

Independent sources:

Current source


Voltage source

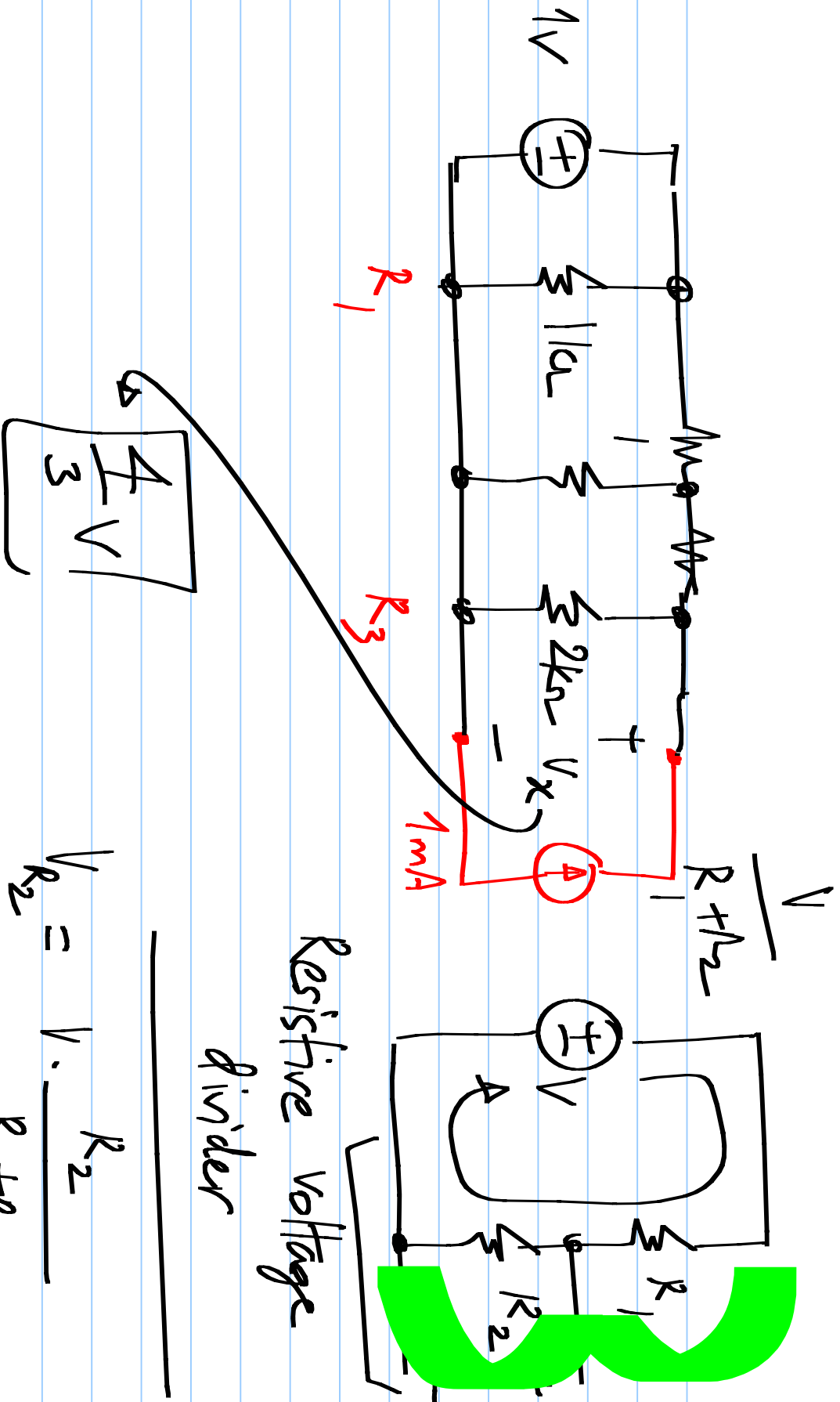

Resistive voltage divider


$$V_{R_2} = V \cdot \frac{R_2}{R_1 + R_2}$$

$$\frac{4}{3} V$$

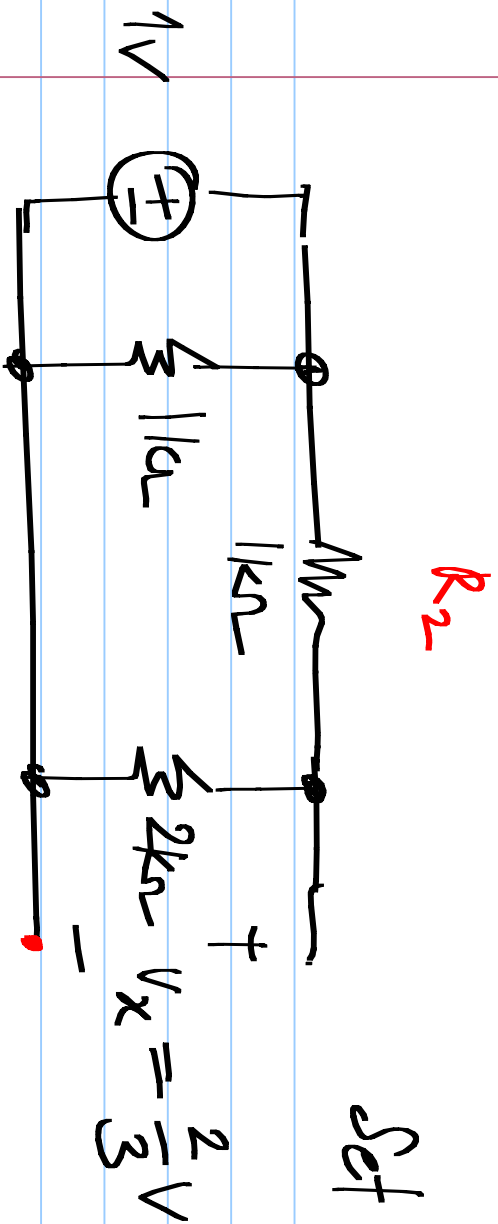


Set the current source

Value $\rightarrow 0$

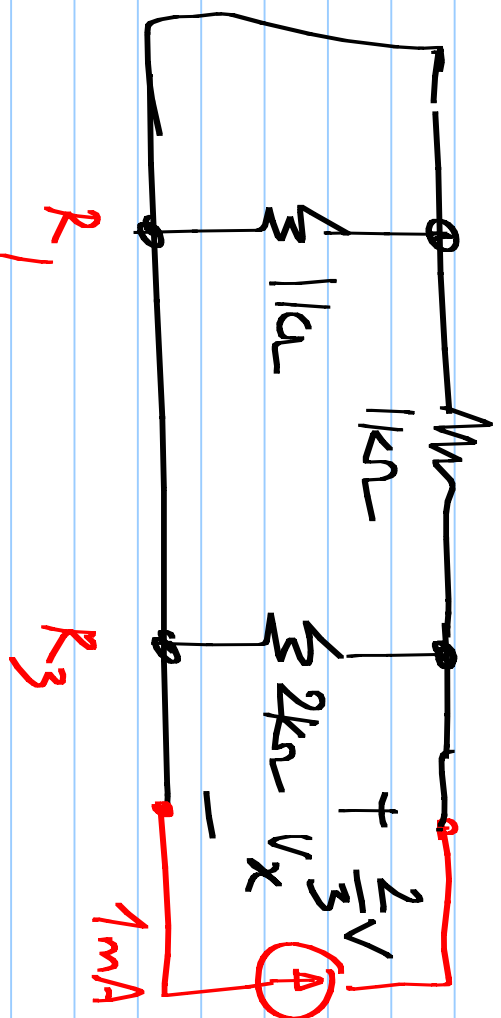

Set Voltage

Source value $\rightarrow 0$

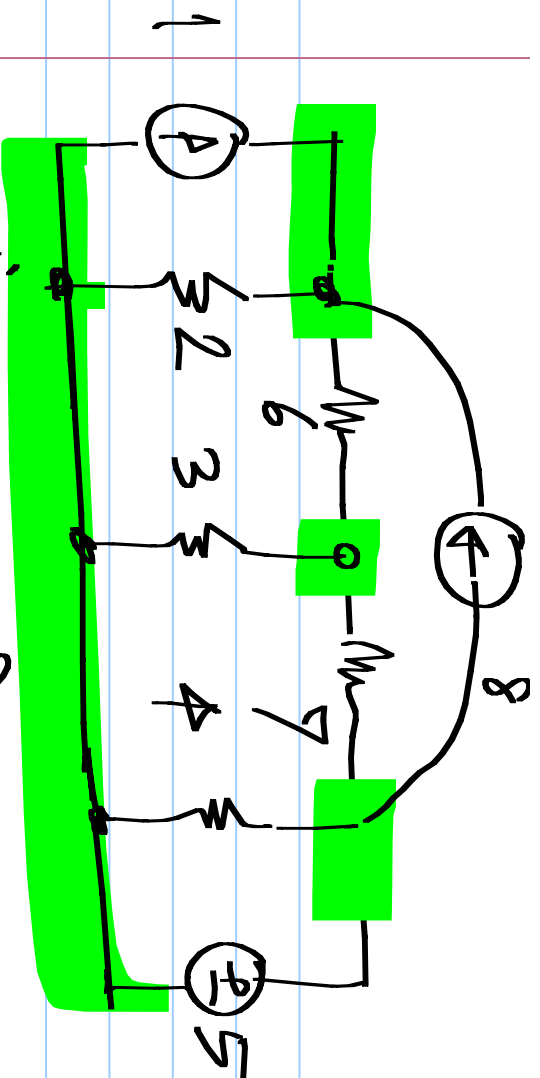


B branches / N nodes

B Voltages &

B currents


2B variables

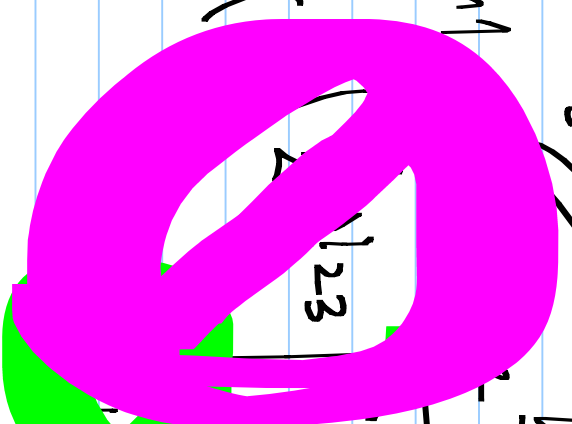

$$\begin{aligned}
 -i_1 - i_2 - i_6 - i_8 &= 0 \\
 i_6 - i_7 - i_3 &= 0 \\
 i_7 + i_8 - i_4 - i_5 &= 0 \\
 -i_1 - i_2 - i_3 - i_4 - i_5 &= 0
 \end{aligned}$$

②

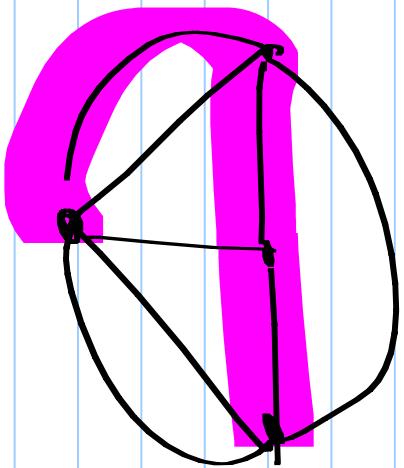Tree: Sub-graph containing all nodes without forming a loop $\{ N-1 \text{ branches} \}$



Adding a branch to a tree $\{ \text{which is not in} \}$ forms a loop. the tree?

$$B - (N-1) = B - N + 1$$

loops

$B - N + 1$ KVL equations

Circuit with B branches & N nodes

* $N-1$ independent KCL equations

* $B-N+1$ " KVL "

* B $V-1$ relationships for each branch

Start with KCL eq: Nodal analysis ✓

Start with KVL eq: Link / Mesh analysis

Nodal analysis :

