

Lecture 8


$$KCL : n_c = \begin{bmatrix} g & -g \\ -g & g \end{bmatrix} \begin{bmatrix} u \\ u' \end{bmatrix}$$


$$KCL : \begin{bmatrix} -1 \\ 1 \end{bmatrix} \begin{bmatrix} i_u \\ i_{u'} \end{bmatrix} = 0$$



$$-i_u + i_{u'} = 0$$


$$[-] [i_u]$$


$$KCL \quad n_d$$

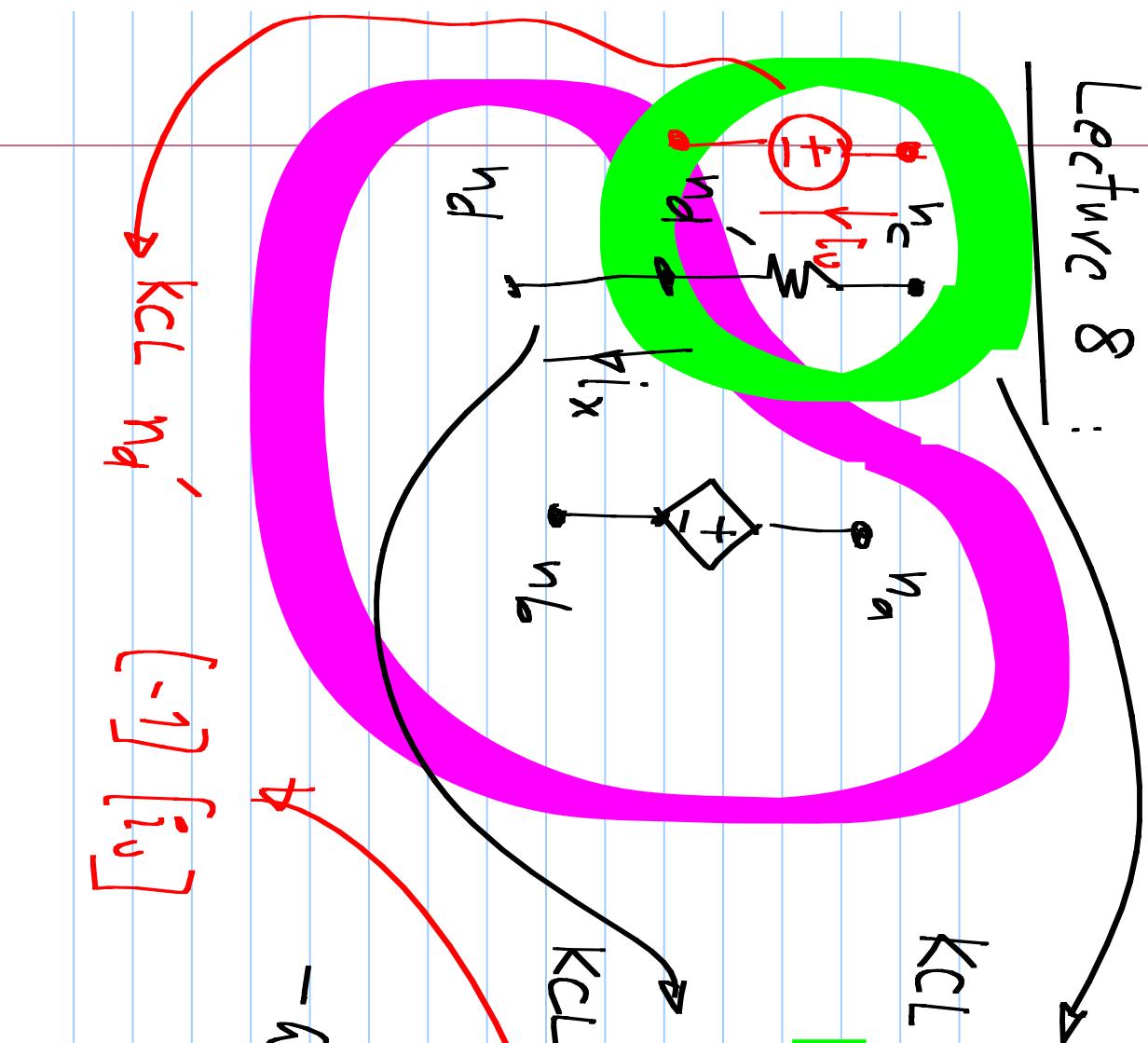


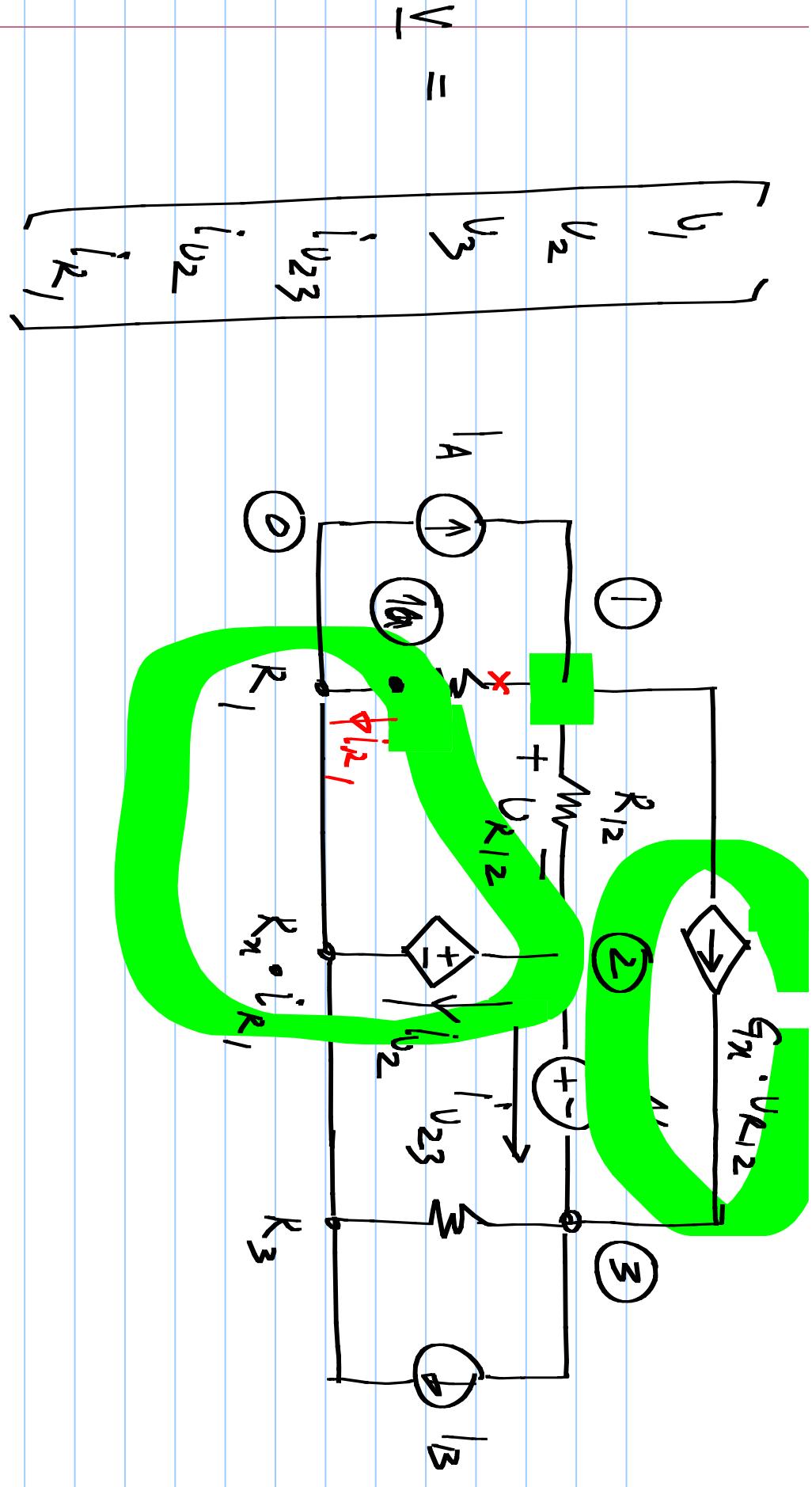

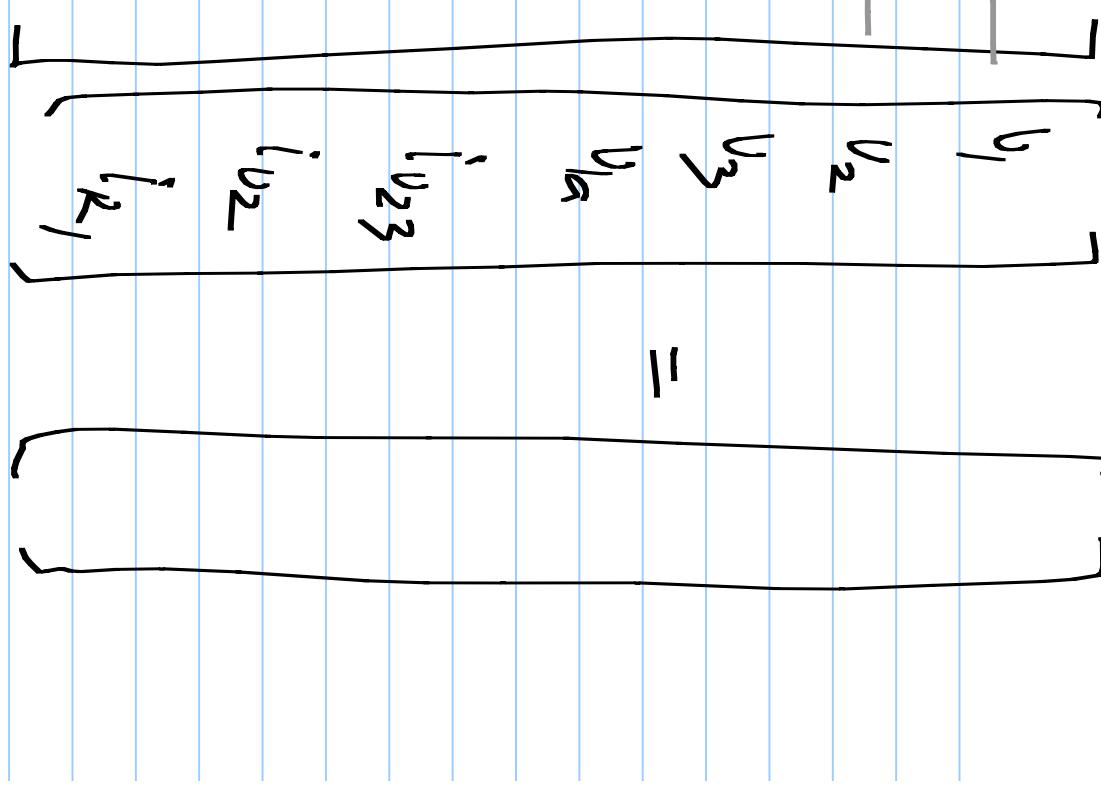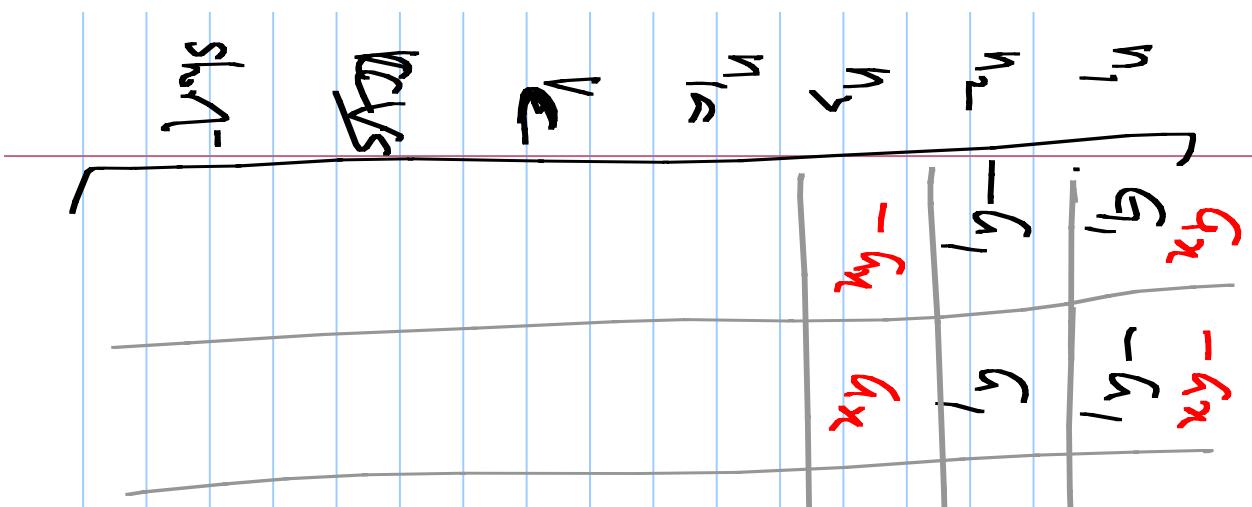

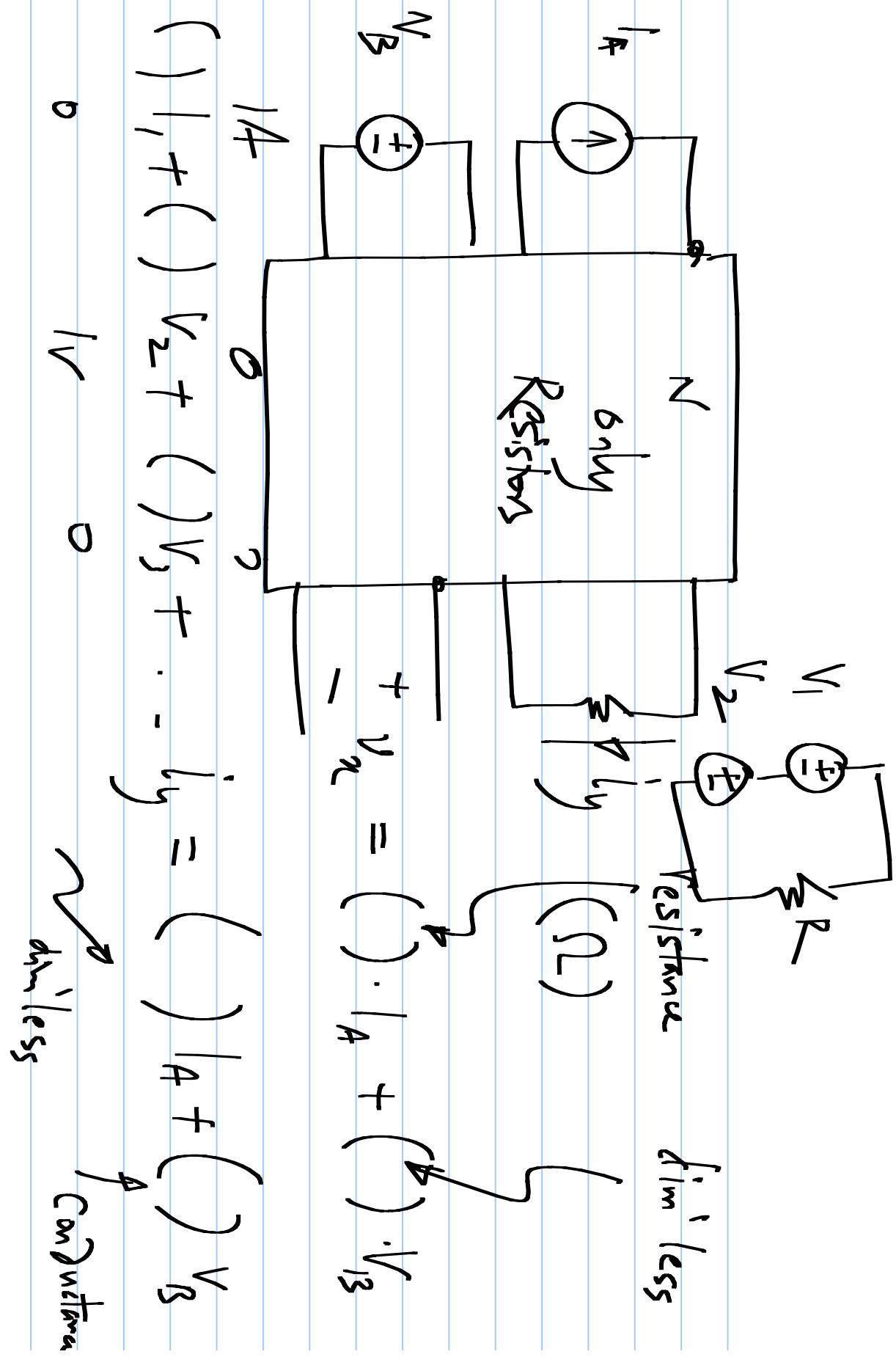

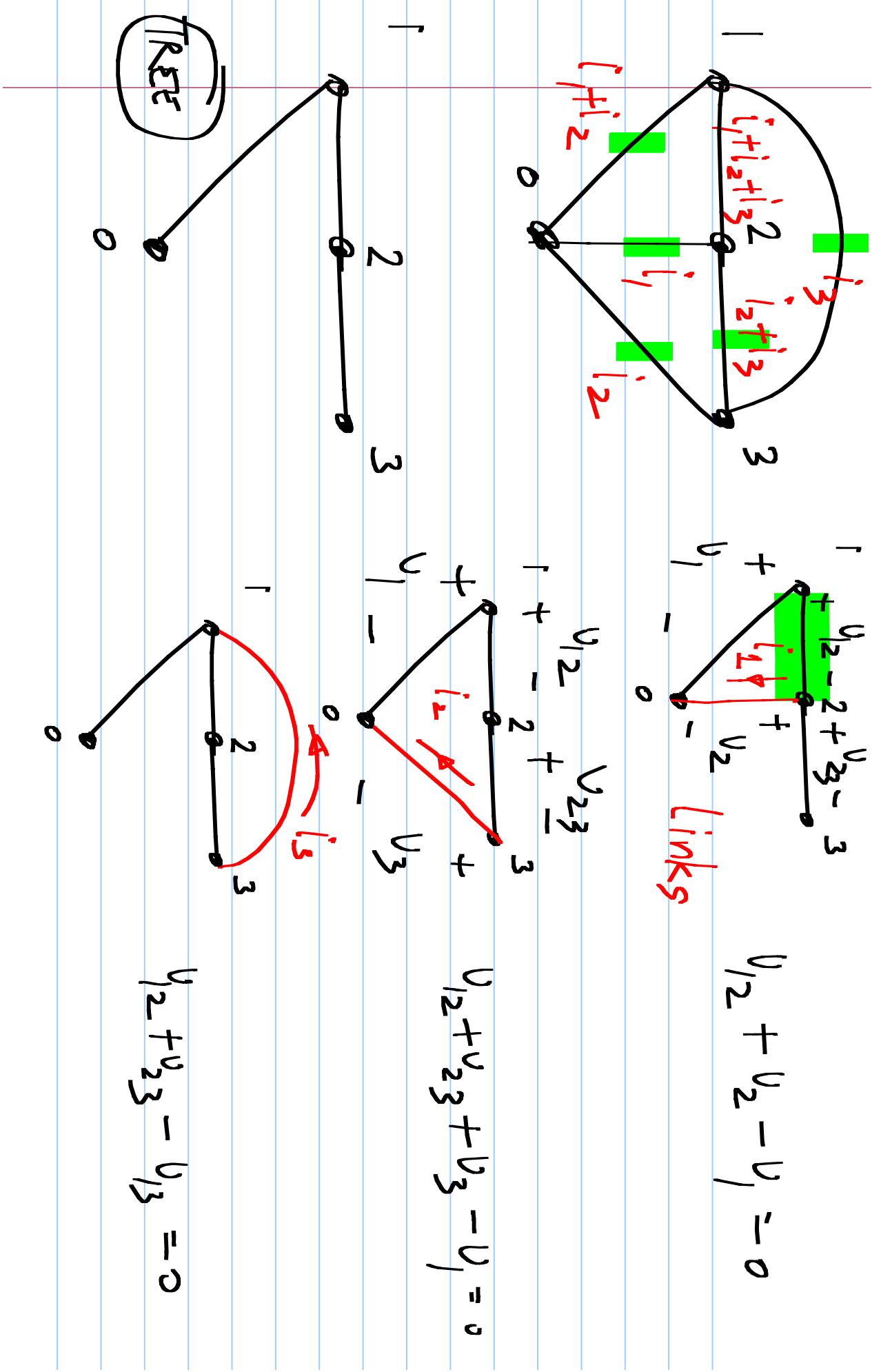

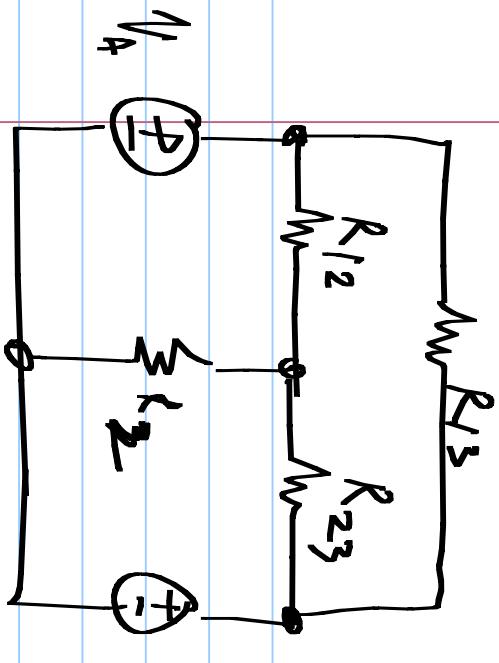

Loop #1

$$V_1 + V_2 - V_3 = 0$$

Loop #1: $V_1 + V_2 + V_3 - V_1 = 0$





$$R_{12}(i_1 + i_2 + i_3) + R_{23}(i_2 + i_3) = -V_B + V_A$$


Loop #2: $V_1 + V_2 + V_3 - V_1 = 0$

$$R_{12}(i_1 + i_2 + i_3) + R_{13}(i_2 + i_3) = -V_B + V_A$$

Loop #3: $V_1 + V_2 + V_3 - V_3 = 0$
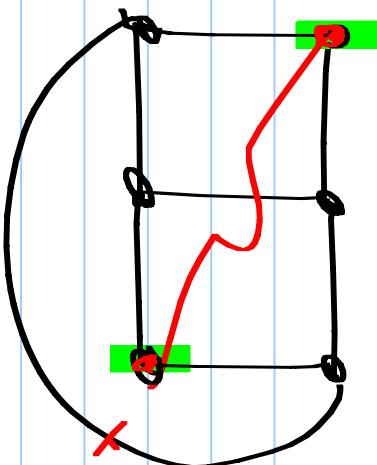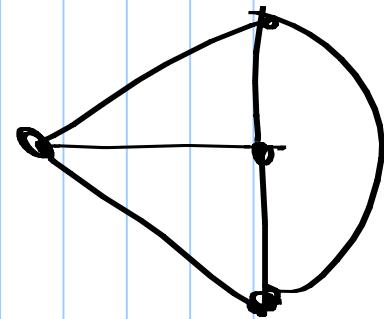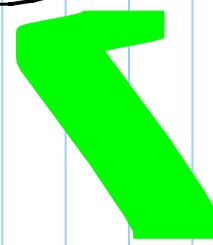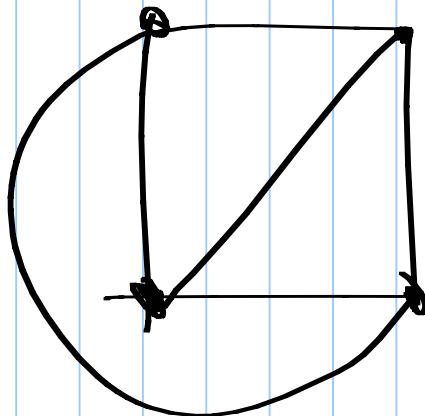
$$R_{12}(i_1 + i_2 + i_3) + R_{23}(i_2 + i_3) + R_{13}(i_3) = 0$$



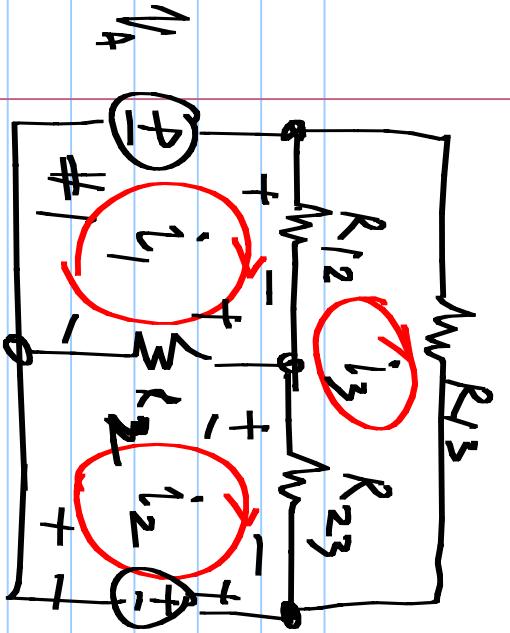

$$\begin{aligned} \#1 \quad & R_{12} (i_1 - i_3) + R_2 \cdot (i_1 - i_2) = V_A \\ \#2 \quad & R_{23} (i_2 - i_3) + R_2 (i_2 - i_1) = -V_B \\ \#3 \quad & R_{13} \cdot i_3 + R_{23} (i_3 - i_2) + R_{12} (i_3 - i_1) = 0 \end{aligned}$$

Meshes

$$\begin{bmatrix} R_{12} + R_2 - R_2 & -R_{12} \\ -R_2 & R_2 + R_{23} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_A \\ -V_B \end{bmatrix}$$

$$\begin{bmatrix} -R_{12} & -R_{23} \\ R_{13} + R_{12} & +R_{23} \end{bmatrix} \begin{bmatrix} i_3 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$