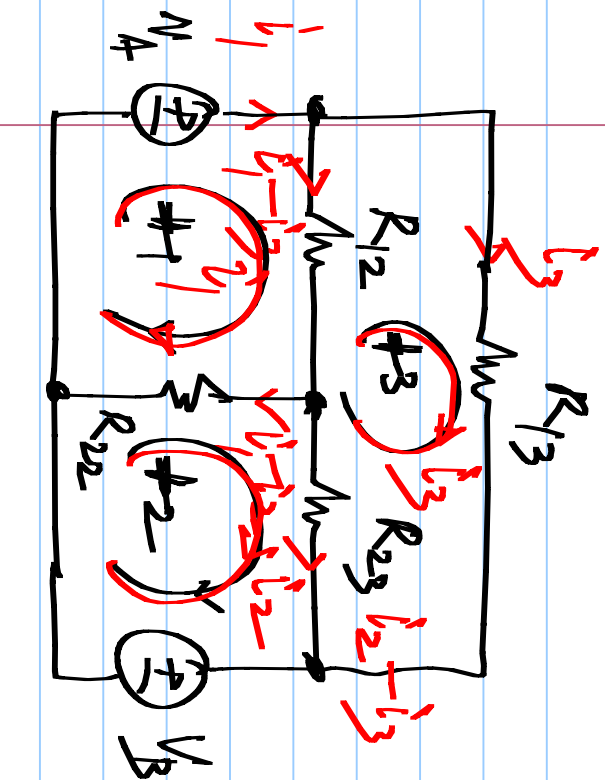


Lecture 9

Mesh analysis:

* Based on KVL around each mesh

* Applicable to planar circuits
* Mesh currents (clockwise direction)



$$\#1: R_{12}(i_1 - i_3) + R_{22}(i_1 - i_2) = -V_A$$

$$\#2: R_{23}(i_2 - i_3) + R_{22}(i_2 - i_1) = -V_B$$


$$\#3: R_{13} \cdot i_3 + R_{12}(i_3 - i_1) + R_{23}(i_3 - i_2) = 0$$

$$\begin{bmatrix} R_{12} + R_{22} & -R_{22} & -R_{12} \\ -R_{22} & R_{22} + R_{23} & R_{23} \\ -R_{12} & -R_{23} & R_{12} + R_{23} + R_{13} \end{bmatrix}
 \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}
 =
 \begin{bmatrix} V_A \\ -V_B \\ 0 \end{bmatrix}$$

$$\underline{R} \cdot \underline{i} = \underline{V}$$


~
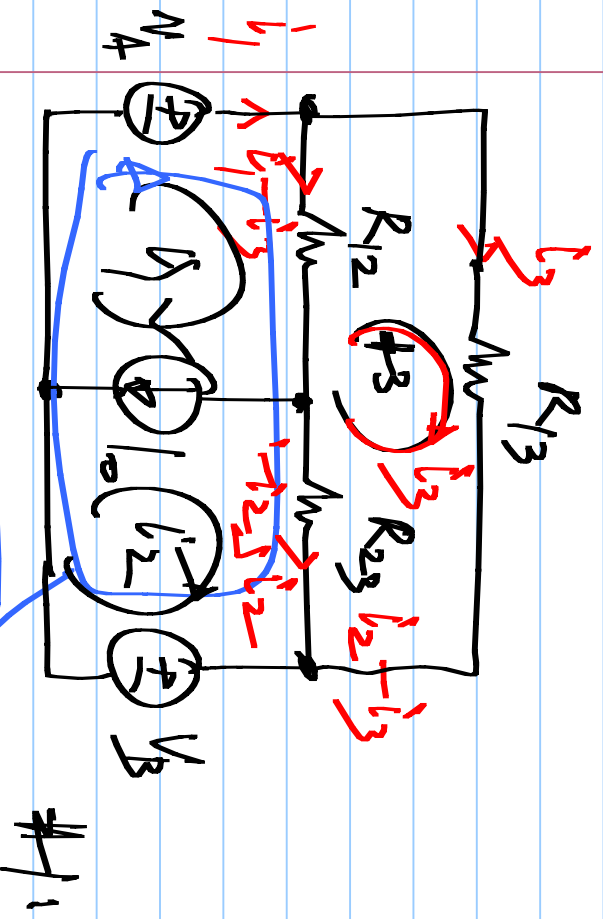
$$\underline{G} \cdot \underline{V} = \underline{I}$$





$$i_1 - i_2 = i_3$$

Supermesh


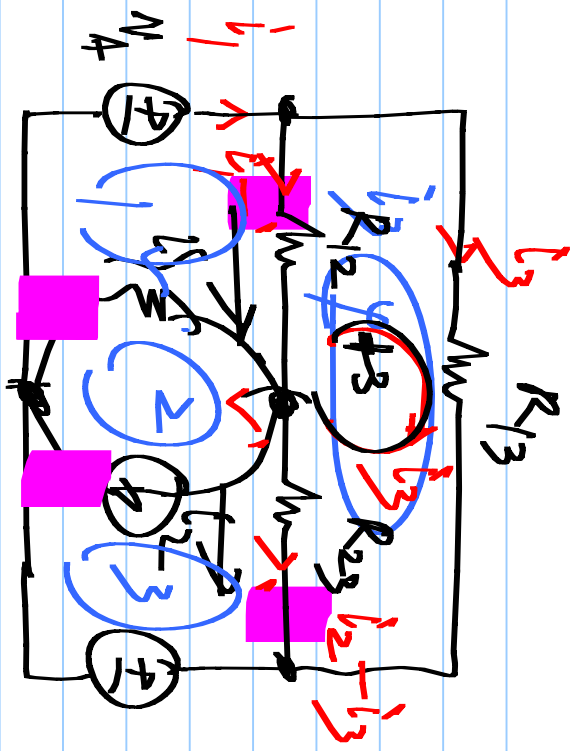


Circuit theorems:

Substitution theorem

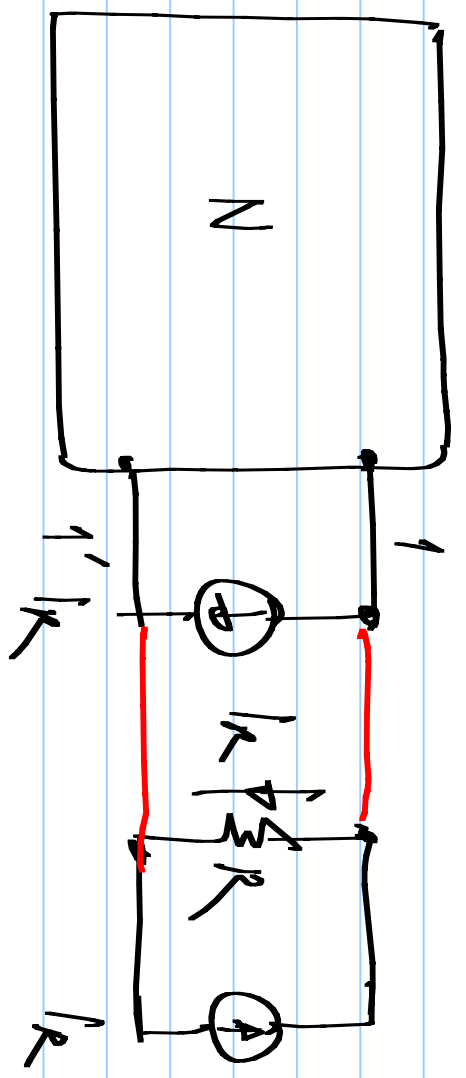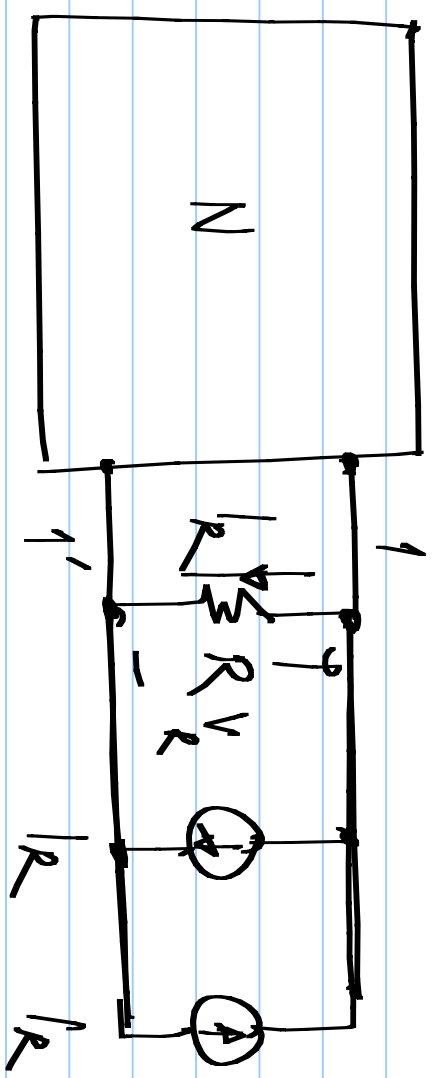

—

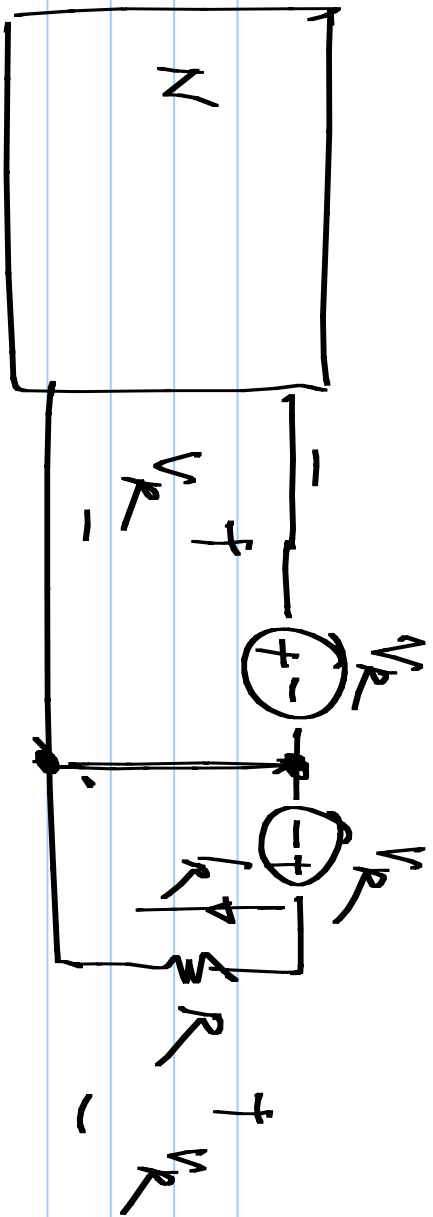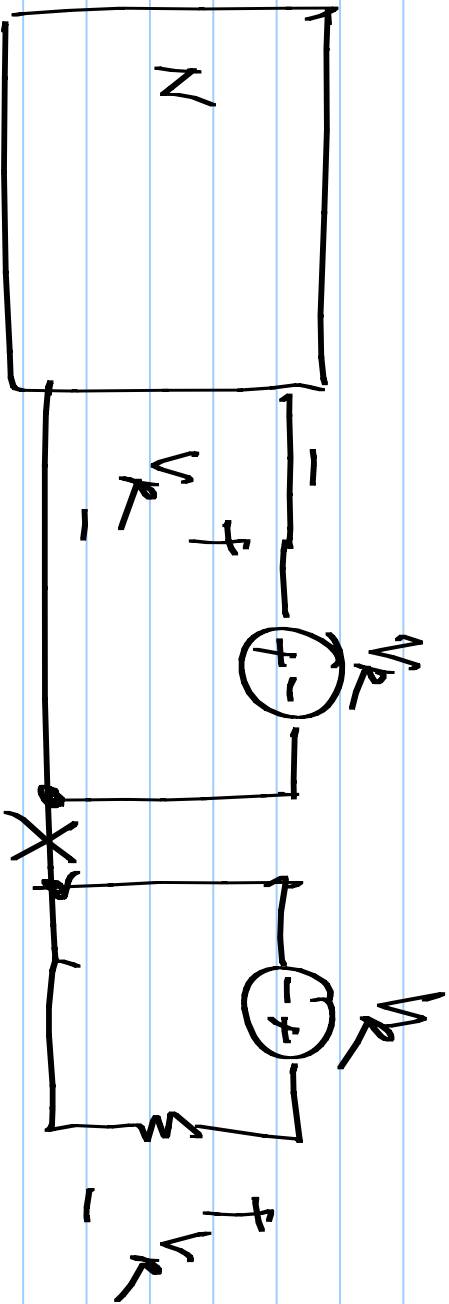

* Substitution theorem:

any two terminal
element-

A resistor R with a voltage V_R across it
and a current I_R through it can be

replaced by a current source I_R OR a
voltage source V_R without changing the solution

voltage / current sources can be substituted by a
resistor if they are dissipating power.

