


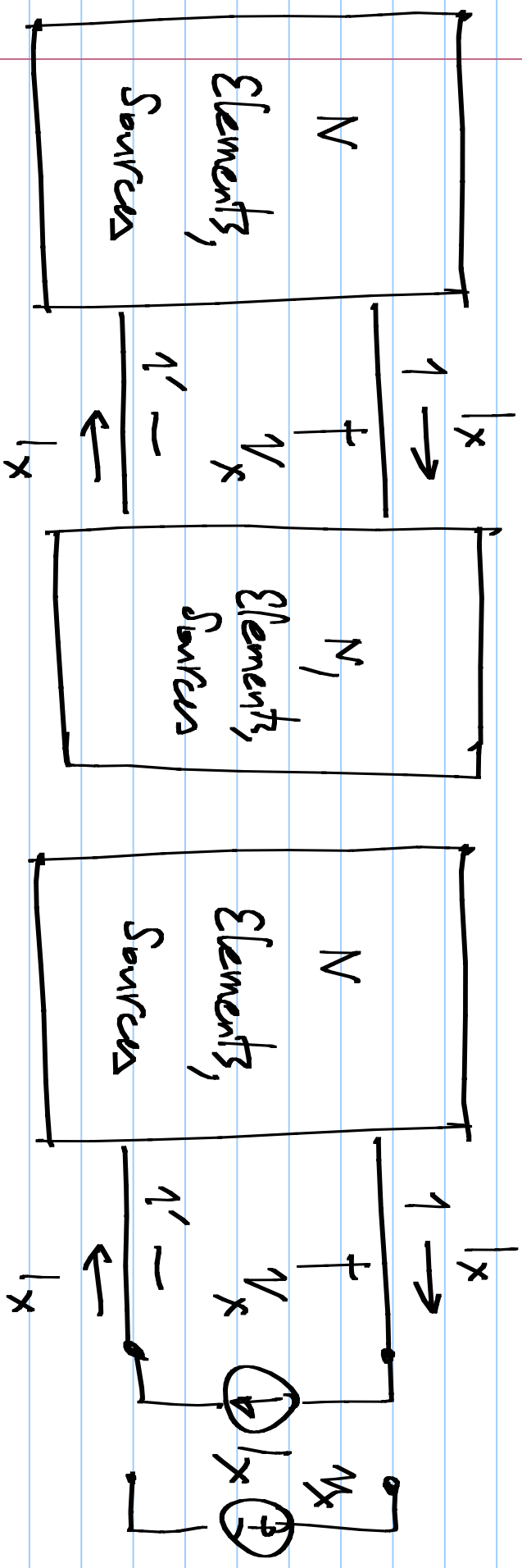
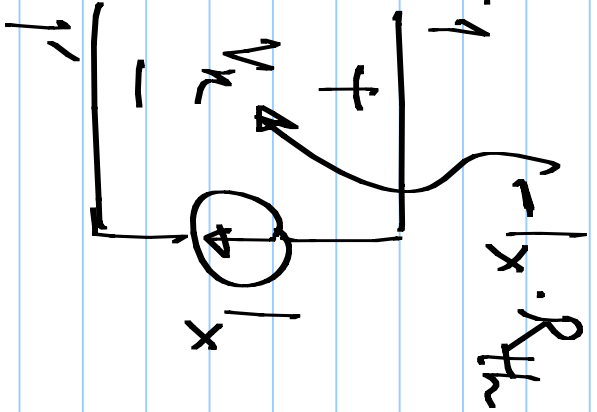
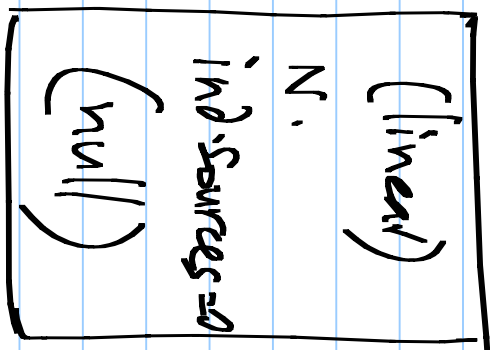
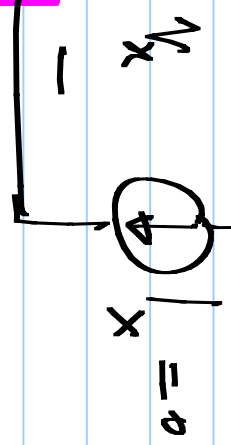
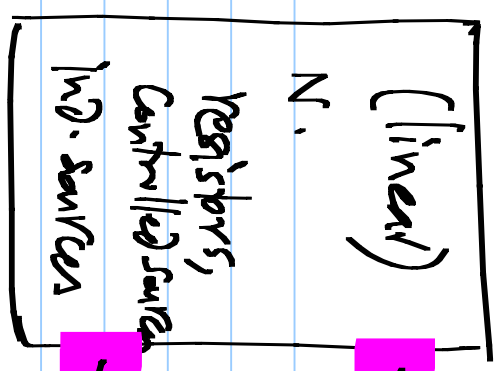
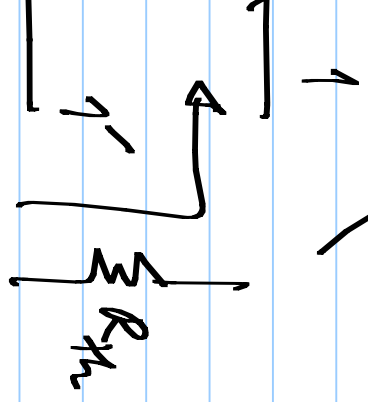



# Lecture 10

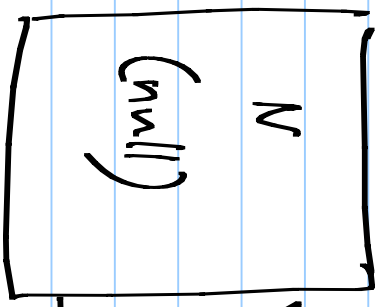

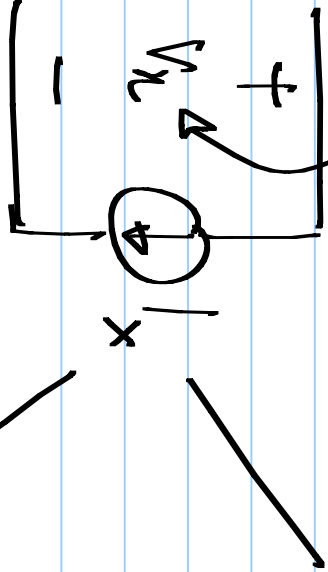

$$V_k - I_k \cdot R_k$$

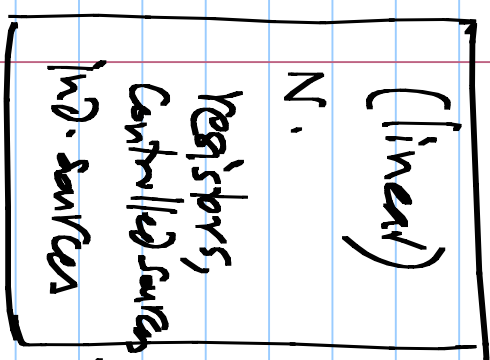

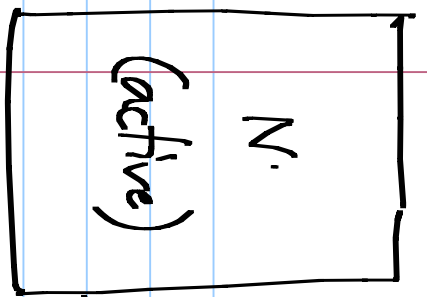


open ckt.

Voltage


Thevenin

voltage


open circuited

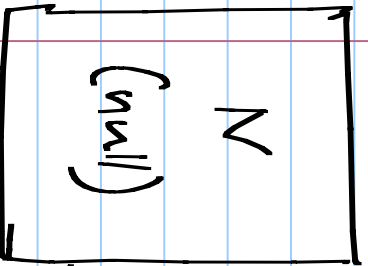


Thevenin  
resistance

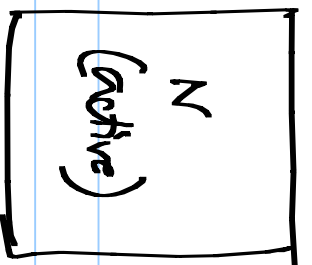


$$= V_{th} - I_x \cdot R_{th}$$

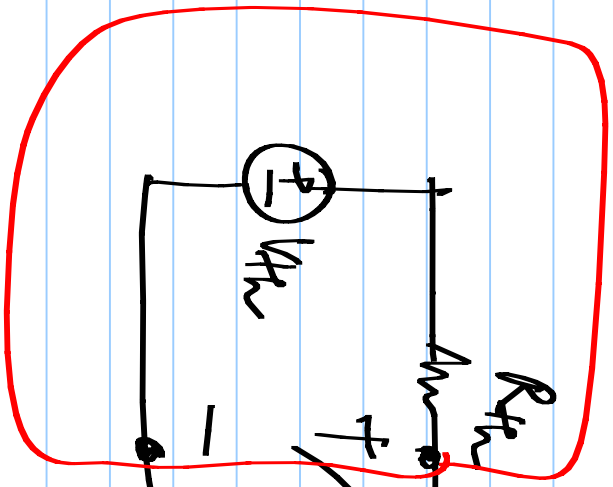



Thevenin  
equivalent

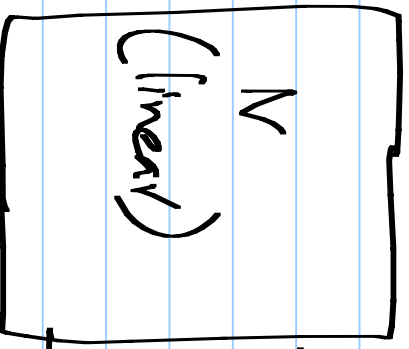


$I_x$  →  $I_N - \frac{V_x}{R_{th}}$

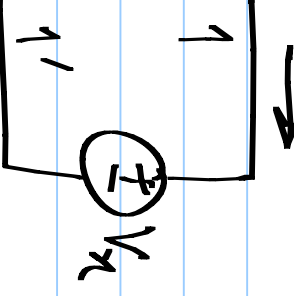

$I_N - \frac{V_x}{R_{th}}$

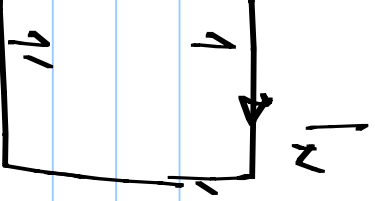
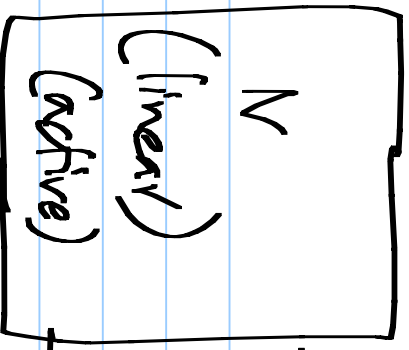


Norton current  
short-ckt. current

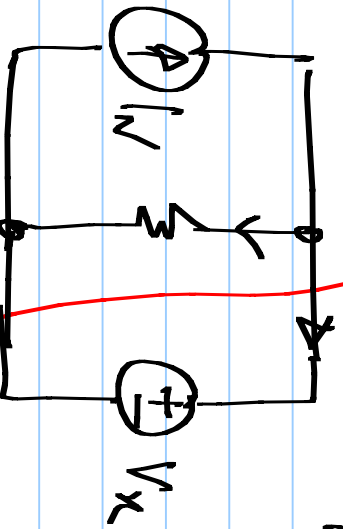


$R_N = R_{th}$

Norton equivalent

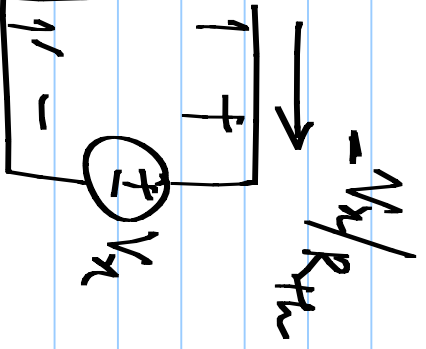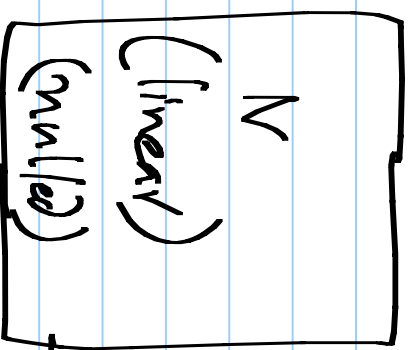


$\frac{V_x}{R_{th}}$


Norton resistance

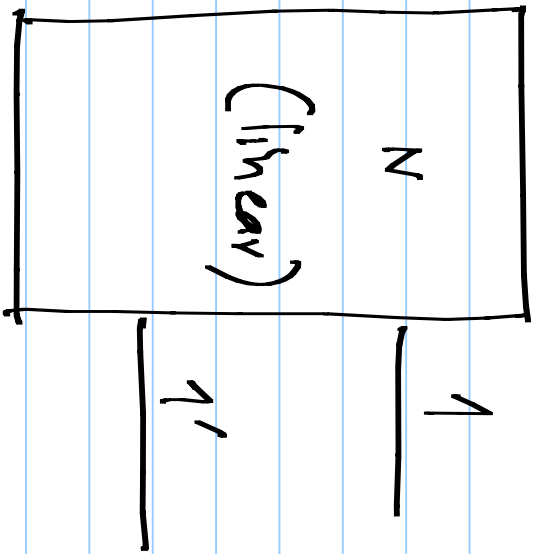


$\equiv$

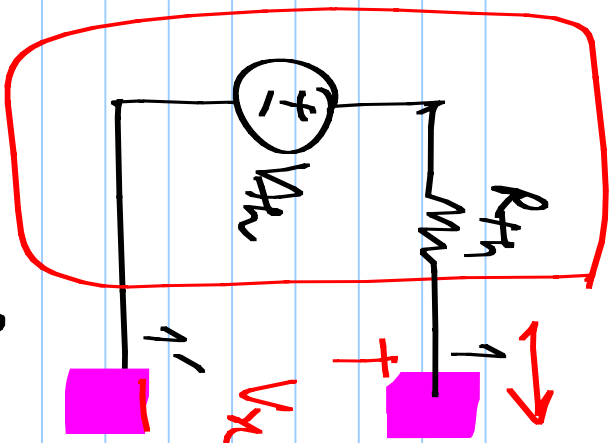

$\equiv$

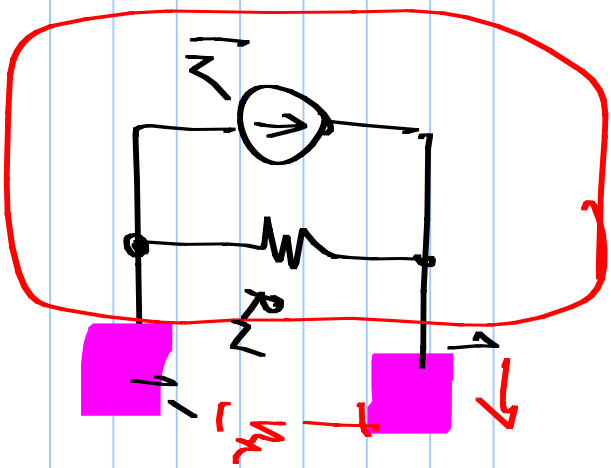


$$R_{th} = R_N$$



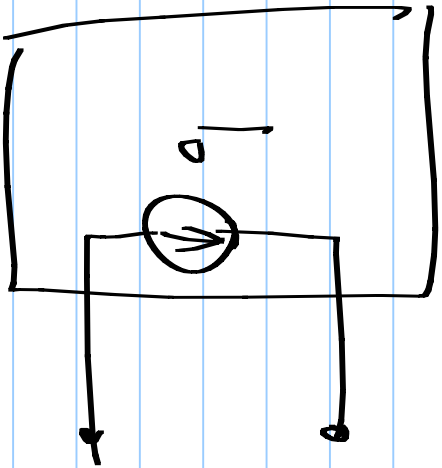



$$V_{th} = I_N \cdot R_{th}$$

# Short circuit:

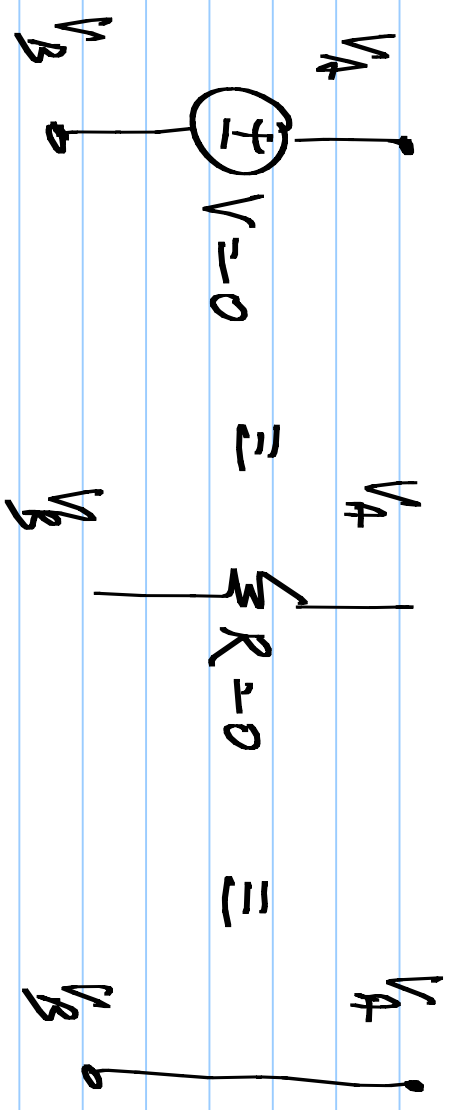

# Open circuit:

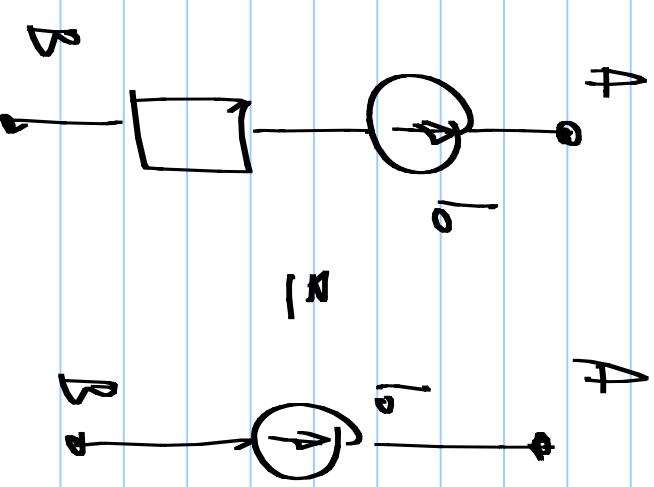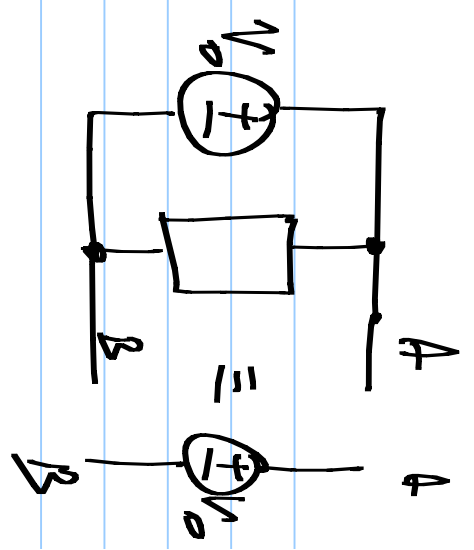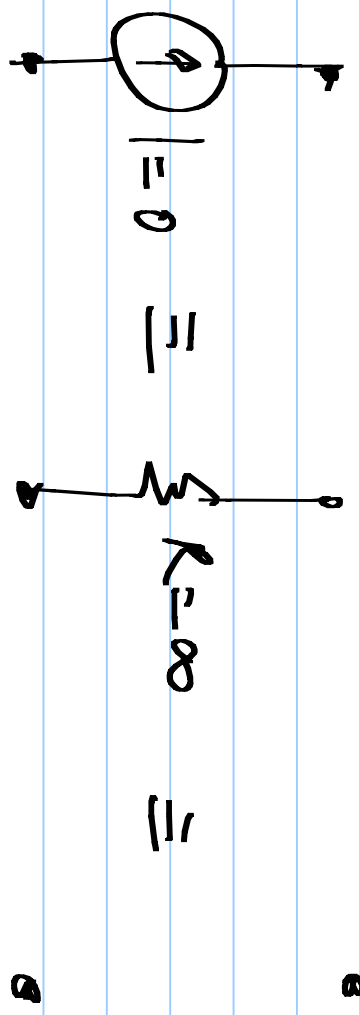


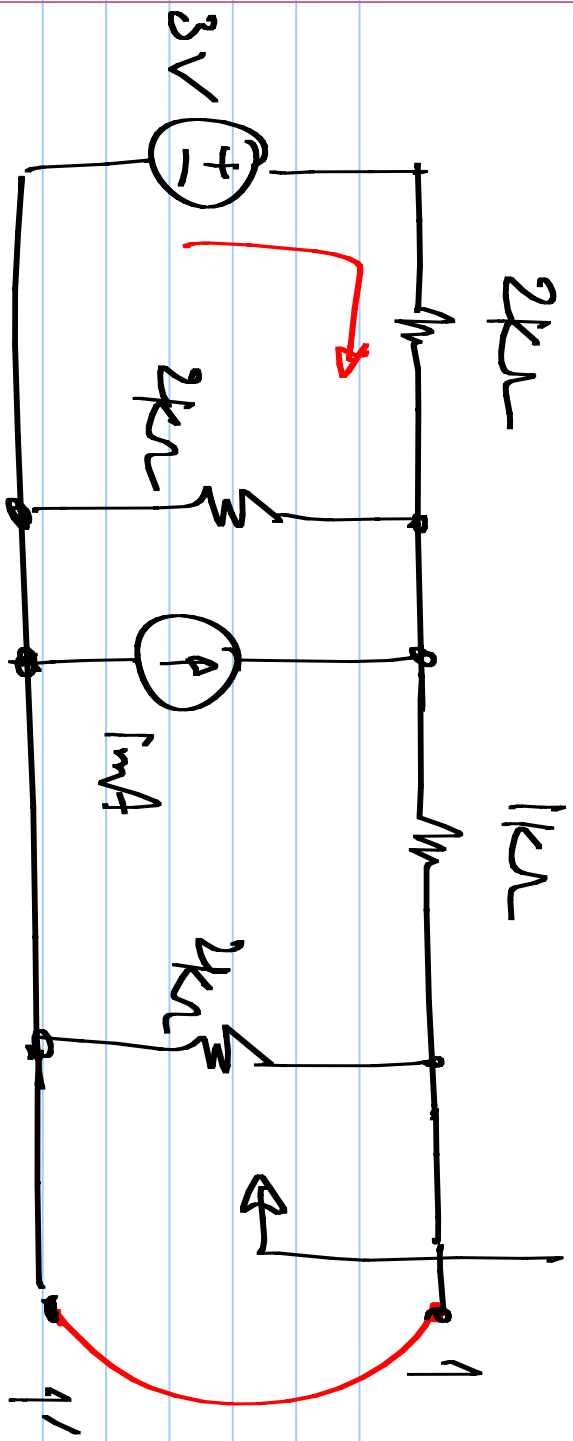

$$\frac{8}{3} k\Omega$$

$$8V \cdot \frac{k}{3}$$
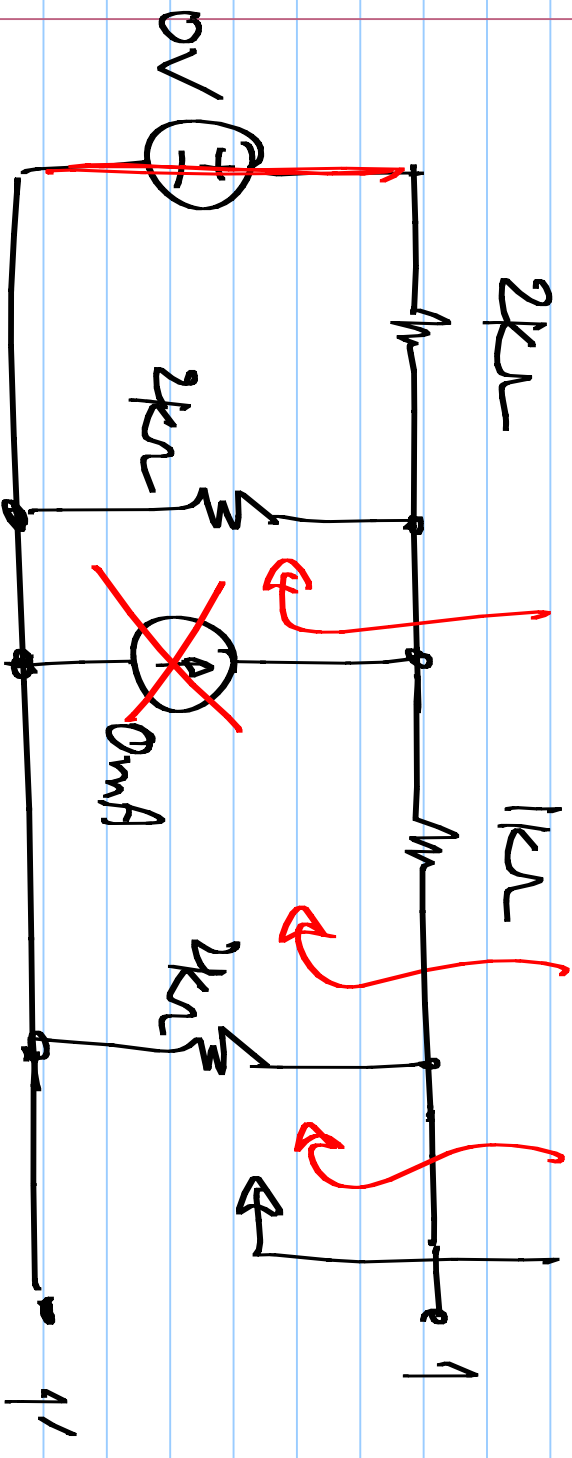
$$\frac{4 \cdot 8}{3} k\Omega = \frac{32}{3} k\Omega$$



$$P_N = P_{R_1} + P_{R_2}$$

$$P_N = \frac{5}{4} \text{mW} + \frac{5}{4} \text{mW} = \frac{5}{2} \text{mW}$$