
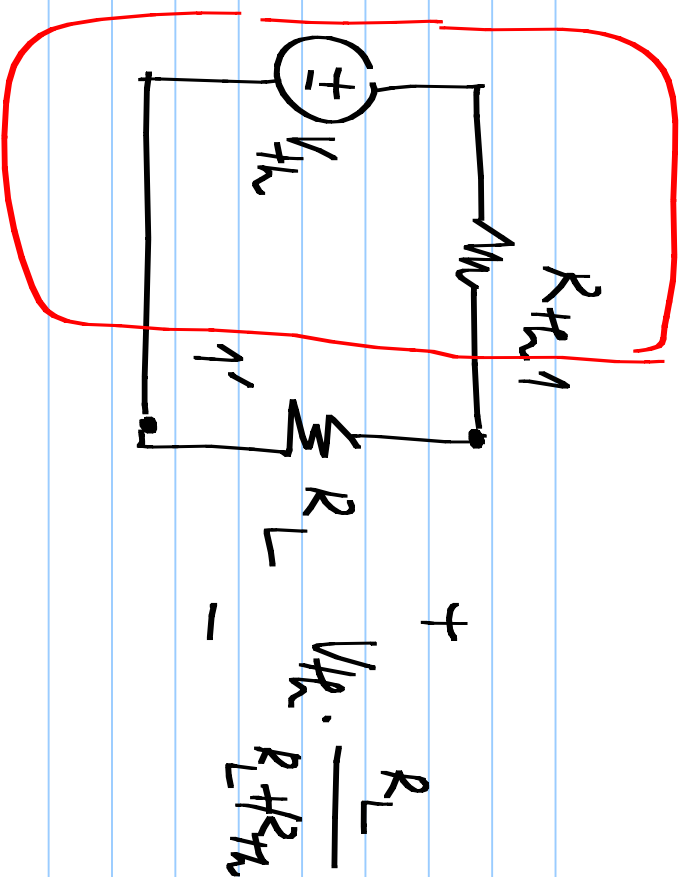


# Lecture # 11

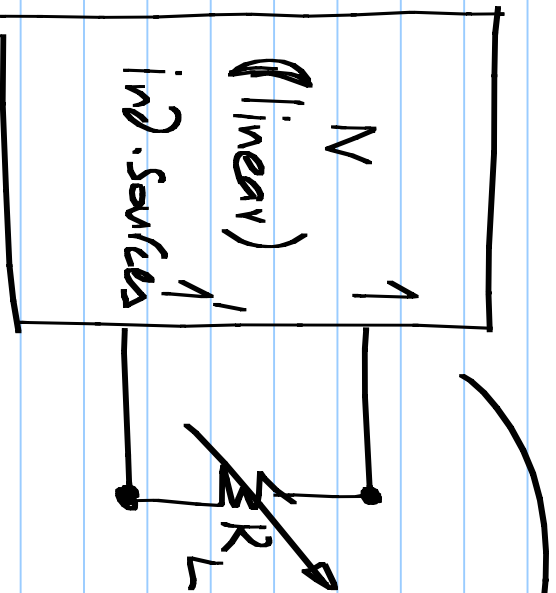


$$P = V_{th}^2 \cdot \frac{R_L^2}{(R_L + R_{th})^2} \cdot \frac{1}{R_L}$$

## Maximum power transfer theorem

$$P_L = V_{Th}^2 \cdot \frac{R_L^2}{(R_L + R_{Th})^2} \cdot \frac{1}{R_L} = \left( \frac{V_{Th}^2}{R_{Th}} \right) \frac{R_L \cdot R_{Th}}{(R_L + R_{Th})^2}$$

$$= \frac{V_{Th}^2}{R_{Th}} \left( \frac{\sqrt{R_L R_{Th}}}{R_L + R_{Th}} \right)^2 = \left( \frac{V_{Th}^2}{R_{Th}} \right) \cdot \frac{1}{\left( \sqrt{\frac{R_L}{R_{Th}}} + \sqrt{\frac{R_{Th}}{R_L}} \right)^2}$$

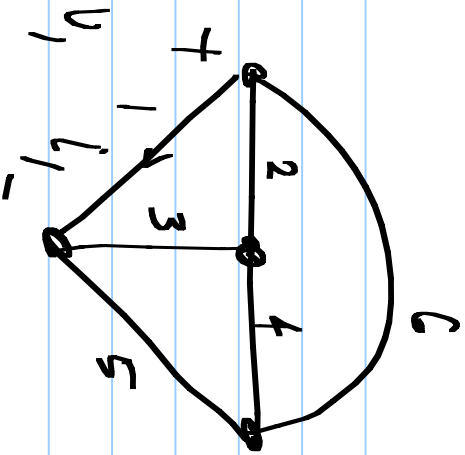
$$P_{L, \max} = \frac{V_{Th}^2}{4R_{Th}} \quad \text{when } R_L = R_{Th}$$



$v_k \cdot i_k$  : Power dissipated in  
the  $k^{\text{th}}$  branch


$$\sum_{\text{all branches}} v_k i_k = 0$$

all branches

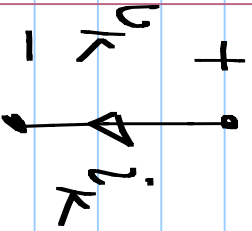

Network  $N$


$v_k, i_k$

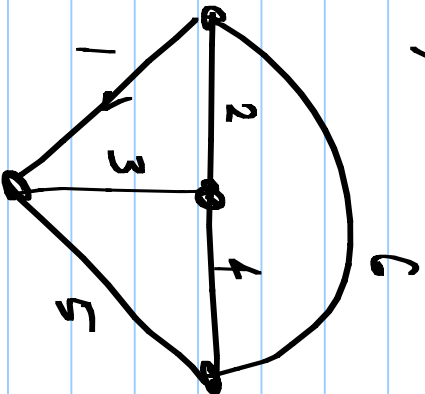


$$\sum_k v_k i_k = 0$$

Network  $\hat{N}$

$\hat{v}_k, \hat{i}_k$

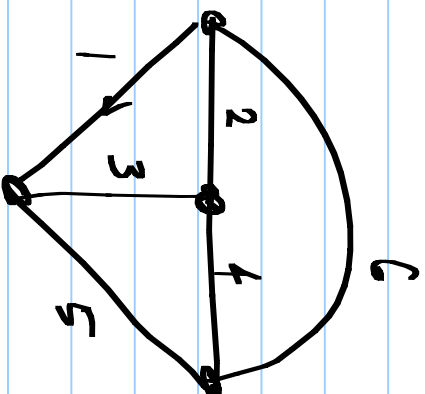


$$\sum_k \hat{v}_k \cdot \hat{i}_k = 0$$

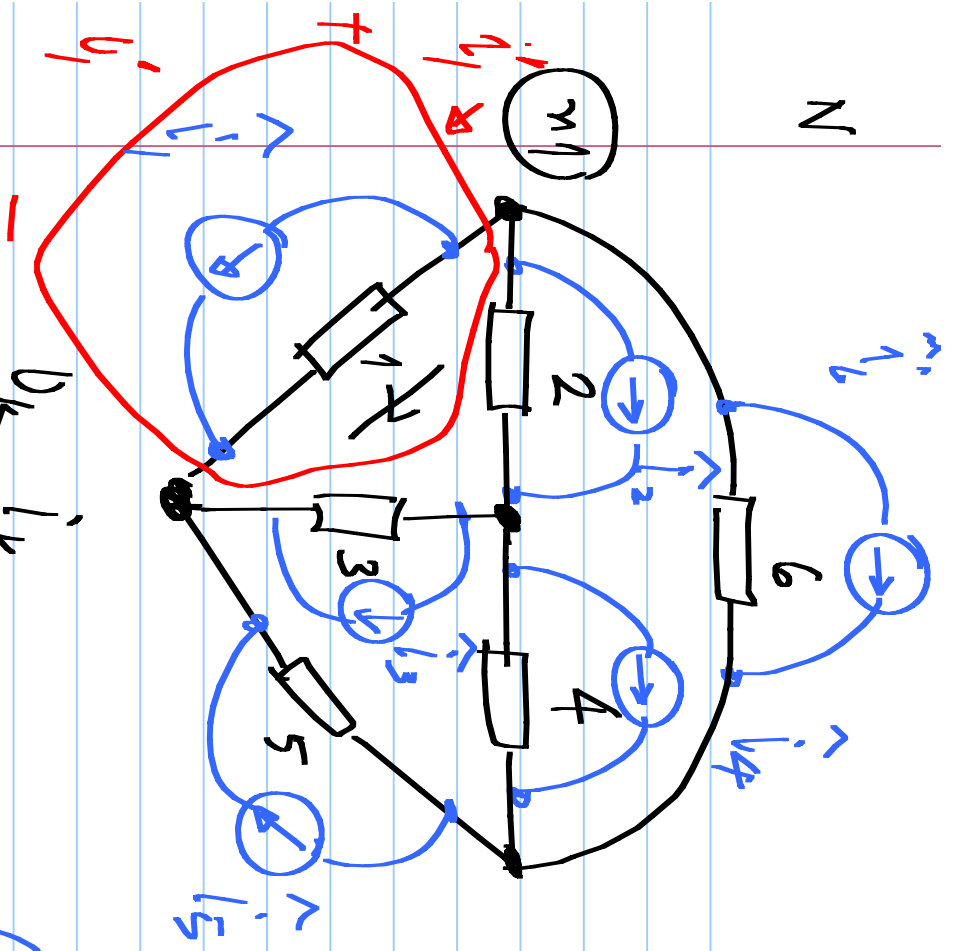

$$= - (i_1 + i_2 + i_6)$$

$$\textcircled{n_1} \quad i_1 + i_2 + i_6 = 0$$

$$i_k + i_k$$

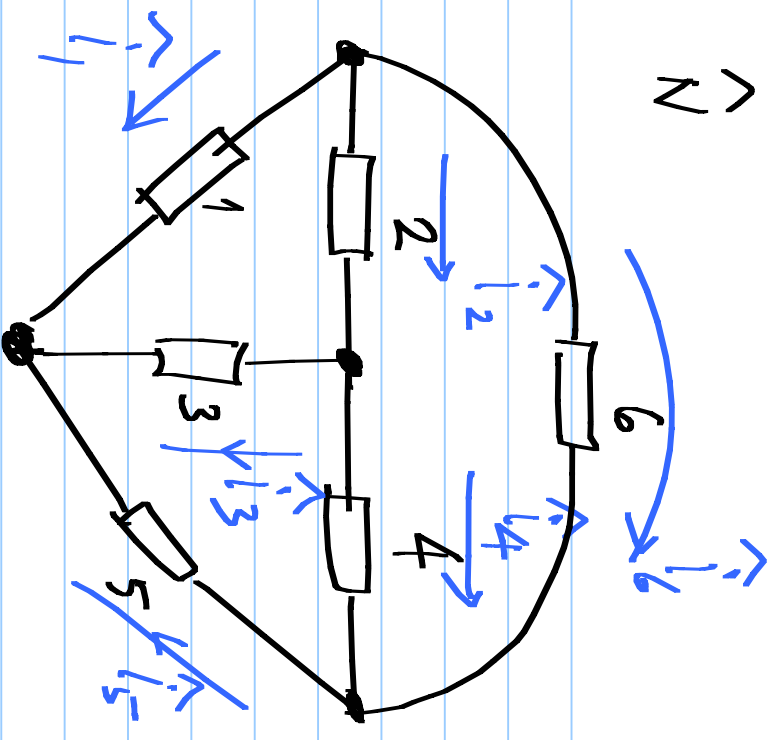

$$\sum_k \hat{v}_k \cdot \hat{l}_k = 0$$

$$\sum_k v_k' \cdot l_k' = 0$$

$$\sum_k v_k \cdot (l_k + \hat{l}_k) = 0$$

$$\sum_k v_k \cdot l_k + \sum_k v_k \cdot \hat{l}_k = 0$$

$$\sum_k v_k \cdot l_k = 0$$

$$\sum_k v_k \cdot \hat{l}_k = 0$$


$$\sum_k v_k(t_1) i_k(t_2) = 0$$

$$\sum_k v_k(t_1) \cdot \hat{i}_k(t_2) = 0$$

---

Tellegen's theorem

---

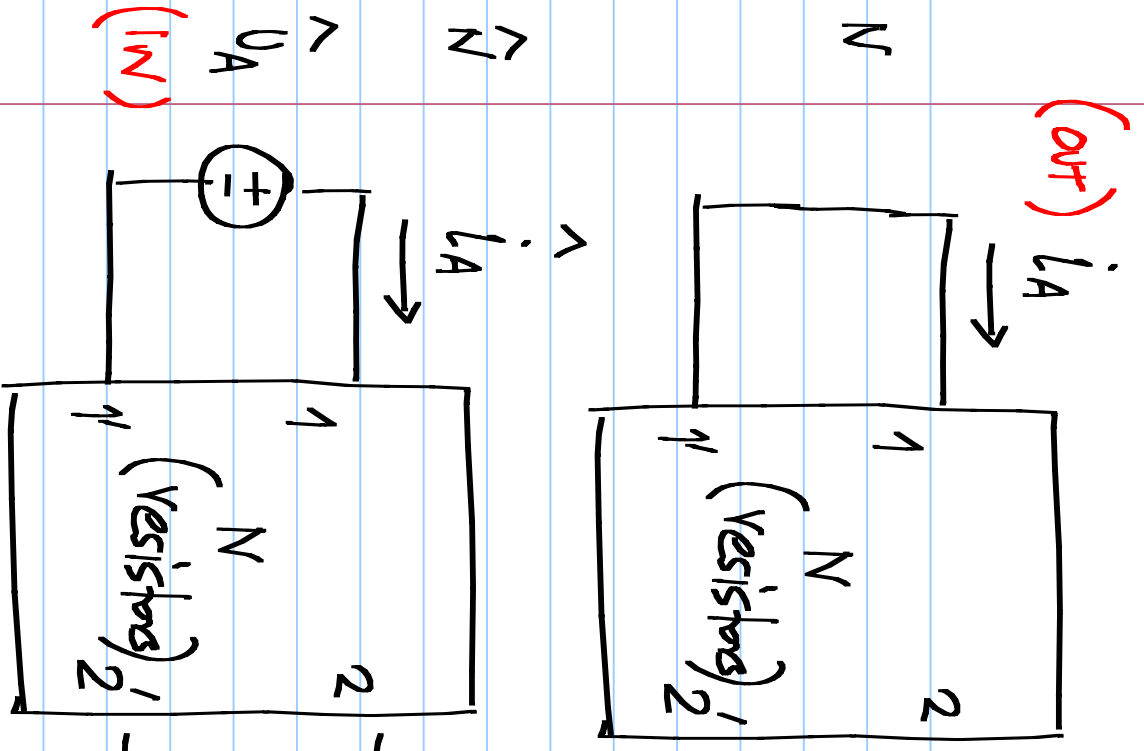

$$D: N; i: \hat{N}$$

$$U_B (-\hat{i}_B) + \sum_k U_k \cdot \hat{i}_k = 0$$

$$U_k = \hat{i}_k \cdot R_k \quad D: N; i: N$$

$$\hat{U}_k = \hat{i}_k \cdot R_{kN} \quad U_A (-i_A) + \sum_k U_k \cdot \hat{i}_k = 0$$



$$U_B(-i\hat{I}_B) + \sum_k U_k \hat{I}_k = 0$$

$$U_B(-i\hat{I}_B) + \sum_k R_k \hat{I}_k = 0$$

$$\hat{U}_A(-i\hat{I}_A) + \sum_k \hat{U}_k \hat{I}_k = 0$$


$$\hat{U}_A(-i\hat{I}_A) + \sum_k R_k \hat{I}_k = 0$$

[R]

[R]


$$V_B (-\hat{I}_B) = \hat{V}_A (-I_A)$$
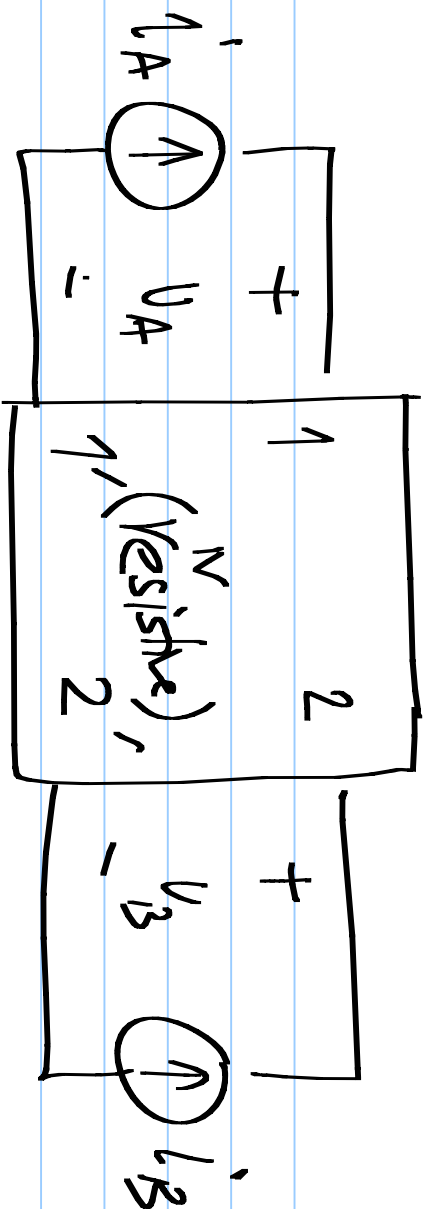
$$\frac{I_A}{V_B} = \frac{\hat{I}_B}{\hat{V}_A}$$




$$\frac{V_A}{i'_B} \Big|_{i'_A=0} \quad \&$$

$$\frac{V_B}{i'_A} \Big|_{i'_B=0}$$

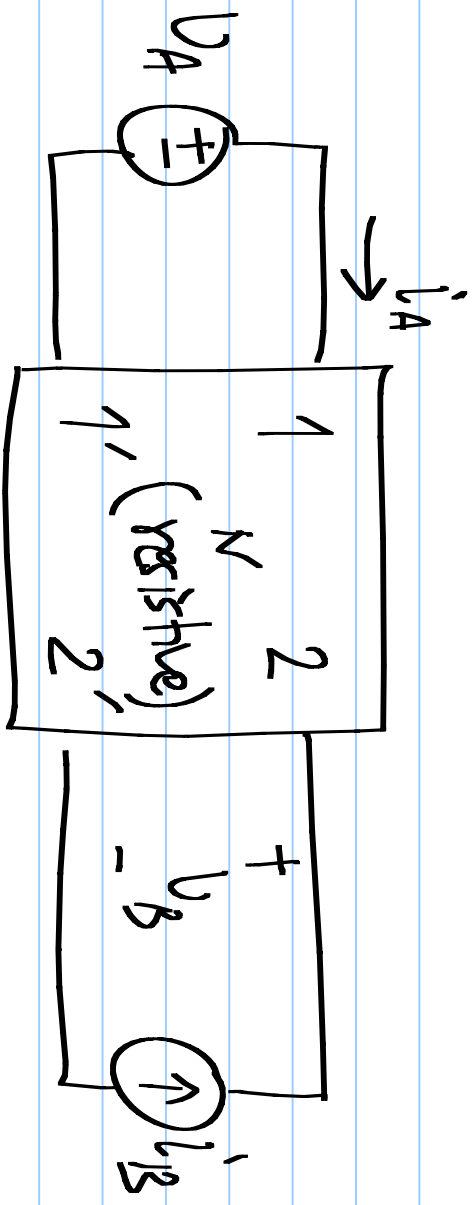


$$\frac{i'_A}{i'_B} \Big|_{V_A=0} \quad \&$$

$$\frac{V_B}{V_A} \Big|_{i'_B=0}$$

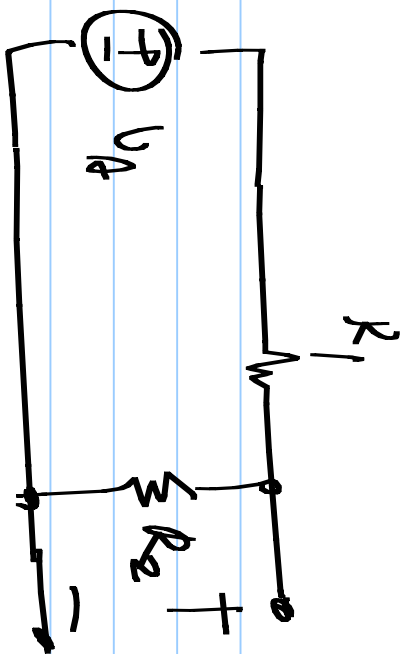

$$U_A = \frac{R_2}{R_1 + R_2}$$

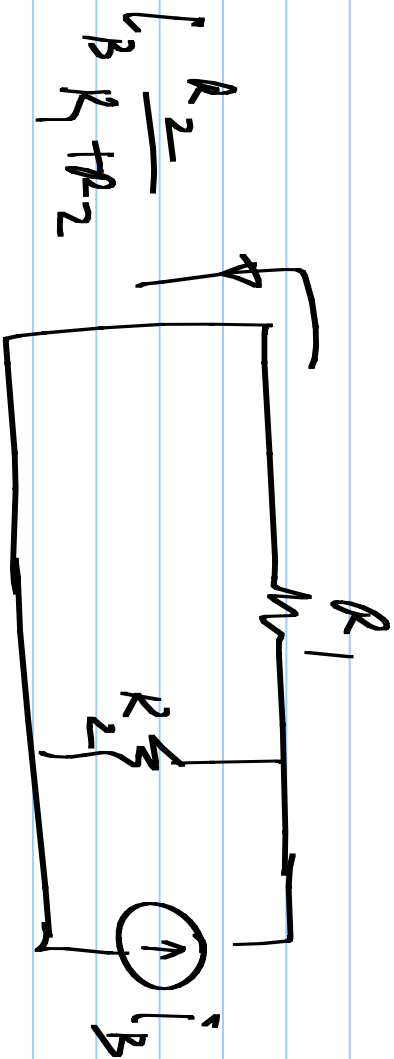

$$I_B = \frac{R_2}{R_1 + R_2}$$