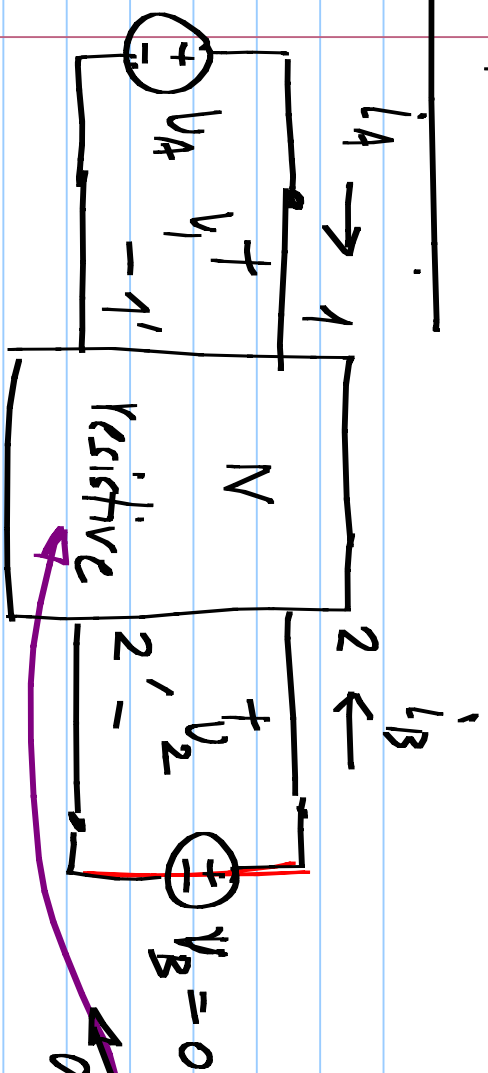



# Lecture 12

By Tellegen's theorem



$$V_A(-\hat{i}_A) + \sum_k V_k \hat{i}_k = 0$$

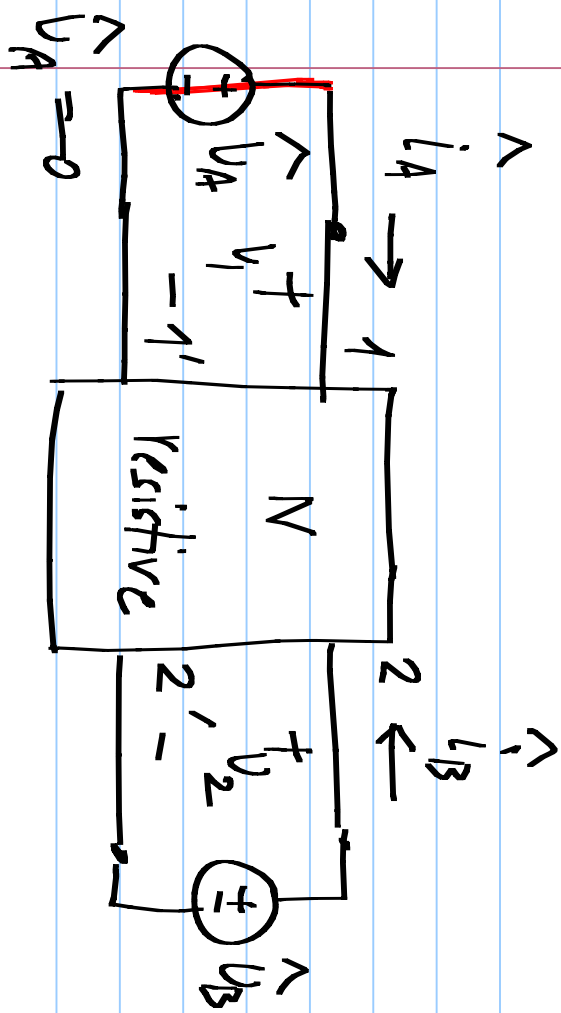$\underbrace{\sum_k R_k \cdot \hat{i}_k \cdot \hat{i}_k}_{\text{branches in } N}$



$$\hat{V}_B(-\hat{i}_B) + \sum_k \hat{V}_k \hat{i}_k = 0$$


$$V_A(-\hat{i}_A)$$

$$= \hat{V}_B(-\hat{i}_B)$$

$$\sum_k R_k \cdot \hat{i}_k \cdot \hat{i}_k$$

"Reciprocal" network
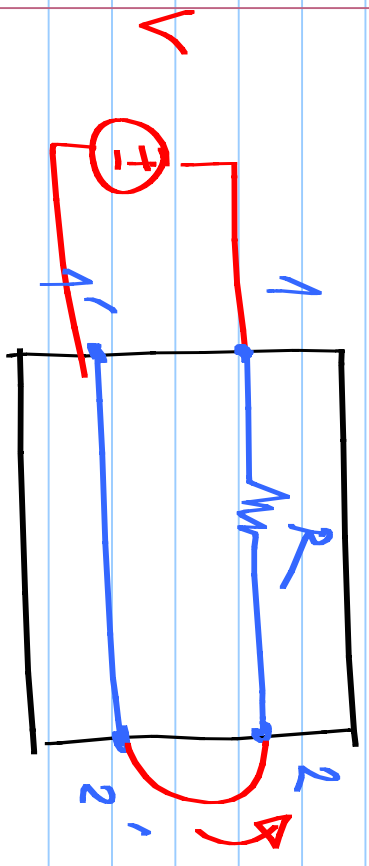
$$\frac{i_B}{U_A} = \frac{\hat{i}_A}{\hat{U}_B}$$





$$\sum V_k \hat{i}_k$$

Capacitor :  $V_k \cdot \hat{i}_k$

$$C_k \cdot V_k \cdot \hat{i}_k$$

$$\sum V_k \hat{i}_k$$

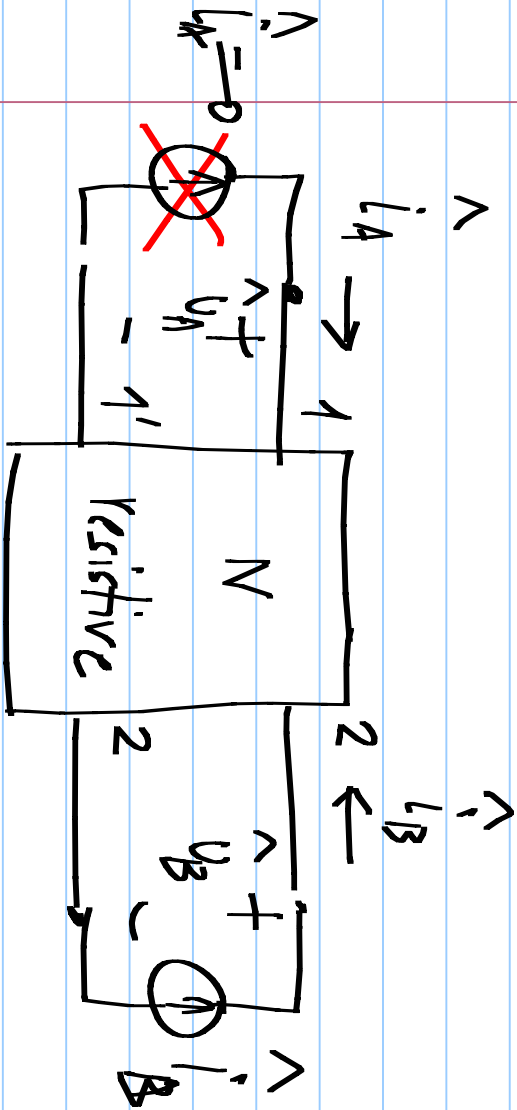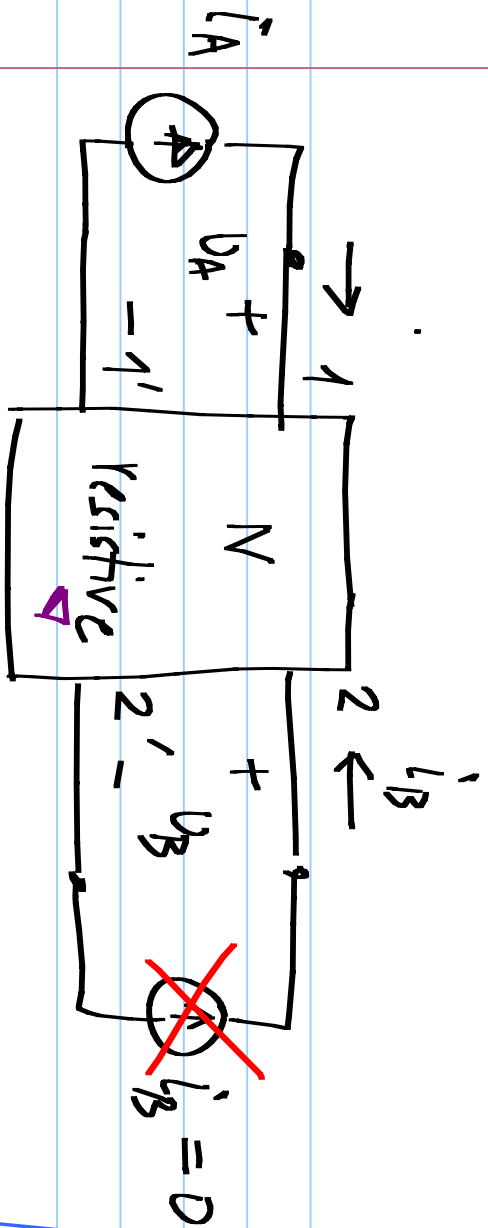Capacitor :  $C_k \cdot V_k \cdot \hat{i}_k$





$$i_A (-\hat{U}_A) + \sum_k i_k \cdot \hat{U}_k = 0$$


$$= \sum_k R_k i_k$$

$$i_B (-U_B) + \sum_k i_k U_k = 0$$


$$\frac{U_B}{i_A} = \frac{U_A}{i_B}$$

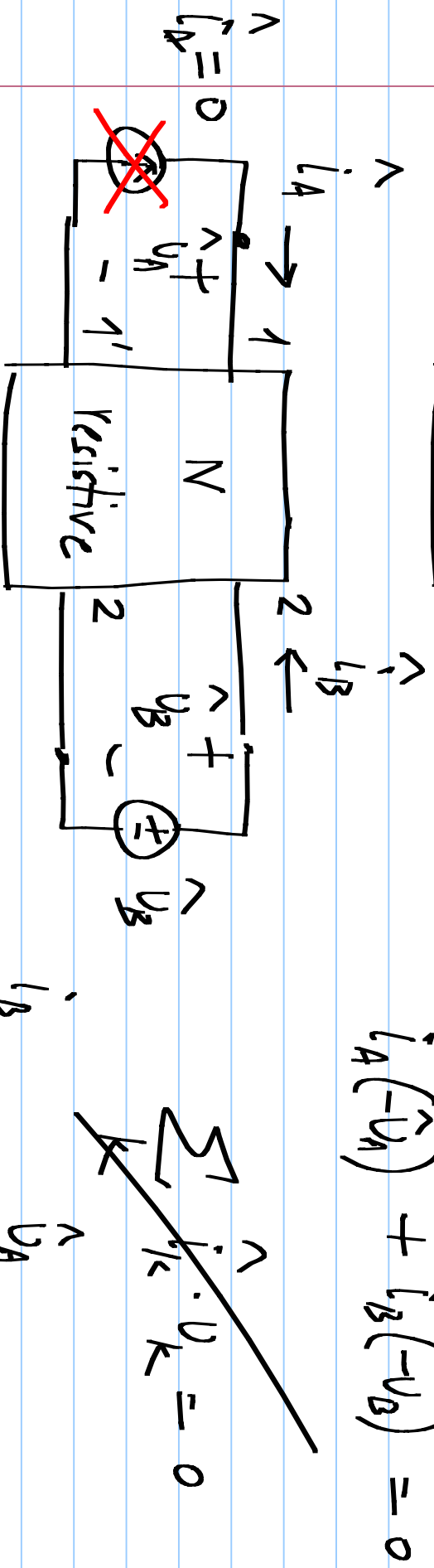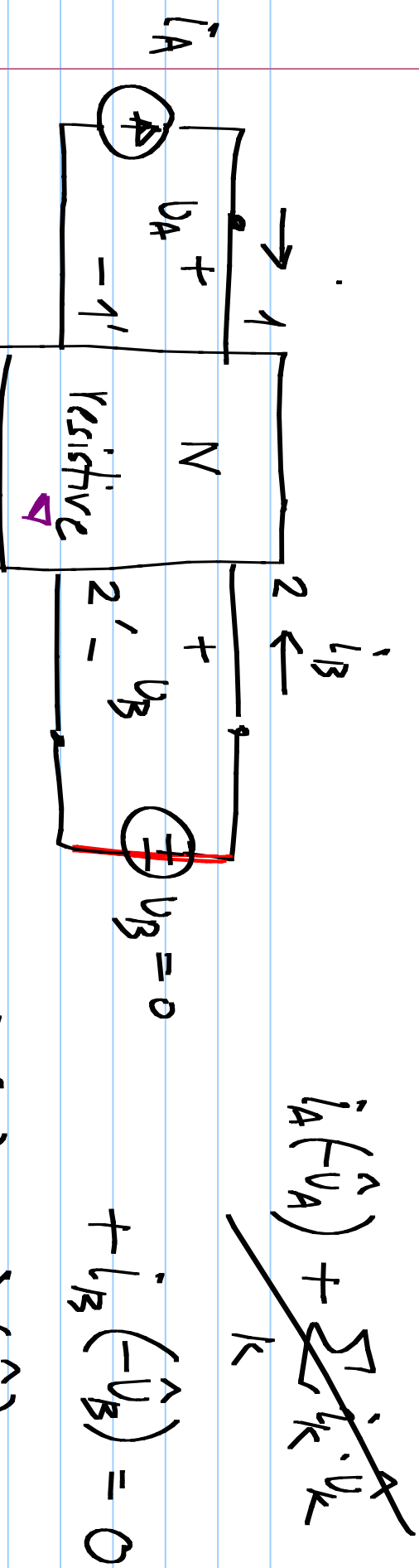


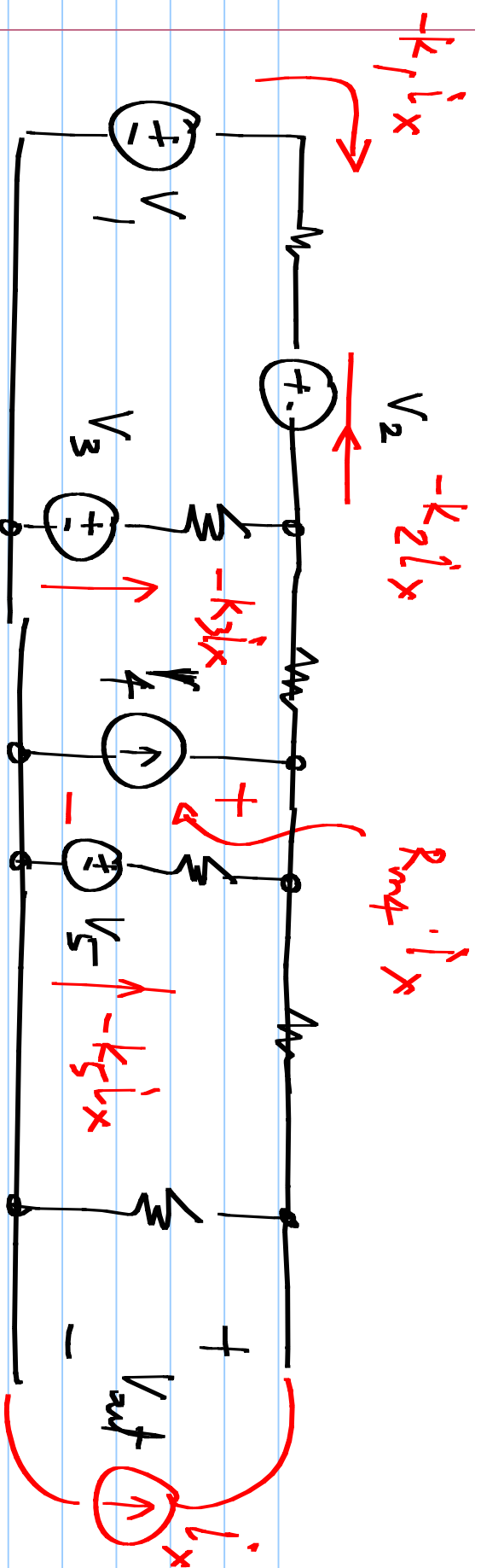~~$\sum_k \hat{i}_k \cdot U_k = 0$~~   
 $\frac{i_B}{i_A} = -\frac{U_A}{U_B}$



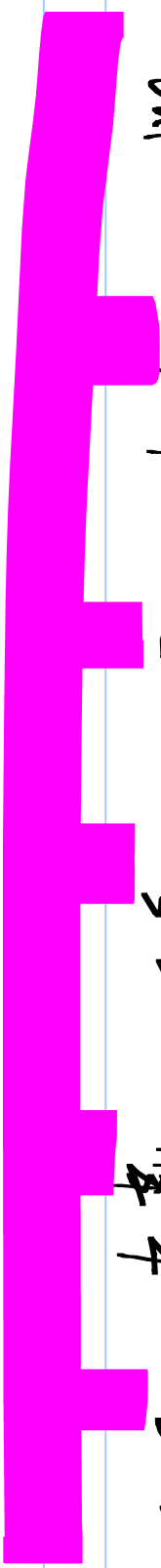
$$V_{out} = k_1 V_1 + k_2 V_2 + k_3 V_3 + R_{m4} i_x + k_4 V_4 + k_5 V_5$$





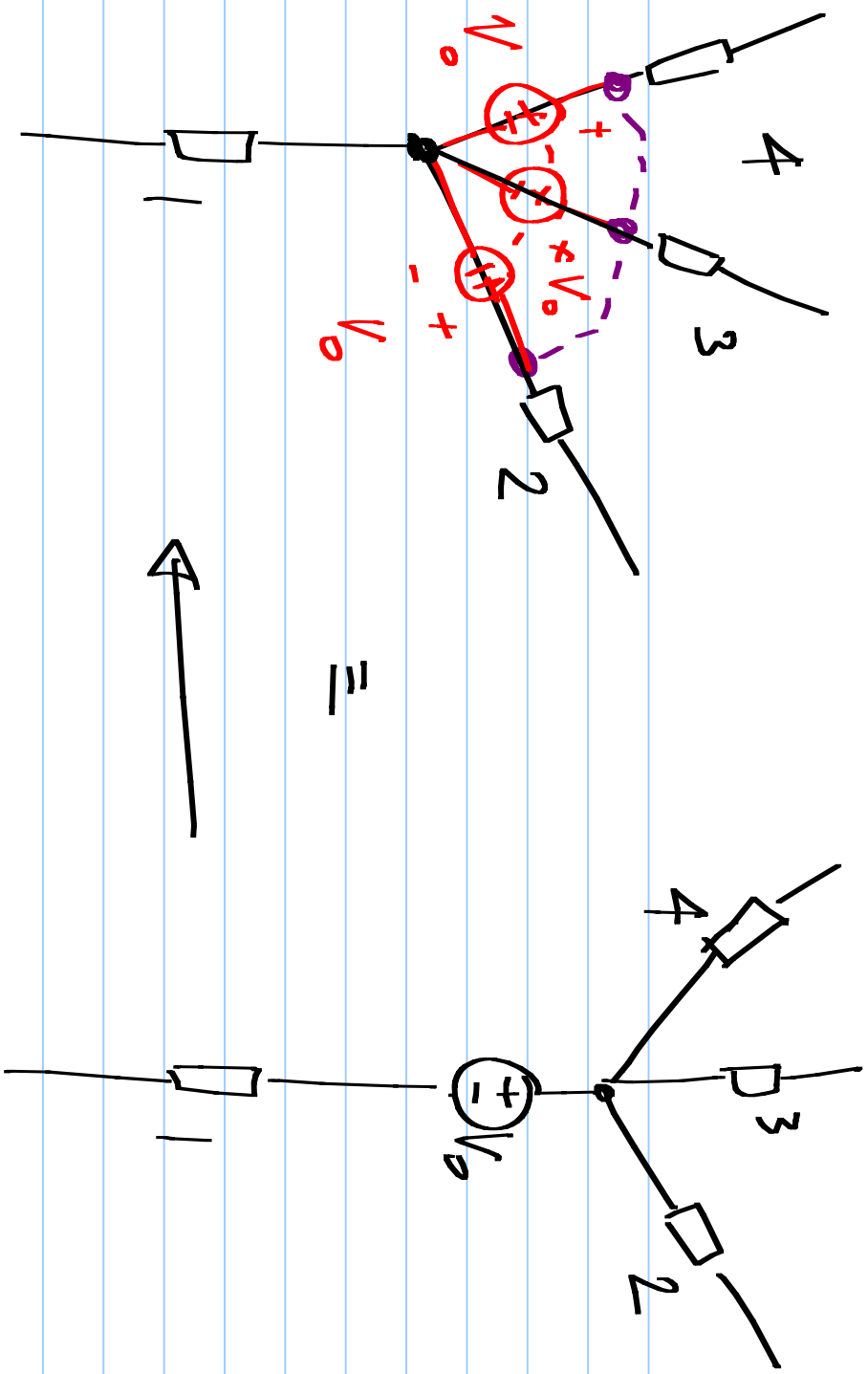

node with many  
branches.

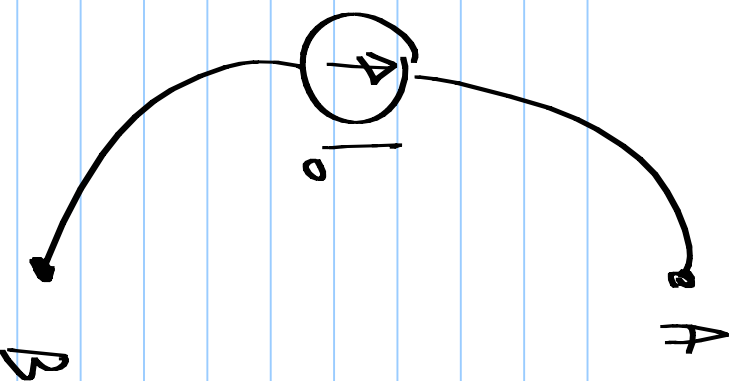

≡

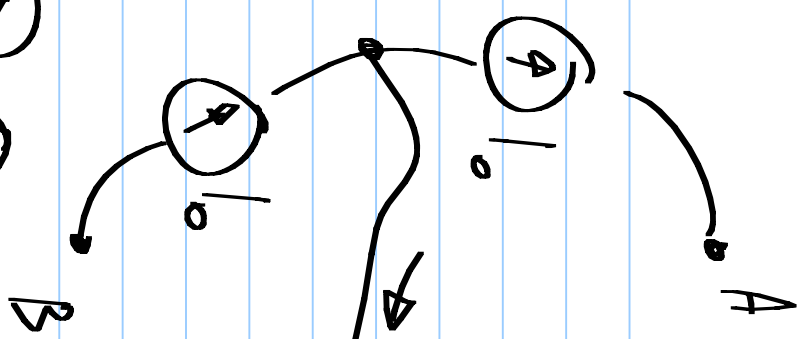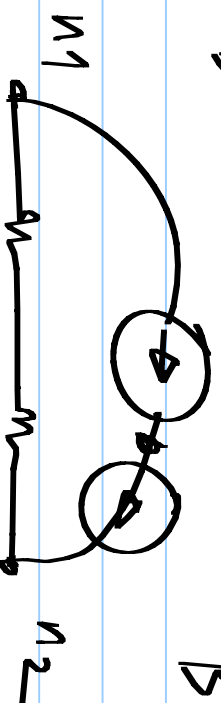

Zero current,

can connect to any other

node