


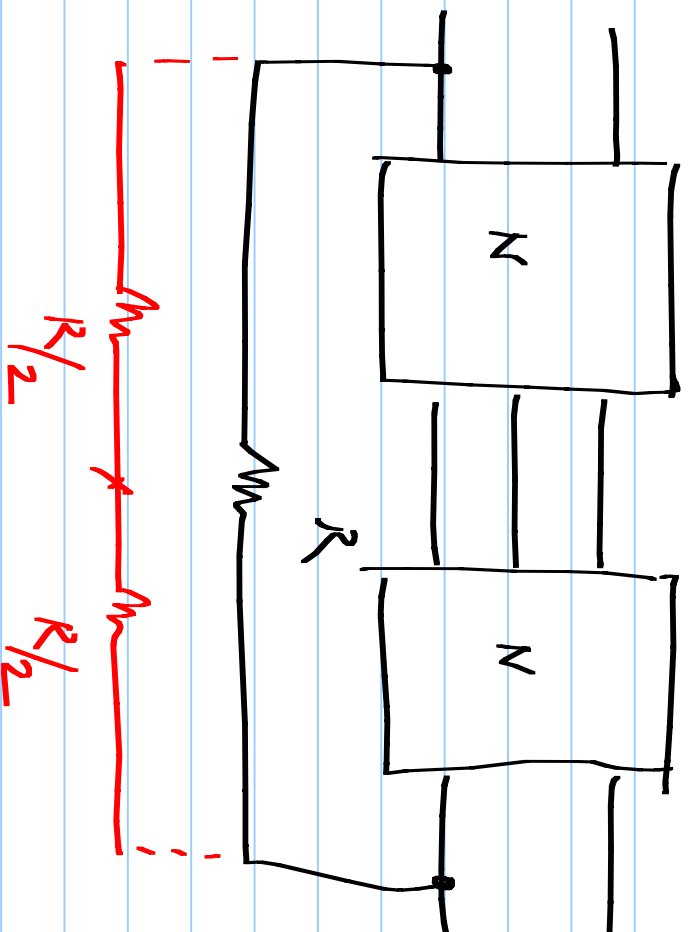
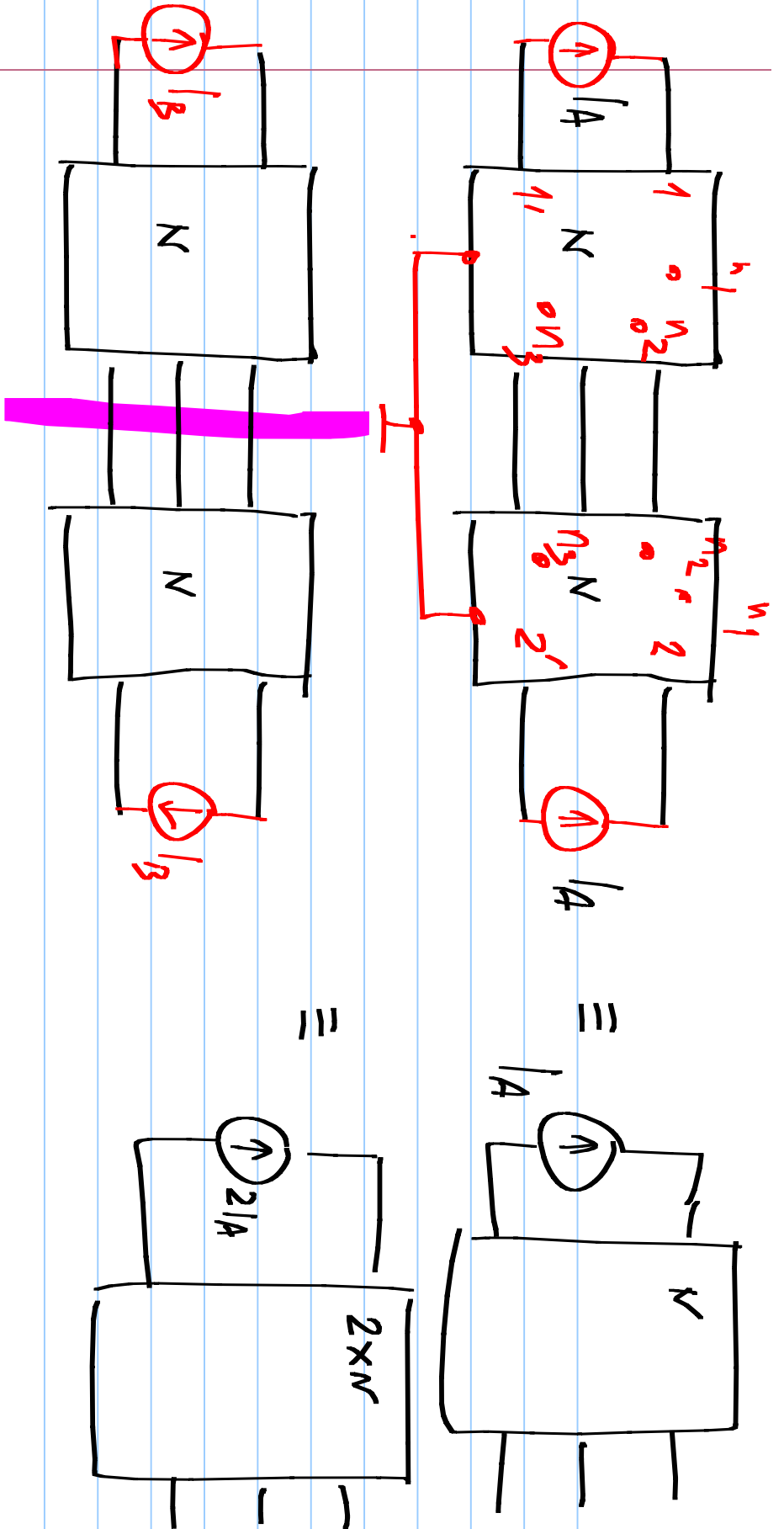


# Lecture 13


## Symmetric circuits

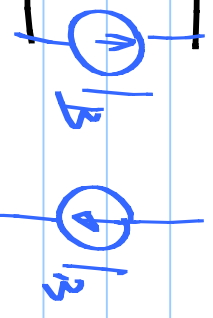

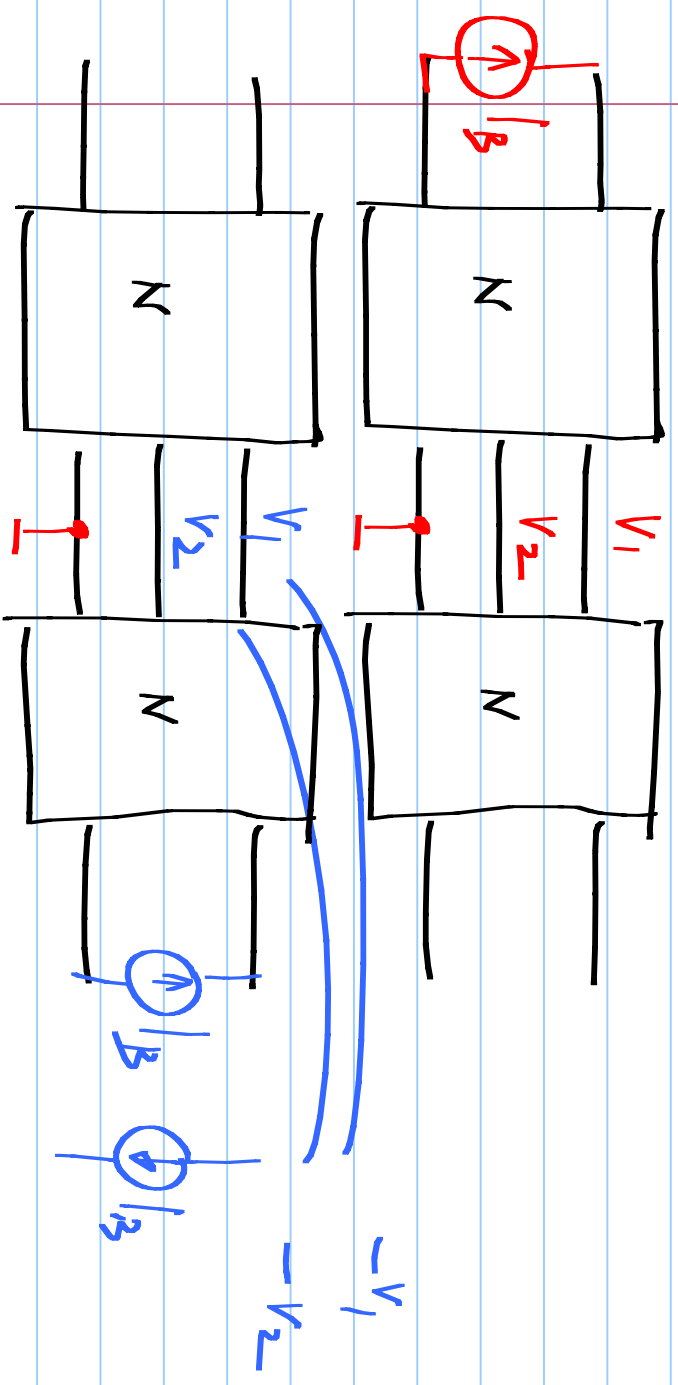

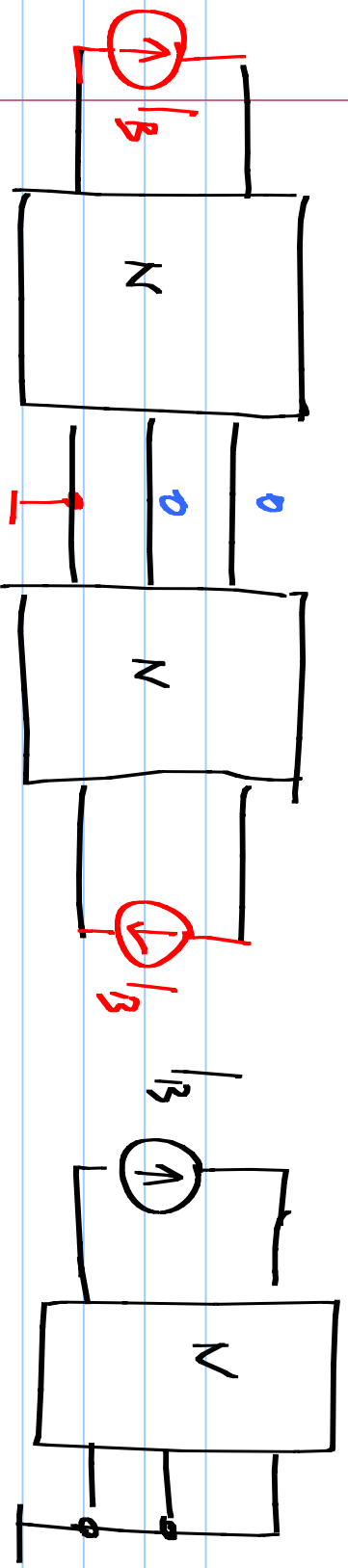

$-V_1$   
 $-V_2$

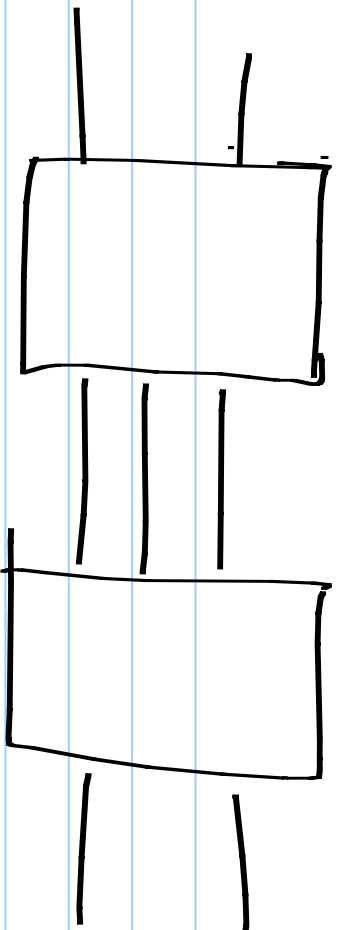

$(2A, 1A)$   
 $(4A, 2A)$

$\{1, 1\}$   
 $\{0\}$

$\{0\}$   
 $\{1, 1\}$

linearly  
 combine

$\{1A\}$


$\{1B\}$

Even mode  
Common mode  
Odd mode  
 Differential

$\{1A\}$

$\{1B\}$

linearly  
 combine



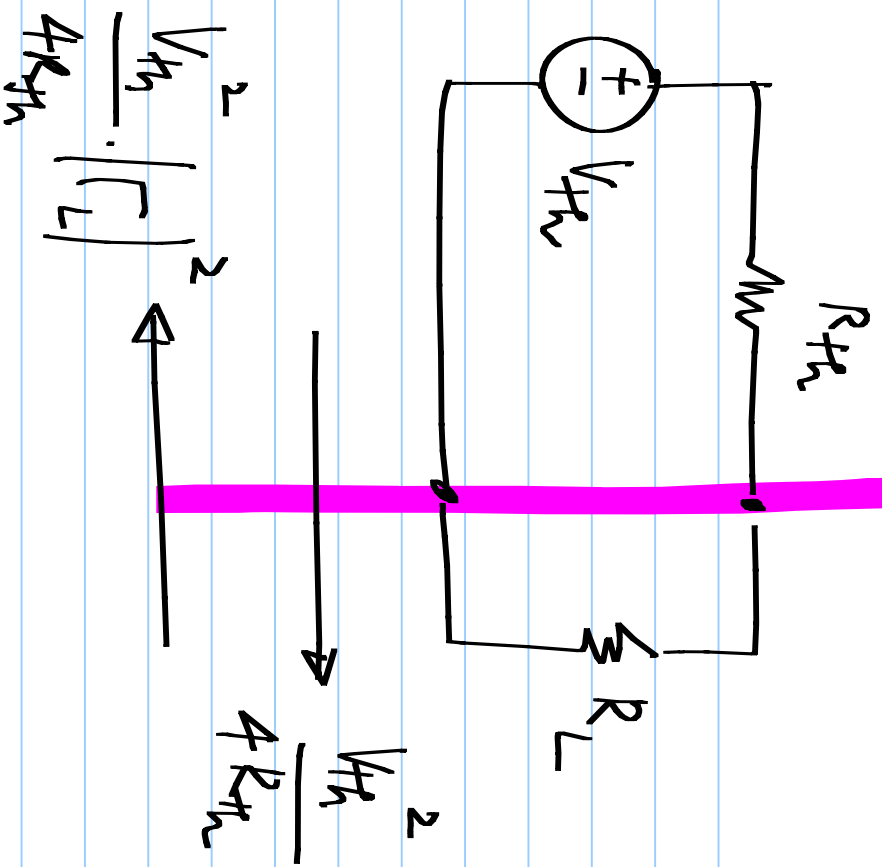


$$\left( \frac{V_{th}}{R_{th} + R_L} \right)^2 \cdot R_L$$


$$\frac{V_{th}^2}{4R_{th}} \left( 1 - |\Gamma|^2 \right)$$

$$|\Gamma| = \left| \frac{R_L - R_{th}}{R_L + R_{th}} \right|$$

Effect of change in component values

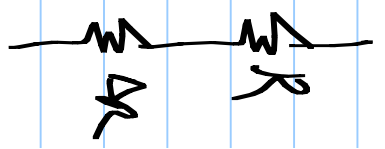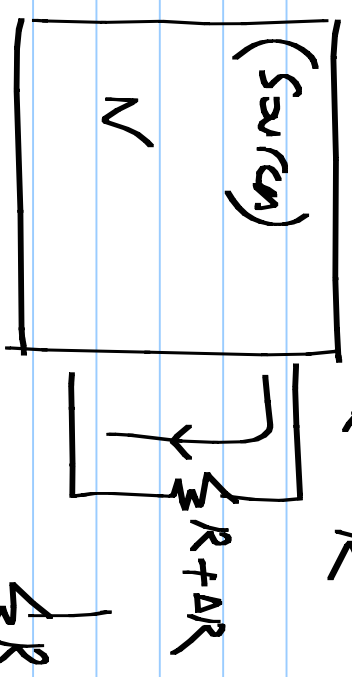
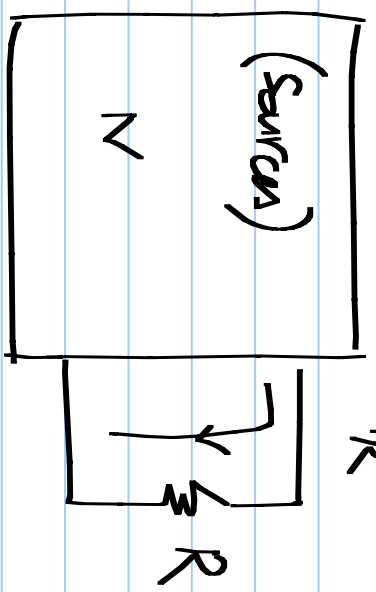


$$\approx \Delta R \cdot \frac{1}{R}$$

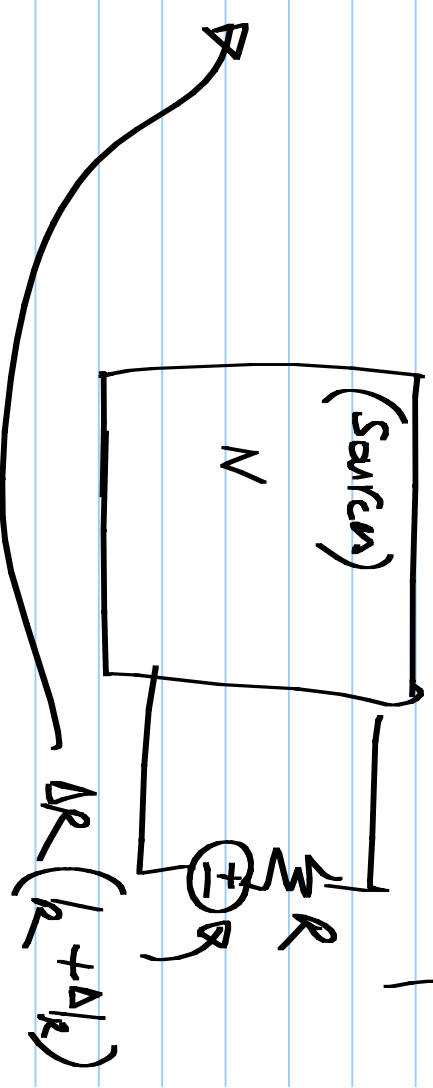

Changes due to the resistance change

---

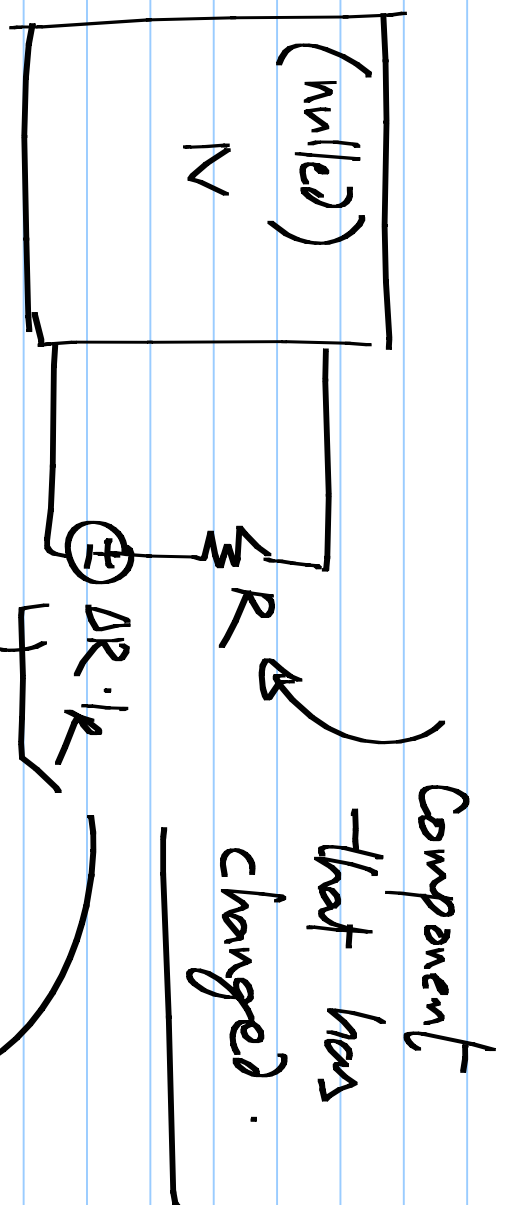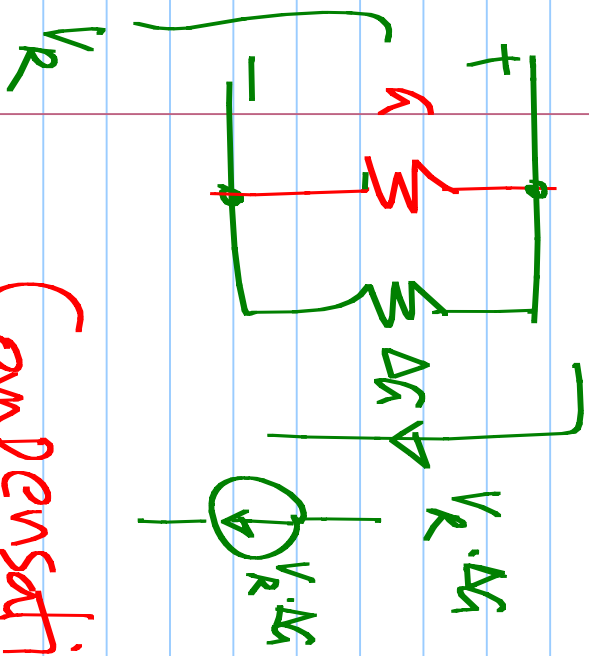


Compensation


$\Delta R = -\frac{\Delta R}{R} R$  theorem

$R \rightarrow R + \Delta R$   
change in  $R$

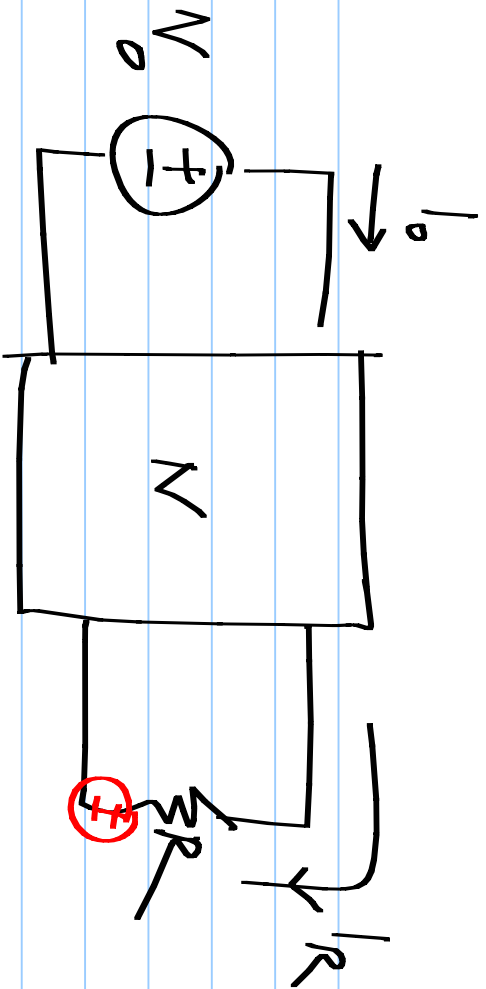~~$\frac{1}{R} = \frac{1}{R + \Delta R}$~~   
Original current -  $\left(1 - \frac{\Delta R}{R}\right)$


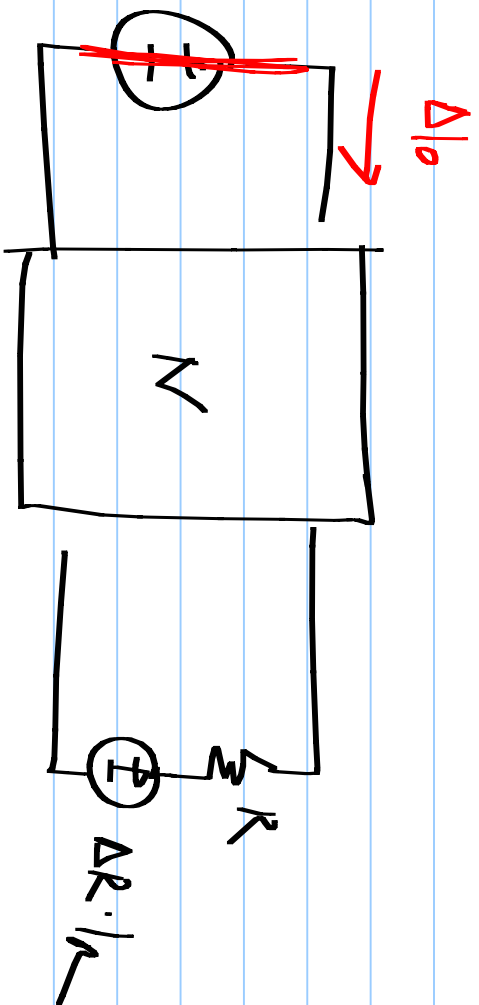
$$\frac{I_0}{V_0} = -\frac{A_0}{\Delta R \cdot I_R}$$





## Circuit - theorems:

- \* Pushing a voltage source through a node
- \* Splitting a current source
- \* Tellegen's theorem - Circuit graph
- \* Thevenin / Norton theorems
- \* Substitution theorem
- \* Reciprocity theorem
- \* Compensation theorem