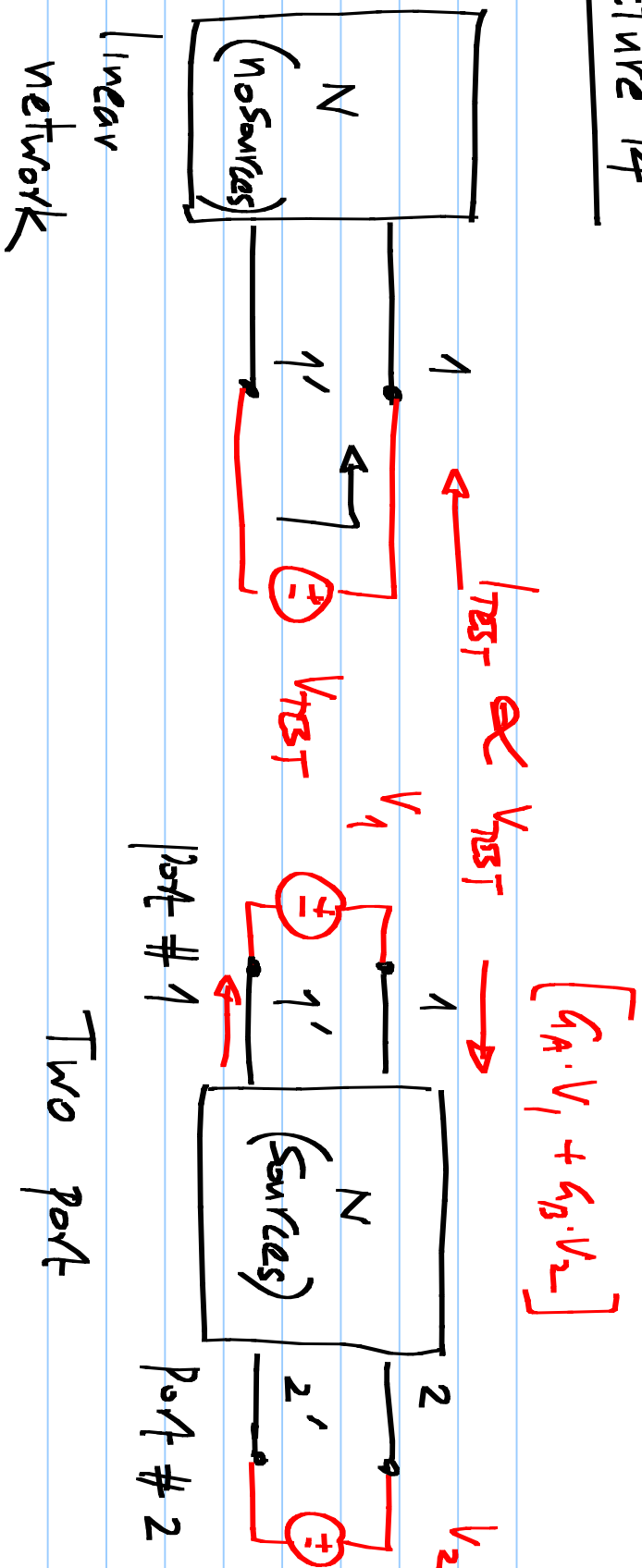



Lecture 14



1-port network


network

Two port:

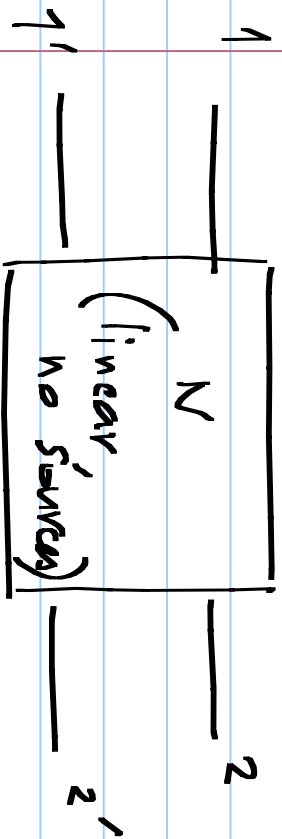

Two port Parameters

| | port #1 | port #2 | |
|--|---------|---------|-----|
| | V_1 | V_2 | Y |
| | I_1 | I_2 | Z |
| | I_1 | V_2 | H |
| | V_1 | I_2 | G |

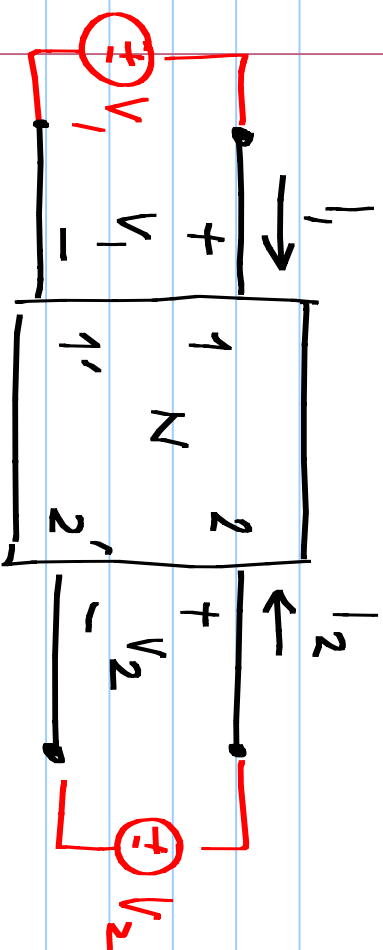

Y parameters: (Short circuit parameters)

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \quad ; \quad y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$I_1 = y_{11} \cdot V_1 + y_{12} \cdot V_2$$

$$y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} \quad ; \quad y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$


$$I_2 = y_{21} V_1 + y_{22} V_2$$

effect cause

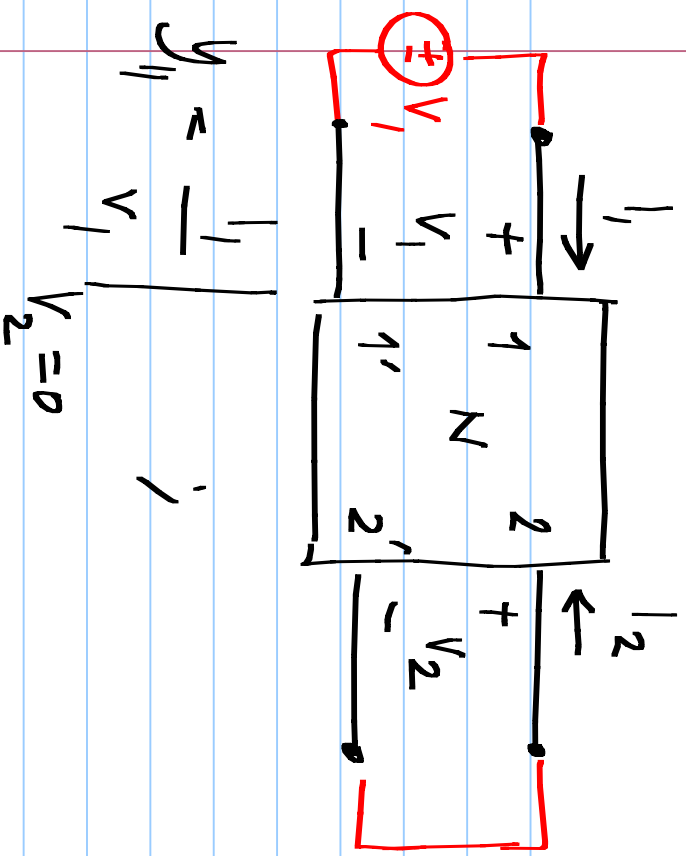

Port 2: terminated
 $V_2=0$ in a short circuit
 Measure I_1 & I_2 to
 obtain y_{11} & y_{21}

$$y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

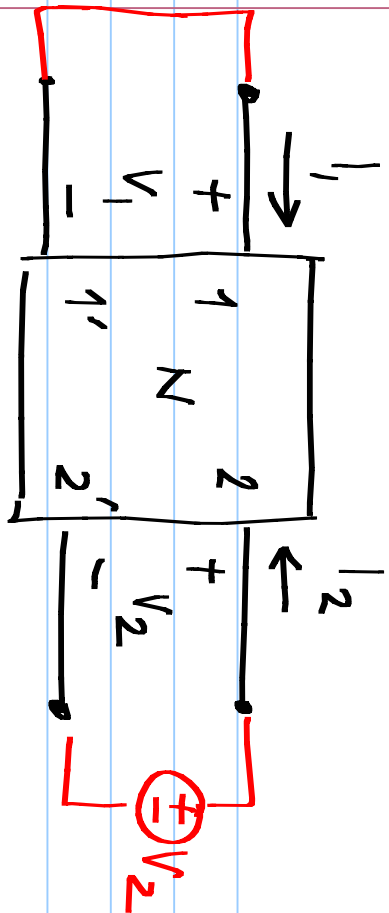


Port 1: terminated
in a short circuit

Measure I_1 & I_2 to


obtain y_{12} & y_{22}

$$y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$


$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

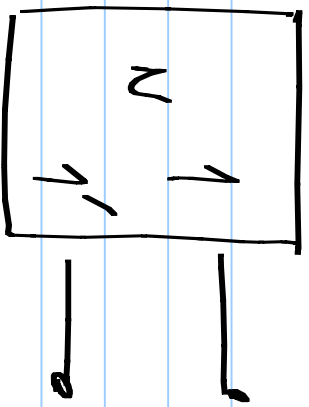


≡

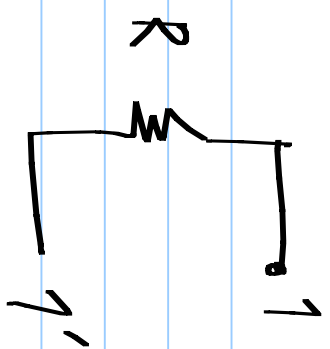


$$I_1 = y_{11}V_1 + y_{12}V_2$$

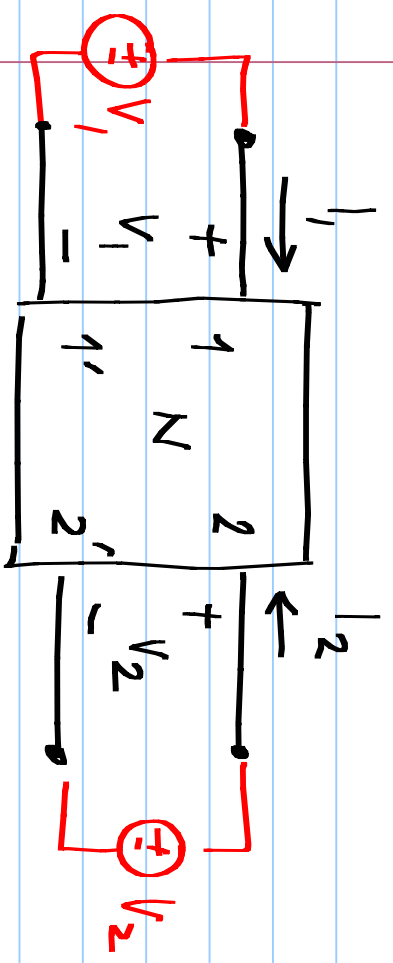

≡

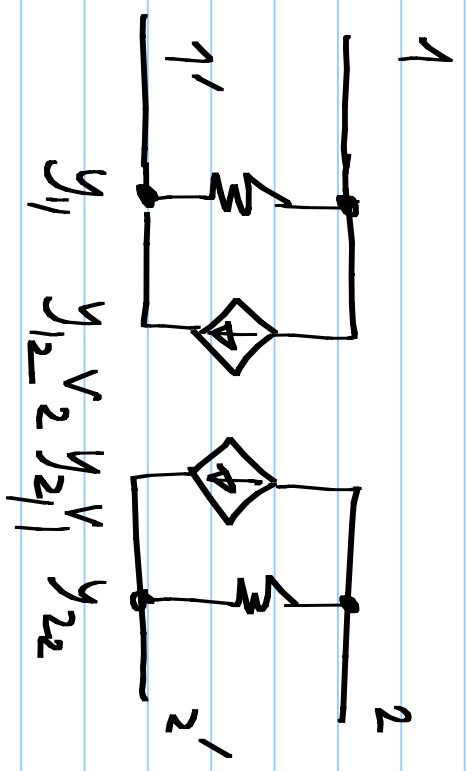


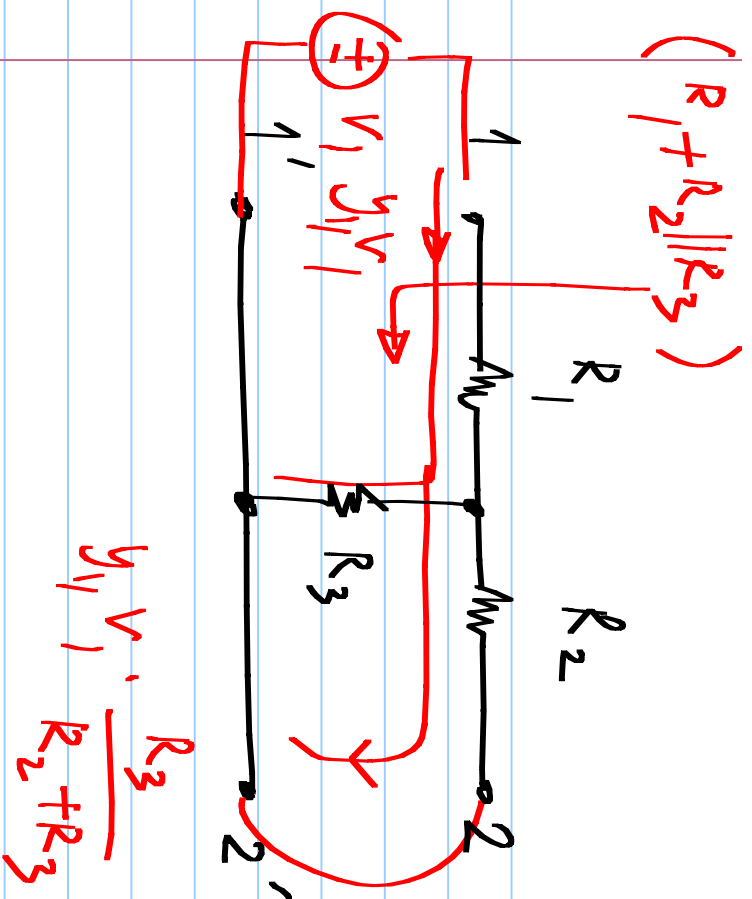

$$y_{11} = \frac{1}{R_1 + (R_2 || R_3)}$$

$$= \frac{R_2 + R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$
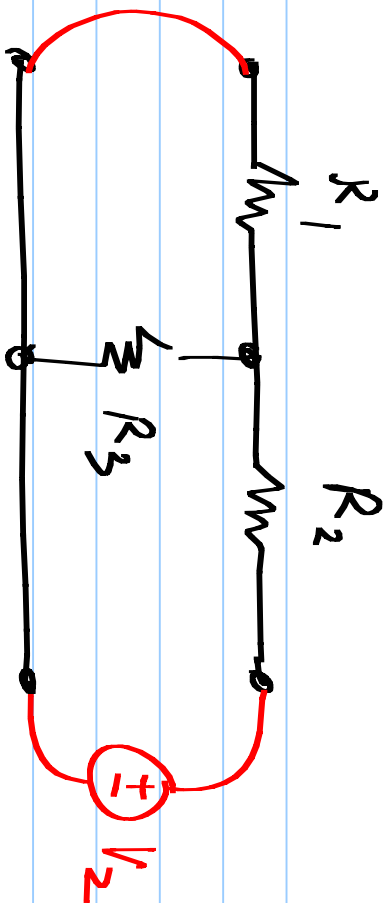
$$y_{21} = -y_{11} \cdot \frac{R_3}{R_2 + R_3} = \frac{-R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$




$$y_{22} = \frac{1}{R_2 + R_1 \parallel R_3}$$

$$= \frac{R_1 + R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$y_{12} = - \frac{R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$= y_{21}$$

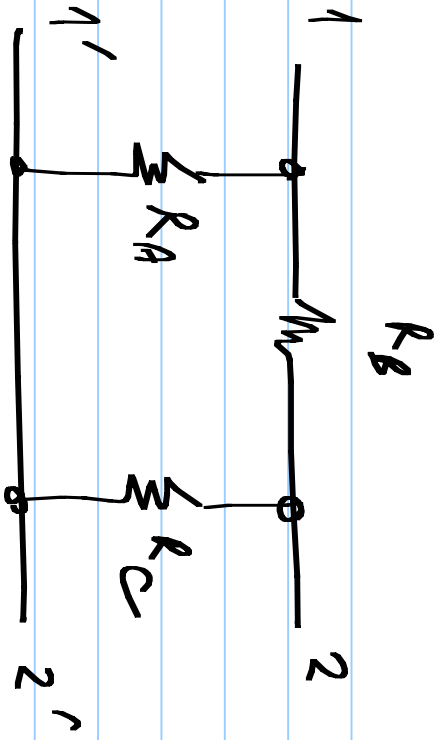


$$y_{11} = \frac{1}{R_A \parallel R_B} = \frac{R_A + R_B}{R_A R_B}$$

$$y_{12} = -\frac{1}{R_B}$$

$$y_{22} = \frac{1}{R_B}$$


$$y_{21} = \frac{R_C + R_B}{R_C R_B}$$

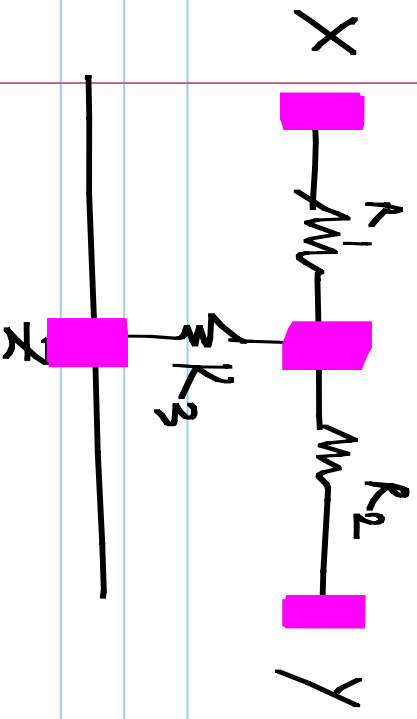

$$y_{11} = \frac{R_2 + R_3}{\sum_i R_i \cdot R_i}$$

$$y_{12} = y_{21} = \frac{-R_3}{\sum_i R_i \cdot R_i}$$
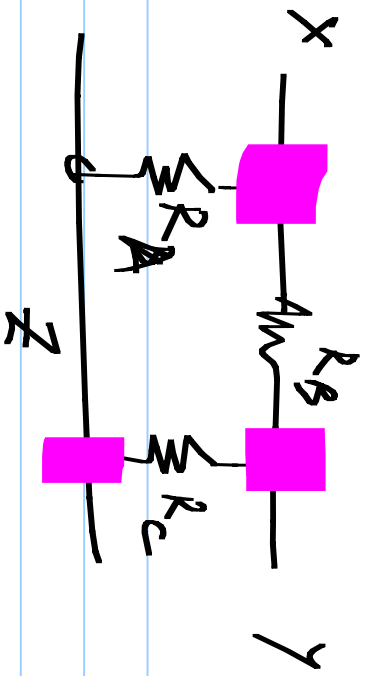
$$y_{22} = \frac{R_1 + R_3}{\sum_i R_i \cdot R_i}$$



$$y_{11} = \frac{R_A + R_B}{R_A R_B}$$

$$y_{12} = y_{21} = -\frac{1}{R_B}$$

$$y_{22} = \frac{R_B + R_C}{R_B R_C}$$


Δ Network

Y Network

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_C = \frac{\sum R_i \cdot R_j}{R_1}$$

$$R_A = \frac{\sum R_i \cdot R_j}{R_2}$$

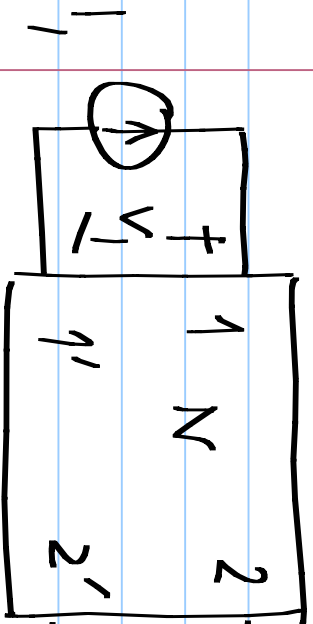

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Z parameters

open-circuit parameters


$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$


$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$
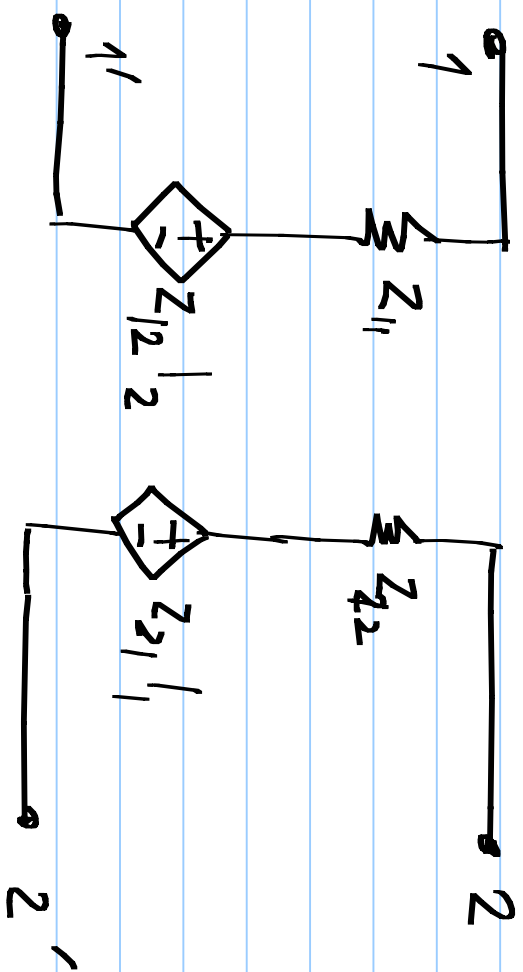
$$\underline{\underline{[Z] = [Y]^{-1}}}$$



VCVS

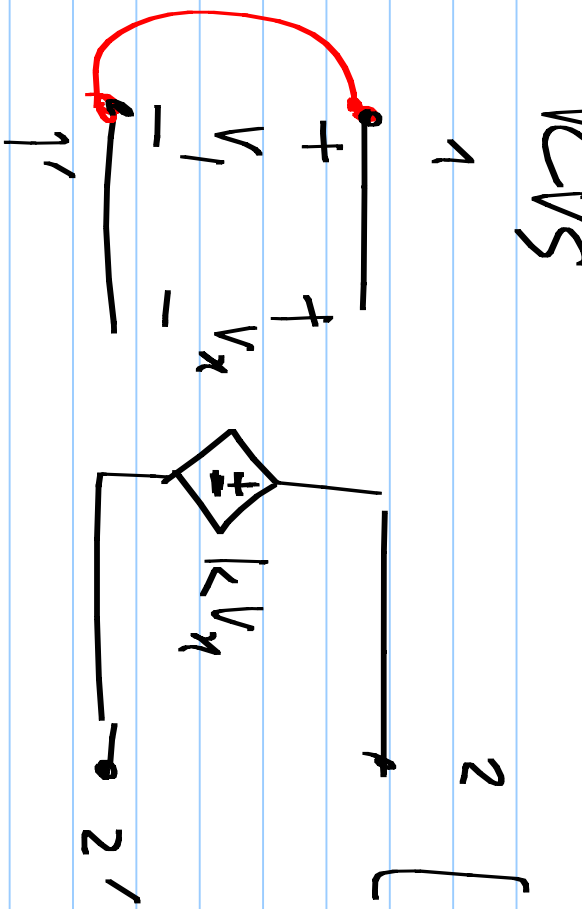

$$[Y] = \begin{bmatrix} 0 & 0 \\ \infty & \infty \end{bmatrix} X$$

$$[Z] = \begin{bmatrix} \infty \\ \infty \end{bmatrix} X$$