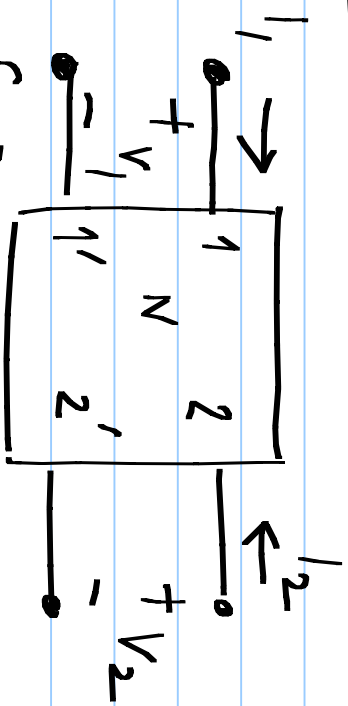


Lecture 15



hybrid parameters

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


Y parameters (conductance)

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


Z parameters (resistance)

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

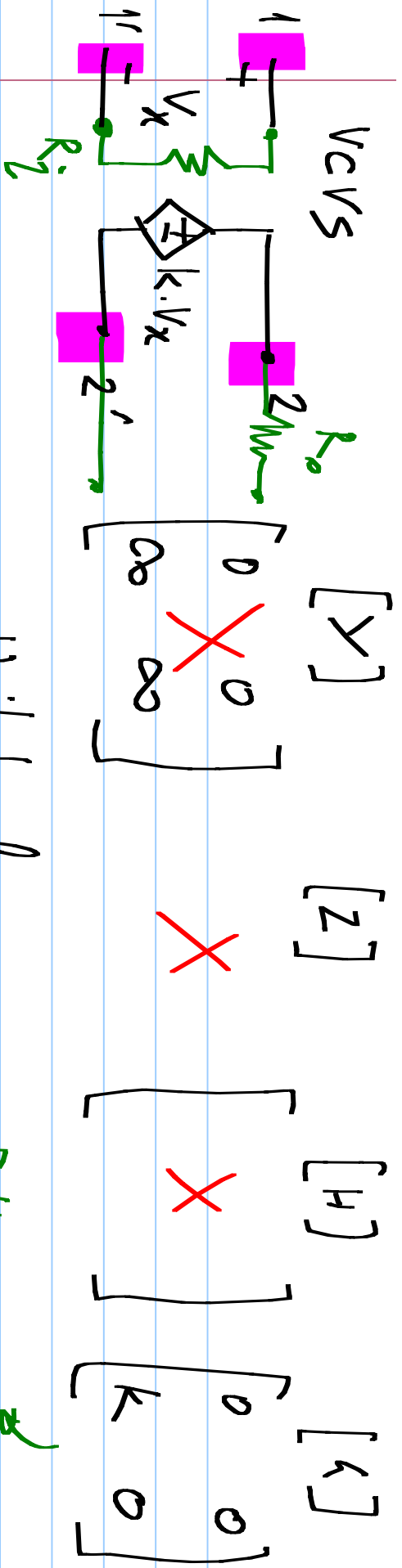
$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$




Unilateral:

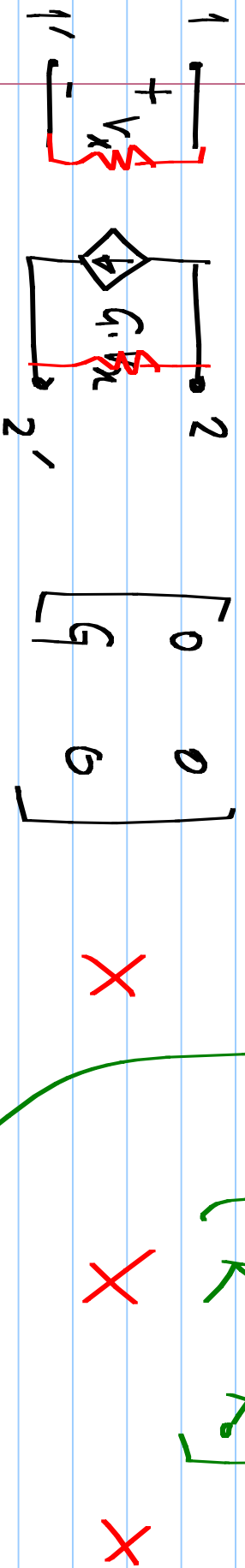

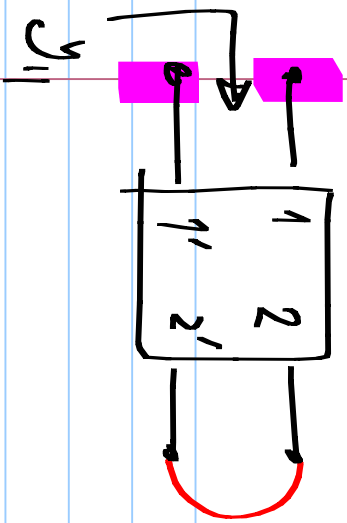
Only one of $\{h_{21}, h_{12}\}$ is non zero



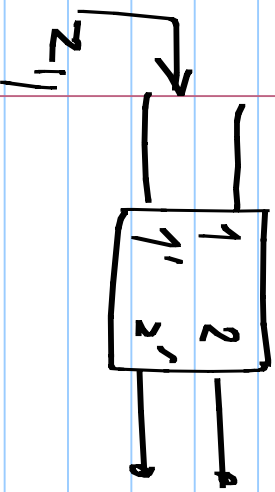
y_{11} : Conductance looking into port 1 (with port 2 shorted)



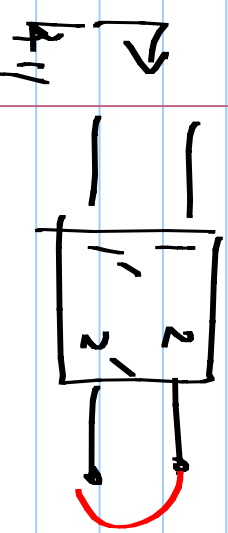
Z_{11} : resistance looking into port 1 with port 2 open



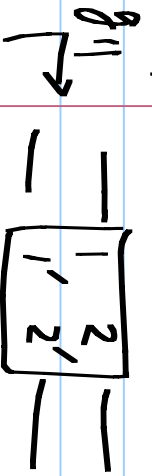h_{11} : Resistance looking into port 1 with port 2 shorted




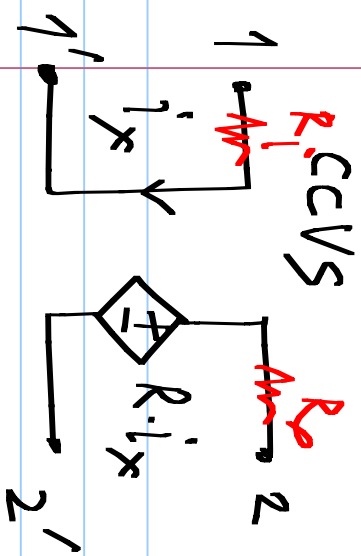g_{11} : Conductance into port 1 (port 2 open)




$$[Z] = \begin{bmatrix} 0 & 0 \\ R & 0 \end{bmatrix}$$

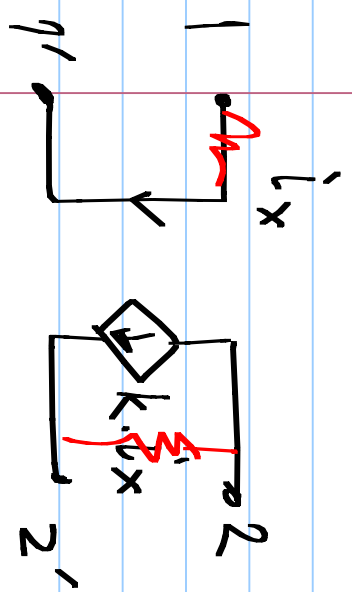
$$[Y] = \begin{bmatrix} 1/R_1 & 0 \\ -R/R_1 R_2 & 1/R_2 \end{bmatrix}$$






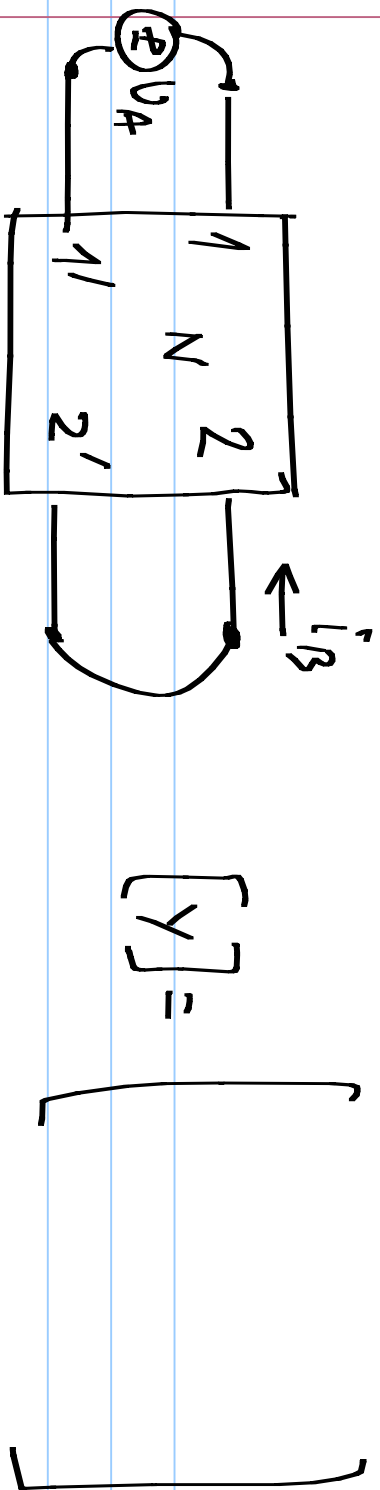
$$[H] = \begin{bmatrix} 0 & 0 \\ k & 0 \end{bmatrix}$$



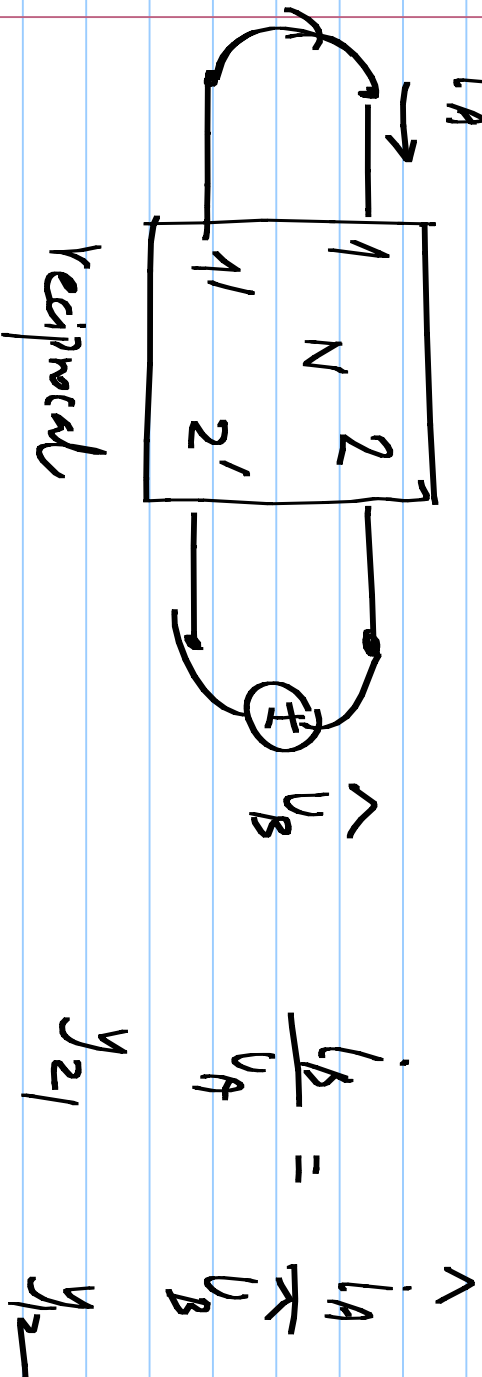Reciprocal $\implies y_{12} = y_{21} \quad / \quad z_{12} = z_{21}$



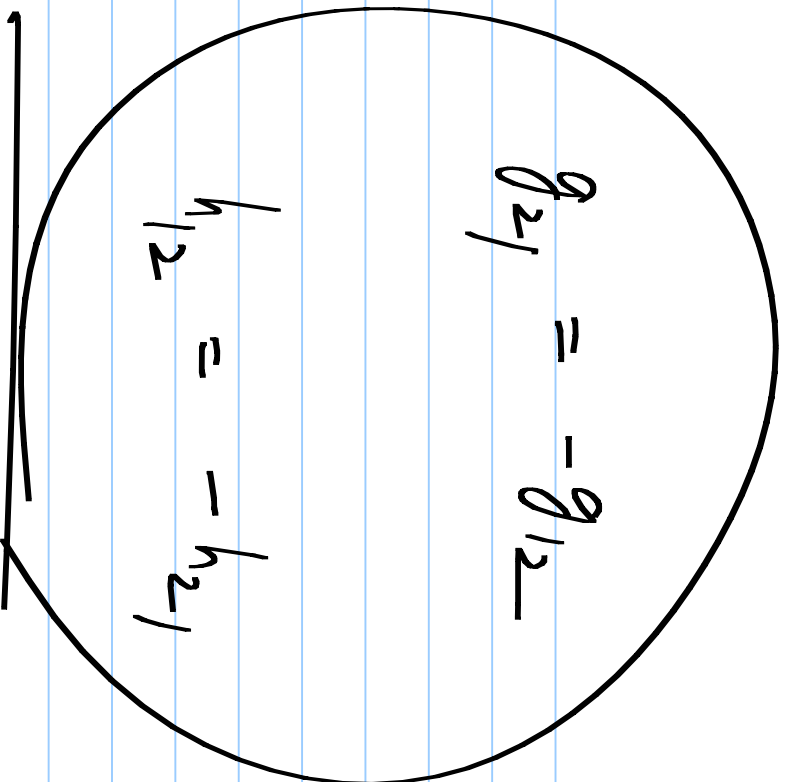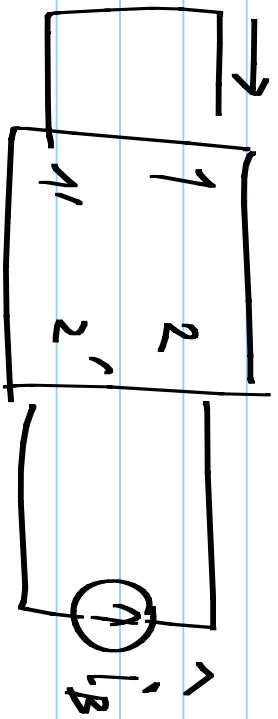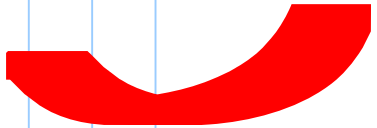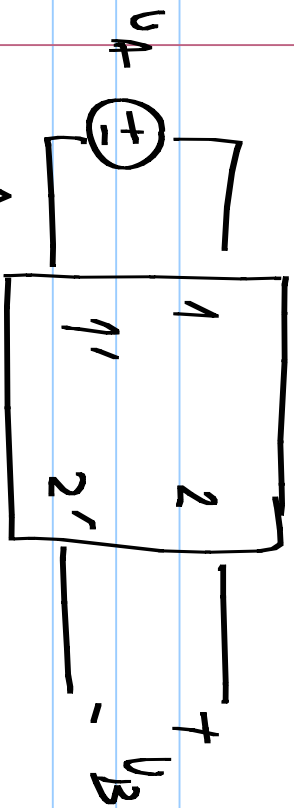
$$i_B = \frac{V_B}{Z_{12}} = \frac{i_A}{K} \frac{V_A}{V_B}$$




Reciprocity $1 \xrightarrow{m} 2$
 $1' \xrightarrow{m} 2'$

$$\frac{V_B}{V_A} = - \frac{I_A}{I_B}$$

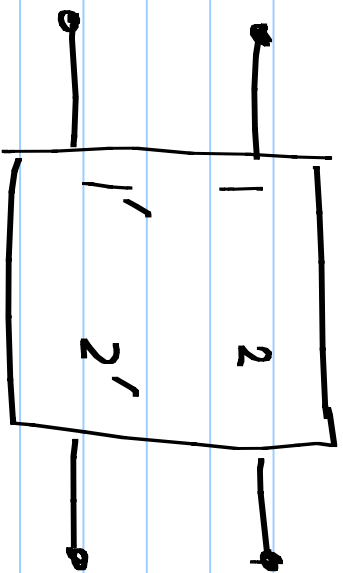


$$I_1 = y_{11} V_1 + y_{12} V_2$$


$$I_2 = y_{21} V_1 + y_{22} V_2$$

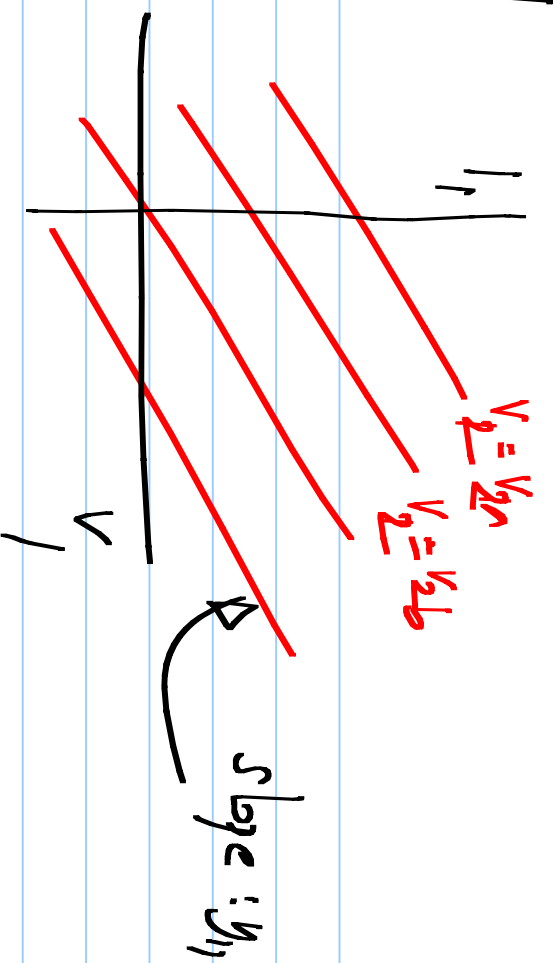

I_1 vs. V_1 for diff. V_2

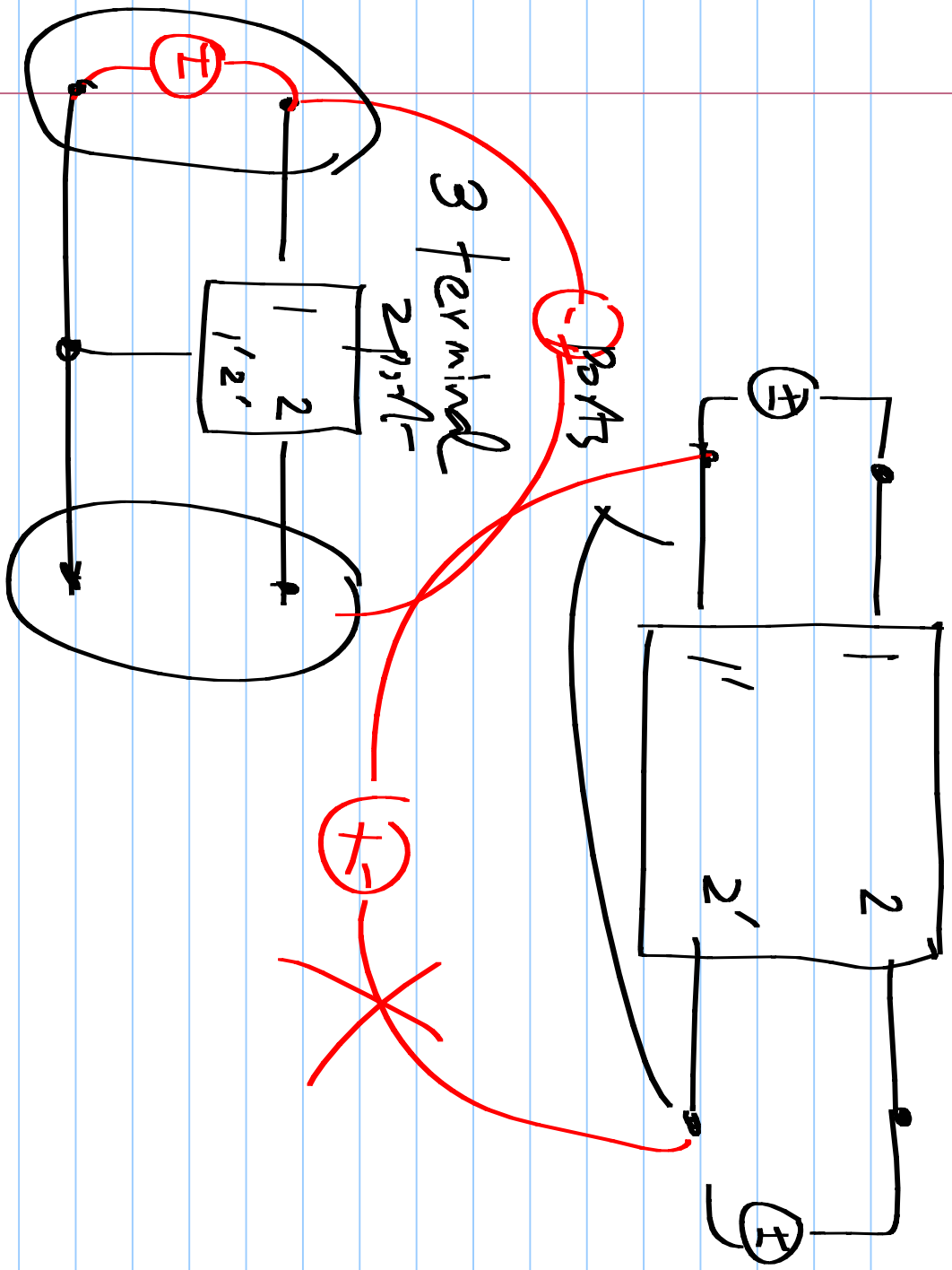

Lecture 16 :

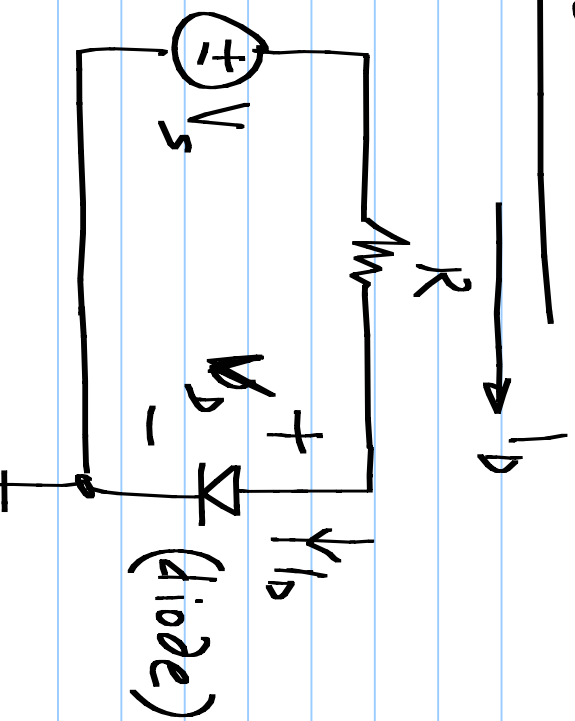


$$I_D = I_s \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right] \quad \text{--- (2)}$$

$$V_s = I_D \cdot R + V_D \quad \text{--- (1)}$$

$$= I_s \cdot R \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right] + V_D \quad \text{---}$$

I_s, V_T : constants

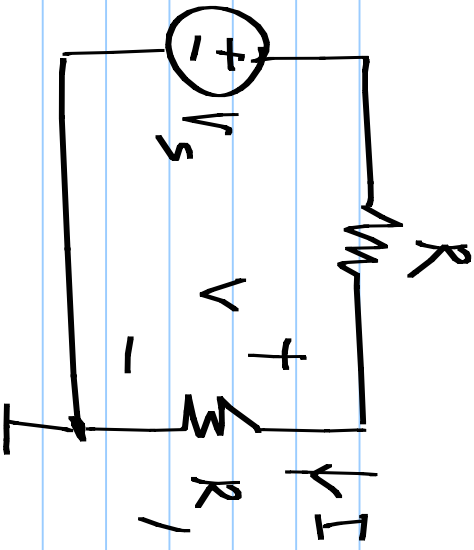
$$I_D = I_s \left(\exp\left(\frac{V_D}{V_T}\right) - 1 \right)$$




$$I = \frac{V}{R_1}$$

$$V_s = I \cdot R + V \quad \text{--- (2)}$$

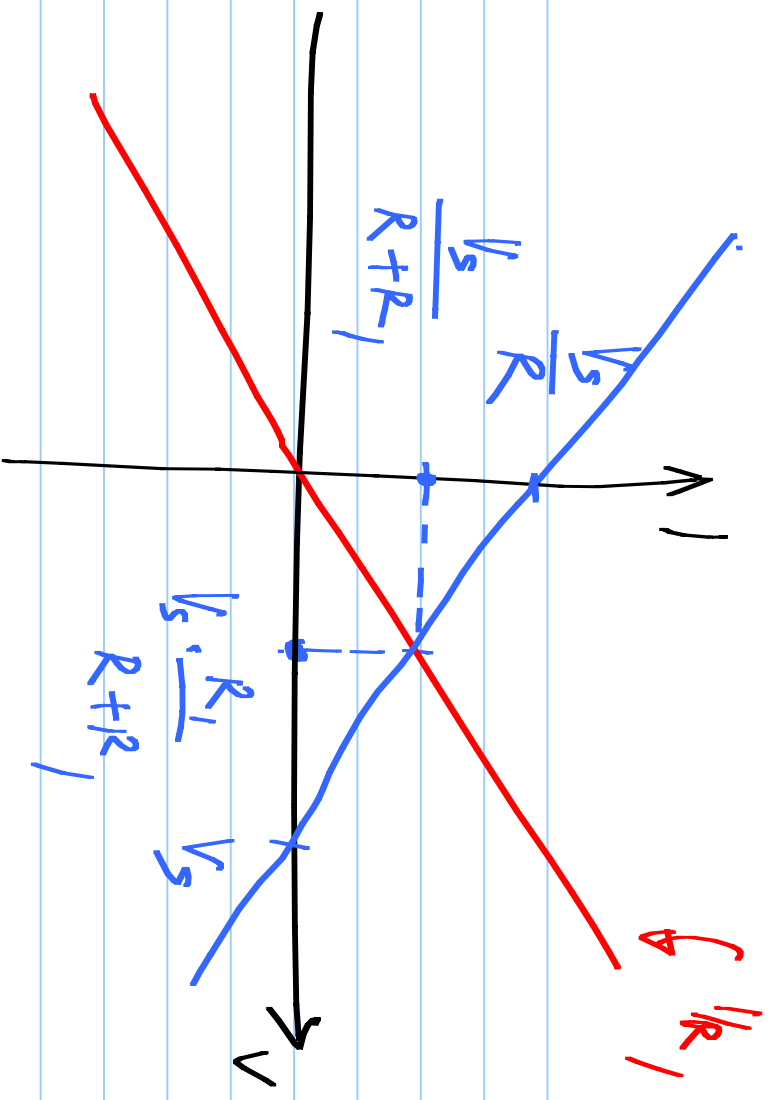
$$I = \frac{V}{R_1} \quad \text{--- (1)}$$



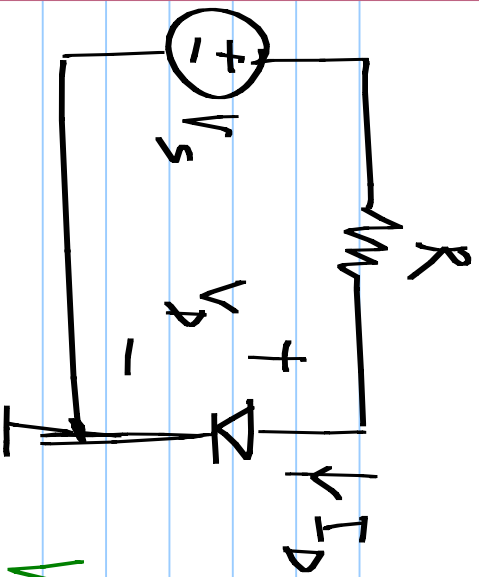

$V_s = 5V$
 $I_s = 10^{-15}A$
 $R = 1k\Omega$
 $V_T = 25mV$

$$I = \frac{V}{R}$$

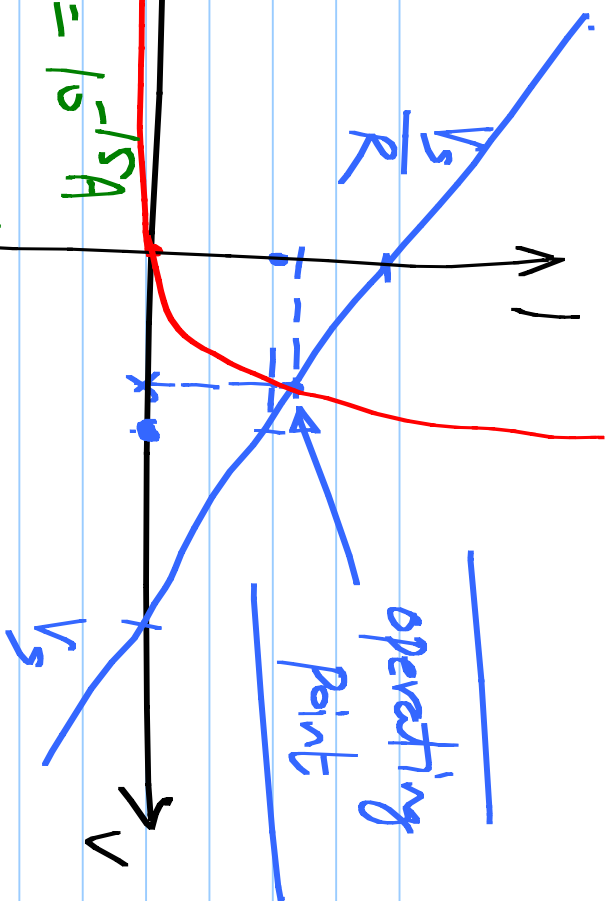


$f(V_D)$

$$V_s = I \cdot R + V \quad \text{--- (2)}$$

$$= I_s R \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right] + V_D - V_s$$

$$I_s = I_s \left(\exp\left(\frac{V_D}{V_T}\right) - 1 \right) - 1 \quad \text{--- (1)}$$

$$= 0$$

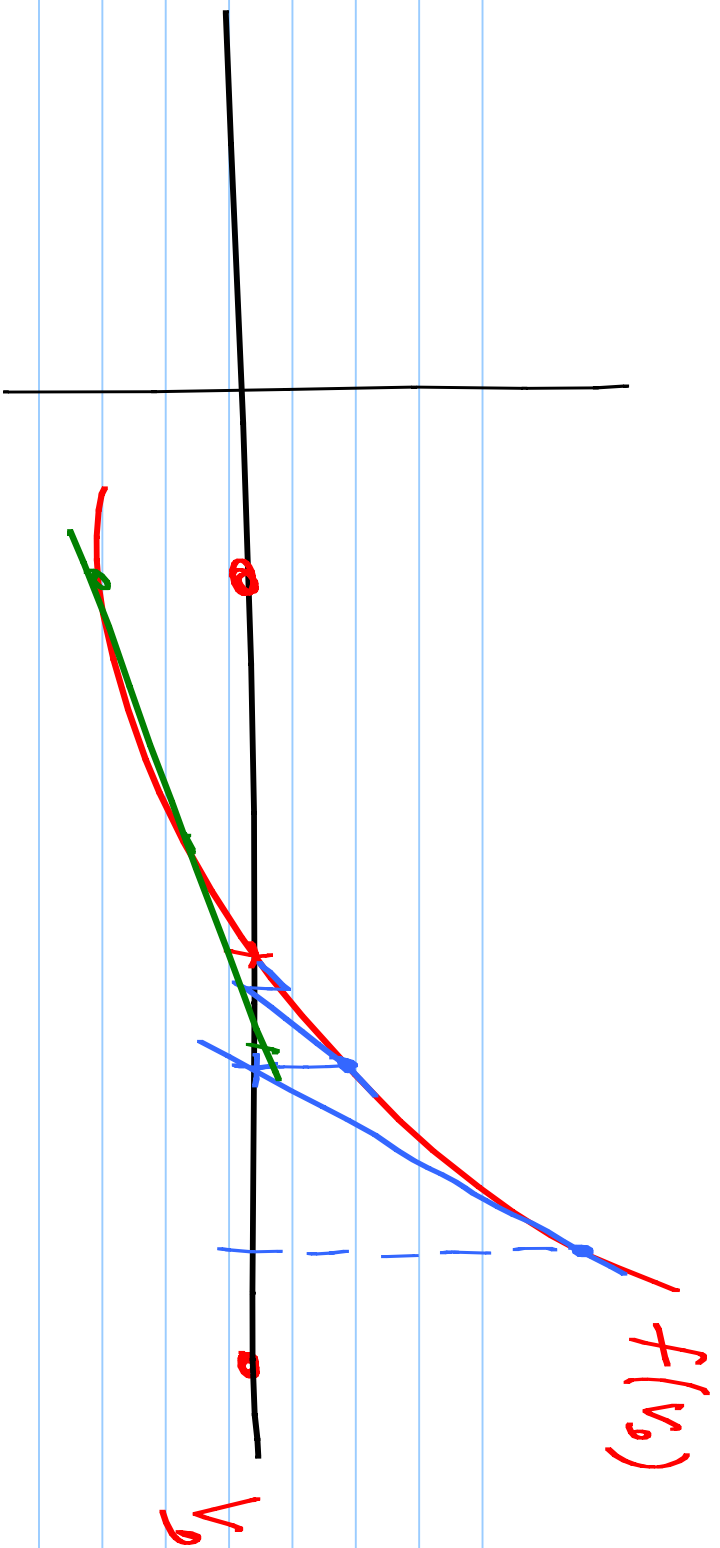

$$f(v_0) = 0$$

$$f(V_0) = 0$$

\swarrow

\neq

$$\frac{g(V_0)}{g(1)} = V_0 \quad V_0 = 1 \quad \text{step \# 1}$$

$$g(1) \neq 1 \quad V_0 = g(1)$$

$$g(g(1)) \neq g(1)$$

$$f(V_s) = I_s R \left[\exp\left(-\frac{V_D}{V_T}\right) - 1 \right] + V_D - V_s = 0 \quad \textcircled{1}$$

V_s : changes I_s to $V_s + \Delta V_s$ ($\Rightarrow V_D$ changes to $V_D + \Delta V_D$)

$$I_s R \left[\exp\left(-\frac{V_D + \Delta V_D}{V_T}\right) - 1 \right] + (V_D + \Delta V_D) - V_s - \Delta V_s = 0$$

$$I_s R \left[\exp\left(-\frac{V_D}{V_T}\right) - 1 + \frac{1}{V_T} \cdot \exp\left(-\frac{V_D}{V_T}\right) \cdot \Delta V_D + \cancel{0.0} \right] \quad \textcircled{2}$$


$$+ (V_D + \Delta V_D) - V_s - \Delta V_s = 0$$

$$g(v) \Big|_{v=v_0} = g(v_0) + g'(v) \Big|_{v=v_0} \cdot (v-v_0) + \frac{g''(v)}{2!} \Big|_{v=v_0} (v-v_0)^2 +$$

② - ① :

$$\frac{15R}{V_f} \exp\left(\frac{V}{V_f}\right) \cdot \Delta V_0 + \Delta V_0 - \Delta V_s = 0$$
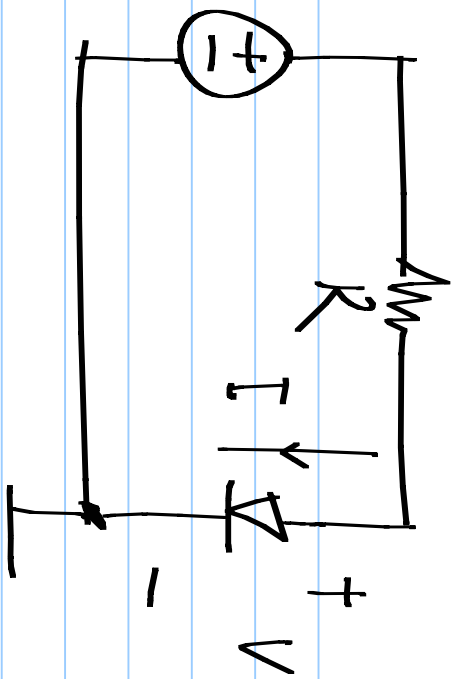
$$\frac{15R}{V_f} \exp\left(\frac{V}{V_f}\right) \cdot \Delta V_0 + \Delta V_0 = \Delta V_s \quad \checkmark$$



op. point: (I_0, V_0)

$$I_0 = f(V_0)$$

$$I_0 + \Delta I = f(V_0 + \Delta V)$$

$$\approx f(V_0) + f'(V_0) \cdot \Delta V$$

$$I = h(V)$$

$$\Delta I = f'(V_0) \cdot \Delta V$$

(higher order terms
neglects)

$$\underline{V_0}$$


Linear relationship between incremental values

$$\Delta I = f' \Big|_V \cdot \Delta V \Rightarrow \begin{matrix} + \\ \downarrow \\ \Delta I \end{matrix} \quad \begin{matrix} \Delta V \\ \downarrow \\ \sim \\ R = \frac{1}{f' \Big|_V} \end{matrix}$$


$$I_D = I_S \left(\exp\left(\frac{V_D}{V_T}\right) - 1 \right) \approx I_S \exp\left(\frac{V_D}{V_T}\right)$$

Incremental resistance \curvearrowright

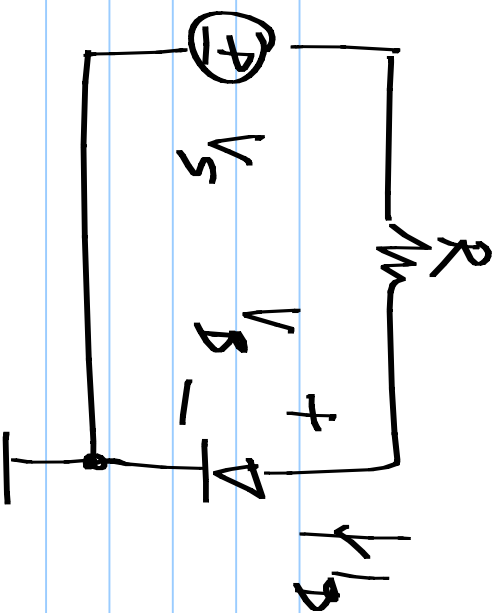
$$r_D = \frac{1}{I_S \exp\left(\frac{V_D}{V_T}\right)} = \frac{V_T}{I_D}$$



1. Calculate the op. point -

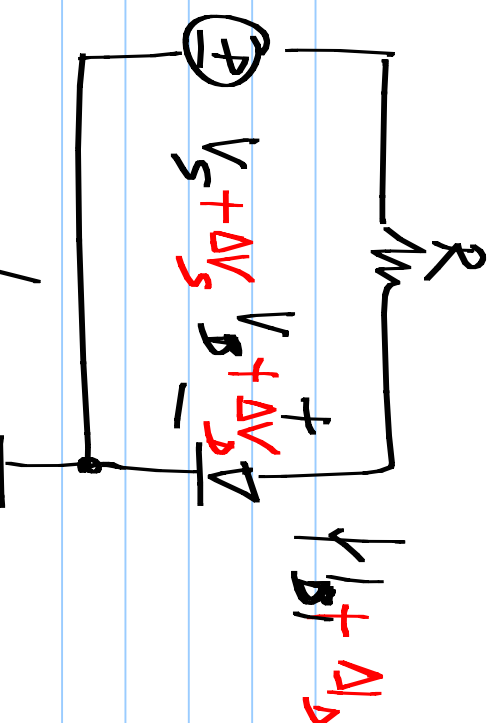

form an incremental ckt. @ op. point

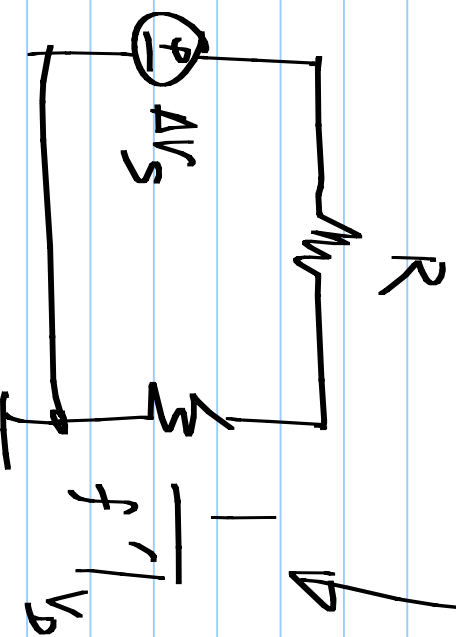

$$\frac{\Delta V_S}{R} = \frac{V_B}{R}$$

total