
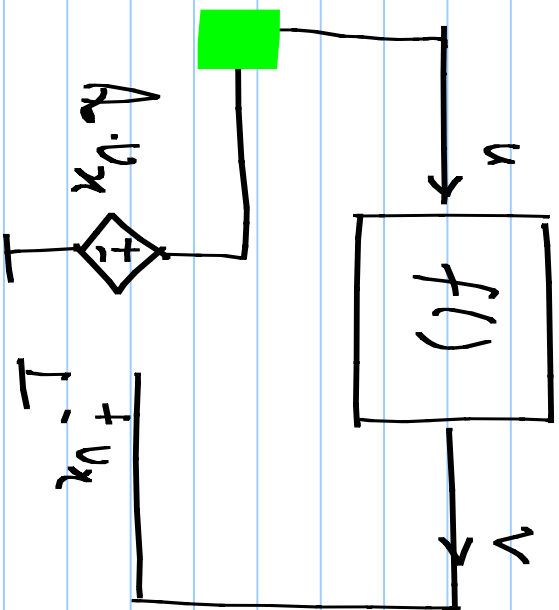


Lecture 18

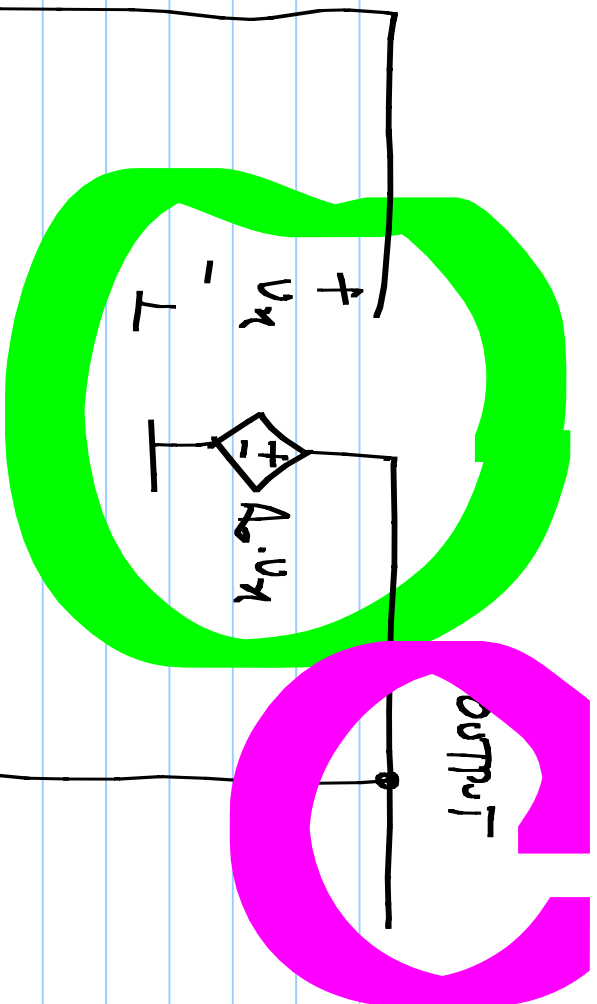

Solving $f(u) = 0$ means
finding u_0 such that


$$f(u_0) = 0$$



For $A_0 \rightarrow \infty$,

output $v = v_0$

$v_0 : f(v_0) = 0$

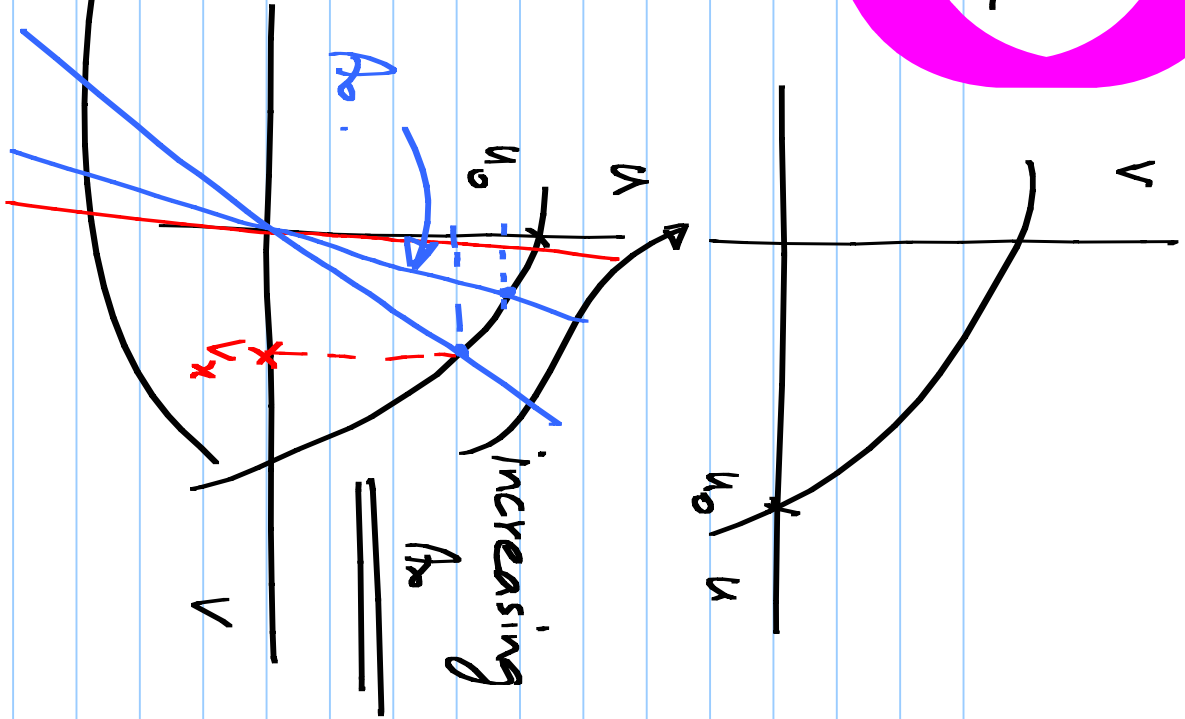

Slope: A_0 .

increasing A_0



$$V_o = k V_i$$


V_i : input voltage

V_o : output voltage ($V_i - V_o/k$)

$$V_o - k V_i = 0 \quad (\text{don't have } k V_i)$$

$$\frac{V_o}{k} - V_i = 0 \quad \checkmark$$

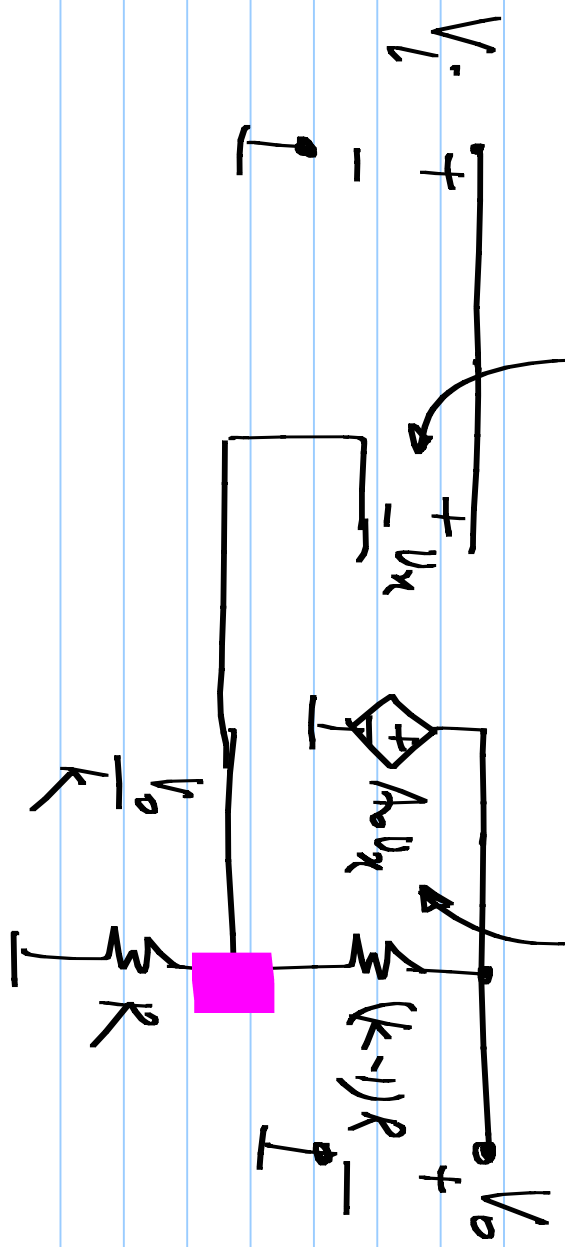
$$A_o \left(V_i - \frac{V_o}{k} \right) = V_o$$



$$N_o = V_L \cdot \frac{1}{\frac{1}{k} + A_o} = k V_L \cdot \left[\frac{1}{1 + \left(\frac{k}{A_o}\right)} \right]$$



if $A_o \rightarrow \infty$

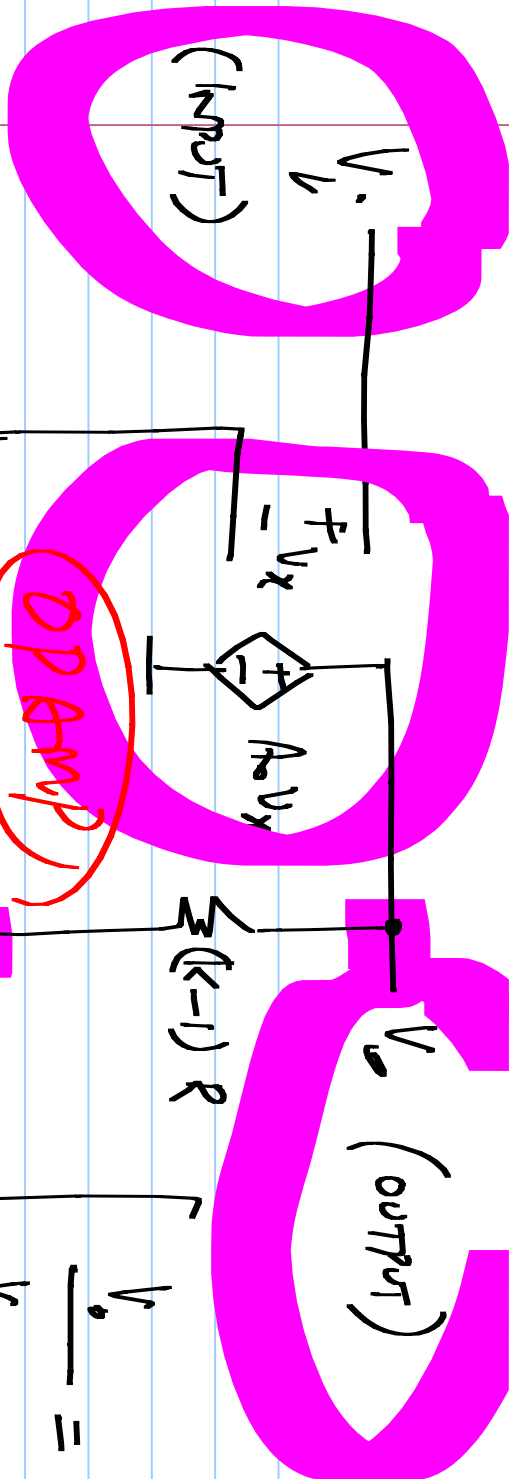

$$k = 10$$

$$A_o = 1000$$

$$A_o = 2000$$


Error.

$$(V_e) = V_i - \frac{V_o}{k}$$

$$\left[\frac{V_o}{V_i} = \frac{k}{\left(1 + \frac{k}{A_o}\right)} \right]$$


$$\approx k \quad A_o \rightarrow \infty$$

Desired: $V_o = k \cdot V_i$

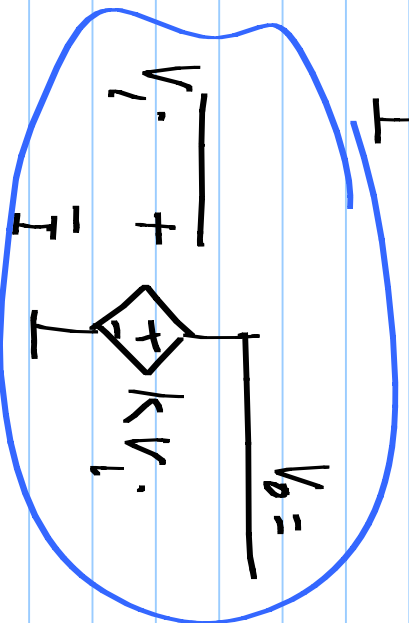

$$\frac{10}{1.01} \quad \frac{10}{1.02}$$

$$\frac{10}{1.025}$$

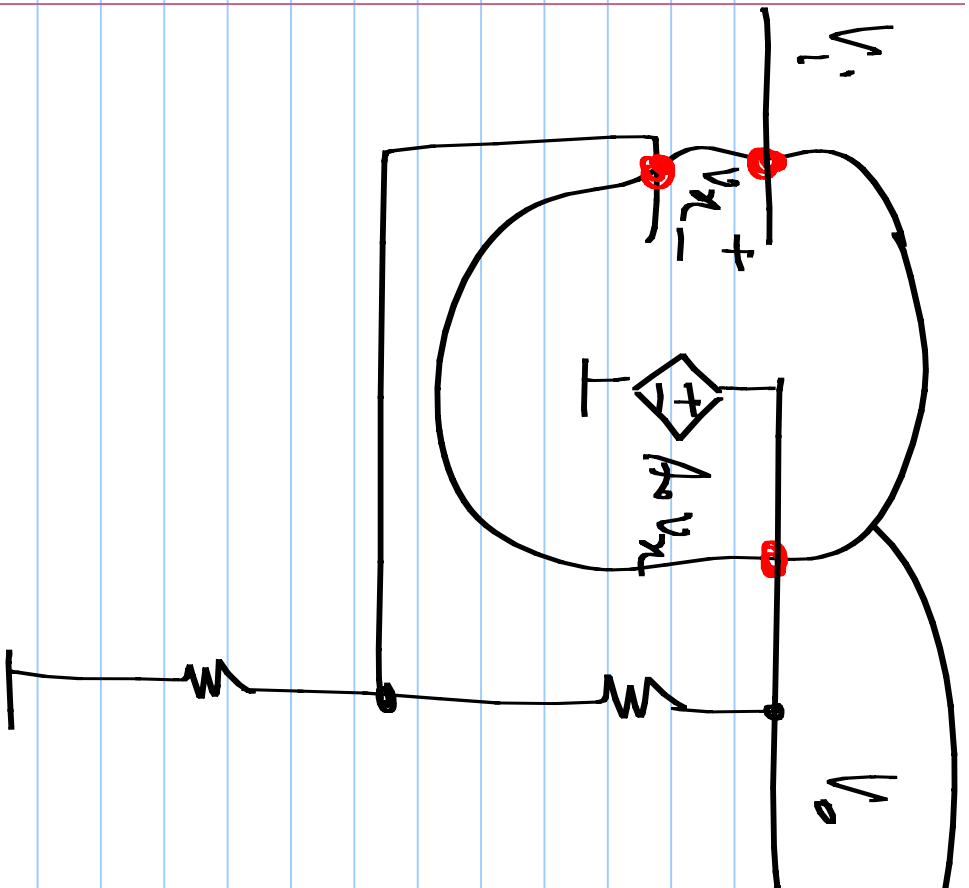

Operational amplifier (opamp)

