
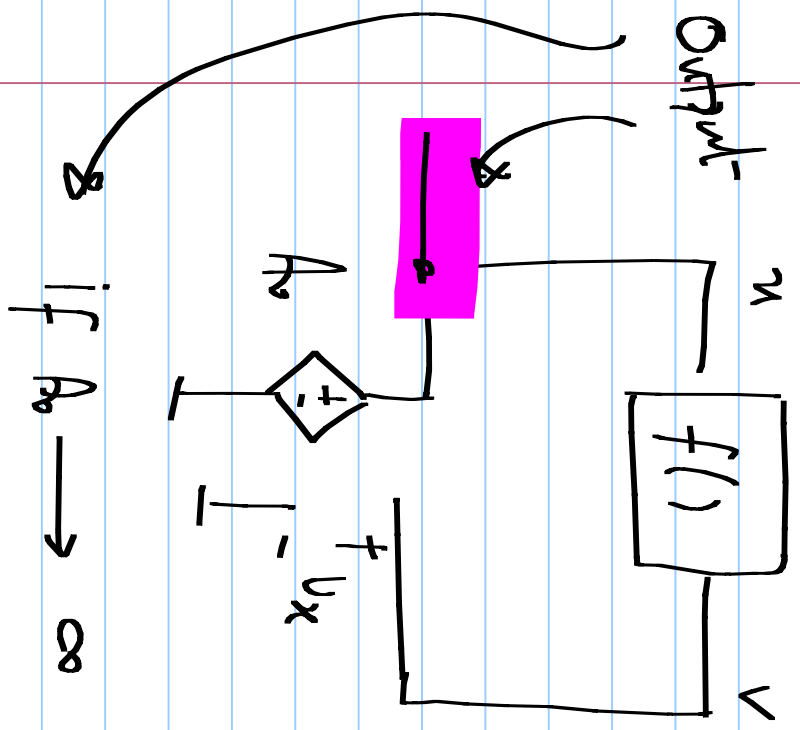


Lecture 19

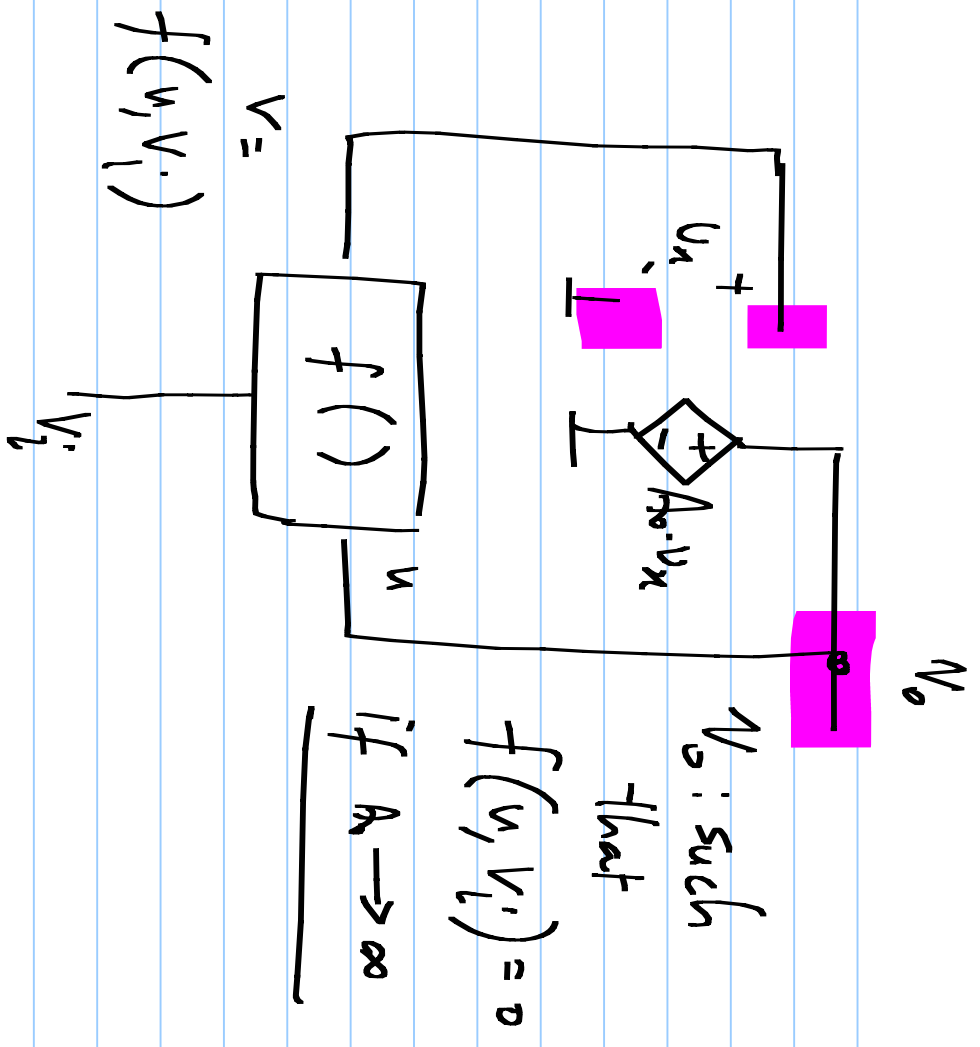

if $A_0 \rightarrow \infty$




v_0 : such that $f(v_1, v_2) = 0$
if $A_0 \rightarrow \infty$


Amplifier:

$$V_o = k \cdot V_i$$

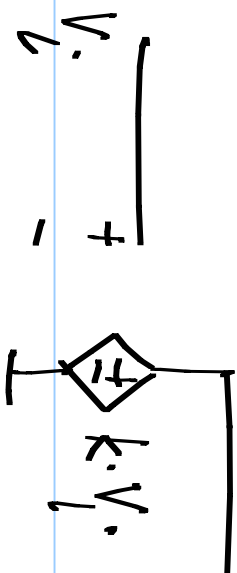
$$\frac{V_o}{k} - V_i = 0 \quad V_o - kV_i = 0$$



$$V_i - \frac{V_o}{k} = 0$$

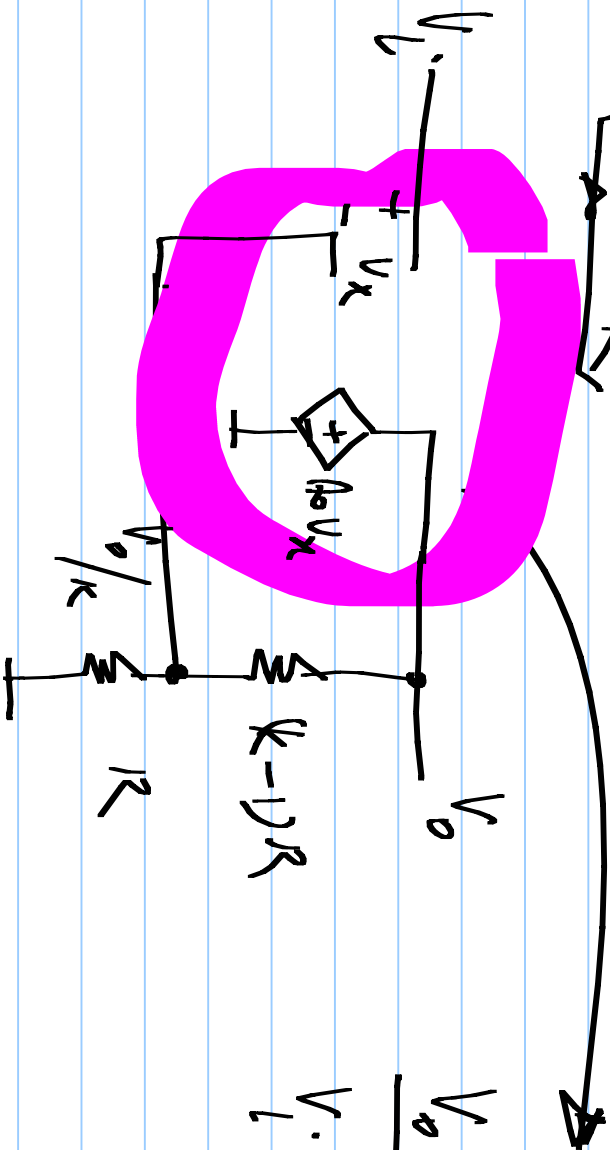

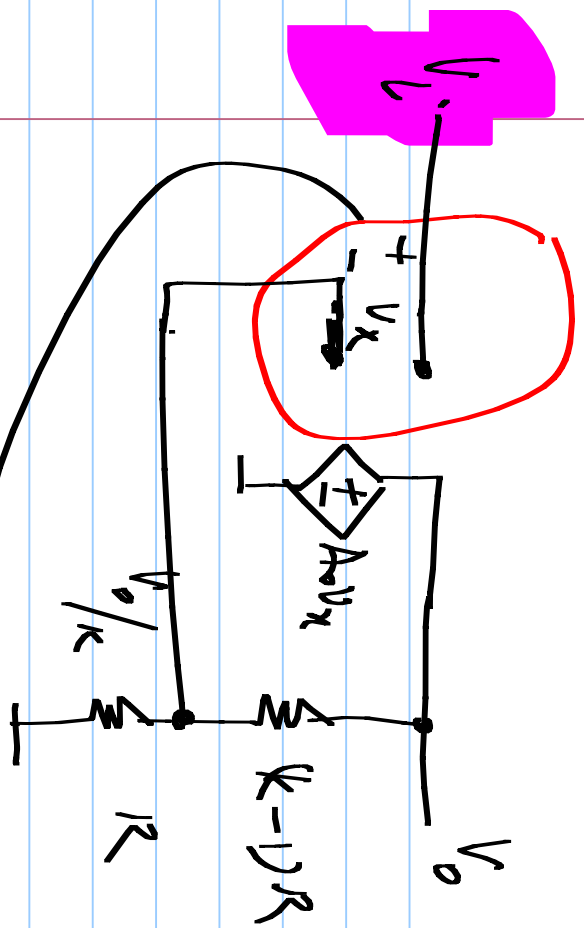
$$\frac{V_o}{V_i} = \frac{k}{1 + \left(\frac{k-1}{A_o}\right)}$$




$$\frac{V_0}{V_L} = \frac{k}{1 - \frac{k}{A_0}}$$

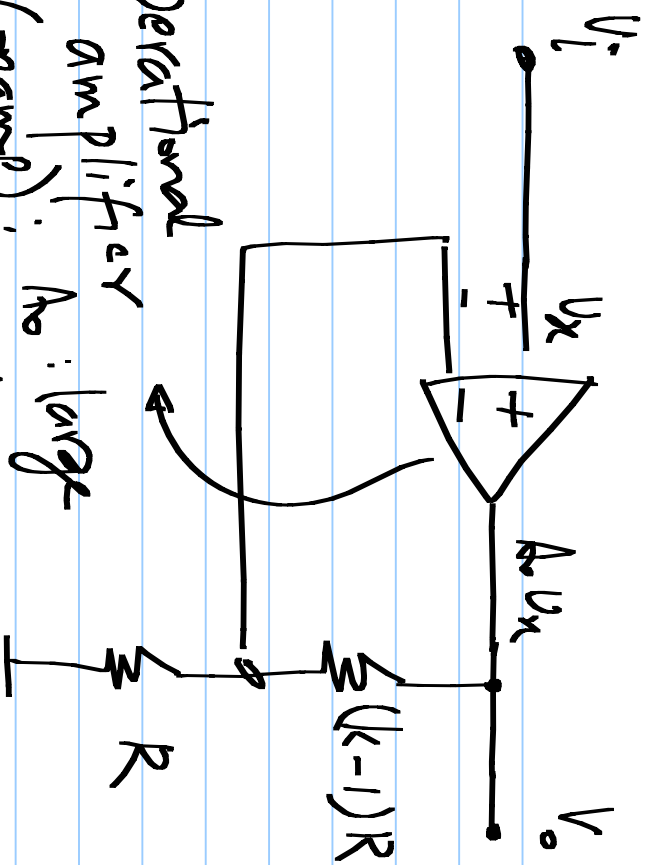Operational amplifier (opamp): $A_0 \gg 1$
 A_0 : large




$$\left(V_L - \frac{V_0}{k} \right) = V_L - \frac{A_0 \cdot V_x}{k}$$


$$V_L + \frac{A_0 V_x}{k}$$

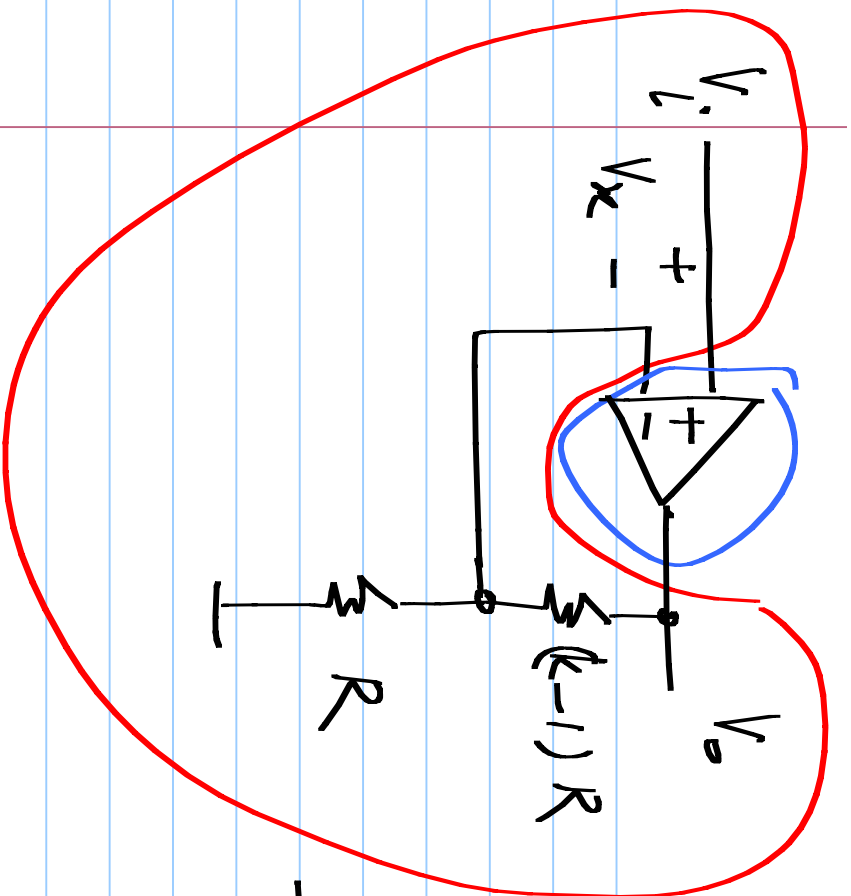

$$V_L = V_o - \frac{V_o}{k}$$

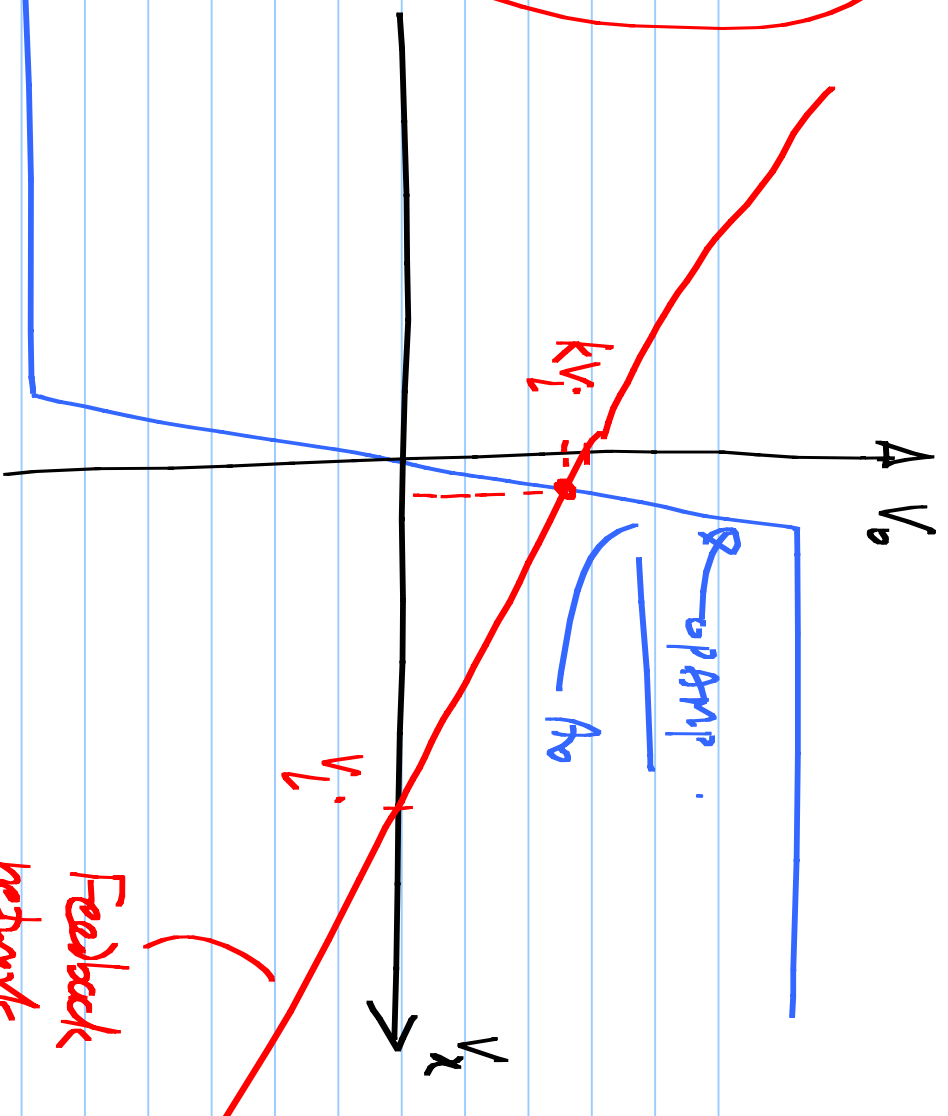


Feedback network




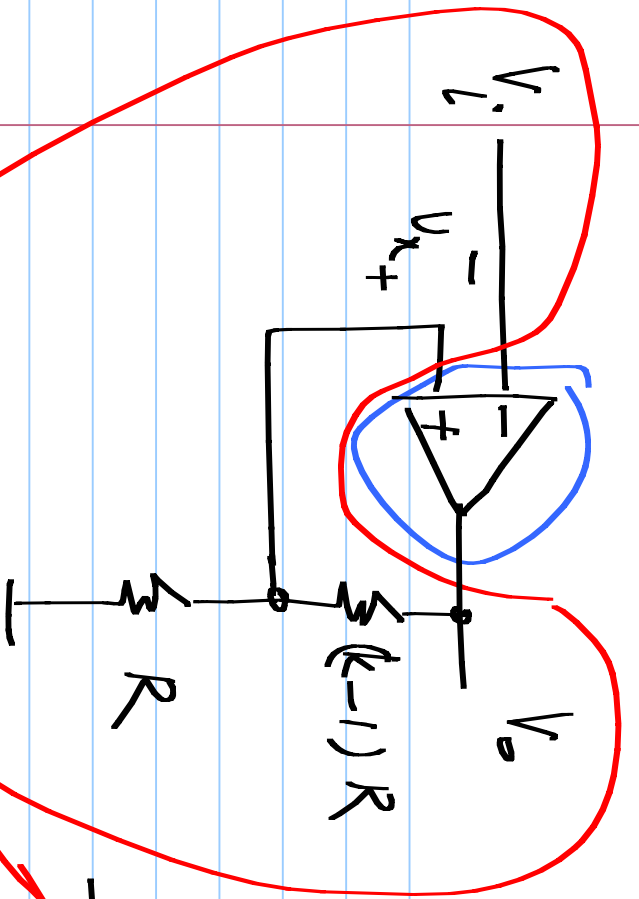


$V_i = -V_o \cdot \frac{R}{(k-1)R}$

Stabile

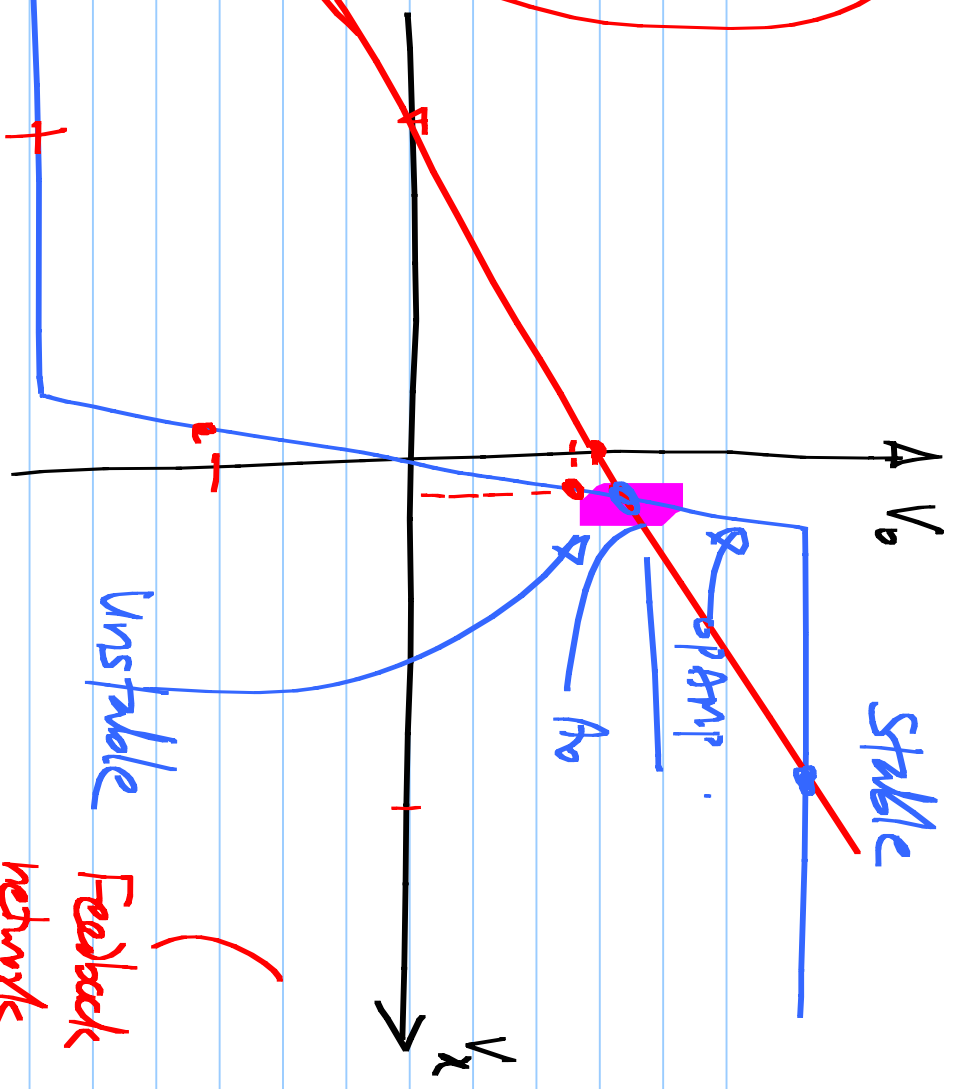



Feedback network

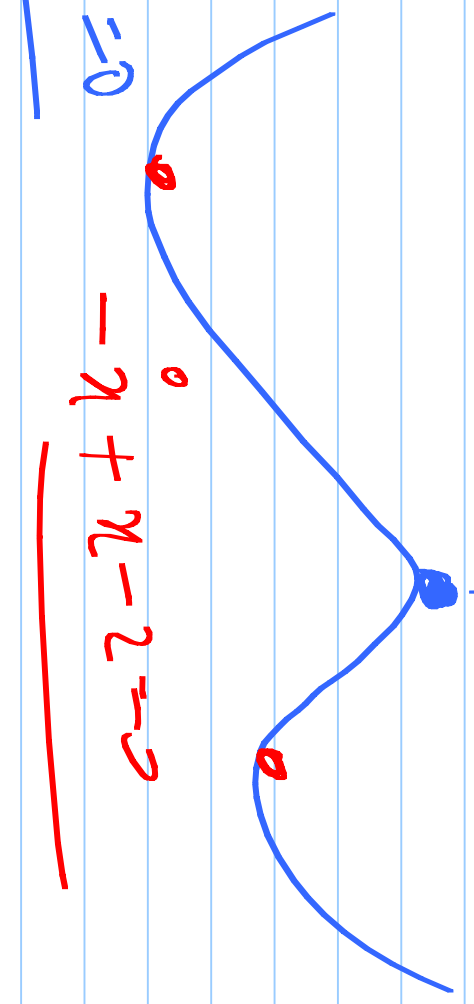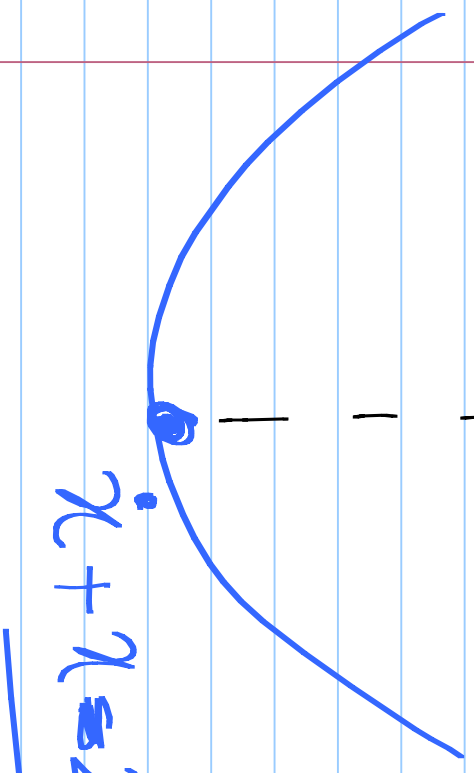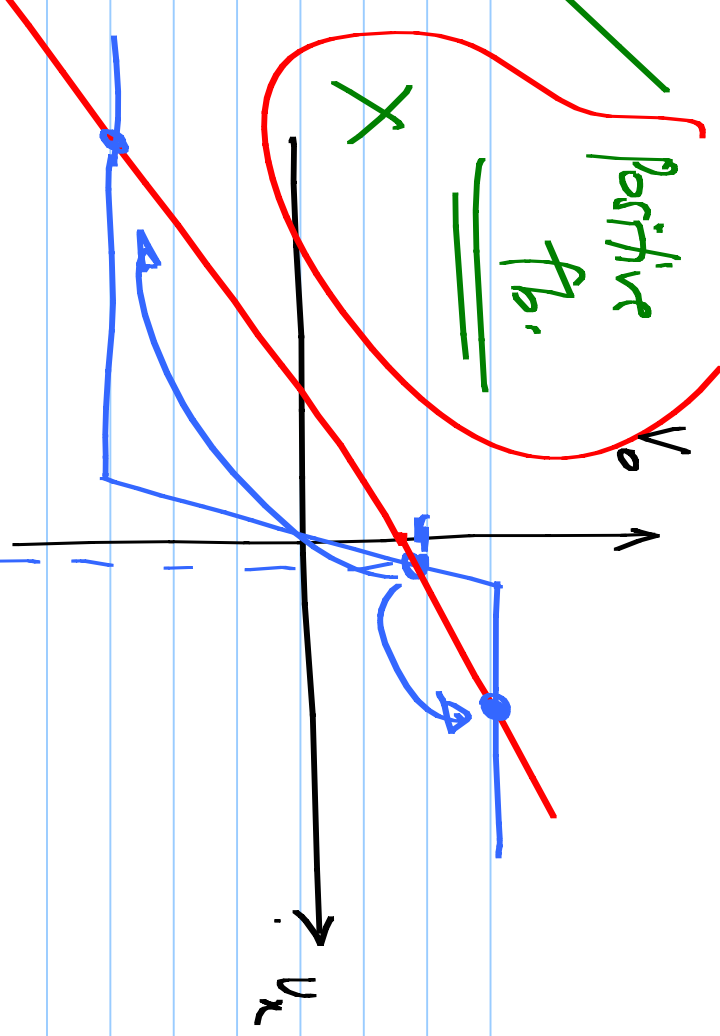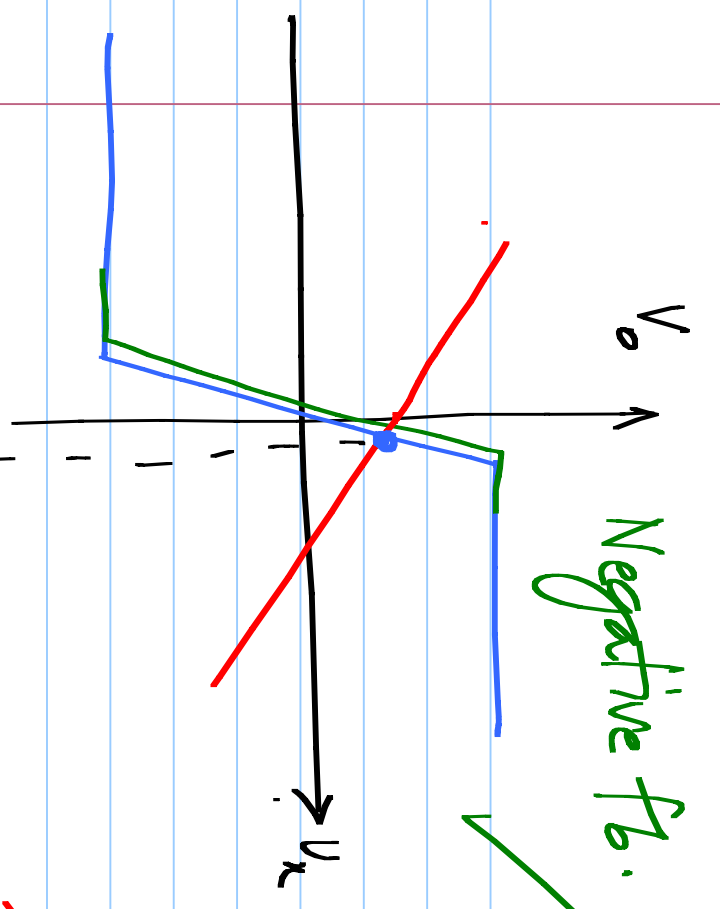


$\chi + \chi = 2 = 0$

$-\chi + \chi - 2 = 0$

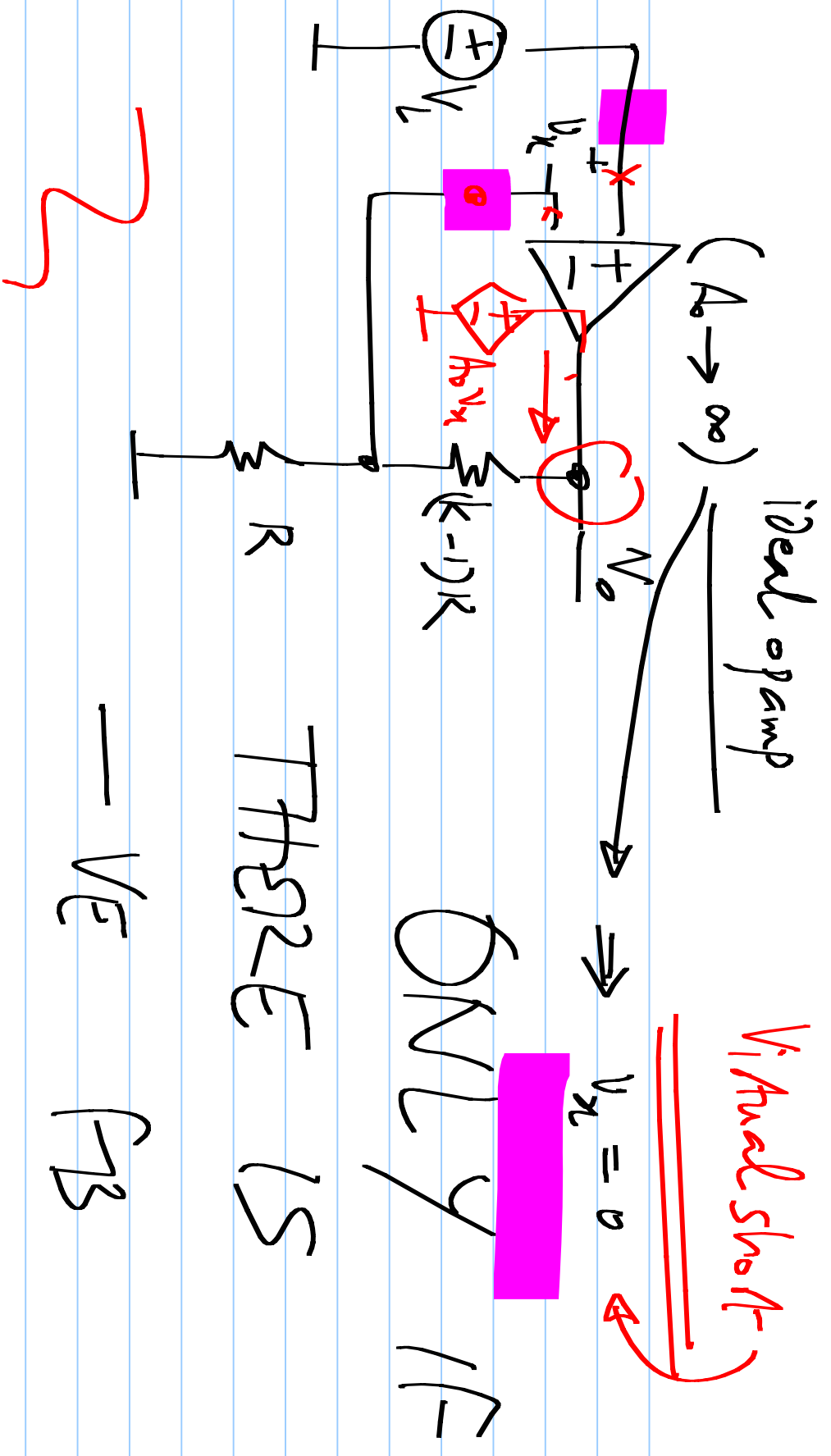

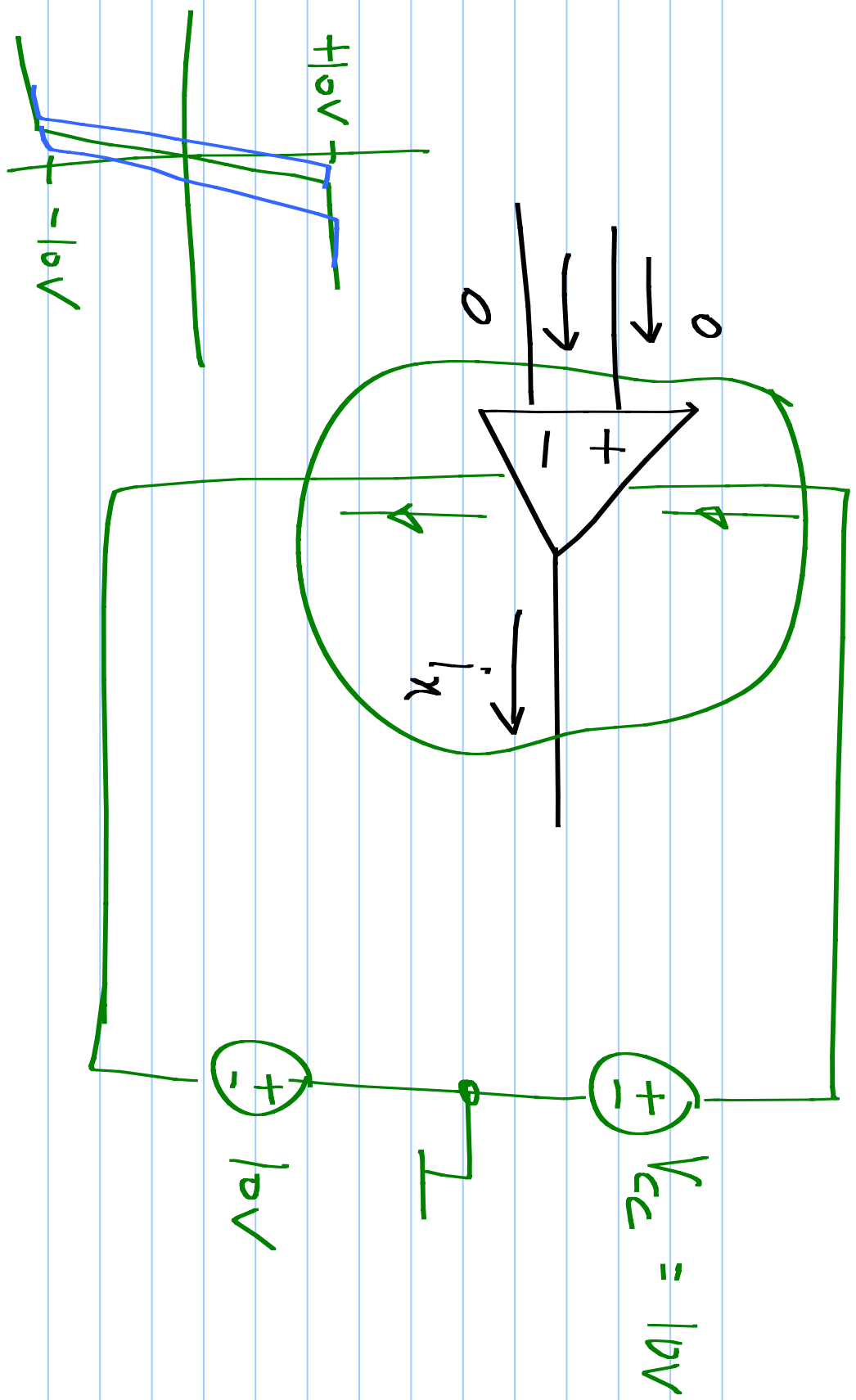

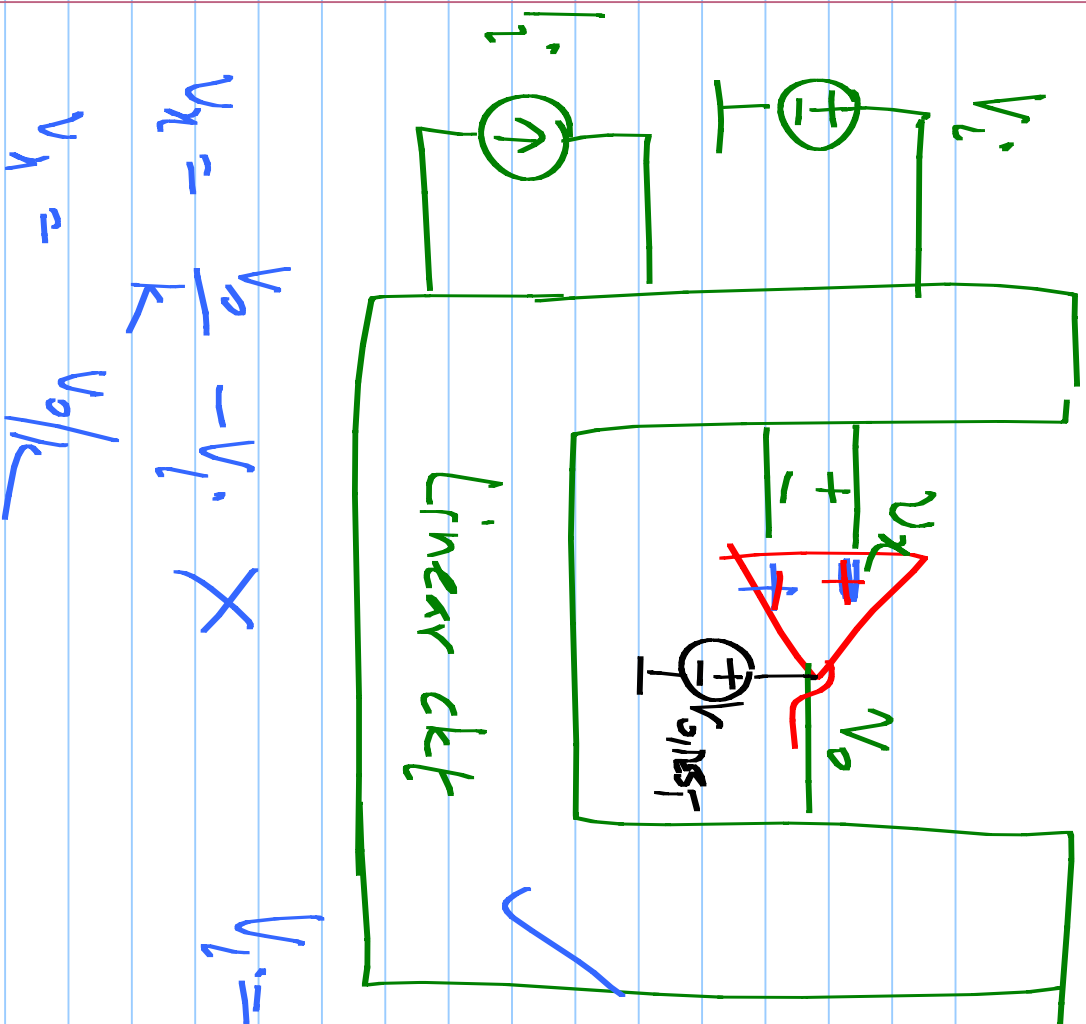

$$V_x = \frac{V_0}{k} - V_1 \quad \times$$

$$V_x = V_0/k$$

