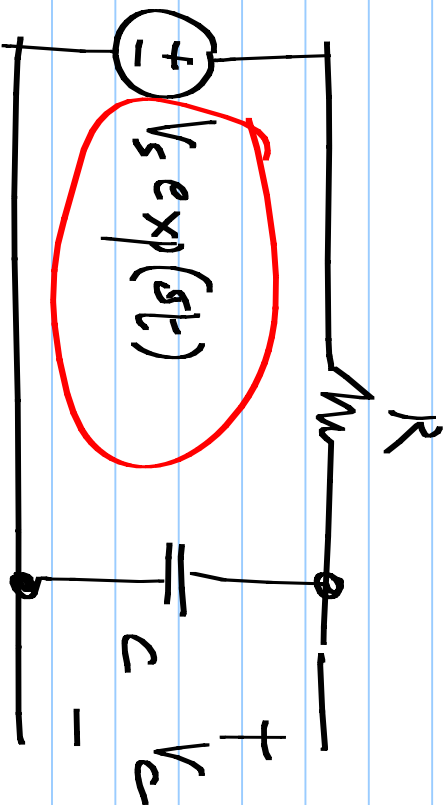


Lecture 23



$$RC \frac{dV_c}{dt} + V_c = V_s \exp(st)$$


$$V_c(t) = V_0 \cdot \exp(-t/RC)$$

$$+ \left[V_s \exp(st) \cdot \frac{1}{1 + sRC} \right]$$

Transient / Natural

Steady state / (forced) response
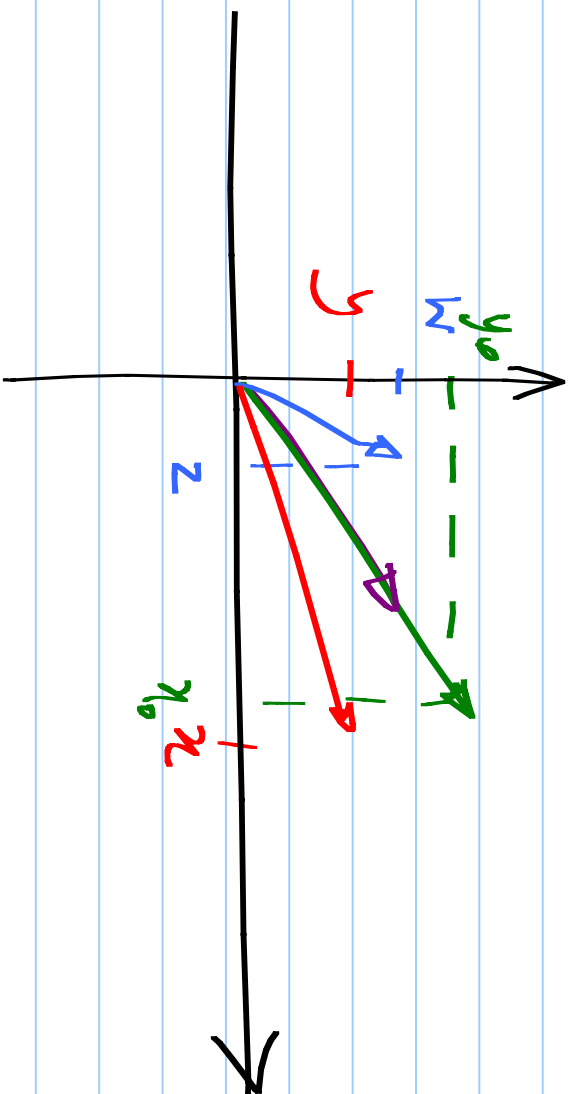
$$\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} z \\ w \end{bmatrix}$$




$$RC \cdot \frac{dV_c}{dt} + V_c = V_s \exp(st)$$

$$V_c = V_c - V_s \exp(st)$$

$$RC \cdot \frac{dV_c}{dt} + \underline{SCR \cdot V_s \cdot \exp(st)} +$$

$$\frac{dV_{c1}}{dt} = \frac{dV_c}{dt} - V_s \cdot s \cdot \exp(st)$$
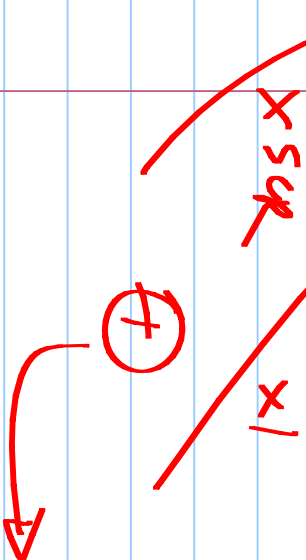
$$V_{c1} + \cancel{V_s \exp(st)} = \cancel{V_s \exp(st)}$$



$$V_c(t) = V_0 \cdot \exp(-t/R_c)$$

$$V_0: V_c(0) = \frac{V_s}{1+sCR}$$

$$s = \frac{s-1}{CR}$$

$$+ \frac{V_s \exp(st)}{1+sCR}$$

$$\frac{1+sCR}{1+sCR} = s$$

$$\lim_{s \rightarrow 0}$$

$$\left(V_c(0) - \frac{V_s}{1+sCR} \right) \exp(-t/R_c) + \frac{V_s \exp(st)}{1+sCR}$$

$$(1+sCR) V_c(0) \exp(-t/R_c) = V_s \exp(-t/R_c) + V_s \exp(st)$$

$$(1+sCR)$$

$$(1 + sCR) V_C(0) \exp(-t/RC) - V_S \exp(-t/RC) + V_S \exp(st) \sqrt{\exp\left(\frac{st}{RC}\right) \exp(-t/RC)}$$

$$(1 + sCR)$$

$$S = 1 + sCR$$

$$V_S \left(1 + \frac{st}{RC} + \left(\frac{st}{2RC}\right)^2 + \dots \right)$$

$$s \rightarrow 0$$

$$s = \frac{s-1}{CR}$$


$$s V_C(0) - \cancel{V_S} + V_S \exp(st/RC)$$


$$\cdot \exp(-t/RC)$$

s

$$\left(V_C(0) + V_S \cdot \frac{t}{RC} \right) \exp(-t/RC)$$
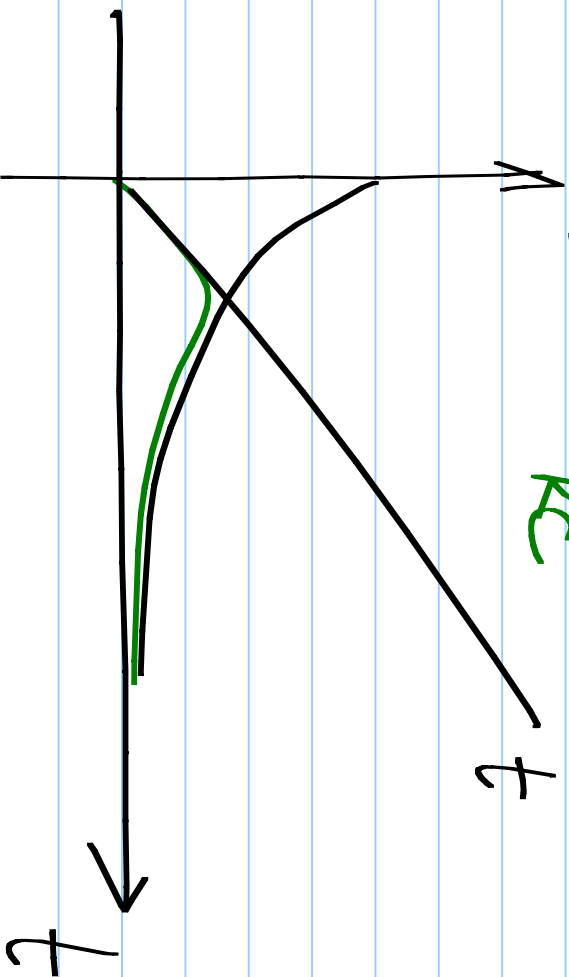
$$(V_c(s) + V_s \cdot \frac{t}{RC}) \exp(-t/RC)$$



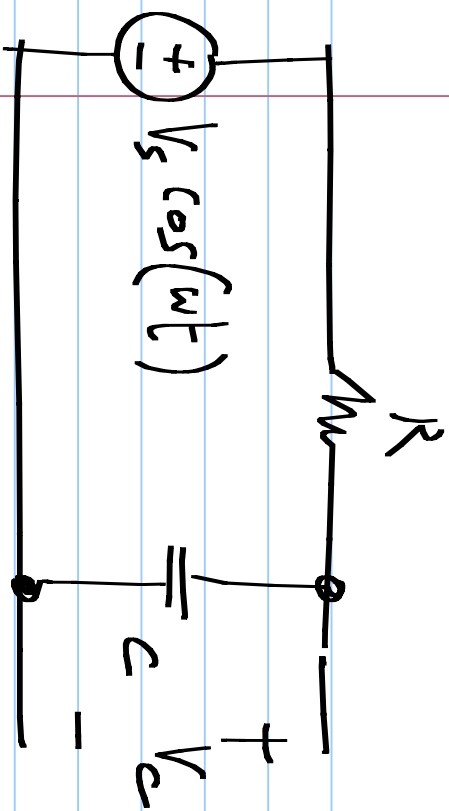



$$RC \frac{dV_c}{dt} + V_c = V_s \cdot \cos(\omega t)$$

$$V_c = j = \sqrt{-1}$$

$$\cos(\omega t) = \frac{\exp(j\omega t) + \exp(-j\omega t)}{2}$$
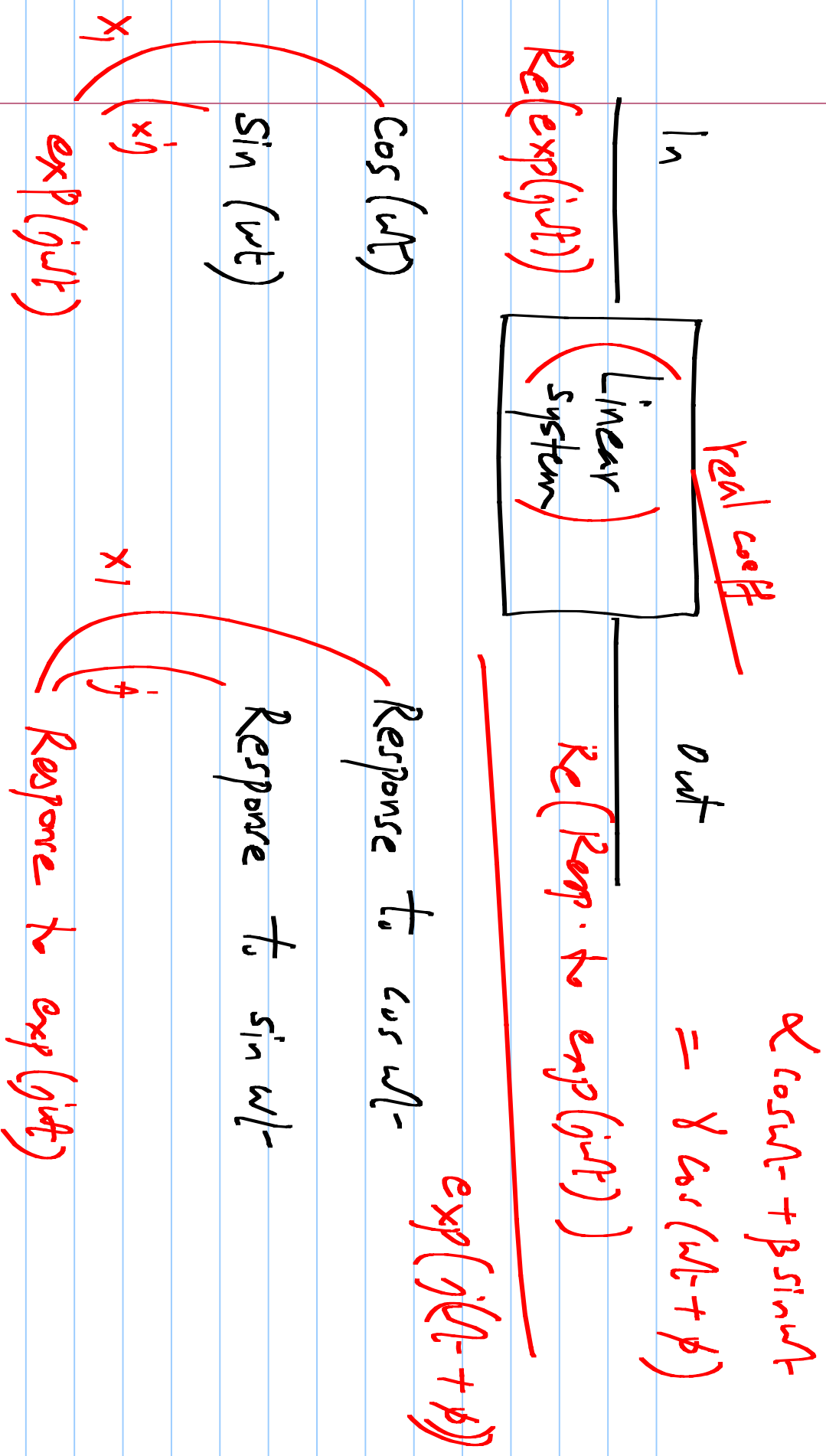
$$\sin(\omega t) = \frac{\exp(j\omega t) - \exp(-j\omega t)}{j2}$$



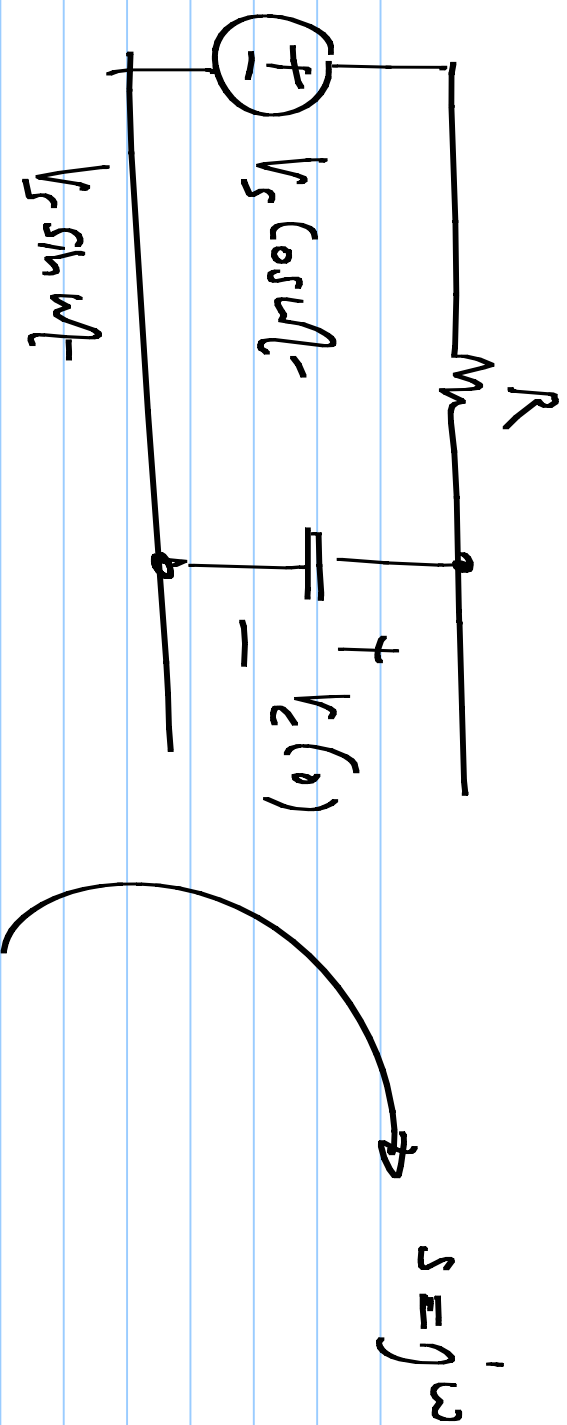

$$(1 + sCR) V_c(s) \exp(-t/RC) = V_s \exp(-t/RC) + V_s \exp(st)$$

$$(1 + sCR)$$

$$V_c(s) \exp(-t/RC) = \left(\frac{V_s}{1 + j\omega RC} \right) \exp(-t/RC) + \frac{V_s \exp(j\omega t)}{1 + j\omega RC}$$

$$V_c(s) \exp(-t/\tau_c) - \left(\frac{V_s}{1+j\omega\tau_c} \right) \exp(-t/\tau_c) + \underbrace{V_s \exp(j\omega t)}_{\text{[redacted]}}$$

$$V_c(s) \exp(-t/\tau_c) - \frac{V_s}{1+(j\omega\tau_c)^2} \exp(-t/\tau_c)$$

$$+ \frac{V_s}{1+(j\omega\tau_c)^2} \left[\underbrace{\cos \omega t + (\omega\tau_c) \sin(\omega t)}_{\text{[redacted]}} \right]$$

$$\cos(\omega t + \beta) \quad -\tan^{-1}(\omega\tau_c)$$

$$\frac{1}{1+j\omega\tau_c} = A \exp(j\phi) \quad \sqrt{1+(\omega\tau_c)^2} = \frac{\exp(-j\tan^{-1}(\omega\tau_c))}{\text{[redacted]}}$$

$A \exp(j\omega t)$

$$\frac{V_s \exp(j\omega t)}{1 + j\omega CR} = V_s \cdot \frac{1}{\sqrt{1 + (\omega CR)^2}} \cdot \exp(-j \tan^{-1}(\omega CR)) \cdot \exp(j\omega t)$$

$$\frac{V_s}{\sqrt{1 + (\omega CR)^2}} \cdot \cos(\omega t - \tan^{-1}(\omega CR))$$

