

Lecture 24


$$+ V_R -$$



$$RC \frac{dV_c}{dt} + V_c = V_s$$


$$RC \frac{dV_c}{dt} + V_c = RC \cdot \frac{dV_s}{dt}$$

Characteristic of the ckt.

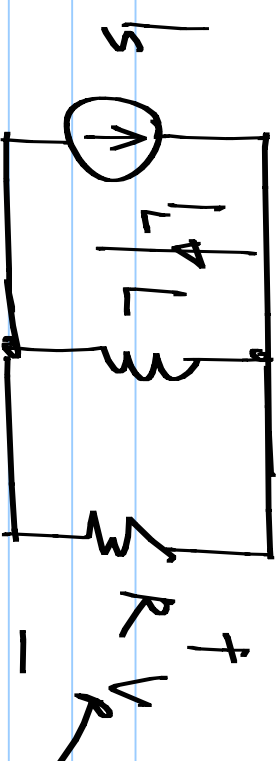


$$\frac{L}{R} \frac{dI}{dt} + I = I_s$$

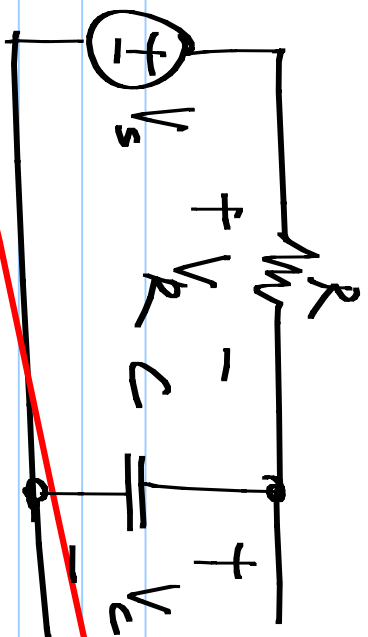
$$\frac{L}{R} \frac{dI}{dt} + I = L \cdot \frac{dI_s}{dt}$$




$$RC \frac{dV_c}{dt} + V_c = V_s$$

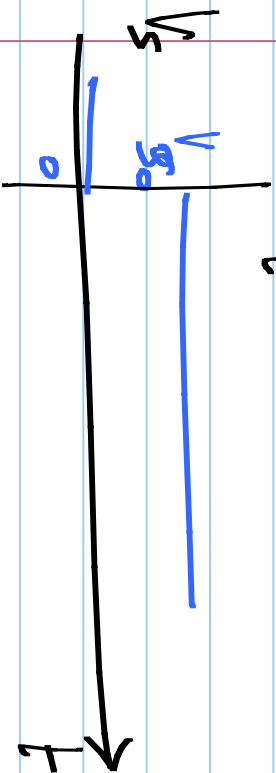

Time constant τ

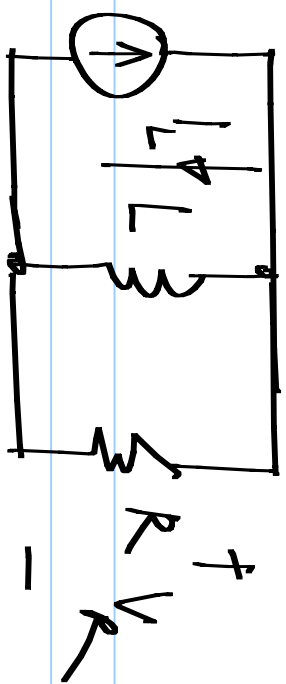

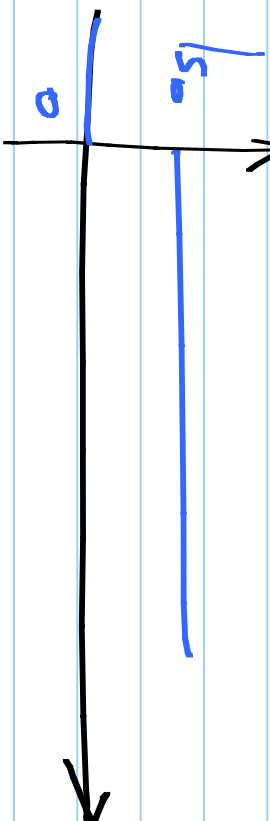
$$\frac{L}{R} \frac{dI_L}{dt} + I_L = I_s$$





$$V_c(t) = V_{s_0} + (V_c(0) - V_{s_0}) \exp\left(-\frac{t}{RC}\right)$$
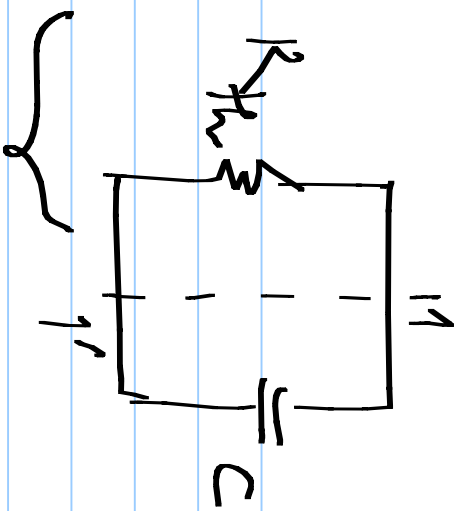
$$I_L(t) = I_{s_0} + (I_L(0) - I_{s_0}) \exp\left(-\frac{t}{L/R}\right)$$



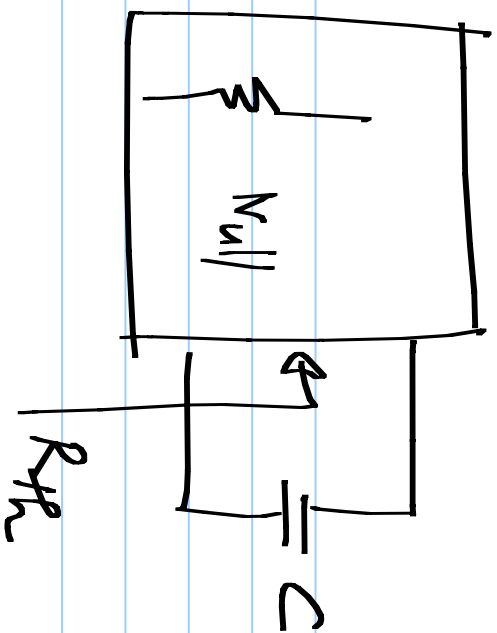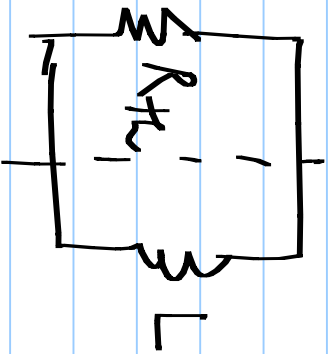
Thevenin eq.
resistance
looking into 1-1'



Determining
time
constants

$$\tau = R_{Th} \cdot C$$

$$\tau = \frac{L}{R_{Th}}$$

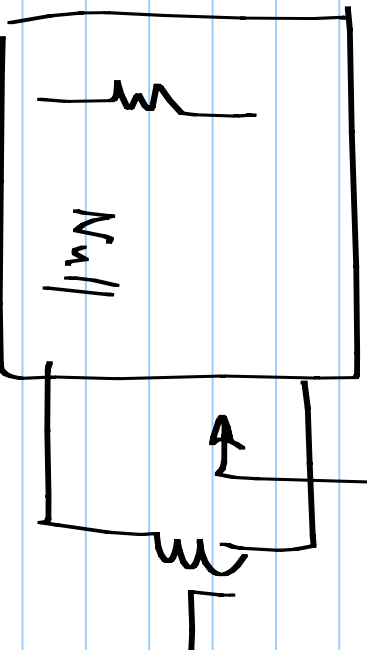

$$V_L(t) = V_{s_0} + \underbrace{(V_L(0) - V_s)}_{\text{Transient}} \exp\left(-\frac{t}{\tau}\right)$$


Steady state

Transient


$$V_R(t) = 0 + V_R(0) \cdot \exp\left(-\frac{t}{\tau}\right)$$

$$V_s - V_L(0)$$

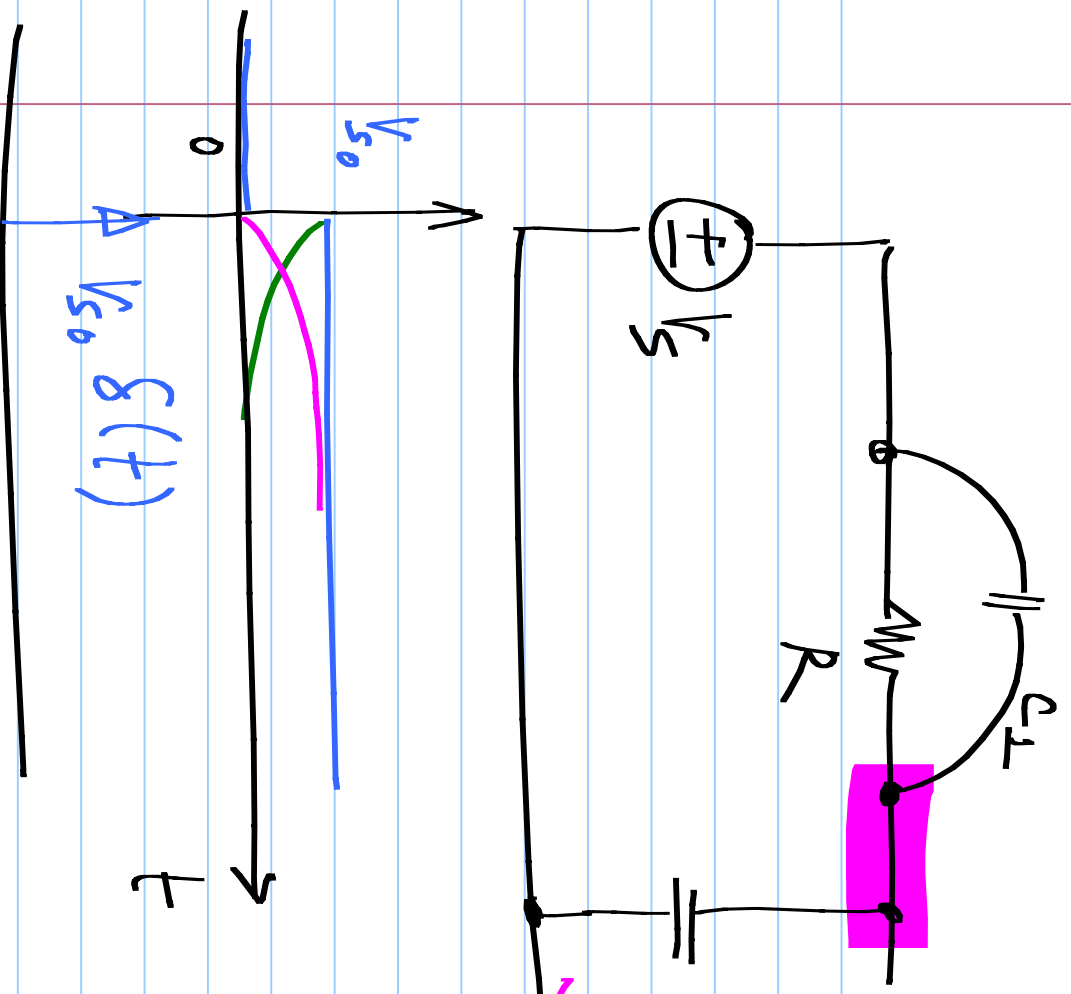
$$\underbrace{V_{s_0} \left(1 - \exp\left(-\frac{t}{\tau}\right)\right)}_{\text{Steady state}} + \underbrace{V_L(0) \exp\left(-\frac{t}{\tau}\right)}_{\text{Transient}}$$



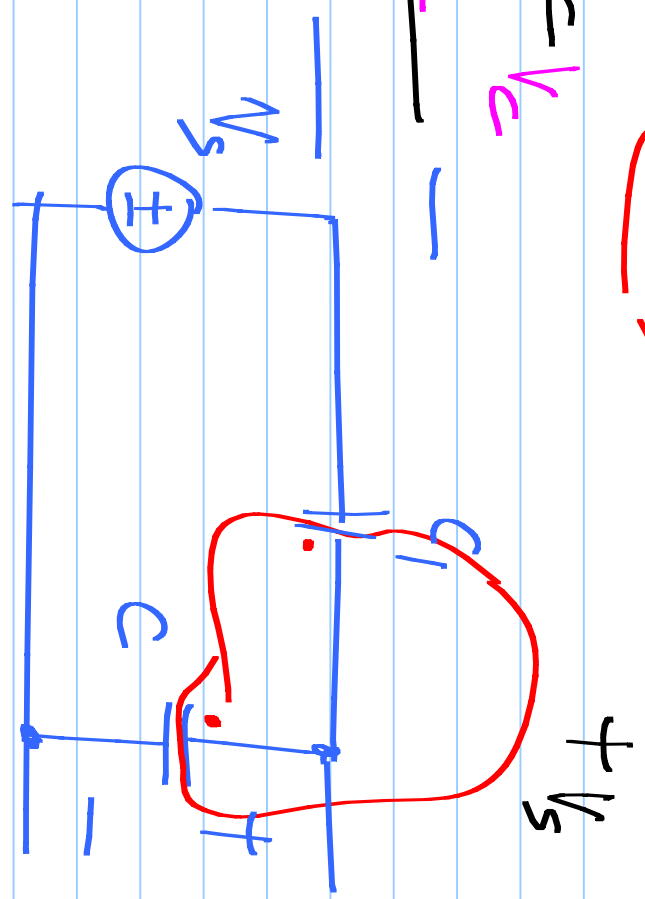
$$R(C + C_1) \frac{dV_c}{dt} + V_c = RC_1 \frac{dV_s}{dt}$$





$$C \cdot V_c + C_1(V_c - V_s) = 0$$

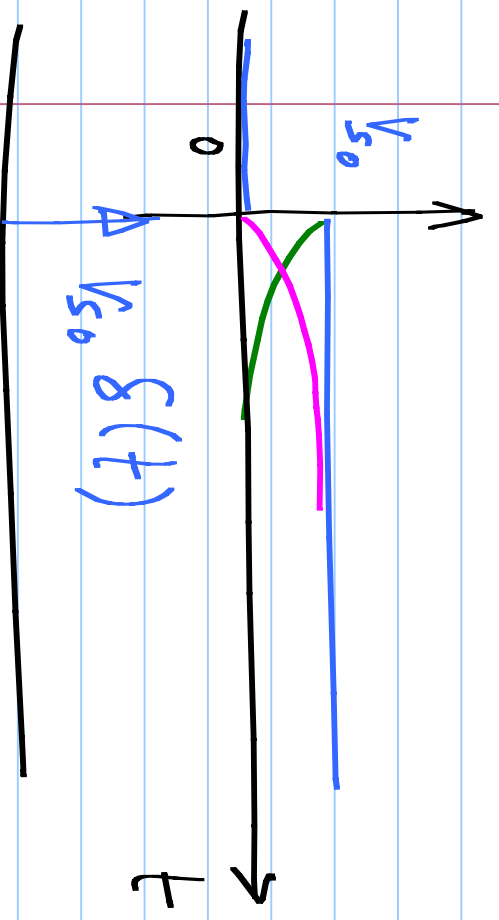

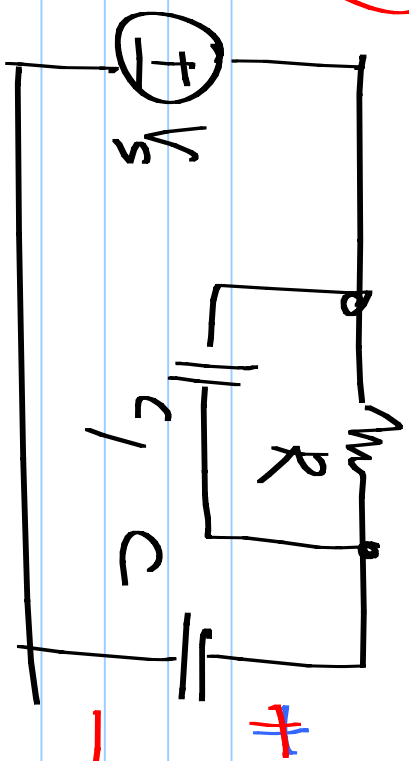

exponential w/ time constant = RC

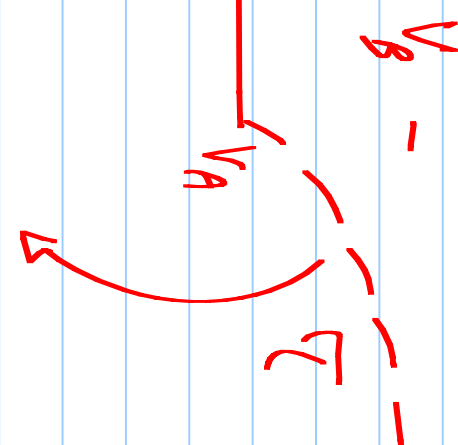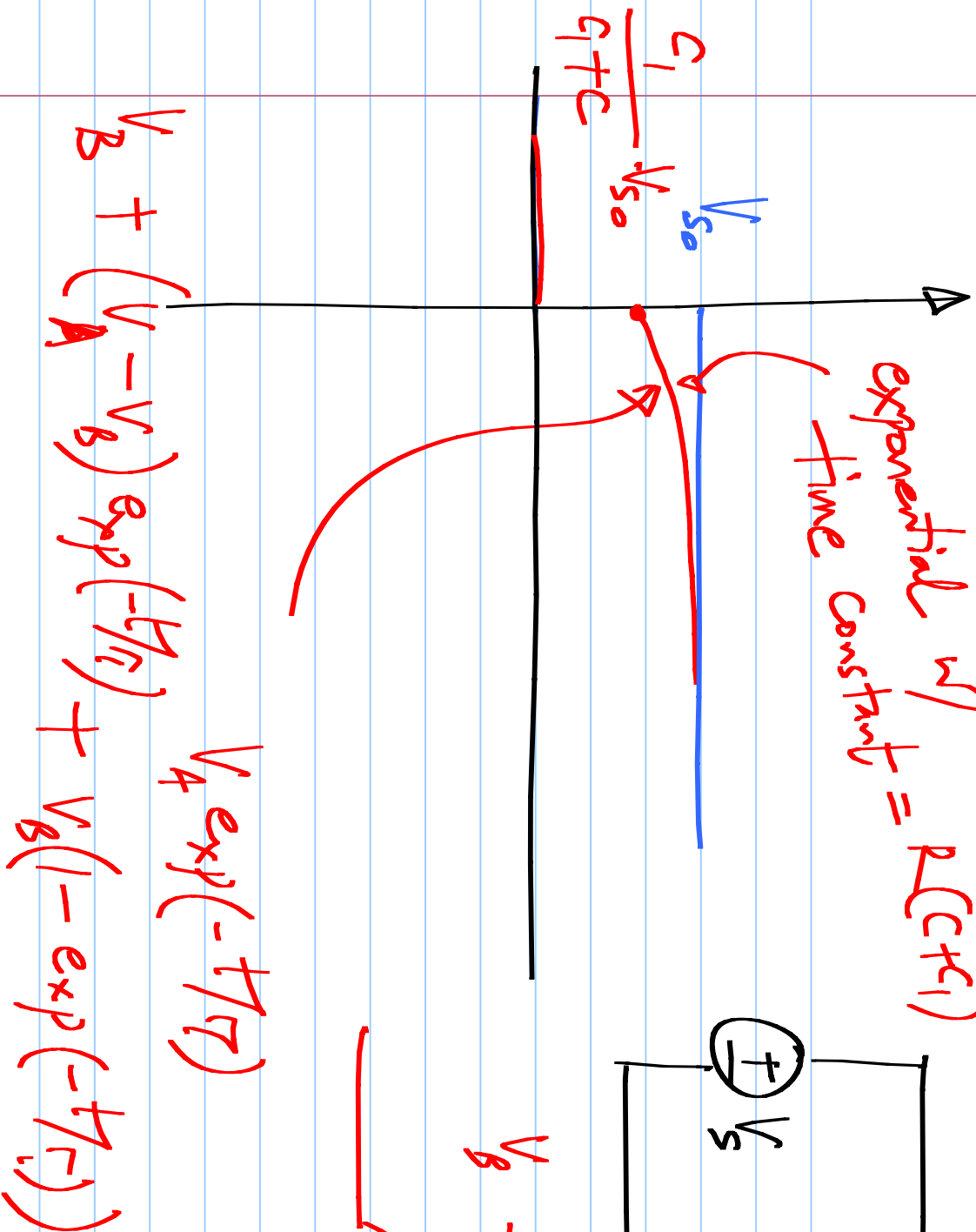

$$V_B + (V_A - V_B) \exp(-t/RC)$$

$$V_A \exp(-t/RC) + V_B(1 - \exp(-t/RC))$$

$$\frac{C_1}{C_1 + C} V_{s0}$$