
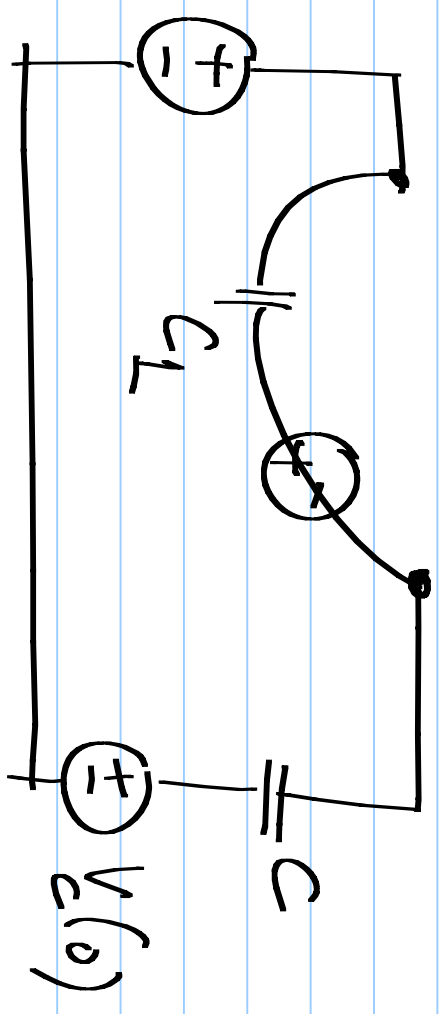


Lecture 25

First order circuit: Single effective 'capacitor' or single effective 'inductor' } Null'd circuit

Step response:

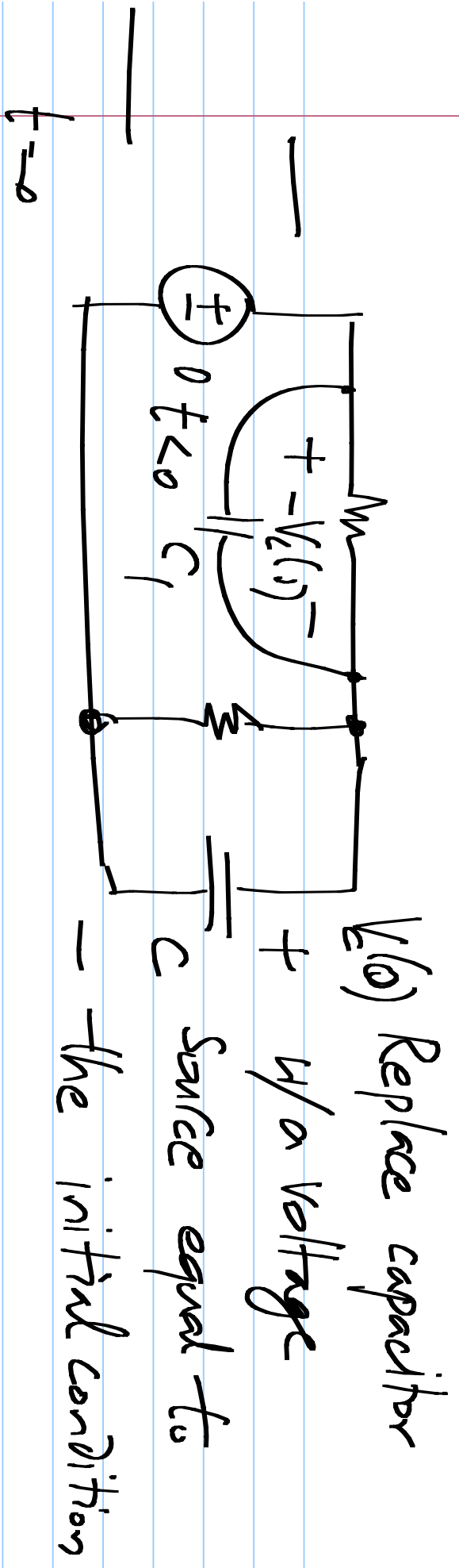- * Discontinuity at the instant of step
- * Exponential with a time constant τ
- * Steady state



Step response:

- * Discontinuity at the instant of step
- * Exponential with a time constant τ
- * Steady state

* Capacitors replaced by voltage sources (initial cond.)

* Capacitor - voltage source loop

Bq. resistance

Capacitors open.

$$V(t) = V(0^+) \exp(-t/\tau) + V(\infty) (1 - \exp(-t/\tau))$$

Response

$$t_0 = \text{exp(j}\omega t) + \text{exp(j}\omega t) \left[\begin{array}{l} \text{frequency} \\ \text{circuit} \end{array} \right]$$

die out with time


Steady state response

Sinusoidal steady state analysis

$$v_c(t) = \left(\right) + \frac{\text{exp(j}\omega t)}{1 + j\omega RC}$$

$$i_6 + v_6 -$$

exp(j\omega t) :

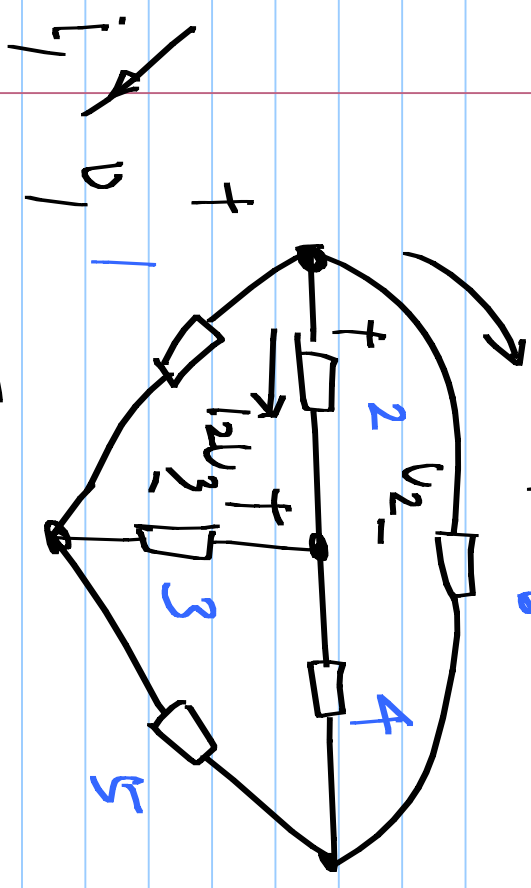

Every branch voltage & current will have a

Steady state part

$$\exp(j\omega t) \cdot [\quad]$$

$$v_1 = \underline{\underline{V_1}} \exp(j\omega t) \quad \underline{\underline{V_1}} - \underline{\underline{V_2}} - \underline{\underline{V_3}} = 0$$

$$v_2 = \underline{\underline{V_2}} \cdot \exp(j\omega t)$$

$$v_3 = \underline{\underline{V_3}} \cdot \exp(j\omega t)$$

Phasors

$$\underline{\underline{I_1}} + \underline{\underline{I_2}} + \underline{\underline{I_6}} = 0$$

$$\bar{V}_y = 1 + j2$$

$$V_y / = \text{Re} \left[(1 + j2) \exp(j\omega t) \right]$$

Steady state

$$V_s = V_p \cos(\omega t + \phi)$$

$$= \text{Re} \left[V_p \cdot \exp(j\phi) \exp(j\omega t) \right]$$

$$\oplus V_p \cos(\omega t + \phi)$$

$$\oplus V_p \cos(\omega t + \theta)$$

All sources should be at the same freq. ω

$$\oplus V_p \exp(j\omega t) \exp(j\omega t)$$

$$\oplus V_p \exp(j\omega t) \cdot \exp(j\omega t)$$

implicit

$$V_p \cos(\omega t + \phi)$$

$$V_p \exp(j\phi) \exp(j\omega t)$$

A circuit diagram showing a resistor R with a voltage V across it. The voltage is labeled as $V_p \cos(\omega t + \phi)$.

$$\frac{V_p \exp(j\phi)}{R} \exp(j\omega t)$$

A circuit diagram showing a resistor R with a voltage V_R across it. The voltage is labeled as V_R .

$$\frac{V_p}{R} = R$$

$$V_p \cos(\omega t + \phi)$$

$$V_p \exp(j\phi) \exp(j\omega t)$$

$$-j\omega C V_p \sin(\omega t + \phi) = j\omega C V_p \exp(j\phi) \exp(j\omega t)$$

$$V_c$$

$$\frac{V_c}{j\omega C} = \frac{1}{j\omega C}$$

$$V_p \cos(\omega t + \phi)$$

$$V_p \exp(j\phi) \exp(j\omega t)$$

$$\int \frac{V_p}{\omega L} \sin(\omega t + \phi)$$

$$-j \frac{V_p}{\omega L} \exp(j\phi) \exp(j\omega t)$$

$$\frac{V_L}{j\omega L} = j\omega L$$

