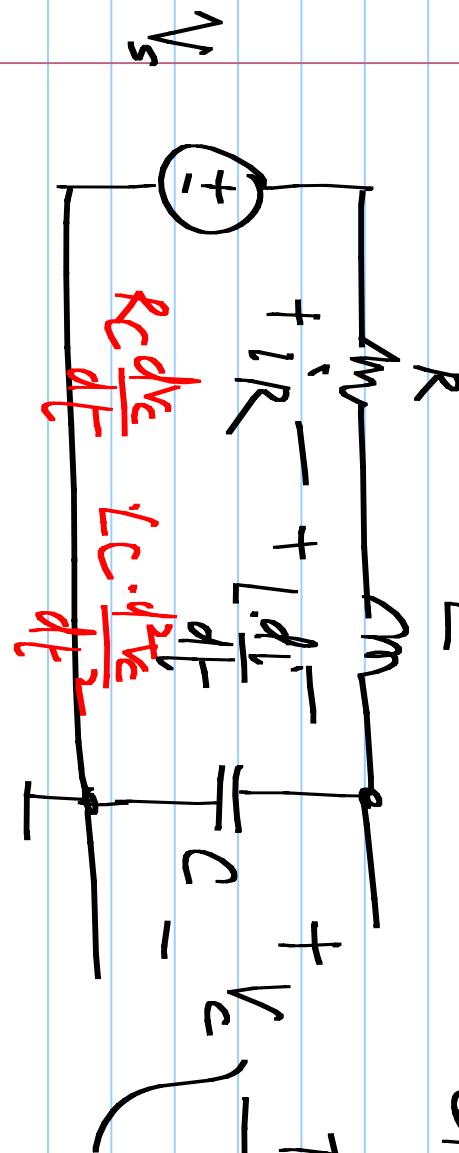


Lecture 26

Differential equation for this circuit (V_c)



$$LC \frac{d^2V_c}{dt^2} + RC \frac{dV_c}{dt} + V_c = V_s(t)$$

Homogeneous equation:

$$\exp(p \cdot t)$$

$$LC \frac{d^2V_c}{dt^2} + RC \frac{dV_c}{dt} + V_c = 0$$

$$LC \cdot p^2 + RC \cdot p + 1 = 0$$

$$RC \cdot p \cdot \exp(pt) + \exp(pt) = 0$$

Two values p_1, p_2

$$p = -\frac{1}{RC}$$

$$k_1 \cdot \exp(p_1 t) + k_2 \cdot \exp(p_2 t)$$

Characteristic equation

$$LC \cdot p^2 + RC \cdot p + 1 = 0$$

$$p_{1,2} = \frac{-RC \pm \sqrt{R^2 C^2 - 4LC}}{2LC}$$

Two values p_1, p_2

Real, distinct roots:

$$= -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Solution: $k_1 \exp(p_1 t) + k_2 \exp(p_2 t)$

$$\left(\frac{R}{2L}\right)^2 - \frac{1}{LC} > 0$$

Identical: $\frac{(k_1 + k_2 t) \exp(p_1 t)}{r_2 \sqrt{3}}$

$$\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$$

$$\frac{R}{2} \sqrt{\frac{C}{L}} > 1 \quad ; \quad \frac{1}{R} \sqrt{\frac{L}{C}} < \frac{1}{2}$$

$$\begin{array}{c}
 \boxed{\frac{dy_1}{dt} + y_1 = u} \quad u \\
 \downarrow \\
 \boxed{\frac{dy_2}{dt} + y_2 = v} \quad v \\
 \downarrow \\
 \boxed{\frac{dy}{dt} + y = \bar{v}} \quad \bar{v} \\
 \downarrow \\
 \boxed{\frac{dy_1}{dt} + y_1 = u} \quad u \\
 \downarrow \\
 \boxed{\frac{dy_2}{dt} + y_2 = v} \quad v \\
 \downarrow \\
 \boxed{\frac{dy}{dt} + y = \bar{v}} \quad \bar{v}
 \end{array}$$

$\exp(p_1 t)$ $\exp(p_2 t)$ $\exp(\bar{p} t)$


Complex conjugate roots:

$$p_{1,2} = -\frac{R}{2L} \pm j\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$$v(t) = k_1 \exp(p_1 t) + k_2 \exp(p_2 t) = p_r \pm j p_i$$

$$= K_0 \exp(prt) \left[\exp(j\phi_k) \cdot \exp(jp_i t) \quad k_1 = K_0 \cdot \exp(j\phi_k) \right. \\ \left. + \exp(-j\phi_k) \exp(-jp_i t) \right] \quad k_2 = k_1^* = K_0 \exp(-j\phi_k)$$
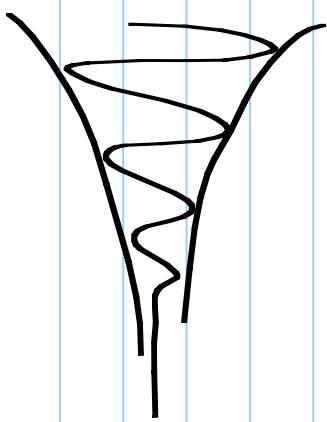
$$= 2 \cdot K_0 \cdot \exp(prt) \cdot \cos(p_i t + \phi_k)$$



Natural response:

$\begin{cases} \text{Damping} \\ \text{factor} \end{cases}$

$$k_1 \exp(p_1 t) + k_2 \exp(p_2 t)$$

• overdamped • real, distinct, $\zeta > 1$

$$(k_1 + k_2 t) \exp(p_1 t)$$

• critically • identical $\zeta = 1$
damped

$$2k_0 \exp(p_1 t) \cos(p_1 t + \phi_k)$$

• under damped

Q : Quality factor

$$[C \cdot p^2 + R C \cdot p +] = 0$$



real, distinct $Q < \frac{1}{2}$

$$\omega_n^2 \cdot p^2 + 2 \zeta \omega_n \cdot p + 1 = 0$$

identical $Q = \frac{1}{2}$

$$\omega_n^2 \cdot p^2 + \frac{\omega_n \cdot p}{\zeta} + 1 = 0$$

complex conj. $Q > \frac{1}{2}$

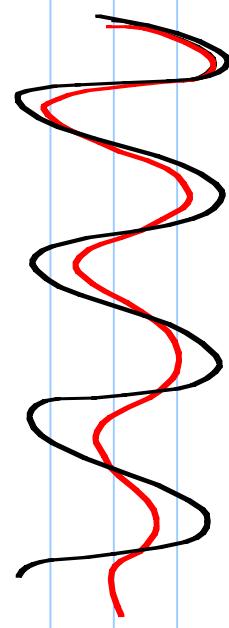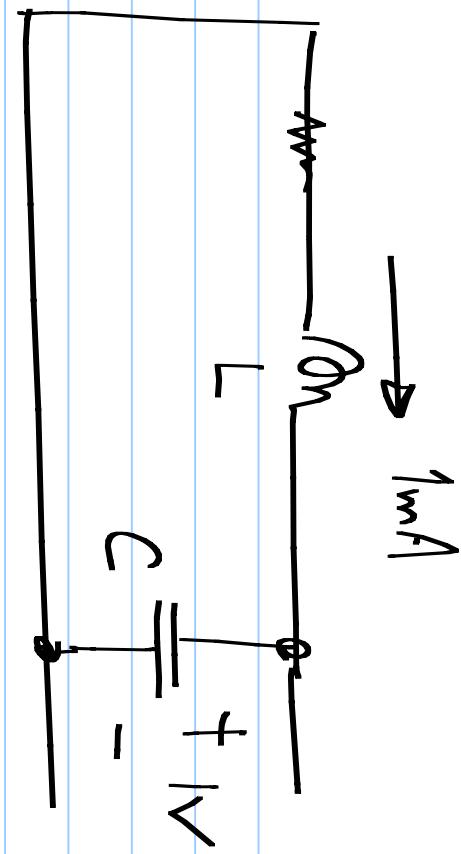

(Natural)
(Free)

Total solution = Transient response + Steady state response

$$k_1 \exp(p_1 t) + k_2 \exp(p_2 t)$$

OR

$$(k_1 + k_2 t) \exp(p_1 t)$$

$$2 \cdot k_0 \exp(p_1 t) \cos(p_1 t + \phi_k)$$

Input:

Constant

$$\exp(st)$$

Output:

Constant
 $() \exp(st)$